

# Module-4 : Transmission Lines

(Chapter-7)

Our discussion on last chapter was essentially on wave propagation on unbounded media, media of infinite extent. Such wave propagation is said to be unguided on that the uniform plane wave exists through out all space, and EM energy associated with the wave spreads over a wide area. This type of wave propagation is used on radio or TV broadcasting, where the information being transmitted is meant for everyone who may be interested. Such means of wave propagation will not help in a situation like telephone conversation, where the information is received privately by one person.

Another means of transmitting power or information is by guided structures. Guided structures serve to guide the propagation of energy from source to the load. Typical example of such structures are transmission lines and wave guides.

Transmission lines are commonly used on power distribution (at low frequencies) and on communications (at high frequencies). A transmission line basically consists of two or more parallel conductors used to connect a source to a load.

The source may be a hydroelectric generator, a transmitter, or an oscillator; a load may be a factory, an antenna or an oscilloscope. Typical transmission lines include coaxial cable, a two-wire line, a parallel-plate or planar line, a wire above the conducting plane, and a microstrip line. These lines are portrayed in fig 7.1.

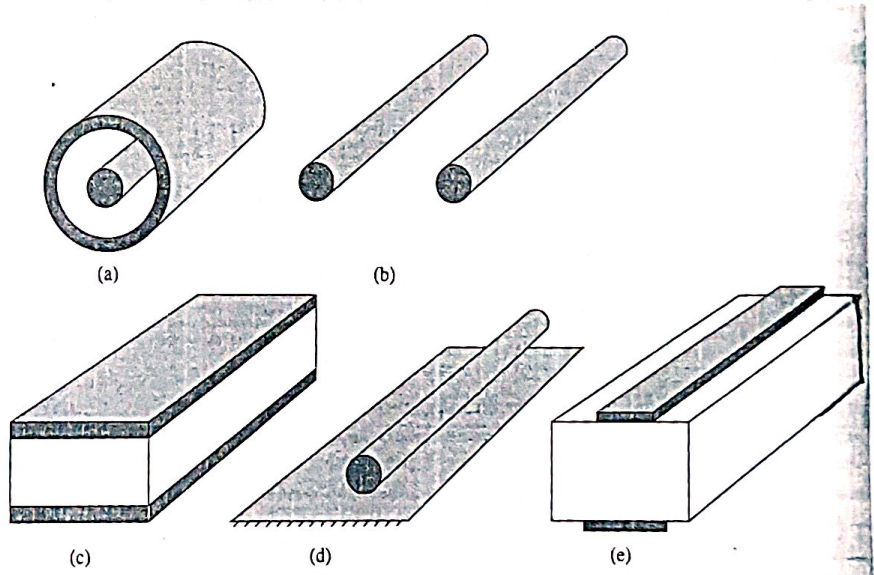


Figure 7.1 Typical transmission lines in cross-sectional view: (a) coaxial line, (b) two-wire line, (c) planar line, (d) wire above conducting plane, (e) microstrip line.

Note that each of these lines consists of two conductors in parallel. Coaxial cables are routinely used in electrical laboratories and in connecting TV sets to antennas. Microstrip lines are particularly important in integrated circuits, where metallic strips connecting electronic elements are deposited on dielectric substrates.

Transmission line problems are usually solved by means of EM field theory and electric circuit theory. In this chapter, we use circuit



theory because it is easier to deal with mathematically.

Transmission Line Parameters

It is customary and convenient to describe a transmission line in terms of its line parameters, which are its resistance per unit length (R), inductance per unit length (L), conductance per unit length (G), and capacitance per unit length (C).

Each of the lines shown in figure 7.1 has specific formulas for finding R, L, G, and C. For coaxial, two-wire, and planar lines, the formulas for calculating R, L, G, and C are provided in Table 7.1. The dimensions of lines are shown in figure 7.2. It should be noted that

Table 7.1 Distributed Line Parameters at High Frequencies\*

Parameters	Coaxial Line	Two-Wire Line	Planar Line
R (Ω/m)	$\frac{1}{2\pi\delta\sigma_c} \left[ \frac{1}{a} + \frac{1}{b} \right]$ ( $\delta \ll a, c - b$ )	$\frac{1}{\pi a \delta \sigma_c}$ ( $\delta \ll a$ )	$\frac{2}{w \delta \sigma_c}$ ( $\delta \ll t$ )
L (H/m)	$\frac{\mu}{2\pi} \ln \frac{b}{a}$	$\frac{\mu}{\pi} \cosh^{-1} \frac{d}{2a}$	$\frac{\mu d}{w}$
G (S/m)	$\frac{2\pi\sigma}{\ln \frac{b}{a}}$	$\frac{\pi\sigma}{\cosh^{-1} \frac{d}{2a}}$	$\frac{\sigma w}{d}$
C (F/m)	$\frac{2\pi\epsilon}{\ln \frac{b}{a}}$	$\frac{\pi\epsilon}{\cosh^{-1} \frac{d}{2a}}$	$\frac{\epsilon w}{d}$ ( $w \gg d$ )

\* $\delta = \frac{1}{\sqrt{\pi f \mu_c \sigma_c}}$  = skin depth of the conductor;  $\cosh^{-1} \frac{d}{2a} = \ln \frac{d}{a}$  if  $\left[ \frac{d}{2a} \right]^2 \gg 1$ .

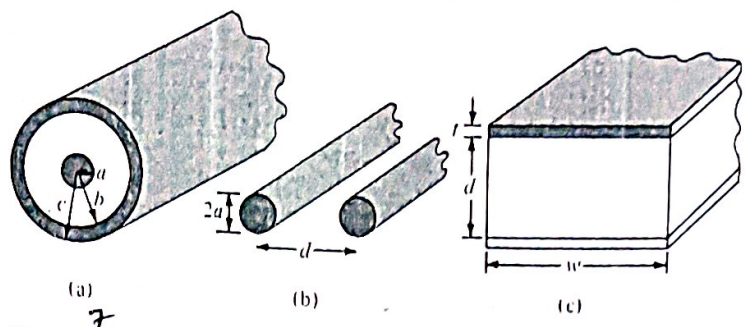


Figure 7.2 Common transmission lines: (a) coaxial line, (b) two-wire line, (c) planar line.

1) The line ~~para~~ parameters  $R, L, G,$  and  $C$  are not discrete or lumped. Rather, they are distributed as shown in figure 7.3. By this we mean that parameters are uniformly distributed along the entire length of the line.

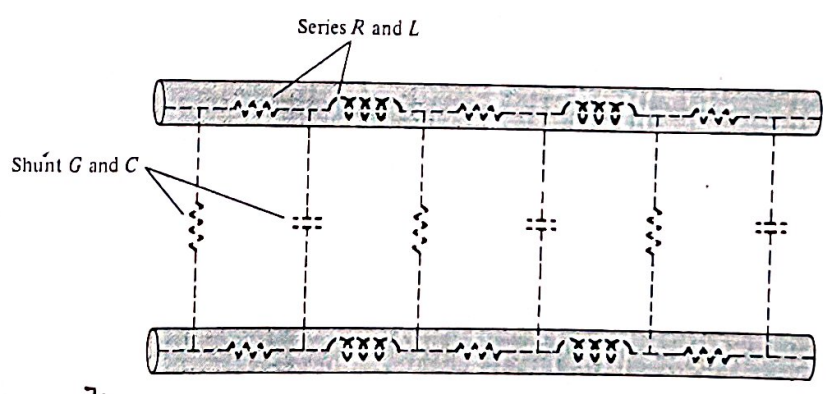


Figure 7.3 Distributed parameters of a two-conductor transmission line.

2) For each line, the conductors are characterized by  $\sigma_c, \mu_c, \epsilon_c = \epsilon_0$ , and the homogeneous dielectric separating the conductors is characterized by  $\sigma, \mu, \epsilon$ .

3)  $G \neq \frac{1}{R}$ ;  $R$  is the ac resistance per



Unit length of the conductors comprising the line, and  $G$  is the conductance per unit length due to the dielectric medium separating the conductors.

4. The value of  $L$  as shown in Table 7.1 is the external inductance per unit length.

The effects of internal inductance ( $= L_{in}$ ) are negligible at high frequencies at which most communication systems operate.

5. For each line, (Table 7.1)

$$LC = \mu\epsilon \quad \text{and} \quad \frac{G}{C} = \frac{\sigma}{\epsilon}$$

$$\begin{aligned} \because V &= I \cdot X_L \\ \Rightarrow X_L &= \frac{V}{I} = R \\ \Rightarrow \omega L &= R \\ \Rightarrow L &= \frac{R}{\omega} \\ \Rightarrow L &= \frac{R}{2\pi f} \end{aligned}$$

Let's consider how an EM wave propagates through a two-conductor transmission line. For ex: consider the coaxial line connecting the generator or source to the load as in figure 7.4 (a). When switch  $S$  is closed, the inner conductor is made +ve w.r. to outer one so that the  $\vec{E}$  field is radially outward as in figure 7.4(b). According to Ampere's law, the  $\vec{H}$  field encircles the current carrying conductor as in figure 7.4(b). The Poynting vector ( $\vec{E} \times \vec{H}$ ) points along the transmission line.

Thus, Closing the switch simply establishes a disturbance, which appears as a transverse electromagnetic (TEM) wave propagating along the line. This wave is a non uniform plane wave and by means of it power is transmitted through the line.


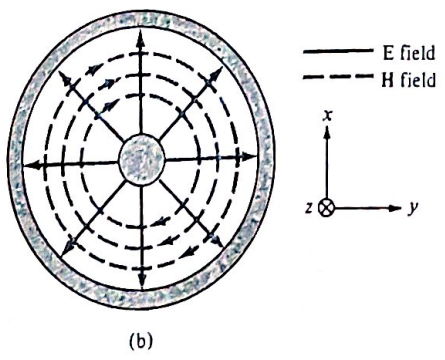


Figure 9.4 (a) Coaxial line connecting the generator to the load; (b) E and H fields on the coaxial line.

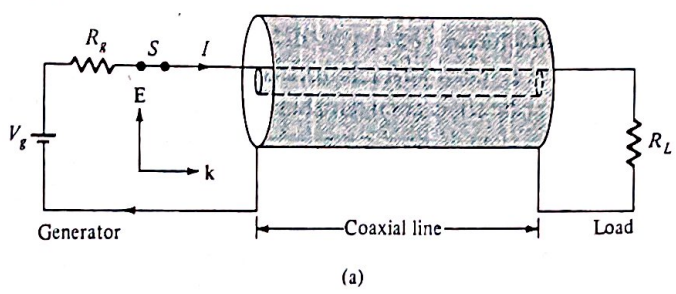


↓ The <sup>→ (Compact)</sup> Lumped-element Circuit model for a transmission line / All theory models of T.L

---

The key difference between circuit theory and transmission line theory is electrical size. Circuit analysis assumes that the physical dimension of a n/w are much smaller than electrical wavelength ( $\lambda$ ), while transmission line may be a considerable fraction of a wavelength  $\lambda$ .


many wavelengths, in size. Thus a transmission line is a distributed-parameter n/w, where voltages and current can vary in magnitude & phase over its length.

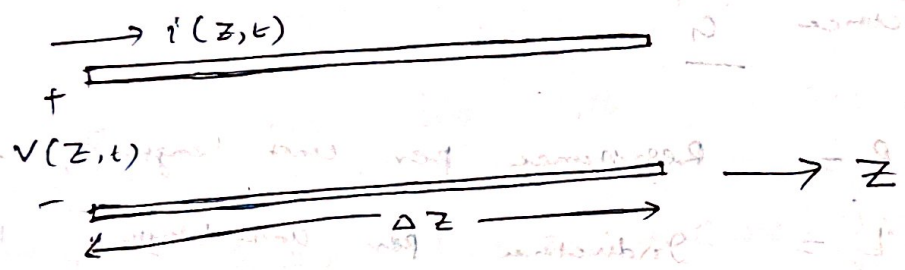As shown in fig 3 (a), a transmission line is often schematically represented as a two-wire line. The piece of line of infinitesimal length  $\Delta z$  of fig 3 (a) can be modeled as a lumped-element circuit, as shown in fig 3 (b), where  $R, L, G, C$  are per unit length quantities. [distributed parameters]



(a)

~~fig 3 (a)~~

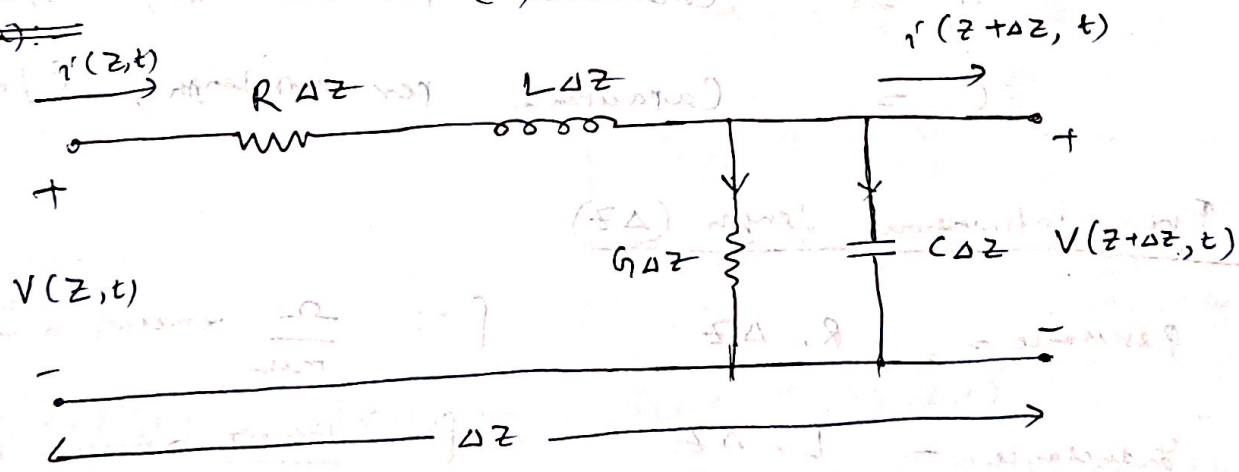

(b)

fig 3 :- Voltage and current definitions and equivalent circuit for an incremental length of transmission line. (a) Voltage and current definitions (b) Lumped-element equivalent circuit.



Since each conductor of the transmission line has finite length, diameter and finite area of cross section, they have resistance ( $R$ ) and self inductance ( $L$ ). As both the transmission lines are separated by dielectric with finite dielectric constant, they have a capacitance ( $C$ ) between the two conductors.

Due to the presence of dielectric, there will be a leakage current through it which is represented by conductance ( $G$ ).

- $\therefore R =$  Resistance per unit length,  $\Omega/\text{meter}$
- $L =$  Inductance per unit length,  $H/\text{meter}$
- $G =$  Conductance per unit length,  $S/\text{meter}$
- $C =$  Capacitance per unit length,  $F/\text{meter}$

For infinitesimal length ( $\Delta z$ )

Resistance =  $R \cdot \Delta z$  [  $\because \frac{\Omega}{\text{meter}} \times \text{meter} = \Omega$  ]

Inductance =  $L \cdot \Delta z$  [  $\frac{\text{Henry}}{\text{meter}} \times \text{meter} = \text{Henry}$  ]

Similarly

Conductance =  $G \cdot \Delta z$

Capacitance =  $C \cdot \Delta z$

Applying KVL in fig 3(b), we have

$$V(z,t) - i(z,t) \cdot R \Delta z - L \Delta z \cdot \frac{\partial i(z,t)}{\partial t} - V(z+\Delta z,t) = 0$$

$$\Rightarrow V(z+\Delta z, t) - V(z, t) = - \left[ i'(z, t) \cdot R \Delta z + L \Delta z \cdot \frac{\partial i(z, t)}{\partial t} \right]$$

Dividing both the sides by  $\Delta z$ , ~~we have~~  
and taking the limit  $\Delta z \rightarrow 0$ , we have

$$\Rightarrow \lim_{\Delta z \rightarrow 0} \frac{V(z+\Delta z, t) - V(z, t)}{\Delta z} = - \left[ i'(z, t) \cdot R + L \frac{\partial i(z, t)}{\partial t} \right]$$

$$\Rightarrow \boxed{\frac{\partial V(z, t)}{\partial z} = - R \cdot i(z, t) - L \frac{\partial i(z, t)}{\partial t}} \quad (1)$$

$$\left[ \because f'(x) = \lim_{h \rightarrow 0} \frac{f(x+h) - f(x)}{h} \right]$$

Applying KCL in fig 3(b), we have

$$i(z, t) = G \Delta z \cdot V(z+\Delta z, t) + C \Delta z \cdot \frac{\partial V(z+\Delta z, t)}{\partial t} + i(z+\Delta z, t)$$

$$\left. \begin{aligned} \therefore I_1 &= \frac{V}{R} = V \cdot G \\ I_2 &= C \frac{dV}{dt} \quad \left( \because \alpha = C V \right. \\ &\quad \left. I_2 = C V \right. \\ &\quad \left. \Rightarrow I_2 = C \frac{dV}{dt} \right) \end{aligned} \right\}$$

$$\Rightarrow i(z+\Delta z, t) - i(z, t) = - G \Delta z \cdot V(z+\Delta z, t) - C \Delta z \cdot \frac{\partial V(z+\Delta z, t)}{\partial t}$$

Dividing both the sides by  $\Delta z$  and taking the limit  $\Delta z \rightarrow 0$ , we have

$$\Rightarrow \lim_{\Delta z \rightarrow 0} \frac{i(z+\Delta z, t) - i(z, t)}{\Delta z} = - G V(z, t) - C \frac{\partial V(z, t)}{\partial t}$$

$$\Rightarrow \boxed{\frac{\partial i(z, t)}{\partial z} = - G V(z, t) - C \frac{\partial V(z, t)}{\partial t}} \quad (2)$$



Equation (1) & (2) are the time-domain form

of transmission line or telegrapher, eq<sup>n</sup> 8.

Instantaneous ~~from~~ <sup>line voltage can be expressed as</sup>  $v(z,t) = \text{Re} [V_s(z) \cdot e^{j\omega t}]$  (3)

$$= \text{Re} [V_s(z) \cdot (\cos \omega t + j \sin \omega t)]$$

$$v(z,t) = V_s(z) \cdot \cos \omega t \quad \text{--- (3)}$$

Similarly,  $i(z,t) = I_s(z) \cdot \cos \omega t$  (4)

where  $V_s(z)$  &  $I_s(z)$  are phasor form whereas original source.

Putting eq<sup>n</sup> (3) & (4) in eq<sup>n</sup> (1), we have

$$\frac{\partial}{\partial z} V_s(z) \cdot \cos \omega t = -R \cdot I_s(z) \cdot \cos \omega t - L \cdot \frac{\partial}{\partial t} I_s(z) \cdot \cos \omega t$$

Taking  $\frac{\partial}{\partial t} = j\omega$  as mathematical operator, we have

$$\Rightarrow \frac{\partial}{\partial z} V_s(z) \cdot \cos \omega t = -R I_s(z) \cdot \cos \omega t - L \cdot (j\omega) \cdot I_s(z) \cdot \cos \omega t$$

Ans:-  $x = A \cdot e^{j\omega t}$

 $\frac{dx}{dt} = A \cdot e^{j\omega t} \cdot j\omega$ 
 $\frac{\partial x}{\partial t} = (j\omega) \cdot x$ 

$\therefore \frac{\partial}{\partial t} = j\omega$

$$\Rightarrow \frac{\partial}{\partial z} V_s(z) = -(R + j\omega L) I_s(z) \quad \text{--- (5)}$$

Similarly

Putting eq<sup>n</sup> (3) & (4) in eq<sup>n</sup> (2), we have

$$\frac{\partial}{\partial z} I_s(z) \cos \omega t = -G V_s(z) \cos \omega t - C \frac{\partial}{\partial t} (V_s(z) \cos \omega t)$$

$$\Rightarrow \frac{\partial}{\partial z} I_s(z) \cos \omega t = -G V_s(z) \cos \omega t - C (\omega) V_s(z) \cos \omega t$$

( $\because \frac{\partial}{\partial t} = \omega$ )

$$\Rightarrow \frac{\partial}{\partial z} I_s(z) = -(G + \omega C) V_s(z) \quad \text{--- (6)}$$

\* Note: - Eq<sup>n</sup> (5) & (6) are also called telegrapher eq<sup>n</sup>. (For sinusoidal steady-state condition, with cosine-based phasors)

Wave Propagation on a transmission line

The eq<sup>n</sup>s (5) & (6) can be solved simultaneously to give wave equations for  $V_s(z)$  &  $I_s(z)$ .

Differentiating eq<sup>n</sup> (5) w.r. to  $z$ , we have

$$\frac{\partial^2}{\partial z^2} V_s(z) = -(R + \omega L) \frac{\partial}{\partial z} I_s(z) \quad \text{--- (7)}$$

Now, putting eq<sup>n</sup> (6) in eq<sup>n</sup> (7), we have

$$\frac{\partial^2}{\partial z^2} V_s(z) = -(R + \omega L) [-(G + \omega C) V_s(z)]$$

$$\therefore \frac{\partial^2}{\partial z^2} V_s(z) - (R + \omega L)(G + \omega C) V_s(z) = 0$$

Let  $\gamma = \sqrt{(R + \omega L)(G + \omega C)}$  = <sup>Complex</sup> Propagation <sub>constant</sub>

$$\therefore \frac{\partial^2}{\partial z^2} V_s(z) - \gamma^2 V_s(z) = 0 \quad \text{--- (8)}$$



Similarly,

Differentiating eq<sup>n</sup> 6, w.r.t to  $z$ , we have

$$\frac{\partial^2}{\partial z^2} I_s(z) = - (G + j\omega C) \cdot \frac{\partial}{\partial z} V_s(z) \quad \text{--- (9)}$$

Putting eq<sup>n</sup> (5), in eq<sup>n</sup> (9), we have

$$\frac{\partial^2 I_s(z)}{\partial z^2} = - (G + j\omega C) \cdot [-(R + j\omega L) I_s(z)]$$

$$\Rightarrow \frac{\partial^2}{\partial z^2} I_s(z) - (R + j\omega L)(G + j\omega C) I_s(z) = 0$$

$$\Rightarrow \frac{\partial^2 I_s(z)}{\partial z^2} \quad \gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \quad \begin{array}{l} \text{Complex} \\ \text{Propagation} \\ \text{Constant} \end{array}$$

$$\Rightarrow \boxed{\frac{\partial^2 I_s(z)}{\partial z^2} - \gamma^2 I_s(z) = 0} \quad \text{--- (10)}$$

$\therefore$  Eq<sup>n</sup> (8) & (10) are ~~called the~~ similar to electro & magnetic wave equations, called in final form of transmission line eq<sup>n</sup>.

$$\gamma = \alpha + j\beta, \quad \text{where } \alpha = \text{Attenuation Constant} \\ \beta = \text{Phase Propagation Constant}$$

### Solution of transmission line equations

If the 2<sup>nd</sup> order differential eq<sup>n</sup> is

$$\frac{d^2 y}{dx^2} - k^2 y = 0$$

The sol<sup>n</sup> of it is of the form

$$y = C_1 e^{-kx} + C_2 e^{kx} \quad \text{where } C_1 \text{ \& } C_2 \text{ are constants.}$$

~~Sol~~  $S_0$  Solution to differential eq<sup>n</sup> (8) & (10)

are in the form,

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (11)$$

$$I_s(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (12)$$

Here,  $C_1 = V_0^+ \text{ or } I_0^+$

$C_2 = V_0^- \text{ or } I_0^-$

$k = \gamma$

and  $V_0^+$  &  $I_0^+$  indicate complex amplitude in the +ve  $z$ -direction,  $V_0^-$  &  $I_0^-$  signify complex amplitude in -ve  $z$ -direction.

From eq<sup>n</sup> (8A),

$$V(z,t) = \text{Re} [ V_s(z) \cdot e^{j\omega t} ]$$

$$= \text{Re} [ (V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}) \cdot e^{j\omega t} ]$$

$$= \text{Re} [ V_0^+ e^{-(\alpha + j\beta)z} e^{j\omega t} + V_0^- e^{(\alpha + j\beta)z} e^{j\omega t} ]$$

$$= \text{Re} [ V_0^+ e^{-\alpha z} e^{j(\omega t - \beta z)} + V_0^- e^{\alpha z} e^{j(\omega t + \beta z)} ]$$

$$\Rightarrow V(z,t) = \left[ V_0^+ \cos(\omega t - \beta z) e^{-\alpha z} + V_0^- \cos(\omega t + \beta z) e^{\alpha z} \right]$$

$\because \text{Re} [ e^{j(\omega t - \beta z)} ] = \text{Re} [ \cos(\omega t - \beta z) + j \sin(\omega t - \beta z) ] = \cos(\omega t - \beta z)$  (13)



Similarly,

$$I(z, t) = \left[ I_0^+ \cos(\omega t - \beta z) \cdot e^{-\gamma z} + I_0^- \cos(\omega t + \beta z) \cdot e^{\gamma z} \right]$$

(14)

Characteristic Impedance (Z<sub>0</sub>)

Ratio of travelling voltage wave to current wave at any point on transmission line.

$$Z_0 = \frac{V_0^+}{I_0^+} \quad [\text{wave propagating in +ve } z \text{ direction}]$$

$$Z_0 = -\frac{V_0^-}{I_0^-} \quad [\text{wave propagating in -ve } z \text{ direction}]$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Proof: From eqn (11),

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$\Rightarrow \frac{\partial V_s(z)}{\partial z} = V_0^+ \cdot (e^{-\gamma z}) \cdot (-\gamma) + V_0^- \cdot e^{\gamma z} \cdot (\gamma)$$

From eqn (5),  $\frac{\partial V_s(z)}{\partial z} = -(R + j\omega L) I_s(z)$

$$-(R + j\omega L) I_s(z) = -V_0^+ \gamma \cdot e^{-\gamma z} + V_0^- \gamma \cdot e^{\gamma z}$$

$$\Rightarrow I_s(z) = \frac{V_0^+ \gamma \cdot e^{-\gamma z}}{R + j\omega L} + \frac{V_0^- \gamma \cdot e^{\gamma z}}{-(R + j\omega L)}$$



$$\Rightarrow I_s(z) = \frac{V_0^+}{\left(\frac{R+j\omega L}{\gamma}\right)} e^{-\gamma z} + \frac{V_0^-}{\left(-\frac{R+j\omega L}{\gamma}\right)} e^{+\gamma z} \quad (15)$$

Comparing eqn (12) & (15),

$$I_0^+ = \frac{V_0^+}{\left(\frac{R+j\omega L}{\gamma}\right)}, \quad I_0^- = \frac{V_0^-}{-\left(\frac{R+j\omega L}{\gamma}\right)}$$

$$\Rightarrow \frac{V_0^+}{I_0^+} = \frac{R+j\omega L}{\gamma}, \quad -\frac{V_0^-}{I_0^-} = \frac{R+j\omega L}{\gamma}$$

But we have defined,  $\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0.$

$$\therefore Z_0 = \frac{R+j\omega L}{\gamma} \quad (15A)$$

$$= \frac{(R+j\omega L)}{\sqrt{(R+j\omega L)(G+j\omega C)}}$$

Using eqn (15A) in eqn (15)

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} \quad (\text{forward})$$

$$I_s(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z} \quad (16)$$

The Wavelength on the line, is

$$\lambda = \frac{2\pi}{\beta} \quad (17)$$

[ Refer - EMT - Plane wave propagation ]

$\beta =$  Phase Constant.

Phase velocity,

$$V_p = \frac{\omega}{\beta} = f\lambda \quad (18)$$

$$\begin{aligned} \because v &= f\lambda = \frac{2\pi f\lambda}{2\pi} \\ &= \frac{(\omega)\lambda}{2\pi} = \frac{\omega}{\left(\frac{2\pi}{\lambda}\right)} = \frac{\omega}{\beta} \end{aligned}$$



The above solution was for general transmission line, including loss effects and it was seen that propagation constant ( $\gamma$ ) and characteristic impedance ( $Z_0$ ) were complex. In many practical cases, however, loss of line is very small and so can be neglected.

A. For lossless line,

$$R = 0, \quad G = 0.$$

A transmission line is said to be lossless, if the conductor of line are perfect ( $\sigma_c = \infty$ ) and dielectric medium is lossless ( $\sigma = 0$ )

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{j\omega L \cdot j\omega C}$$

$$\gamma = j\omega \sqrt{LC} \quad \text{--- (19)}$$

But

$$\gamma = \alpha + j\beta$$

$$\Rightarrow j\omega \sqrt{LC} = \alpha + j\beta$$

$$\alpha = 0 \quad \text{--- (20)}$$

$$\beta = \omega \sqrt{LC} \quad \text{--- (21)}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{0 + j\omega L}{0 + j\omega C}} = \sqrt{\frac{L}{C}}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad \text{--- (22)}$$

Since,  $\alpha = 0$ ,  $\gamma = j\beta = j\omega \sqrt{LC}$

From Eq<sup>n</sup> (11) & (16), the general solution for voltage & current on lossless transmission line can be written as,

$$V_s(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad \text{--- (23)}$$

$$I_s(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad \text{--- (24)}$$

~~Wavelength~~ Wavelength,  $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}}$  (From eq<sup>n</sup> 21) --- (25)

and Phase velocity,  $V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}}$

$\therefore$   $V_p = \frac{1}{\sqrt{LC}}$  --- (26)



B. Distortionless line

A signal normally consists of band of frequencies; wave amplitudes of different frequency components will be attenuated differently on a lossy line because  $\alpha$  is frequency dependent. Since, in general, the phase velocity ( $v = \frac{\omega}{\beta}$ ) of each frequency component is also frequency dependent, this will result in distortion.

A distortionless line is one on which the attenuation constant  $\alpha$  is frequency independent while the phase constant  $\beta$  is linearly dependent on frequency.

Let's derive the condition for distortionless line.

We know

$$\begin{aligned}
 \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\
 &= \sqrt{R \left(1 + \frac{j\omega L}{R}\right) G \left(1 + \frac{j\omega C}{G}\right)} \\
 &= \sqrt{RG \left(1 + \frac{j\omega L}{R}\right) \left(1 + \frac{j\omega C}{G}\right)}
 \end{aligned}$$

$$Z_f \quad 1 + \frac{j\omega L}{R} = 1 + \frac{j\omega C}{G} \quad \text{--- (1)}$$

Then

$$\gamma = \sqrt{RG \left(1 + \frac{j\omega L}{R}\right)^2}$$

$$\gamma = \sqrt{RG} \left(1 + \frac{j\omega L}{R}\right)$$

$$\Rightarrow \alpha + j\beta = \sqrt{RG} + j \frac{\omega L}{R} \sqrt{RG}$$

$$\therefore \alpha = \sqrt{RG}, \quad \beta = \frac{\omega L}{R} \sqrt{RG}$$

$$\therefore \boxed{\alpha = \sqrt{RG}, \quad \beta = \omega L \sqrt{\frac{G}{R}}} \quad \text{--- (2)}$$

Thus,  $\alpha$  is frequency independent  
and  $\beta$  is linearly dependent on frequency.

$\therefore$  The condition for a line to be distortionless is

$$1 + \frac{j\omega L}{R} = 1 + \frac{j\omega C}{G}$$

$$\Rightarrow \frac{j\omega L}{R} = \frac{j\omega C}{G}$$

$$\Rightarrow \frac{L}{R} = \frac{C}{G}$$

$$\Rightarrow \boxed{RC = LG} \quad \sim \quad \boxed{\frac{R}{L} = \frac{G}{C}} \quad \text{--- (3)}$$



Also

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

becomes,

$$= \sqrt{\frac{R \left[ 1 + \frac{j\omega L}{R} \right]}{G \left[ 1 + \frac{j\omega C}{G} \right]}}$$

$$\therefore \frac{1 + j\omega L}{R} = 1 + \frac{j\omega C}{G}$$

$$\Rightarrow \boxed{Z_0 = \sqrt{\frac{R}{G}}} = R_0 + jX_0 \quad \text{--- (4)}$$

$$\therefore R_0 = \sqrt{\frac{R}{G}}, \quad X_0 = 0$$

from eqn (3)

$$\frac{R}{G} = \frac{L}{C}$$

$$\therefore \boxed{Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}} \quad \text{--- (5)}$$

$$U = \frac{V_0}{\beta} = \omega$$

from eqn (2)

$$\beta = \omega L \sqrt{\frac{G}{R}} = \omega L \sqrt{\frac{C}{L}} = \omega \sqrt{LC}$$

from eqn (2)

$$\beta = \omega L \sqrt{\frac{G}{R}}$$

from eqn (3)

$$\frac{G}{R} = \frac{C}{L}$$

$$\therefore \boxed{\beta = \omega \sqrt{LC}} \quad \text{--- (6)}$$

$$= f \lambda \quad \text{--- (7)}$$

$$U = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

Note:

(270)

1) The Phase velocity  $U = \frac{1}{\sqrt{LC}}$  i.e.

independent of frequency. If  $d$  is independent of freq, then there is no distortion of signals.

2) Both  $U$  and  $Z_0$  are same as lossless line.

3) A lossless line is also distortionless line, but a distortionless line is not necessarily lossless.

### Table 7.2 Transmission Line Characteristics

Case

Prop. Const.

$$\gamma = \alpha + j\beta$$

Characteristics Impedance

$$Z_0 = R + jX_0$$

General

$$\sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Lossless

$$0 + j\omega\sqrt{LC}$$

$$\sqrt{\frac{L}{C}} + j.0$$

Distortionless

$$\sqrt{R_G + j\omega L} \sqrt{\frac{G}{R}}$$

$$\sqrt{\frac{L}{C}} + j.0$$

or  $\sqrt{R_G} + j\omega\sqrt{LC}$



Example 1:- An air line has characteristic impedance of  $70 \Omega$  and a phase constant of  $3 \text{ rad/m}$  at  $100 \text{ MHz}$ . Calculate the inductance per meter and capacitance per meter of the line.

Ans :- Given

An air line can be regarded as a lossless line because  $\sigma \approx 0$ , and  $\epsilon_c \rightarrow \infty$ , hence

$R = 0 = G$  and  $\alpha = 0$

$Z_0 = R_0 = \sqrt{\frac{L}{C}}$  ,  $\beta = \omega \sqrt{LC}$

$\therefore \frac{Z_0}{\beta} = \frac{\sqrt{\frac{L}{C}}}{\omega \sqrt{LC}} = \frac{\sqrt{L}}{\sqrt{C}} \times \frac{1}{\omega \sqrt{L} \sqrt{C}} = \frac{1}{\omega C}$

$\Rightarrow Z_0 \omega C = \beta$

$\Rightarrow C = \frac{\beta}{Z_0 \omega} = \frac{3}{70 \times 2\pi \times (100 \times 10^6)} = 68.2 \frac{\text{pF}}{\text{m}}$

$Z_0 = \sqrt{\frac{L}{C}}$

$\Rightarrow \frac{L}{C} = Z_0^2 \Rightarrow L = Z_0^2 \cdot C$

$\Rightarrow L = (70)^2 \times (68.2 \times 10^{-12}) = 334.2 \frac{\text{nH}}{\text{m}}$

$\therefore C = 68.2 \frac{\text{pF}}{\text{m}}, L = 334.2 \frac{\text{nH}}{\text{m}}$

(Ans)

A distortionless line has  $Z_0 = 60 \Omega$ , (272)

$\alpha = 20 \text{ m Np/m}$ ,  $U = 0.6c$ ,  $c = \text{velocity of light in vacuum}$

Find,  $R, L, G, C$ , and  $\lambda$

at  $100 \text{ MHz}$ .

Ans: For distortionless line

$$RC = LG \Rightarrow G = \frac{RC}{L} \quad \text{--- (1)}$$

and  $Z_0 = \sqrt{\frac{L}{C}} \quad \text{--- (2)}$

$$\alpha = \sqrt{RG} = \sqrt{R} \times \sqrt{\frac{RC}{L}} = R \sqrt{\frac{C}{L}} = \frac{R}{Z_0} \quad \text{--- (2A)}$$

$$\therefore R = \alpha Z_0 \quad \text{--- (3)}$$

But  $U = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad \text{--- (4)}$

$$\therefore R = \alpha Z_0 = 20 \times 10^{-3} \times 60 = 1.2 \frac{\Omega}{\text{m}}$$

$\frac{\text{Eqn (2)}}{\text{Eqn (4)}} \Rightarrow \text{gives } \frac{Z_0}{U} = \frac{\sqrt{L}}{\sqrt{C}} \times \frac{\sqrt{L}}{\sqrt{C}}$

$$\Rightarrow L = \frac{Z_0^2}{U}$$

$$\therefore L = \frac{60}{0.6 \times 3 \times 10^8} = 333 \frac{\text{mH}}{\text{m}}$$

From eqn (2A),  $\alpha^2 = RG$

$$\Rightarrow G = \frac{\alpha^2}{R} = \frac{(20 \times 10^{-3})^2}{1.2} = 333 \frac{\text{MS}}{\text{m}}$$



From eqn ①

273

$$C = \frac{L G}{R}$$

$$= \frac{333 \times 10^{-9} \times 333 \times 10^{-6}}{1.2}$$

$$= 92407.5 \times 10^{-15}$$

$$= 92.4075 \times 10^{-12}$$

$$\Rightarrow C = 92.4075 \frac{\text{pF}}{\text{m}}$$

$$\lambda = \frac{v}{f} = \frac{0.6 \times 3 \times 10^8}{100 \times 10^6} = 1.8 \text{ meter}$$

But we know

$$V_p = \frac{1}{\sqrt{\mu\epsilon}}$$

[ Refer EMT ]

Case - I

for free space / air (contains no ferromagnetic material)

$$V_p = \frac{1}{\sqrt{\mu_0\epsilon_0}} = c = 3 \times 10^8 \text{ m/sec.} \quad (33)$$

Case - II

when dielectric of a lossy microwave transmission line is not air,  $V_p <$  velocity of light

$$V_p = \frac{1}{\sqrt{\mu\epsilon}} = \frac{c}{\sqrt{\mu_r\epsilon_r}} \quad (34)$$

$$\begin{aligned} \mu_r &= \frac{\mu}{\mu_0} \\ \epsilon_r &= \frac{\epsilon}{\epsilon_0} \\ \frac{1}{\sqrt{\mu\epsilon}} &= \frac{1}{\sqrt{\mu_0\mu_r\epsilon_0\epsilon_r}} \\ &= \frac{1}{\sqrt{\mu_0\epsilon_0} \sqrt{\mu_r\epsilon_r}} \\ &= \frac{c}{\sqrt{\mu_r\epsilon_r}} \end{aligned}$$

Ex - 1)

A transmission line has the

following parameters

$$R = 2 \Omega/m, \quad G = 0.5 \text{ mho/m}, \quad f = 1 \text{ GHz}$$

$$L = 8 \text{ nH/m}, \quad C = 0.23 \text{ pF/m}$$

Calculate (a) the characteristic impedance (b) propagation constant

$$\begin{aligned} \text{Ans :- } Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{2 + j \cdot 2\pi \cdot 10^9 \times 8 \times 10^{-9}}{0.5 \times 10^{-3} + j \cdot 2 \cdot \pi \cdot 10^9 \times 0.23 \times 10^{-12}}} \\ &= \sqrt{\frac{2 + j16\pi}{10^{-3}(0.5 + j0.46\pi)}} = \sqrt{\frac{50.31 \angle 87.72^\circ}{15.29 \times 10^4 \angle 70.91^\circ}} \end{aligned}$$

Use Rectangular to Polar conversion in calculator



$$\therefore Z_0 = \sqrt{\frac{50.31 \times 10^4}{15.29}} \angle \left( \frac{87.72 - 70.91}{2} \right)$$

$$Z_0 = 181.39 \angle 8.40^\circ \quad \left\{ \text{Polar form} \right\}$$

$$Z_0 = 179.44 + j 26.50 \text{ ohm} \quad \left\{ \text{Rectangular form} \right\}$$

(b) Propagation Constant,  $(\gamma)$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(50.31 \angle 87.72^\circ) (15.29 \times 10^4 \angle 70.91^\circ)}$$

$$\sqrt{(50.31 \times 15.29 \times 10^4) \angle 158.63^\circ}$$

$$= 0.2774 \angle 79.31^\circ$$

$$\left( \because \frac{158.63}{2} = 79.31^\circ \right)$$

$$\gamma = 0.051 + j 0.273$$


2009-BPUT - 2 marks

1) Write down 2 difference bet<sup>n</sup> a parallel wire line and a Co-axial line.

Ans :

Parallel wire line

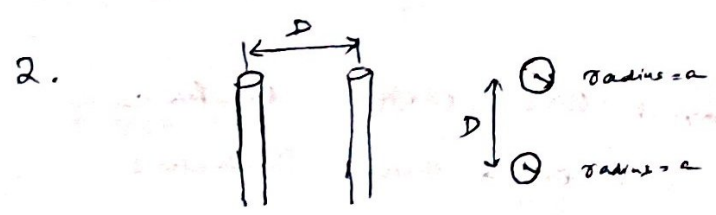
1) It contains 2-parallel conductors or wires without shielded.



- 3. More power loss due to radiation.
- 4. It is less effective in unbalanced load condition

Co-axial line

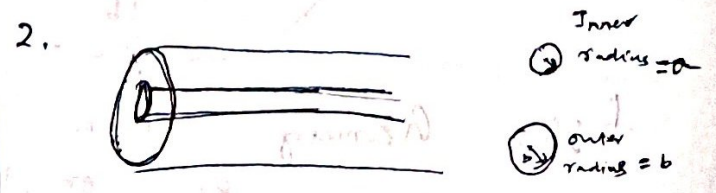1. It contains 2-parallel conductors in a shielded tube.




- i.e.
- 
- Less radiation,
  - 3. Less power is lost
  - 4. It is more effective in unbalanced load condition.



The terminated transmission line :-

In the analysis of the solutions of transmission line eq's, the traveling wave along the line contains two components: one traveling in +ve Z-direction and other traveling the -ve Z direction. If the load impedance is equal to the line characteristic impedance, however, the reflected traveling wave doesn't exist.

Figure 6, shows a transmission line terminated on an impedance  $Z_L$ .

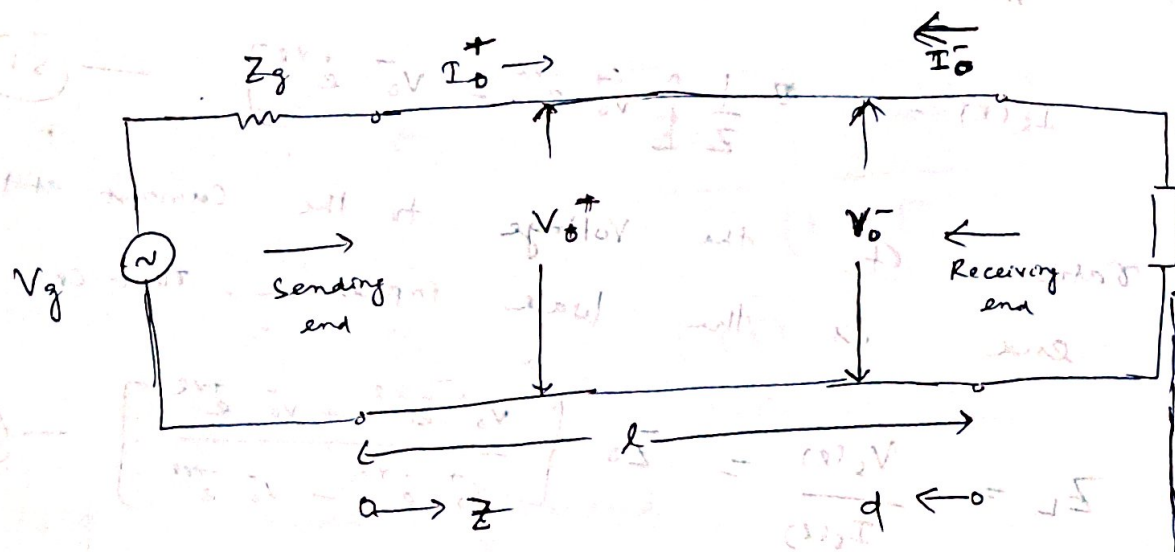

Note:-  
 of a point  
 $Z \rightarrow$  distance from source end.  
 $d \rightarrow$  distance from receiving end.  
 $V_g =$  Voltage at generating end.  
 $Z_g \rightarrow$  Impedance of generator.  
 $V_0^+ \rightarrow$  Incident voltage amplitude  
 $V_0^- \rightarrow$  Reflected voltage amplitude  
 for  
 Similarly for current.  
 and  $l = Z + d$

Fig 6:- Transmission line terminated on a load impedance.

It is usually more convenient to start solving the transmission line problem from the receiving rather than the sending end, since the voltage-current relationship at the load point is fixed by the load impedance. The incident voltage and current waves traveling along the

The transmission line are given by 28

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad (47)$$

$$I_s(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \quad (48)$$

in which current wave can be expressed in terms of the voltage by

$$I_s(z) = \frac{V_0^+ e^{-\gamma z}}{Z_0} - \frac{V_0^- e^{+\gamma z}}{Z_0} \quad (49) \quad \left[ \text{Refer eqn (16)} \right]$$

If the line has a length  $l$ , the voltage and current at the receiving end become

$$V_s(l) = V_0^+ e^{-\gamma l} + V_0^- e^{+\gamma l} \quad (50)$$

$$I_s(l) = \frac{1}{Z_0} \left[ V_0^+ e^{-\gamma l} - V_0^- e^{+\gamma l} \right] \quad (51)$$

The ratio of the voltage to the current at the receiving end is the load impedance. That is,

$$Z_L = \frac{V_s(l)}{I_s(l)} = Z_0 \left[ \frac{V_0^+ e^{-\gamma l} + V_0^- e^{+\gamma l}}{V_0^+ e^{-\gamma l} - V_0^- e^{+\gamma l}} \right] \quad (52)$$

The reflection coefficient, which is denoted by

$\Gamma$  (gamma), is defined as

Voltage reflection coefficient ( $\Gamma_v$ ) =  $\frac{\text{Reflected voltage wave}}{\text{Incident voltage wave}}$

$$\Gamma_v = \frac{V_0^- e^{+\gamma l}}{V_0^+ e^{-\gamma l}} \quad (53)$$



Similarly  
 Current reflection coefficient ( $\Gamma_I$ ) =  $\frac{I_0^- e^{+\gamma L}}{I_0^+ e^{-\gamma L}}$  — (54)

Generally reflection coefficient means voltage

reflection coefficient,  $\Gamma_V = \Gamma$

$$\Gamma = \frac{V_0^- e^{+\gamma L}}{V_0^+ e^{-\gamma L}} \quad \text{--- (53)}$$

From eqn (52),

$$Z_L = \frac{Z_0 \cdot \cancel{V_0^+ e^{-\gamma L}} \left[ 1 + \frac{V_0^- e^{+\gamma L}}{V_0^+ e^{-\gamma L}} \right]}{\cancel{V_0^+ e^{-\gamma L}} \left[ 1 - \frac{V_0^- e^{+\gamma L}}{V_0^+ e^{-\gamma L}} \right]}$$

$$\Rightarrow Z_L = \frac{Z_0 (1 + \Gamma)}{(1 - \Gamma)}$$

$$\Rightarrow \frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$$

Using Componendo & dividendo,

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(1 + \Gamma) - (1 - \Gamma)}{(1 + \Gamma) + (1 - \Gamma)} = \frac{\cancel{1 + \Gamma} + 1 + \Gamma}{1 + \cancel{1 - \Gamma} - 1 + \Gamma}$$

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2\Gamma}{2}$$

$$\Rightarrow \boxed{\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}} \quad \text{--- (56)}$$

If  $Z_L = Z_0$  (i.e.) the terminating or load impedance is equal to the ~~load~~ characteristic impedance then

$$\Gamma = 0, \quad \left[ \text{from Equation (56)} \right]$$

and there will be no reflection from the receiving end. Thus a terminating impedance that differs from the characteristic impedance will create a reflected wave traveling toward the source from the termination.

Current reflection Coefficient

Note:  $\Gamma = 0$

$$\Rightarrow \frac{V_0^- e^{-\gamma x}}{V_0^+ e^{+\gamma x}} = 0$$

$$\Rightarrow \frac{V_0^- e^{-\gamma x}}{V_0^+ e^{+\gamma x}} = 0$$

$$\Rightarrow \text{Reflected Voltage} = 0$$

$$I_s(x) = I_0^+ e^{-\gamma x} + I_0^- e^{+\gamma x}, \quad \text{from eqn (48)}$$

$$V_s(x) = I_0^+ Z_0 e^{-\gamma x} + (-I_0^- Z_0) e^{+\gamma x}$$

$$\left. \begin{array}{l} \because Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} \\ \text{from eqn (47)} \end{array} \right\}$$

$$\frac{V_s(x)}{I_s(x)} = \frac{Z_0 [I_0^+ e^{-\gamma x} - I_0^- e^{+\gamma x}]}{[I_0^+ e^{-\gamma x} + I_0^- e^{+\gamma x}]}$$

$$\left. \begin{array}{l} \therefore \\ \Gamma_r = \frac{I_0^- e^{+\gamma x}}{I_0^+ e^{-\gamma x}} \end{array} \right\}$$

$$= Z_0 \cdot \frac{I_0^+ e^{-\gamma x} [1 - \frac{I_0^- e^{+\gamma x}}{I_0^+ e^{-\gamma x}}]}{I_0^+ e^{-\gamma x} [1 + \frac{I_0^- e^{+\gamma x}}{I_0^+ e^{-\gamma x}}]}$$

$$= Z_0 \cdot \frac{[1 - \Gamma_r]}{[1 + \Gamma_r]}$$

$$Z_L = \frac{Z_0 [1 - \Gamma_r]}{[1 + \Gamma_r]}$$

$$\Rightarrow \frac{Z_L}{Z_0} = \frac{1 - \Gamma_r}{1 + \Gamma_r}$$



Using components and dividends,

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(1 - \Gamma_v) - (1 + \Gamma_v)}{(1 - \Gamma_v) + (1 + \Gamma_v)}$$

$$\Rightarrow \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\cancel{1} - \Gamma_v - \cancel{1} - \Gamma_v}{1 - \cancel{\Gamma_v} + 1 + \cancel{\Gamma_v}} = \frac{-2\Gamma_v}{2}$$

$$\Rightarrow \boxed{\Gamma_v = \frac{Z_0 - Z_L}{Z_0 + Z_L} = -\Gamma_i} \quad \text{--- (57)}$$

∴ Current reflection coefficient is -ve of voltage reflection coefficient.

Transmission Coefficient :-

A transmission line terminated on its characteristic impedance  $Z_0$  is called a properly terminated line. Otherwise it is called an improperly terminated line. There is a reflection coefficient  $\Gamma$  at any point along an improperly terminated line. According to the principle of conservation of energy, the incident power minus the reflected power must be equal to the power transmitted to the load.

Thus, Transmission coefficient 'T', is defined

as

$$T = \frac{\text{Transmitted Voltage}}{\text{Incident Voltage}} = \frac{\text{Transmitted Current}}{\text{Incident Current}}$$

or

$$T = \frac{V_{tr}}{V_{inc}} = \frac{I_{tr}}{I_{inc}} \quad \text{--- (58)}$$

Consider a length  $l$  of transmission line, terminated at load impedance ( $Z_L$ ). Let the travelling wave at the receiving end be,

$$V_{tr} e^{-\gamma l} = V_0^+ e^{-\gamma l} + V_0^- e^{+\gamma l} \quad \text{--- (59)}$$

$$I_{tr} e^{-\gamma l} = I_0^+ e^{-\gamma l} + I_0^- e^{+\gamma l} \quad \text{--- (60)}$$

Dividing eq<sup>n</sup> (59), by  $V_0^+ e^{-\gamma l}$ , we have

$$\frac{V_{tr}}{V_0^+} = 1 + \frac{V_0^- e^{+\gamma l}}{V_0^+ e^{-\gamma l}}$$

$$\Rightarrow \frac{V_{tr}}{V_0^+} = 1 + \Gamma_v$$

$$\Rightarrow \boxed{T = 1 + \Gamma_v} \quad \text{--- (61)}$$

$$\left[ \because T = \frac{V_{tr}}{V_{inc}} = \frac{V_{tr}}{V_0^+} \right]$$

$$\Rightarrow T = 1 + \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Rightarrow T = \frac{Z_L + Z_0 + Z_L - Z_0}{Z_L + Z_0}$$

$$\Rightarrow \boxed{T = \frac{2Z_L}{Z_L + Z_0}} \quad \text{--- (62)}$$

$$\text{Transmitted Power} = \text{Incident power} - \text{Reflected power} \quad \text{--- (63)}$$



~~Incident~~

~~Power = V~~

Incident voltage =  $V_0^+ e^{-\gamma l}$

$= V_0^+ \frac{1}{e^{(\alpha + j\beta)l}}$

$= V_0^+ \frac{e^{-\alpha l} \cdot e^{-j\beta l}}{e}$

$= V_0^+ \cdot e^{-\alpha l} [\cos \beta l - j \sin \beta l]$

~~Power~~

$(V_{rms} = \frac{V_m}{\sqrt{2}})$

In this case power,

$P_{inc} = \frac{\left(\frac{V_0^+ e^{-\alpha l}}{\sqrt{2}}\right)^2}{Z_0} = \frac{\left(V_0^+ e^{-\alpha l}\right)^2}{2Z_0}$  (64)

Repeating the same for, transmitted and reflected

power, eq<sup>n</sup> (63), becomes,  $\frac{Z_L}{Z_0}$

$\downarrow$  (Power transmitted to the load)  $\frac{Z_L}{Z_0}$

$\frac{(V_{tr} e^{-\alpha l})^2}{2Z_L} = \frac{(V_0^+ e^{-\alpha l})^2}{2Z_0} - \frac{(V_0^- e^{+\alpha l})^2}{2Z_0}$

$\Rightarrow \frac{Z_0}{Z_L} \cdot (V_{tr} e^{-\alpha l})^2 = (V_0^+ e^{-\alpha l})^2 - (V_0^- e^{+\alpha l})^2$

$\Rightarrow \frac{Z_0}{Z_L} \cdot (V_{tr} e^{-\alpha l})^2 = (V_0^+ e^{-\alpha l})^2 \left[ 1 - \left(\frac{V_0^- e^{+\alpha l}}{V_0^+ e^{-\alpha l}}\right)^2 \right]$

$\Rightarrow \frac{Z_0}{Z_L} \cdot \left(\frac{V_{tr} e^{-\alpha l}}{V_0^+ e^{-\alpha l}}\right)^2 = 1 - \Gamma_v^2$  ∴  $\Gamma_v = \frac{V_0^- e^{+\alpha l}}{V_0^+ e^{-\alpha l}}$

$\Rightarrow \frac{Z_0}{Z_L} \cdot T^2 = 1 - \Gamma_v^2$   $T = \frac{V_{tr} e^{-\alpha l}}{V_0^+ e^{-\alpha l}}$

$\Rightarrow T^2 = \frac{Z_L}{Z_0} (1 - \Gamma_v^2)$

} (65)

Simply  $T^2 = \frac{Z_L}{Z_0} (1 - \Gamma^2)$

39  
 Ex-2 :- A certain transmission line has a characteristic impedance of  $75 + j0.01 \Omega$  and is terminated in a load impedance of  $70 + j50 \Omega$ . Compute (a)

reflection coefficient; (b) the transmission coefficient

(c) verify that  $T^2 = \frac{Z_L}{Z_0} (1 - \Gamma^2)$  (eqn 65)

(d) verify that  $T = 1 + \Gamma$  (eqn 61)

Ans :- Given

$$Z_0 = 75 + j0.01 \Omega$$

$$Z_L = 70 + j50 \Omega$$

(a) Reflection Coefficient ( $\Gamma$ ) =  $\frac{Z_L - Z_0}{Z_L + Z_0}$

$$= \frac{(70 + j50) - (75 + j0.01)}{(70 + j50) + (75 + j0.01)}$$

$$= \frac{-5 + j49.99}{145 + j50.01}$$

$$= \frac{50.24 \angle 95.71^\circ}{153.38 \angle 19.03^\circ}$$

$$= \frac{50.24}{153.38} \left( \angle (95.71) - (19.03) \right)$$

$$= (0.33) \angle 76.68^\circ$$

$$\Gamma = 0.076 + j0.32$$

(Ans)



(b) Transmission Coefficient (T) =  $\frac{2Z_L}{Z_L + Z_0}$

$$T = \frac{2 \times (70 + j50)}{(70 + j50) + (75 + j0.01)} = \frac{140 + j100}{153.38 \angle 19.03^\circ}$$

(As derived earlier)

$$= \frac{172.05 \angle 35.54^\circ}{153.38 \angle 19.03^\circ}$$

$$T = 1.12 \angle 16.51^\circ$$

$T = 1.08 + j0.32$

(c) R.I.S  $T^2 = [1.12 \angle 16.51^\circ]^2$   
 $T^2 = 1.25 \angle 33.02^\circ$  ( $\because 2 \times 16.51 = 33.02$ )

R.I.S

$$\frac{Z_L}{Z_0} (1 - \Gamma^2)$$

$$= \frac{70 + j50}{75 + j0.01} [1 - (0.33 \angle 76.68^\circ)^2]$$

$$= \frac{86 \angle 35.54^\circ}{75 \angle 0.01^\circ} [(1) - (0.109 \angle 153.36^\circ)]$$

( $\because 2 \times 76.68 = 153.36$ )

$$= \frac{86 \angle 35.54^\circ}{75 \angle 0.01^\circ} \times [1 - (-0.097 + j0.049)]$$

$$= \frac{86 \angle 35.54^\circ}{75 \angle 0.01^\circ} \times (1.097 + j0.049)$$

$$\begin{aligned} \therefore \frac{Z_L}{Z_0} [1 - \Gamma^2] &= \frac{86 \angle 35.54}{75 \angle 0.01} \quad 1.10 \angle -2.55 \\ &= \left( \frac{86 \times 1.10}{75} \right) \angle [35.54 - 0.01 - 2.55] \\ &= 1.26 \angle 33^\circ \quad \begin{matrix} L, 11.05 \\ R, 14.5 \end{matrix} \end{aligned}$$

(d)

To verify,  $\Gamma = 1 + \Gamma$

$$\Gamma = 1.08 + j0.32 \quad (L, 11.5)$$

$$1 + \Gamma = 1 + (0.076 + j0.32)$$

$$1 + \Gamma = 1.076 + j0.32 \quad (R, 11.5)$$

$$L, 11.5 = R, 11.5$$

Time - Average Power flow along the line

For a lossless transmission line terminated by an arbitrary load impedance  $Z_L$ ,

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad (66)$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad (67)$$

$\therefore \gamma = \alpha + j\beta$   
 lossless line,  $\alpha = 0$   
 $\gamma = j\beta$

$$\Gamma = \left. \frac{V_0^-}{V_0^+} \right|_{z=0} = \text{Reflection Coefficient}$$

$$\Rightarrow V_0^- = \Gamma V_0^+$$



Eqn (66) becomes,

$$V(z) = V_0^+ \left[ e^{-j\beta z} + \Gamma e^{j\beta z} \right]$$

$$I(z) = \frac{V_0^+}{Z_0} \left[ e^{-j\beta z} - \Gamma e^{j\beta z} \right]$$

Time-avg power flow along the line at the point z;

$$P_{av} = \frac{1}{2} \text{Re} \left[ V(z) \cdot I^*(z) \right]$$

$$= \frac{1}{2} \text{Re} \left\{ V_0^+ \left[ e^{-j\beta z} + \Gamma e^{j\beta z} \right] \cdot \frac{V_0^+}{Z_0} \left[ e^{+j\beta z} - \Gamma^* e^{-j\beta z} \right] \right\}$$

$$= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \text{Re} \left\{ 1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{+2j\beta z} - |\Gamma|^2 \right\}$$

$$P_{av} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \left[ 1 - |\Gamma|^2 \right]$$

← (only Real part)

Which shows that the avg. power flow is constant at any point on the line and the total power delivered to the load ( $P_{av}$ ) is equal to the incident power  $\left( \frac{|V_0^+|^2}{2Z_0} \right)$ , minus the reflected power  $\left( \frac{1}{2Z_0} |V_0^+|^2 \cdot |\Gamma|^2 \right)$ .

→ If  $\Gamma = 0$ , max<sup>m</sup> power is delivered to the load.  
If  $\Gamma = 1$ , no power is delivered. (All reflected)

→ Return Loss :-

When the load is mismatched, not all of the

available power from the generator is delivered to the load. This "loss" is called return loss (RL) and is defined (in dB) as

$$RL = -20 \log |\Gamma| \text{ dB}$$

So, for a matched load ( $\Gamma = 0$ ),  $RL = \infty \text{ dB}$ .

When total reflection takes place,  $\Gamma = 1$ ,  $RL = 0 \text{ dB}$ .

\* (Derivation not required)

I/P Impedance of a transmission line ( $Z_{in}$ ) or line impedance ( $Z_L$ )

Real power flow on the line is a constant but that the voltage amplitude, at least for a mismatched line, is oscillatory with position on the line. Thus the impedance seen looking into the line varies with position.

The line impedance of a transmission line is the complex ratio of the voltage phasor at any point to the current phasor at that point. It is defined as,

$$Z_L = \frac{V_L(z)}{I_L(z)}$$

Let's consider a transmission line of length  $l$  is terminated by load impedance  $Z_L$ . In general, the voltage and current along a line is sum of respective incident and reflected wave



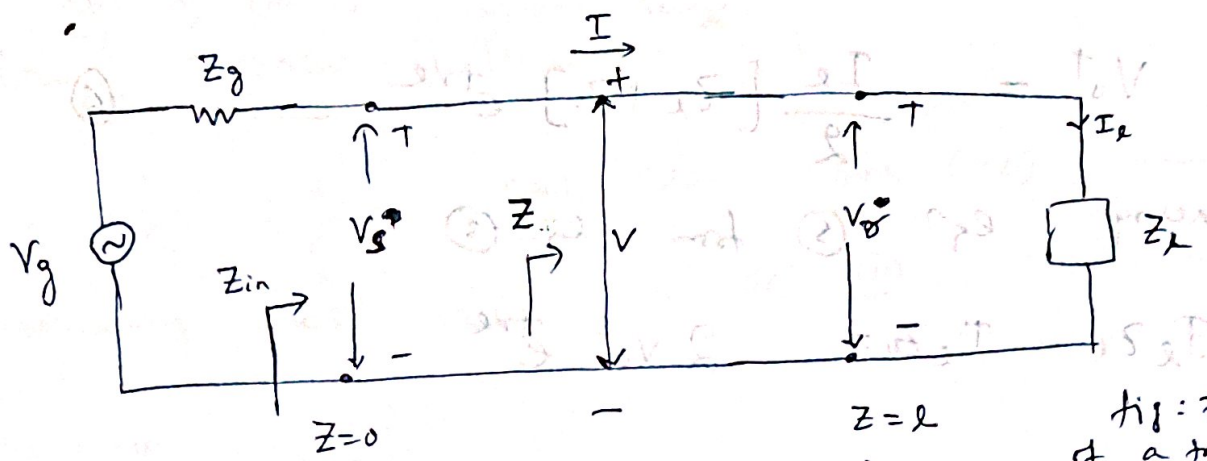


fig: 7 - Diagram of a transmission line showing notation

fig: 7

i.e.  $V_s(z) = V_{inc} + V_{ref} = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$  — (1)

$I_s(z) = I_{inc} + I_{ref} = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$  — (2)

Line impedance can be expressed in terms of  $Z_L + Z_0$ . At  $z=l$ ,  $V_r = I_r \cdot Z_L$ .

Eqn (1) becomes,

$I_r \cdot Z_L = V_0^+ e^{-\gamma l} + V_0^- e^{+\gamma l}$  — (3)

Eqn (2), can be written as

$I_s(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z}$

At  $z=l$ ,  $I_s(z) \cdot Z_0 = V_0^+ e^{-\gamma l} - V_0^- e^{+\gamma l}$  — (4)

At  $z=l$ , eqn (4) becomes,

$I_r \cdot Z_0 = V_0^+ e^{-\gamma l} - V_0^- e^{+\gamma l}$  — (5)

Solving eqn (3) & (5),

Adding eqn (3) & (5)  
 $I_r Z_L + I_r Z_0 = 2V_0^+ e^{-\gamma l}$

$$V_0^+ = \frac{I_e}{2} [z_L + z_0] e^{+\gamma l} \quad \text{--- (6)}$$

Subtracting eqn (5) from eqn (3)

$$I_e z_L - I_e z_0 = 2 V_0^- e^{+\gamma l}$$

$$\Rightarrow V_0^- = \frac{I_e}{2} [z_L - z_0] \cdot e^{-\gamma l} \quad \text{--- (7)}$$

Substituting eqn (6), in eqn (1), ~~we have~~ and letting  $z = l - d$ , we obtain

$$V_S(z) = \frac{I_e}{2} [z_L + z_0] \cdot e^{+\gamma l} \cdot e^{-\gamma(l-d)} + \frac{I_e}{2} [z_L - z_0] \cdot e^{-\gamma l} \cdot e^{+\gamma(l-d)}$$

$$V_S(z) = \frac{I_e}{2} \left[ (z_L + z_0) \cdot e^{+\gamma d} + (z_L - z_0) \cdot e^{-\gamma d} \right] \quad \text{--- (8)}$$

Substituting eqn (7), in eqn (4), we have and letting  $z = l - d$ ,

$$I_S(z) = \frac{1}{z_0} \left[ \frac{I_e}{2} (z_L + z_0) \cdot e^{+\gamma l} \cdot e^{-\gamma(l-d)} - \frac{I_e}{2} (z_L - z_0) \cdot e^{-\gamma l} \cdot e^{+\gamma(l-d)} \right]$$

$$I_S(z) = \frac{I_e}{2 z_0} \left[ (z_L + z_0) e^{+\gamma d} - (z_L - z_0) e^{-\gamma d} \right] \quad \text{--- (9)}$$

$Z_{in} = \frac{V_S(z)}{I_S(z)}$ , dividing eqn (8) by eqn (9), we have

$$Z_{in} = z_0 \left[ \frac{(z_L + z_0) e^{+\gamma d} + (z_L - z_0) e^{-\gamma d}}{(z_L + z_0) e^{+\gamma d} - (z_L - z_0) e^{-\gamma d}} \right] \quad \text{--- (10)}$$



above eq<sup>n</sup> can be simplified using  
The hyperbolic function

$$e^{\pm \gamma z} = \cosh(\gamma z) \pm \sinh(\gamma z) \quad \text{--- (11)}$$

Substituting eq<sup>n</sup> (11), in eq<sup>n</sup> (10), we have

Numerator

$$\begin{aligned} & (Z_L + Z_0) \cdot e^{(\cosh \gamma d + \sinh \gamma d)} + (Z_L - Z_0) \left[ \cosh \gamma d - \sinh \gamma d \right] \\ &= Z_L \cosh \gamma d + Z_L \sinh \gamma d + Z_0 \cosh \gamma d + Z_0 \sinh \gamma d \\ & \quad + Z_L \cosh \gamma d - Z_L \sinh \gamma d - Z_0 \cosh \gamma d + Z_0 \sinh \gamma d \\ &= 2 \left[ Z_L \cosh \gamma d + Z_0 \sinh \gamma d \right] \end{aligned}$$

Denominator

$$\begin{aligned} & (Z_L + Z_0) \cdot (\cosh \gamma d + \sinh \gamma d) - (Z_L - Z_0) \cdot (\cosh \gamma d - \sinh \gamma d) \\ &= Z_L \cosh \gamma d + Z_L \sinh \gamma d + Z_0 \cosh \gamma d + Z_0 \sinh \gamma d \\ & \quad - Z_L \cosh \gamma d + Z_L \sinh \gamma d + Z_0 \cosh \gamma d - Z_0 \sinh \gamma d \\ &= 2 \left[ Z_0 \cosh \gamma d + Z_L \sinh \gamma d \right] \end{aligned}$$

∴ Eq<sup>n</sup> (10), becomes,

$$Z_{in} = Z_0 \cdot \left[ \frac{Z_L \cosh \gamma d + Z_0 \sinh \gamma d}{Z_0 \cosh \gamma d + Z_L \sinh \gamma d} \right] \quad \text{--- (12)}$$

For lossless line,  $\gamma = j\beta$  ( $\alpha = 0$ )

$$\sinh \gamma z = \sinh (j\beta z) = \int \sin \beta z \quad \text{--- (13)}$$

$$\cosh \gamma z = \cosh (j\beta z) = \int \cos \beta z \quad \text{--- (14)}$$

Putting eq<sup>n</sup> (13) + (14) in eq<sup>n</sup> (12), we have

$$Z_{in} = Z_0 \left[ \frac{Z_L (j \cos \beta d) + Z_0 (j \sin \beta d)}{Z_0 (j \cos \beta d) + Z_L (j \sin \beta d)} \right]$$

$$Z_{in} = Z_0 \left[ \frac{Z_L \cos \beta d + j Z_0 \sin \beta d}{Z_0 \cos \beta d + j Z_L \sin \beta d} \right]$$

V.V. Imp


$$Z = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta d}{Z_0 + j Z_L \tan \beta d} \right] \quad \text{--- (15)}$$

~~When~~ When  $d = \lambda$ ,

V.V. Imp

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta \lambda}{Z_0 + j Z_L \tan \beta \lambda} \right] \quad \text{--- (16)}$$

Standing wave :-

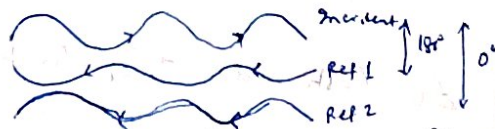

In case of improperly terminated line i.e. when

line terminated with  $Z_L \neq Z_0$  [e.g.  $Z_L = 0$ , or  $Z_L = \infty$ ]  
Short circuit      open circuit etc.

there will be reflection from the load end resulting in the reflected wave from the load end to generator end i.e. in a direction



Opposite to that of traveling wave. So, In 43

a mismatched terminated line, the incident & reflected wave interfere to produce a standing wave pattern along the line. These two oppositely directed traveling wave interfere at some points constructively and at some other points destructively gives rise to maximum and minimum voltage and results standing wave.

The general solutions of the transmission-line consist of 2 waves traveling in opposite directions with unequal amplitude is given by,

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$= V_0^+ e^{-(\alpha + j\beta)z} + V_0^- e^{(\alpha + j\beta)z}$$

$$= V_0^+ \cdot e^{-\alpha z} \cdot \frac{e^{-j\beta z}}{e} + V_0^- e^{\alpha z} \cdot \frac{e^{+j\beta z}}{e}$$

$$= V_0^+ e^{-\alpha z} [\cos \beta z - j \sin \beta z] + V_0^- e^{\alpha z} [\cos \beta z + j \sin \beta z]$$

$$V_s(z) = [V_0^+ e^{-\alpha z} + V_0^- e^{\alpha z}] \cos \beta z - j [V_0^+ e^{-\alpha z} - V_0^- e^{\alpha z}] \sin \beta z$$

1. The maximum amplitude is

$$V_{max} = V_0^+ e^{-\alpha z} + V_0^- e^{\alpha z}$$

$$V_{max} = V_0^+ e^{-\alpha z} [1 + |\Gamma_v|] \quad \text{---} \quad \left( \because |\Gamma_v| = \frac{V_0^- e^{\alpha z}}{V_0^+ e^{-\alpha z}} \right)$$

This occurs at  $\beta z = n\pi$ , where  $n = 0, \pm 1, \pm 2, \dots$

and  $\sin \beta z = 0$  and  $V_s(z) = [V_0^+ e^{-\alpha z} + V_0^- e^{\alpha z}] \cos \beta z$

2) The min<sup>m</sup> amplitude is,

$$V_{min} = V_0^+ e^{-\alpha z} - V_0^- e^{+\alpha z}$$

This occurs at  $\beta z = (2n-1) \frac{\pi}{2}$  where

$$n = 0, \pm 1, \pm 2 \dots$$

$$\therefore V_{min} = V_0^+ e^{-\alpha z} [1 - |\Gamma_v|] \quad \text{--- (18)}$$

3) Distance between two successive maxima is one-half of wavelength ( $\frac{\lambda}{2}$ ).

[e.g.:-  $n=1, \beta z = \frac{\pi}{2}$   
 $n=2, \beta z = \frac{3\pi}{2}$ ] For 2 successive minima, phase diff =  $\frac{3\pi}{2} - \frac{\pi}{2} = \pi$

4) Similarly, for  $2\pi$  phase difference  $\rightarrow \lambda$   
 $\pi$  " "  $\rightarrow \frac{\lambda}{2}$

$$I_{max} = I_0^+ e^{-2\alpha z} (1 + |\Gamma_v|) \quad \text{--- (19)}$$

$$I_{min} = I_0^+ e^{-2\alpha z} (1 - |\Gamma_v|) \quad \text{--- (20)}$$

The standing wave pattern of 2 oppositely traveling waves with unequal amplitude in lossless line are shown in fig (8) and (9).

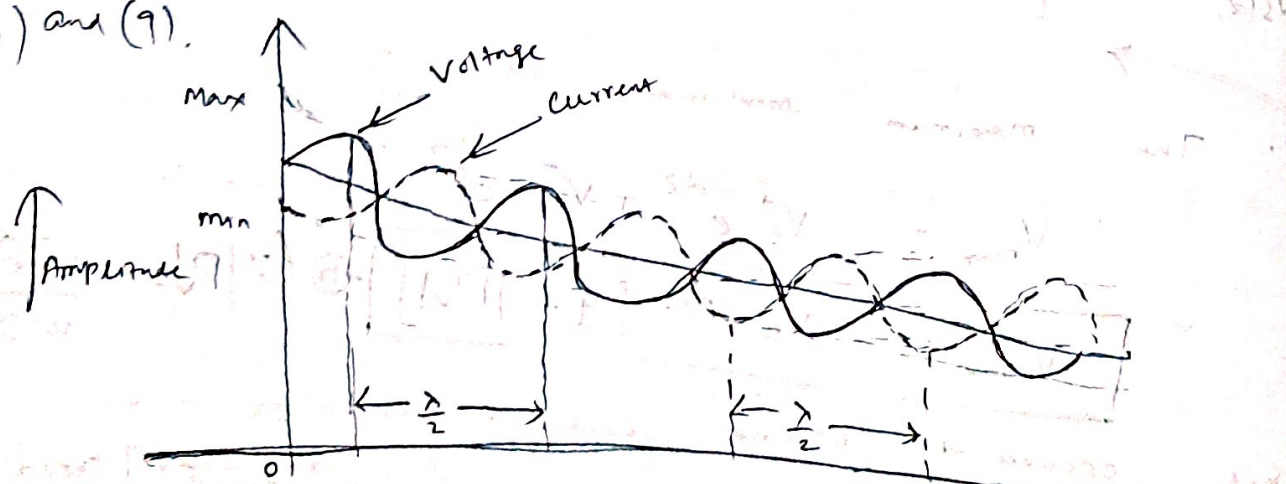


Fig 8:- Standing-Wave Pattern in a lossless line.



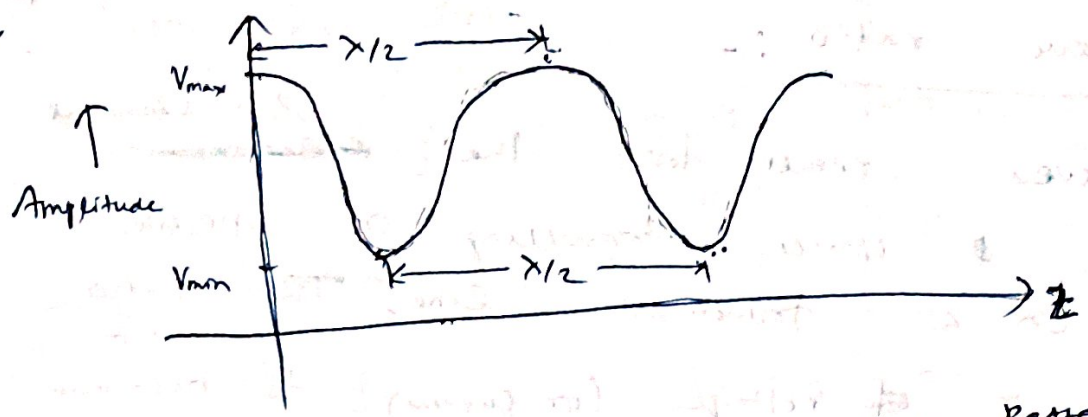


fig 9: - Voltage Standing wave pattern on a lossless line.

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

When  $V_0^+ \neq 0$  and  $V_0^- = 0$ , then ~~the standing wave~~

$$V_s(z) = V_0^+ e^{-\gamma z}$$
(Pure traveling wave)

(21)

When  $V_0^+ = 0$ ,  $V_0^- \neq 0$

$$V_s(z) = V_0^- e^{\gamma z}$$
(Pure reflecting wave)

(22)

When  $V_0^+ = V_0^- = V_0$

$$V_s(z) = V_0 (e^{-\gamma z} + e^{\gamma z})$$

$$V_s(z) = 2V_0 \cosh(\gamma z)$$
(23)

$\cosh(\gamma z) = \frac{e^{-\gamma z} + e^{\gamma z}}{2}$

For lossless line  $\alpha = 0$ ,  $V_s(z) = 2V_0 \cosh(j\beta z)$

$$V_s(z) = 2V_0 \cos(\beta z)$$
(24)

(Pure Standing wave) ( $\because \cosh(j\beta z) = \cos \beta z$ )

Standing-Wave ratio :-

Standing waves result from the ~~interference~~ <sup>simultaneous</sup> presence of waves travelling in opposite directions on a transmission line. The ratio of the maximum voltage (or current) to minimum voltage (or current) is defined as standing-wave ratio.

→ therefore constructively →  $V_{max}$  occurs  
 - " " " " →  $V_{min}$  "

$VSWR = \frac{V_{max}}{V_{min}}$  (25) ,  $ISWR = \frac{I_{max}}{I_{min}}$  (26)

(Voltage Standing Wave Ratio) (Current Standing Wave Ratio)

$VSWR(f) = \frac{V_{max}}{V_{min}} = \frac{V_0^+ e^{-\alpha z} (1 + |\Gamma|)}{V_0^+ e^{-\alpha z} (1 - |\Gamma|)} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$

$f = \frac{1 + |\Gamma|}{1 - |\Gamma|}$

$1 \leq \Gamma \leq 1$   
 $1 \leq f < \infty$

$0 \leq |\Gamma| \leq 1$  (Magnitude)

when  $\Gamma = 0, f = 1$   
 $\Gamma = \pm 1, f = \infty$

Note: -  $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ ,  $Z_L \rightarrow \infty, \Gamma = \frac{Z_0}{Z_0 + \infty} \left( \frac{1 - \frac{Z_0}{Z_L}}{1 + \frac{Z_0}{Z_L}} \right)$   
 $\Gamma = 1 \Rightarrow V_0^- = V_0^+$

- if  $Z_L = 0$ , Short circuit,  $\Gamma = -1$
- if  $Z_L = \infty$ , open circuit,  $\Gamma = 1$
- if  $Z_L = Z_0$ , Matching load,  $\Gamma = 0$

- 1) For pure travelling wave,  $V_0^- = 0, |\Gamma| = 0, f = 1$  (C.A.S)
- 2) For pure standing wave;  $V_0^- = V_0^+, |\Gamma| = 1, f = \infty$
- 3)  $VSWR = 1$ , mean No reflection, Matching load ( $Z_L = Z_0$ )  
 (3) ( $\Gamma = 0$ )



From eq<sup>n</sup> (27)

$$\Gamma = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Using Componendo & dividendo,

$$\frac{\Gamma - 1}{\Gamma + 1} = \frac{1 + |\Gamma| - 1 + |\Gamma|}{1 + |\Gamma| + 1 - |\Gamma|} = \frac{2|\Gamma|}{2}$$

$$\Rightarrow |\Gamma| = \frac{\Gamma - 1}{\Gamma + 1} \quad (28)$$

①  $0 \leq |\Gamma| \leq 1$  (Reflection Coefficient magnitude lies between 0 to 1)

→ Standing wave ratio only defined for lossless line. (on lossy line VSWR changes from position to position)

Input Impedance in different cases

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right] \quad \left[ \text{from eq}^n 16 \right]$$

Case-I (Line is terminated in a short ckt,  $Z_L = 0$ )

$$Z_{in} = Z_0 \left[ \frac{j Z_0 \tan \beta l}{Z_0} \right]$$

$$\boxed{Z_{in} = j Z_0 \tan \beta l}$$

$$Z_{sc} = |Z_{in}|_{Z_L=0} = j Z_0 \tan \beta l \quad (29)$$

So the input impedance at short ckt line is pure reactive, it may be capacitive or inductive depending upon the value of  $l$ .

Note:-

$$Z_{in} = +jx \quad (\text{inductive})$$

$$= -jx \quad (\text{capacitive})$$

Note:-

1)  $\Gamma = 0$ , No reflected wave.

2)  $\Gamma = 1$ , Incident & reflected wave are in same phase. 100% reflection.

3)  $\Gamma = -1$ , Incident & reflected wave are 180° out of phase. 100% reflection.

$$\Gamma_v = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1$$

Voltage reflection coefficient  $\Gamma_v = -1$ .

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \infty$$

Case - II :- Open circuited line ( $Z_L = \infty$ )

$$Z_{oc} = \lim_{Z_L \rightarrow \infty} Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$= \lim_{Z_L \rightarrow \infty} Z_0 \left[ \frac{1 + j \frac{Z_0}{Z_L} \tan \beta l}{\frac{Z_0}{Z_L} + j \tan \beta l} \right]$$

$$= Z_0 \left[ \frac{1 + 0}{0 + j \tan \beta l} \right]$$

$$\therefore \frac{1}{j} = \frac{j}{j^2} = -j$$

$$Z_{oc} = -j Z_0 \cot \beta l \quad \text{--- (30)}$$

So the impedance for open circuited line is also reactive. It may be capacitive or inductive depending upon the value of  $\beta l$ .

Note:-

$$Z_{in} = +jX \text{ (Inductive)}$$

$$= -jX \text{ (Capacitive)}$$

Reflection Coefficient

$$\Gamma_v = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$(\Gamma_v)_{oc} = \lim_{Z_L \rightarrow \infty} \frac{Z_L - Z_0}{Z_L + Z_0}$$



$$\left(\Gamma_v\right)_{oc} = \lim_{Z_L \rightarrow \infty} \frac{1 - \frac{Z_0}{Z_L}}{1 + \frac{Z_0}{Z_L}} = \frac{1-0}{1+0} = 1$$

$$\boxed{\left(\Gamma_v\right)_{oc} = 1}$$

$$V_{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \infty$$

$$\therefore Z_{sc} = j \tan \beta l \cdot Z_0$$

$$Z_{oc} = -j Z_0 \cot \beta l$$

$$Z_{sc} \cdot Z_{oc} = j \tan \beta l \cdot Z_0 \cdot (-j) \cdot Z_0 \cot \beta l$$

$$\boxed{Z_{sc} \cdot Z_{oc} = Z_0^2} \quad (31)$$

$Z_{sc}$  = Short circuited Impedance  
 $Z_{oc}$  = Open circuited Impedance  
 $Z_0$  = Characteristic Impedance

Case-3 (Terminated by Matched load  $Z_L = Z_0$ )

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$= Z_0 \left[ \frac{(Z_0 + j Z_0 \tan \beta l)}{(Z_0 + j Z_0 \tan \beta l)} \right]$$

$$\boxed{Z_{in} = Z_0} \quad \text{or} \quad \boxed{Z_{in} = Z_L} \quad (32) \quad (\because Z_0 = Z_L)$$

Reflection coefficient  $(\Gamma) = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$

$$V_{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0}{1 - 0} = 1$$

$\Gamma = 0$ , No reflection.

$\therefore$  Maxm power is transferred during this matched load condition.

### Special Cases

(i)  $l = \frac{\lambda}{2}$ ,  $\tan \beta l = \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \tan \pi = 0$   
 or  $(l = \text{multiple of } \frac{\lambda}{2})$   $\tan \beta l = 0$ .

$$Z_m = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$= Z_0 \left[ \frac{Z_L}{Z_0} \right] \quad (\because \tan \beta l = 0)$$

$$\Rightarrow \boxed{Z_m = Z_L} \quad \text{--- (33)}$$

$\therefore$  A half-wavelength line (or any multiple of  $\lambda/2$ ) does not alter or transform the load impedance, regardless of the characteristic impedance,  $Z_m$  is purely resistive if  $Z_L$  is purely resistive.

(ii)  $l = \frac{\lambda}{4}$

$$\tan \beta l = \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \tan \frac{\pi}{2} = \infty$$



$$\therefore Z_m = \lim_{\tan \beta l \rightarrow \infty} Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$= \lim_{\tan \beta l \rightarrow \infty} Z_0 \left[ \frac{\frac{Z_L}{\tan \beta l} + j Z_0}{\frac{Z_0}{\tan \beta l} + j Z_L} \right]$$

$$Z_{in} = \frac{Z_0 \times j Z_0}{j Z_L} = \frac{Z_0^2}{Z_L}$$

$$Z_m = \frac{Z_0^2}{Z_L}$$

$Z_m = \frac{Z_0^2}{Z_L}$

(34)

From eq (31) & (34)

$Z_0^2 = Z_{sc} \cdot Z_{oc}$

→ [ True for any length 'l' ]

and 
 $Z_0^2 = Z_m \cdot Z_L$ 
→ [ True only for  $l = \frac{\lambda}{4}$  ]

Thus,  $l = \frac{\lambda}{4}$ , line is known as Quarter-wave transformer because it has the effect of transforming the load impedance, in an inverse manner,  $(Z_m = \frac{Z_0^2}{Z_L})$ , depending on the characteristic impedance of the line.

$$\frac{Z_m}{Z_0} = \frac{Z_0}{Z_L} \Rightarrow = \frac{1}{\left(\frac{Z_L}{Z_0}\right)}$$

⇒ Normalized i/p impedance =  $\frac{1}{\text{Normalized load impedance}}$

Insertion Loss :-

$$\boxed{\text{Insertion loss} = -20 \log |T| \text{ dB}} \quad \text{--- (35)}$$

where  $T =$  Transmission Coefficient  $\left[ T = \frac{1}{1 + \Gamma} \right]$

$$T = \frac{2Z_L}{Z_L + Z_0} \quad \text{(As discussed earlier)}$$

Decibel / Neper / dBm

1) The ratio of two power levels,  $P_1$  &  $P_2$ , in microwave system is expressed as,

$$10 \log \frac{P_1}{P_2}, \text{ dB.} \quad \text{--- (36)}$$

→ voltage,  $20 \log \frac{V_1}{V_2}, \text{ dB.} \quad \text{--- (37)}$

The ratio of 2 voltages across equal load resistance can express in terms of

→ 2) Neper as,  $\boxed{\ln \frac{V_1}{V_2} \text{ Np}} \quad \text{--- (38)}$

Corresponding expression for power,

$$\boxed{\frac{1}{2} \ln \frac{P_1}{P_2} \text{ Np}} \quad \text{--- (39)} \quad \left( \because P = \frac{V^2}{R} \right) \rightarrow V = \sqrt{P \cdot R}$$

$$\boxed{1 \text{ Np} = 8.686 \text{ dB}} \quad \text{--- (40)}$$



Not required

Proof :- Power Gain  
Power, in dB

$$G = 10 \log_{10} \left( \frac{P_1}{P_2} \right) \text{ dB}$$

$$= 10 \frac{\ln \left( \frac{P_1}{P_2} \right)}{\ln 10} \text{ dB} \quad \left( \because \log_{10} x = \frac{\ln x}{\ln 10} \right)$$

$$= \left( \frac{10}{\ln 10} \right) \cdot \left( \ln \frac{P_1}{P_2} \right) \text{ dB}$$

$$G = \left( \frac{10}{\ln 10} \right) 2 \times \left[ \frac{1}{2} \ln \frac{P_1}{P_2} \right] \text{ dB} \quad \text{--- (41)}$$

~~$$\frac{20}{\ln 10} \text{ NP}$$~~

$$\boxed{1 \text{ dB} = 8.686 \text{ NP}}$$

Power gain in NP,

$$G = \left[ \frac{1}{2} \ln \frac{P_1}{P_2} \right] \text{ NP} \quad \text{--- (42)}$$

Dividing eq<sup>n</sup> (41), by 42

$$1 = \frac{20}{\ln 10} \frac{\text{dB}}{\text{NP}}$$

$$1 = 8.686 \frac{\text{dB}}{\text{NP}}$$

$$\Rightarrow \boxed{1 \text{ NP} = 8.686 \text{ dB}} \quad \text{--- (43)}$$

37 If reference power  $P_2 = 1 \text{ mW}$ , Power gain (G)

~~$$1 \text{ dBm} = G = 10 \log \frac{P_1}{1 \text{ mW}}$$~~

$$G = 10 \log \frac{P_1}{1 \text{ mW}}$$

If  $P_1 = 1 \text{ Watt}$ ,  $G = 10 \log 10^3 = 30 \text{ dBm}$ .

Ex-3 A transmission line has a characteristic impedance of  $50 + j0.01 \Omega$  is terminated in a load impedance  $73 - j42.5 \Omega$ .

- Calculate
- (a) The reflection coefficient
  - (b) The standing-wave ratio

Ans: Given,

$$Z_0 = 50 + j0.01 \Omega$$

$$Z_L = 73 - j42.5 \Omega$$

(a) Reflection coefficient ( $\Gamma$ ) =  $\frac{Z_L - Z_0}{Z_L + Z_0}$

~~$$\Gamma = \frac{73 - j42.5 - (50 + j0.01)}{73 - j42.5 + (50 + j0.01)}$$~~

$$\Gamma = \frac{(73 - j42.5) - (50 + j0.01)}{(73 - j42.5) + (50 + j0.01)}$$

$$= \frac{23 - j42.51}{123 - j42.49}$$

$$= \frac{48.33 \angle -61.58}{130.13 \angle -19.05}$$

$$= 0.371 \angle (-61.58 + 19.05)$$

$$\Gamma = 0.371 \angle -42.53^\circ$$



(b)

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$= \frac{1 + 0.371}{1 - 0.371}$$

$$VSWR = \text{2.17}$$

Ex-4:  
BPUT-2010

A Certain transmission line has a characteristic impedance  $75 + j0.01 \Omega$  and is terminated on a load impedance of  $70 + j50 \Omega$ .

- Calculate (i)
- (a) Reflection Coefficient
  - (b) SWR
  - (c) Transmission Coefficient
  - (d) Insertion loss.

Ans :-

(a) Reflection Coefficient

$$Z_0 = 75 + j0.01 \Omega$$

$$Z_L = 70 + j50 \Omega$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0.076 + j0.32 \Omega}{1.076 + j0.32 \Omega} = 0.33 \angle 76.68^\circ$$

As derived in Ex-2  
Page - 34

(b)

VSWR

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.33}{1 - 0.33} = 1.98$$

(c)

Transmission Coefficient

$$T = 1 + \Gamma = 1 + (0.076 + j0.32) = 1.076 + j0.32 \Omega$$

(d) Insertion loss

$$IL = -20 \log |T| \text{ dB}$$

$$= -20 \log |(1.076 + j0.32)|$$

$$= -20 \log 1.12$$

$$IL = -0.98 \text{ dB}$$

(ii) A lossless Co-axial cable is used to delay a pulse by 100 ns. The inductance and capacitance of the cable are 0.20  $\mu\text{H}/\text{m}$  and 60  $\text{pF}/\text{m}$  respectively. Determine the length of cable?

Ans :-

$$L = 0.20 \frac{\mu\text{H}}{\text{m}}$$

$$C = 60 \text{ pF}/\text{m}$$

Phase velocity,  $V_p = \frac{1}{\sqrt{LC}}$

$$= \frac{1}{\sqrt{0.20 \times 10^{-6} \times 60 \times 10^{-12}}}$$

$$= \frac{1}{\sqrt{12 \times 10^{-18}}}$$

$$= \frac{1}{3.46 \times 10^{-9}}$$

$$V_p = 2.89 \times 10^8 \text{ m/sec.}$$



$$\text{time taken} = 100 \text{ ns}$$

$$\Rightarrow \frac{l}{V_p} = 100 \times 10^{-9}$$

$$\Rightarrow l = 100 \times 10^{-9} \times 2.88 \times 10^8$$

$$= 28.8 \times 10^1$$

$$l = 28.8 \text{ meter}$$

(ii) A 25 m long lossless transmission line is terminated with a load having an equivalent impedance of  $40 + j30 \Omega$  at  $10 \text{ MHz}$ . The inductance and capacitance of the line are  $310.4 \text{ nH/m}$  and  $38.28 \text{ pF/m}$  respectively. Calculate,

- Characteristic Impedance
- Phase Constant
- Input Impedance at the sending end and
- Input Impedance at the midpoint of line.

Ans :-  $l = 25 \text{ m}$ ,  $Z_L = 40 + j30 \Omega$ ,  $f = 10 \text{ MHz}$   
 $L = 310.4 \frac{\text{nH}}{\text{m}}$ ,  $C = 38.28 \frac{\text{pF}}{\text{m}}$

(a) Characteristic Impedance

For lossless line [ Eqn (22), Page 18 ]

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{310.4 \times 10^{-9}}{38.28 \times 10^{-12}}}$$

$$= \sqrt{\frac{3104 \times 10^2}{38.28}} = 90.04 \Omega$$

$$Z_0 = 90.04 \Omega$$

(b) Phase Constant

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{c}$$

$$= \frac{2\pi \times 10 \times 10^6}{3 \times 10^8} = \frac{2\pi}{30} = \frac{2\pi}{15}$$

$$\beta = 0.209$$

~~$c = f\lambda$~~   
 $\Rightarrow \lambda = \frac{c}{f}$   
 $c = v_p$

$$\beta = \omega \sqrt{LC} = 2\pi f \sqrt{LC}$$

$$\beta = 2\pi \times 10 \times 10^6 \sqrt{310.4 \times 10^{-9} \times 38.28 \times 10^{-12}}$$

$$= 2\pi \times 10 \times 10^6 \times 34.47 \times 10^{-10}$$


$$\beta = 0.216 \frac{\text{rad}}{\text{m}}$$

(c) Input impedance at the sending end.

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

At the sending end

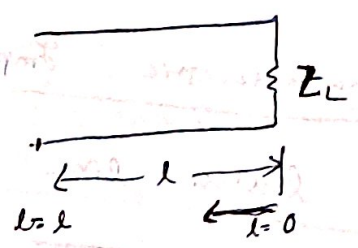$l =$  length of the line  
 $l = 25 \text{ m}$



~~$\tan \beta l = \tan(0.216 \times 25) =$~~

$$\beta l = 0.216 \frac{\text{rad}}{\text{m}} \times 25 \text{ m} = 5.4 \text{ rad.}$$

$$\tan \beta l = -1.21, \quad Z_0 = 90.04 \Omega, \quad Z_L = 40 + j30 \Omega$$



$$Z_{in} = 90.04 \left[ \frac{(40 + j30) + j \cdot (90.04) \cdot (-1.21)}{90.04 + j(40 + j30) \cdot (-1.21)} \right]$$

$$= 90.04 \left[ \frac{40 - j78.94}{126.34 - j48.4} \right]$$

$$= 90.04 \times 88.49 \angle -63.12^\circ$$

$$\underline{135.29 \angle -20.96^\circ}$$

$$= 58.89 \angle -42.15^\circ \quad (-63.12 + 20.96 = -42.15)$$

$$(Z_{in})_{\text{sending end}} = \frac{43.66 - j39.51}{43.66 - j39.51}$$

(φ)  $Z_{in}$  at the midpoint of the line

$$l = \frac{25}{2} = 12.5 \text{ meters}$$

$$\tan \beta l = \tan(0.216 \times 12.5) = \tan(2.7 \text{ rad}) = -0.472$$

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$= 90.04 \left[ \frac{(40 + j30) + j(90.04)(-0.472)}{90.04 + j(40 + j30)(-0.472)} \right]$$

$$= 90.04 \left[ \frac{40 - j12.5}{9104.2 - j18.88} \right]$$

$$= \frac{90.04 \times 41.90 \angle -17.35^\circ}{105.89 \angle -10.27^\circ} = \frac{35.62 \angle -7.08^\circ}{35.34 - j4.39}$$

$$(Z_{in})_{\text{At mid point of transmission line}} = 35.34 - j4.39 \Omega$$

Ex - 5 GPUT 2010

The characteristic impedance of 10m long lossless loss co-axial cable is  $50 \Omega$ . The dielectric ~~lossless~~ material between the inner and outer conductor of the cable has  $\epsilon_r = 3.5$  and  $\mu_r = 1$ .

If the radius of the inner conductor is 1mm,

- \* (a) What should be the outer radius of the cable?
- (b) Find R, L, C, G parameters of co-axial transmission line.

Ans:  $Z_0 = \frac{\eta}{2\pi} \ln\left(\frac{b}{a}\right)$  [  $f = 100 \text{ MHz}$  ]

$\because Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right)}{\frac{2\pi \epsilon}{\ln\left(\frac{b}{a}\right)}}} = \sqrt{\frac{\mu \epsilon}{2\pi \cdot 2\pi \epsilon}} = \sqrt{\frac{\mu \epsilon}{4\pi^2 \epsilon}} = \frac{\sqrt{\mu \epsilon}}{2\pi}$

Where  $\eta = \sqrt{\frac{\mu}{\epsilon}} = \sqrt{\frac{\mu_0 \mu_r}{\epsilon_0 \epsilon_r}} = \sqrt{\frac{\mu_0}{\epsilon_0}} \cdot \sqrt{\frac{\mu_r}{\epsilon_r}} = \frac{\eta_0}{\sqrt{\epsilon_r}}$

(Intrinsic wave impedance)

$\eta = 120\pi \times \sqrt{\frac{1}{3.5}} = 201.51$

$\sqrt{\frac{\mu_0}{\epsilon_0}}$ ,  $\mu_0 = 4\pi \times 10^{-7} \frac{H}{m}$ ,  $\epsilon_0 = \frac{10^{-9}}{36\pi} \frac{F}{m}$

$\sqrt{\frac{4\pi \times 10^{-7} \times 36\pi}{10^{-9}}} = \sqrt{144 \times \pi^2 \times 10^2} = 120\pi$

$Z_0 = \frac{\eta}{2\pi} \ln\left(\frac{b}{a}\right)$

$\Rightarrow 50 = \frac{201.51}{2\pi} \ln\left(\frac{b}{1}\right)$

$\Rightarrow \frac{100\pi}{201.51} = \ln \frac{b}{1}$

$\Rightarrow b = e^{1.559} = 4.754 \text{ mm}$  (Ans)



(b)  $R = \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$

$$= \frac{50}{2\pi} \left[ \frac{1}{1 \times 10^3} + \frac{1}{4.754 \times 10^3} \right]$$

$$= \frac{50}{2\pi} \left[ 1.21 \times 10^3 \right]$$

$R = 9.63 \text{ k}\Omega$

$L = \frac{\mu}{2\pi} \ln \left( \frac{b}{a} \right)$

$$= \frac{\mu_r \mu_0}{2\pi} \ln \left( \frac{4.754}{1} \right)$$

$$= \frac{4\pi \times 10^{-7} \times 1}{2\pi} \ln(4.754)$$

$$= 3.11 \times 10^{-7} \times 10^{-2}$$

$L = 311 \frac{\mu\text{H}}{\text{m}}$

$C = \frac{2\pi \epsilon}{\ln(b/a)} = \frac{2\pi \epsilon_0 \epsilon_r}{\ln(4.754)}$

$$= \frac{2\pi \times \left( \frac{10^{-9}}{36\pi} \right) \times 3.5 \times 1}{1.558}$$

$$= 0.1248 \times 10^{-9}$$

$C = 124.8 \text{ pF/m}$

$G = \frac{2\pi \omega \epsilon'}{\ln(b/a)} = 2\pi \times (2\pi \times 100 \times 10^3) \times \left( \frac{10^{-9}}{36\pi} \right) \times 3.5 \times \frac{1}{1.558}$

( $\because \omega = 2\pi f = 2\pi \times 100 \text{ kHz}$ ),  $\epsilon_0 = \frac{10^{-9}}{36\pi}$ )

$$= 0.784 \times 10^{-4} = 78.4 \frac{\mu\text{S}}{\text{m}}$$

$G = 78.4 \frac{\mu\text{S}}{\text{m}}$

# Smith Chart

Many of the computations required to solve transmission-line problems involves the use of rather complicated equations. The solution of such problems is tedious and difficult because the accurate manipulation of numerous equation is necessary. To simplify their solution, we need a graphic method of arriving at a quick answer.

The Smith Chart, developed by Phillip H. Smith, is a very useful tool, for solving transmission line problems.

→ ~~In Smith chart, we plot~~

→ The Smith Chart consists of a plot of the normalized impedance or admittance with angle and magnitude of a generalized complex reflection coefficient on a unity circle.

→ The chart is applicable to the analysis of a lossless line as well as lossy line.

→ It is used to find out

- (a) Unknown impedance at any distance 'l' on the transmission line.
- (b) VSWR and reflection coefficient
- (c) Return loss and transmission coefficient
- (d) Quarter wave matching and stub matching

→ A Smith chart is a graph that enables any



Complex impedance to be plotted

→ It can use any value of resistance from 0 to ∞ and reactance from -j∞ to +j∞.

→ By using Smith Chart we can get a graphical solution very quickly with accuracy.

\* Mathematical Analysis

\* [ Deviations not required for exam point of view. For knowledge you can refer how these const resistance & reactance circle come in Smith Chart ]

Smith Chart consist of 2 Part Come in Smith Chart

- ✓ (i) Normalized Resistance
- ✓ (ii) Normalized Reactance

We know Reflection coefficient, ( $\Gamma$ )

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Rightarrow \frac{\Gamma}{1} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Using Component & dividendo

$$\frac{\Gamma - 1}{\Gamma + 1} = \frac{(Z_L - Z_0) - (Z_L + Z_0)}{(Z_L - Z_0) + (Z_L + Z_0)}$$

$$\Rightarrow \frac{\Gamma - 1}{\Gamma + 1} = \frac{Z_L - Z_0 - Z_L - Z_0}{Z_L - Z_0 + Z_L + Z_0} = - \frac{2Z_0}{2Z_L}$$

$$\Rightarrow \frac{\Gamma - 1}{\Gamma + 1} = - \frac{Z_0}{Z_L}$$

$$\Rightarrow \frac{Z_L}{Z_0} = \frac{1 - \Gamma}{1 + \Gamma}$$

$$\Rightarrow \boxed{\frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}}$$

Normalized Impedance, defined as,  $\frac{\text{Impedance}}{Z_0}$  ( $Z_0$  (Characteristic Impedance))

$Z = \text{Normalized Impedance} = \frac{Z_L}{Z_0}$

$Z = \frac{1 + \Gamma}{1 - \Gamma}$  (52)

Let  $\Gamma$  consist of real & imaginary part -

$Z$  consist of real & imaginary part -

$\Gamma = \Gamma_r + j \Gamma_i$  (53)

$Z = \sigma + j \alpha$  (54)

Using eqn (53) & (54) in eqn (52), we have

$\sigma + j \alpha = \frac{1 + (\Gamma_r + j \Gamma_i)}{1 - (\Gamma_r + j \Gamma_i)} = \frac{(1 + \Gamma_r) + j \Gamma_i}{(1 - \Gamma_r) - j \Gamma_i}$

$= \frac{\{(1 + \Gamma_r) + j \Gamma_i\} \{(1 - \Gamma_r) + j \Gamma_i\}}{\{(1 - \Gamma_r)^2 + \Gamma_i^2\}}$  [ multiply and divide by  $(1 - \Gamma_r) + j \Gamma_i$  ]

$= \frac{1 - \Gamma_r^2 + j \Gamma_i (1 + \Gamma_r) + j \Gamma_i (1 - \Gamma_r) - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$

Equating the real & imaginary part, we have

$\sigma = \left\{ \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \right\}$  (55)



$$j\alpha = \frac{+j\pi_r + j\pi_i\cancel{\pi_r} + \delta\pi_i - j\cancel{\pi_r}\pi_r}{(1-\pi_r)^2 + \pi_i^2}$$

$$\alpha = \frac{2\pi_i}{(1-\pi_r)^2 + \pi_i^2} \quad \text{--- (56)}$$

[ Rearranging eqn 55, i.e

$$\gamma = \frac{1 - \pi_r^2 - \pi_i^2}{(1-\pi_r)^2 + \pi_i^2}$$

$$\Rightarrow \gamma(1-\pi_r)^2 + \gamma\pi_i^2 = 1 - \pi_r^2 - \pi_i^2$$

$$\Rightarrow \gamma(1 + \pi_r^2 - 2\pi_r) + (\gamma + 1)\pi_i^2 + \pi_r^2 - 1 = 0$$

$$\Rightarrow \gamma + \gamma\pi_r^2 - 2\gamma\pi_r + (1+\gamma)\pi_i^2 + \pi_r^2 - 1 = 0$$

$$\Rightarrow (1+\gamma)\pi_r^2 - 2\gamma\pi_r + (1+\gamma)\pi_i^2 = 1-\gamma$$

$$\Rightarrow \pi_r^2 - 2\pi_r \cdot \frac{\gamma}{1+\gamma} + \pi_i^2 = \frac{1-\gamma}{1+\gamma}$$

$$\Rightarrow \pi_r^2 - 2\pi_r \cdot \frac{\gamma}{1+\gamma} + \left(\frac{\gamma}{1+\gamma}\right)^2 - \left(\frac{\gamma}{1+\gamma}\right)^2 + \pi_i^2 = \frac{1-\gamma}{1+\gamma}$$

$$\Rightarrow \left(\pi_r - \frac{\gamma}{1+\gamma}\right)^2 + \pi_i^2 = \frac{1-\gamma}{1+\gamma} + \left(\frac{\gamma}{1+\gamma}\right)^2$$

$$\Rightarrow \left(\pi_r - \frac{\gamma}{1+\gamma}\right)^2 + \pi_i^2 = \frac{(1-\gamma)(1+\gamma) + \gamma^2}{(1+\gamma)^2} = \frac{1-\cancel{\gamma} + \cancel{\gamma} + \gamma^2}{(1+\gamma)^2}$$

$$\Rightarrow \left(\pi_r - \frac{\gamma}{1+\gamma}\right)^2 + \pi_i^2 = \left(\frac{1}{1+\gamma}\right)^2 \quad \text{--- (57)}$$

Eq<sup>n</sup> (57) represents a family of circles in which each circle has a constant resistance  $r$ . The radius of any circle is  $\frac{1}{1+r}$  and center of any circle is  $\frac{r}{1+r}$  along the real axis in the unity circle, where  $r$  varies from zero to  $\infty$ . All constant resistance circles are plotted in fig 17, according to eq<sup>n</sup> (57).

Center  $(\frac{r}{1+r}, 0)$ , Radius  $= \frac{1}{1+r}$

→ If  $r=0$ , then  $C(0,0)$  and  $R=1$

→ If  $r=1$ , then  $C(0.5,0)$  and  $R=\frac{1}{2}$

→ If  $r=2$ , then  $C(\frac{2}{3},0)$  and  $R=\frac{1}{3}$

→ If  $r=\infty$ , then  $C(1,0)$  and  $R=0$

$\therefore C = (\frac{r}{1+r}, 0)$   
 $= (\frac{1}{1+\frac{1}{r}}, 0)$   
 $\sigma \rightarrow \infty, C = (1, 0)$

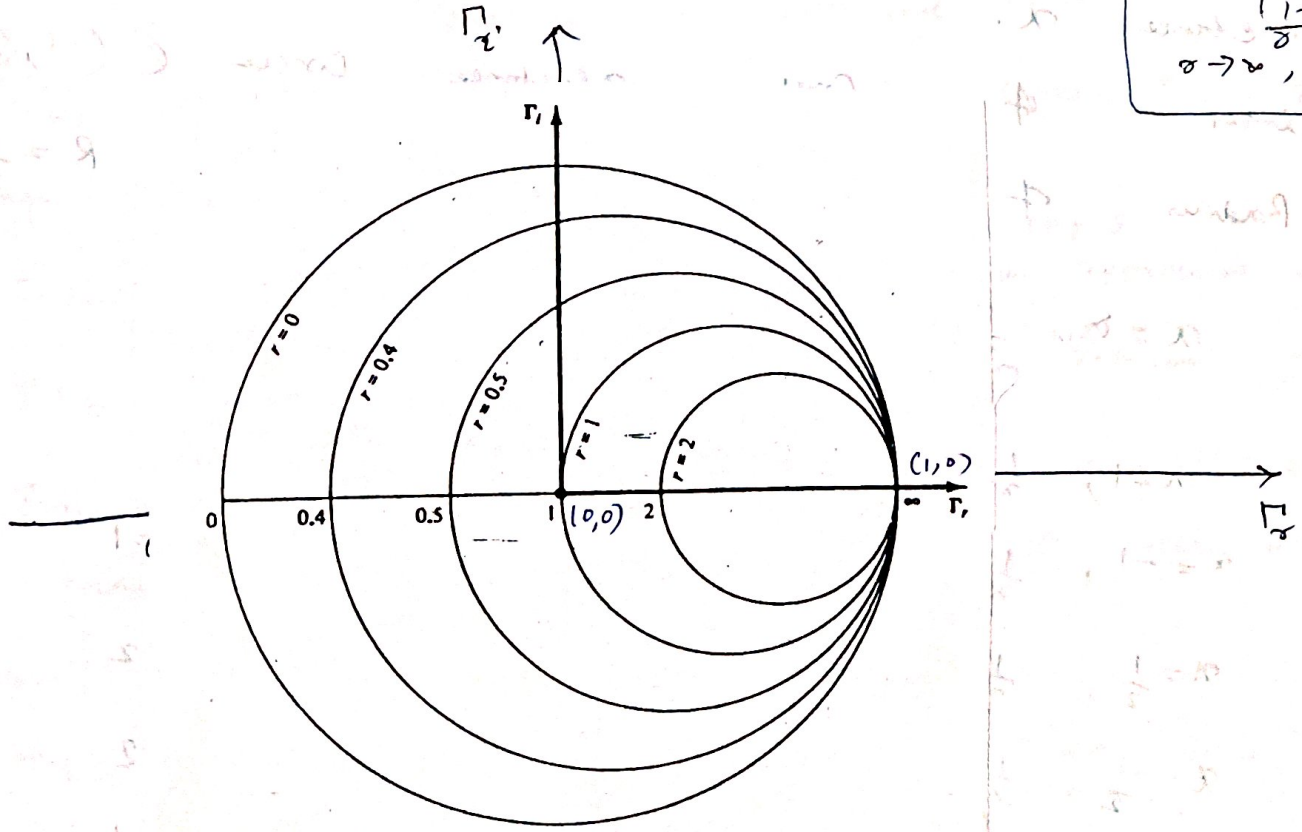


Figure 3-5-2 Constant resistance r circles.



Rearranging

eq<sup>n</sup> (56), i.e

$$\alpha = \frac{2\Gamma_i}{(1-\Gamma_r)^2 + \Gamma_i^2}$$

$$\Rightarrow \alpha(1-\Gamma_r)^2 + \alpha(\Gamma_i^2) = 2\Gamma_i$$

$$\Rightarrow (1-\Gamma_r)^2 + \Gamma_i^2 = \frac{2}{\alpha}\Gamma_i$$

$$\Rightarrow (\Gamma_r - 1)^2 + \Gamma_i^2 - 2\Gamma_i \cdot \frac{1}{\alpha} + \left(\frac{1}{\alpha}\right)^2 - \frac{1}{\alpha^2} = 0$$

$$\Rightarrow (\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{\alpha}\right)^2 = \left(\frac{1}{\alpha}\right)^2 \quad \text{--- (58)}$$

This equation describes a family of circles, but each circle specifies a constant reactance  $\alpha$ .

Center of constant reactance circle  $C(1, \frac{1}{\alpha})$ .

Radius of constant reactance circle  $R = \frac{1}{\alpha}$ .

If  $\alpha = \infty$ ,  $\frac{1}{\alpha} = 0$ , then  $C(1, 0)$  and  $R = 0$

If  $\alpha = 1$ ,  $\frac{1}{\alpha} = 1$ , then  $C(1, 1)$ , and  $R = 1$

If  $\alpha = -1$ ,  $\frac{1}{\alpha} = -1$ , then  $C(1, -1)$ , and  $R = 1$

If  $\alpha = \frac{1}{2}$ ,  $\frac{1}{\alpha} = 2$ , then  $C[1, 2]$ ,  $R = 2$

If  $\alpha = -\frac{1}{2}$ ,  $\frac{1}{\alpha} = -2$ , then  $C[1, -2]$ ,  $R = 2$

If  $\alpha = 2$ ,  $\frac{1}{\alpha} = \frac{1}{2}$ , then  $C[1, \frac{1}{2}]$ ,  $R = \frac{1}{2}$  ]

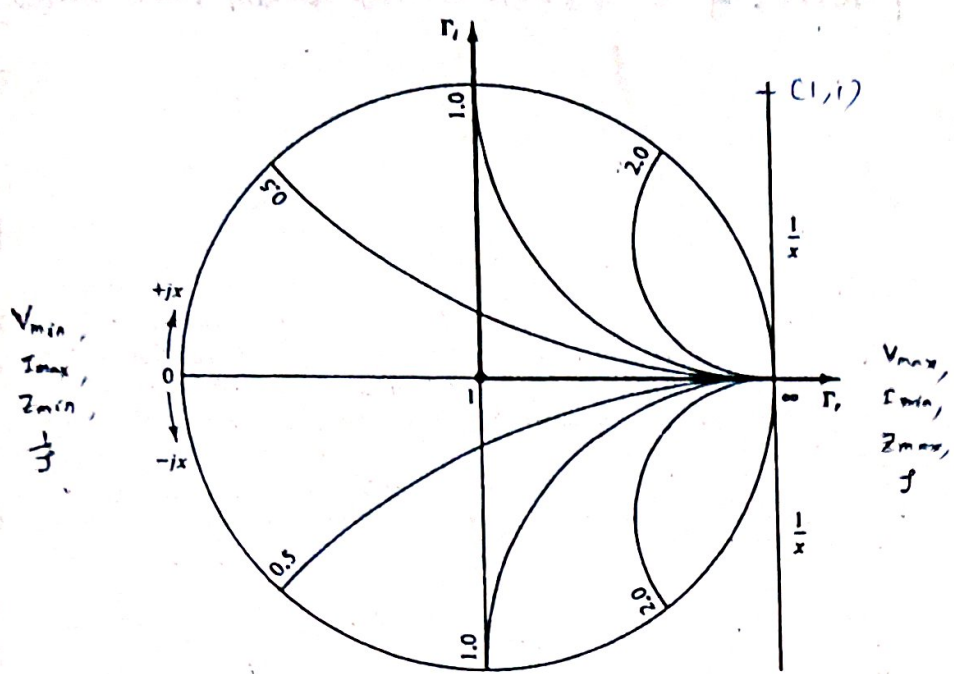


Figure 3-5-3 Constant reactance x circles.

Characteristics of Smith Chart :-

- 1) The constant 'r' (resistance) and constant 'x' (reactance) loci form two families of orthogonal circles in the chart.
- 2) The constant 'r' and constant 'x' circles all pass through the point  $(\Gamma_r = 1, \Gamma_i = 0)$ . (fig 18)
- 3) The upper half of the diagram represents  $+jx$ .
- 4) The lower half of the diagram represents  $-jx$ .  
[or upper or lower half of Real axis]
- 5) For admittance the constant 'r' circles become constant 'g' (conductance) circles and the constant 'x' circle become constant 'b' (susceptance) circles.
- 6) The distance around the Smith chart once is one-half wavelength  $(\lambda/2)$
- 7) At a point of  $Z_{min} = 1/j$ , there is  $V_{min}$  on



the line. [Note:  $\rho = \text{VSWR}$  (Voltage Standing wave Ratio)] 87

8) At a point  $Z_{\max} = \rho$ , there is  $V_{\max}$  on the line.

9) The horizontal radius to the right of the Chart Center corresponds to  $V_{\max}$ ,  $I_{\min}$ ,  $Z_{\max}$  and  $\rho$ .  $\hookrightarrow$  [fig 18]

10) The horizontal radius to the left of the Chart Center corresponds to  $V_{\min}$ ,  $I_{\max}$ ,  $Z_{\min}$  and  $\frac{1}{\rho}$ .

11) Since the normalized admittance 'y' is a reciprocal of the normalized impedance 'z', the corresponding quantities in the admittance chart are  $180^\circ$  out of phase with those in the impedance chart.

12) The normalized impedance or admittance is repeated for every half wavelength of distance.

13) The distances are given in wavelengths toward the generator and also toward the load.


Note: Derived earlier The magnitude of reflection coefficient is related to standing-wave ratio by the following relation

$$|\Gamma| = \frac{\rho - 1}{\rho + 1}$$

EX-9:- (Pozar book, ex-2.2, page 67)

A load impedance of  $40 + j70 \Omega$  terminates a lossless transmission line that is  $0.3\lambda$  long. Find the reflection coefficient at the load,

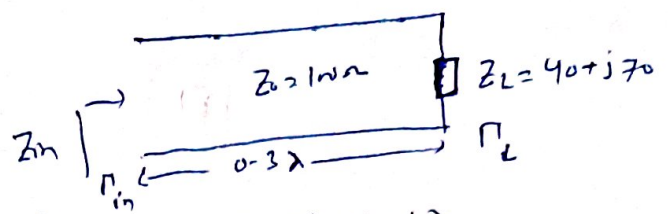the reflection coefficient at the rtp to the line,  
 the input impedance, the SWR on the line  
 and the return loss.



Soln ÷ Steps (Refer the Smith chart attached)

1) First find the normalized impedance. (Because the Smith Chart uses normalized impedance)

Given  $Z_0 = 100 \Omega$   
 $Z_L = 40 + j70 \Omega$

$$Z = \frac{Z_L}{Z_0} = \frac{40 + j70}{100} = 0.4 + j0.7$$

2) Then locate the  $0.4 + j0.7$  point  
 i.e. Find the intersection of  $0.4$  resistance circle and  $0.7$  ~~inductance~~ inductive reactance ( $+jx$ ) circle.

3) Then draw a circle, whose center is the center of Smith Chart ( $1.0$ ), and radius is distance betn center of Smith Chart and the point  $0.4 + j0.7$ . [Use compass to measure the radius]

4) The location intersected by the circle, at the right position of real axis indicates the SWR. [In this example [it is found 3.87]]

5) To find reflection coefficient, use the (at the load)




Example - 9

Join the center with point, which  $[0.14 + j0.7]$  gives reference location of Load ~~on the~~ on the wavelength-towards generator scale.

# The Complete Smith Chart
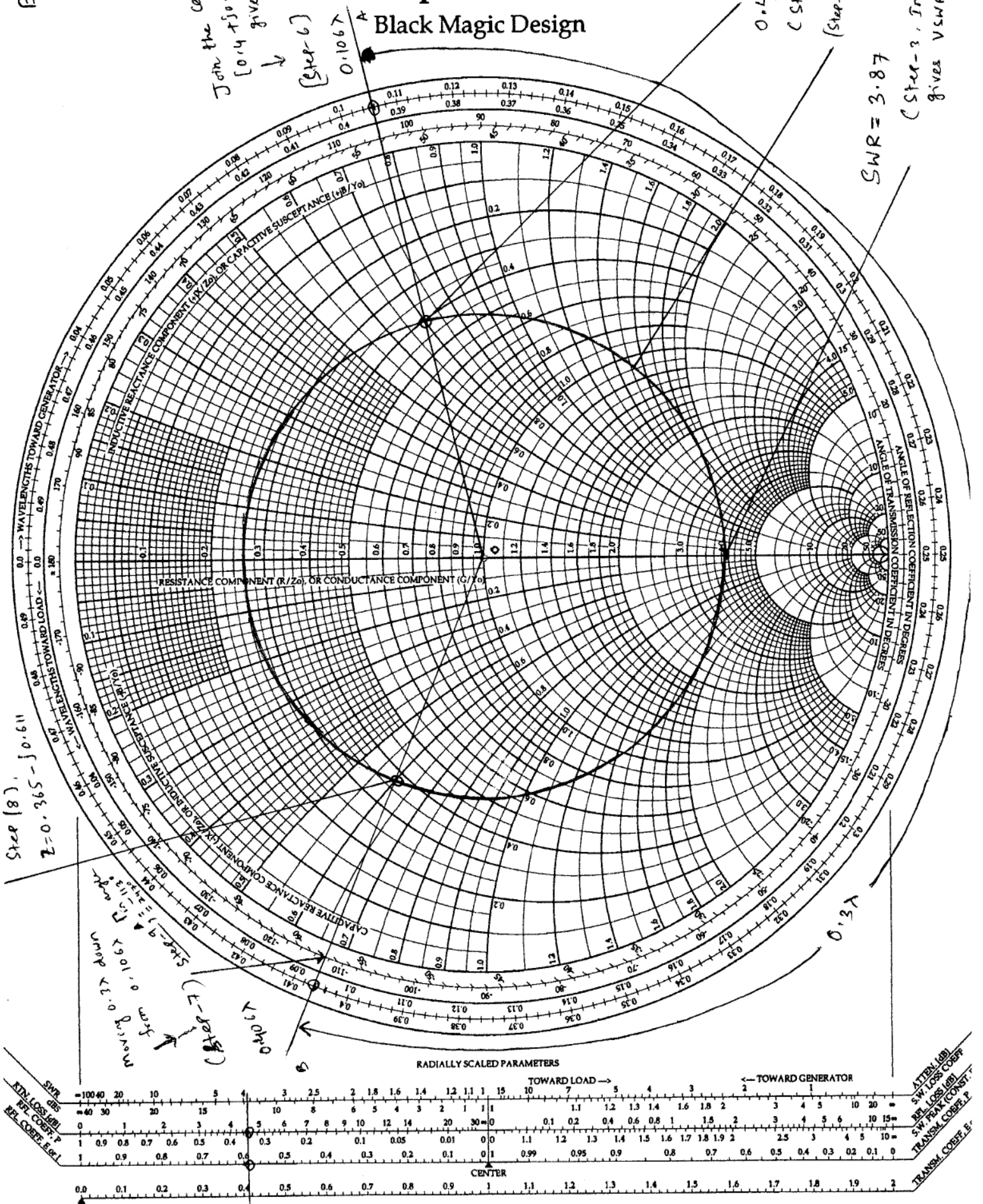
## Black Magic Design


$0.4 + j0.7$   
 (Step-1) Locate the point  
 (Step-2) - Draw the circle  
 (Step-3, Intersection Point gives VSWR)



Step (8),  
 $Z = 0.365 - j0.611$

Step 9  
 $Z = 0.1067$   
 moving 0.31 wavelengths

$V_{SWR} = 3.87$

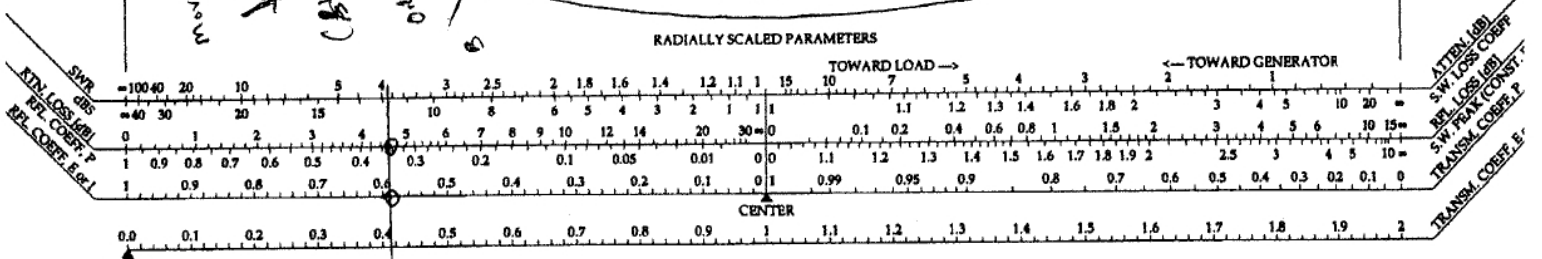

Step (4)  $\Gamma = 0.59$  (Reflection Coefficient For V), Step (3), Return Loss = 4.6 dB

formula

~~$$|\Gamma| = \frac{Z-1}{Z+1}$$~~

$$|\Gamma| = \frac{Z-1}{Z+1} = \frac{3.87-1}{3.87+1} \approx 0.59$$

$$|\Gamma| = 0.59$$

2) In the center of Smith Chart, see the radially scaled parameters. For SWR 3.87, check the corresponding reflection coefficient (E or I) i.e. Voltage reflection coefficient or Current reflection coefficient. [It is found  $|\Gamma| = 0.59$ .]

6) Return loss (dB) = 4.6 dB. [From the scaled parameter]

7) Draw the line between center of Smith Chart and load impedance point  $(0.4 + j0.7)$ .

Extension of this line gives, Reflection coefficient angle  $104^\circ$ ,  $[\Gamma_c = 0.59 \angle 109^\circ]$   
Wavelength towards generator =  $0.106 \lambda$ .

[i.e. reference position of the load on the wavelength-towards-generator scale]

8) Since the transmission line has length  $(0.3 \lambda)$ , moving  $0.3 \lambda$  towards the generator brings us to  $0.406 \lambda$  [ $0.106 + 0.3$ ] on wavelength towards generator (WTG) scale.



9) <sup>With a straight line</sup> Now a join  $0.406\lambda$  point <sup>and</sup> ~~with~~ center of Smith Chart point. The intersection of this line with the circle gives normalized  $Z/P$  impedance. From the chart it is found to be  $0.365$  (Resistance component)  $-j0.611$  (Capacitive reactance) <sup>-ve</sup>

$$Z = 0.365 - j0.611$$

$$\Rightarrow \frac{Z_m}{Z_0} = 0.365 - j0.611$$

$$\Rightarrow Z_m = Z_0 (0.365 - j0.611)$$

$$\Rightarrow Z_m = 100 (0.365 - j0.611)$$

$$\Rightarrow \boxed{Z_m = 36.5 - j61.1} \quad \Omega$$

10) The reflection coefficient at the T/P <sup>8711</sup> has magnitude  $|\Gamma| = 0.59$ . The phase angle can be calculated as follows



(i) Find the intersection of line OB [line joining center of Smith Chart and  $0.406\lambda$ ] with angle of ~~reflection~~ reflection coefficient in degree' scale. It gives angle  $-113^\circ$

$$\text{i.e. } 360^\circ - 113^\circ = 247^\circ$$

$$\Gamma_{in} = 0.59 \angle 247^\circ$$

Ex-10 (Liao) ex-3.5.1: Location determination of voltage maximum and minimum from load.

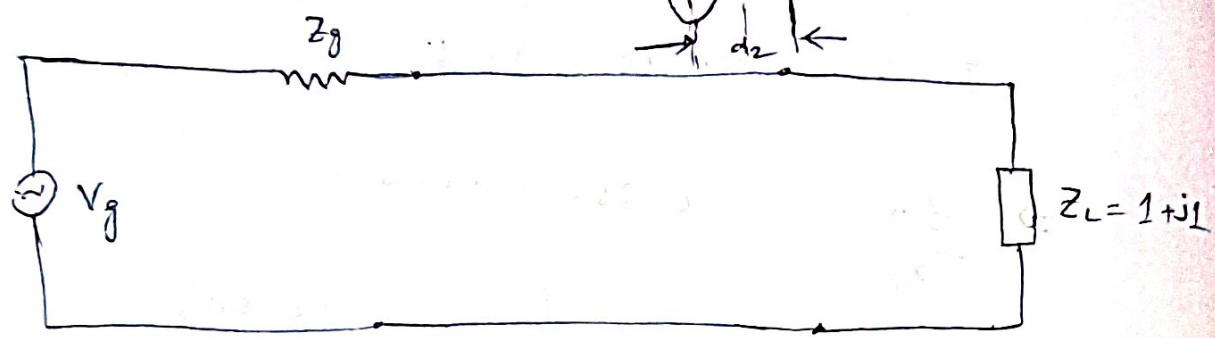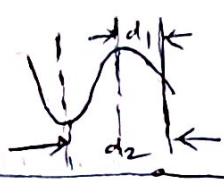Given the normalized load impedance  $Z_L = 1 + j1$  and the operating wavelength  $\lambda = 5 \text{ cm}$ , determine the first  $V_{\text{max}}$ , first  $V_{\text{min}}$  from the load, and the VSWR ( $\rho$ ).



- Ans: 1) Locate  $1 + j1$  point on the Smith chart  
 2) Draw the line between center of Smith chart and load impedance point ( $1 + j1$ ). Extension of this line gives, wavelength towards generator

=  $0.162 \lambda$

We know,  $V_{\text{max}}$  occurs at  $0.25 \lambda$

$\therefore$  Distance from load end,

$d_1 = 0.25 \lambda - 0.162 \lambda = 0.088 \lambda$

$\Rightarrow d_1 = 0.088 (5 \text{ cm})$

$\Rightarrow d_1 = 0.44 \text{ cm}$

$V_{\text{min}}$  occurs at  $0.5 \lambda$





Example-10

# The Complete Smith Chart

## Black Magic Design

0.162λ

VSWR = 2.6

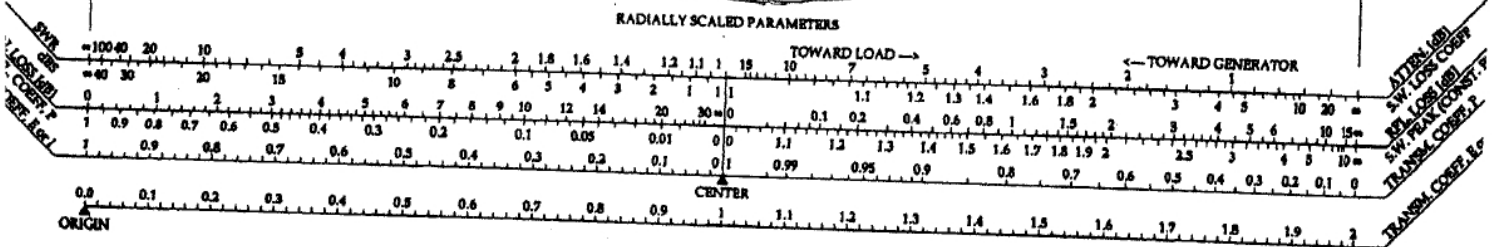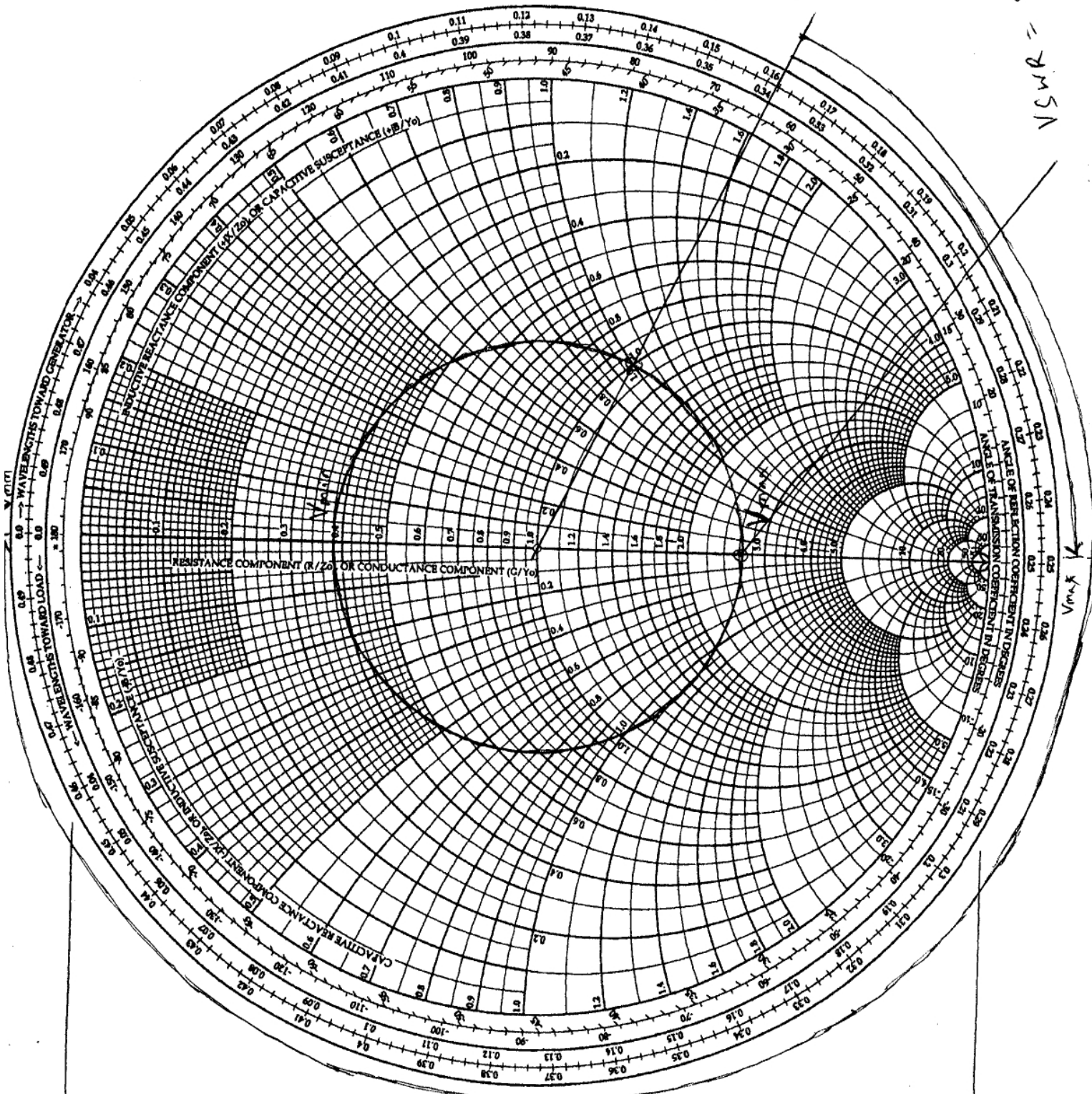

distance of  $V_{min}$  from the load,

$$d_2 = (0.50 - 0.162) \lambda$$

$$d_2 = 0.338 \times (5 \text{ cm})$$

$$\Rightarrow d_2 = 1.69 \text{ cm}$$


5) VSWR can be found out, by the drawing the circle, center at center of Smith Chart and radius is the distance between center and point  $1 + j1$ .

6) As derived in earlier problem, the SWR found to be 2.6, from the Smith Chart.

EX-11 (L100) :- Determination of unknown Impedance

Given that characteristic impedance of line ( $Z_0$ ) is  $50 \Omega$ , SWR  $S = 2$ , when the line is loaded. When the load is shorted, the minima shift  $0.15 \lambda$  towards the load. Determine the load impedance

Ans:

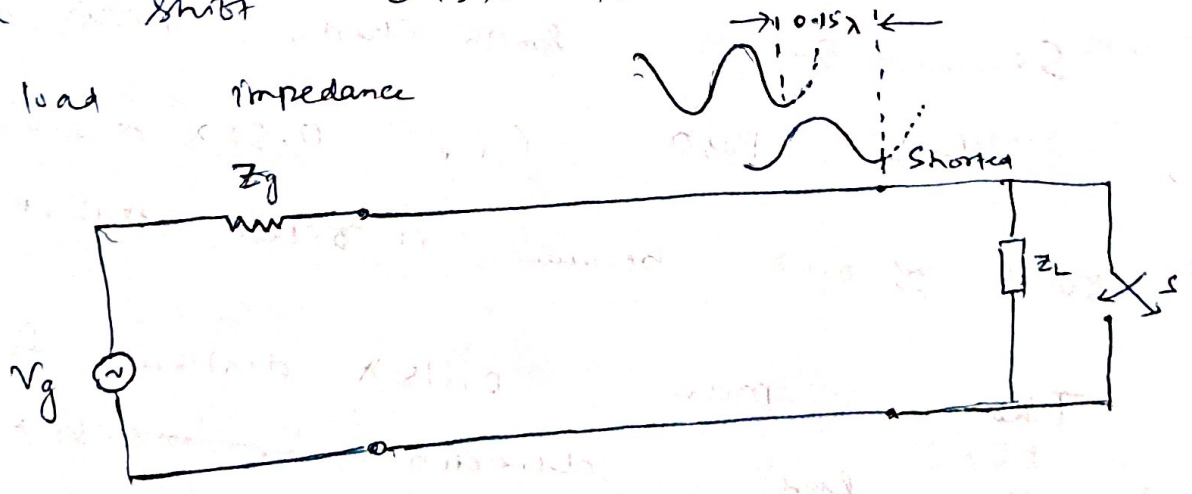




Example - 11

# The Complete Smith Chart

## Black Magic Design

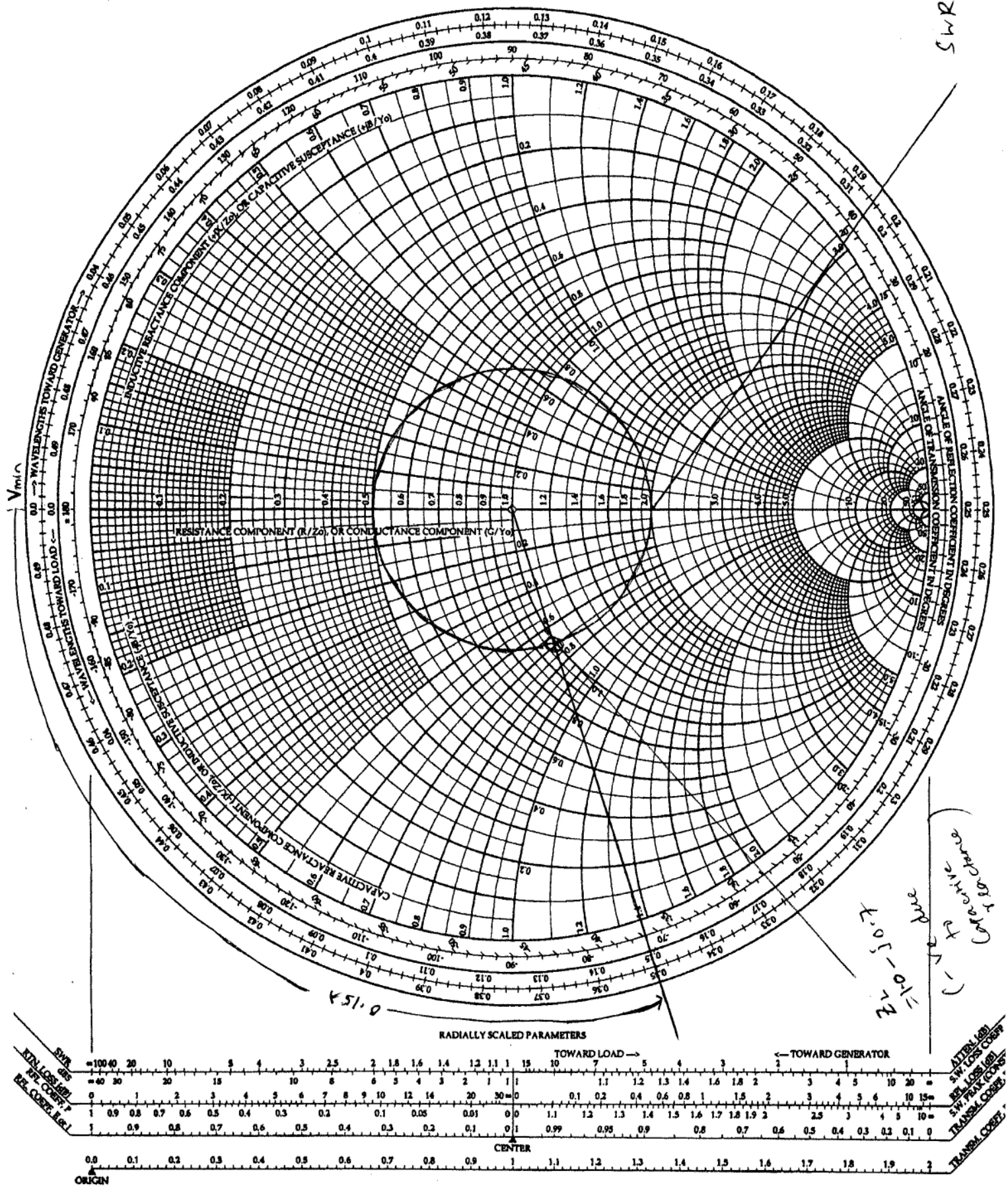


Ans = 1) We know, when the line is shorted, the first voltage minimum occurs at the place of load.

2) When the line is loaded, the voltage minimum occurs at  $0.15\lambda$  from the load.

3) In the last question, load position was known, we have to go to the minimum position. (Towards generator).

4) Now ~~voltage min~~ to find the

6) unknown load position,

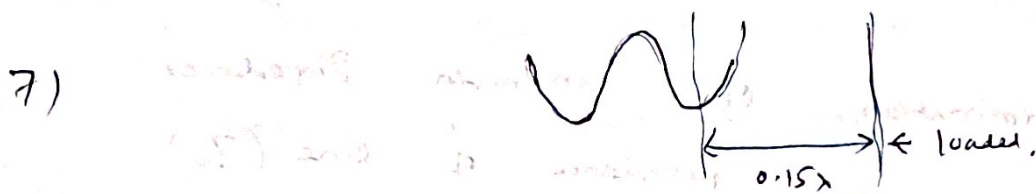

on Ext  
" C  
" r

So we have to move  $0.15\lambda$  towards the load to get the unknown impedance.

5) So in Smith Chart, first locate the  $V_{min}$  pos<sup>n</sup> (i.e.  $0.50\lambda$  or  $0.0\lambda$ )

8) ( $0.50\lambda \approx 0.0\lambda$  because it repeats itself at  $0.5\lambda$ )

6) Then move  $0.15\lambda$  distance from  $V_{min}$  towards load direction. ~~i.e.  $0.35\lambda$~~



7) Join this point  $(0.15\lambda)$  <sup>point on</sup>  $\times$  Wavelength <sup>towards the</sup> load scale)

with center of the Smith chart.

8) Then draw the circle, corresponds to  $V_{SWR} = 2$ , from the center of the Smith chart.

9) The intersection of circle & the line gives the unknown impedance value.

10) From the Smith chart, it is found to be

$$Z = 1.0 - j0.7$$

$$\Rightarrow \frac{Z_L}{Z_0} = 1.0 - j0.7$$

$$\Rightarrow Z_L = 50(1.0 - j0.7) = 50 - j35 \Omega$$

$$\therefore \boxed{Z_L = 50 - j35 \Omega}$$

EX-12 (Pozar) Determination of admittance.

A load of  $Z_L = 100 + j50 \Omega$  terminates a  $50 \Omega$  line. What are the load admittance and  $\Gamma/P$  admittance if the line is  $0.15\lambda$  long.

Ans: 1)  $Z_L = 100 + j50 \Omega$   
 $Z_0 = 50$

Normalized impedance  $Z = \frac{Z_L}{Z_0} = 2 + j1 \Omega$ .


Locate  $(2 + j1)$  point on the Smith chart.

Example-12

0.61 + j0.66

# The Complete Smith Chart

## Black Magic Design

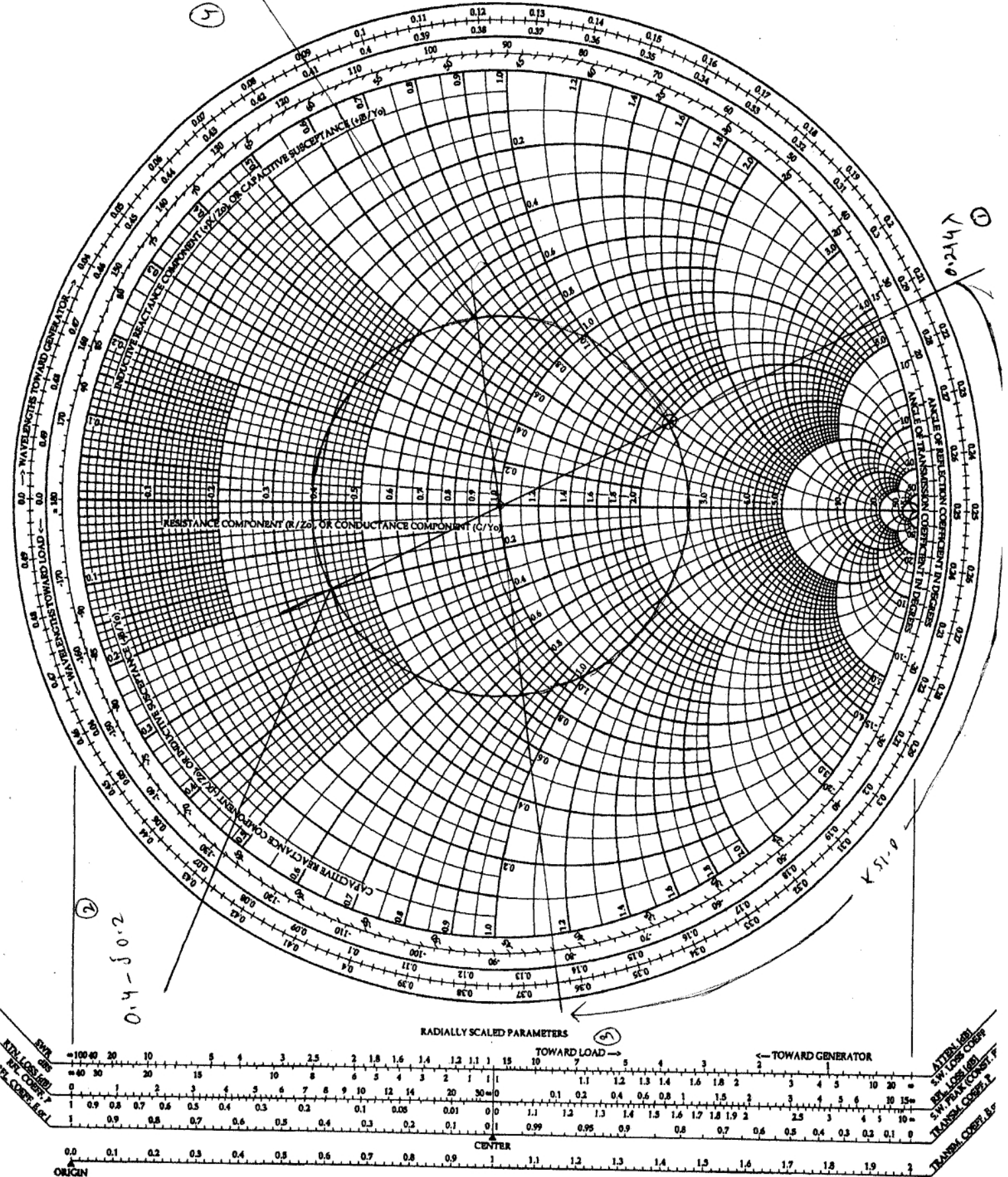



2) Draw a circle, with center at center of Smith Chart & radius is the distance between center and  $(2 + j1)$  point.

3) Draw a straight line between center of Smith Chart and  $(2 + j1)$  point, extend it in both the direction, so that it intersects the circle at another point.

This point is exactly opposite of impedance point, and this is the admittance point.

From the Smith Chart, it was found  
 $y = 0.4 - j0.2$  (-ve due to capacitive reactance)

$$\Rightarrow \frac{Y_L}{Y_0} = 0.4 - j0.2$$

$$\Rightarrow Y_L = Y_0 (0.4 - j0.2)$$

$$\Rightarrow Y_L = \frac{1}{Z_0} (0.4 - j0.2)$$

$$= \frac{0.4 - j0.2}{50}$$

$$Y_L = 0.008 - j0.004 \text{ Siemens}$$

4) To determine i/p admittance, first find i/p impedance. The line joining center & load  $(2 + j1)$  gives the

location of load =  $0.214 \lambda$

Since the line is  $0.15 \lambda$ , moving  $0.15 \lambda$  towards generator gives the r/p impedance.

$$0.214 \lambda + 0.15 \lambda = 0.364 \lambda$$

$\therefore$  Joining  $0.364 \lambda$ , with center ~~at~~  
~~Extend~~ intersect the circle at a point. This  
point ~~is~~ gives r/p impedance. Extending  
the line further intersect the  $\beta$  circle  
on another point. This point gives  
the r/p admittance.

5) From the Smith Chart it gives,

$$y_{in} = 0.61 + j0.66$$

$$\Rightarrow \frac{Y_{in}}{Y_0} = 0.61 + j0.66$$

$$\begin{aligned} \Rightarrow Y_{in} &= Y_0 (0.61 + j0.66) \\ &= \frac{0.61 + j0.66}{Z_0} \\ &= \frac{0.61 + j0.66}{50} \end{aligned}$$

$$\Rightarrow Y_{in} = 0.0122 + j0.0132 \text{ S/men}$$



A  $50\Omega$  lossless transmission line is terminated in a load with impedance  $Z_L = (30 - j60)\Omega$ .

The wavelength =  $5\text{cm}$ ; Find the following

- (i) Reflection Coefficient at the load
- (ii) Standing wave ratio on the line.
- (iii) The position of voltage max<sup>m</sup> nearest the load.
- (iv) The position of current max<sup>m</sup> nearest the load.

Ans:

Given

$Z_0 = 50\Omega$ ,  $Z_L = 30 - j60$ ,  $\lambda = 5\text{cm}$ .

(a) 
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(30 - j60) - (50)}{(30 - j60) + 50}$$

$$\Gamma_L = \frac{-20 - j60}{80 - j60} = \frac{63.24 \angle -108.43}{100 \angle -36.86}$$

$\Gamma_L = 0.6324 \angle -71.57$

$\Gamma_L = 0.199 - j0.59$

$\therefore |\Gamma_L| = 0.6324$

(b) 
$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.6324}{1 - 0.6324} = 4.44$$


(c)

Normalized impedance =  $\frac{Z_L}{Z_0} = \frac{30 - j60}{50} = (0.6 - j1.2)$

Example-13

# The Complete Smith Chart

## Black Magic Design

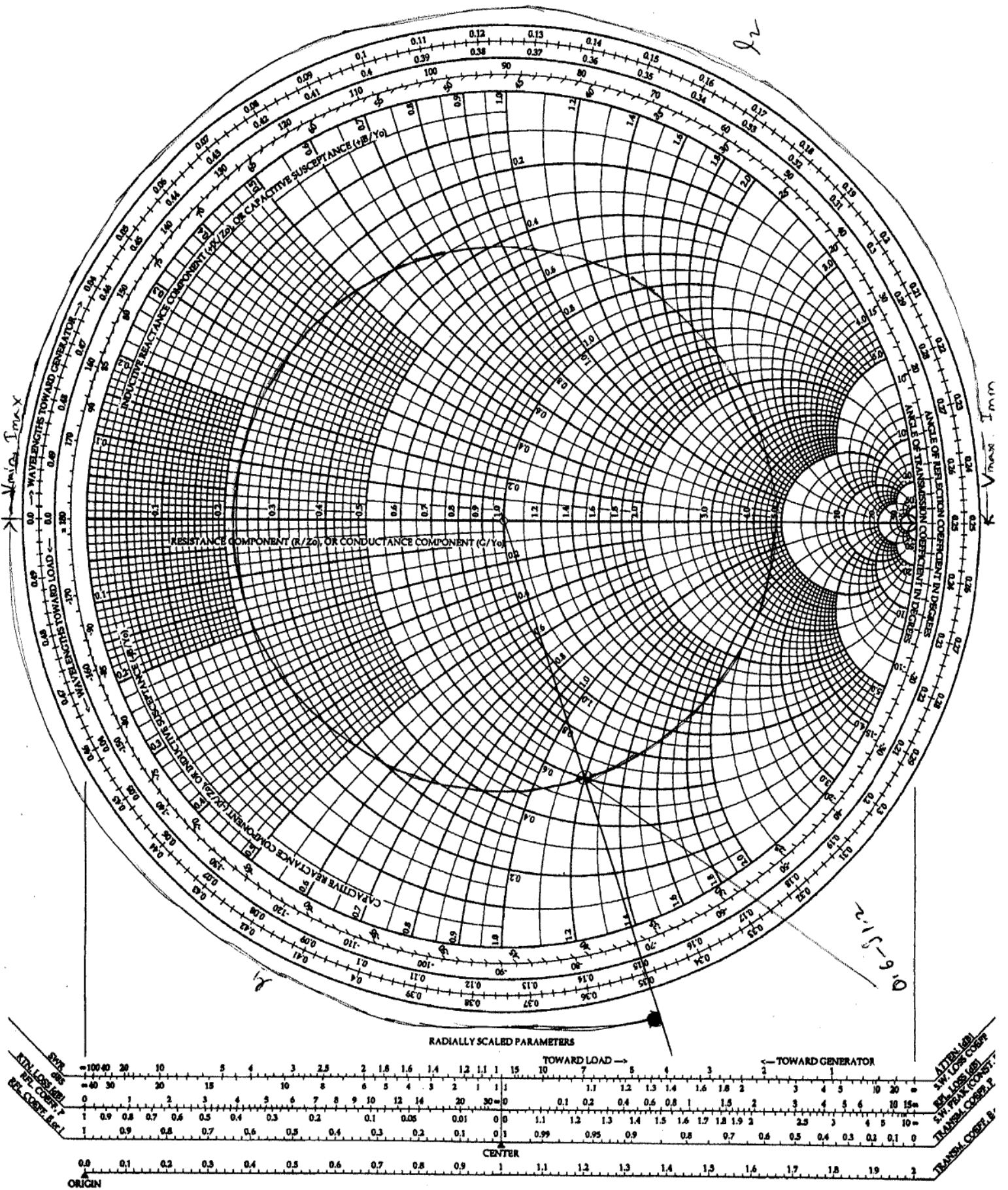



95  
→ Plot the point  $0.6 - j1.2$  on the Smith Chart.

→ Join this point with center of Smith Chart and extend the line, so that we can get the location of load. It is found to be  $0.35\lambda$ .

→  $V_{min}$  or  $I_{max}$  occurs at  $0.5\lambda$ .

$$l_1 = 0.5\lambda - 0.35\lambda = 0.15\lambda = 0.15 \times 5$$

(a) -  $I_{max}$  occurs at  $0.75\text{ cm}$  from the load.  $\left[ \begin{array}{l} l_1 = .75\text{ cm} \\ \text{from the load} \end{array} \right]$

→ (b)  $V_{max}$  or  $I_{min}$  occurs at  $0.25\lambda$

$$l_2 = 0.15\lambda + 0.25\lambda = 0.40\lambda = .4 \times 5 = 2\text{ cm.}$$

∴  $V_{max}$  occurs at  $2\text{ cm}$  from the load.

EX-14 - BPUT - 2012 - 8th Sem.

A low loss coaxial cable of characteristic impedance  $50\Omega$  is terminated on a resistive load of  $75\Omega$ . The peak voltage across the load is found to be  $+30\text{V}$ . Calculate

(i) Reflection coefficient of the load.

(ii) The amplitude of the forward and reflected

Voltage waves.

(iii) Amplitude of the forward and reflected current waves.

(iv) The VSWR

Ans: Given  $Z_0 = 50 \Omega$ ,  $Z_L = 75 \Omega$ ,  $V_0^+ = 30V$

$$(i) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{75 - 50}{75 + 50} = \frac{25}{125} = \frac{1}{5} = 0.2$$

(ii) Amplitude of forward wave =  $30V$ .

$$|\Gamma_L| = \frac{V_0^+}{V_0^+}$$

$$\Rightarrow 0.2 = \frac{V_0^+}{V_0^+}$$

$$\Rightarrow V_0^- = V_0^+ \times 0.2 = 30 \times 0.2 = 6V$$

Reflected wave amplitude  $6V$ .

$$(iii) I_{incident} = \frac{V_{incident}}{Z_0} = \frac{V_0^+}{Z_0} = \frac{30}{50} = 0.6A$$

$$\Gamma_i = -\Gamma_v \quad |\Gamma_i| = |\Gamma_v| = 0.2$$

$$\Gamma_i = \frac{I_{ref}}{I_{inc}} = \frac{I_{ref}}{0.6}$$

$$\Rightarrow \frac{0.2}{0.6} = \frac{I_{ref}}{0.6}$$



$$\Rightarrow 0.2 = \frac{I_{ref}}{0.6}$$

$$\Rightarrow I_{ref} = 0.2 \times 0.6 = 0.12 \text{ Amp.}$$

$$(10) \text{ VSWR } (\gamma) = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.2}{1 - 0.2} = \frac{1.2}{0.8}$$

$$\gamma = \frac{12}{8} = \frac{3}{2} = 1.5 \quad (\text{Ans}).$$

### Impedance Matching :-

When  $Z_0 \neq Z_L$ , we say that the load is mismatched and a reflected wave exists on the line. Thus impedance matching is required

- (i) To transfer maximum power from source to load.
- (ii) To avoid reflected signal in the main line.
- (iii) To avoid ~~loading~~ the loading effect.

A line terminated in the characteristic impedance ( $Z_L = Z_0$ ) has a standing wave ratio ( $\gamma$ ) unity and transmits a given power without reflection. [ $\Gamma_v = 0, \gamma = 1$ ]

There are 2 types of impedance matching

- (a) Quarter-wave transformer ( $\lambda/4$ ) matching
- (b) Stub Matching

Stub matching are again 2 types

- (i) Single stub matching
- (ii) Double stub matching

(a) Quarter Wave transformer matching:-

A transmission line having length  $\frac{1}{4}^{\text{th}}$  (quarter) of wavelength ( $\lambda$ ), of the wave ~~trans~~ propagating through it is called quarter wave transformer.

→ It has a effect of transforming the load impedance in such a manner that ~~the~~ the ~~load~~ load impedance & characteristic impedance match with each other.

→ Consider a transmission line having length 'l'.

It has a characteristic impedance =  $Z_0$ .

Consider a quarter wave transmission line, length  $l' = \frac{\lambda}{4}$

connected in series with the main line.

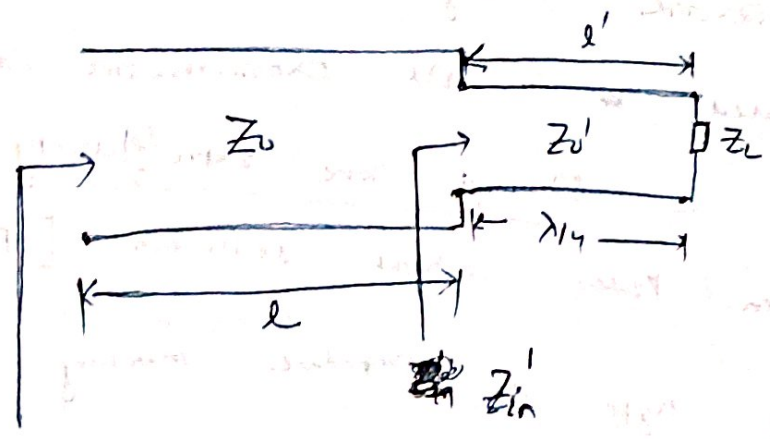


Fig 19:- Load matching using  $\lambda/4$  transformer

We know, Input impedance of a Transmission line is given by

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$



For  $\frac{\lambda}{4}$  line,

$$Z'_{in} = Z_0' \left[ \frac{Z_L + j Z_0' \tan \beta l}{Z_0' + j Z_L \tan \beta l} \right]$$

$$\tan \beta l = \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \tan \frac{\pi}{2} = \infty$$

$$Z'_{in} = Z_0' \left[ \frac{\frac{Z_L}{\tan \beta l} + j Z_0'}{\frac{Z_0'}{\tan \beta l} + j Z_L} \right]$$

$$= Z_0' \left[ \frac{j Z_0'}{j Z_L} \right]$$

$$\Rightarrow Z'_{in} = \frac{(Z_0')^2}{Z_L}$$

$$\Rightarrow (Z_0')^2 = Z'_{in} Z_L$$

$$\Rightarrow Z_0' = \sqrt{Z'_{in} \cdot Z_L} \quad \text{--- (59)}$$

For Impedance matching, characteristic impedance of main transmission line ( $Z_0$ ) should be equal to input impedance ( $Z'_{in}$ ) of  $\frac{\lambda}{4}$  line.

$$\therefore Z_0 = Z'_{in} \quad \text{--- (60)}$$

Putting eq<sup>n</sup> (60) in eq<sup>n</sup> (59), we have

$$\sqrt{Z_0} \cdot Z_0 = \sqrt{Z_0 \cdot Z_L} \quad \text{--- (61)}$$

$$Z_0' = \sqrt{Z_0 Z_L}$$

Where  $Z_0'$ ,  $Z_0$ ,  $Z_L$  all are real. <sup>for example</sup> If  $a$

120Ω load is to be matched to a 75Ω

line the quarter-wave transformer must have

Characteristic impedance  $\sqrt{75 \times 120} = 95\Omega$ . Thus

95Ω quarter-wave transformer will also match

a 75Ω ~~the~~ load to a 120Ω line. (Because

both the cases product  $(75 \times 120)$  is equal)  
or  $(120 \times 75)$ )

Disadvantage :-

→ The reflected wave is eliminated only at the desired wavelength (or freq 'f').

→ There will be reflection at a slightly different wavelength. [ $\lambda \rightarrow \lambda'$ ,  $\lambda$  line won't work]


→ Thus, the main disadvantage of the quarter-wave transformer is that it is a narrow-band or freq-sensitive device. we need  $\lambda'/4$  line.
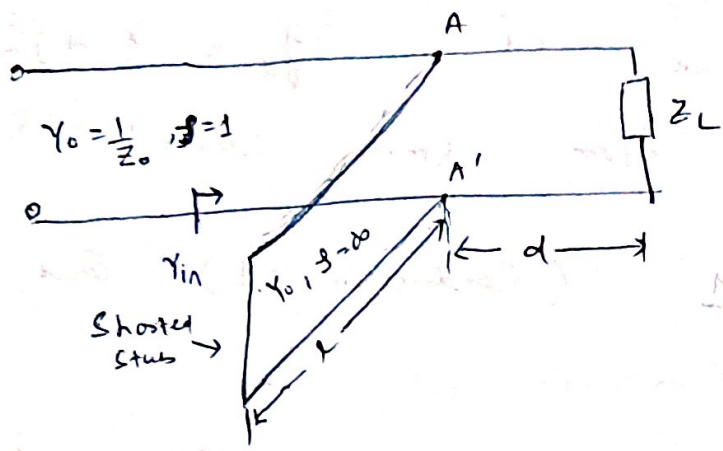
### (b) Stub Matching (Short note)

The major drawback of using ~~quarter-wave~~ quarter-wave transformer as a line matching device is eliminated by using a stub-matching. A Stub consists of an open or shorted section of transmission line.



A length 'l' connected in parallel with main line at some distance 'd' from the load as shown in figure 20.



$Y_L = g_L + j b_L$   
 $Y_L = \text{Admittance}$   
 $g_L = \text{Conductance}$   
 $b_L = \text{Susceptance}$

fig 20:- Matching with single-stub tuner.

Notice that the stub has same characteristic impedance as the main line, although stubs may be designed with different values of  $Z_0$ . It is more difficult to use a series

stub although it is theoretically feasible. An open-circuited stub radiates some energy at high frequencies. Consequently, Shunt Short-circuited parallel stubs are preferred. } 2 more BPUT

(i) Single - Stub Matching

Consider a transmission line having characteristic impedance ( $Z_0$ ) is terminated by a load ( $Z_L$ ) of admittance  $Y_L = g_L + j b_L$ . (Fig 20: above)

$g_L = \text{Conductance}$ ,  $b_L = \text{Susceptance of the load}$

→ The stub of length  $(l)$  which is at a distance 'd' from the load.

→ Let's consider a point on T. line where admittance is  $y_L = 1 + j b_L$  (which is located from Smith chart) (small letter 'L')

where  $g_L = 1$  (Conductance = 1) and susceptance is  $b_L$ .

→ We have to design a stub which offers a susceptance of  $y_S = -j b_L$ , so that total admittance will be  $(y_S + y_L)$

$$y_{in} = (-j b_L) + (1 + j b_L) = 1 \text{ (only conductance part)}$$

Ⓞ 2

∴ Normalized input admittance = 1, which can be visualised on Smith chart.

$$\Rightarrow Z_{in} = 1$$

$$\Rightarrow \frac{Z_{in}}{Z_0} = 1$$

$$\Rightarrow Z_{in} = Z_0$$

We have derived earlier [Page 44 - eqn 32] that

At <sup>matched load,</sup>  $Z_L = Z_0$ ,  $Z_{in} = Z_0$

∴ Here  $Z_L = Z_0 \Rightarrow$  (Matched)



→ So in this way the characteristic admittance and load admittance will be matched to get conductance value (one).

→ Since  $Z_L = Z_0$ ,  $\Gamma$  (Reflection Coefficient) is zero.

~~Ex-14~~ Note: - For Smith Chart Problems

$|Z_{in}|_{max}$  (Maxim s/p impedance)

$$|Z_{in}|_{max} = \frac{V_{max}}{I_{min}} = \frac{I_{max} \cdot Z_0}{I_{min}} = \left(\frac{I_{max}}{I_{min}}\right) \cdot Z_0$$

Similarly,

$$|Z_{in}|_{min} = \frac{V_{min}}{I_{max}} = \frac{I_{min} \cdot Z_0}{I_{max}} = \frac{Z_0}{\left(\frac{I_{max}}{I_{min}}\right)} = \frac{Z_0}{S}$$

Ex-15 :- (Problem on Stub matching)

An antenna (load) with an impedance of  $40 + j30 \Omega$  to be matched to a  $100 \Omega$  lossless line with a shorted stub. Determine

- (a) The required stub admittance
- (b) The distance between stub and the antenna
- (c) The stub length
- (d) The standing wave ratio on each segment of the system.

Solution:- (a) Normalized impedance

$$Z = \frac{Z_L}{Z_0} = \frac{40 + j30}{100} = 0.4 + j0.3$$

1) Locate  $Z$  on the Smith chart. Then draw a circle with center at center of Smith chart & radius = distance bet<sup>n</sup> center &  $0.4 + j0.3$  point.

2) Join center &  $0.4 + j0.3$  point & extend the line in the opposite <sup>of</sup>  $0.4 + j0.3$  point, so the it intersect the circle, to get the admittance. It was found to be  $\underline{1.6 - j1.2}$

Other way

$$Y = \frac{1}{Z} = \frac{Z_0}{Z_L} = \frac{100}{40 + j30} = \frac{100 \times (40 - j30)}{1600 + 900} = \frac{100}{2500} (40 - j30)$$

$$Y = \frac{40}{25} - j \frac{30}{25} = 1.6 - j1.2$$

3) Locate point A & B where the constant ~~resistance~~ resistance circle / conductance circle

( $r=1/g=1$ ) ~~circle~~ intersects the circle we have drawn.

4) At A,  $Y_A = 1 + j1.04$  ,  $Y_S = -j1.04$  (∵  $Y_A + Y_S = 1$ )  
At B,  $Y_B = 1 - j1.04$  ,  $Y_S = +j1.04$  (∵  $Y_B + Y_S = 1$ )

∴ The required stub admittance

$$Y_S = \frac{Y_S}{Y_0} \Rightarrow Y_S = Y_S \cdot Y_0 = \pm j1.04 \times \left(\frac{1}{100}\right) = \pm j10.4 \text{ mS}$$






5) 2 Stubs can be possible,  
 at A,  $\rightarrow -j10.4 \text{ mS}$   
 B,  $\rightarrow +j10.4 \text{ mS}$

6) To determine Stub position

If we choose stub at A

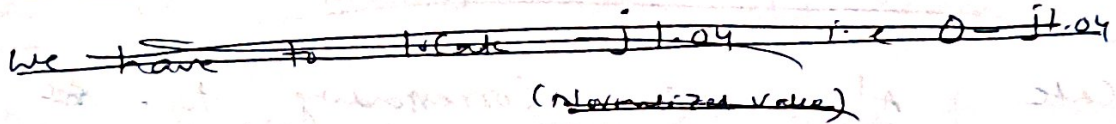

Position of stub (Admittance)  $1 + j10.4 = \underline{0.372\lambda}$  (Wavelength towards generator scale)

Position of load (Admittance)  $\underline{0.5\lambda}$

Reference

Position of A =  $0.163\lambda$  (Wavelength towards generator scale)  
 (Admittance  $1 + j10.4$ )

Reference position of load (Admittance  $1.6 - j1.2$ ) =  $0.304\lambda$

Distance =  $\int (0.5 - 0.304) + 0.163 \lambda$

=  $(0.196 + 0.163) \lambda$

=  $0.359 \lambda$

$\approx 0.36 \lambda$

If we choose stub at B

Reference posn of B =  $0.337 \lambda$

" " " Load =  $0.304 \lambda$

Distance =  $0.033 \lambda$



$\therefore$  If Choose stub at A, stub pos<sup>n</sup> is  $0.36\lambda$  from load.

If Choose stub at B, stub pos<sup>n</sup> is  $0.033\lambda$  from load.

(c) To find stub length

Locate  $A'$  &  $B'$  corresponding to stub admittance  $-j1.04$  &  $+j1.04$

Determine stub length (Distance from  $0.25\lambda$  point or  $Y = \infty$  point or short cut point)

Stub length at A = Location of  $A' - 0.25\lambda$   $\rightarrow (-j1.04)$

$$= 0.372 - 0.25$$

$$= 0.122\lambda$$

Stub length at B =  $\rightarrow (+j1.04)$   $\left[ \begin{array}{l} \text{Length of} \\ \text{Location of } B' \text{ from } 0.25\lambda \end{array} \right]$  point

$$= [(0.5 - 0.25) + 0.128] \lambda$$

$$= [0.25 + 0.128] \lambda$$

Stub length at B =  $0.378\lambda$

(d) Standing wave ratio bet<sup>n</sup> load to stub = 2.8  $\left[ \begin{array}{l} \text{As shown} \\ \text{in} \\ \text{chart} \end{array} \right]$

" " " " from stub towards generator = 1

(Because matching is done)

and  $V_{SWR} = \infty$  along the stub because stub is short circuited.

Ex-16 (Home work) [ Here stub admittance & line admittance are not equal ]  
(Refer the Smith chart attached)  $= Y_0$

A T-L having  $Z_L = 75 - j150 \Omega$  and  $Z_0 = 50 \Omega$  is matched with stub having  $Z_0' = 100 \Omega$ .

Find the location & length of stubs for matching.

Ans = 1)  $Z = \frac{Z_L}{Z_0} = \frac{75 - j150}{50} = 1.5 - j3$   
 $Y = \frac{1}{1.5 - j3} = \frac{1.5 + j3}{(1.5)^2 + 3^2} = \frac{1.5 + j3}{2.25 + 9} = 0.13 + j0.26$

or first locate  $Z$ , then extend the line in opposite direction to get 'y'.

2) Draw the circle with center at center of Smith chart & radius = distance bet<sup>n</sup> center & Z point or y point.

3) Check where the constant circle  $r=1 / g=1$  intersect the circle we have drawn. It will intersect at two points A & B. Lets take the point A.  $[ 1 + j2.5 ]$

4) Location of stub =  $0.196 \lambda - 0.042 \lambda = 0.154 \lambda$  from load.



Example - 16

# The Complete Smith Chart


## Black Magic Design

Step 3 - Location of  $S_{11}$   
(0.196 - j0.042)  $\lambda$


Step 2 -  $A(1 + j2.5)$

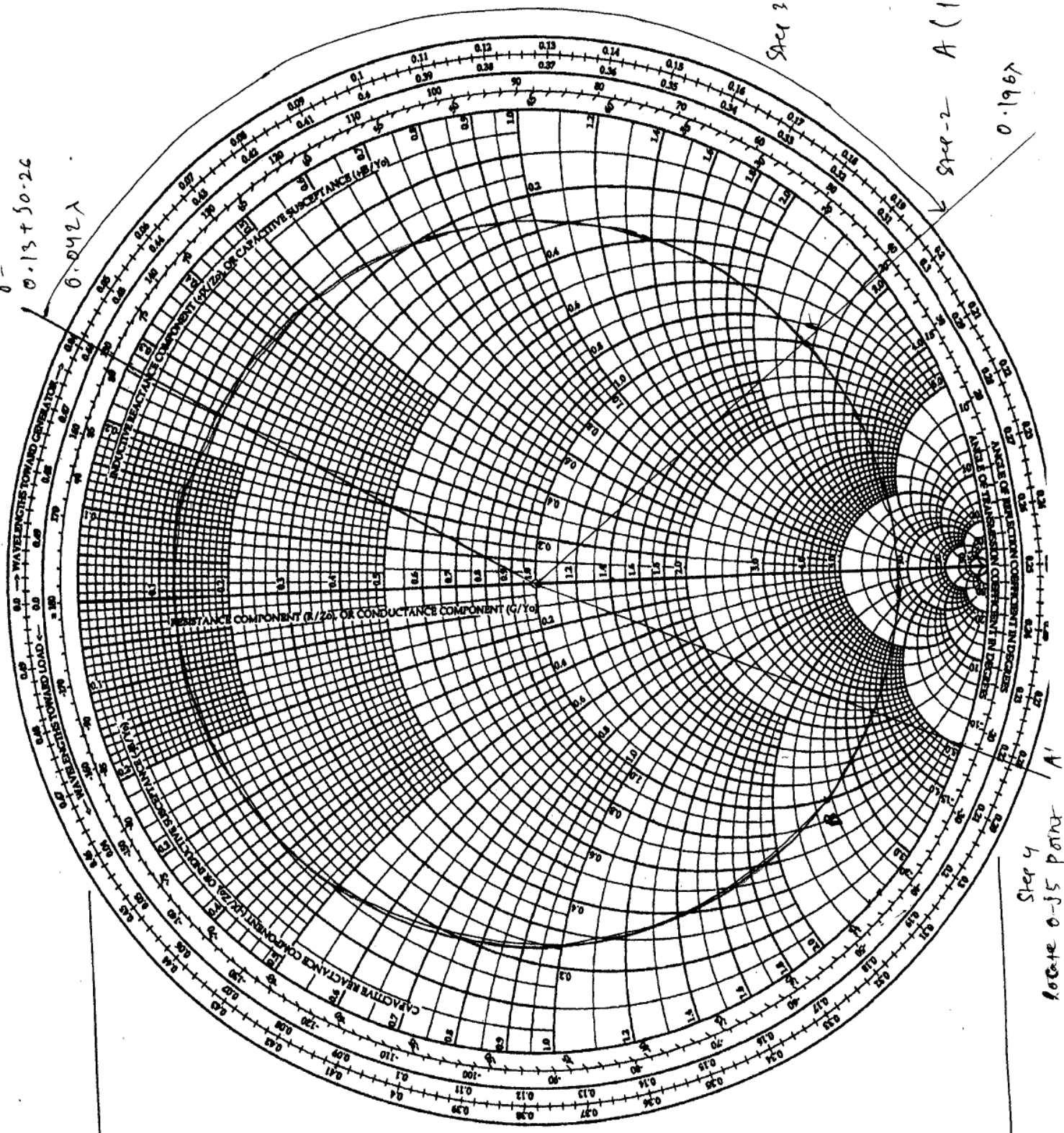0.196  $\lambda$

Step 1 -  $Y = 0.13 + j0.26$   
0.042  $\lambda$



Step 4  
locate 0.196 point A'

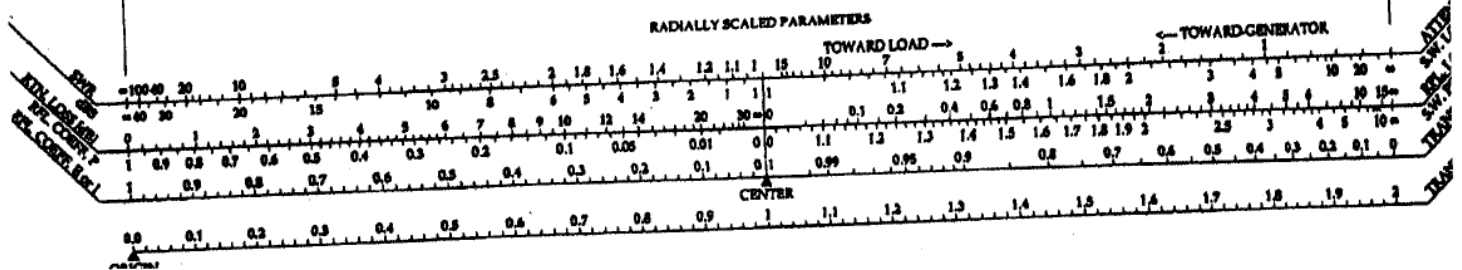

57) Stub should have admittance =  ~~$j0.25$~~

$$Y_s = -j2.5$$

So that net admittance,  $= (1 + j0.25) - j2.5 = 1$ .

6) ~~Locate  $0 - j2.5$~~

Since characteristic impedance of T.L  $\neq$  characteristic impedance of Stub,

$$Y_s = -j2.5 \times \frac{Z_s}{Z_0} = -j2.5 \times \frac{100}{50} = -j5.0$$

1st case: -

<del><math>Z_0 = 50</math></del>	for $Z_0 = 50$	, $Y_s = -j2.5$
$Z_0 = 1$	=	$Y_s = -j2.5$
$Z_0 = 100$	, $Y_s = -j5.0$	

$= -j2.5 \times 100 / 50$

77) Now locate  $0 - j5$  point.

87) Find the length of the stub

= Distance from  $0.25 \lambda$  point [Short circuit point]

$$= 0.281 - 0.25$$

$$= 0.031 \lambda$$

97) Stub is at  $0.154 \lambda$  distance from load having length  $0.031 \lambda$ .