

BJT & JFET Frequency Response

1) Consider the following mathematical eqⁿ,

$$a = b^x$$

$$\Rightarrow \boxed{x = \log_b a}$$

2) Common logarithm $x = \log_{10} a$, base = 10

Natural logarithm $y = \log_e a = \ln a$, base = e

3) $\ln a = 2.3 \log_{10} a$

Proof:-

$$\log_a b = \frac{\log_{10} b}{\log_{10} a}$$

$$\therefore \log_e a = \frac{\log_{10} a}{\log_{10} e} = \frac{\log_{10} a}{\log_{10} 2.718} = \frac{\log_{10} a}{0.434}$$

$$\Rightarrow \log_e a = 2.3 \log_{10} a$$

$$\Rightarrow \boxed{\ln a = 2.3 \log_{10} a}$$

4) $\log_{10} 1 = 0$, $\log_{10} 10 = 1$, $\log_{10} 100 = 2$, $\log_{10} 1000 = 3$, etc

Decibel :-

The background surrounding the term decibel has its origin in the established fact that power and audio levels are related on a logarithmic basis.

That is, an increase in power level, say 4 to 16 watt, does not result in an audio level

Increase by a factor of $\frac{16}{4} = 4$. It will increase ³⁹⁵ by a factor 2, i.e.

$$\log_4 16 = 2$$

$$\text{or } \frac{\log 16}{\log 4} = \log_4 16 = 2$$

For standardization, the bel (B) [derived from surname of Alexander Graham Bell] is defined by

the following eqⁿ to relate power levels P_1 & P_2 :

$$G = \log_{10} \frac{P_2}{P_1} \text{ Bel} \quad \text{--- (1)}$$

For practical purpose, decibel (dB) is defined such that 10 decibel = 1 Bel.

$$\therefore G_{dB} = 10 \log_{10} \frac{P_2}{P_1} \text{ dB} \quad \text{--- (2)}$$

QNT → 2mark

1) Difference between dBm & dBW

Ans ÷ The decibel rating is a measure of the difference between two power levels. For a specified terminal (output) power P_2 there must be a reference power level (P_1). When the 1-mW level is employed as the reference level, the decibel symbol appears as dBm.

$$G_{dBm} = 10 \log_{10} \frac{P_2}{1 \text{ mW}} \text{ dBm}$$

Similarly, if 1 - MW (Micro Watt) is employed as reference level, the decibel symbol appears as **dBμ**.

$$G_{dB\mu} = 10 \log_{10} \frac{P_2}{1 \mu W}, \text{ dB}\mu$$

$$\begin{aligned} \rightarrow G_{dB} &= 10 \log \frac{P_2}{P_1} \\ &= 10 \log \left(\frac{\frac{V_2^2}{R}}{\frac{V_1^2}{R}} \right) \\ &= 10 \log \frac{V_2^2}{V_1^2} \\ &= 10 \log \left(\frac{V_2}{V_1} \right)^2 \end{aligned}$$

$$\begin{aligned} 1 \text{ Watt} &= 30 \text{ dBm} = 60 \text{ dB}\mu \\ G_{dBm} &= 10 \log \left(\frac{1}{10^{-3} \text{ W}} \right) = 30 \text{ dBm} \\ G_{dB\mu} &= 10 \log \left(\frac{1}{10^{-6} \text{ W}} \right) = 60 \text{ dB}\mu \end{aligned}$$

$$G_{dB} = 20 \log \frac{V_2}{V_1}, \text{ dB}$$

→ If magnitude of overall voltage gain of a cascaded system is given by

$$|A_{VT}| = |A_{V1}| |A_{V2}| \dots |A_{Vn}|$$

In dB,

$$20 \log |A_{VT}| = 20 \log |A_{V1}| + 20 \log |A_{V2}| + \dots + 20 \log |A_{Vn}|$$

$$\Rightarrow G_{dB \text{ Total}} = (G_{dB1} + G_{dB2} + \dots + G_{dBn}) \text{ dB}$$

General Freq Considerations


The freq of the applied signal can have a pronounced effect on the response of a single-stage or multistage n/w. All the analysis done before has been for midfreq spectrum.

At low frequency, the coupling and bypass capacitors can no longer be replaced by the short-circuit approximation because of the increase in reactance of these elements.


The freq-dependent parameters of the small-signal equivalent circuits and stray capacitive elements associated with active device and the n/w will limit the high-freq response of the system.

An increase in the number of stages of a cascaded system will also limit both the high and low freq response.

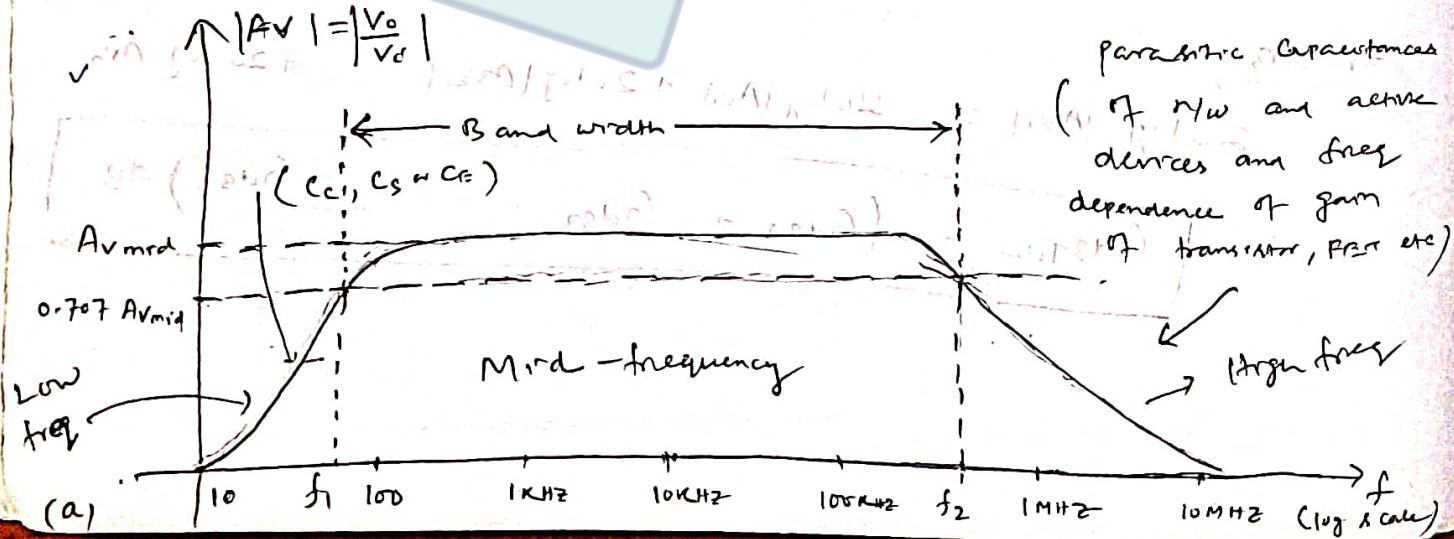
The magnitude of the gain response curves of an RC-coupled, direct-coupled and transformer-coupled amplifier systems are provided in fig 1, a, b, c. The primary reason for the drop in



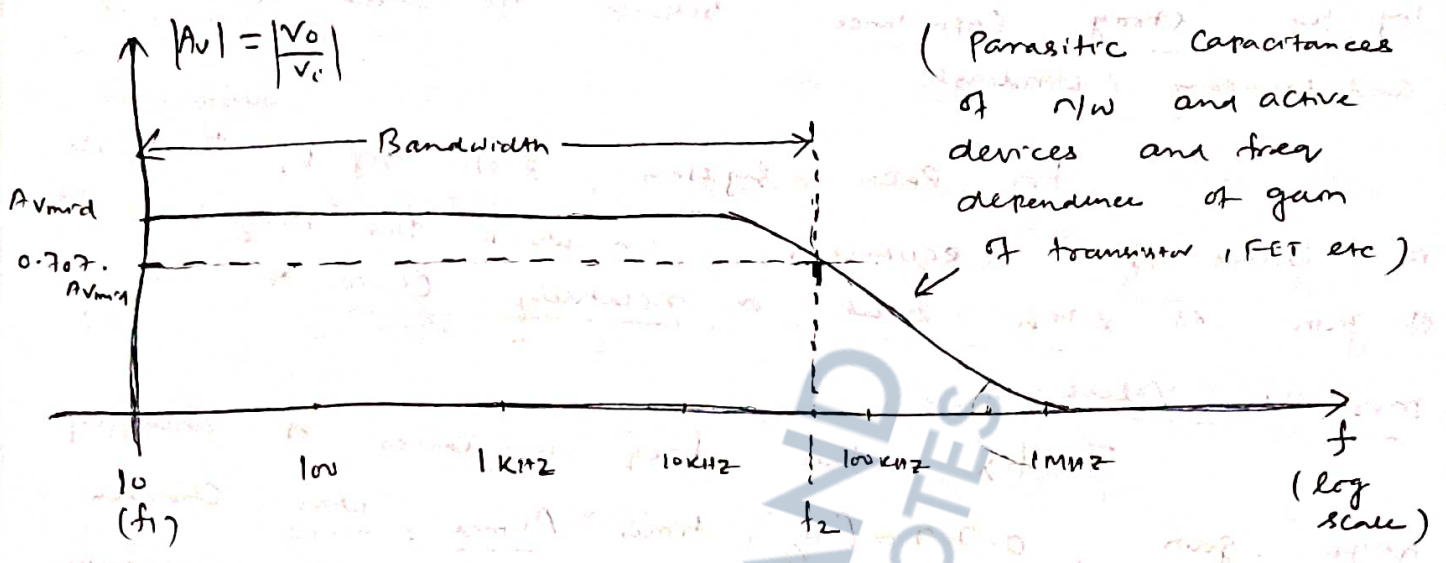gain at low & high freq have been indicated within the parenthesis.



(b)

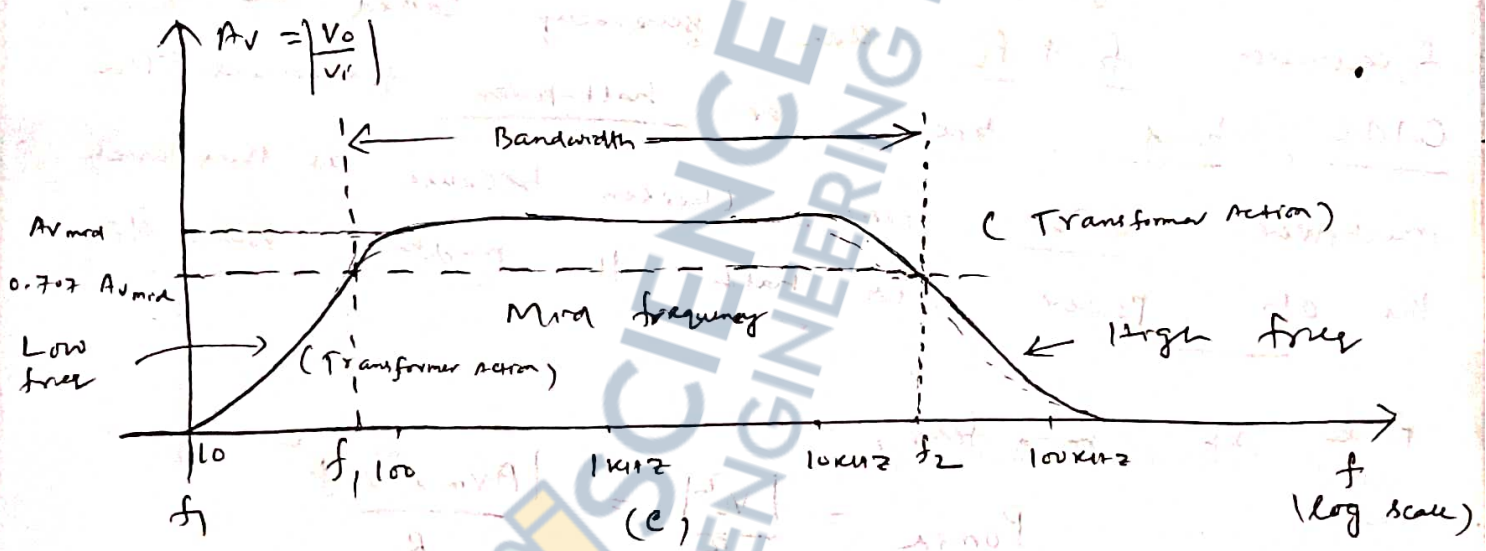

(c)

Fig 1 :- Gain versus freq : (a) RC-Coupled amplifier
(b) Direct-Coupled amplifier (c) Transformer-Coupled amplifier

Note :- Drop in gain for transformer-coupled system :-

At low freq, ($X_L = 2\pi fL$), due to shorting effect (across the i/p terminals of the transformer) of magnetizing inductance reactance. The gain must be zero at $f=0$, since at this point there is no longer change in flux established through the core to induce a secondary or o/p

Voltage.

The High freq response is controlled primarily by the stray capacitance between the turns of primary and secondary windings.

For each system, β of fig 1, there is a band of frequencies in which the magnitude of gain is either equal or relatively close to the midband value.

To fix the freq boundaries of relatively high gain, 0.707 or $(\frac{1}{\sqrt{2}})$ times A_{Vmid} was chosen to be gain at the cutoff levels. The corresponding frequencies f_1 & f_2 are generally called the corner, cutoff, band, break or half-power frequencies. The multiplier 0.707 was chosen because at this level the o/p power is half the midband power o/p.

~~f=2~~ At mid freq,

$$P_{omid} = \frac{|V_o|^2}{R_o} = \frac{|A_{Vmid} \cdot V_i|^2}{R_o}$$

half-power

At ~~mid~~ frequencies,

$$P_{OHF} = \frac{|0.707 A_{Vmid} \cdot V_i|^2}{R_o} = 0.5 \frac{|A_{Vmid} \cdot V_i|^2}{R_o}$$

$$\Rightarrow \boxed{P_{OHF} = 0.5 P_{omid}}$$

→ The Bandwidth or passband of each system is determined by f_1 & f_2 , i.e

$$\text{bandwidth (BW)} = f_2 - f_1$$

Normalized Plot: -

Previously Plot is A_v Vs freq

In normalized plot, Plot is $\frac{A_v}{A_{v_{mid}}}$ Vs freq.

When $A_v = A_{v_{mid}}$, i.e. at mid band freq, the

value of $\frac{A_v}{A_{v_{mid}}} = 1$. At half-power freq,

the resulting level is $0.707 \approx \frac{1}{\sqrt{2}}$.

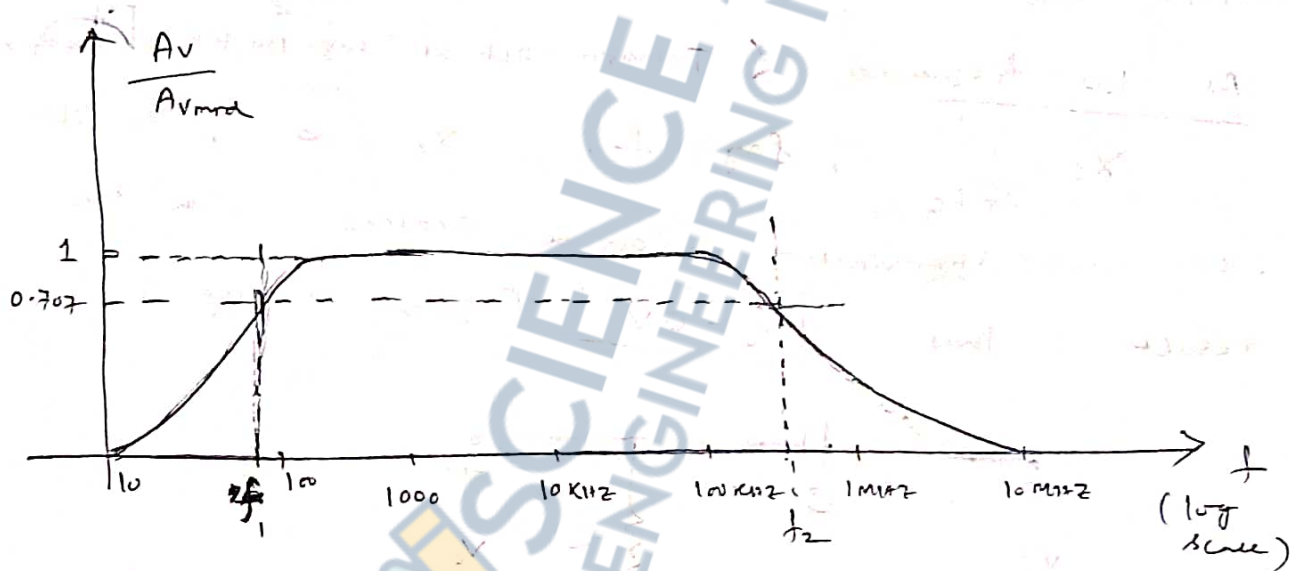


Fig 2:- Normalized gain vs freq. plot

dB Plot: -

$$\left. \frac{A_v}{A_{v_{mid}}} \right|_{dB} = 20 \log_{10} \frac{A_v}{A_{v_{mid}}}$$

At $A_v = A_{v_{mid}}$, $20 \log 1 = 0$ dB
 At cutoff freq, $20 \log \frac{1}{\sqrt{2}} = -3$ dB.

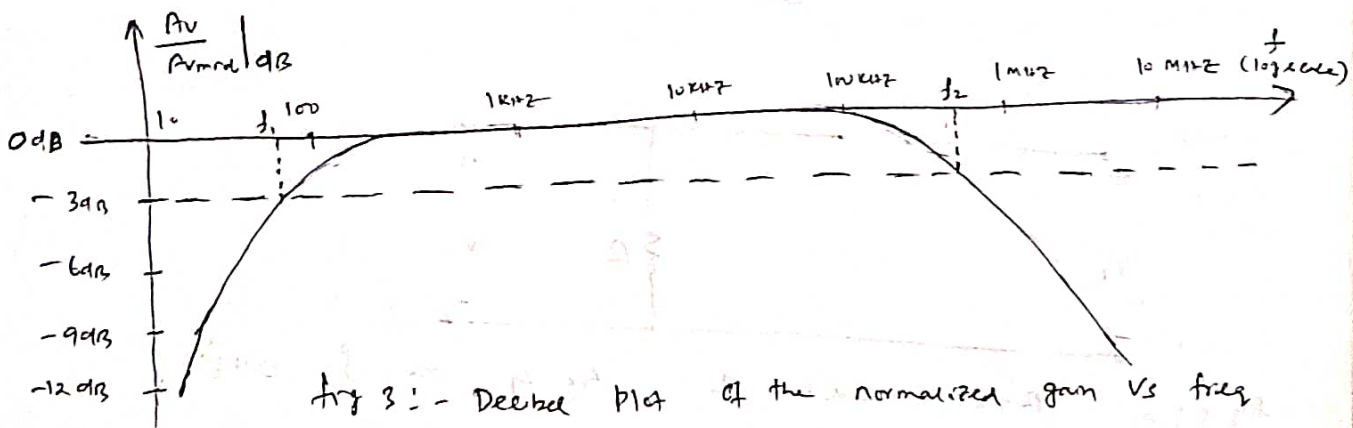


Fig 3:- Decibel plot of the normalized gain vs freq

Low-freq Analysis - Bode Plot

In the low-freq region of the single-stage BJT or PNP amplifier, it is the R-C combination formed by the resistive parameters that determine the cutoff frequencies.

An R-C n/w similar to fig 4 (given below) can be established for each capacitance element and the freq at which off voltage drops to 0.707 of its maxm value determined.

At low frequencies, \angle Transistor act as high pass filter

$X_C = \frac{1}{2\pi f C}$, say $f=0$, $X_C = \infty$, an open

Ckt approximation can be applied, with the result that $V_o = 0V$. [shown in fig 5]

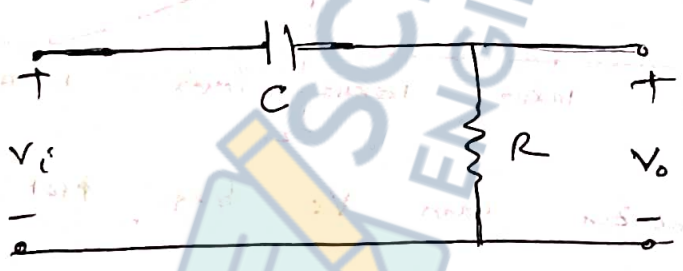


fig: 4:- RC combination that will define a low cutoff frequency.

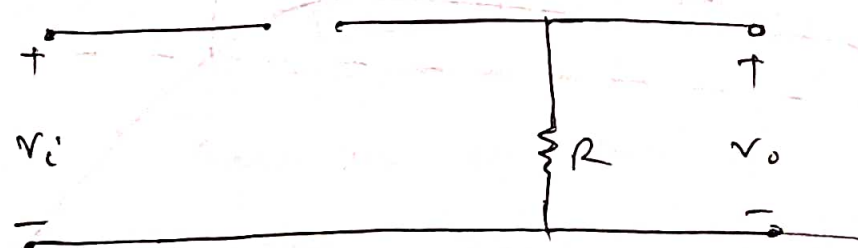


fig 5:- R-C ckt of fig 4 at $f = 0Hz$

At ^{very} high freq

$X_c = \frac{1}{2\pi f c} \approx 0 \Omega$ and the short-circuit equivalent can be substituted for capacitor as shown in fig 6. The result is that $V_o = V_i$ at high frequencies.



Fig 6:- RC equivalent of fig 4 at very high frequencies

Between the 2 extremes, the ratio $A_v = \frac{V_o}{V_i}$ is shown in fig 7. As the freq increases, the capacitive reactance decreases and more of the i/p voltage appears across the o/p terminals.

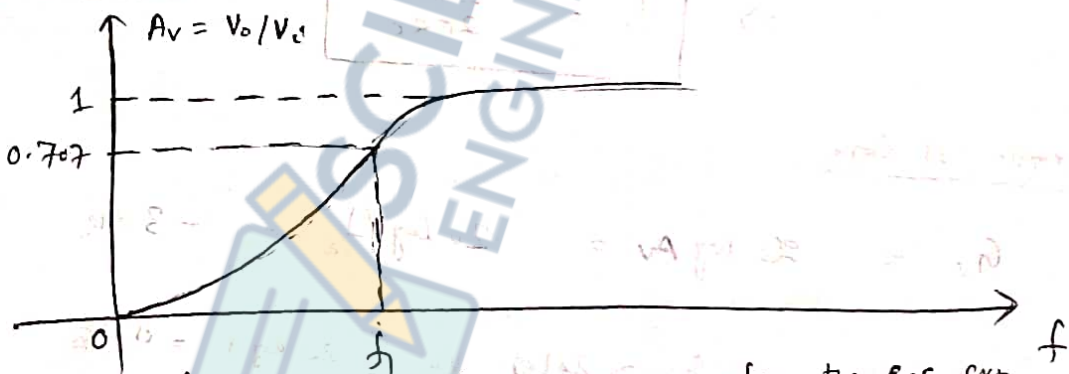


Fig 8:- Low freq response for the RC circuit

The o/p & i/p voltage are related by the voltage divider rule in the following manner; [fig 4]

$$V_o = \frac{V_i \cdot R}{R - jX_c} \quad \text{--- (1)}$$

$$|V_o| = \frac{R V_i}{\sqrt{R^2 + X_c^2}}$$

$$\begin{aligned} \therefore X_c &= \frac{1}{j\omega c} \\ &= \frac{-j}{\omega c} \\ &= -jX_c \end{aligned}$$

Let's take $X_c = \frac{1}{\omega c}$

When $X_c = R$,

$$V_o = \frac{R v_i}{\sqrt{R^2 + R^2}} = \frac{R v_i}{\sqrt{2R}} = \frac{v_i}{\sqrt{2}}$$

$$\Rightarrow |A_v| = \frac{V_o}{v_i} = \frac{1}{\sqrt{2}} = 0.707$$

So, the freq at which $X_c = R$, the o/p will be 70.7% of the i/p.

The freq at which this occurs is determined from,

$$X_c = R$$

$$\Rightarrow \frac{1}{2\pi f_c} = R$$

$$\Rightarrow f_c = \frac{1}{2\pi RC} \quad \text{--- (2)}$$

Interms of logs,

$$G_v = 20 \log A_v = 20 \log \left(\frac{1}{\sqrt{2}}\right) = -3 \text{ dB}$$

$$\text{When } V_o = V_i, \quad G_v = 20 \log \frac{V_o}{V_i} = 20 \log 1 = 0 \text{ dB}$$

\therefore The freq at which there is a 3dB drop from midband level or the freq at which o/p is 70.7% or $\frac{1}{\sqrt{2}}$ of i/p is known as -3dB freq or Cutoff freq.

$$A_v = \frac{V_o}{V_i} = \frac{R}{R - j\omega C} \quad [\text{from eqn (1), last page}]$$

$$= \frac{1}{1 - j\left(\frac{\omega C}{R}\right)}$$

$$= \frac{1}{1 - j\left(\frac{1}{2\pi fRC}\right)}$$

$$= \frac{1}{1 - j\left(\frac{1}{2\pi fRC}\right)}$$

$$A_v = \frac{1}{1 - j\left(\frac{f_1}{f}\right)} \quad \text{--- (3)} \quad \left[\begin{array}{l} \because f_1 = \frac{1}{2\pi RC} \\ \text{eqn (2)} \end{array} \right]$$

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}} \angle \tan^{-1}\left(\frac{f_1}{f}\right)$$

Magnitude of A_v
Phase by which V_o leads V_i

$\left[\begin{array}{l} \because \tan^{-1}\left(-\frac{1}{x}\right) \\ = \tan^{-1}\left(\frac{1}{x}\right) \end{array} \right]$

For the magnitude,
when $f = f_1$,

$$|A_v| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707 = -3 \text{ dB}$$

In logarithmic form, the gain in dB,

$$A_v(\text{dB}) = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}} \quad \text{--- (4)}$$

$$\therefore (A_v)_{\text{dB}} = -20 \log_{10} \left[1 + \left(\frac{f_1}{f}\right)^2 \right]^{\frac{1}{2}}$$

$$= -\frac{1}{2} \times 20 \log_{10} \left[1 + \left(\frac{f_1}{f}\right)^2 \right]$$

$$(A_v)_{\text{dB}} = -10 \log_{10} \left[1 + \left(\frac{f_1}{f}\right)^2 \right] \quad \text{--- (5)}$$

For frequencies, where $f \ll f_1$ or $(\frac{f_1}{f}) \gg 1$,
Then eqⁿ (5), can be approximated as,

$$(A_v)_{dB} = -10 \log_{10} \left(\frac{f_1}{f}\right)^2$$

finally,

$(A_v)_{dB} = -20 \log_{10} \frac{f_1}{f}$

(6)
for $f \ll f_1$

At $f = f_1$, $\frac{f_1}{f} = 1$, and $(A_v)_{dB} = -20 \log_{10} 1 = 0 \text{ dB}$

At $f = \frac{f_1}{2}$, $\frac{f_1}{f} = 2$, $(A_v)_{dB} = -20 \log_{10} 2 \approx -6 \text{ dB}$

At $f = \frac{f_1}{4}$, $\frac{f_1}{f} = 4$, $(A_v)_{dB} = -20 \log_{10} 4 \approx -12 \text{ dB}$

At $f = \frac{f_1}{10}$, $\frac{f_1}{f} = 10$, $(A_v)_{dB} = -20 \log_{10} 10 = -20 \text{ dB}$

Plot of these points as indicated in fig 9 from $0.1 f_1$ to f_1 . This results in a straight line when plotted against a log scale. A straight line is also drawn for the condition of 0dB for $f \gg f_1$.

$$\therefore (A_v)_{dB} = -20 \log \left[1 + \left(\frac{f_1}{f}\right)^2 \right]^{\frac{1}{2}}$$

$$\text{At } f \gg f_1, \quad \frac{f_1}{f} \approx 0$$

$$= -20 \log 1$$

$$\approx 0$$

→ ∴ For $f \ll f_1$, it is a sloped line.
for $f \gg f_1$, it is 0dB. [Asymptotes]

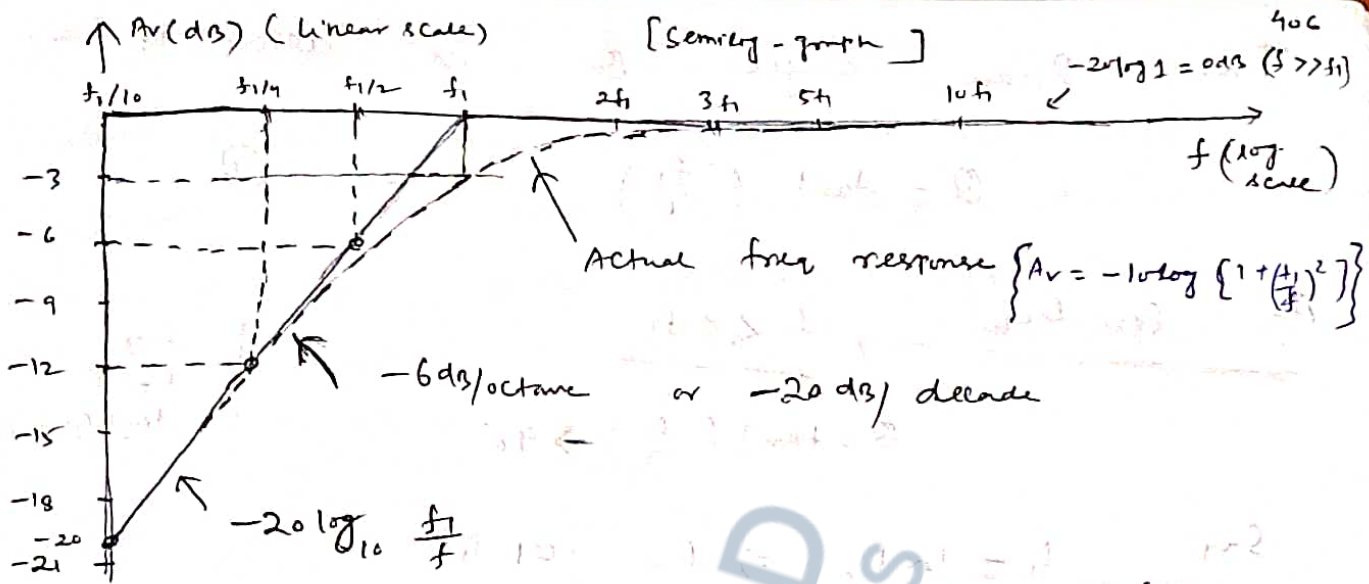


fig: -9 Bode Plot for low-freq region
 $[-10 \log [1+1] = -3 \text{ dB}]$

→ When $f = f_1$, there is a 3 dB drop from mid-band level. The piecewise linear plot of the asymptotes and associated breakpoints is called a Bode Plot of the magnitude versus freq.

→ At $f = f_1/10$, gain = 0 dB, At $f = f_1/2$, gain = -6 dB
 At $f = f_1$, gain = 0 dB, At $f = f_1/4$, gain = -12 dB

∴ A change in freq by a factor of 2, equivalent to 1 octave, results in a 6 dB change in the gain.

At $f = f_1$, gain = 0 dB, At $f = f_1/10$, gain = -20 dB
 ∴ A change in freq by a factor of 10, equivalent to 1 decade, results in a 20 dB change in the gain.

∴ Slope of the straight line = -6 dB/octave or -20 dB/decade.
 (Asymptote)

The phase angle ϕ is determined from, 407

$$\phi = \tan^{-1} \left(\frac{f}{f_c} \right) \quad \text{--- (7)}$$

At low freq, $f \ll f_c$

$$\phi \approx \tan^{-1} \left(\frac{f}{f_c} \right) \rightarrow 0^\circ$$

Say
 $f = 0$
 $\tan^{-1}(\infty) = 90^\circ$

Say $f = 0.1 f_c \Rightarrow f = 0.1 f_c$

$$\phi = \tan^{-1} \left(\frac{f}{f_c} \right) = \tan^{-1}(0.1) = 89.4^\circ$$

For $f = f_c$, $\tan^{-1}(1) = 45^\circ$

for $f \gg f_c$, $\tan^{-1} \left(\frac{f}{f_c} \right) \rightarrow 0^\circ$

EX: - $f = 0.1 f_c$, $\tan^{-1}(0.1) = 0.573^\circ$

V_o leads V_i

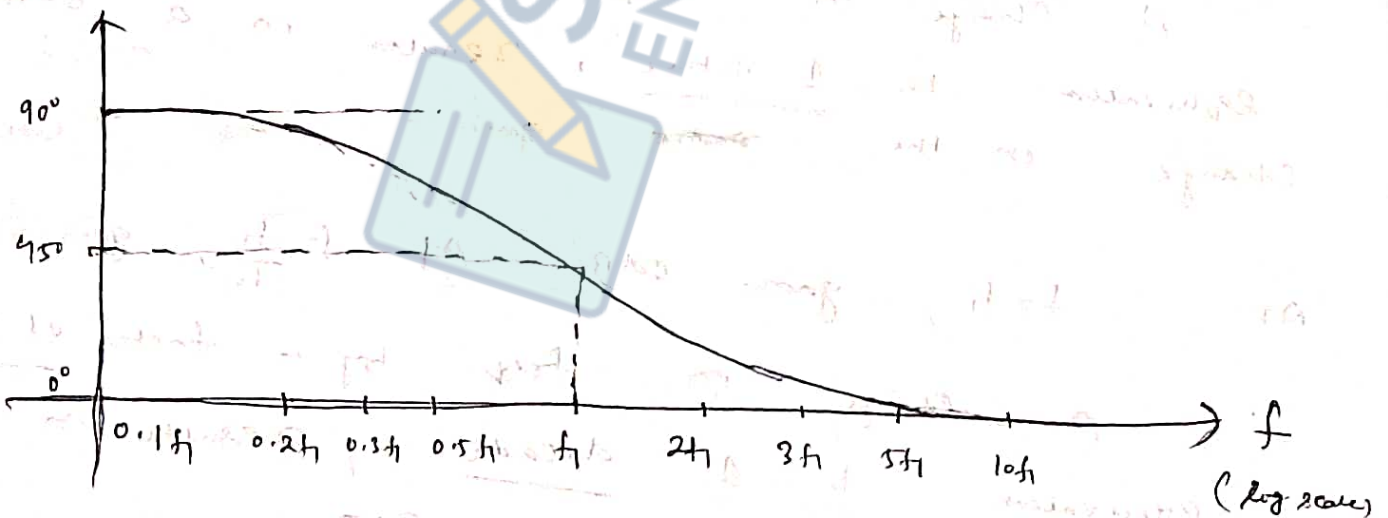


Fig: 10 - Phase Response for the R-C circuit

Low-freq response - BJT Amplifier :-

Consider a loaded voltage-divider BJT bias configuration. As shown in the figure the capacitors C_s , C_c and C_E will determine the low-freq response. We will now examine the impact of each independently.

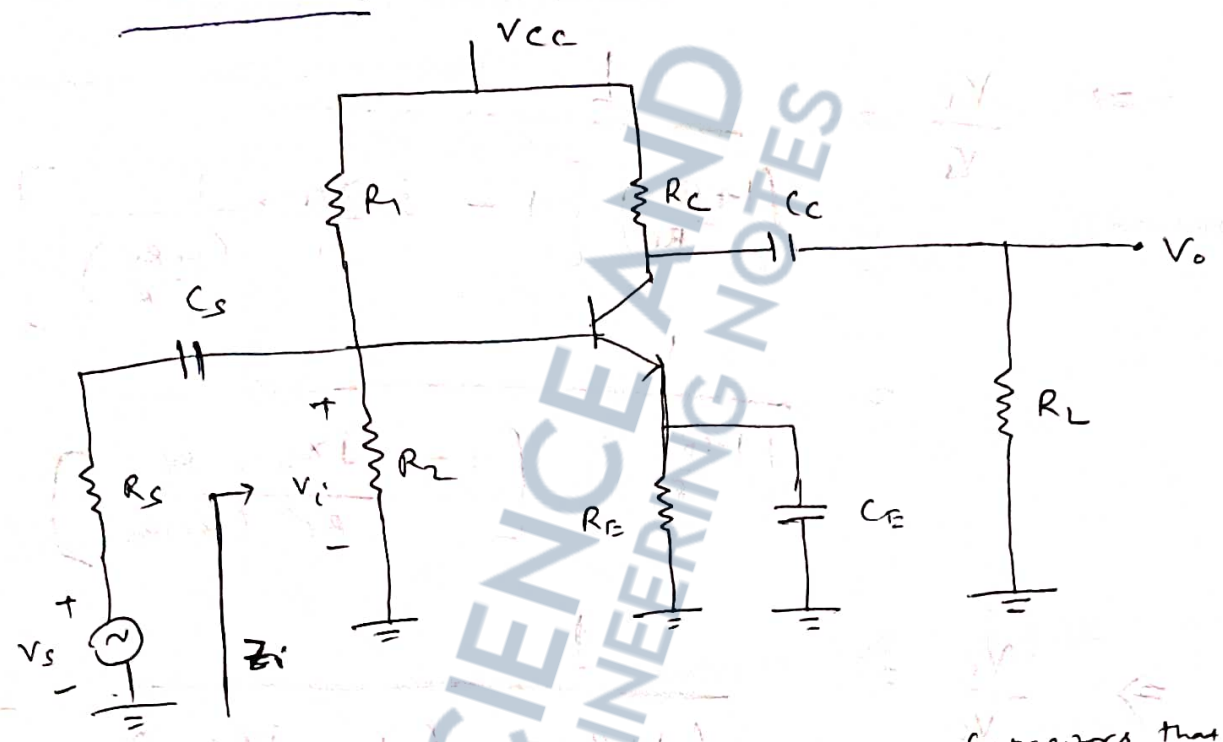


Fig 11: - Loaded BJT amplifier with capacitors that affect the low-freq response.

Cs

Since C_s is normally connected between the applied source and the active device, the general form of the RC configuration is established by the n/w given below.

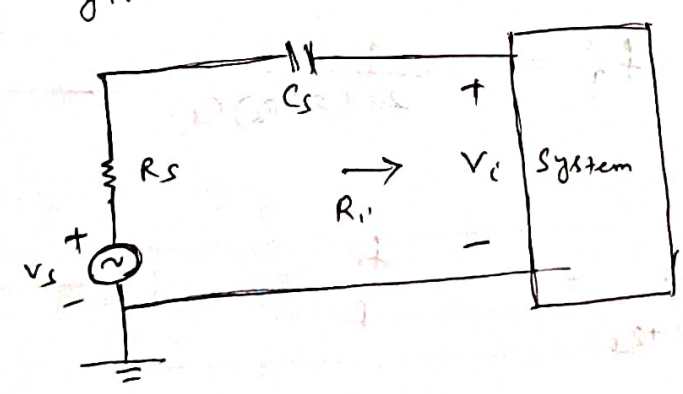


Fig 12: - Determining the effect of C_s on the low freq response

Applying the voltage divider rule;

$$V_i = \frac{V_s}{R_s + R_i - jX_{Cs}} \times R_i$$

$$\Rightarrow \frac{V_i}{V_s} = \frac{R_i}{R_s + R_i - jX_{Cs}} = \frac{1}{1 + \frac{R_s}{R_i} - j \frac{X_{Cs}}{R_i}}$$

$$\Rightarrow \frac{V_i}{V_s} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left[1 - j \frac{X_{Cs}}{R_i} \times \frac{1}{\left(1 + \frac{R_s}{R_i}\right)}\right]}$$

$$= \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left[1 - \frac{jX_{Cs} \times R_i}{R_i (R_i + R_s)}\right]}$$

$$\Rightarrow \frac{V_i}{V_s} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - \frac{jX_{Cs}}{R_i + R_s}\right)} \quad \text{--- (1)}$$

Let the factor,

$$\frac{X_{Cs}}{R_i + R_s} = \frac{1}{2\pi f C_s} \cdot \frac{1}{(R_i + R_s)} \quad \left. \begin{array}{l} \therefore X_{Cs} = \frac{1}{2\pi f C_s} \\ \therefore \frac{1}{2\pi (R_i + R_s) C_s} = \frac{1}{f} \end{array} \right\}$$

$$= \frac{1}{2\pi (R_i + R_s) C_s} \cdot \frac{1}{f}$$

Defining, $f_i = \frac{1}{2\pi (R_i + R_s) C_s}$ --- (1A)

We have,

$$\frac{X_{Cs}}{R_i + R_s} = \frac{f_i}{f} \quad \text{--- (2)}$$

Putting eqn (2), in eqn (1), we have

$$\frac{V_i}{V_s} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - j \frac{f_i}{f}\right)}$$

$$\Rightarrow A_v = \left[\frac{R_i}{R_i + R_s} \right] \cdot \left[\frac{1}{1 - j (f_i/f)} \right] \quad \text{--- (3)}$$

Comparing the above

For midband frequencies, the r/w will appear as shown in fig below (Capacitor Short Ckted)

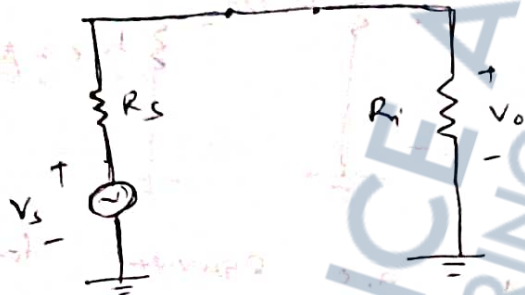


Fig 13: - High freq equivalent of fig 12.

$$A_{v \text{ mid}} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} \quad \text{--- (4)}$$

$$\therefore V_o = \frac{V_s \times R_i}{R_s + R_i}$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_i}{R_s + R_i}$$

Dividing eqn (3) by eqn (4), we have

$$\Rightarrow \frac{A_v}{A_{v \text{ mid}}} = \frac{1}{1 - j \left(\frac{f_i}{f}\right)} \quad \text{--- (5)}$$

Comparing eqn (5) with eqn $\left[A_v = \frac{1}{1 - j \left(\frac{f_i}{f}\right)} \right]$ - eqn (5) - Page 409

The cutoff freq is defined by 'fi' above

$$f_{Ls} = f_i = \frac{1}{2\pi (R_i + R_s) C_s} \quad \text{--- (6)}$$

L → Low
C → Cs

[Note: - 'fi' is defined in eqn 1(A) Last page]

At f_{LS} , the voltage V_o will be 70.7% of the midband value determined by eqⁿ (4).

Assuming only C_s is there and C_E & C_C are short circuited, the a.c equivalent of ~~fig 11~~ o/w for r/p section of fig 11 will appear as shown below.

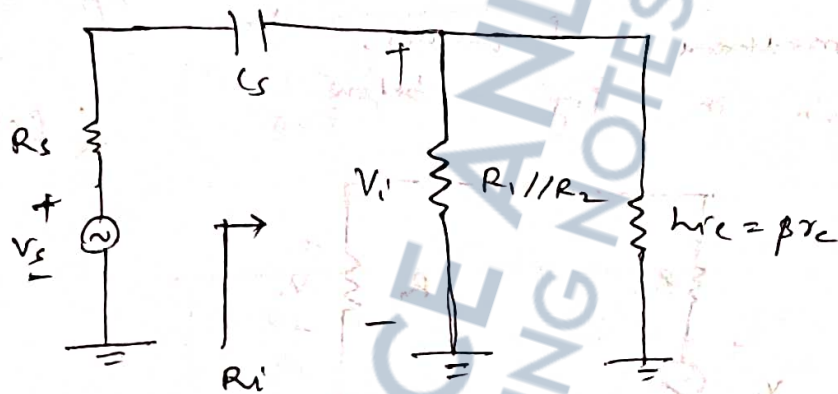


Fig 14:- Localized a.c equivalent for C_s

The value of R_i is determined by,

$$R_i = R_1 // R_2 // \beta r_c \quad \text{--- (7)}$$

C_c (Coupling Capacitor)

Since the coupling capacitor is normally connected between the o/p of the active device and the applied load, the RC configuration that determines the low-cut off freq due to C_c appears in Fig 15. From Fig 15, the total series resistance is now $(R_o + R_L)$, and cut-off freq due to

C_c is determined by
$$f_{LC} = \frac{1}{2\pi (R_o + R_L) C_c} \quad \text{--- (8)}$$

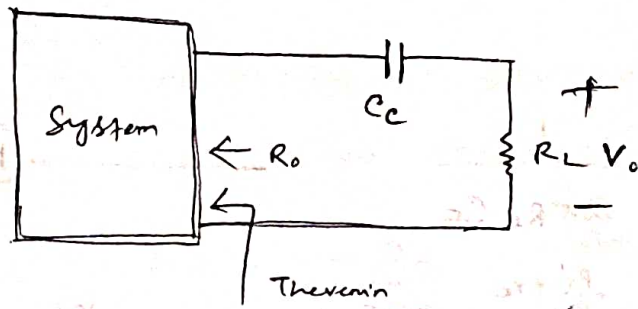


Fig 15 Determining the effect of C_c on the low-frequency response.

Ignoring the effect of C_s & C_E , we have that the o/p voltage V_o will be 70.7% of its midband value at f_{LE} .

For the n/w of fig 11, the ac equivalent n/w for the o/p section with $V_i = 0V$ appears in fig 16.

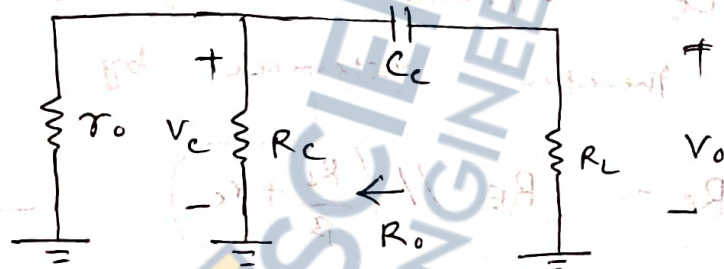


Fig 16:- Localized ac equivalent for C_c with $V_i = 0V$

$$R_o = R_c \parallel r_o \quad \text{--- (9)}$$

C_E (Emitter Bypass Capacitor)

To determine f_{LE} , the n/w 'seen' by C_E must be determined as shown in fig 17. Once the level of R_e is established, the cutoff frequency

due to C_E can be determined using the following eqⁿ,

$$f_{LE} = \frac{1}{2\pi R_E C_E} \quad \text{--- (10)}$$

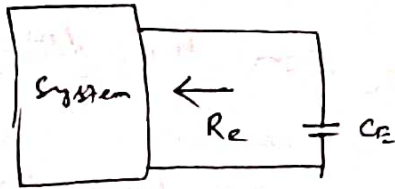


Fig 17:- Determining the effect of C_E on the low-freq response

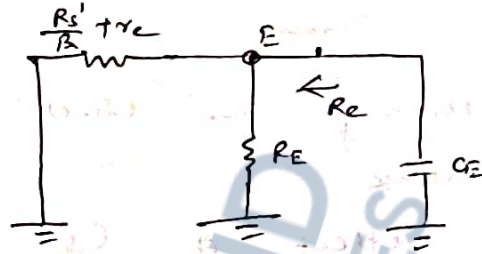


Fig 18:- Localized a.c. equivalent of C_E

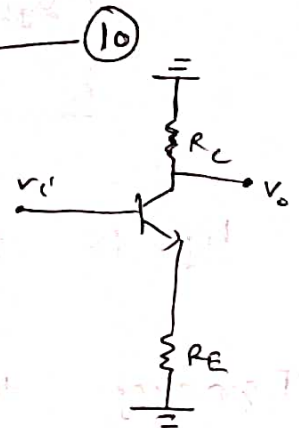


Fig 19:- N/w employed to describe the effect of C_E on the amplifier gain.

→ For the n/w of fig 11, the a.c. equivalent as 'seen' by C_E appears in fig 18. The value of R_E is therefore determined by

$$R_E = R_E \parallel \left(\frac{R_i'}{\beta} + r_c \right) \quad \text{--- (11)}$$

where $R_i' = R_s \parallel R_1 \parallel R_2$

Gain

$$A_v = \frac{-R_C}{R_E + r_c} \quad \text{--- (12)} \quad \left[\begin{array}{l} \text{See voltage-divider} \\ \text{unbypassed capacitor} \\ \text{re model} \end{array} \right]$$

When $R_E = 0\Omega$, max^m gain is available.

At low freq, $X_C = \frac{1}{2\pi f C} \approx \infty$, by pass capacitor is 'open ckted', so R_E appears in the gain eqⁿ above, resulting max gain.

At ~~high~~ ^{increases} freq, $X_C = \frac{1}{2\pi f C} \approx 0$

R_E is effectively shorted by C_E . The result is a max or midband gain is determined,

$A_v = -\frac{R_c}{r_e}$ (13)


At f_{LE} , the gain will be 3 dB below midband value determined with R_E "shorted".

EX: -1

Determine the lower cutoff freq for the n/w given below, using the following parameters

- $C_s = 10\mu F$, $C_E = 20\mu F$, $C_c = 1\mu F$
- $R_s = 1k\Omega$, $R_1 = 40k\Omega$, $R_2 = 10k\Omega$, $R_E = 2k\Omega$, $R_c = 4k\Omega$
- $R_L = 2.2k\Omega$, $\beta = 100$, $r_o = \infty$, $V_{CC} = 20V$

Ans:

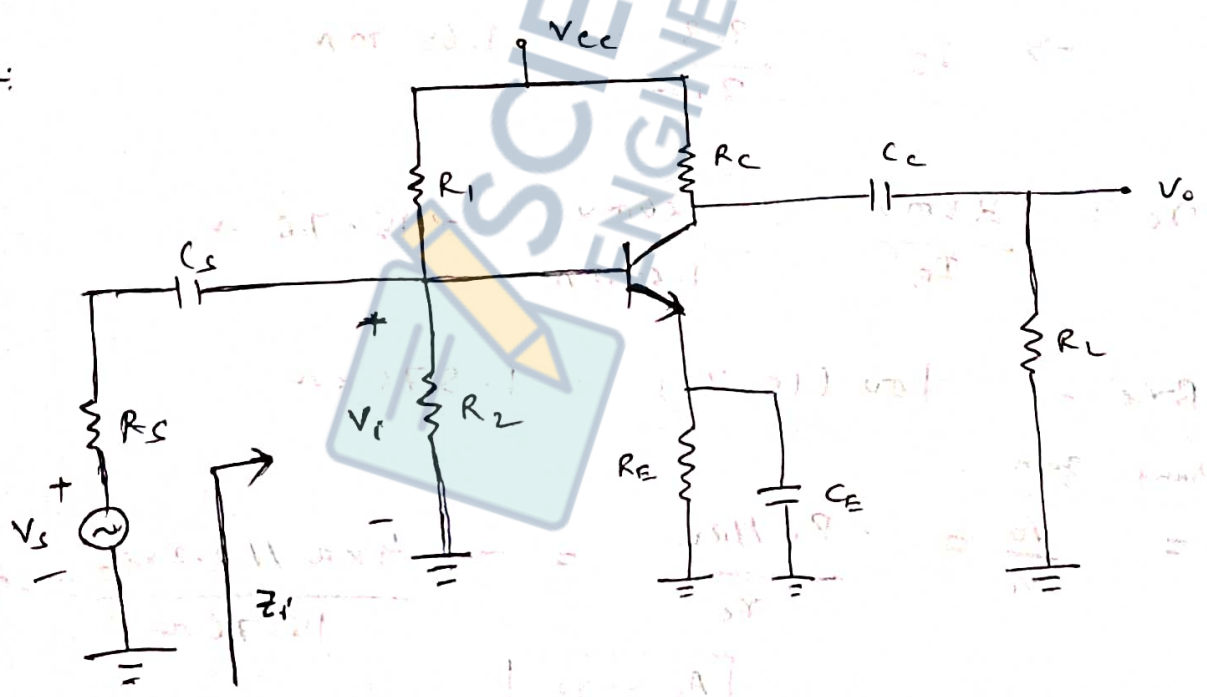

Determining $r_{e'}$ for d.c condition

Checking the condition $\beta R_E \gg 10 R_2$
 $100 \cdot 2k\Omega \gg 10 \cdot 10k\Omega$
 $200k\Omega \gg 100k\Omega$

For applying approximate model in voltage divider biasing

Since the condition is satisfied, we have

415

$$V_B \approx \frac{V_{CC} R_2}{R_1 + R_2}$$

$$= \frac{20 \times 10}{40 + 10}$$

$$= \frac{20 \times 10}{50}$$

$$V_B = 4 \text{ volt}$$

$$V_{BE} = V_B - V_E = 4 - V_E$$

$$\Rightarrow 0.7 = 4 - V_E$$

$$\Rightarrow V_E = 4 - 0.7 = 3.3 \text{ V}$$

$$\Rightarrow I_E R_E = 3.3 \text{ V}$$

$$\Rightarrow I_E = \frac{3.3}{2 \text{ k}\Omega} = 1.65 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.65 \text{ mA}} \approx 15.76 \Omega$$

$$\beta r_e = 100 (15.76) = 1.576 \text{ k}\Omega$$

Midband gain :-

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} = \frac{-4 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega}{15.76 \Omega} \approx -90$$

$$A_v = -90$$

Input impedance

$$\begin{aligned} Z_i = R_i &= R_1 \parallel R_2 \parallel \beta r_e \\ &= 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega \\ &= 8 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega \end{aligned}$$

$Z_i = 1.32 \text{ k}\Omega = R_i$

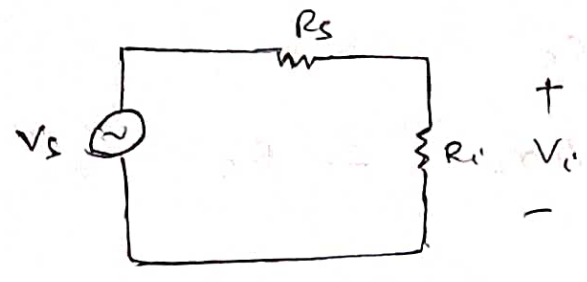


Fig: 20:- Determining the effect of R_s on gain A_v .

$V_i = \frac{V_s}{R_i + R_s} \times R_i$

or $\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1.32 \text{ k}\Omega}{1.32 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.569$

$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_v \cdot \frac{V_i}{V_s} = (-90) (0.569)$

$A_{v_s} = -51.21$

To determine cut-off frequencies

Due to C_s

$f_{Ls} = \frac{1}{2\pi (R_i + R_s) C_s} = \frac{1}{2\pi (1.32 + 1) \text{ k}\Omega \times 10 \times 10^{-6}}$

$f_{Ls} = \frac{1}{2\pi \times 2.32 \times 10^2}$

$f_{Ls} = 6.86 \text{ Hz}$

Due to C_c

$$f_{Lc} = \frac{1}{2\pi(R_o + R_L)C_c}$$

Where $R_o = R_c // r_o \approx R_c$ ($r_o \approx \infty$)

$$\begin{aligned} \therefore f_{Lc} &= \frac{1}{2\pi(R_c + R_L)C_c} \\ &= \frac{1}{2\pi(4k\Omega + 2.2k\Omega) \cdot 1 \times 10^{-6}} \\ &= \frac{1}{2\pi \times 6.2 \times 10^{-3}} \end{aligned}$$

$f_{Lc} \approx 25.68 \text{ Hz}$

Due to C_E

$$f_{LE} = \frac{1}{2\pi R_E C_E}$$

Where

$$R_E = R_E // \left(\frac{R_S'}{\beta} + r_e \right)$$

and $R_S' = R_S // R_1 // R_2$

$$\therefore R_S' = 1k\Omega // 40k\Omega // 10k\Omega$$

$$= 1k\Omega // 8k\Omega$$

$$R_S' \approx 0.889k\Omega$$

$$R_E = R_E // \left(\frac{R_S'}{\beta} + r_e \right)$$

$$\begin{aligned}
 \therefore R_e &= R_E \parallel \left(\frac{0.889 \text{ m}}{100} + 15 \text{ } \cancel{\Omega} \right) \\
 &= 2 \text{ k}\Omega \parallel 24.65 \\
 R_e &\approx 24.35
 \end{aligned}$$

$$f_{LE} = \frac{1}{2\pi \times 24.35 \times 20 \times 10^6}$$

$$f_{LE} \approx 327 \text{ Hz}$$

Low-freq response - FET amplifier

- Analysis is similar to BJT amplifier.
- C_s, C_c, C_E (BJT) \leftrightarrow C_g, C_c, C_s (FET)

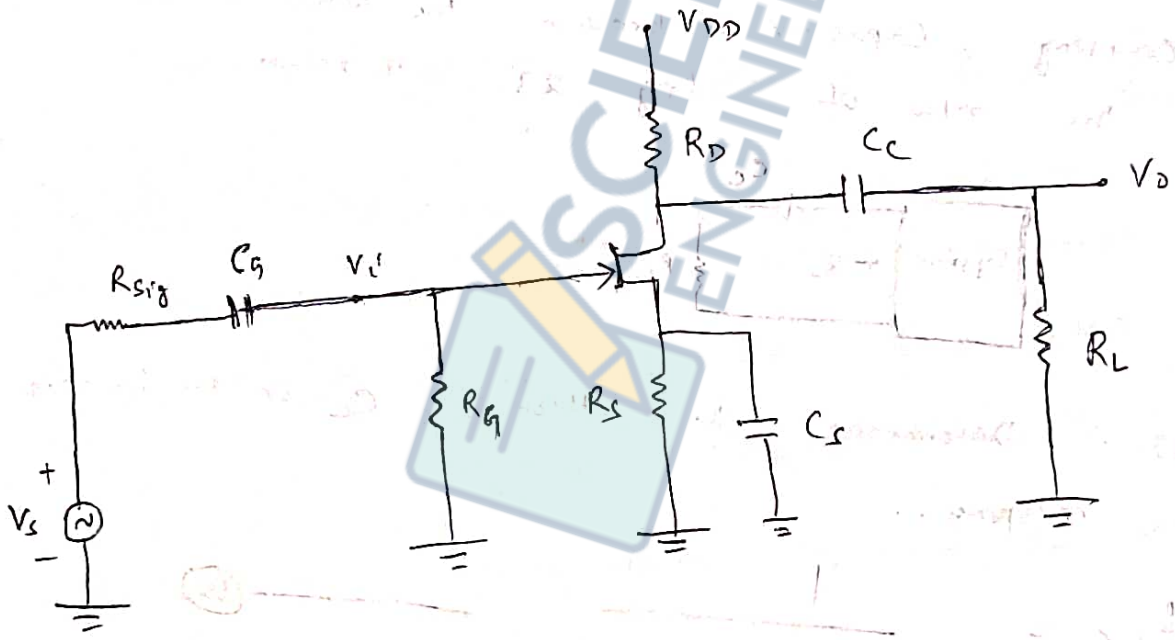


fig 21 :- Capacitive elements that affect the low-freq response of a JFET amplifier.

C_g :- For the coupling capacitor between the source of the active device, the ac equivalent n/w will

appear as shown in fig 22

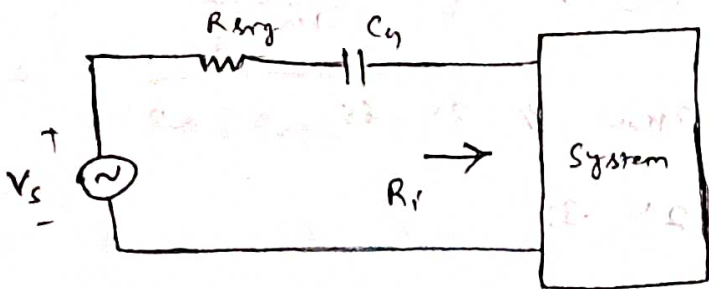


fig 22:- Determining the effect of C_s on the low-freq response.

The cutoff freq determined by C_s will then be,

$$f_{Lc} = \frac{1}{2\pi (R_l + R_s) C_s} \quad (14)$$

(Similar to eq (6))

where $R_l = R_o$ [fig 21]

C_c :-

For coupling capacitor between the active device and the load the n/w of fig 23 will result.

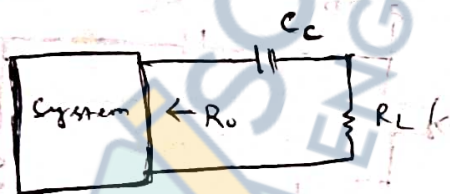


fig 23:- Determining the effect of C_c on the low-freq response.

$$f_{Lc} = \frac{1}{2\pi (R_o + R_L) C_c} \quad (15)$$

where $R_o = R_D // R_q$

C_s :- For the source capacitor C_s , the resistance level of importance is defined by fig 24.

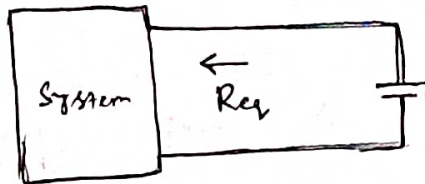


Fig 24:- Determining the effect of C_s on the low-freq response

$$f_{Ls} = \frac{1}{2\pi R_{eq} C_s} \quad (16)$$

where $R_{eq} = \frac{R_s}{1 + R_s (1 + g_m r_d) / (r_d + R_D // R_L)}$

$$R_{eq} = \frac{R_s}{1 + R_s \frac{(1 + g_m r_d)}{(r_d + R_D // R_L)}} \quad (17)$$

When $r_d \rightarrow \infty$, $R_{eq} = R_s // \frac{1}{g_m} \quad (18)$

EX-2:- Determine the lower cutoff freq for fig 21 using the following parameters:

$$C_g = 0.01 \mu F, \quad C_c = 0.5 \mu F, \quad C_s = 2 \mu F$$

$$R_{sig} = 1 k\Omega, \quad R_g = 1 M\Omega, \quad R_D = 4.7 k\Omega, \quad R_s = 1 k\Omega$$

$$R_L = 2.2 k\Omega, \quad I_{DSS} = 8 mA, \quad V_p = -4V, \quad r_d = \infty \Omega, \quad V_{DD} = 20V$$

Ans:- $g_{m0} = \frac{2I_{DSS}}{|V_p|} = \frac{2 \times 8 mA}{|-4V|} = 4 mS$

$$g_m = g_{m0} \left(1 - \frac{V_{GSQ}}{V_p}\right) = 4 \times 10^{-3} \left(1 - \frac{(-2)}{-4}\right) = 2 mS$$

Note V_{GSQ} is obtained either by graphical method or mathematical analysis - Discussed in FET biasing

$$\frac{C_u}{f_{L_u}} = \frac{1}{2\pi (R_i + R_{sig}) C_u}$$

$$f_{L_u} = \frac{1}{2\pi (1\text{M}\Omega + 10\text{k}\Omega) \cdot 0.01 \times 10^{-6}}$$

$$\therefore R_i = R_g = 1\text{M}\Omega$$

$$f_{L_u} = 15.8 \text{ Hz}$$

$$\frac{C_c}{f_{L_c}} = \frac{1}{2\pi (R_o + R_L) C_c}$$

$$f_{L_c} = \frac{1}{2\pi (4.7\text{k}\Omega + 2.2\text{k}\Omega) \times 0.5 \times 10^{-6}}$$

$$\begin{aligned} R_o &= R_D \parallel r_d \\ &= R_D \parallel \infty \\ &= R_D \end{aligned}$$

$$f_{L_c} = 46.13 \text{ Hz}$$

$$\frac{C_s}{f_{L_s}} = \frac{1}{2\pi R_{eq} C_s}$$

$$f_{L_s} = \frac{1}{2\pi R_{eq} C_s}$$

$$\text{where } R_{eq} = R_s \parallel \frac{1}{g_m}$$

$$= 1\text{k}\Omega \parallel \frac{1}{2\text{mS}}$$

$$= 1\text{k}\Omega \parallel 500\Omega$$

$$= 333.33\Omega$$

$$f_{L_s} = \frac{1}{2\pi (333.33) \times 2 \times 10^{-6}} = 238.73 \text{ Hz}$$

Since f_{L_s} is the largest of 3 cutoff frequencies,

It defines the low cutoff freq of the n/w.

→ Mid band gain of the system is determined by,

$$A_{v_{mid}} = \frac{V_o}{V_i} = -g_m (R_D || R_L)$$

$$A_{v_{mid}} = - (2 \times 10^{-3}) (4.7 \text{ k}\Omega || 2.2 \text{ k}\Omega)$$

$$= -2 \times 10^{-3} \times 1.499 \times 10^3$$

$$A_{v_{mid}} \approx -3$$

✓ Miller Effect Capacitance :- (para fig 30 p. 431)

In high-freq region, the capacitive elements of importance are the inter-electrode (between terminals) capacitances internal to the active device and the wiring capacitance between leads of the network. The large capacitors of the n/w that contained the low-freq response have all been replaced by their short-circuit equivalents due to their very low reactance levels. $[X_C = \frac{1}{2\pi f C} \rightarrow 0]$

For inverting amplifiers (Phase shift of 180° between i/p and o/p resulting in a -ve value for A_v), the i/p & o/p capacitance is increased, because a capacitive level is sensitive to the inter-electrode capacitance between the i/p & o/p terminals of the device and gain of the amplifier. In fig 25, this 'feedback' capacitance is defined by C_f .

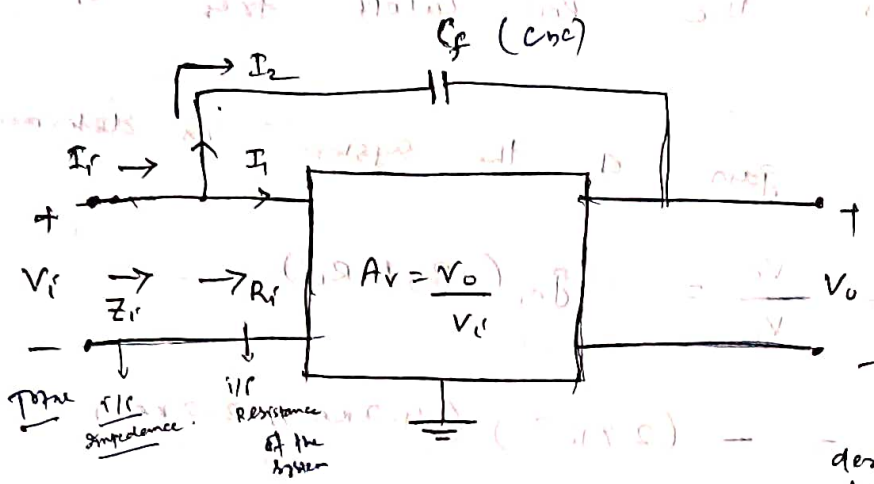


Fig 25: - N/W employed on the derivation of an equation for the Miller C_{iP} Capacitance

Applying Kirchoff's Current law gives

$$I_i = I_1 + I_2 \quad \text{--- (19)}$$

Using Ohm's law yields

$$I_i = \frac{V_i}{Z_i}, \quad I_1 = \frac{V_i}{R_i} \quad \text{--- (20)}$$

and

$$I_2 = \frac{V_i - V_o}{X_{Cf}} = \frac{V_i - A_v V_i}{X_{Cf}} \quad \left(\because A_v = \frac{V_o}{V_i} \right)$$

$$\Rightarrow V_o = A_v V_i$$

$$I_2 = \frac{V_i (1 - A_v)}{X_{Cf}} \quad \text{--- (21)}$$

Substituting I_i , I_1 & I_2 on eqn (19), we have

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{V_i (1 - A_v)}{X_{Cf}}$$

$$\Rightarrow \frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{(X_{Cf} / (1 - A_v))} \quad \text{--- (22)}$$

$$X_{cf} = \frac{1}{\omega C_f}$$

$$\therefore \frac{X_{cf}}{1-A_v} = \frac{1}{\omega C_f(1-A_v)} = \frac{1}{\omega C_m} = X_{cm} \quad \text{where } C_m = C_f(1-A_v) \quad (23)$$

Putting eqn (23), in eqn (22), we have

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{cm}} \quad (24)$$

This equation establish a new

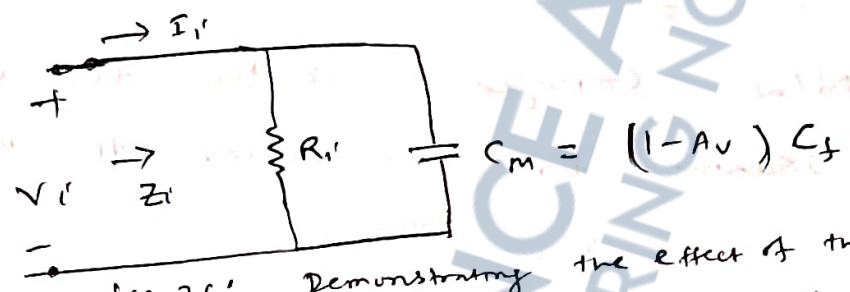


Fig 26: Demonstrating the effect of the Miller effect capacitance. The feedback capacitor is magnified by

Here the gain of the amplifier. Any interelectrode capacitance at the i/p terminals to the amplifier will simply be added in parallel with elements of fig 26.

In general, the Miller effect i/p capacitance is defined by,

$$C_{M,i} = (1-A_v) C_f \quad (25)$$

\therefore For any inverting amplifier, the i/p capacitance will be increased by a Miller effect capacitance which is sensitive to the gain of the amplifier and the interelectrode (parasitic) capacitance between i/p & o/p terminals of the active device

→ Miller effect will also increase the level of OP Capacitance, In Fig 27, the parameters of importance to determine the OP Miller effect are in place.

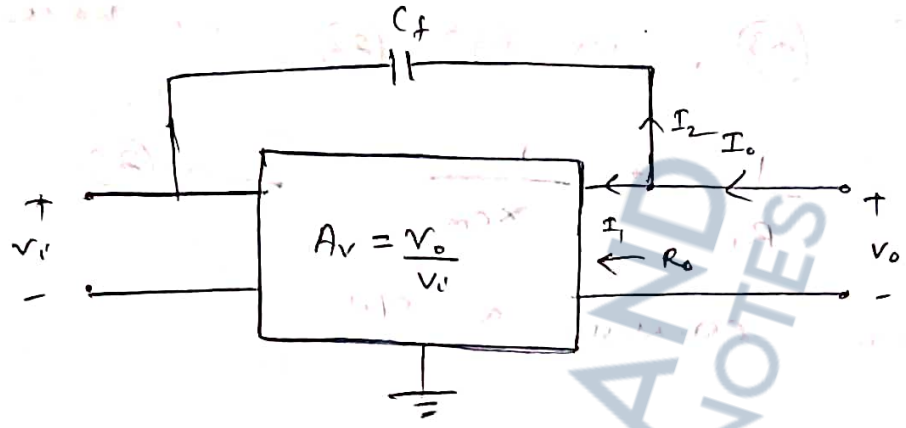


Fig 27:- N/W employed in the derivation of an equation for the Miller OP Capacitance.

Applying KLC

$$I_0 = I_1 + I_2 \tag{2c}$$

with $I_1 = \frac{V_o}{R_o}$ and $I_2 = \frac{V_o - V_i}{X_{Cf}}$

R_o is very large, $I_1 \approx 0$

$$\begin{aligned} \tag{2d} I_0 &\approx I_2 \\ \Rightarrow I_0 &= \frac{V_o - V_i}{X_{Cf}} \end{aligned} \quad \left. \begin{aligned} A_v &= \frac{V_o}{V_i} \\ V_i &= \frac{V_o}{A_v} \end{aligned} \right\}$$

$$= \left(V_o - \frac{V_o}{A_v} \right) / X_{Cf}$$

$$\Rightarrow I_0 = V_o \left(1 - \frac{1}{A_v} \right) / X_{Cf}$$

$$\Rightarrow I_0 / V_o = \left[1 - \frac{1}{A_v} \right] / X_{Cf}$$

$$\Rightarrow \frac{V_o}{I_o} = \frac{X_{cf}}{1 - 1/A_v}$$

But $X_{cf} = \frac{1}{\omega C_f}$

$$\therefore \frac{V_o}{I_o} = \frac{1}{\omega C_f (1 - 1/A_v)} = \frac{1}{\omega C_{M_0}}$$

where $C_{M_0} = C_f \left(1 - \frac{1}{A_v}\right)$

C_{M_0} is called Miller C/P capacitance.

$$C_{M_0} = C_f \left(1 - \frac{1}{A_v}\right) \quad \text{--- (27)}$$

For the usual situation, $|A_v| \gg 1$, eqⁿ (27)

reduces to $C_{M_0} \approx C_f$ --- (28)

$|A_v| \gg 1$

From eqⁿ (25) & (27), both capacitance increased, because

C/P & O/P ~~amplifier~~

A_v is $-V_C$ [Inverting Amplifier]

both are +ve.

So $(1 - A_v)$ or $\left(1 - \frac{1}{A_v}\right)$

$\therefore C_{M_0}$ & C_{M_0} are always greater than


or equal to C_f .

High-freq response ~~of amplifier~~

In the high-freq region, the RC network of concern has the configuration appearing in fig 28.

$$X_c = \frac{1}{2\pi f c}$$

LPF

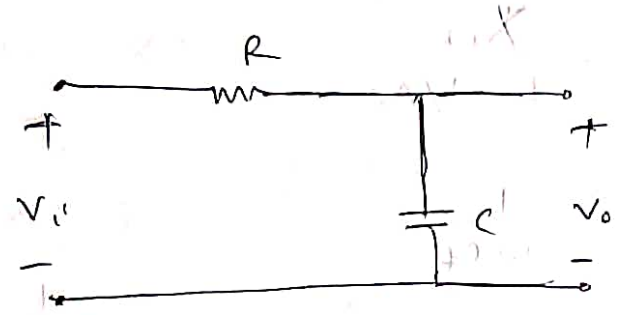


$V_o = R$

Fig 28:- RC (Combination) that will define a high cut-off frequency.

At ^{very} low freq

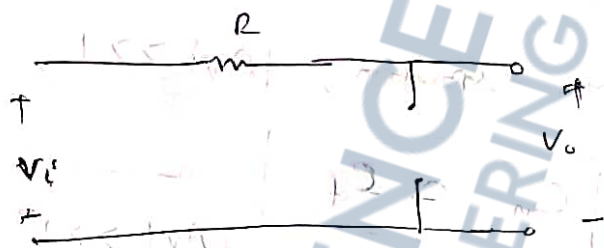(15) $X_c = \frac{1}{2\pi f c}$ (if $f \rightarrow 0$, $X_c \rightarrow \infty$)



Capacitor open circuit.

$V_o = V_i$

At ^{very} high freq

$X_c = \frac{1}{2\pi f c}$ (if $f \rightarrow \infty$, $X_c \rightarrow 0$)



Capacitor short circuit.

$V_o = 0$

Mathematically, from fig - 28, using voltage divider rule,

$|V_o| = \frac{V_i \cdot X_c}{R + X_c} = \frac{V_i}{\frac{R}{X_c} + 1}$

At $f \rightarrow 0$, $X_c \rightarrow \infty$, $|V_o| = \frac{V_i}{\frac{R}{\infty} + 1} = \frac{V_i}{0 + 1} = V_i$

At $f \rightarrow \infty$, $X_c \rightarrow 0$, $|V_o| = \frac{V_i}{\frac{R}{0} + 1} = \frac{V_i}{\infty + 1} = \frac{V_i}{\infty} = 0$

In general, from Eq 28,

$$V_o = \frac{V_i \cdot (-jX_c)}{R - jX_c}$$

Using voltage divider rule, and Reactance of capacitor is $\frac{1}{j\omega C} = -jX_c$

where $X_c = \frac{1}{\omega C}$

$$\Rightarrow \frac{V_o}{V_i} = \frac{-jX_c}{R - jX_c}$$

$$= \frac{1}{\left(\frac{R}{-jX_c}\right) + 1} \quad \left(\begin{array}{l} \text{Dividing n.r \& d.r} \\ \text{by } -jX_c \end{array} \right)$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j \frac{R}{X_c}} = \frac{1}{1 + j \frac{R}{\left(\frac{1}{2\pi f C}\right)}}$$

$$\begin{aligned} \therefore \frac{1}{-j} &= \frac{j}{-j^2} \\ &= \frac{j}{-(-1)} = j \end{aligned}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j 2\pi f RC}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j (2\pi RC) f}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j \frac{f}{\left(\frac{1}{2\pi RC}\right)}}$$

At, $R = X_c \Rightarrow A_v = \frac{1}{\sqrt{2}}$
 $R = \frac{1}{2\pi f_c C} \Rightarrow f_c = \frac{1}{2\pi RC}$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{1 + j \frac{f}{f_H}}$$

where $f_H = \frac{1}{2\pi RC} = \text{cutoff frequency}$

$$\Rightarrow \boxed{A_v = \frac{1}{1 + j(f/f_H)}} \quad (29)$$

$$\Rightarrow |A_v| = \frac{1}{\sqrt{1 + (f/f_H)^2}} \quad (30)$$

In dB,

$$(A_v)_{dB} = 20 \log |A_v|$$

$$= 20 \log \frac{1}{\sqrt{1 + (f/f_H)^2}}$$

$$= 20 \log \left[1 + \left(\frac{f}{f_H}\right)^2 \right]^{-\frac{1}{2}}$$

$$= 20 \times -\frac{1}{2} \log \left[1 + \left(\frac{f}{f_H}\right)^2 \right]$$

$$(A_v)_{dB} = -10 \log \left[1 + \left(\frac{f}{f_H}\right)^2 \right] \quad \text{--- (31)}$$

For high freq

$$f \gg f_H$$

$$\text{So } 1 + \left(\frac{f}{f_H}\right)^2 \approx \left(\frac{f}{f_H}\right)^2$$

$$\therefore (A_v)_{dB} = -10 \log \left(\frac{f}{f_H}\right)^2$$

$$(A_v)_{dB} = -20 \log \left(\frac{f}{f_H}\right) \quad \text{--- (32)}$$

(i) At $f = f_H$, $(A_v)_{dB} = 0 \text{ dB}$

(ii) At $f = 2f_H$, $(A_v)_{dB} = -20 \log (2) = -6 \text{ dB}$

(iii) At $f = 4f_H$, $(A_v)_{dB} = -20 \log 4 = -12 \text{ dB}$

E.g. (32) is a approximate formula, for $f \gg f_H$

For Actual response eqn (31) gives, $|A_v| = -10 \log \left[1 + \left(\frac{f}{f_H}\right)^2 \right]$

at $f = f_H$,

$$|A_v| = -10 \log(|H|) = -10 \log 2$$


$$|A_v| = -3 \text{ dB}$$

i.e. there is 3 dB drop from midband level (0 dB)

at $f = f_H$.

$$\rightarrow f \ll f_H, -10 \log[1] = 0$$
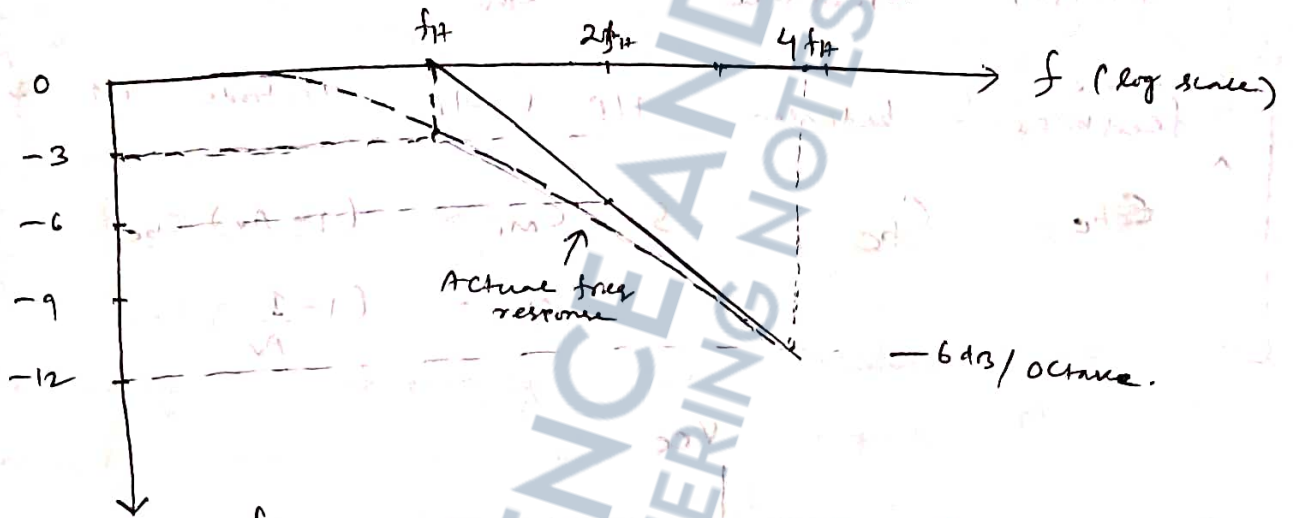
$$\log\left[1 + \left(\frac{f}{f_H}\right)^2\right] \approx \log[1] = 0$$



$(A_v)_{dB}$


→ Phase

High-freq response of

fig 29 = - Asymptotic plot as defined by eqn 29

$$\phi = -\tan^{-1}\left(\frac{f}{f_H}\right)$$

BJT Amplifier

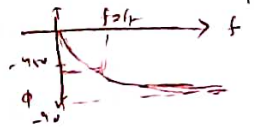


At high freq operation capacitors like C_S, C_C, C_E become short circuited due to their low reactance value.

$$X_C = \frac{1}{2\pi f C}$$

At high freq,
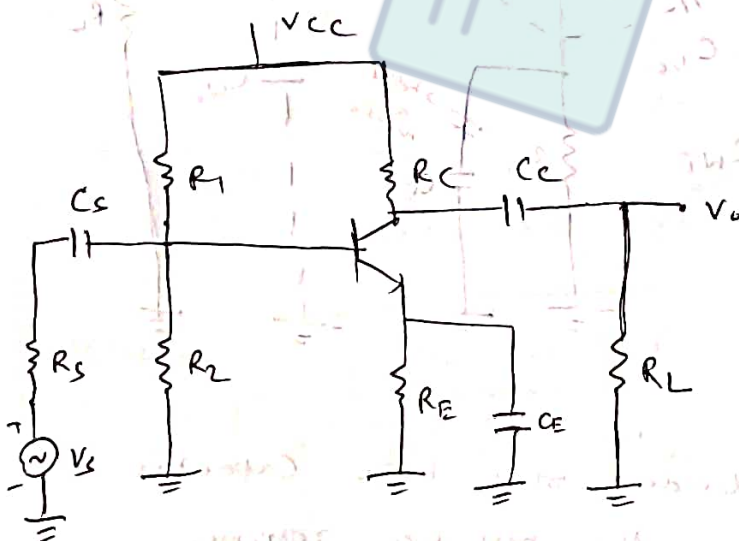
$$f \rightarrow \infty, X_C \rightarrow 0$$



[Normal Biasing form]

New Capacitance resulted at high freq [fig 30]

(i) Various Parasitic Capacitance & Transition Capacitance
 (C_{be} , C_{ce})

(ii) Winding Capacitance $\left[\begin{matrix} C_{wi} \text{ (at i/P)} \\ C_{wo} \text{ (at o/P)} \end{matrix} \right]$

(c) Miller Capacitance C_{wi} & C_{wo} .

Capacitance feedback between i/P & o/P electrode 'CM'

C_{bc} , So $C_{wi} = (1 - A_v) C_{bc}$
 $C_{wo} = (1 - \frac{1}{A_v}) C_{bc}$

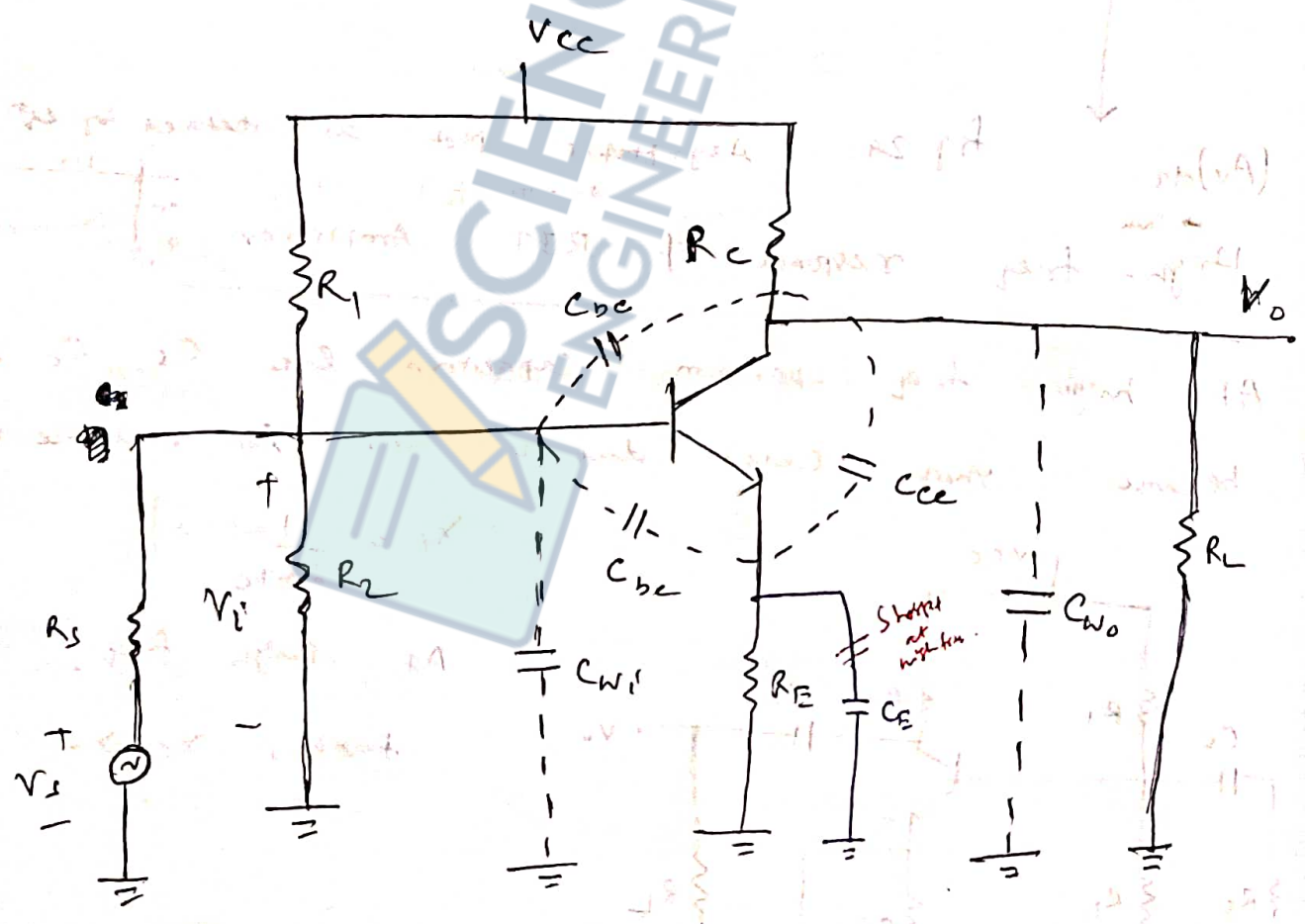


Fig 30:- Voltage divider bias with capacitors that affect the high-freq response.

In general, the Capacitance C_{be} is largest parasitic capacitance & C_{ce} the smallest.

The High-freq a.c equivalent model for π/w of fig 30 is shown below.

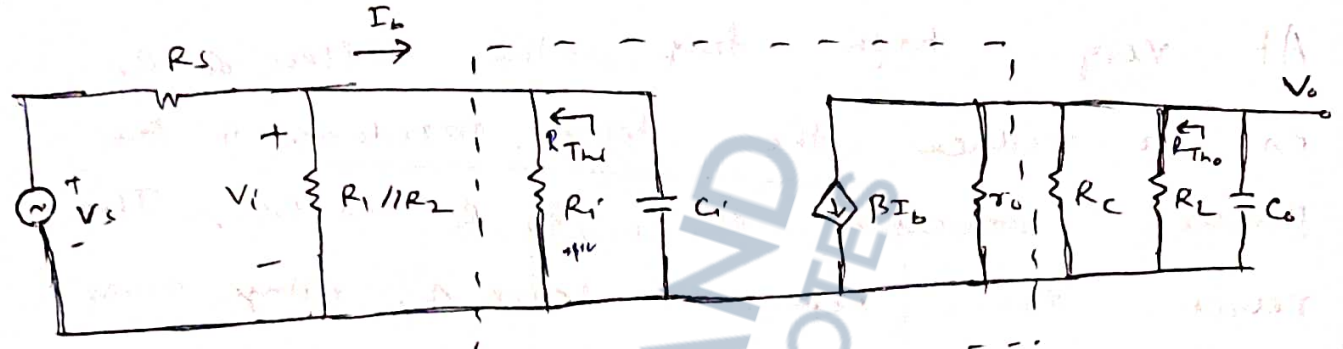


fig 31:- a.c equivalent model of fig 30.

~~Determining~~ Determining the Thevenin equivalent circuit for i/p & o/p networks of fig 31 results the configuration of fig 32.

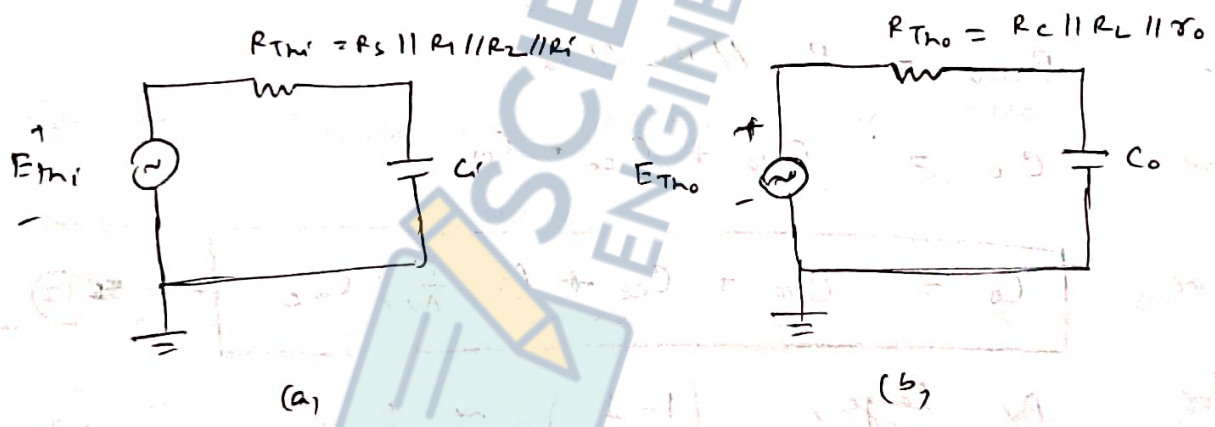


fig 32:- Thevenin ckt's for i/p & o/p π/w of π/w fig 31.

Where $R_{Thi} = R_s || R_1 || R_2 || R_i$ — (33)

$C_i = C_{wi} + C_{be} + C_{mi}$
 $C_i = C_{wi} + C_{be} + C_{be}(1-A_v)$ — (34)

For T/P n/w, $-3dB$ freq. is defined as

$$f_{HT} = \frac{1}{2\pi R_{Th} C_i} \quad (35) \quad \left[R_{Th} \text{ \& } C_i \text{ are defined in eq (33) \& (34)} \right]$$

At very high freq, the effect of C_i is to reduce the total impedance of the parallel combination of R_1, R_2, R_i and C_i . The result is reduced level of voltage across C_i , a reaction in I_o & a gain for the system.

For O/P n/w

$$f_{HO} = \frac{1}{2\pi R_{Th0} C_o} \quad (36)$$

where $R_{Th0} = R_c // R_L // r_o$

and $C_o = C_{wo} + C_{ce} + C_{mo}$

$$\text{or } C_o = C_{wo} + C_{ce} + \left(1 - \frac{1}{A_v}\right) C_{bc} \quad (37)$$

for A_v large, $\left(1 - \frac{1}{A_v}\right) \approx 1$

$$\therefore C_o \approx C_{wo} + C_{ce} + C_{bc}$$

At very high freq, the capacitive reactance of C_o will decrease and consequently reduce the total impedance of the O/P parallel branches. The net result is that V_o will also decline towards zero as reactance X_c becomes smaller.

The frequencies f_{H1} & f_{H0} each define a -6dB/octave asymptote as depicted in fig 29. [$*$ \rightarrow h_{fe} or β Variation - 4th page]

High freq response - FET Amplifier

\rightarrow Similar to BJT analysis.

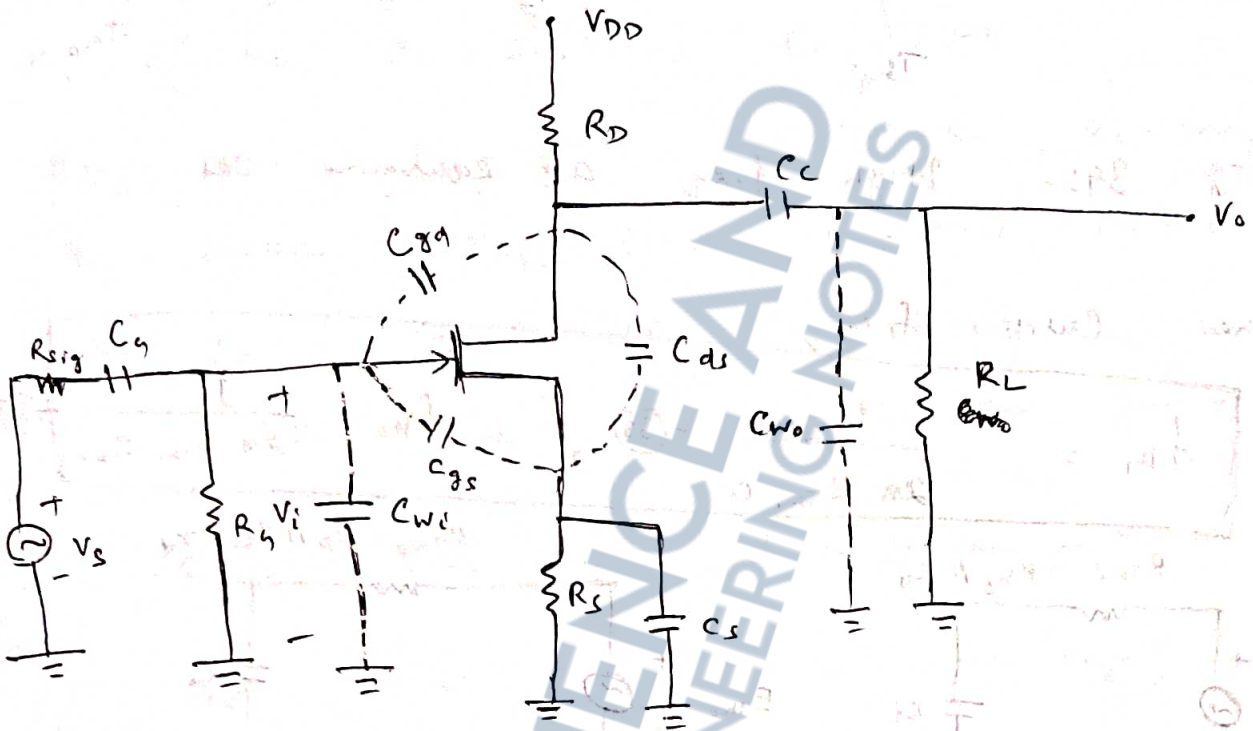


Fig 33: Capacitive element that affect the high freq response of a JFET amplifier.

\rightarrow At high freq C_{gs} , C_s & C_c are short circuited. The inter electrode and wiring capacitances determine the high-freq characteristics of the amplifier.

\rightarrow Similar to BJT, At high freq C_i will approach a short-circuit equivalent & V_{gs} will drop in value and reduce overall gain.

\rightarrow Similarly, C_o approaches its short-circuit equivalent, the parallel o/p voltage V_o will drop in magnitude.

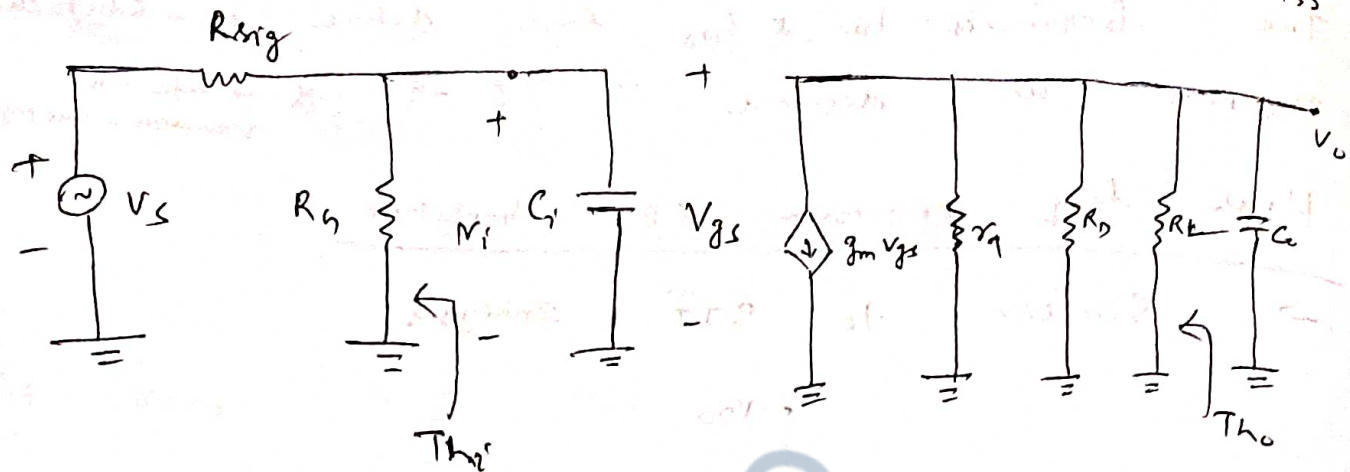


Fig 34:- High freq ac equivalent CRT

The Cutoff freq,

$$f_{Hi} = \frac{1}{2\pi R_{Thi} C_i} \quad (38), \quad f_{Ho} = \frac{1}{2\pi R_{Tho} C_o} \quad (39)$$

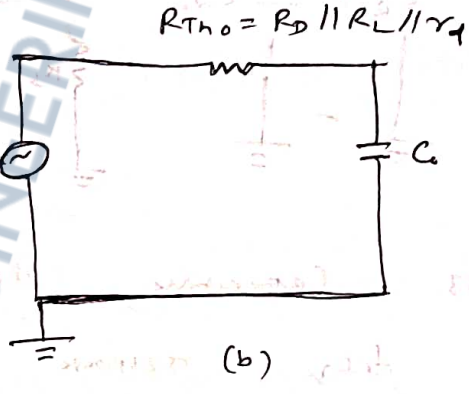
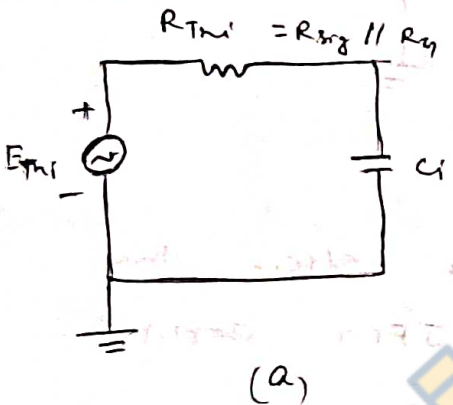


Fig 35:- The Thevenin equivalent CRT for

(a) the i/p CRT (b) o/p CRT

where $R_{Thi} = R_{sig} \parallel R_G$

$C_i = C_{wi} + C_{gs} + C_{mi}$ — (40)

where $C_{mi} = (1 - A_v) C_{gd}$ = Miller Capacitance

Similarly for o/p CRT,

$$R_{Tho} = R_D \parallel R_L \parallel r_o \quad (41)$$

$$C_o = C_{wo} + C_{ds} + C_{mo} \quad \text{--- (42)}$$

where $C_{mo} = (1 - \frac{1}{A_v}) C_{gd} = \text{OIP Miller Capacitance.}$

Ex: - 3 : Determine the high-cut off freq for fig 33, given

$$C_g = 0.01 \mu F, \quad C_c = 0.5 \mu F, \quad C_s = 12 \mu F$$

$$R_{sig} = 10 k\Omega, \quad R_g = 1 M\Omega, \quad R_D = 4.7 k\Omega, \quad R_s = 1 k\Omega$$

$$R_L = 2.2 k\Omega, \quad I_{DSS} = 8 \text{ mA}, \quad V_p = -4 \text{ V}, \quad r_d = \infty,$$

$$V_{DD} = 20 \text{ V}, \quad C_{gd} = 2 \text{ pF}, \quad C_{gs} = 4 \text{ pF}, \quad C_{ds} = 0.5 \text{ pF},$$

$$C_{wi} = 5 \text{ pF}, \quad C_{wo} = 6 \text{ pF}, \quad \text{Use the gain of Ex-2.}$$

Ans : $R_{Thi} = R_{sig} \parallel R_g = 10 k\Omega \parallel 1 M\Omega = 9.9 k\Omega$

$$A_v = -3 \quad [\text{Ex-2, 422 Page}]$$

$$C_i = C_{wi} + C_{gs} + (1 - A_v) C_{gd}$$

$$= 5 \text{ pF} + 4 \text{ pF} + (1 - (-3)) 2 \text{ pF}$$

$$= 9 \text{ pF} + 8 \text{ pF}$$

$$= 17 \text{ pF}$$

$$f_{Hi} = \frac{1}{2\pi R_{Thi} C_i} = \frac{1}{2\pi \times 9.9 \times 10^3 \times 17 \times 10^{-12}} = 945.67 \text{ kHz}$$

$$R_{Tho} = R_D \parallel R_L \parallel \infty = R_D \parallel R_L = 4.7 k\Omega \parallel 2.2 k\Omega = 1.5 k\Omega$$

$$C_o = C_{wo} + C_{ds} + C_{mo} = 6 \text{ pF} + 0.5 \text{ pF} + (1 - \frac{1}{-3}) 2 \text{ pF} = 9.17 \text{ pF}$$

$$f_{H0} = \frac{1}{2\pi R_{Th0} C_0}$$


$$= \frac{1}{2\pi \cdot 1.5 \times 10^3 \times 9.7 \times 10^{-12}}$$

$$f_{H0} = 11.57 \text{ MHz}$$

Multi-stage freq effects :-

For a second transistor stage connected directly to the OIP of a first stage, there will be a significant change in the overall freq response. In the high-freq region, the OIP capacitance C_0 must now include the wiring capacitance (C_{w1}), parasitic capacitance (C_{be}) and Miller capacitance (C_{m1}) of the following stage. Further, there will be additional low-freq cutoff levels due to the second stage that will further reduce the overall gain of the system in this region. The effect of increasing number of identical stages can be clearly demonstrated by considering the situation illustrated in fig 36.

Fig: -36

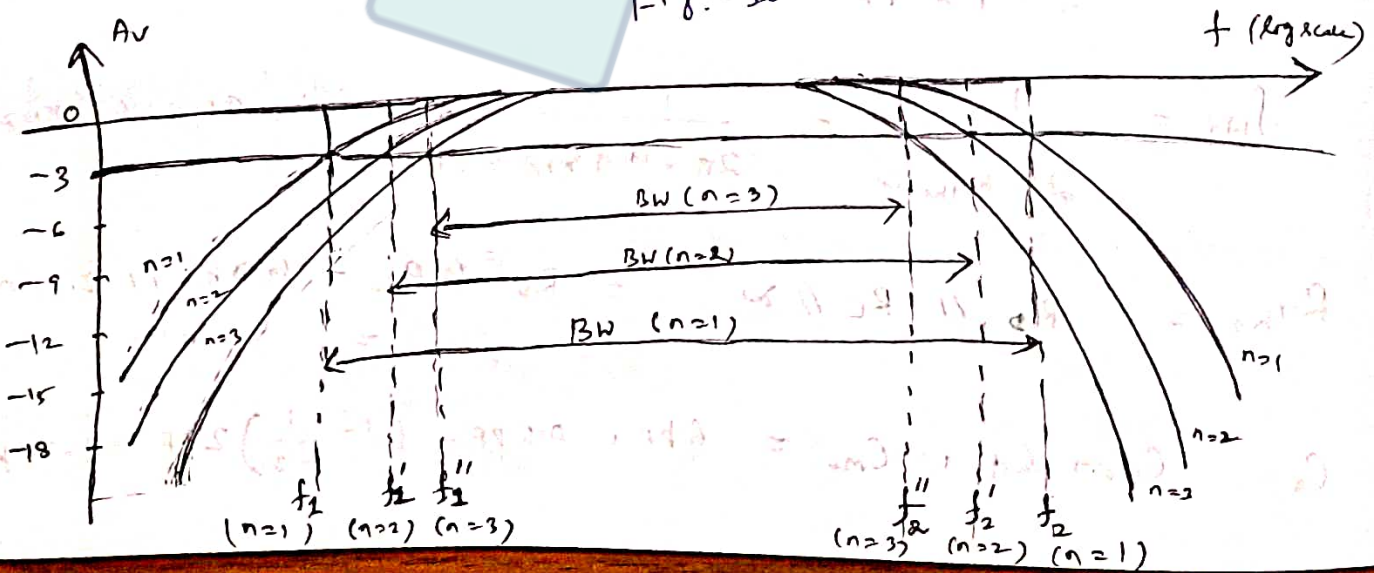

Ex 30:- Effect of an increased number of stages on the cutoff frequencies and the BW. 438

In each case, the upper and lower cutoff freq of each ~~stage~~ of the cascaded stages are identical. For a single stage the cutoff freq f_1 & f_2 are increased. For 2 identical stages in cascade, the drop-off rate in the high freq & low freq regions has increased to -12 dB/octave ≈ -40 dB/decade, and -3 dB point shifted to f_1' & f_2' .

A -18 dB/octave ≈ -60 dB/decade slope will result for a 3 stage system with reduction in bandwidth (f_1'' & f_2'')

Assuming identical stages, an equation for each band freq as a function of the number of stages (n) can be determined in following manner. For low freq region

$$A_{v_{low, (overall)}} = A_{v_{1, low}} \cdot A_{v_{2, low}} \dots A_{v_{n, low}} \quad (43)$$

Since each stage is identical,

$$A_{v_{1, low}} = A_{v_{2, low}} = A_{v_{low}}$$

$$\therefore A_{v_{low, (overall)}} = (A_{v_{low}})^n \quad (44)$$

But
$$A_{v_{low}} = \frac{1}{1 - j \left(\frac{f_1}{f} \right)}$$

$$|A_{v_{low}}| = \frac{1}{\sqrt{1 + \left(\frac{f_1}{f} \right)^2}} \quad (45)$$

$$|A_{v_{low, (over)}}| = |A_{v_{low}}|^n \quad \text{--- (46)}$$

Putting eqⁿ (45) in eqⁿ (46), we have

$$|A_{v_{low, over}}| = \left[\frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}} \right]^n \quad \text{--- (47)}$$

$$= \frac{1}{\left[1 + \left(\frac{f}{f_c}\right)^2 \right]^{\frac{n}{2}}}$$

At -3dB cut off freq, $[f_T] \Rightarrow f$, $|A_{v_{low, over}}| = \frac{1}{\sqrt{2}}$
 $f = f_T$, $T \rightarrow \text{Total}$

$$\frac{1}{\left[1 + \left(\frac{f_T}{f_c}\right)^2 \right]^{\frac{n}{2}}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \left[1 + \left(\frac{f_T}{f_c}\right)^2 \right]^{\frac{n}{2}} = \sqrt{2}$$

$$\Rightarrow \left[1 + \left(\frac{f_T}{f_c}\right)^2 \right]^n = 2$$

$$\Rightarrow 1 + \left(\frac{f_T}{f_c}\right)^2 = 2^{\frac{1}{n}}$$

$$\Rightarrow \left(\frac{f_T}{f_c}\right)^2 = 2^{\frac{1}{n}} - 1$$

$$\Rightarrow \frac{f_T}{f_c} = \sqrt{2^{\frac{1}{n}} - 1}$$

$$\Rightarrow f_T = \frac{f_c}{\sqrt{2^{\frac{1}{n}} - 1}} \quad \text{--- (48)}$$

Similar

n	$\frac{\sqrt{2^{1/n} - 1}}$
2	→ 0.64
3	→ 0.51
4	→ 0.43
5	→ 0.39

∴ f_1 (low) → f_2

For $n=2$, $f_1' = \frac{f_1}{0.64} = 1.5625 f_1$

$n=3$, $f_1'' = \frac{f_1}{0.51} = 1.96 f_1$

∴ $f_1'' > f_1' > f_1$ [tr 36]

Similarly: - For high freq region

$$| \text{Av High, overall} | = \frac{1}{\left[1 + \left(\frac{f}{f_2} \right)^2 \right]^{n/2}}$$

[Similar to eqn 47]

See, for low freq

$$\frac{f_1}{f}$$

but high freq

$$\frac{f}{f_2}$$

At -3 dB cut-off freq, $f = [f_T]$, $\text{Av High, overall} = \frac{1}{\sqrt{2}}$

$$\Rightarrow \frac{1}{\left[1 + \left(\frac{f_T}{f_2} \right)^2 \right]^{n/2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \left[1 + \left(\frac{f_T}{f_2} \right)^2 \right]^{n/2} = \sqrt{2}$$

$$\Rightarrow \left[1 + \left(\frac{f_T}{f_2} \right)^2 \right]^n = 2$$

$$\Rightarrow 1 + \left(\frac{f_1}{f_2}\right)^2 = 2^{1/n}$$

$$\Rightarrow \left(\frac{f_1}{f_2}\right)^2 = 2^{1/n} - 1$$

$$\Rightarrow \left(\frac{f_1}{f_2}\right)^2 = \sqrt{2^{1/n} - 1}$$

$$\Rightarrow \boxed{f_1 = f_2 \sqrt{2^{1/n} - 1}} \quad - (49)$$

$$f_2'' < f_2' < f_2 \quad [\text{try 30}]$$

Ex-4 :- BPUT - 2011

An amplifier consists of 3 identical stages in cascade. The BW of overall amplifier extends from 20 Hz to 20 kHz. Calculate BW of individual stages.

Ans :- Given

$$f_L = f_1 = 20 \text{ Hz}, \quad f_H = f_2 = 20 \text{ kHz}$$

$$f_{L2} \text{ or } f_1' = \frac{f_1}{\sqrt{2^{1/2} - 1}} = \frac{20}{\sqrt{2^{1/2} - 1}} = 31.07 \text{ Hz}$$

(n=2)

$$f_{L3} \text{ or } f_1'' = \frac{f_1}{\sqrt{2^{1/3} - 1}} = \frac{20}{\sqrt{2^{1/3} - 1}} = 39.22 \text{ Hz}$$

n=3

~~$$f_{H2} \text{ or } f_2' = \frac{f_2}{\sqrt{2^{1/2} - 1}} = \frac{20 \text{ kHz}}{\sqrt{2^{1/2} - 1}}$$~~

(n=2)

$$f_{H2} \approx f_2' = f_2 \sqrt{2^{1/n} - 1}$$

$$[n=2] = 20 \text{ kHz} \sqrt{2^{1/2} - 1}$$

$$= 12.87 \text{ kHz}$$

$$f_{H3} \approx f_2'' = f_2 \sqrt{2^{1/3} - 1}$$

n=3

$$= 20 \text{ kHz} \sqrt{2^{1/3} - 1}$$

$$f_2'' = 10.19 \text{ kHz}$$

Bandwidth of Individual Stages [fig 36]

$$BW_1 = f_2 - f_1 = 20 \text{ kHz} - 20 \text{ Hz} = 19.98 \text{ kHz}$$

$$BW_2 = f_2' - f_1' = 12.87 \text{ kHz} - 31.07 \text{ Hz} = 12.83 \text{ kHz}$$

$$BW_3 = f_2'' - f_1'' = 10.19 \text{ kHz} - 39.22 \text{ Hz} = 10.15 \text{ kHz}$$

∴ Bandwidth gradually reduces, with increase in number of stages.

gms Square-wave Testing :- [BPUT - Short Note - 2010]


A sense for the freq response of an amplifier can be determined experimentally by applying a square-wave signal to the amplifier and noting the O/P response. The shape of the O/P waveform will reveal whether the high or low frequencies are being properly amplified.

gms Why square wave is taken? (BPUT)

The use of square-wave testing

is significantly less time-consuming than applying 493 a series of sinusoidal signals at different frequencies and magnitude to test the freq response of the amplifier.

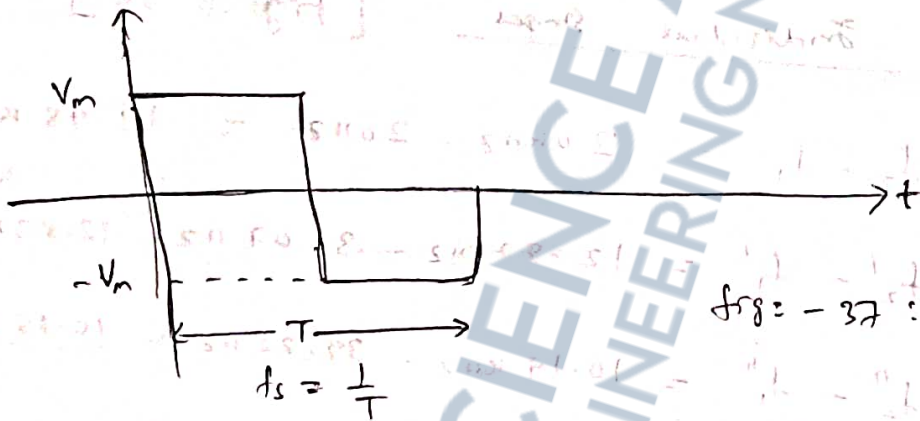The reason for choosing a square-wave signal for the testing process is best described by examining the Fourier Series expansion of a square wave composed of a series of sinusoidal components of different magnitudes & frequencies. The summation of the terms of the series will result in the original waveform.



The Fourier series expansion for the square wave given above is

$$V = \frac{4V_m}{\pi} \left(\sin 2\pi f_s t + \frac{1}{3} \sin 2\pi (3f_s)t + \frac{1}{5} \sin 2\pi (5f_s)t + \frac{1}{7} \sin 2\pi (7f_s)t + \frac{1}{9} \sin 2\pi (9f_s)t + \dots + \frac{1}{n} \sin 2\pi (nf_s)t \right) \quad \text{--- (50)}$$

The first term of the series is called the fundamental term and in this case has the same freq, f_s , as the square wave.

The next term has a freq equal to three times the fundamental and is referred to as the

Third harmonic, its magnitude is one third the magnitude of the fundamental term. The frequencies of the succeeding terms are odd multiples of the fundamental term and the magnitude decreases with each higher harmonic.

The generation of the square wave of fig 37 require infinite number of terms. But fig 38 shows, including fundamental, 3rd, 5th & 7th harmonics takes us a step closer to the wave form of fig 37.

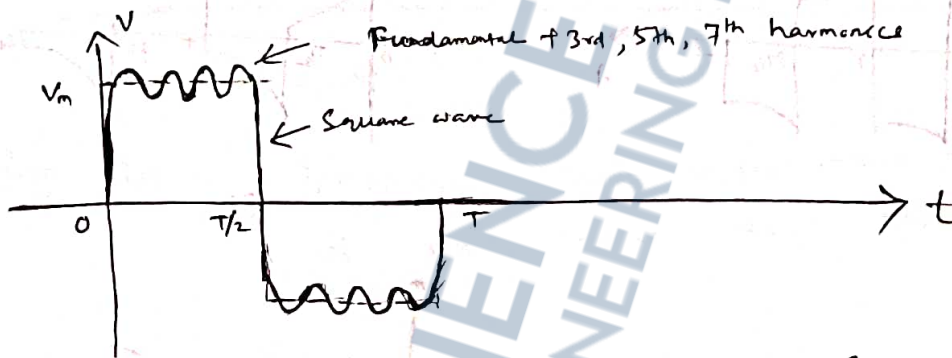


Fig: 37 Harmonic Content of a Square wave.

Since the q th harmonic has a magnitude greater than 10% of the fundamental term $[\frac{1}{q} \times 100 = 11.1\%]$, the fundamental term through the q th harmonic are the major contributors to the Fourier series expansion of the square-wave function. It is therefore reasonable to assume that if the application of a square-wave of a particular freq results in a nice clean square wave at the OP, then the fundamental through the ninth harmonic are being amplified without visual distortion by the amplifier.

If the response of an amplifier to an applied square wave is an undistorted replica of the i/p, the freq response (BW) of the amplifier is obviously sufficient for the applied frequency. If the response is as shown in fig 38 (a) and (b), the low frequencies are not amplified properly - and the low cutoff freq has to be investigated

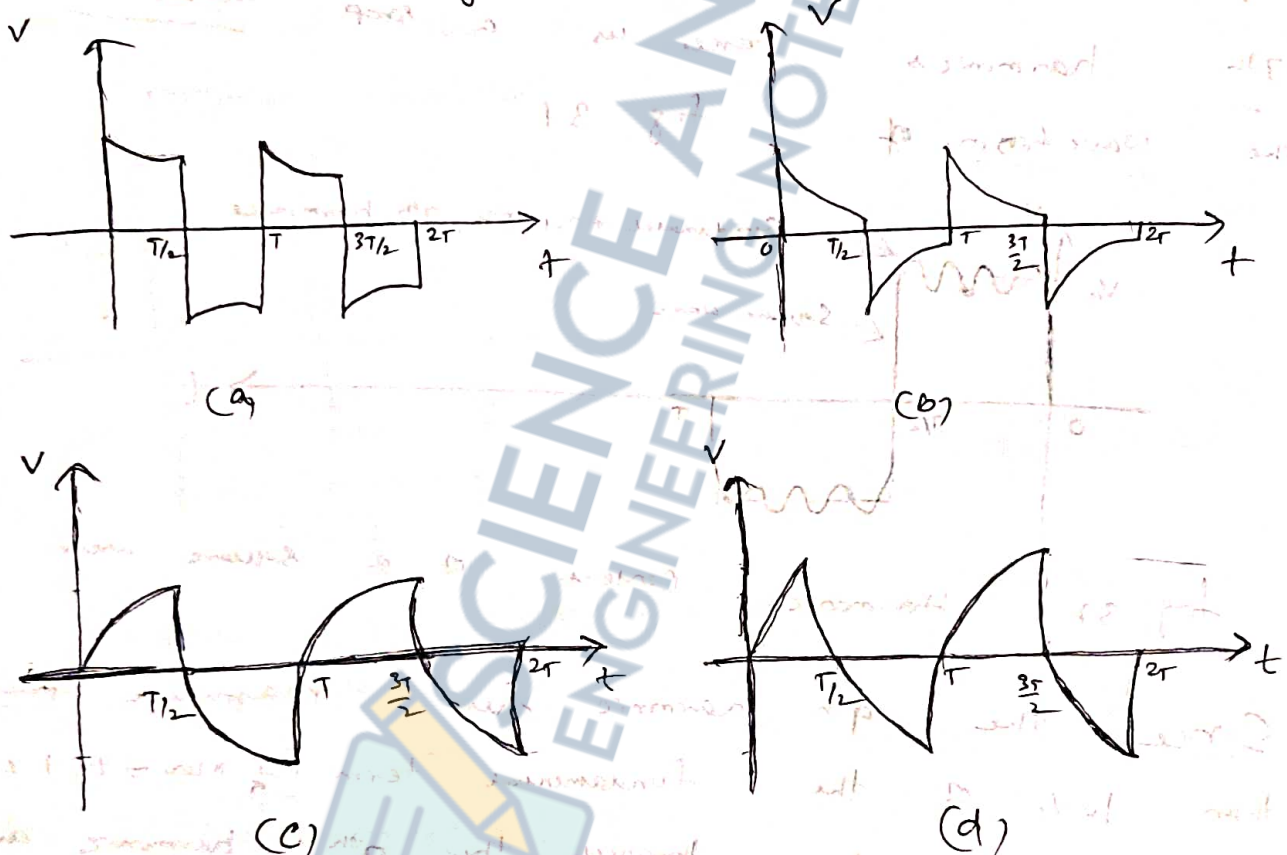


fig 38 : (a) Poor low freq response
 (b) Very poor low freq response
 (c) Poor high-freq response
 (d) Very poor high-freq response.

→ Similarly, if the waveform has appearance of fig 38 (c) & (d), the high freq components are not receiving sufficient amplification & high

Cutoff freq (or BW) has to be reviewed.

The actual high cutoff freq (or BW) can be ~~also~~ determined from the output waveform by carefully measuring the rise time defined between 10% and 90% of the peak value, as shown in fig 39.

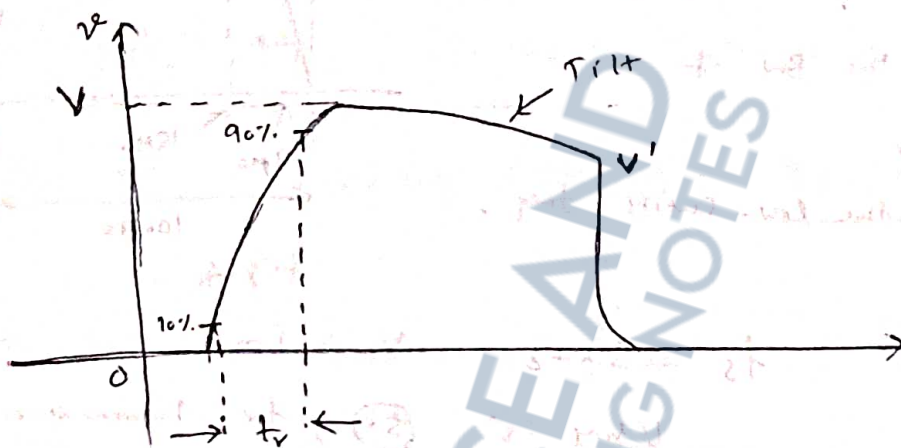


fig 39:- Defining the rise time and trit of a square wave response.

$$BW = f_{Hi} - f_{Lo} \approx f_{Hi}$$

$$\therefore BW \approx f_{Hi} = \frac{0.35}{t_r} \quad \text{--- (51)}$$

The low cutoff freq can be determined from the ~~the~~ ~~o/p~~ ~~response~~ by carefully measuring the trit of fig 39.

$$\% \text{ trit} = P\% = \frac{V - V'}{V} \times 100\% \quad \text{--- (52)}$$

$$\text{trit} = P = \frac{V - V'}{V} \quad \text{(decimal form) --- (53)}$$

The low cutoff freq is then determined from

$$f_{Lo} = \frac{P}{\pi} f_s \quad \text{--- (54)}$$

$f_s \rightarrow$ Fundamental freq

Ex: 5 The application of a 1 mV, 5 kHz square wave to an amplifier result on the O/P wave form [fig 40].

- (a) Write the Fourier series expansion of square wave through 9th harmonic
- (b) Determine the BW of the amplifier
- (c) Calculate the low-cut off freq.

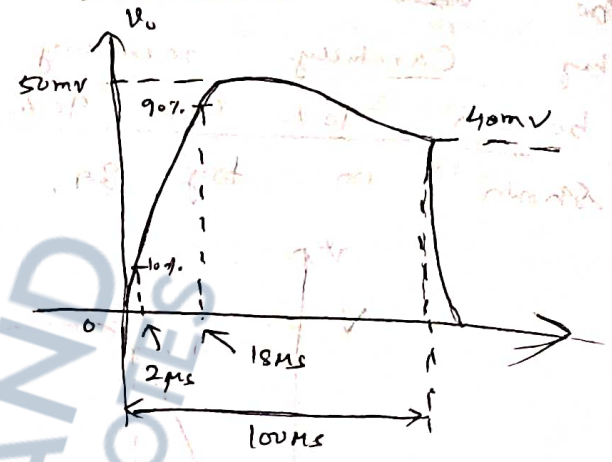


fig 40:-

Ans ⇒ (a) Given $f_s = 5 \text{ kHz}$, $V_m = 1 \text{ mV}$
 Using eqⁿ (50), for Fourier series expansion

$$V_i = \frac{4 \cdot (1 \text{ mV})}{\pi} \left[\sin 2\pi (5 \times 10^3) t + \frac{1}{3} \sin 2\pi (15 \times 10^3) t + \frac{1}{5} \sin 2\pi (25 \times 10^3) t + \frac{1}{7} \sin 2\pi (35 \times 10^3) t + \frac{1}{9} \sin 2\pi (45 \times 10^3) t \right]$$

(b) $t_r = (18 - 2) \mu\text{s} = 16 \mu\text{s}$

$$BW = \frac{0.35}{t_r} = \frac{0.35}{16 \times 10^{-6}} = 21,875 \text{ Hz} \approx 4.4 f_s$$

(c) $P = \frac{V - V'}{V} = \frac{50 \text{ mV} - 40 \text{ mV}}{50 \text{ mV}} = \frac{10}{50} = 0.2$

$$f_{L0} = \frac{P}{\pi} \cdot f_s = \frac{0.2}{\pi} \times 5 \times 10^3 = 318.31 \text{ Hz}$$

Ex - 6 - Internal question

Three voltage amplifiers with gain & BW ($A_1 = 100, BW_1 = 30\text{kHz}$), ($A_2 = 20, BW_2 = 30\text{kHz}$), ($A_3 = 40, BW_3 = 30\text{kHz}$) are connected in cascade. Calculate the overall gain in dB & overall BW.

Ans :- $(A_v)_{\text{overall}} = 100 \times 20 \times 40 = 8 \times 10^4$
In dB, $20 \log (8 \times 10^4) = 98.06 \text{ dB}$ (Ans)

$$\begin{aligned} \text{Overall BW} &= 30\text{kHz} \times \sqrt{2^{1/n} - 1} \\ &= 30 \times 10^3 \times \sqrt{2^{1/3} - 1} \\ (BW)_{\text{overall}} &= 15.29 \text{ kHz} \quad \text{(Ans)} \end{aligned}$$

High freq response - BJT Amplifier [Remaining portion]
↓
with freq, it's given
hfe or β variation
The variation of hfe or (β)
by
$$h_{fe} = \frac{h_{\text{temid}}}{1 + j(f/f_{\beta})} \quad \text{--- (1)}$$

Using hybrid - π model
 f_{β} is defined as
$$f_{\beta} = \frac{1}{2\pi \beta_{\text{mid}} r_e (C_{be} + C_{bc})} \quad \text{--- (2)}$$

→ Common base Configuration displays improved high-freq characteristics over Common-emitter Configuration.

In common base, there is absence of Miller effect capacitance due to non-inverting configuration. Characteristics For this reason, common base high-freq parameters rather than CE parameters are specified for transistors - especially those designed specifically to operate in the high-freq regions.

Conversion

$$f_B = f_c (1 - \alpha) \quad \text{--- (3)}$$

→ A quantity called gain-BW product is defined for the transistor by the Condⁿ,

$$\left| \frac{h_{fe} m_{ca}}{1 + j f/f_B} \right| = 1 \quad \text{--- (4)}$$

From eqⁿ (3),

$$\therefore |h_{fe}| = 20 \log \left| \frac{h_{fe} m_{ca}}{1 + j f/f_B} \right| = 20 \log 1 = 0 \text{ dB} \quad \text{--- (5)}$$

The freq at which $|h_{fe}|_{dB} = 0 \text{ dB}$ is given by f_T , from eqⁿ (1)

$$\therefore \frac{h_{fe} m_{ca}}{\sqrt{1 + j \left(\frac{f_T}{f_B}\right)^2}} = 1$$

$$\text{If } f_T \gg f_B, \quad \sqrt{1 + \left(\frac{f_T}{f_B}\right)^2} \approx \left(\frac{f_T}{f_B}\right)$$

$$\frac{h_{fe} m_{ca}}{\frac{f_T}{f_B}} = 1$$

$$\Rightarrow \frac{h_{fe} m_{vq} \times f_{\beta}}{f_T} = 1$$

$$\Rightarrow f_T = f_{\beta} \cdot h_{fe} m_{vq}$$

$$\Rightarrow f_T = f_{\beta} \cdot \beta m_{vq} \quad \text{--- (5) } \quad | \quad h_{fe} = \beta$$



Putting eqⁿ (2), in eqⁿ (5), we have

$$f_T = \frac{1}{2\pi \cdot \beta m_{vq} \cdot r_c (C_{be} + C_{bc})} \quad \beta m_{vq}$$

$$\Rightarrow f_T = \frac{1}{2\pi r_c (C_{be} + C_{bc})}$$

Note: In multistage, there is decrease in BW with increase in number of stages. $f_{T3} < f_{T2} < f_{T1}$, $BW_3 < BW_2 < BW_1$.
 → But if midband gain can remain fixed, then BW will not decrease.

Ex:

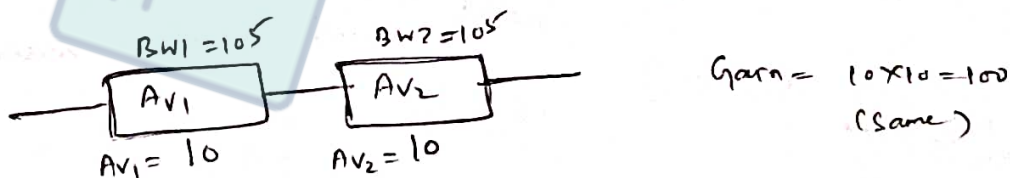
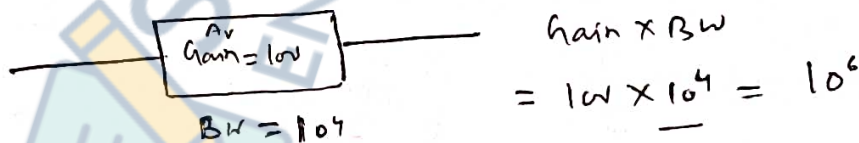


But $BW_1 = 10^5$, $10 \times 10^5 = 10^6$
 $BW_2 = 10^5$, $10 \times 10^5 = 10^6$

∴ BW of each stage increases by a factor 10 to make Gain \times BW = constant.

Darlington Connection :-

Current gain

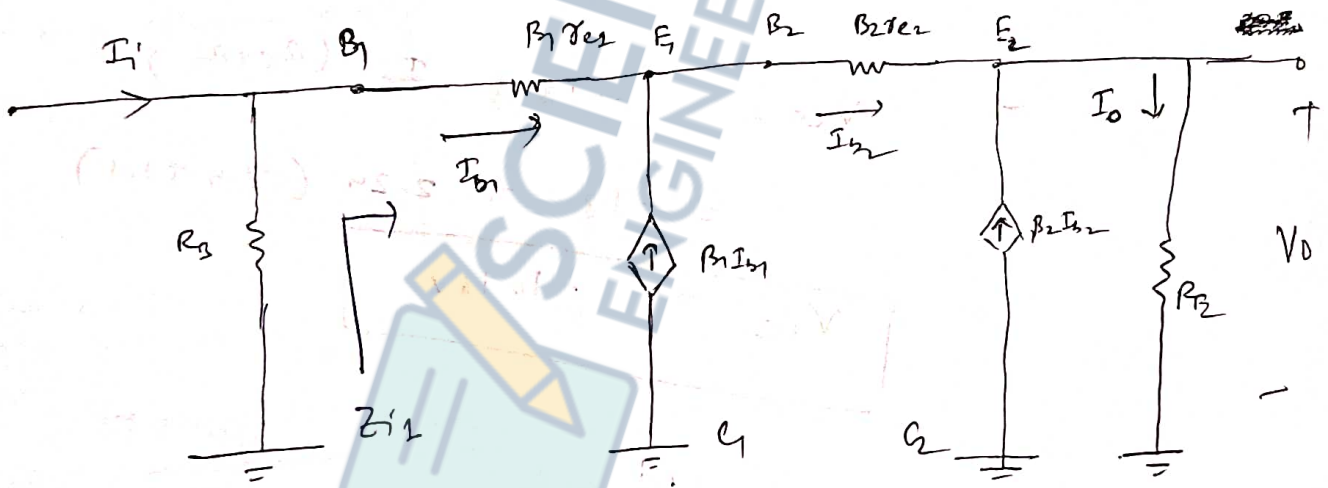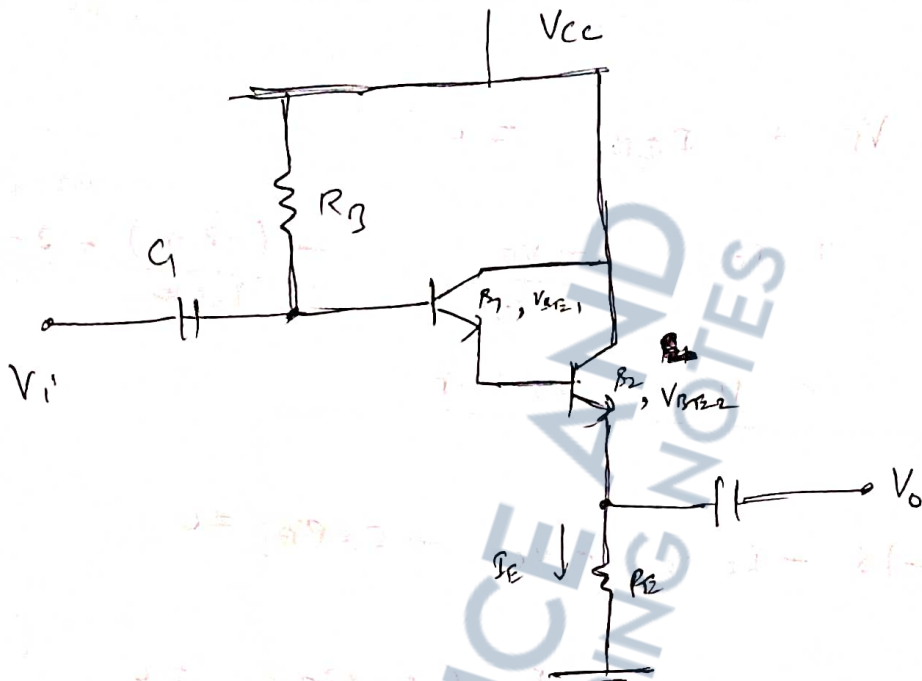

Solving for O/P current

$$I_o = I_{E2} + \beta_2 I_{B2} = (\beta_2 + 1) I_{E2} \quad \text{--- (1)}$$

With $I_{E2} = I_{B1} + \beta_1 I_{B1} = (\beta_1 + 1) I_{B1} \quad \text{--- (2)}$

$$\therefore I_o = (\beta_2 + 1) I_{E2} = (\beta_2 + 1) (\beta_1 + 1) I_{B1} \quad \text{--- (3)}$$

Using current division rule on the r/p circuit,

$$I_{B1} = \frac{I_i \times R_B}{R_B + Z_{i1}} = \frac{I_i R_B}{R_B + (\beta_1 \beta_2 R_E)}$$

∴ from eqⁿ (3),

$$I_o = (\beta_2 + 1) (\beta_1 + 1) \times \frac{I_i \times R_B}{R_B + (\beta_1 \beta_2) R_E}$$

$$\Rightarrow \frac{I_o}{I_i} = \frac{(\beta_1 + 1) (\beta_2 + 1) R_B}{R_B + \beta_1 \beta_2 R_E}$$

$$\Rightarrow A_i = \frac{\beta_1 \beta_2 R_B}{R_B + \beta_1 \beta_2 R_E}$$

$$\Rightarrow A_i = \frac{\beta_1 \beta_2 R_B}{R_B + \beta_1 \beta_2 R_E}$$

Voltage gain

$$V_o = I_o R_E \quad \text{--- (1)}$$

$$V_i = I_i \times (R_B \parallel Z_{i1})$$

$$V_i = I_i \times (R_B \parallel \beta_1 \beta_2 R_E) \quad \text{--- (2)}$$

Dividing eq (1) by eq (2),

$$\frac{V_o}{V_i} = \frac{I_o R_E}{R_i \times (R_B \parallel \beta D R_E)}$$

$$\Rightarrow A_v = A_i \times \frac{R_E}{R_B \parallel \beta D R_E}$$

$$\Rightarrow A_v = A_i \times \frac{R_E (R_B + \beta D R_E)}{R_B \times \beta D \times R_E}$$



$$\Rightarrow A_v = \left(\frac{\beta D R_B}{R_B + \beta D R_E} \right) \times \frac{(R_B + \beta D R_E)}{R_B \times \beta D}$$

$$\Rightarrow \boxed{A_v = 1} \quad \text{In Reality } < 1$$

which is an expected result for the emitter follower configuration.

O/P Impedance:

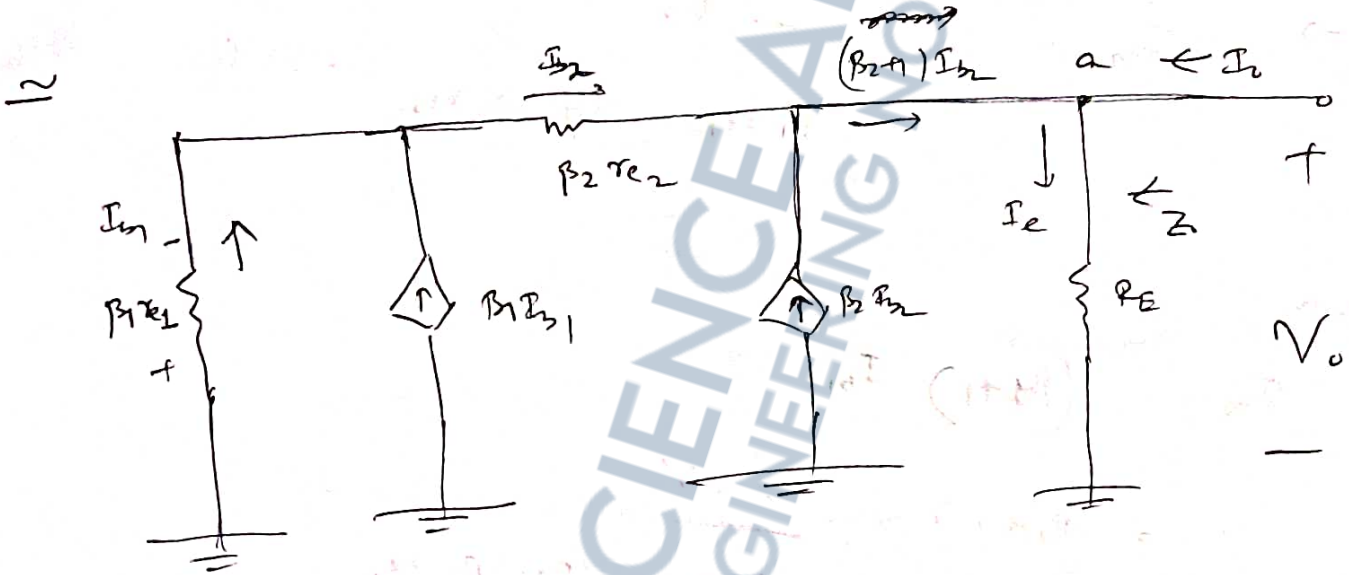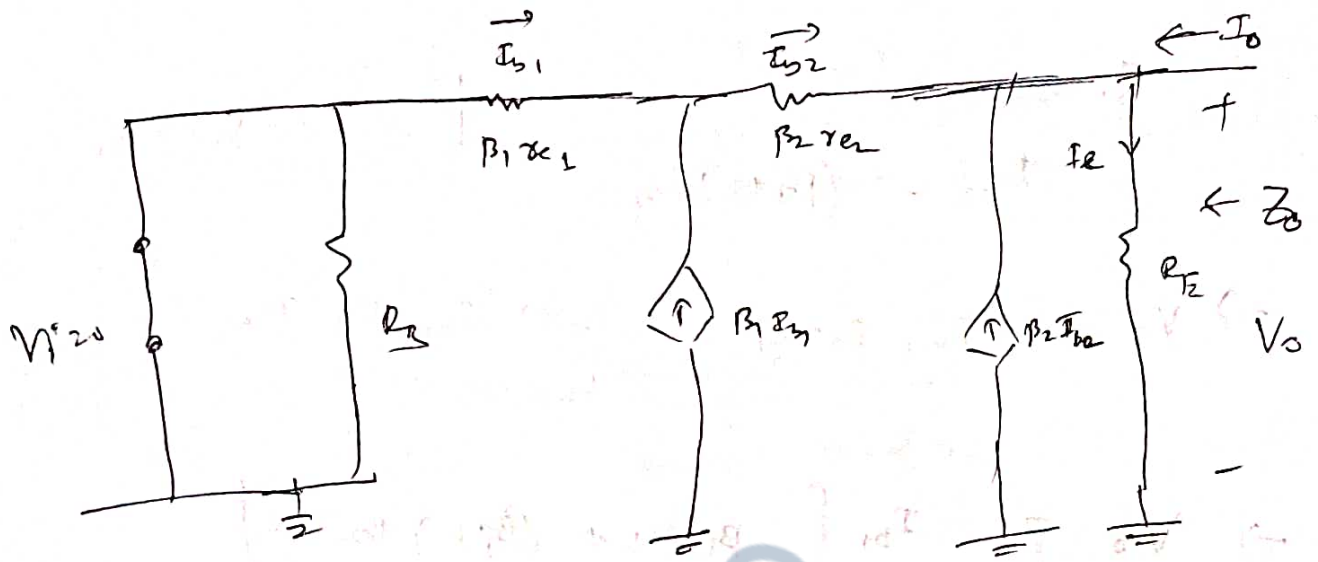The O/P impedance will be determined by setting V_i to zero. and the resistor R_B is short circuited. The O/P current has been redefined to match the standard nomenclature and properly defined Z_o .



At point a KCL will result,

$$I_o + (\beta_2 + 1) I_{b2} = I_e$$

$$\Rightarrow I_o = I_e - (\beta_2 + 1) I_{b2} \quad \text{--- (1)}$$

Applying KVL around the entire outside loop,

$$- I_{i1} \times \beta_1 r_{e1} - I_{b2} \times \beta_2 r_{e2} - V_o = 0$$

$$\Rightarrow V_o = - I_{i1} \beta_1 r_{e1} - I_{b2} \beta_2 r_{e2} \quad \text{--- (2)}$$

Substituting

$$I_{b2} = (\beta_1 + 1) I_{b1}$$

$$I_{b2} = \beta_1 I_{b1} + I_{b1}$$

$$\Rightarrow V_o = -I_{b1} \beta_1 r_{e1} - \underbrace{(\beta_1 + 1) I_{b1}}_{I_{b2}} \beta_2 r_{e2}$$

$$\Rightarrow V_o = -I_{b1} \left[\beta_1 r_{e1} + (\beta_1 + 1) \beta_2 r_{e2} \right]$$

$$\Rightarrow I_{b1} = \frac{-V_o}{\beta_1 r_{e1} + (\beta_1 + 1) \beta_2 r_{e2}} \quad \text{--- (3)}$$

with

$$I_{b2} = (\beta_1 + 1) I_{b1} \\ = (\beta_1 + 1) \times \frac{-V_o}{\beta_1 r_{e1} + (\beta_1 + 1) \beta_2 r_{e2}}$$

$$\Rightarrow I_{b2} = \left[\frac{-(\beta_1 + 1)}{\beta_1 r_{e1} + (\beta_1 + 1) \beta_2 r_{e2}} \right] V_o \quad \text{--- (4)}$$

From eqn (1),

$$I_o = I_e - (\beta_2 + 1) I_{b2}$$

$$= I_e - (\beta_2 + 1) \times \left[\frac{-(\beta_1 + 1)}{\beta_1 r_{e1} + (\beta_1 + 1) \beta_2 r_{e2}} \right] V_o$$


$$\Rightarrow I_0 = \frac{V_0}{R_E} + \frac{(\beta_1 + 1)(\beta_2 + 1) V_0}{\beta_1 r_{e1} + (\beta_1 + 1)\beta_2 r_{e2}}$$

$$\Rightarrow I_0 \approx \frac{V_0}{R_E} + \frac{\beta_1 \beta_2 V_0}{\beta_1 r_{e1} + (\beta_1 + 1)\beta_2 r_{e2}}$$

$$\Rightarrow I_0 \approx \frac{V_0}{R_E} + \frac{\beta_1 \beta_2 V_0}{\beta_1 r_{e1} + \beta_1 \beta_2 r_{e2}} \quad \left(\begin{array}{l} \therefore \beta_1 + 1 \approx \beta_1 \\ \beta_2 + 1 \approx \beta_2 \end{array} \right)$$

$$\Rightarrow I_0 = \frac{V_0}{R_E} + \frac{V_0}{\frac{r_{e1}}{\beta_2} + r_{e2}}$$

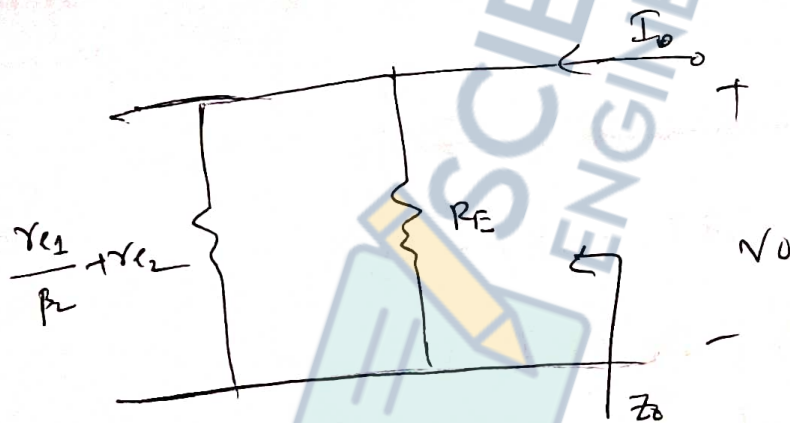which defines a parallel resistance r_w .




In general, $R_E \gg \frac{r_{e1}}{\beta_2} + r_{e2}$

$$Z_0 = R_E \parallel \left(\frac{r_{e1}}{\beta_2} + r_{e2} \right) \approx \frac{r_{e1}}{\beta_2} + r_{e2}$$

$$Z_0 \approx \frac{r_{e1}}{\beta_2} + r_{e2}$$

Some Important Questions

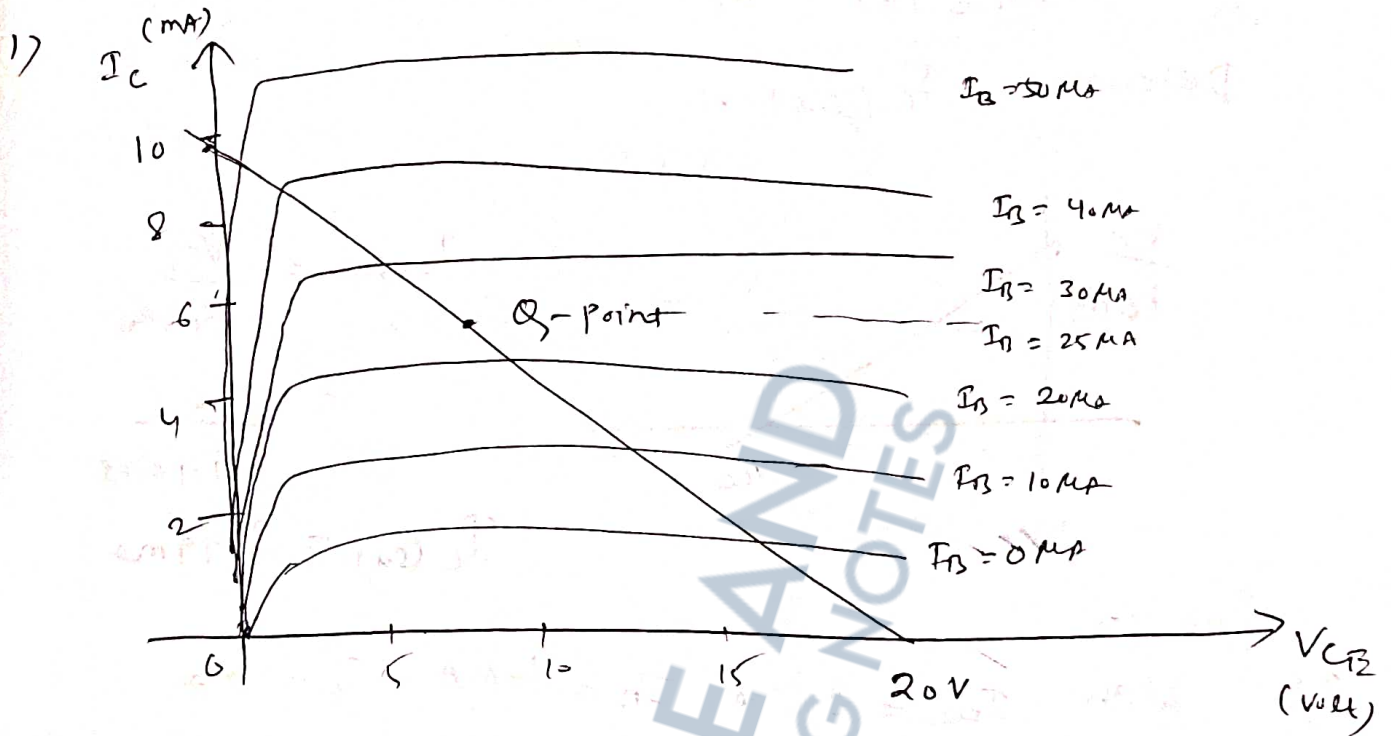

For the given figure, determine the required values of V_{CC} , R_C , and R_B for fixed-bias configuration.

Ans:

$$I_C(\text{max}) = \frac{V_{CC}}{R_C} = 10 \text{ mA} \quad \text{--- (1)}$$

$$V_{CC} = 20 \text{ V} \quad \text{--- (2)}$$

$$\Rightarrow \frac{20}{R_C} = 10$$

$$\Rightarrow R_C = \frac{20 \text{ V}}{10 \text{ mA}} = 2 \times 10^3$$

$$\Rightarrow R_C = 2 \text{ k}\Omega$$


From graph, $I_B = 25 \mu A$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20 - 0.7}{25 \times 10^{-6}} = 772 \text{ k}\Omega$$

2) For voltage divider bias circuit with

$$V_{CC} = 16V, R_C = 3.9k, R_E = 0.68k$$

Determine I_C (sat).

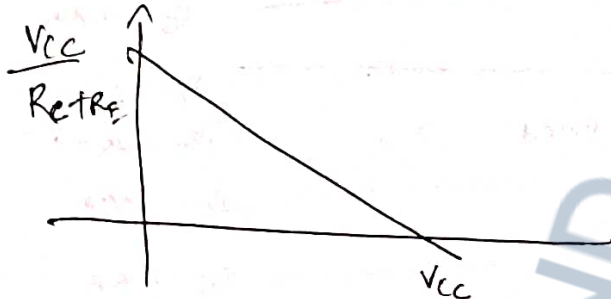

$$I_{C(sat)} = \frac{V_{CC}}{R_C + R_E}$$

$$= \frac{16}{3.9 + 0.68}$$

$$I_C(sat) = 3.49 \text{ mA}$$

3) With $I_{CE0} = 0.5 \text{ mA}$, $I_B = 16 \mu\text{A}$, $I_C = 2 \text{ mA}$
Calculate α , β , I_{CB0} .

Ans.. $\beta = \frac{I_C}{I_B} = \frac{2 \times 10^{-3}}{16 \times 10^{-6}} = \frac{1}{8} \times 10^3 = 125$

$$I_{CE0} = (\beta + 1) I_{CB0}$$

$$\Rightarrow 0.5 \times 10^{-3} = (125 + 1) I_{CB0}$$

$$\Rightarrow I_{CB0} = \frac{0.5 \times 10^{-3}}{126} = 3.96 \mu\text{A}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{125}{126} = 0.99$$

4) Determine R_C , R_E , V_E , V_B , R_2 and B
 for V.D bias ckt with $V_{CC} = 24V$, $R_C = 3R_E$,
 ~~$B = 120$~~ , $R_1 = 24k$, $I_B = 38.5 \mu A$, $I_C = 5mA$

$$I_C (\text{mA}) = 7.5 \text{ mA}$$

Ans ::

$$I_C (\text{mA}) = \frac{V_{CC}}{R_C + R_E}$$

$$\Rightarrow 7.5 \text{ mA} = \frac{24}{3R_E + R_E}$$

$$\Rightarrow 4R_E = \frac{24}{7.5 \times 10^{-3}} = 3.2 \times 10^3$$

$$\Rightarrow R_E = 0.8 \text{ k}\Omega$$

$$R_C = 3R_E = 2.4 \text{ k}\Omega$$

$$V_E = I_E R_E = (I_C + I_B) R_E$$

$$\Rightarrow V_E = (5 + 0.0385) \times 10^{-3} \times 0.8 \text{ k}\Omega$$

$$\Rightarrow V_E = 4.0308 \text{ V}$$

$$V_{BE} = V_B - V_E$$

$$\Rightarrow 0.7 = V_B - 4.0308$$

$$\Rightarrow V_B = 4.7308 \text{ V}$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1 + \beta) R_E}$$

$$= \frac{V_{CC} \times R_2 - V_{BE}}{R_1 + R_2} \cdot \frac{R_1 R_2 - (1 + \beta) R_E}{R_1 R_2}$$

$$\beta = \frac{I_C}{I_B} = \frac{5 \text{ mA}}{38.5 \text{ mA}} = \frac{5 \times 10^{-3}}{38.5 \times 10^{-6}} = 129.87$$

$$\Rightarrow 38.5 \times 10^{-6} = \frac{24 \times R_2 - 0.7}{24 \times 10^3 + R_2}$$

$$\frac{24 \times 10^3 R_2 - (129.87 + 1) \times 0.7 \times 10^3}{24 \times 10^3 + R_2}$$

$$\Rightarrow \boxed{\text{Find } R_2 =}$$

Approximate Analysis

$$V_D = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

$$\Rightarrow 4.7308 = \frac{24}{24 \times 10^3 + R_2} \times R_2$$

$$\Rightarrow 113.53 \times 10^3 + 4.7308 \times R_2 = 24 R_2$$

$$\Rightarrow 19.26 R_2 = 113.53 \times 10^3$$

$$\Rightarrow R_2 = 5.89 \times 10^3 = 5.89 \text{ k}\Omega$$

Check

$$\beta_{RE} \approx 7,10R_2$$

$$129.87 \times 0.8k\Omega \approx 10 \times 5.89 \times 10^3$$

$$103.89k\Omega \approx 50.89k\Omega$$

