
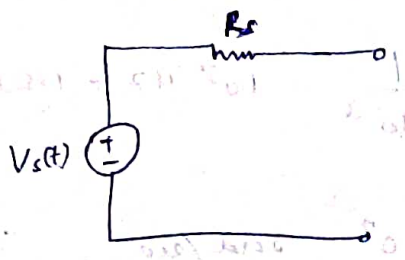


Exercises: Sedra, Smith

1.1

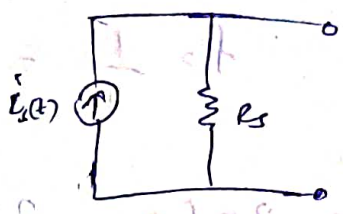

(a)



(b)

Q → (a) What are the open-circuit o/p voltage that would be observed.
 For each o/p terminal short-circuited;
 (b) → What current would flow?
 (c) For the representation to be equivalent, what must the relationship between V_s , R_s & I_s be?

Ans: $P_{oc} (a) = \frac{V}{I}$

$V_{oc} = V_s(t)$

For (b)

$V_{oc} = R_s \cdot I_s(t)$

$I_{sc} = \frac{V_s(t)}{R_s}$

For (c)

$I_{sc} = I_s(t)$

For equivalency $V_s(t) = R_s \cdot I_s(t)$

1.2 A signal source has an open-circuit voltage 10 mV & s.c. current 10 mA . What is the source resistance?

Ans: $R_s = \frac{V_{oc}}{I_{sc}} = \frac{10 \times 10^{-3}}{10 \times 10^{-6}} = 10^3 \Omega = 1\text{ k}\Omega$

1.3 Find the frequency f of a sine wave signal with period of 1 ms .

T = 1ms = 10^-3 sec.

f = 1/T = 1/10^-3 = 10^3 Hz = 1KHz.

W = 2πf = 2π x 10^3 rad/sec.

1.4) What is the period T of sine waveforms characterized by freq of

(a) f = 60 Hz

(b) f = 10^-3 Hz

(c) f_0 = 1 MHz

T = 1/60 = 0.016 = 0.0167 x 10^-3 = 16.7 ms.

T = 1/10^-3 = 10^3 sec = 1000 sec.

T = 1/10^6 = 10^-6 sec = 1 μs.

1.5// The UHF (Ultra High freq) television

broad cast band begins with channel 14

& extends from 470 MHz to 806 MHz. If

6 MHz is allocated for each channel, how

many channels can this band accommodate.

Ans: (806 - 470) / 6 = 336 / 6 = 56 channels. (a)

- Channels 14 to (475-1)
14 to (70-1)
14 to 69 (b)

1.6

1.7 Consider a 4 bit digital word

$D = b_3 b_2 b_1 b_0$ used to represent

an analog signal V_A that varies between 0V to +15V.

(a) Give D corresponding to $V_A = 0V, 1V, 2V, 15V$

(b) What change in V_A causes a change from 0 to 1 on (i) b_0 (ii) b_1 (iii) b_2 (iv) b_3 ?

(c) If $V_A = 5.2V$, what do you expect D to be? What is the resulting error representation?

Ans: (a) $\rightarrow 0 \rightarrow 0000$

$\rightarrow 2 \begin{array}{l} 1 \\ 0 \end{array} \rightarrow 0001$

$\rightarrow 2 \begin{array}{l} 2 \\ 0 \end{array} \rightarrow 0010$

$\rightarrow 2 \begin{array}{l} 7 \\ 0 \end{array} \rightarrow 0111$

$\rightarrow 2 \begin{array}{l} 15 \\ 7 \\ 3 \\ 1 \\ 0 \end{array} \rightarrow 1111$

(b)

$0000 \rightarrow 0$

$\rightarrow 0001 \rightarrow 1 \rightarrow 1V$

$\rightarrow 0010 \rightarrow 2 \rightarrow 2V$

$\rightarrow 0100 \rightarrow 4 \rightarrow 4V$

$\rightarrow 1000 \rightarrow 8 \rightarrow 8V$

c/

5.2 ✓

5 → 0.101

error → $5 - \frac{5 \cdot 2}{5} \times 100 = \frac{-20}{5} = -4\%$

Example 1.1

Consider an amplifier operating from $\pm 10V$ power supplies. It is fed with sinusoidal voltage having 1V peak & delivers a sinusoidal voltage of 9V peak to 1k Ω load.


The amplifier draws a current of 9.5 mA from each of its 2 power supplies.

The clt current of the amplifier is found to be sinusoidal with 0.1 mA peak.

Find the voltage gain, current gain; power gain & power drawn from dc supplies, power dissipated in the amplifier and the amplifier efficiency.

Ans: (a) $AV = \frac{9}{1} = 9$

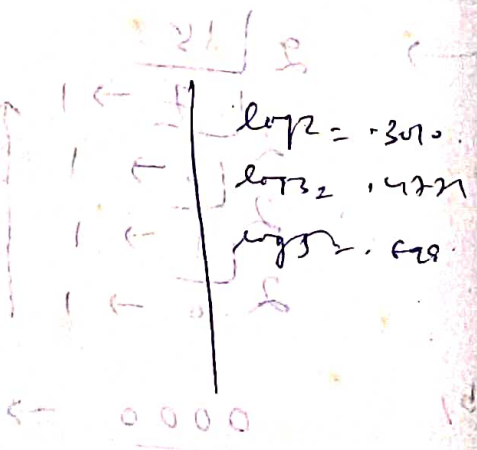$AV = 20 \log 9 = 20 \log 3^2$
 $= 40 \log 3$
 $= 40 \times 0.4771$
 $AV = 19.08 \text{ dB}$



$$(b) A_r = \frac{I_o}{I_i}$$

$$I_o = \frac{qV}{1 \mu s} = 9 \text{ mA}$$

$$A_r = \frac{9 \text{ mA}}{0.1 \text{ mA}} = 90$$

$$A_r = 20 \log 90 = 39.1 \text{ dB}$$

$$(c) P_L = V_{rms} I_{rms} = \frac{qV}{\sqrt{2}} \times \frac{9 \text{ mA}}{\sqrt{2}} = \frac{81}{2} = 40.5 \text{ mW}$$

$$P_I = V_{rms} I_{rms} = \frac{1}{\sqrt{2}} \times \frac{0.1 \text{ mA}}{\sqrt{2}} = \frac{0.1}{2} = 0.05 \text{ mW}$$

$$A_p = \frac{40.5}{0.05} = \frac{4050}{5} = 810$$

$$A_p = 10 \log 810 = 29.1 \text{ dB}$$

(d) Power drawn $P_{ac} = 2 \times 10 \times 9.5 = 2 \times 95 = 190 \text{ mW}$

$$P_{dissipated} = P_{ac} + P_I - P_L$$

$$= 190 + 0.05 - 40.5 = 149.55 \text{ mW}$$

$$(e) \eta = \frac{P_L}{P_{ac}} = \frac{40.5}{190} \times 100 = 21.3 \%$$

Ex: 1.2:

A transistor amplifier has the transfer characteristics

$$V_o = 10 - 10^{11} e^{40V_i} \quad (1)$$

which applies for $V_i \geq 0$ & $V_o \geq 0.3V$.

Find the limits L^- & L^+ & corresponding values of V_i . Also find the value of dV_o/dV_i

bias voltage V_B that results in $V_o = 5V$ & voltage gain at corresponding operating point.

Ans: The limit L^- is obviously $0.3V$.

The corresponding value V_i obtained by substituting $V_o = 0.3V$ in eq (1)

$$0.3 = 10 - 10^{11} e^{40V_i}$$

$$\Rightarrow 10^{11} e^{40V_i} = 10 - 0.3 = 9.7$$

$$e^{40V_i} = \frac{9.7}{10^{11}}$$

$$40V_i = \ln\left(\frac{9.7}{10^{11}}\right)$$

$$\Rightarrow V_i = \frac{\ln\left(\frac{9.7}{10^{11}}\right)}{40} = \frac{20.0278160}{40} = 0.690$$

L^+ , determined by $V_i = 0$,

$$L^+ = 10 - 10^{-11} = 10$$

To bias the device so that $V_o = 5V$,

We require V_B whose value is obtained by

Substituting

$$V_0 = 5V$$

$$V_0 = 10 - 10^{-11} e^{40V_2}$$

$$\rightarrow 5 = 10 - 10^{-11} e^{40V_2}$$

$$\Rightarrow 5 = 10^{-11} e^{40V_2}$$

$$\Rightarrow \frac{40V_2}{e} = \frac{5}{10^{-11}} = 5 \times 10^{11}$$

$$\Rightarrow 40V_2 = \ln(5 \times 10^{11})$$

$$\Rightarrow V_2 = \frac{\ln(5 \times 10^{11})}{40} = 0.673 \text{ V.}$$

→ The gain at the operating point is obtained by evaluating the derivative $\frac{dV_0}{dV_2}$ at $V_2 = 0.673 \text{ V.}$

$$V_0 = 10 - 10^{-11} e^{40V_2}$$

$$\Rightarrow \left. \frac{dV_0}{dV_2} \right|_{V_2=0.673} = 10^{-11} \cdot 40 \cdot e^{40 \cdot 0.673}$$

$$= 10^{-11} \times 40 \times (e^{269.2})$$

$$= 10^{-11} \times 4.91 \times 10^{11} \times 40$$

$$= 196.4$$

$$A_v \approx 200 \text{ V/V.}$$

Exercise

1.8. An amplifier has a voltage gain of $100 \frac{V}{V}$ & current gain 1000 A/A. Express voltage & current gain in dB & find the power gain.

Ans :

0

$$A_v = 20 \log (v_o)$$

$$= 20 \times 2$$

$$A_v = 40 \text{ dB}$$

$$A_p = 20 \log (v_o)$$

$$= 20 \times 3$$

$$A_p = 60 \text{ dB}$$

$$A_p = A_v \times A_p$$

$$= 100 \times 1000$$

$$= 10^5$$

$$A_p = 10 \log 10^5$$

$$= 5 \times 10$$

$$A_p = 50 \text{ dB}$$

19/11

NSVT-2008

2/ An amplifier operating from $\pm 3V$ supplies provides a $2-2 V_{peak}$ sine wave across a load load, when provided with $0.2V_{peak}$ output from which $10mA$ peak is drawn. The avg. current in each supply is measured to be $20mA$. Find the voltage gain, current gain & power gain expressed as ratios in dB as well as supply power, amplifier dissipation & amplifier efficiency.

Ans :

Voltage gain = $\frac{\text{O/P Voltage}}{\text{I/P Voltage}}$

$$= \frac{2.2}{0.2} = 11$$

A_v in dB = $20 \log 11 = 20.827 \text{ dB}$

Current gain (A_I) = $\frac{\text{O/P Current}}{\text{I/P Current}}$

O/P Current = $\frac{\text{O/P Voltage}}{\text{O/P load resistance}} = \frac{2.2}{100} = 0.022 \text{ Amp}$

$= 22 \text{ mA}$


$A_I = \frac{\text{O/P Current}}{\text{I/P Current}} = \frac{22 \text{ mA}}{1.0 \text{ mA}} = 22$

A_I in dB = $20 \log 22 = 26.848 \text{ dB}$

A_P = Power gain = $\frac{\text{O/P Power}}{\text{I/P Power}}$

O/P Power = $V_{\text{rms}} \cdot I_{\text{rms}} = \frac{2.2}{\sqrt{2}} \times \frac{22 \text{ mA}}{\sqrt{2}}$

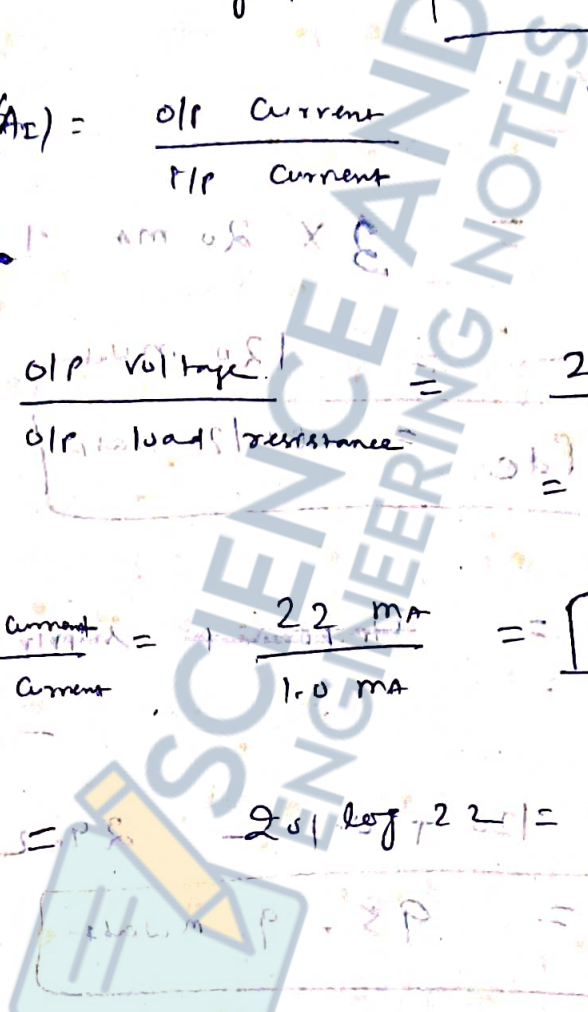I/P Power = $V_{\text{rms}} \times I_{\text{rms}} = \frac{0.2}{\sqrt{2}} \times \frac{1 \text{ mA}}{\sqrt{2}} = 0.1 \text{ mWatt}$



$$A_p = \frac{24.2}{0.1} = 242$$

$$(A_p)_{dB} = 10 \log 242 = 23.838$$

Supply power

$$P_{dc} = 3 \times 20 \text{ mA} + 3 \times 20 \text{ mA}$$

$$= 120 \text{ mA}$$

$$P_{dc} = 0.12 \text{ watt}$$

$$P_{dissipated} = \text{supply power} + \text{I/P power} - \text{O/P power}$$

$$= 120 + 10 - 24.2$$

$$P_{dissipated} = 95.8 \text{ mWatt}$$



Amplifier efficiency

$$\eta = \frac{\text{O/P power}}{\text{supply power}} = \frac{24.2}{120} = 20.16\%$$

$$\eta = 20.16\%$$

Clipper :-

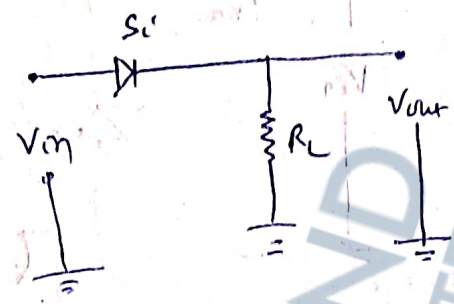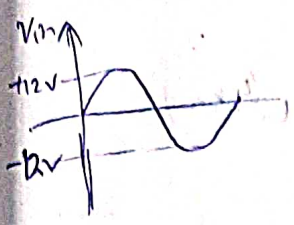1) For -ve series clipper shown in fig (1), what is the peak o/p voltage from the ckt?



Ans: During +ve half cycle, →

($V_{in} > 0.7V$)




$V_m < 0.7$
Diode reverse biased,
o/p = open ckt,
o/p = 0.

The diode is forward biased. The voltage drop across the diode is 0.7V.

$$V_m - 0.7 = V_{out} = 0$$




$$\Rightarrow V_{out} = V_m - 0.7 = 12 - 0.7 = 11.3V.$$

During -ve half cycle :-

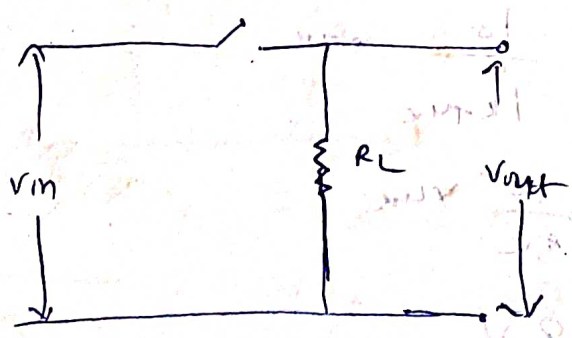

The diode is reverse biased. It acts as an open ckt. o/p is zero.

V_{out} is

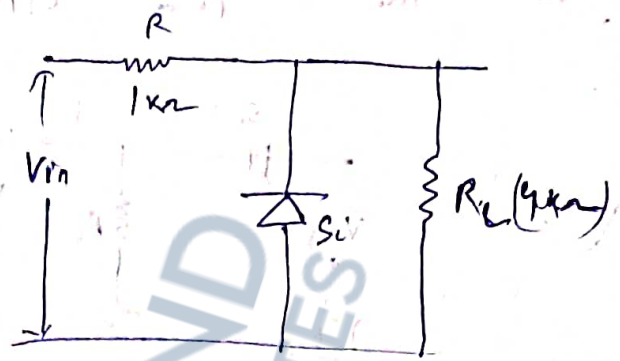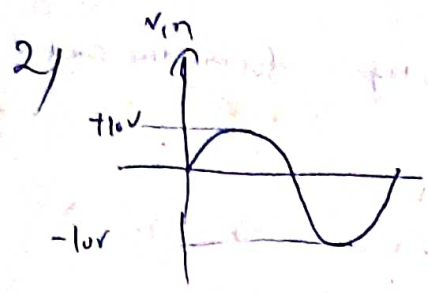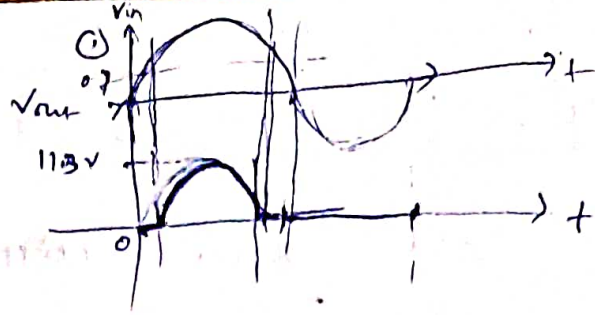

Find the V_{out} voltage waveform.

Ans: During the half cycle


The diode is reverse biased.



$$\begin{aligned}
 V_{out} &= I \times R_L \\
 &= \frac{V_{in}}{R + R_L} \times R_L \\
 &= \frac{10}{1k + 4k} \times 4k \\
 &= \frac{10}{5k} \times 4k \\
 V_{out} &= 8V
 \end{aligned}$$

During -ve half cycle

The diode is forward biased.

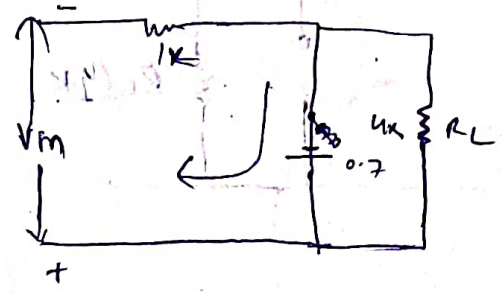


The o/p across Load is ~~0.7V~~ -0.7V.

∴ The o/p voltage waveform will be




3)

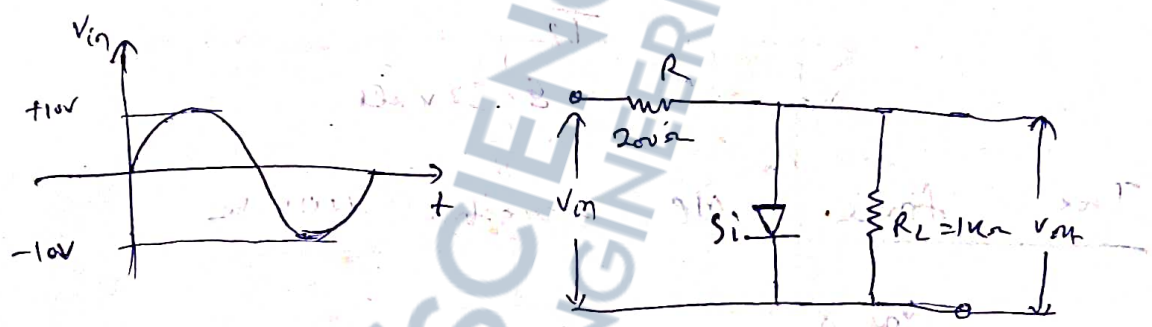

What is the o/p?


During the half cycle:

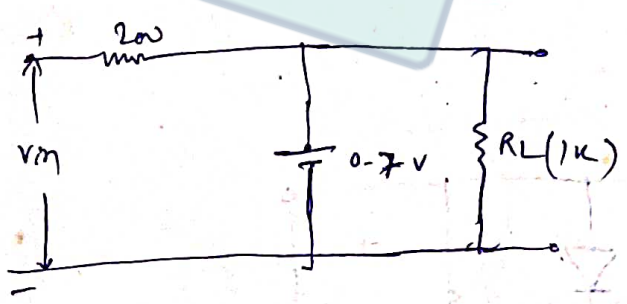

The diode is forward biased.




$V_{out} = 0.7V$

During -ve half cycle


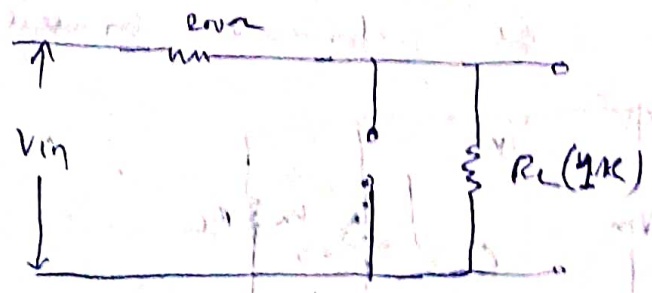


$$\begin{aligned}
 V_{out} &= I \times R_L \\
 &= \frac{V_m}{2\omega + 1000} \times 1000 \\
 &= \frac{-10}{12} \times 1000 \\
 &= -\frac{1000}{12} \\
 V_{out} &= -8.33 \text{ Volt}
 \end{aligned}$$



The final O/P waveform will be

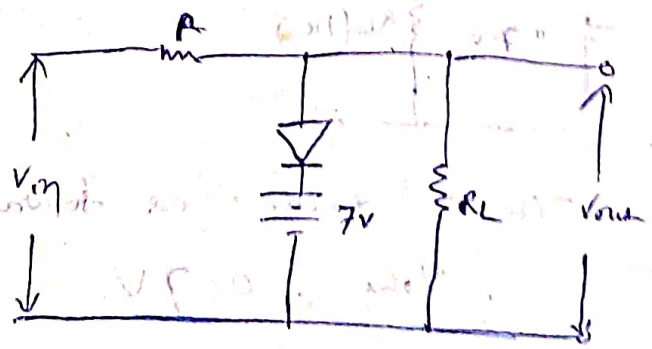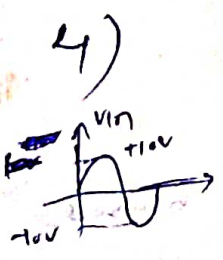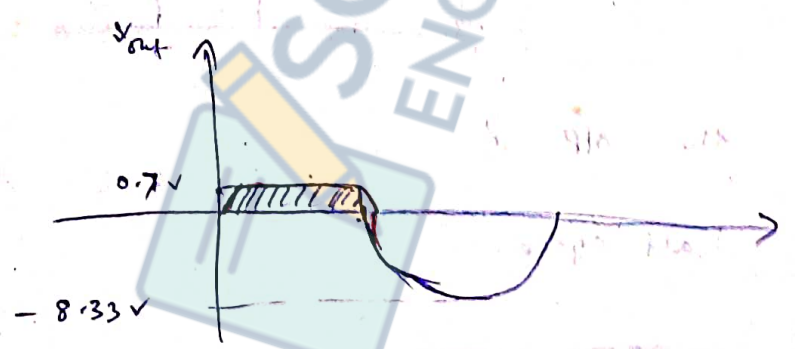

Five biased clipper

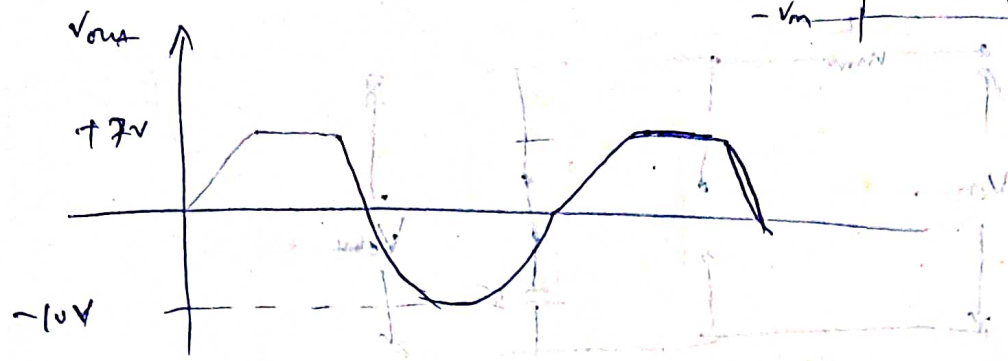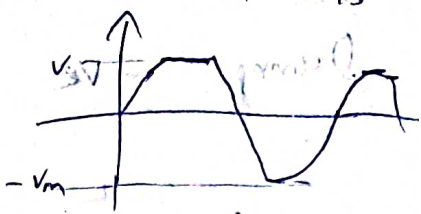


5)

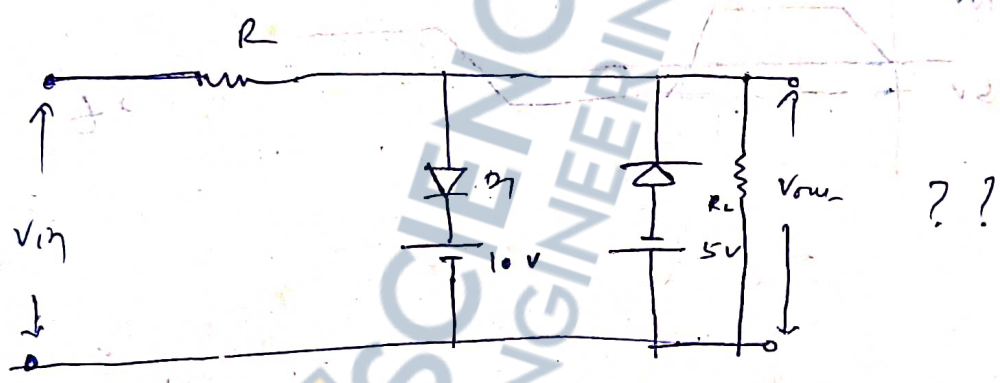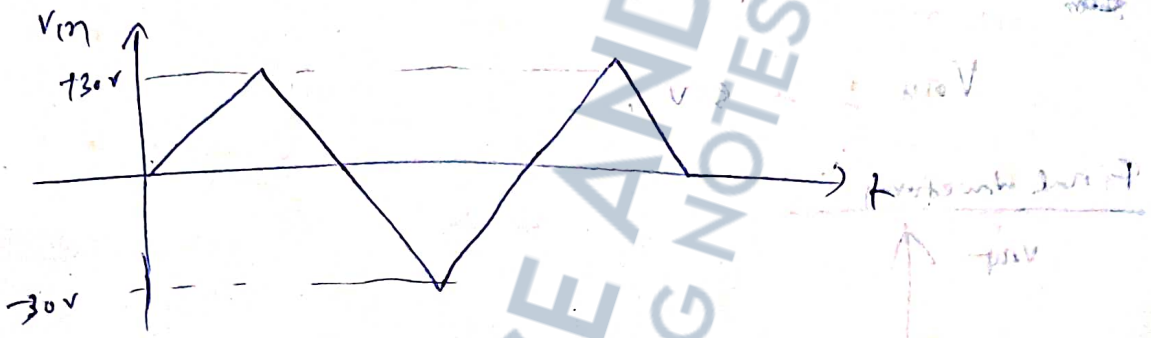


Ans: During the half cycle D_1 is forward biased.

and D_2 is reverse biased.

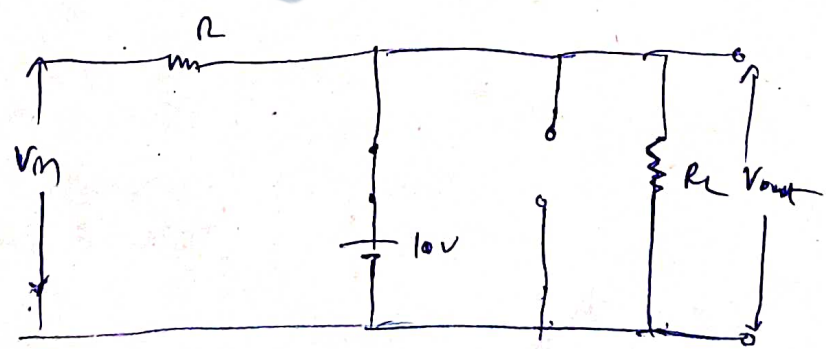

$V_{out} = 10V$

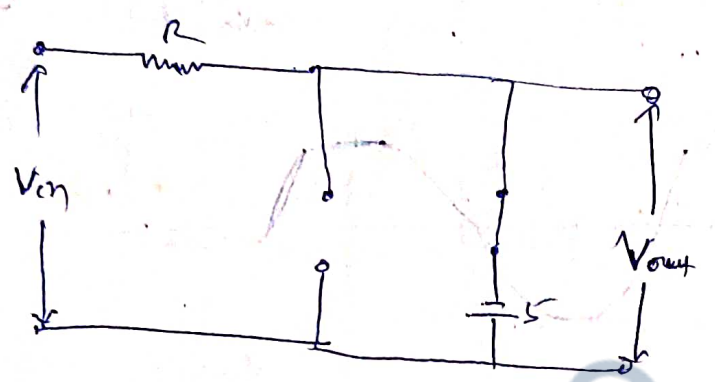Dummy -ve half cycle (D1 is reverse biased, D2 is forward biased)



$V_{out} = -5V$

Final waveform



79. A silicon diode is said to be 1 mA device displays a forward voltage of 0.7 V, at current of 1 mA. Evaluate the junction scaling constant I_S in the event when $n = 1$ or 2.

Ans :-

$$I_D = I_S \left(e^{V_D / n V_T} - 1 \right)$$

~~$$I_D \approx I_S e^{V_D / n V_T}$$~~

$$I_D \approx I_S \left(e^{V_D / n V_T} \right)$$

$$\Rightarrow I_S = I_D \cdot e^{-\frac{V_D}{n V_T}}$$

$$= (1 \times 10^{-3})$$

$$e^{-\frac{0.7}{(1) \cdot 25 \times 10^{-3}}} \quad \left. \begin{array}{l} n = 1 \\ V_T = 25 \text{ mV} \end{array} \right\}$$

$$= 10^{-3} \cdot e^{-\frac{700}{25}}$$

$$I_S = 6.9 \times 10^{-16} \text{ Amp}$$

for $\eta = 2$

$$I_s = 10^{-3} \cdot e^{-\frac{700}{2 \times 25}}$$

$$I_s = 8.3 \times 10^{-11} \text{ Amp}$$

80) A crystal diode having an internal resistance $r_f = 10 \Omega$ is used for center tapped full wave rectification. If the applied voltage is $V = 50 \sin(\pi t)$ and load resistance is $R_L = 1k\Omega$.

- (a) Find efficiency
- (b) Ripple factor
- (c) Draw O/P ~~current~~ current/voltage waveform.

Ans :- $I_m = \frac{V_m}{r_f + R_L} = \frac{50}{10 + 1000} = 0.0495 \text{ Amp.}$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.0495}{\pi} = 0.0315 \text{ Amp.}$$

$$V_{dc} = I_{dc} \times R_L = 0.0315 \times 1000 = 31.5 \text{ Volt.}$$


$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.0495}{\sqrt{2}} = 0.035 \text{ Amp.}$$

(a) Efficiency $(\eta) = 0.812 \times \frac{R_L}{R_f + R_L}$

$$= 0.812 \times \frac{1000}{10 + 1000}$$

$$= 0.8039$$

$$\eta = 80.39 \%$$

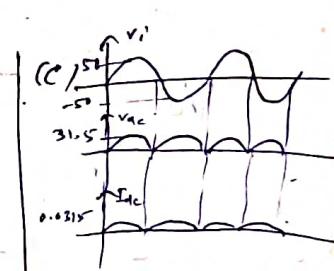

(b) Ripple factor = $\sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{0.035}{0.0315}\right)^2 - 1}$

$$= 0.4842$$

More Problems

✓ BPUT-2013

A Silicon diode having 20Ω internal resistance is used as half wave rectifier.

If the applied input voltage is $50 \sin 100\pi t$ and load resistance 80Ω .

then find

- (a) I_m, I_{dc}, I_{rms}
- (b) output freq and ripple factor
- (c) AC i/p and o/p power and efficiency.

Ans :-

Given

Internal resistance, $r_f = 20\Omega$.

$V_i = 50 \sin 100\pi t$

$R_L = 80\Omega$.

$$(a) \quad I_m = \frac{V_m}{r_f + R_L} = \frac{50}{20 + 80} = \frac{50}{100} = 0.06 \text{ Amp.}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{0.06}{\pi} = 0.019 \text{ Amp.}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.06}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{2} = \frac{0.06}{2} = 0.03 \text{ Amp.}$$

(b) O/P freq for half wave = (i/p) freq (Supply)

$$W = I_{rms} \pi$$

$$\Rightarrow 2\pi f_m I_{rms} = I_{rms} \pi$$

$$\Rightarrow f_m = 50 \text{ Hz}$$

$$\Rightarrow f_{out} = f_m = 50 \text{ Hz}$$

ripple factor (r)

$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{0.03}{0.019}\right)^2 - 1}$$

$$r = 1.22$$

(c) A/c i/p power = $I_{rms}^2 (r_f + R_L)$

$$= (0.03)^2 (20 + 8)$$

$$P_m = 0.738 \text{ watt}$$

d.c o/p power, $P_{out} = I_{dc}^2 R_L$

$$= (0.019)^2 \times 8$$

$$P_{out} = 0.2888 \text{ watt}$$

$$\eta = \frac{P_{out}}{P_m} = \frac{0.2888}{0.738} = 0.3913$$


(efficiency)

$$\eta (\text{efficiency}) = 39.13 \%$$

Note :

If we consider

Silicon diode,

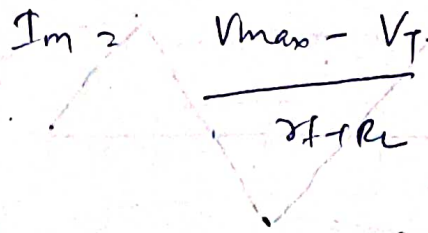

V_{TF} Cut-in voltage of 'Si' diode.
or Threshold voltage for $V_{Si} = 0.7V_{out}$

$$I_m = \frac{V_{max} - V_T}{R_f + R_L} = \frac{50 - 0.7}{20 \times 10^3 + 800} = 0.0601 \text{ Amp.}$$

Ideal diode

$$(I_m)_{Ideal} = \frac{V_{max}}{R_f + R_L} = \frac{50}{820} = 0.0609 \text{ Amp.}$$

$$(I_m)_{Si} \approx (I_m)_{Ideal} \approx 0.06 \text{ Amp.}$$

→ For accurate calculation take

$$(I_m)_{Si} = 0.0601 \text{ Amp.}$$


→ Rest procedure are same as mentioned.


2) BPUT - 2012

Consider the half-wave rectifier.


If V_{in} is a triangle wave with peak voltage of 2V and diode has

$V_d = 0.5V$. Sketch the V_{out} .

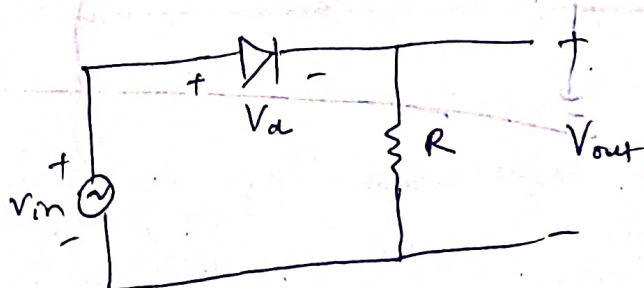

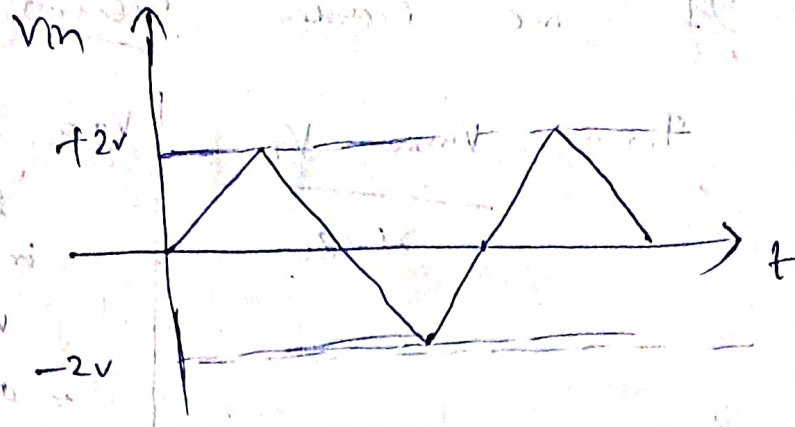

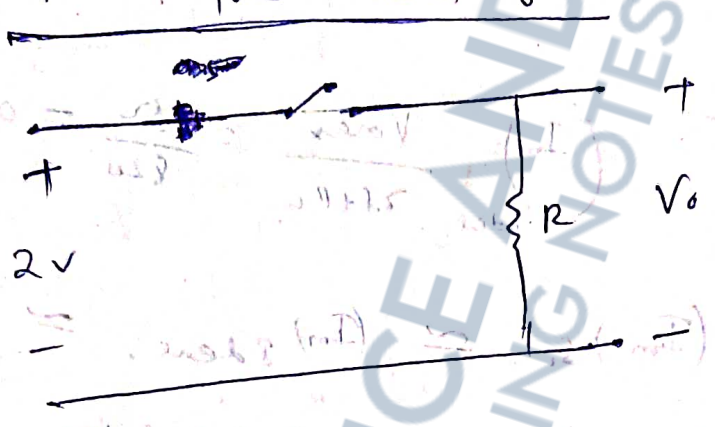
Ans :- For the half cycle, (less than 0.5v)



For \uparrow voltage less than $\frac{0.5v}{}$, (cutoff)

No current flows, diode reverse biased
 (open circuit), $V_o = 0v$.

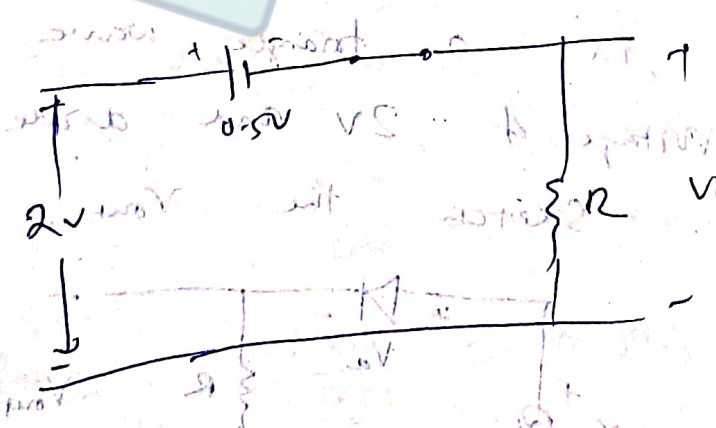→ When \uparrow voltage exceeds $\frac{0.5v}{}$, (short circuit)
 diode forward biased, (short circuit)



Applying KVC



$$2 - 0.5 - V_o = 0$$

$$\Rightarrow V_o = 1.5 \text{ V}$$

→ For i/p 0.5 V to 0 V , diode R.B. $O/P = 0$.

For -ve half cycle.

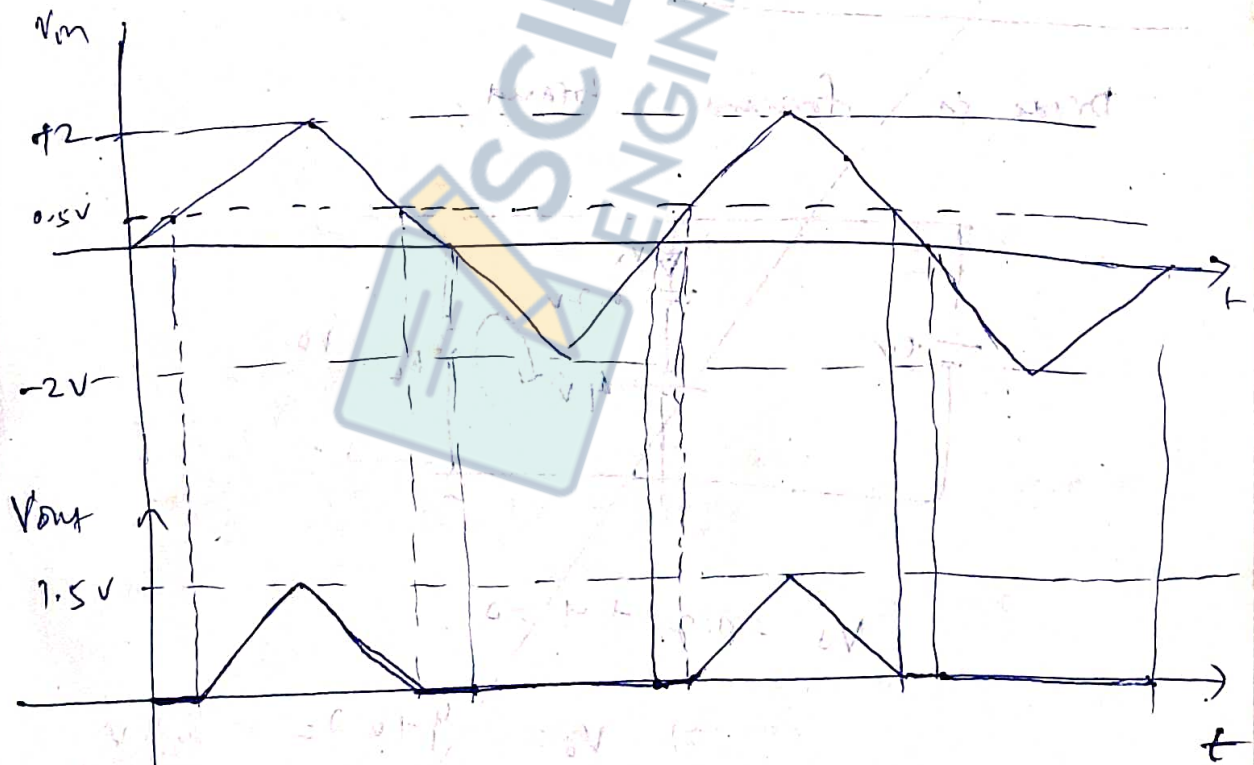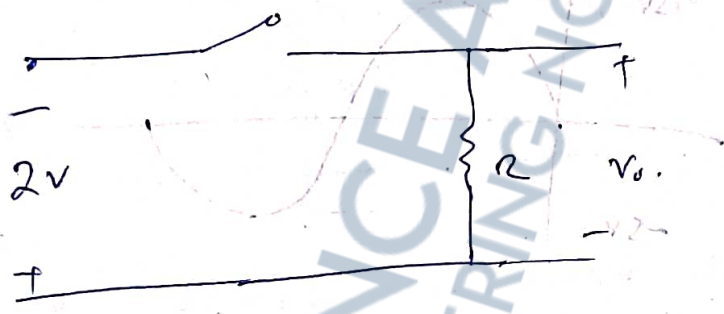
Diode is reverse biased open circuit.
The $O/P = 0$ volt.



So positive i/p above 0.5 V F. Biased.
" " below " R. Biased.


37


10V (r-r)

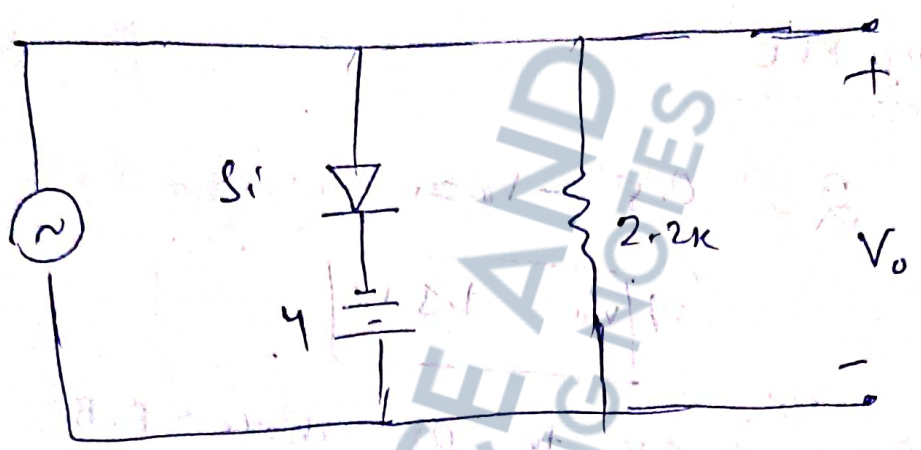


P_{rms} $V_{o2}?$

Ans. = $\frac{1}{P}$ voltage

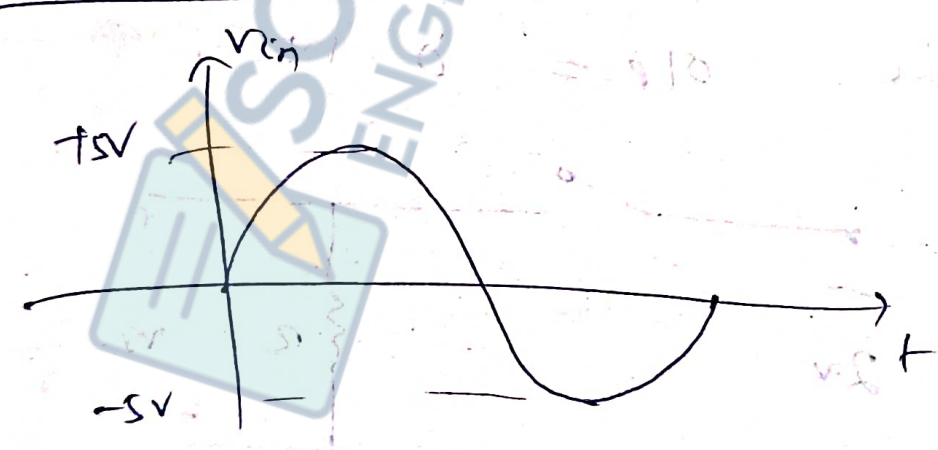

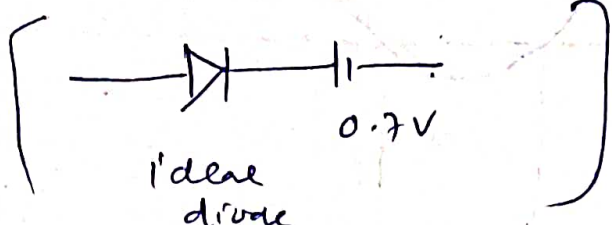→ as Si diode can be redrawn
 as 

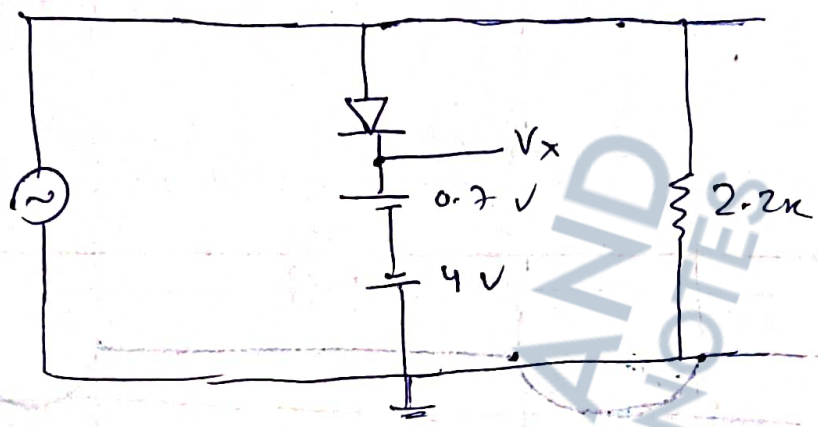

To find potential across, -ve end of diode
 (V_x), Applying KVL


$$V_x + 0.7 + 4 = 0$$

$$\Rightarrow V_x = -4 + 0.7 = -3.3V$$




So for all the ≥ 0 voltages i.e. more than
 diode is forward biased.
 $-3.3V$

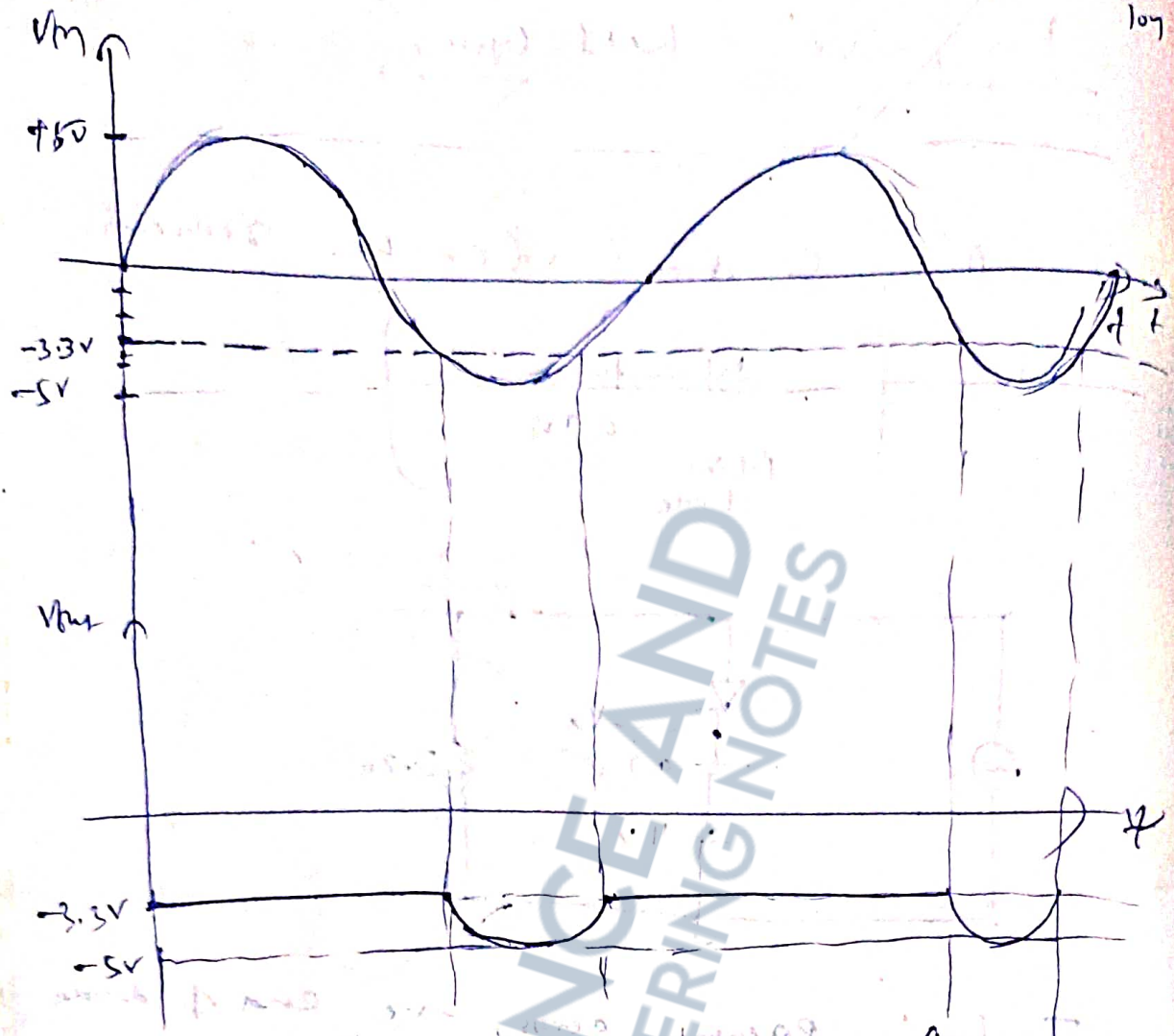
and less than $-3.3V$ is
 reverse biased.




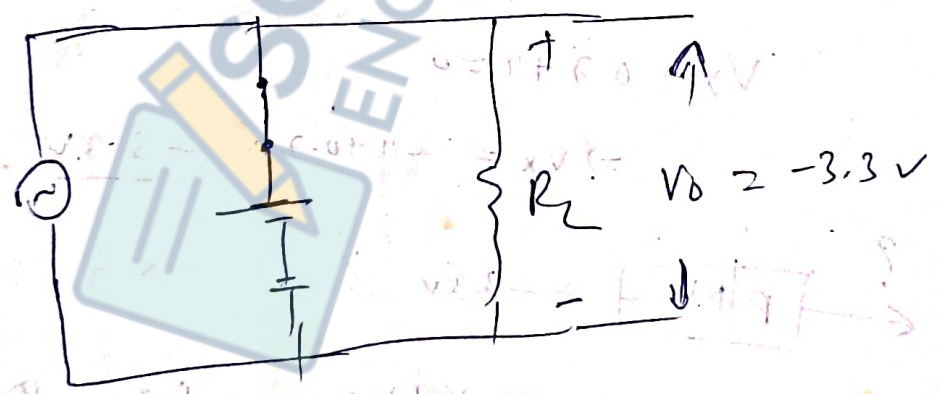
For the V_r voltage above $-3.3V$ (i.e. 0 to $-3.29V$)



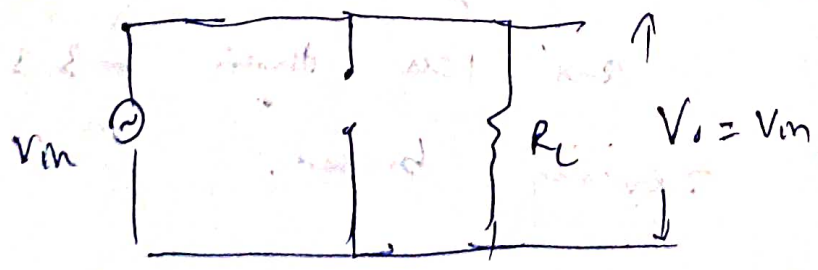
or below $-3.3V$ i.e. $(-3.3V \text{ to } -5V)$



4.)

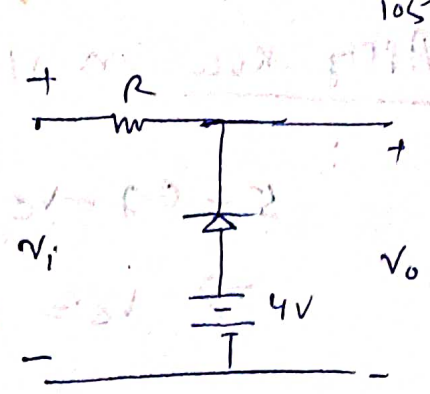
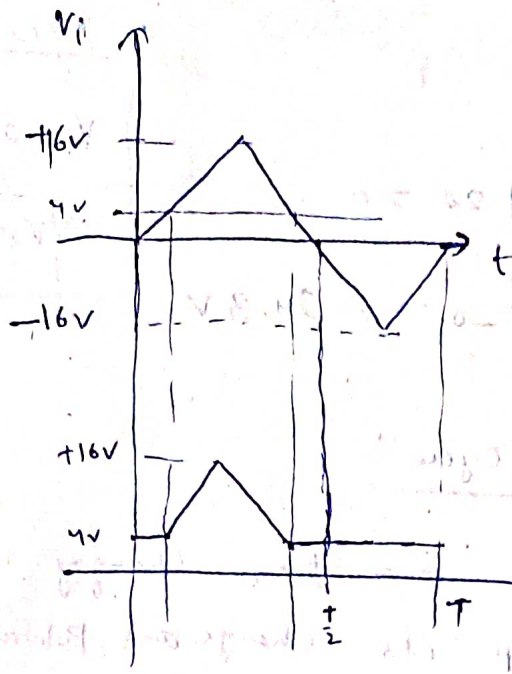


Ans. =>

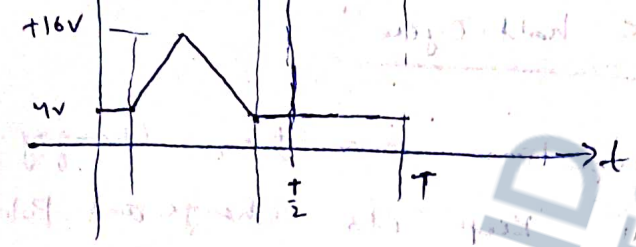


5)

Clamper Ckt. Problem

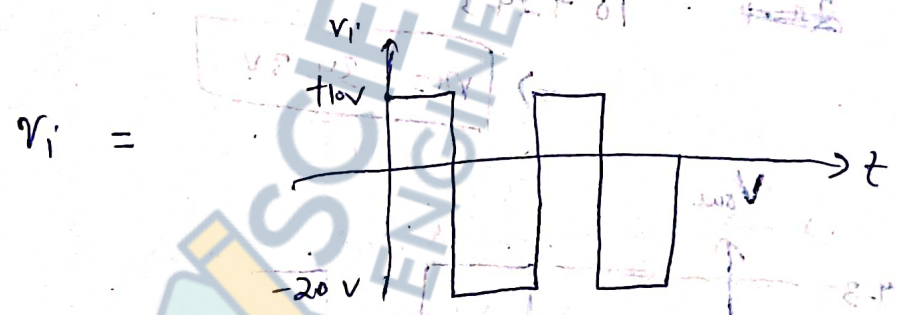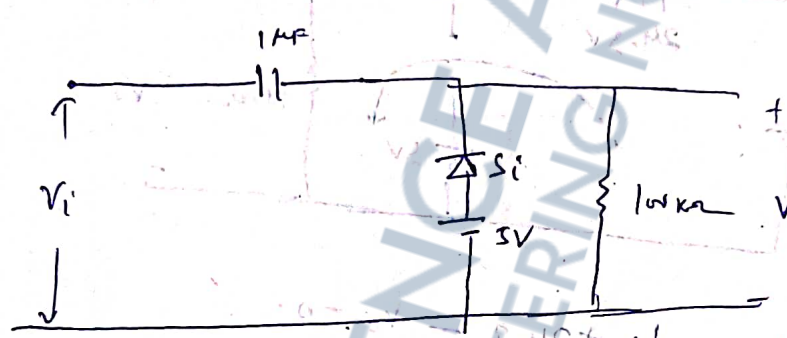

Ans.:

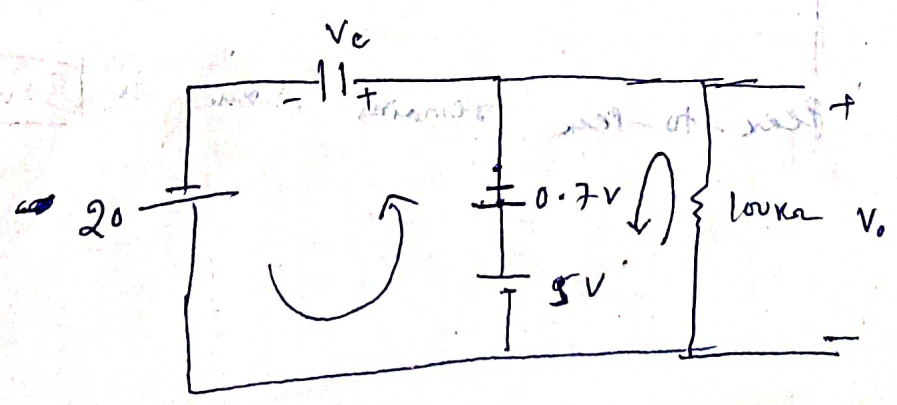First start the analysis for the cycle, when the diode is forward biased. i.e. -ve half cycle.



Apply KVL in r/p

$$5 - 0.7 - V_C + 25 = 0$$

$$\Rightarrow V_C = 25 - 0.7 = 24.3 \text{ V}$$


KVL in r/p

$$V_0 + 0.7 - 5 = 0$$

$$\Rightarrow V_0 = 4.3 \text{ V}$$


Then for +ve half cycle

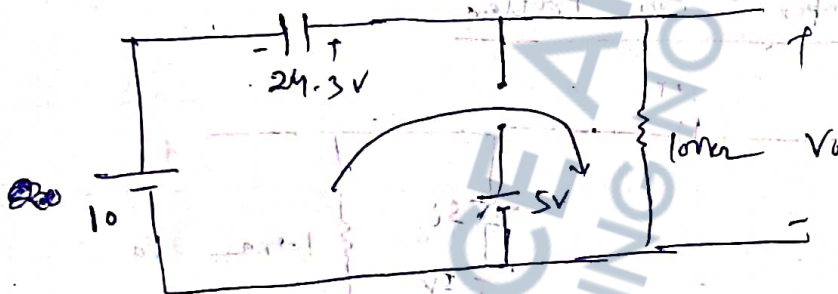Since discharge time more than charging time, capacitor will keep its charge and polarity.




$$10 + 24.3 - V_0 = 0$$

$$\Rightarrow V_0 = 34.3 \text{ V}$$

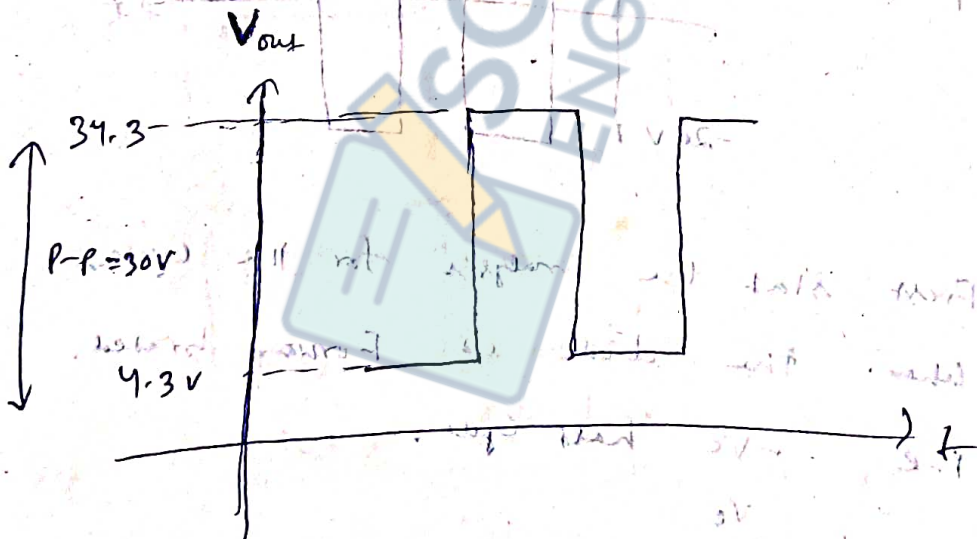


Peak-to-peak remains same as 30 V .

Zener diode

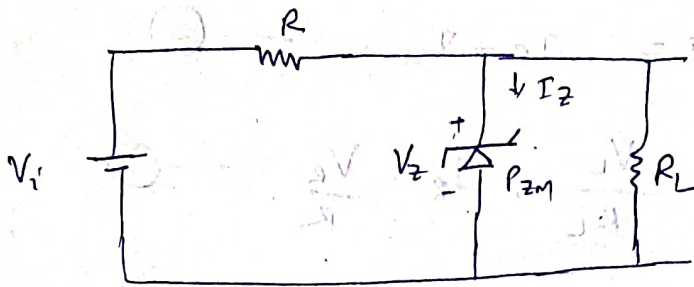

Basic Zener regulator

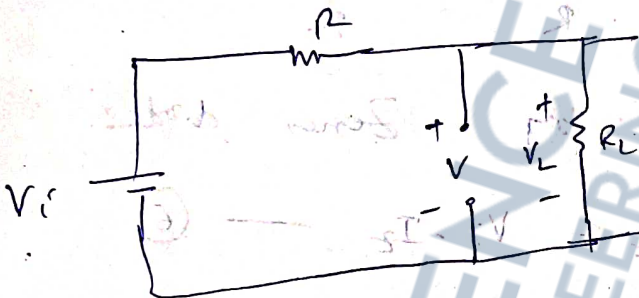1) Determine the state of the Zener diode by removing it from the circuit and calculating the voltage across the resulting open ckt.



$$V = V_L = \frac{V_i \cdot R_L}{R + R_L}$$

If $V < V_Z$, the diode is off, open ckt equivalence is substituted.

If $V \geq V_Z$, the Zener diode is on, it is replaced by a battery source having voltage equal to breakdown voltage of Zener diode.

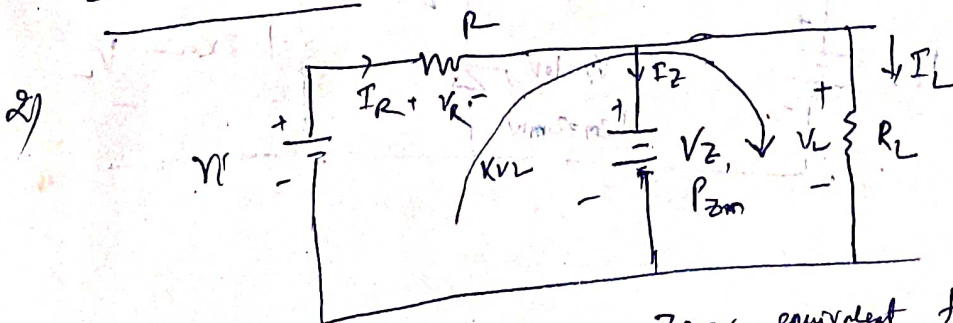


Fig:- Zener equivalent for "on" situation.

$$I_R = I_Z + I_L \quad \text{--- (1)}$$

$$I_Z = I_R - I_L \quad \text{--- (2)}$$

$$I_L = \frac{V_L}{R_L}, \quad I_R = \frac{V_R}{R} \quad \text{--- (3)}$$

Applying KVL in the outer loop,

$$V_i - V_R - V_L = 0$$

$$\Rightarrow V_R = V_i - V_L \quad \text{--- (4)}$$

$$\therefore I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R} \quad \text{--- (5)}$$

Power dissipated by Zener diode

$$P_Z = V_Z \cdot I_Z \quad \text{--- (6)}$$


which must be less than P_{ZM} specified

for the device.


Ex: - (6) For the Zener diode n/w, determine

(a) V_L, V_R, I_Z, P_Z .

(b) Repeat (a) with $R_L = 3k\Omega$

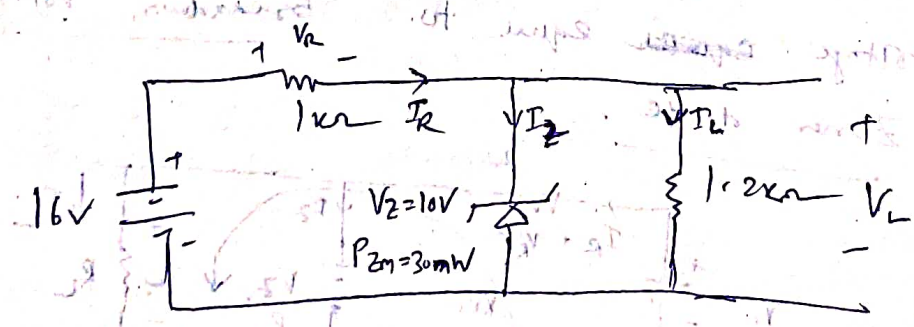

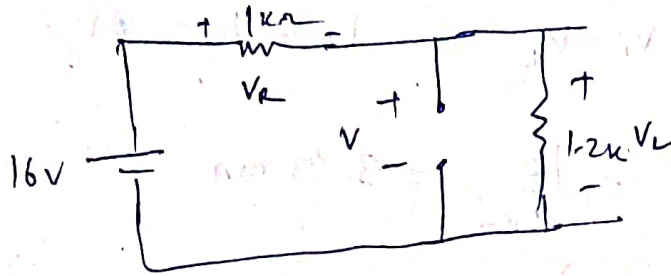Ans (a) Determining the state of Zener diode



$$V = \frac{16 \times 1.2k\Omega}{(1 + 1.2)k\Omega} = 8.73V$$

Since $V < V_Z$, i.e. $8.73V < 10V$, the diode is off state.

$$\therefore V_L = V = 8.73V$$

$$V_R = V - V_L = 16 - 8.73 = 7.27V$$

$$I_Z = 0A$$

$$P_Z = 0 \text{ watt } (\because V_Z \cdot I_Z = 0)$$


(b)

When $R_L = 3k\Omega$

$$V = \frac{16 \times 3k\Omega}{(1 + 3)k\Omega} = \frac{16 \times 3}{4} = 12V$$

Since $V > V_Z$, i.e. $12V > 10V$, diode is on state

Replacing by "on" state model.

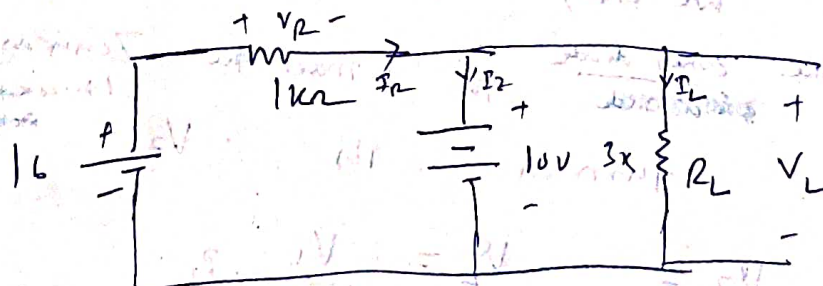

$$V_L = V_Z = 10V$$

$$V_R = V_i - V_L = 16 - 10 = 6V$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{3k\Omega} = 3.33 \text{ mA}$$

$$I_R = \frac{V_R}{R} = \frac{6}{1k\Omega} = 6 \text{ mA}$$


$$I_Z = I_R - I_L = 6 - 3.33 = 2.67 \text{ mA}$$

power dissipated is

$$P_Z = I_Z \cdot V_Z = 2.67 \times 10^{-3} \times 10V = 26.7 \text{ mW}$$

which is less than P_{ZM} i.e. 30mW.

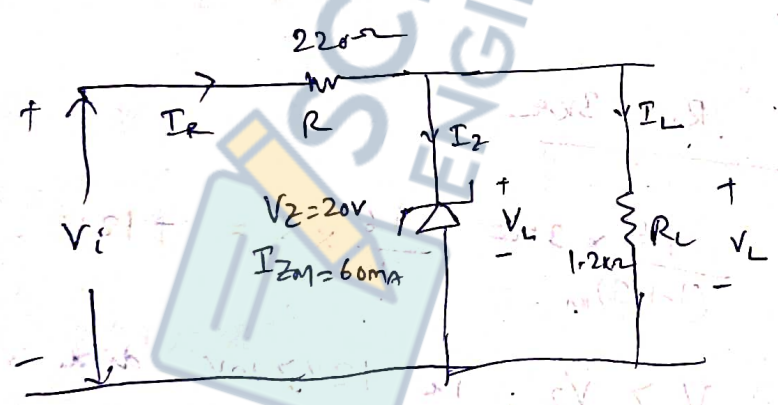7) For the given circuit, determine the range of values of V_i that will maintain the Zener diode in "on" state.



Ans: We know, the minimum voltage required across the Zener diode to make the Zener diode (breakdown voltage) turn on is V_Z .

$$V_Z = V_L = \frac{V_i}{R + R_L} \times R_L$$

So min input voltage required is, 111

$$(V_i)_{\min} = \frac{V_Z \times (R_1 + R_2)}{R_2}$$

$$= \frac{20 \times (220\Omega + 120\Omega)}{120\Omega}$$

$$= \frac{24 \times 142}{6}$$

$(V_i)_{\min} = 23.67 \text{ V}$

→ Since Zener voltage will act as voltage regulator, V_L will be always 20V.

$$I_L = \frac{V_L}{R_L} = \frac{20}{1.2 \text{ k}\Omega} = 16.67 \text{ mA}$$

→ → To find the max $\% \text{P}$ Variation

$$I_L = \text{const} = 16.67 \text{ mA}$$

I_Z will max vary up to 60mA as specified for the Zener diode.

$$(I_R)_{\max} = I_L + I_{Z\max}$$

$$= 16.67 \text{ mA} + 60 \text{ mA}$$

$$(I_R)_{\max} = 76.67 \text{ mA}$$


$$(V_i)_{\max} = (V_R)_{\max} + V_Z$$

$$= I_{R\max} R_1 + V_Z$$

$$= 76.67 \times 220 + 20$$

$$(V_i)_{\max} = 16.87V + 20$$


$$(V_o)_{\max} = 36.87V$$

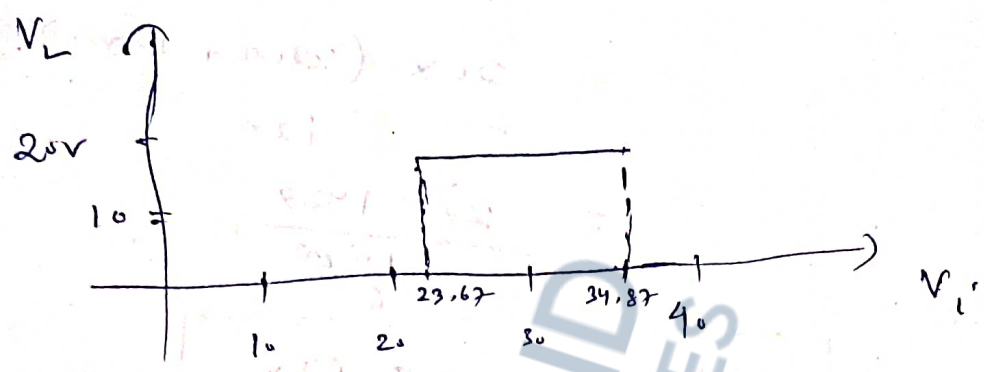

We can see from the plot that, even if the input voltage is fluctuating between 23.67 to 34.87 V, the output voltage remains constant as $\frac{20V}{1}$.

8) (a) Determine the range of R_L & I_L that will result in V_{RL} being maintained at 10V.

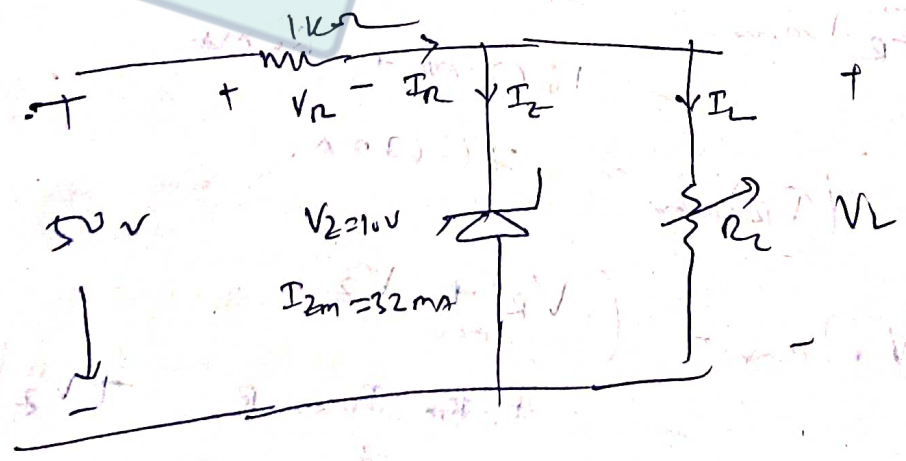(b) Determine the max^m wattage rating of diode.



Ans: We know to make the Zener turn on, min voltage required is V_Z .

$$\text{and } V_Z = V_L = \frac{V_i \times R_L}{R + R_L}$$

$$\Rightarrow 10 = \frac{50 \times R_L}{1k + R_L}$$

$$\Rightarrow 10 = \frac{50 \times R_L}{1000 + R_L}$$

$$\Rightarrow 10,000 + 10R_L = 50R_L$$

$$\Rightarrow 40R_L = 10,000$$

$$\Rightarrow R_L = 250 \Omega$$

Min R_L , (R_L) min required is $\boxed{250 \Omega}$.

To make the diode 'on'.

To find (R_L) max, to maintain Zener

as voltage stabilizer

We know Applying KVL,

$$V_i - V_R - V_L = 0$$

$$\Rightarrow V_i - I_R R - 10 = 0$$

$$\Rightarrow I_R R = V_i - 10$$

$$\Rightarrow R = \frac{V_i - 10}{I_R}$$

$$\Rightarrow 1000 = \frac{50 - 10}{I_R} \quad \text{--- (1)}$$

To find $(R_L)_{max}$, (I_L) should be minimum. $(I_L)_{min}$.

→ Since R is const = $1k\Omega$

from eqn ①, $I_R = \text{const}$.

⇒ $I_L + I_Z = \text{const}$.

To find $(I_L)_{min}$, (I_Z) has to be max

$(I_Z)_{max} = 32\text{mA}$.

⇒ ~~$(I_L)_{min} = 40$~~

from eqn

$1000 = \frac{40}{(I_L)_{min} + (I_Z)_{max}}$

⇒ $(I_L)_{min} + (I_Z)_{max} = 40\text{mA}$

⇒ $(I_L)_{min} + 32\text{mA} = 40\text{mA}$

⇒ $(I_L)_{min} = 8\text{mA}$

∴ $(R_L)_{max} = \frac{V_L}{(I_L)_{min}} = \frac{10}{8\text{mA}} = 1.25k\Omega$.

$(R_L)_{max} = 1.25k\Omega$



$(R_L)_{min} = 250 \Omega$, $\therefore (I_L)_{max} = \frac{10V}{250 \Omega} = 40mA$

So $(R_L) \rightarrow$ varying from 250Ω to $1.25k\Omega$

the O/P remains const = 10V

i.e (I_L) varying from $40mA$ to $8mA$

O/P remains const = 10V

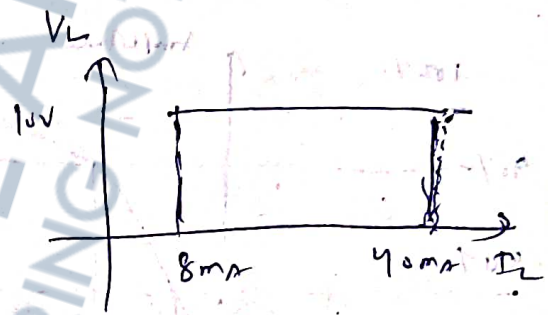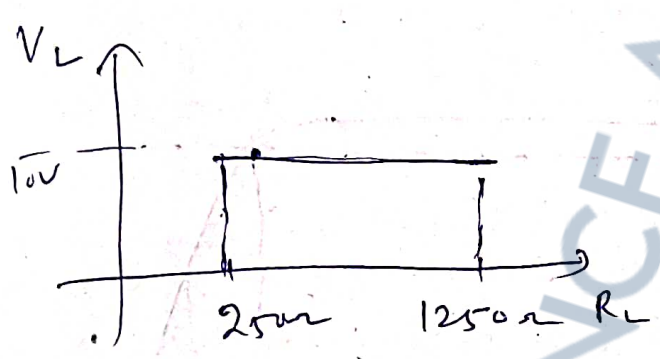


(b) Max^m wattage rating of diode

$= V_Z \times I_{ZM}$



$= 10 \times 32mA$

$P_{ZM} = 320mWatt$

Digital waveform :-

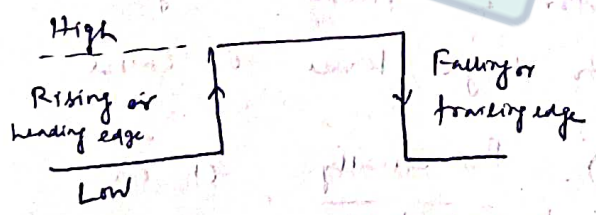


(a) +ve going pulse

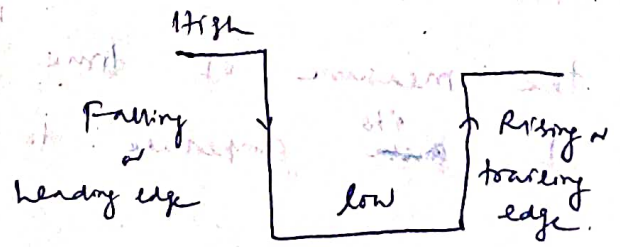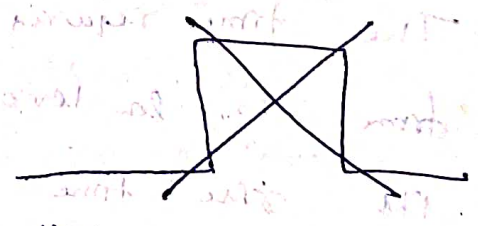

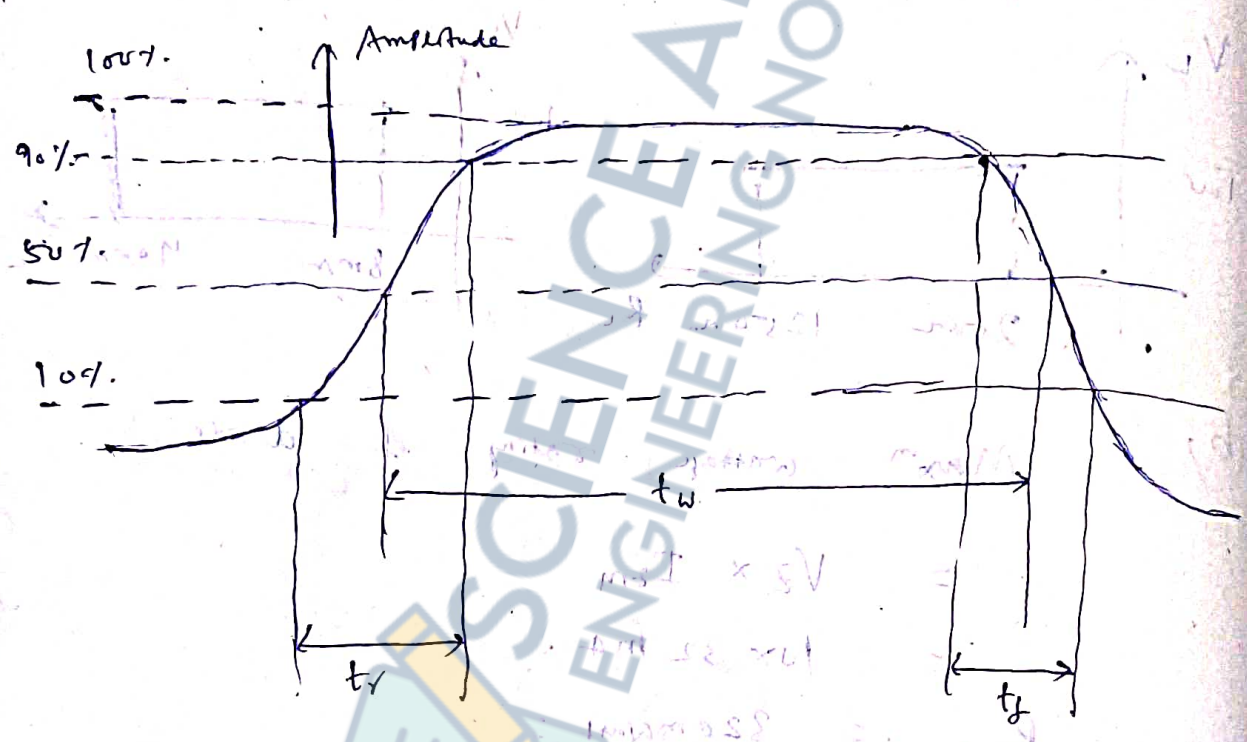(b) -ve going pulse

→ A +ve going pulse is generated when the voltage (current) goes from its normally low level to its high and then backs to low level.

→ A -ve going pulse is generated when the voltage goes from its normally high level to its low level and backs to high level.



→ t_r (rise time)

The time required for a pulse to go from its low level to high level is called its rise time (t_r). Practically, it is

the measure of time taken by the pulse to rise from 10% of its amplitude to 90% of its amplitude.

t_f (fall time)

a pulse's

The time required for a transition from high level to low level is called the fall time (t_f)

Practically it is the measure of the time taken by pulse to go from 90% to 10% of its amplitude.

Pulse width (t_w)

It is the time interval between 50% of leading edge to 50% of trailing edge amplitude.

Duty Cycle

It is the ratio of pulse width to its time period.

$$\text{Duty cycle} = \frac{t_w}{T} = \frac{\text{Pulse width}}{\text{Time period}}$$

$$\left(f = \frac{1}{T} \text{ i.e. frequency} = \frac{1}{\text{Time period}} \right)$$

or Pulse width:-

It is a measure of the duration of the pulse. and it is often defined as the time interval between 50% of points on the rising and falling edge.

1) P-N Junction diode made up of which material (Si, Ge, GaAs) will have highest thermal stability and why?

A:- P-N Jⁿ diode made up of Si material will have highest thermal stability, because Silicon diodes operated in avalanche breakdown are available with maximum voltages from several volts to several hundred volts with power rating up to 50 Watts. They can operate in high temperature.

2) A signal is represented by

$$y = 5 \sin(628t + 30^\circ)$$

Find ~~is~~ frequency, amplitude and initial phase of signal.

Ans:- Standard eqⁿ of signal,

$$y = A \sin(\omega t + \phi)$$

$$\boxed{A = \text{Amplitude} = 5 \text{ V}}$$


$$\omega = 628 \Rightarrow 2\pi f = 628$$

$$\Rightarrow 2 \times 3.14 \times f = 628$$

$$\Rightarrow \boxed{f = 100 \text{ Hz}}$$

$$\text{Phase, } \phi = 30^\circ$$

More Problems

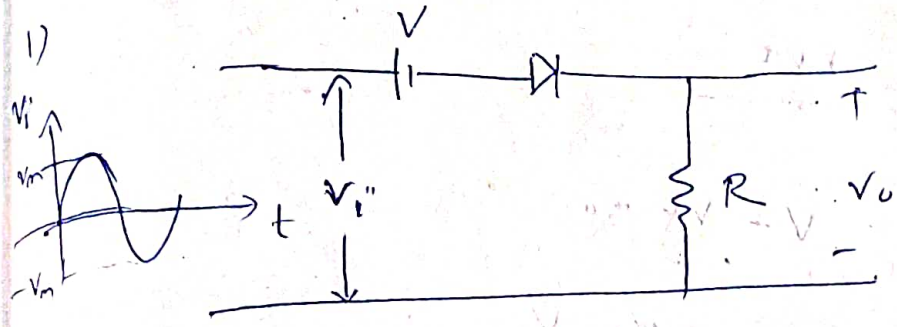


Answer : - Steps

1) If diode is F.B. What is the OP.

$$V_i - V - V_o = 0$$


$$\Rightarrow V_o = V_i - V$$

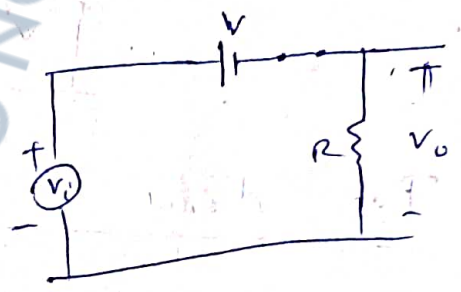

2) If diode is R.B., diode is open ckted, OP is Zero.

$$V_o = 0$$

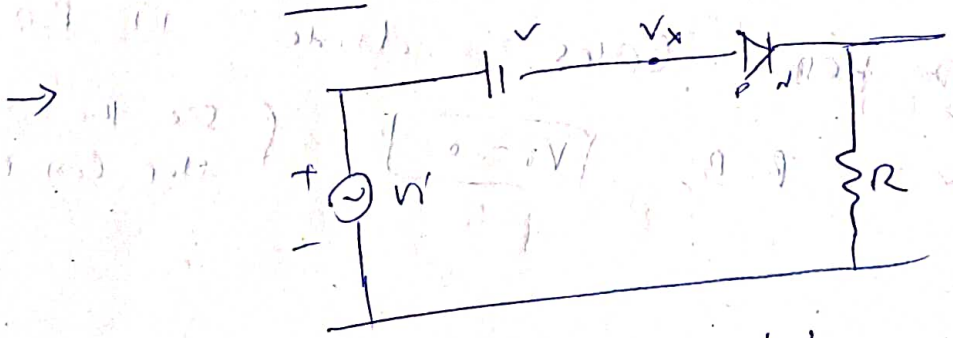3) What is the condition for diode to be F.B



For the PN junction, 'N' is connected to ground. So potential at P (V_x)

$$V_x > 0$$

Applying KVL

$$V_i - V - V_x = 0$$

$$\Rightarrow V_x = V_i - V$$

$$\Rightarrow V_x > 0$$

$$V_i - V > 0$$

$$\boxed{V_i > V}$$

To draw the wave form.

1) First draw the LIP wave form.



2) Draw a line at $V_i = V$.

3) For $V_i > V$, Draw F-B

OP is $\boxed{V_i - V}$ [See the
 → Max^m Amplitude $V_m - V$ step 1
 as last page]

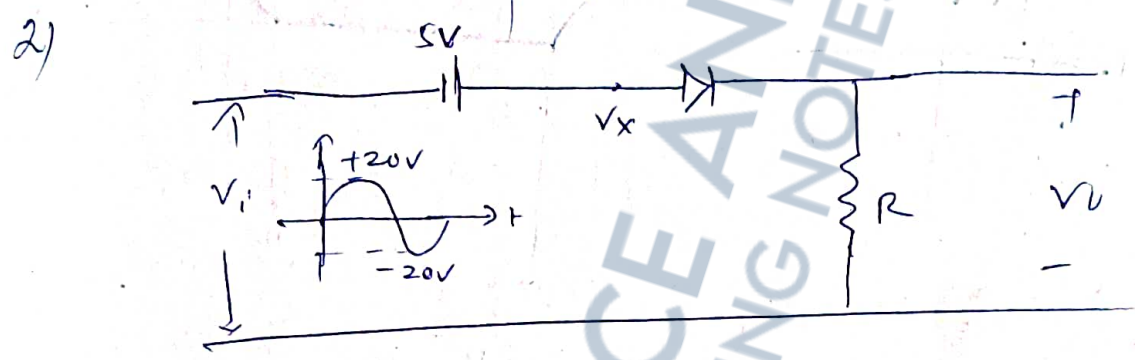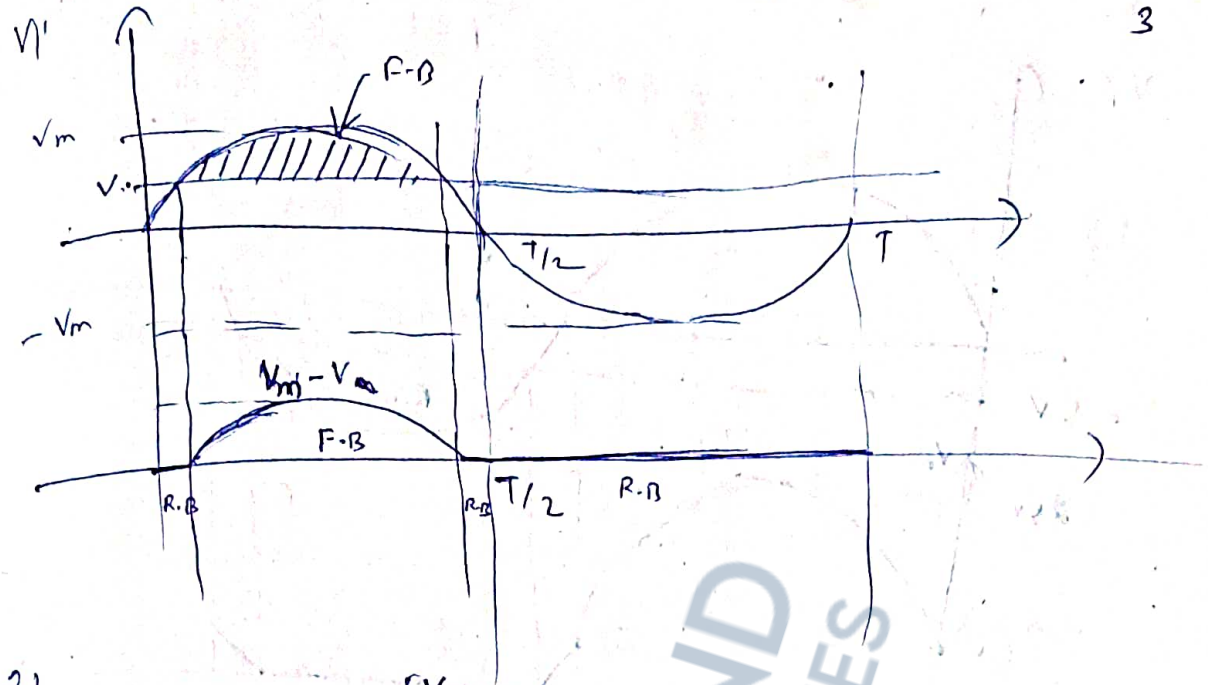4) For Rest Cases draw in R-B.

For R-B, $\boxed{V_i = 0}$ [see the 2nd
 after last page]



Step 1: - If diode is F-B

$$v_i + 5 - v_o = 0 \Rightarrow \boxed{v_o = v_i + 5}$$

If diode is R-B, $i_p = 0$

3) Condition for diode is F-B


$$v_i + 5 - v_x = 0$$

$$\Rightarrow v_x = v_i + 5$$

$$v_x > 0$$

$$v_i + 5 > 0$$

$$\boxed{v_i > -5V}$$

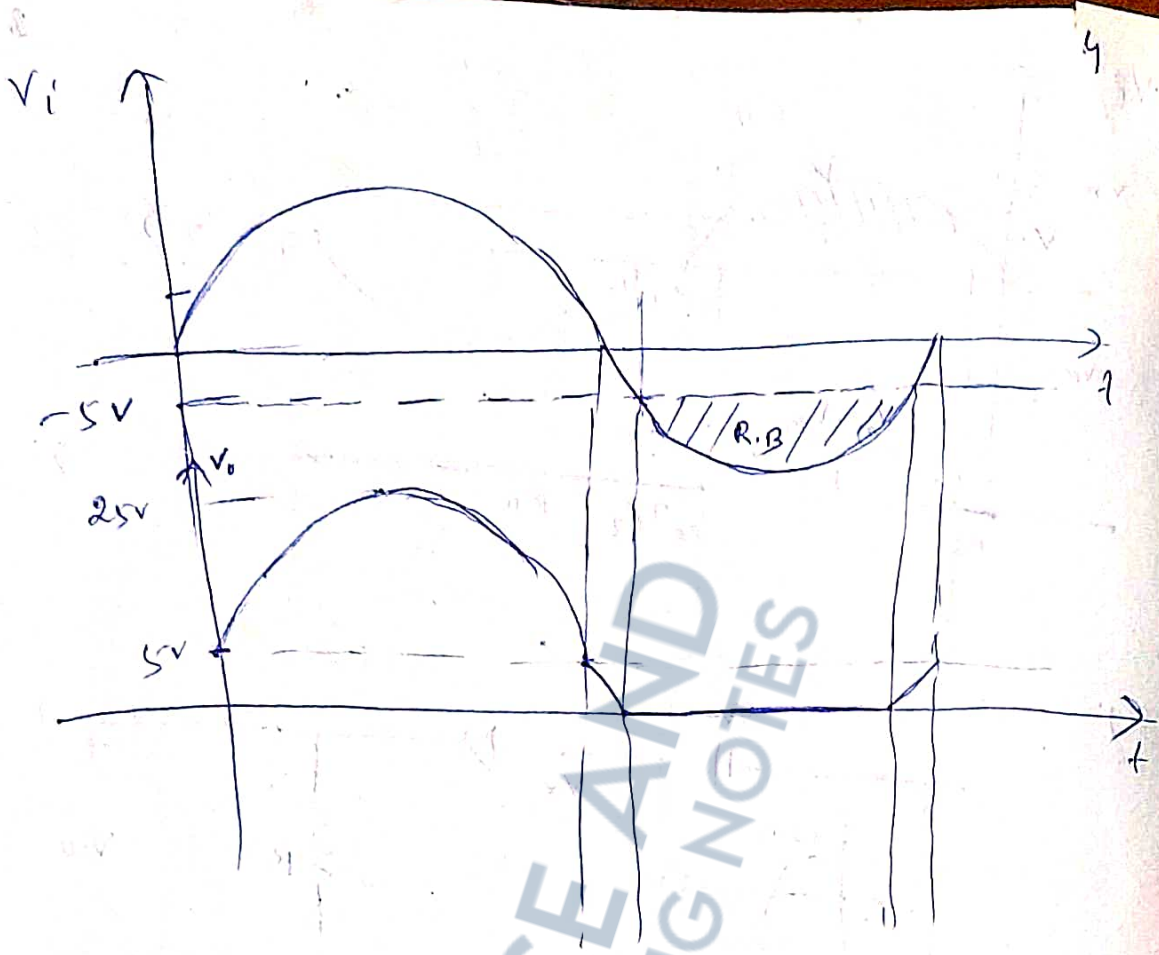

For $V_i < -5V$, diode is R.B. O/P = zero

Rest cases of $V_i > -5V$, $V_i + 5$

$V_i = 0, V_o = 5$



$V_i = 2.5, V_o = 2.5$

$V_i = -5, V_o = 0$

$V_i = -4, V_o = 1$

$V_i = 0, V_o = 5$

3)

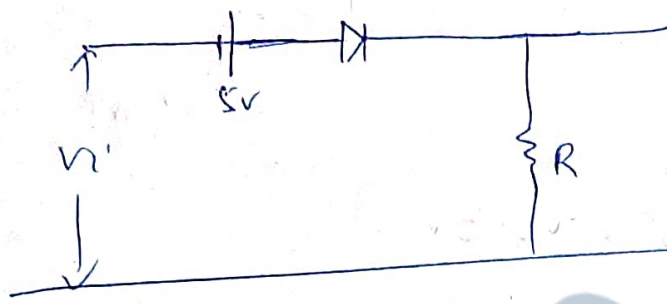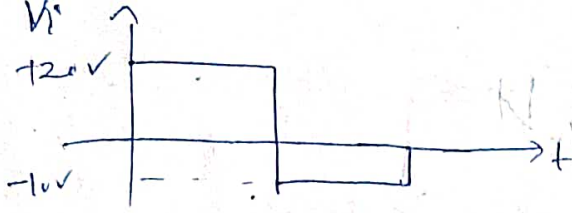

→ A: Analysis of clipper with square wave. A clip is lower because only 2 levels to be considered.


Step 1: When divide ch R-B, $\frac{OP}{IP}$



20 + 5 - $V_D = 0 \Rightarrow \boxed{V_o = 25V}$


Step 2: - When divide ch R-B, $\boxed{V_o = 0}$

For the half cycle

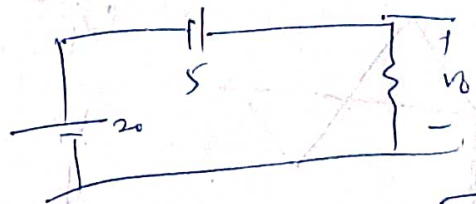

+20 + 5 - $V_D = 0 \Rightarrow \boxed{V_o = 25V}$


For -ve half cycle

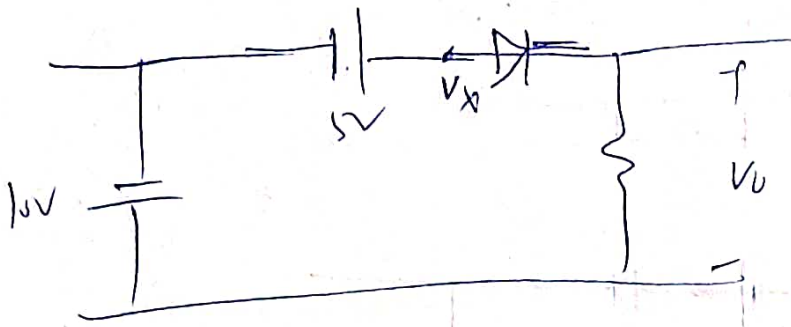



$$-10 + 5 - V_x = 0$$

$$\Rightarrow V_x = 10 - 5 = \underline{\underline{-5V}}$$

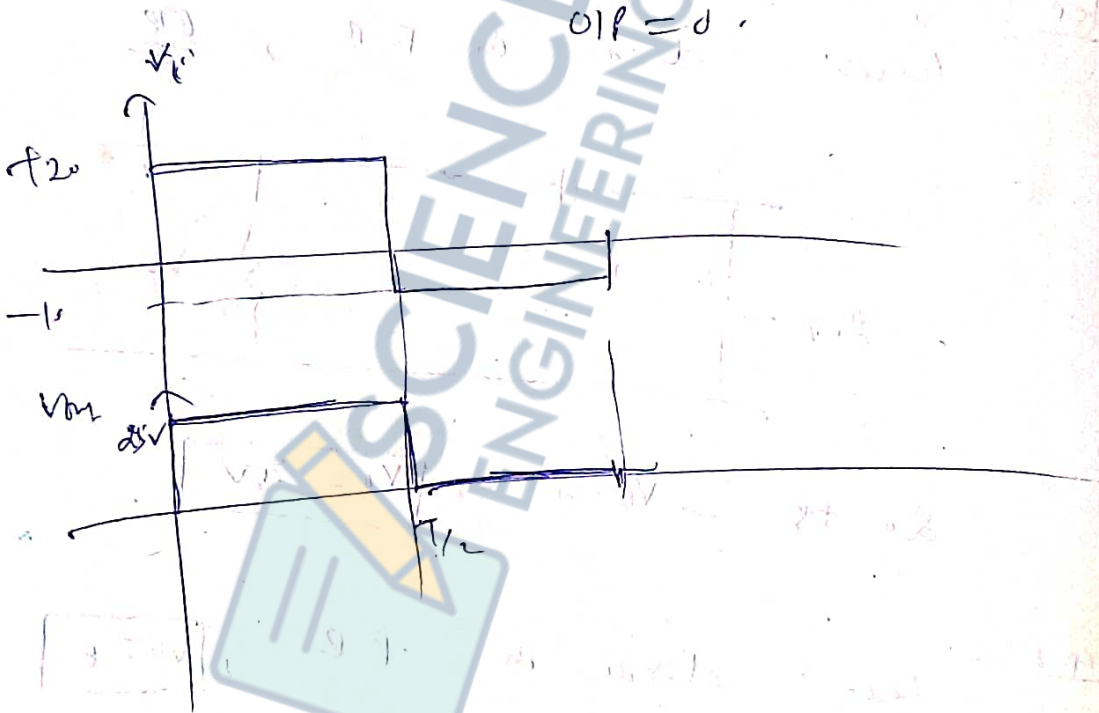Since diode is in P.B. for -ve half cycle
 O/P = 0.



4)

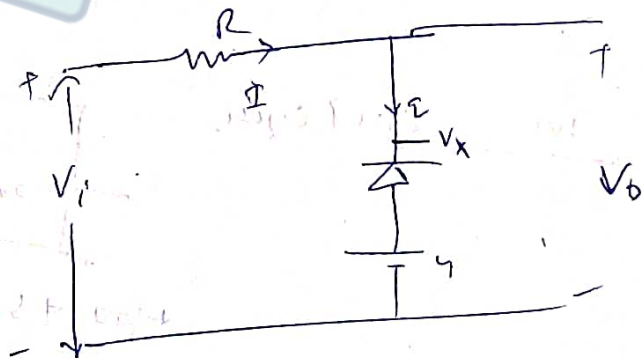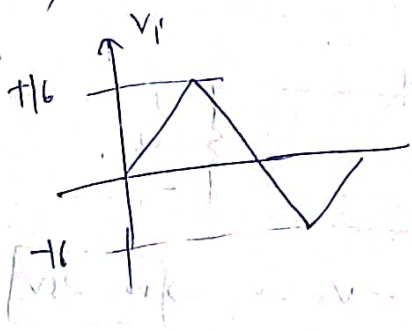

Ans: (i) when diode is F.B.

7

~~$V_o = V_i$~~ $V_o = \underline{4V}$

(ii) when diode is R.B., open circuit.

$I = 0$

$V_o = V_i$

(iii) Comp, when diode is F.B.

$V_i - IR - V_x = 0$

↳ Current has not started, diode is off state.

$V_x = V_i$



~~V_x~~ To make the diode F.B.

$V_x < 4V$


$V_i < 4V$

any at R.B. $OP = 4V$




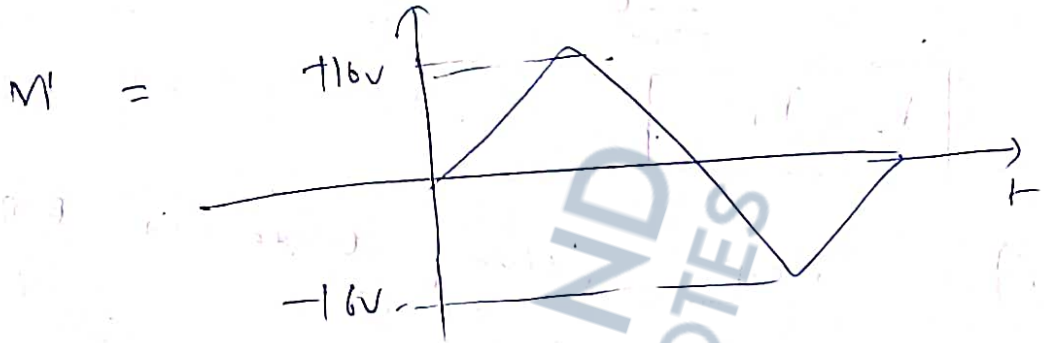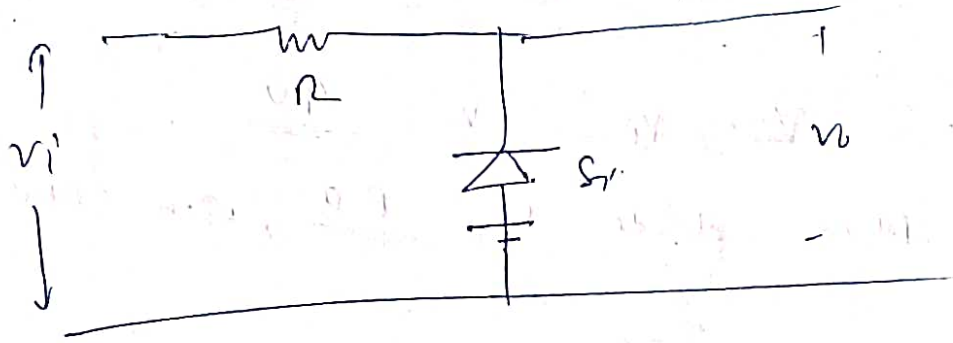

Ans:

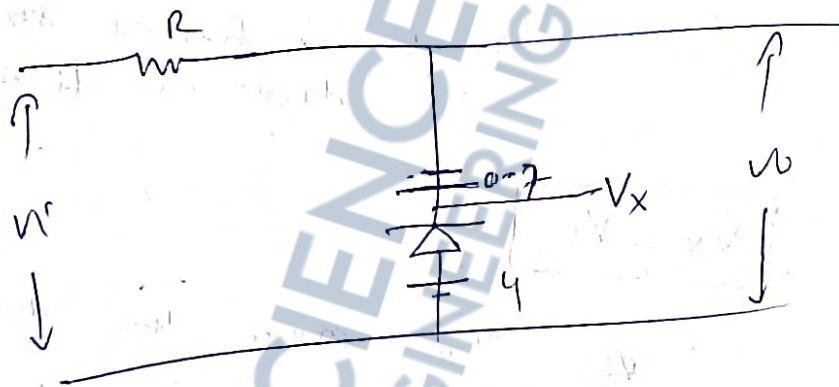

1) When diode F.O.

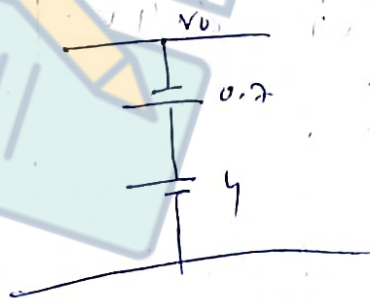

$$V_o + 0.7 - 4 = 0$$

$$\Rightarrow V_o = 4 - 0.7 = \underline{3.3V}$$

2) R.B.,

$$V_i = V_o$$

(As discussed in
previous part)

37

§ Coman for diode F.B.


$$V_i - 0.7 - V_x \Rightarrow$$

$$\Rightarrow V_x = V_i - 0.7$$

$$V_x < 4$$



$$V_i - 0.7 < 4$$

$$\Rightarrow V_i < 4.7$$

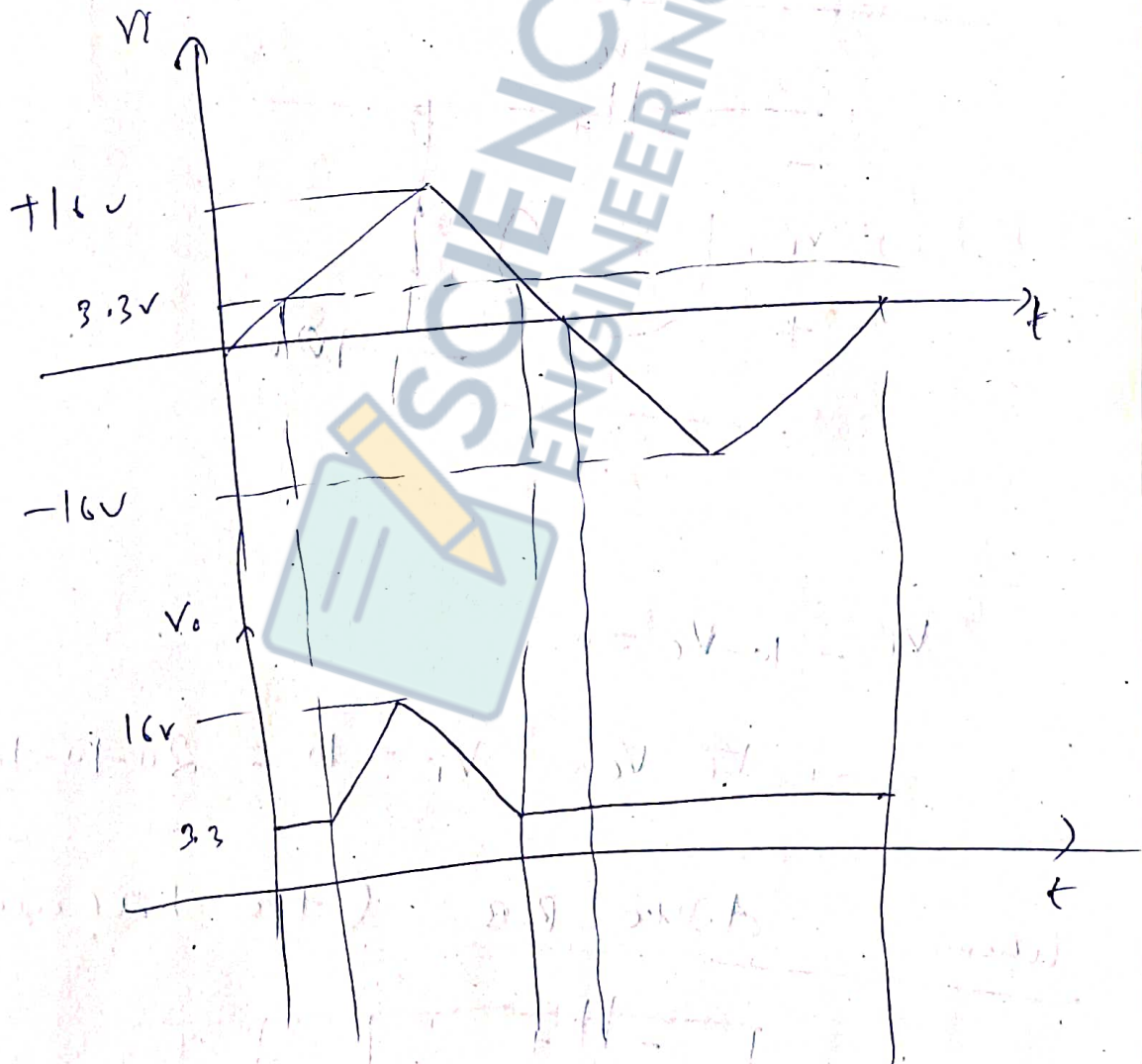

67

10

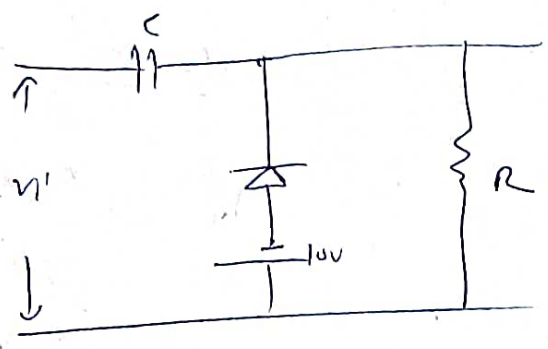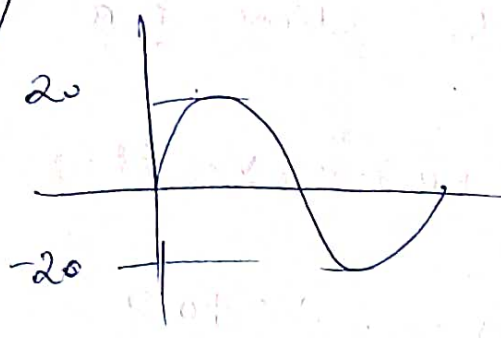

~~the half cycle~~

When diode F-B (~~is~~) (-ve half cycle)
Op is (-10V) (bidirectional)


Capacitor is charged



$$V_i - 10 - V_c = 0$$


$$\Rightarrow V_c = V_i - 10 = 20 - 10 = \underline{\underline{10V}}$$

When diode F.B (pos half cycle)

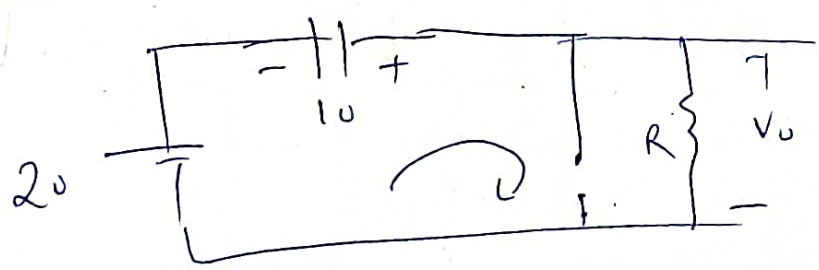

$$2.0 + 10 - V_0 = 0$$
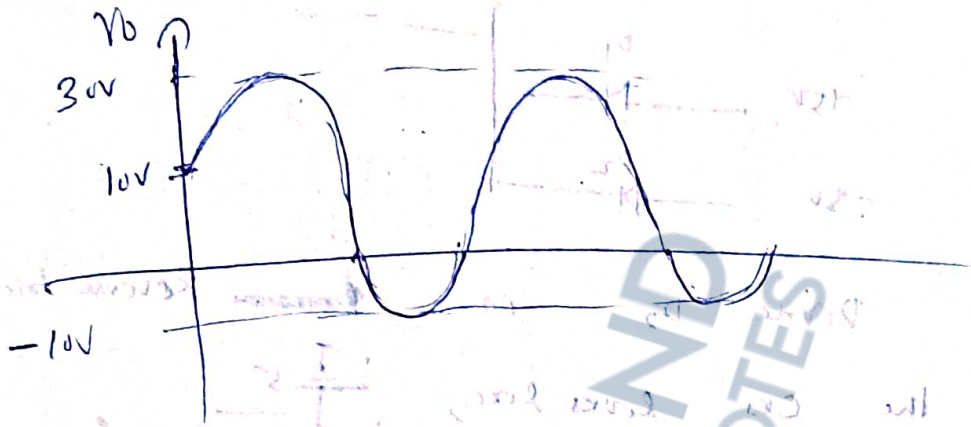
$$\Rightarrow \boxed{V_0 = 30V} \quad (\text{Answer})$$




$V = 0$



(Faint, mostly illegible handwritten notes and diagrams are visible in the background and foreground, including a circuit diagram with a 100k resistor and a 12V source.)


Solution to BE - Internal Question (21.02.2015)

1) (d) Find V_o

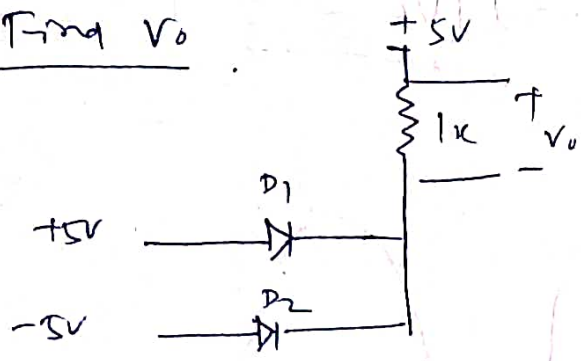


Ans: Diode D_2 is ~~forward~~ Reverse biased

So the ckt looks like,

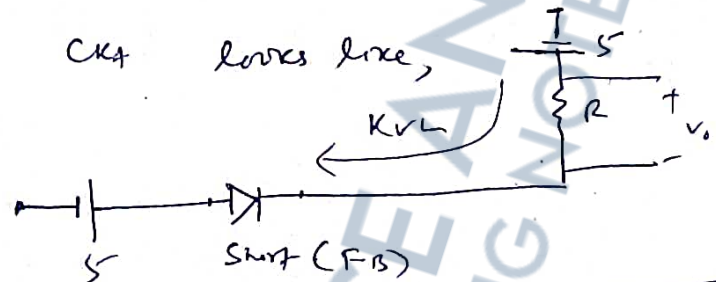

$$5 - V_o - 5 \Rightarrow \boxed{V_o = 0}$$

2) (f)

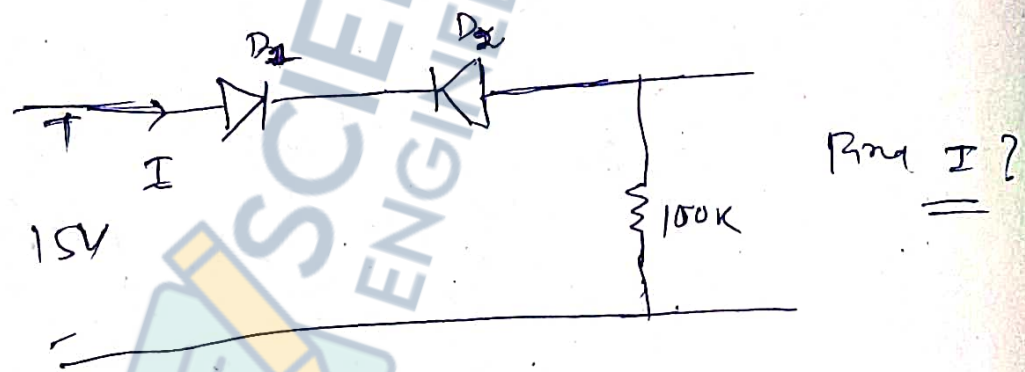

Given: $I_s = 0.1 \text{ mA}$, $V_T = 25 \text{ mV}$, $\beta = 2$.
Supply voltage = 15V.

Ans: Here diode, D_1 is F.B.
 D_2 is R.B.

Ideally it should be open circuit, but practically in R.B there exist a reverse saturation current.

So. Current in the ckt is

$$I_s = 0.1 \text{ mA}$$

27 (b) Given

$$V_z = 5.6 \text{ V}$$

$$I_{z \text{ min}} = 1 \text{ mA}$$

$$I_{z \text{ max}} = 5 \text{ times } I_{z \text{ min}}$$

$$= 5 \times 1 \text{ mA}$$

$$I_{z \text{ max}} = 5 \text{ mA}$$

$$V_{\text{supply}} = +15 \text{ V}$$

$$(I_L)_{\text{min}} = 0 \text{ mA}$$

$$(I_L)_{\text{max}} = 15 \text{ mA}$$

We have to find suitable values of R when

~~Case I: $(I_L)_{\text{min}} + (I_z)_{\text{min}} = I$~~


Always $I = I_L + I_z$ is a const.

$$I = (I_L)_{\text{min}} + (I_z)_{\text{max}}$$

$$I = (I_L)_{\text{max}} + (I_z)_{\text{min}}$$

and $V - IR - V_z = 0$

$$\Rightarrow 15 - IR - 5.6 = 0$$

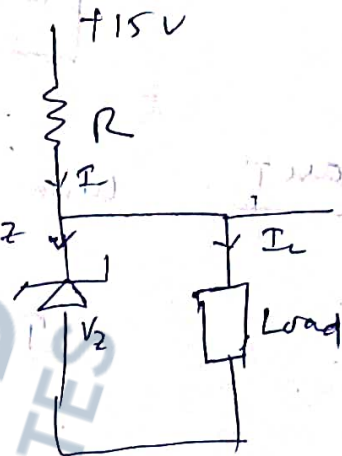

$$\Rightarrow IR = 15 - 5.6 = 9.4 \text{ V}$$

$$IR = 9.4 \text{ V}$$

Case I

When $(I_L)_{\min}$ & $(I_2)_{\max}$

$$I = (I_L)_{\min} + (I_2)_{\max}$$

$$= 0 + 5$$

$$I = 5 \text{ mA}$$

$$IR = 9.4 \text{ V}$$

$$\Rightarrow R = \frac{9.4}{5 \times 10^{-3}} = \frac{9400}{5} = 1880$$

$$= 1.8 \text{ k}\Omega$$

Case II

When $(I_L)_{\max}$ & $(I_2)_{\min}$

$$IR = 9.4 \text{ V}$$

$$I = (I_L)_{\max} + (I_2)_{\min}$$

$$= 15 + 1$$

$$I = 16 \text{ mA}$$

$$IR = 9.4 \text{ V}$$

$$\Rightarrow R = \frac{9.4}{16 \times 10^{-3}} = \frac{9400}{16} = 587.5 \Omega$$

So, 'R' will vary from

$$587.5 \Omega < R < 1.8 \text{ k}\Omega$$

b) Max Power

dissipation

$$= V_L \times I_{L_{\max}}$$

$$= 5.6 \times 5 \text{ mA}$$

$$= 28.0 \text{ mWatt} \times 10^3$$

$$= 28 \text{ mWatt}$$

37 (a)

Given

$$I_S = 10^{-10} \text{ A}, \quad \eta = 2$$

$$I_D = ? \quad \text{if } V_D = 0.65 \text{ V}$$

$$I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

$$= 10^{-10} \left(e^{\frac{0.65}{2 \times 28 \times 10^{-3}}} - 1 \right)$$

$$\left(\because V_T = 28 \text{ mV for room temp} \right)$$

$$I_D = 10^{-10} \left(e^{12.5} - 1 \right) = 2.68 \times 10^{-5} \text{ Ampere}$$

(b)

Given

$$I_D = 200 \text{ } \mu\text{A, find } V_D$$

$$I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

$$\Rightarrow 200 \times 10^{-6} = 10^{-10} \left(e^{\frac{V_D}{2 \times 28 \times 10^{-3}}} - 1 \right)$$



$$\Rightarrow \frac{\frac{V_D}{28 \times 10^{-3}}}{e - 1} = \frac{200 \times 10^{-6}}{10^{-10}} = 200 \times 10^4$$

$$\Rightarrow \frac{V_D}{28 \times 10^{-3}} \approx 200 \times 10^4$$


$$\Rightarrow \frac{V_D}{28 \times 10^{-3}} = \ln(200 \times 10^4) = 14.50$$

$$\Rightarrow V_D = 14.5 \times 28 \times 10^{-3} = 0.406 \text{ V}$$

4)

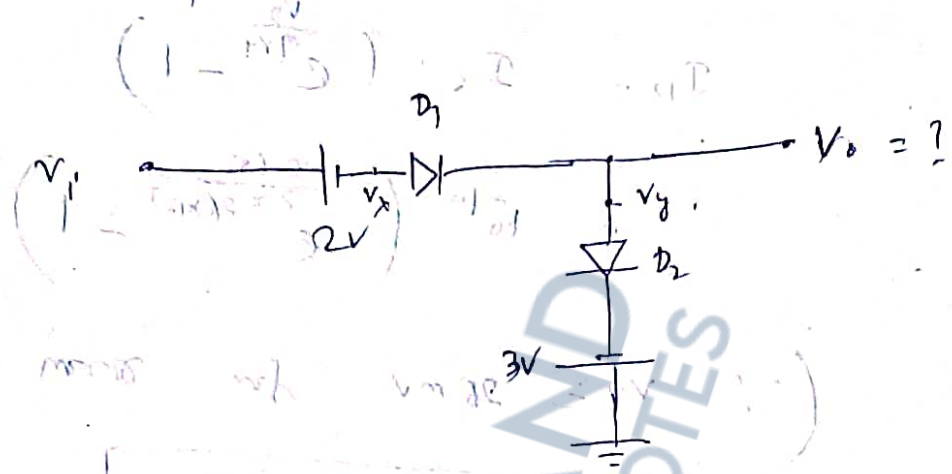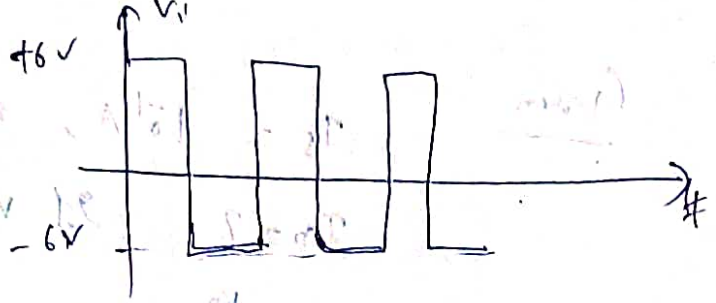

Ans: For the half cycle

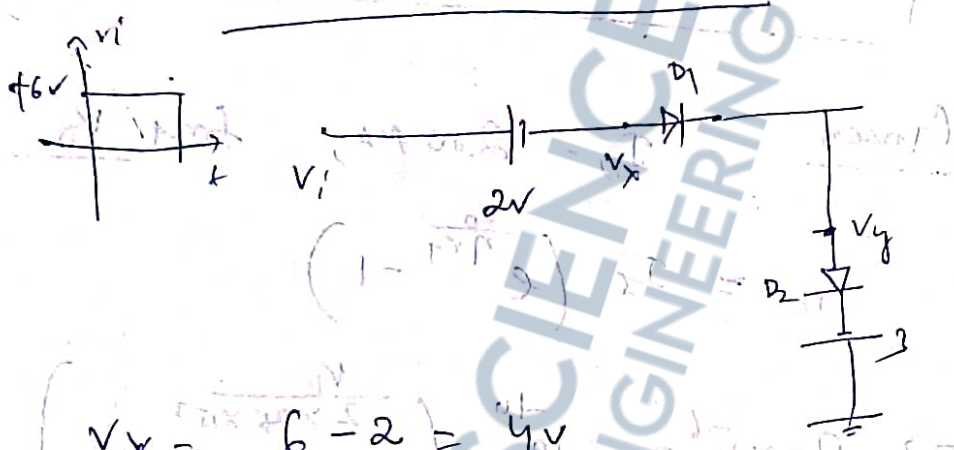


$$V_x = 6 - 2 = 4V$$

$D_1 =$ Forward biased.


$D_2 =$ Forward biased, [D_2 has N end $-ve$ (Pent $+ve$)]

Voltage with respect to a is $-3V$

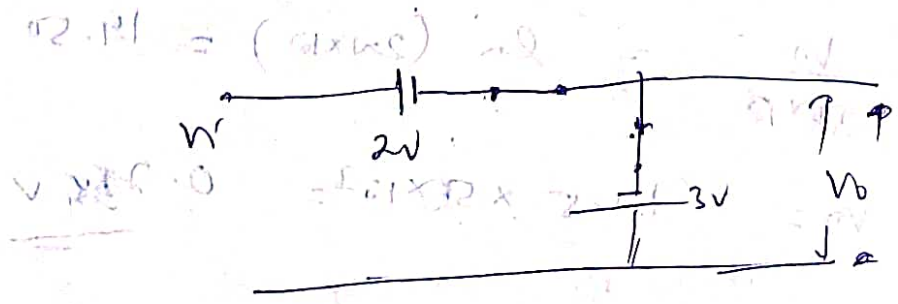

For -ve half cycle

17

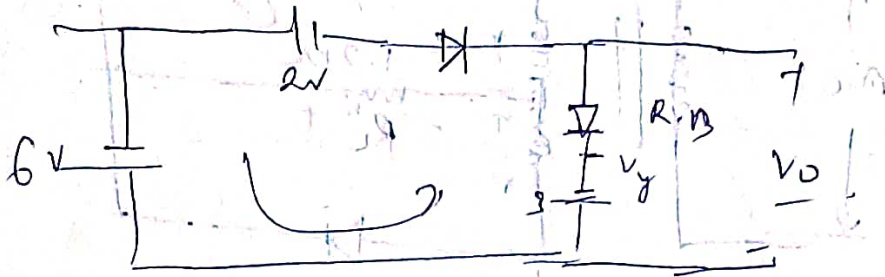


$$6 - 2 - V_y = 0$$

$$\Rightarrow V_y = 3V$$


Since V_y is connected to the diode D_2 R_L .

$$V_o = 0$$

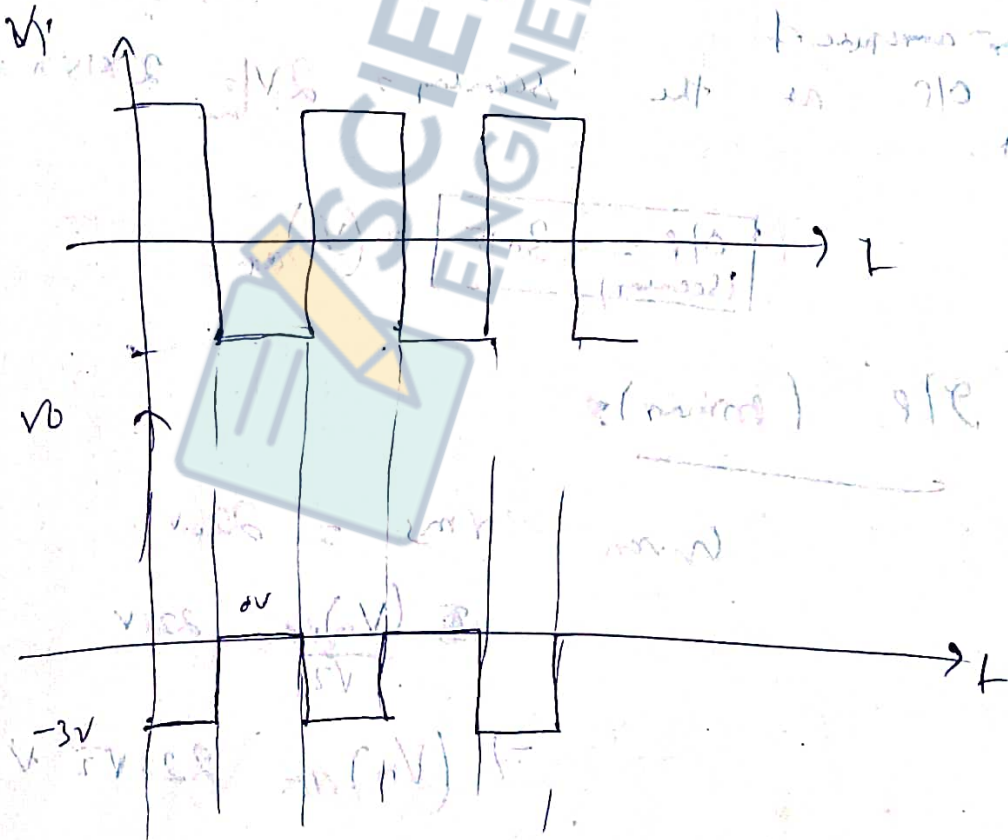

$\frac{6V}{100\mu s} = 60 \text{ (V)}$
 $\frac{3V}{100\mu s} = 30 \text{ (mV)}$

5)

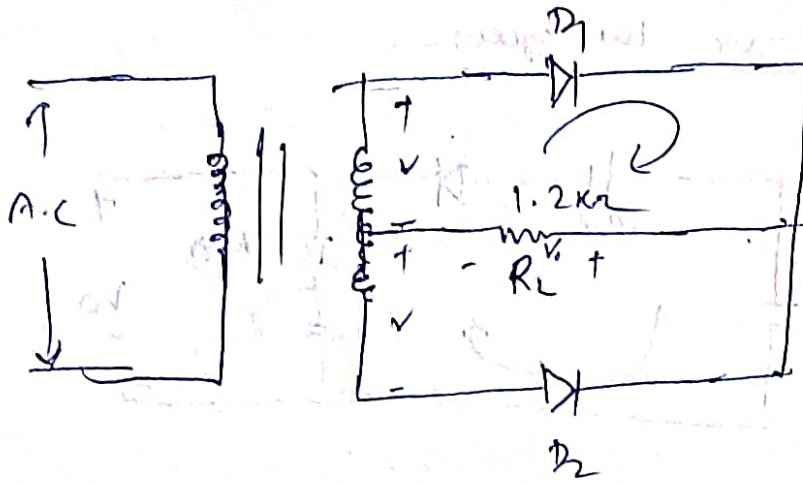

Given: -

$V_{dc} = 30V$ (Drop across the load R_L)

$\Rightarrow \frac{2V_m}{\pi} = 30V \Rightarrow V_m = \frac{15 \times 30}{\pi} = 15\pi$

$V - V_{d0} = 0 \Rightarrow (V_o)_{min} = 15\pi$

$\Rightarrow V = \frac{V_o}{max}$

$V = \frac{2V_m}{\pi} \Rightarrow V_{max} = 15\pi$

Min amplitude of

O/P at the secondary $\Rightarrow 2V = 2 \times 15\pi = 30\pi$

$O/P = 30\pi = (V_m)_{out}$


O/P (Primary)

Given $V_{rms} = 220V$


$\frac{(V_m)_{in}}{\sqrt{2}} = 220V$

$\Rightarrow (V_m)_{in} = 220\sqrt{2} V$

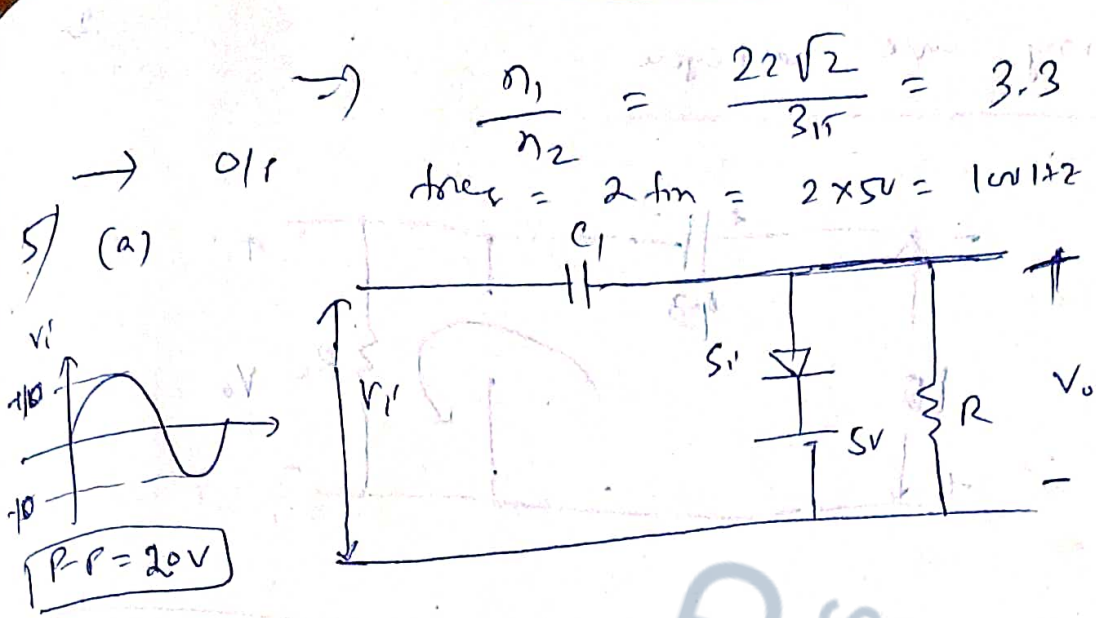$\frac{(V_m)_{in}}{(V_m)_{out}} = \frac{n_1}{n_2} \Rightarrow \frac{n_1}{n_2} = \frac{220\sqrt{2}}{30\pi}$



Ans: For -ve half cycle

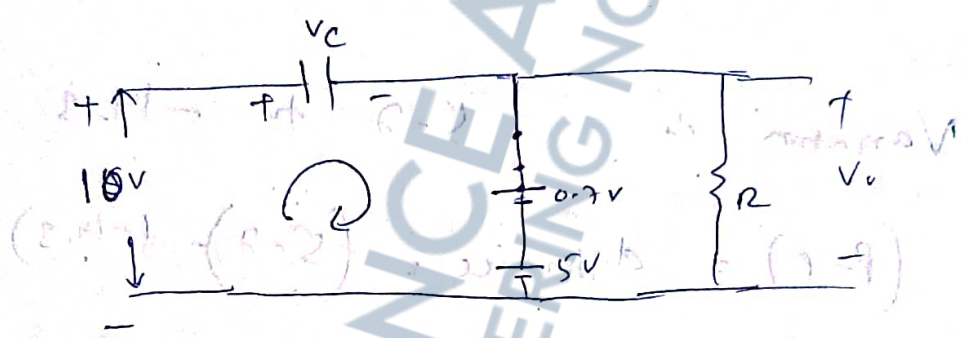

Diode is short circuited (F.B)

Since S_1 diode 0.7V drop occurs.

$V_o = 5$

$V_o = 5.7 \text{ V}$

$(\because V_o - 0.7 - 5 = 0 \Rightarrow V_o = 5.7 \text{ V})$


→ Capacitor will charge in this cycle.

To find (V_c)

$10 - V_c - 0.7 - 5 = 0$

$\Rightarrow V_c = -4.3 \text{ V}$


Dummy -ve half cycle

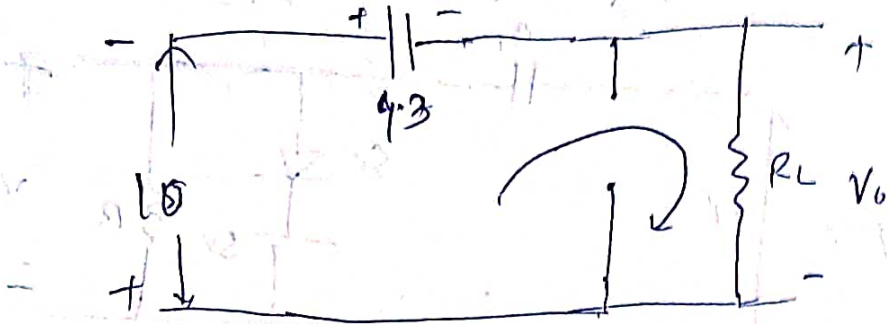


$$-10 - 4.3 - V_0 = 0 \Rightarrow V_0 = -14.3$$

Variation is 5.7 to -14.3
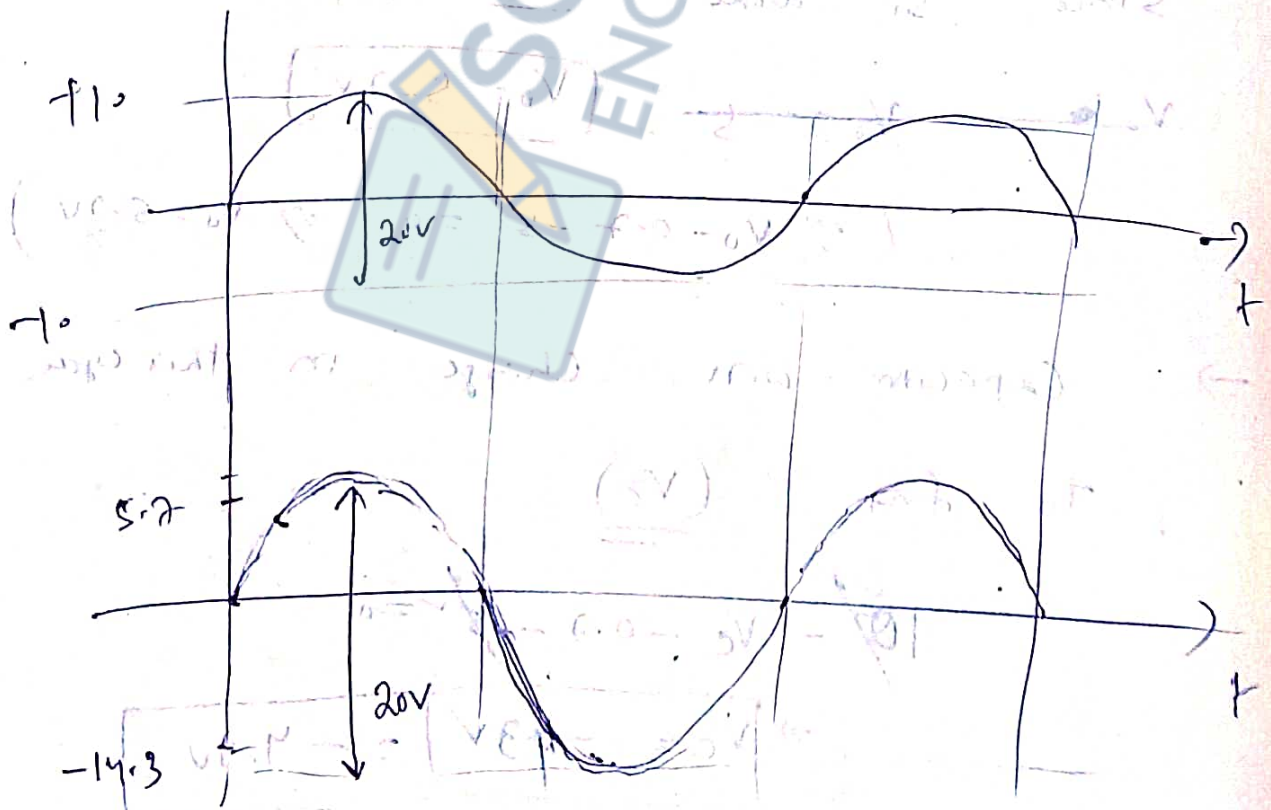
$$(P-P) = \text{difference} = (5.7) - (-14.3) = 20.0 \text{ V}$$



(b)

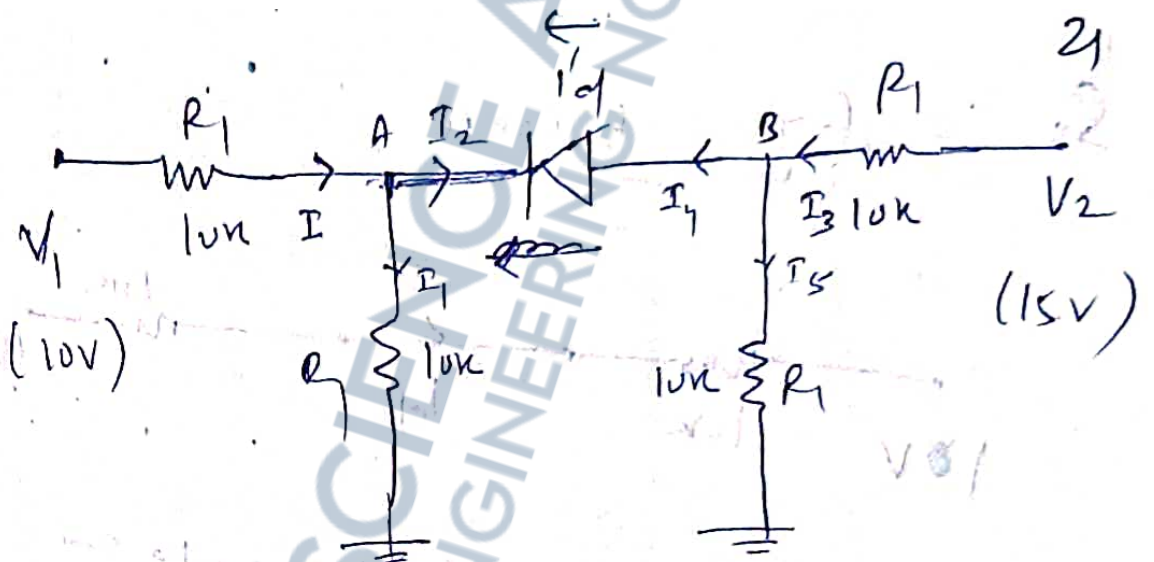

SCIENCE AND ENGINEERING NOTES

Using Node Analysis. (At Point A)

$$\frac{V_1 - V_A}{10k} = \frac{V_A}{10} + I_2$$

$$\Rightarrow \frac{10 - V_A}{10k} = \frac{V_A}{10} + I_2$$

$$\Rightarrow \frac{10}{10k} = \frac{11V_A}{10} + I_2$$

$$\Rightarrow I_2 = \frac{10 - V_A}{10k} - \frac{V_A}{10} = \frac{10 - 2V_A}{10k} \quad \text{--- (1)}$$

At Point B

$$\frac{V_2 - V_B}{10k} = I_3 + \frac{V_B}{10k}$$

$$\Rightarrow I_3 = \frac{V_2 - V_B - V_B}{10k} = \frac{15 - 2V_B}{10k} \quad \text{--- (2)}$$

→ We know

~~$V_A = V_B$~~

~~$I_2 = I_3$~~

~~$\frac{10 - 2V_A}{10k} = \frac{15 - 2V_B}{10k}$~~

$V_A = V_B$

Putting this in eqⁿ (1)

$I_2 = \frac{10 - 2V_B}{10k}$ (3)

and $I_2 = -I_3$ (4) (same magnitude opposite direction)

Putting eqⁿ (3) & (4) in eqⁿ (4)

~~$\frac{10 - 2V_B}{10k} = -\left(\frac{15 - 2V_B}{10k}\right)$~~

$10 - 2V_B = -15 + 2V_B$

$\Rightarrow 4V_B = 25$


$\Rightarrow V_B = \frac{25}{4}$

$\therefore I_3 = \frac{15 - 2V_B}{10k} = \frac{15 - 2 \times (\frac{25}{4})}{10k}$

$= \frac{15 - 12.5}{10k} = \frac{2.5}{10k} = 0.25 \text{ mA}$

$I_3 = I_d = 0.25 \text{ mA}$

Actual Current direction

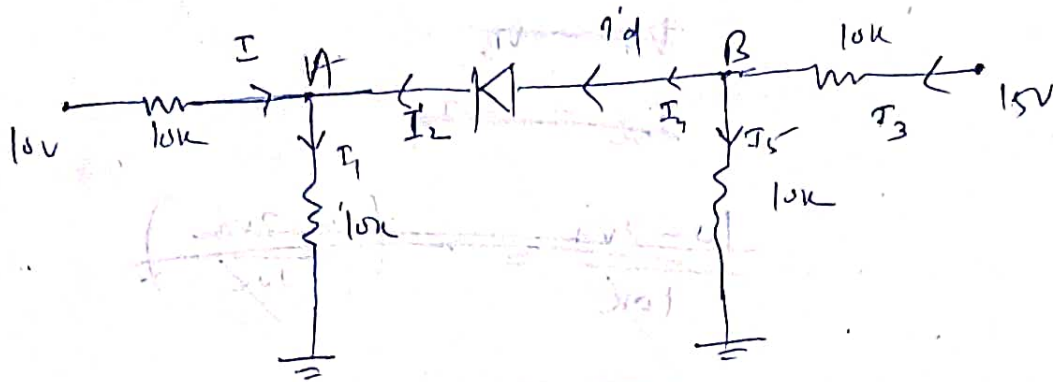

(1) Node A

$$V_A = V_B = \frac{25}{4} \text{ V}$$

$$I_1 = \frac{\frac{25}{4} - 0}{10k} = \frac{5 \cdot 25}{8 \cdot 40k} = \frac{5}{8} \text{ mA}$$

→ Since \$V_A < 10\text{V}\$, current flows from 10V to \$V_A\$.

$$I = \frac{10 - V_A}{10k} = \frac{10 - \frac{25}{4}}{10k} = \frac{40 - 25}{40k} = \frac{15}{40k} = \frac{3}{8} \text{ mA}$$

$$I_2 = I_d = 0.25 \text{ mA} = \frac{1}{4} \text{ mA}$$

Let's check

$$I + I_2 = I_1$$

Let's

$$I + I_2 = \frac{3}{8} + \frac{1}{4} = \frac{3+2}{8} = \frac{5}{8} \text{ A.D.S.}$$

Similarly

at Node B


$$I_3 = \frac{15 - V_B}{10k} = \frac{15 - \frac{25}{4}}{10k} = \frac{60 - 25}{40k}$$

$$V_B < 15\text{V} \Rightarrow \frac{25}{4} < 15 \Rightarrow \frac{25}{40k} > \frac{7}{8} \text{ mA}$$

So \$I_3\$ flows from 15V to

$$\begin{aligned}
 I_5 &= I_3 - I_7 \\
 &= I_8 - 0.25 \text{ mA} \\
 &= I_8 - \frac{1}{7} \\
 &= \frac{7-2}{8} \\
 I_8 &= \frac{5}{8} \text{ mA}
 \end{aligned}$$

→ If we draw the Ckt

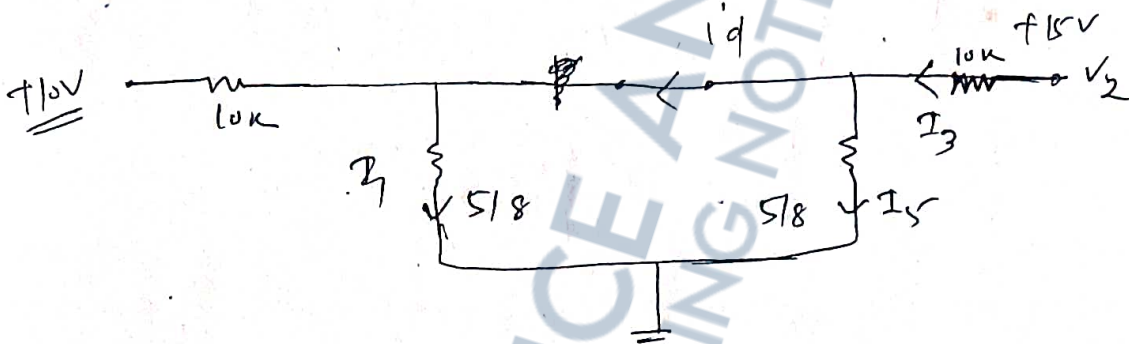

I_7 & I_5 will cancel each other

Net current = 0 in lower branch.

I_3

Direct

$$V_2 - i_d \times 10k - i_d \times 10k = 0$$

$$\Rightarrow 15 - i_d \times 20k - 10 = 0$$


$$\Rightarrow i_d = \frac{5}{20k} = \frac{5}{20} \times 10^3 = \underline{\underline{0.25 \text{ mA}}}$$

Answer → When current I_3 comes it has 2 path, ' i_d ' path another possible path.

Current goes through ' i_d ' path.

Current in the lower branch Zero.

So the ckt becomes

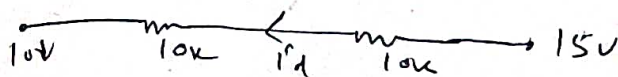

1d 2

$$\frac{15-10}{20k} = \frac{25}{20k}$$

$$= \frac{1}{4} \text{ mA}$$

$$= 0.25 \text{ mA}$$

(Ans)

