

Module-I

Ch-1:-

BJT (Bipolar Junction Transistor): Fundamentals

→ A transistor consists of 2 PN junctions formed by sandwiching either p-type or n-type semiconductor between a pair of opposite types.

→ There are 2 types of transistor.

(a) N-P-N transistor (b) P-N-P transistor

→ Invented by Dr. William Shockley, Dr. J. Barden, Dr. W.H. Brattain. It is invented.

→ 1948

→ 1956 they got Nobel prize



→ Bipolar (B) → 2 charge carriers (electron & holes) both are

→ An n-p-n transistor composed of 2 n-type semiconductors separated by a thin section of p-type.

→ But P-n-p transistor composed of 2 p-type semiconductors separated by a thin section of n-type.

Why transistor?


A transistor consists of 2 PN junctions, one junction is forward biased and other

is reverse biased. The forward biased junction has low resistance path where as reverse biased junction has a high resistance path.

The weak signal is introduced on a low resistance cut & o/p is taken from the high resistance cut. Therefore, transistor transfers a signal from low resistance to high resistance.

$\text{Transistor + Resistor} = \text{Transistor}$


→ Transistor Terminals :-

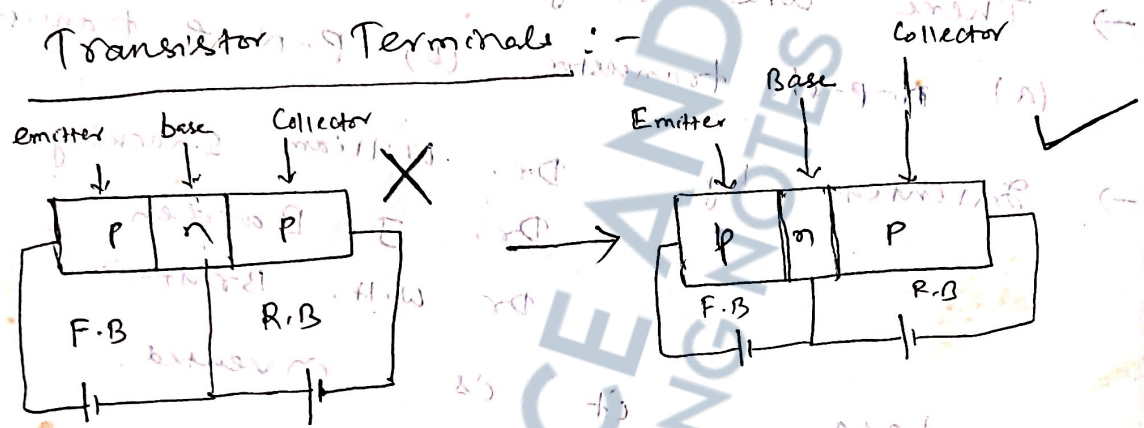

Width of emitter, base & collector are not equal

$W_C > W_E > W_B$

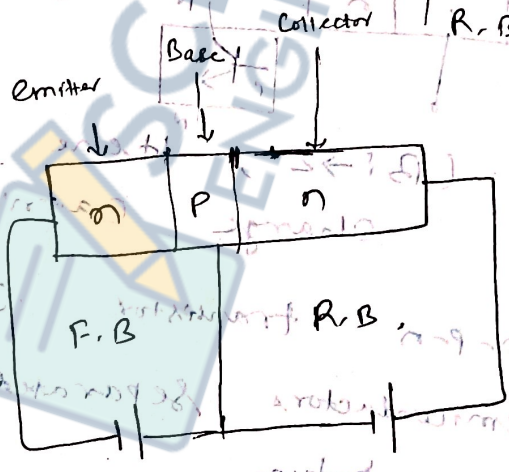W = width
 F.B = Forward Biased
 R.B = Reverse Biased.



Emitter :- The section on one side that supplies charge carriers (e⁻ or h⁺) is called emitter.
 e⁻ → electron
 h⁺ → hole

The emitter is always forward biased w.r. to base so that it can supply

a large number of majority carriers. The emitter is heavily doped so that it can inject large number of charge carriers (e or h) to the base.

Collector :-

The section on the other side which collects the charges is called the collector. The collector is always reverse biased w.r. to base.

In p-n-p transistor it receives the holes and in n-p-n transistor, it receives the electrons. Collector is moderately doped.

During the transistor operation, much heat is produced at the collector junction. So collector is made larger in size to dissipate the heat.

Base :-




The middle section which forms a p-n junction between the emitter & collector is called the base. The base-emitter junction is forward biased, allowing low resistance for emitter ckt. The base-collector is reverse biased and provides high resistance in the collector ckt.

The base has thin area of cross section & is lightly doped. It passes most of the emitter injected charge carriers to the collector.

Transistor Operation :-

PNP transistor can be redrawn without base-to-collector bias. It is similar to PN junction i.e. forward biased. The depletion

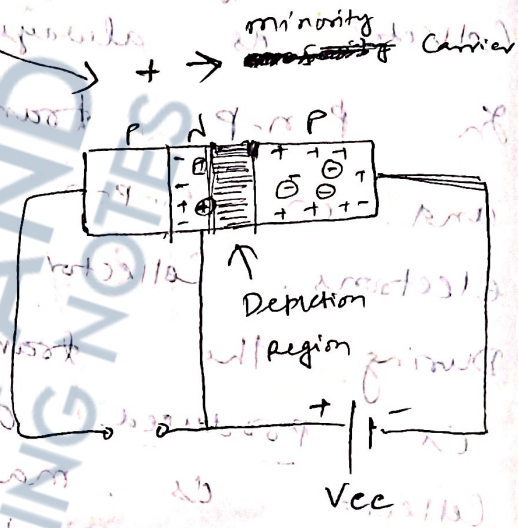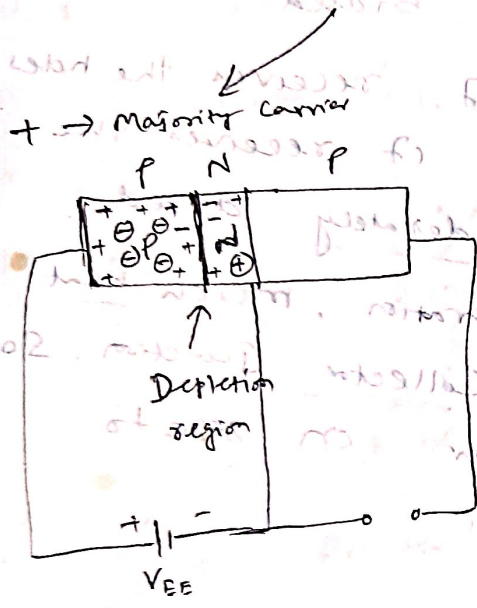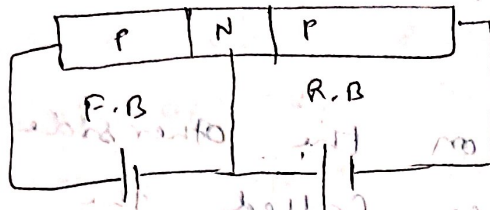region has been reduced in width due to applied bias, resulting in a heavy flow of majority carriers from p to n type material.



F.B PNP

R.B PNP

Now remove base-emitter bias of PNP transistor. Similarly reverse bias the diode. The flow of majority carrier is zero, resulting only the minority carrier flow.

→ One p-n junction where other is forward biased.

→ When both biasing potential have been applied to PNP transistor, with the resulting majority and minority carrier flows indicated in figure 1.

→ The width of depletion layer indicates which junction is F.B and which is R.B.

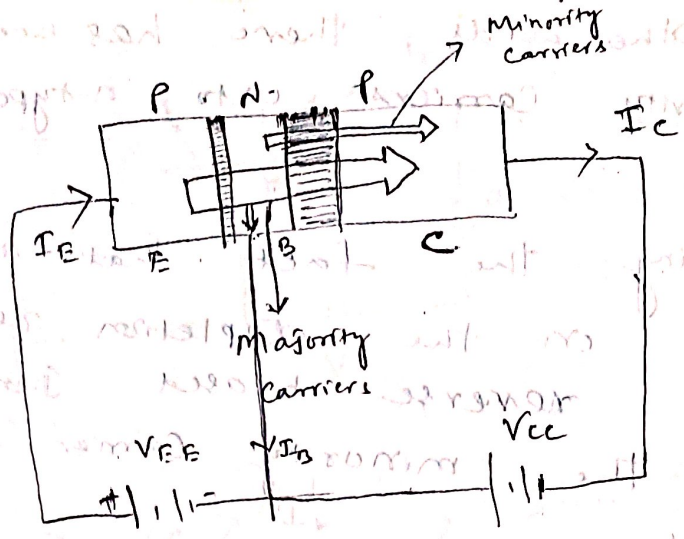


Fig. 1 :- Majority and minority carrier flow of PNP transistor

- A large no. of majority carriers will diffuse across the forward-biased P-n junction into n-type material.
- Since the sandwiched n-type material is very thin & has low conductivity, a very small no. of these carriers will take their path of high resistance to the base material.
- The magnitude of the base current is typically of the order of μA , as compared to the order of milli ampere for emitter & collector currents.
- The large no. of majority carriers will diffuse across the reverse-biased junction into p-type material connected to the collector terminal.
- The reason for the relative ease with which majority carrier can cross the reverse-biased junction is easily understood if we consider that for reverse biased diode injected majority carriers will appear as minority carriers in the n-type material.

→ In other words, there has been an injection of minority carriers into n-type base-region material.

→ Combining the fact that all the minority carriers in the depletion region will cross the reverse biased junction of a diode, the minority carrier flow is shown in fig 1.

→ ∴ Total Current

$$I_E = I_B + I_C$$

→ The Collector current, however, comprises two components → (majority, minority)


→ The minority current component is called leakage current & it is given symbol I_{CO} (I_C current with emitter ~~base~~ terminal open)


$$\Rightarrow I_C = I_{C \text{ majority}} + I_{CO \text{ minority}}$$

Transistor Configuration :-

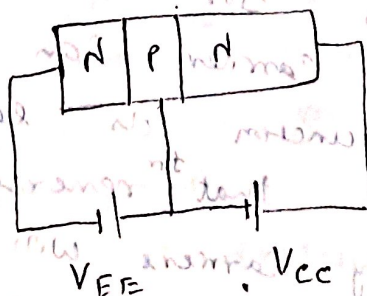1) Common-Base configuration :-

In this configuration, base terminal is common to the i/p and o/p. Input is applied between emitter and base and o/p is taken across collector to base.



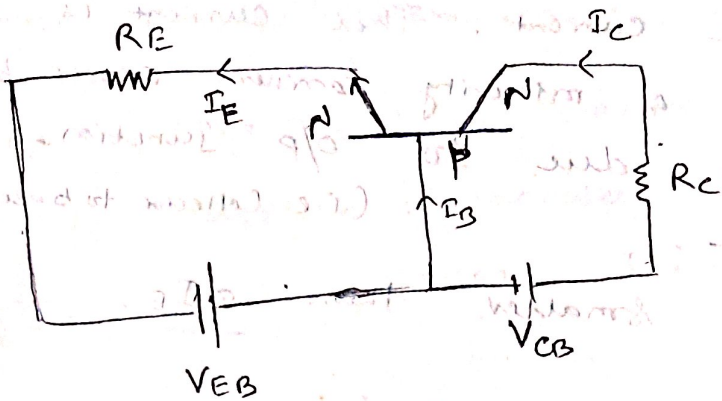

$I_E > I_C > I_B$, Since I_B is in mA
 $I_E \approx I_C$

→ Since base is common betⁿ C/P & E, it is called common base configuration. So C/P is O/P.


→ During the connection, E-B junction should be forward biased and C-B junction should be reverse biased.

Common Base current gain (α)

It is defined as the rate of change of collector current with the change of emitter current under the assumption that voltage betⁿ collector to base is constant.

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad V_{CB} = \text{const.} \quad \alpha \approx 0.95$$

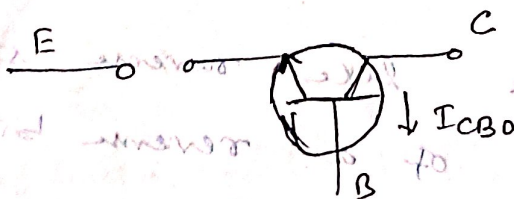I_{CBO} = It is the leakage current between base & collector when emitter is open.



→ Therefore total collector current consists of

(a) Part of emitter current which reaches the collector terminal i.e. αI_E

(b) The leakage current. This current is due to the movement of minority carriers across base collector junction due to o/p junction, i.e reverse biased. (i.e Collector to base)

It is much smaller than αI_E .

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C (1 - \alpha) = \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

$$\therefore I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

I_{CBO} may be called I_{CO} .

(1)

To calculate I_B

$$I_C = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_E - I_B = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_E - \alpha I_E - I_{CBO} = I_B$$

$$\Rightarrow I_B = (1 - \alpha) I_E - I_{CO}$$

(2)

Note :-

$\rightarrow I_{CBO}$ is like reverse saturation current,


I_S w I_0 of a reverse biased diode.

\rightarrow It is extremely temp. dependent. I_{CBO}


doubles every 10°C rise of temp for Ge
 & 6°C for Si.

Common Emitter Configuration :-

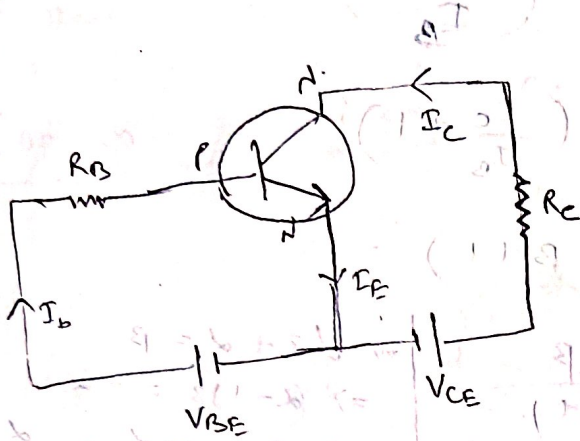Emitter terminal is common between i/p & o/p.
 i/p → applied between base & emitter.
 o/p → is taken from collector & emitter.



(NPN)

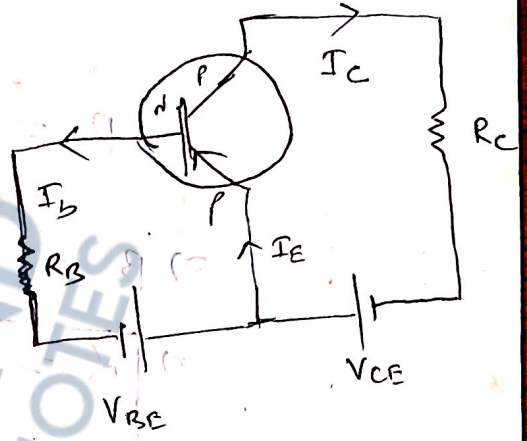

(PNP)

Current Amplification factor

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \left[V_{CE} = \text{const} \right]$$

$\beta \approx 50 \text{ to } 450$

Relation betⁿ α & β

$$\beta = \frac{I_C}{I_B}$$

$$= \frac{\alpha I_E}{I_B} \quad \left(I_E = \frac{I_C}{\alpha} \right)$$

$$= \frac{\alpha (I_C + I_B)}{I_B}$$

$$\alpha \frac{I_C}{I_B} + \alpha$$

$$\beta = \alpha \cdot \beta + \alpha \quad \Rightarrow \quad \alpha = \frac{\beta}{1 + \beta}$$

$$\Rightarrow \quad \alpha = \frac{\beta}{1 + \beta}$$

(3)

Or

$$\beta = \frac{I_C}{I_B}$$

$$= \frac{I_C}{I_E} \cdot \frac{I_E}{I_B}$$

$$= \alpha \cdot \left(\frac{I_E + I_B}{I_B} \right)$$

$$\left(\because \alpha = \frac{I_C}{I_E} \right)$$

$$\beta = \alpha \left(\frac{I_C}{I_B} + 1 \right)$$

$$\Rightarrow \beta = \alpha (\beta + 1)$$

$$\Rightarrow \alpha = \frac{\beta}{\beta + 1}$$

$$\begin{aligned} \Rightarrow \alpha \beta + \alpha &= \beta \\ \Rightarrow (\alpha - 1)\beta &= -\alpha \\ \Rightarrow \beta &= \frac{-\alpha}{\alpha - 1} = \frac{\alpha}{1 - \alpha} \end{aligned}$$


Concept of I_{CEO}

$$\Rightarrow \beta = \frac{\alpha}{1 - \alpha} \quad \text{--- (4)}$$

In CE Configuration, if $I_B = 0$, still a leakage current flows from collector to emitter. It is called I_{CEO} . The subscript specifies that for collector to emitter current when base is open.

From the eqn (1),
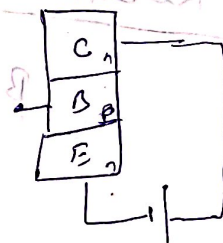
$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$



$$\text{If } I_B = 0, \quad I_C = I_{CEO}$$

$$\Rightarrow I_{CEO} = \frac{1}{1 - \alpha} \cdot I_{CBO}$$

$$\Rightarrow I_{CEO} = (1 + \beta) I_{CBO} \quad \text{--- (5)}$$

$$\because \beta = \frac{\alpha}{1 - \alpha}$$

$$\Rightarrow 1 + \beta = 1 + \frac{\alpha}{1 - \alpha}$$

$$= \frac{1 - \alpha + \alpha}{1 - \alpha}$$

$$\Rightarrow 1 + \beta = \frac{1}{1 - \alpha}$$

Relⁿ

between 2 leakage currents.

Considering leakage current into account


Common emitter

$$I_C = \beta I_B + I_{CEO}$$

Common Base

$$I_C = \alpha I_E + I_{CBO}$$

Common Collector Configuration :-

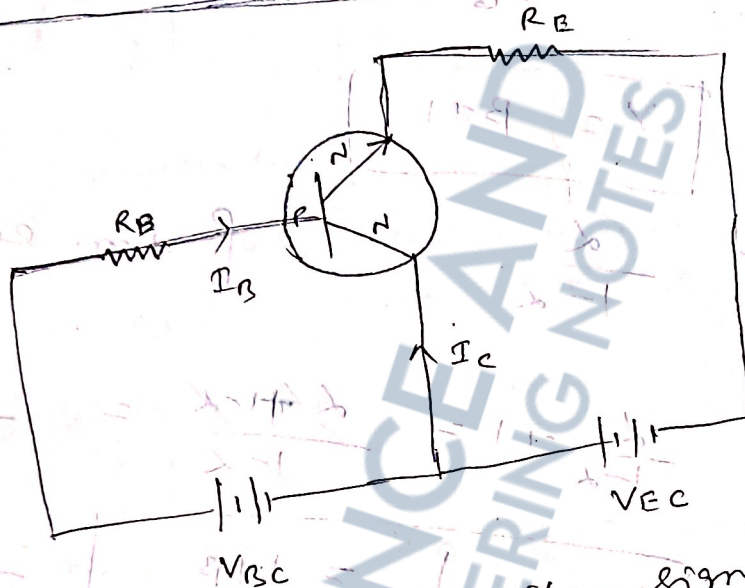

→ In this configuration, signal is applied between base & collector & o/p signal is taken out from emitter collector ckt.

→ Here i/p current is (I_B) & o/p current is emitter current (I_E)

→ The current gain of the ckt denoted by (γ) [gamma] is defined as ratio of change in emitter current (ΔI_E) to change in base current (ΔI_B) , i.e.

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\gamma \approx 500$$

Relation between α, β, γ

$$\gamma = \frac{\Delta I_E}{\Delta I_B}, \quad \beta = \frac{\Delta I_C}{\Delta I_B}, \quad \alpha = \frac{\Delta I_C}{\Delta I_E}$$

Relⁿ betⁿ γ & β

$$\gamma = \frac{I_E}{I_B} = \frac{I_C + I_B}{I_B} \Rightarrow \frac{I_C}{I_B} + 1 = \beta + 1$$

$$\boxed{\gamma = \beta + 1}$$

But $\beta = \frac{\alpha}{1 - \alpha}$ [from eqⁿ (4)]

$$\therefore \gamma = \frac{\alpha}{1 - \alpha} + 1 = \frac{\alpha + 1 - \alpha}{1 - \alpha} = \frac{1}{1 - \alpha}$$

$$\boxed{\gamma = \frac{1}{1 - \alpha} = 1 + \beta} \quad \text{--- (8)}$$

$$\beta = \frac{I_C}{I_B} = \frac{I_C}{I_E} \cdot \frac{I_E}{I_B} = \alpha \cdot \gamma$$

$$\boxed{\beta = \alpha \gamma} \quad \text{--- (9)}$$


Previously

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}} \quad \text{--- (10)}$$

$$\boxed{\alpha = \frac{\beta}{1 + \beta}} \quad \text{--- (11)}$$

Characteristics of BJT :-

Common-base Characteristics :-

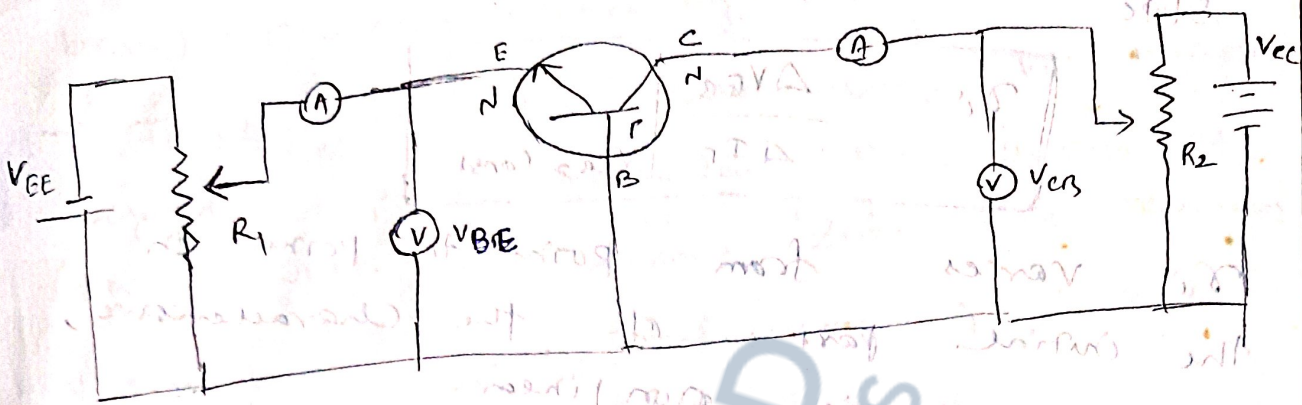


I/P Characteristics :-

The I/P Characteristics shows how I_E (emitter current) varies with V_{BE} (base-emitter voltage) when V_{CB} (collector voltage) is held constant.

The voltage V_{CB} is adjusted to a suitable value with help of R_2 , then V_{BE} is increased in a number of discrete steps and corresponding value of I_E are noted in milliammeter. When plotted, we get the I/P characteristics as shown in fig 2.

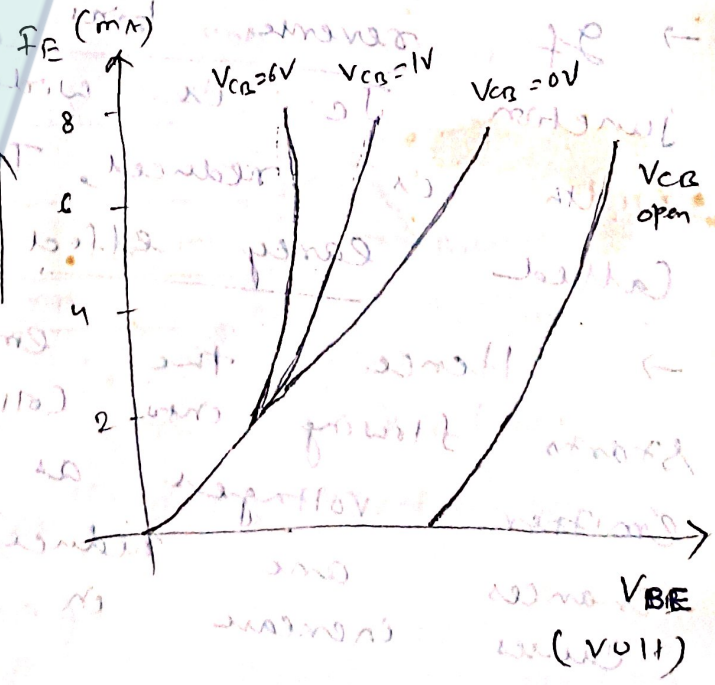For a given value of V_{CB} the curve is just like forward biased P-N junction because emitter-base junction is forward biased mode similar to P-N junction.



The characteristics may be used to determine r_i resistance (r_i) of the transistor. Its value is given by reciprocal of its slope

$$r_i = \frac{\Delta V_{EB}}{\Delta I_E} \quad | \quad V_{CB} = \text{Const}$$

r_i varies from point to point on the initial part of the characteristic, because it is non-linear

→ With increase in V_{CB} , the current gains its max value early.

✓ Early effect :-

→ In P-N junction, we have seen, the barrier potential proportional to the square of the space charge region width.

$$W \propto \sqrt{\text{Reverse Bias}}$$

$$\Rightarrow W^2 = K \cdot (\text{Reverse bias})$$

→ If reverse bias is increased, the junction width is widened & effective base width is reduced, This phenomenon is called early effect.

→ Hence the emitter current I_E starts flowing into collector region at lower voltages as the recombination is reduced in the base. This causes increase in current gain β .


Secondly, as the base width get narrowed the conc. gradient increases, so that in section of minority carriers (say holes for an n base) increases, there by increasing I_E .

→ Thirdly, if the reverse bias V_{CB} increased beyond point, breakdown may occur as the width w becomes zero. The phenomenon (base width becomes narrow & narrow) called Punch through or slack through.

→ Early effect is also known as base width modulation.

Output Characteristics

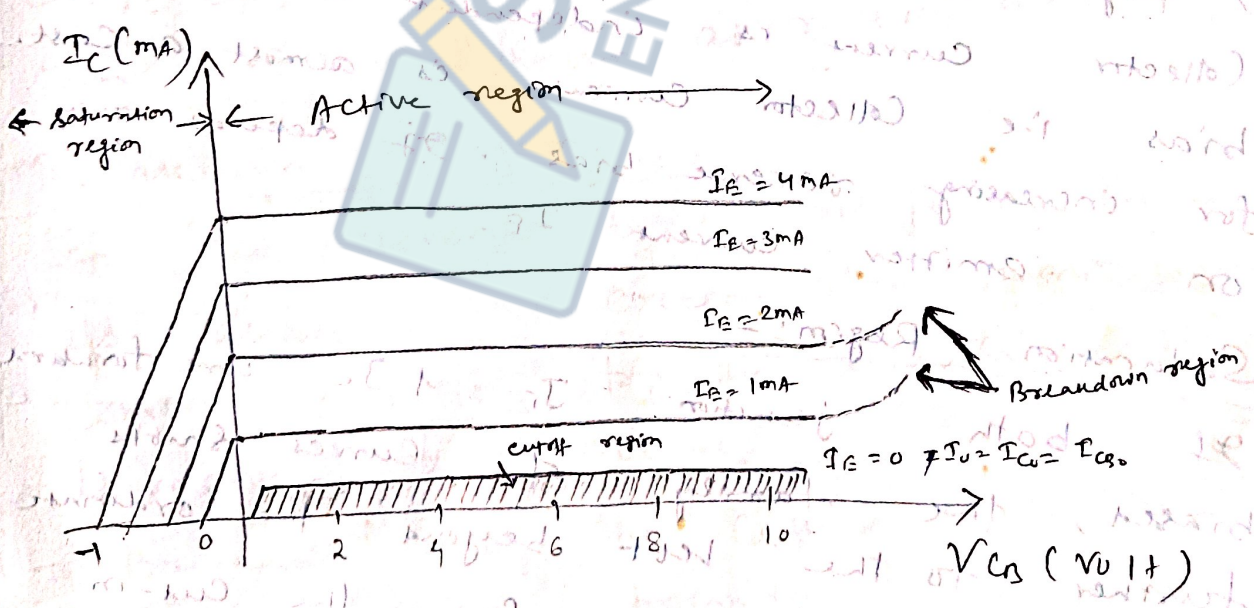The O/P characteristics as a family of curves of collector current (I_C) versus collector base voltage V_{CB} at different emitter current I_E .



(O/P Characteristics of CB Configuration for NPN transistor)

J_E	J_C	Remarks
F.B	R.B	Active
F.B	F.B	Saturation
R.B	F.B	Reverse Active
R.B	R.B	Cut off

$J_E \rightarrow$ Emitter-base Junction.

$J_C \rightarrow$ Collector-base Junction.

\rightarrow If $I_E = 0$, i.e. when no forward bias applied to J_E , the reverse saturation current I_{CO} flows on the collector side.

Active region:-

The region of the curve on $V_{CB} - I_C$, when J_E is forward biased & J_C is reverse biased is called active region.

\rightarrow Figure shows, in the active region the collector current is independent of reverse bias i.e. collector current is almost a const. for increasing reverse bias. It depends only on emitter current I_E .

Saturation Region:-

If both junction J_E & J_C are forward biased, the family of curves shifts further to the left beyond the ordinate (y-axis) and starts from the cut-in voltage of collector-base diode.

\rightarrow In this region, collector current I_C flows

Even when $V_{CB} \approx 0$. Even when the externally applied bias voltage is reduced to zero, there is still a barrier potential existing at the collector base junction and this assists in the flow of I_C .

→ I_C increases exponentially as per the law of junction studied on PN junction. The region around the knee is the saturation region.

Cut-off region:-

→ This is the region when both J_E and J_C are reverse biased. A very small current I_C flows even when $I_E = 0$. This is the collector leakage current I_{CBO} or I_{CO} . The region below the curve is the cutoff region.

Reverse Active region:-

If emitter junction (J_E) is reverse biased and collector junction is forward biased (J_C) then it is known as reverse active mode.

Breakdown Region:-

If the reverse bias voltage on CB config is allowed to exceed the max^m safe limit specified by the manufacturer, device breakdown may occur.

→ Breakdown may be caused by the same effect as diodes breakdown.

① → Breakdown can also result from the CB depletion region penetrating into the base until it makes contact with EB depletion


Region. This condition is known as punch through or reach through and very large current can flow when it occurs, possibly destroy the device.

Base-spreading Resistance :-

Lets consider a NPN transistor, with depletion layer penetrating the base, the base holes are confined to the thin region of P-type semiconductor. The resistance of this region (or section) is called the base-spreading resistance r_{bb}

* extra
Eber-Moll Model :-

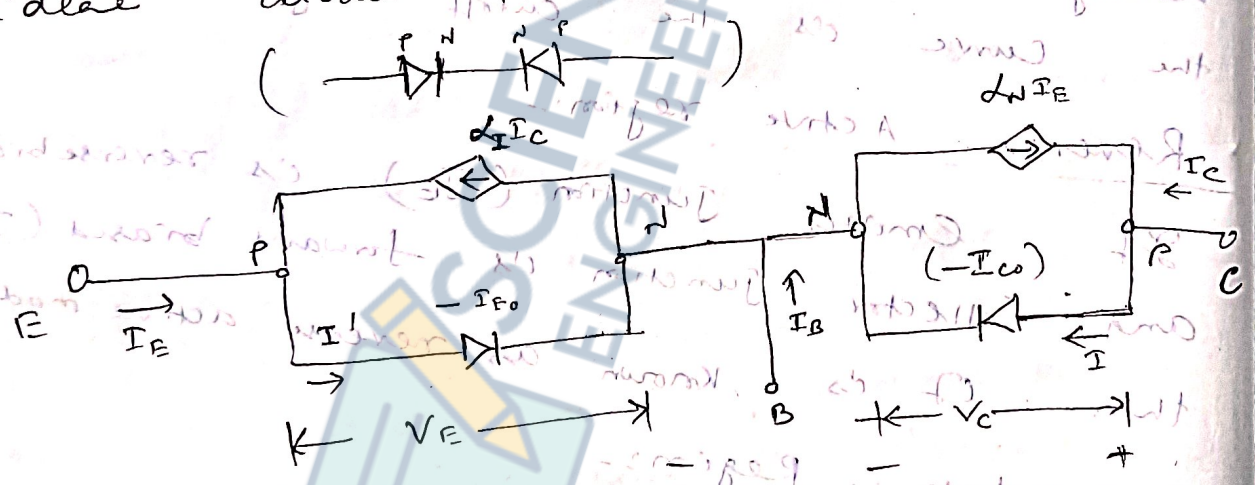→ A transistor can be thought as 2 ideal diodes placed back to back,



→ For a P-N-P transistor, both I_{C0} and I_{E0} are -ve, so that $-I_{C0}$ & $-I_{E0}$ are +ve values, giving the magnitude of the reverse saturation currents of the diodes.

$$I_C = -\alpha_N I_E - I_{C0} \left[e^{V_C/V_T} - 1 \right] \quad \text{--- (1)}$$

$$I_E = -\alpha_I I_C - I_{EO} \left[e^{V_E/V_T} - 1 \right] \quad \text{--- (2)}$$


Subscript N to α has been added in order to indicate the normal operation of the transistor.

→ Subscript I stands for inverted mode. α_I is the inverted current gain. I_{EO} is the emitter junction reverse saturation current & V_E is the voltage drop from P side to N side (at the emitter) junction and is positive for a forward-biased emitter.

→ The dependency of currents in a transistor upon the junction voltages in reverse are shown in eqn (1) & (2).

→ The dependent current sources can be eliminated provided $\alpha_N = \alpha_I = 0$, length of the minority carriers in the base, all the minority carriers will recombine in the base & none will survive to reach collector, in such condⁿ transport factor β and hence current gain factor α will be zero. Thus under these condⁿ the transistor action ceases & we simply have 2 diodes placed back to back.


Common Emitter Characteristics: -

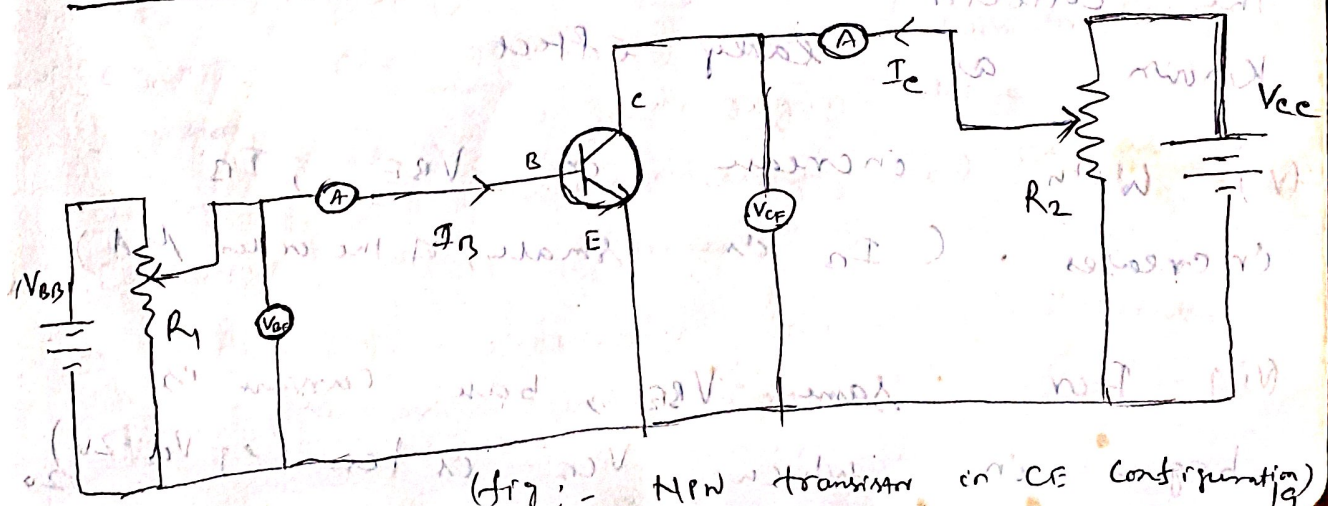

I/P Characteristics

I/P Characteristics are the family of curves of $V_{BE} - I_B$. Base current at different base emitter voltage keeping V_{CE} as constant.

→ We note the following from the curves.

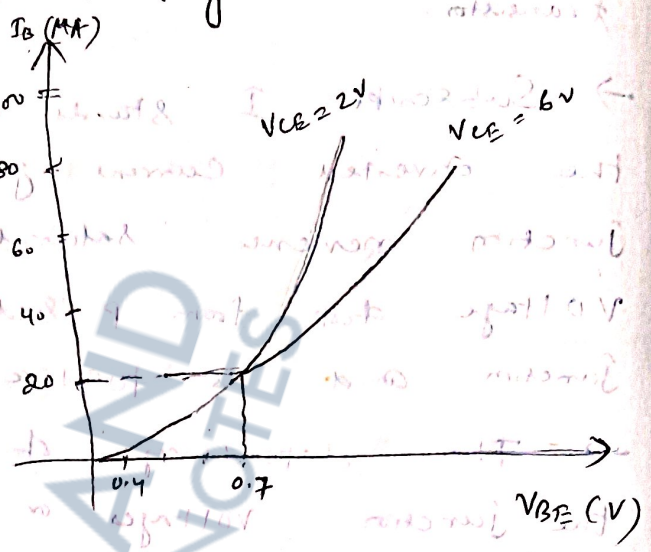

(i) When both i/p voltage V_{BE} and o/p voltage V_{CE} are 0V.

No o/p current
 $I_C = 0, I_B = 0.$

(ii) Current starts flowing into base after the cut-in voltage $V = 0.5V.$

(iii) If the CE junction is short circuited ($V_{CE} = 0V$) the forward biased BE (Base-emitter) junction behaves essentially like a diode.

(iv) When V_{CE} is increased, the space charge width increases reducing the base width so that the majority carriers, 98% of them are able to reach the collector with minimum recombination, known as Early effect.

(v) With increase in V_{BE} , I_B increases. (I_B is small, of the order μA)

(vi) For same V_{BE} , base current is higher in which V_{CE} is less (e.g. $V_{CE} = 2V$)

Because as V_{CE} increases, I_C will increase but I_B will decrease.

$$(I_E = I_B \downarrow + I_C \uparrow)$$

(VII) Dynamic resistance (r_i)

$$r_i = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE} = \text{constant}} = \frac{1}{\text{Slope}}$$

O/p Characteristics :-

The O/p characteristics are the family of curves of collector current at different emitter voltages for a given values of base current.

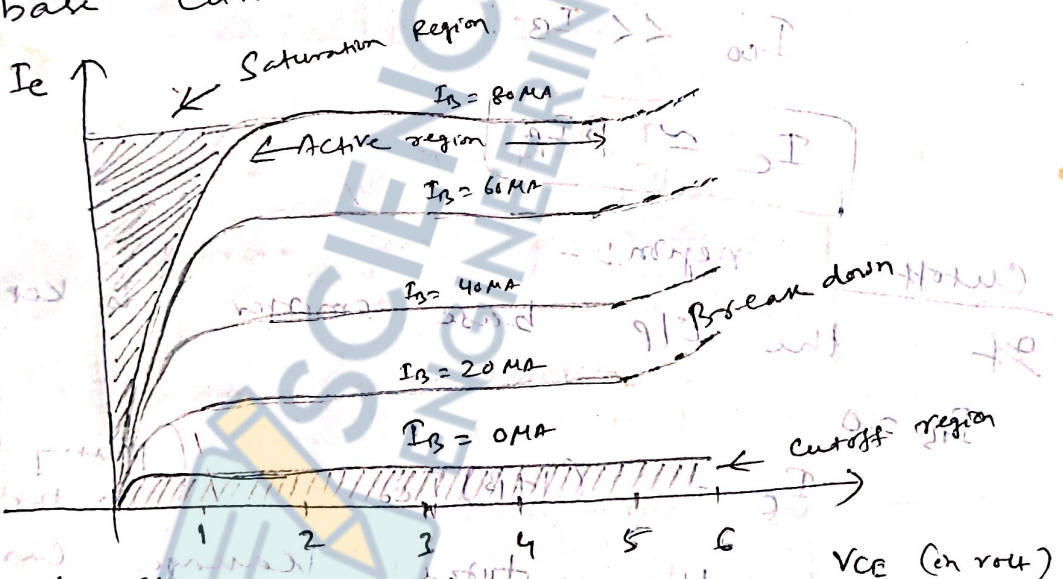


Fig:- O/p characteristics for CE NPN transistor

Active Region :-

It is the forward biased base-emitter junction and reverse biased collector-emitter junction. It is the region where the O/p current i.e. collector current (I_C) is almost constant for different I_B .

→ As the forward bias is increased, I_B increases with consequent increase in I_C .

$$\begin{aligned} \rightarrow I_C &= \alpha I_E + I_{CO} \\ &= \alpha (I_B + I_C) + I_{CO} \\ &= \alpha I_B + \alpha I_C + I_{CO} \end{aligned}$$

$$\Rightarrow I_C (1 - \alpha) = \alpha I_B + I_{CO}$$

$$\Rightarrow I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CO}$$

$$\Rightarrow I_C = \beta I_B + (1 + \beta) I_{CO}$$

$$\therefore \frac{1}{1 - \alpha} = 1 + \beta$$

I_{CO} = Reverse saturation current due to reverse biasing of CB junction which is very small.

$$I_{CO} \ll I_B$$

$$I_C \approx \beta I_B$$

Cutoff region:-

If the CB base-emitter is kept open,

$$I_B = 0$$

$$I_C = (1 + \beta) I_{CO}$$

(putting $I_B = 0$, in the above eq)

This is the total leakage current flowing through the whole transistor.

Saturation region:-

If both base-emitter & emitter-collector junction are forward biased, $V_{CE} = V_{BE} + V_{BC}$,

$\rightarrow V_{BE}$ is only few tenths of the volt,

V_{BC} is also of the same order, Hence,

the family of curves starts off from very

Close to the coordinate (V_{CE}, I_C) . The knee of curves represent the saturation region.

$$\rightarrow R_C(\text{sat}) = \frac{V_{CE}}{I_C}$$

Saturation resistance is very low, of the order 5Ω or less.

O/p Resistance -


Defined as the ratio of change in collector-emitter voltage (ΔV_{CE}) to the change in the collector current (ΔI_C) at const. base current.

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C} \Big|_{I_B = \text{const.}}$$

DC Current gain $\beta = \frac{I_C}{I_B}$

AC Current gain $\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE} = \text{const.}}$


Common Collector Characteristics:-

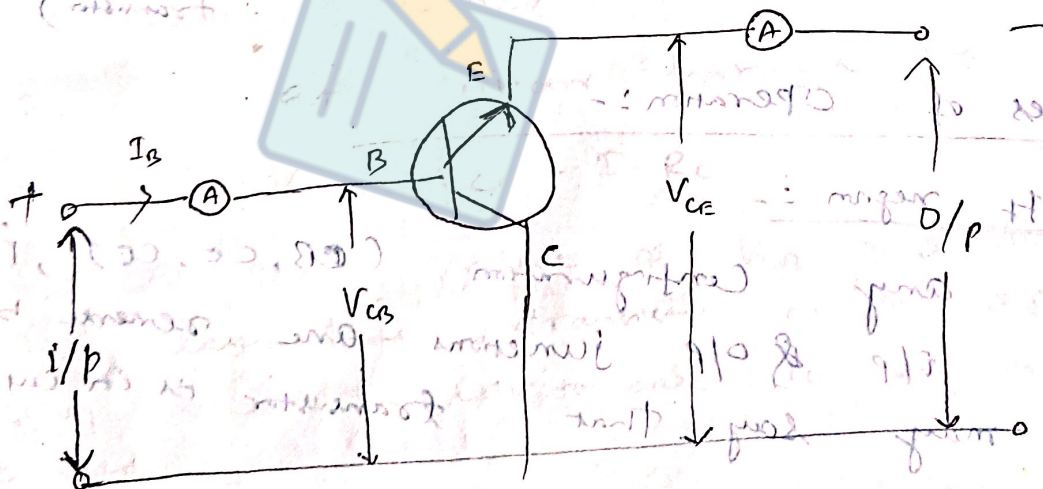


\rightarrow The collector terminal is common to both I/P (CCB) & O/P (CE).

→ Common (Collector) (CC) i/p characteristics
 is a plot of V_{CE} versus I_B for different values of V_{CE} . (Fig. 1)

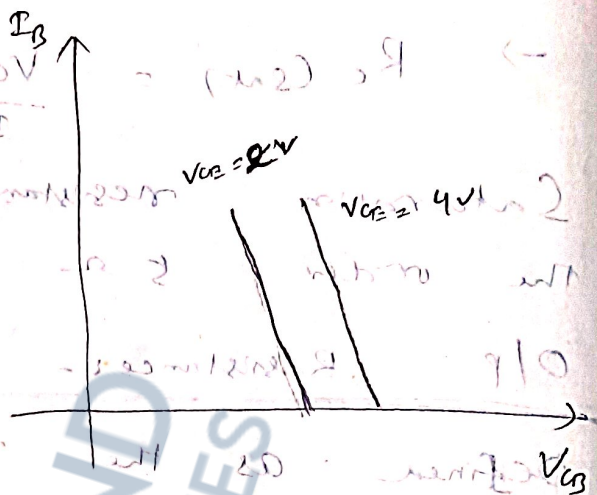→ The o/p characteristics is I_E (o/p current) versus V_{CE} for different I_B .



→ The o/p characteristics is practically identical to that of CE cut, as shown in fig. 2

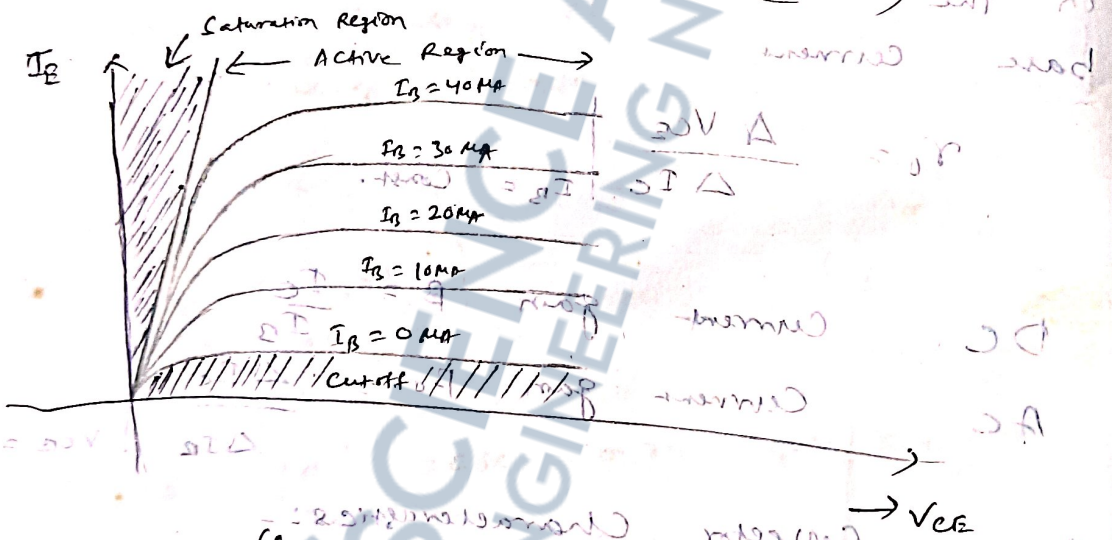


(Fig. 2) - o/p characteristics of CC NPN transistor

Modes of operation :-

Cut off region :-

→ In any configuration (CB, CE, CC), if both i/p & o/p junctions are reverse biased we may say that transistor is in cut off mode.

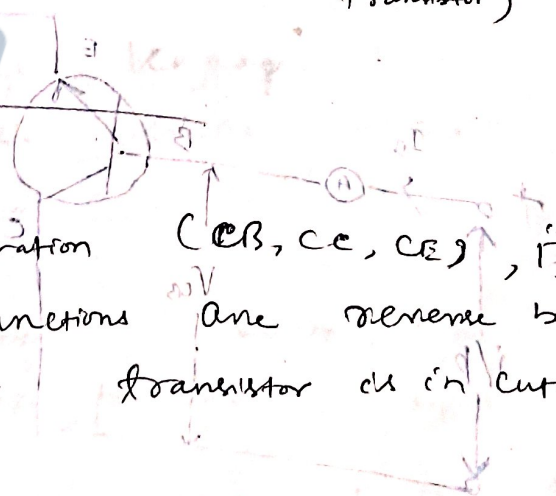→ Even if the value of the i/p applied voltage V_i is less than the threshold value of transistor (for $V_s = 0.7V$ & $V_{be} = 0.3V$)



The transistor will not conduct, very small current will flow. (25)

→ Therefore, in cutoff mode, the following condⁿ will mate.

i.e base current, $I_B = 0$

emitter current, $I_E = 0$

collector current, $I_C = 0$

collector potential, $V_C = V_{CC}$

Active Region :-

→ In a active mode of transistor, i/p junction i.e emitter junction should be forward biased and o/p junction must be reverse biased.

→ Since i/p junction is forward biased, the i/p voltage V_i is greater than threshold value of transistor, then we have

$$I_B = \frac{V_i - V_{BE}}{R_B}$$

Now current gain in CE configuration is β

$$I_C = \beta I_B$$

Potential at collector terminal i.e

$$V_C = V_{CC} - I_C R_C$$

→ If the value of $V_C > 0$, then we will say that transistor is in active region because collector-base junction is reverse biased.

Therefore in active region following steps to be followed.

(i) Calculate i/p current i.e base current (I_B)

(ii) Calculate the collector current (I_C)

(iii) Calculate $V_c = V_{cc} - I_c R_c$

(iv) Calculate $V_{ce} = V_c - V_b$

(v) If $V_{ce} > 0$, then transistor is in active region.

Saturation Region :-

If both the junctions are forward biased then the transistor is in saturation region.

$$\rightarrow I_c (\text{sat}) = \frac{V_{cc} - V_{ce}}{R_c}$$

and $I_B = \frac{I_c (\text{sat})}{\beta_{\text{force}}}$

from the cut, $I_B = \frac{V_i - V_{BE}}{R_B}$


If $I_B > I_B (\text{sat})$, then transistor is in saturation region & the ratio $\frac{I_c (\text{sat})}{I_B}$ is called the overdrive factor (β_{force}).

$$\beta_{\text{force}} = \frac{I_c (\text{sat})}{I_B}$$

BJT as an amplifier :-

→ A device that raises the strength of a weak signal is called an amplifier.

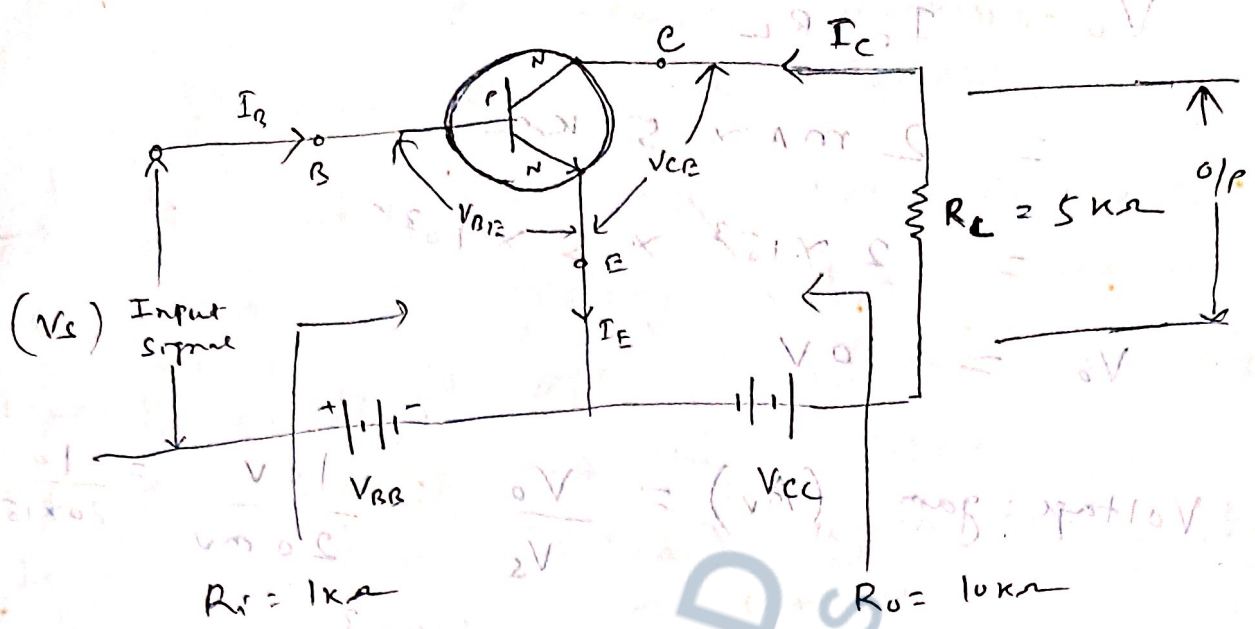→ Generally CE configuration is used for transistor's amplifying action.



→ A signal source V_s is connected in the i/p ckt. The load resistance $5k\Omega$ is connected across the o/p terminal.

→ Since the base-emitter junction is forward biased, it offers very low resistance to the signal source V_s .

→ However collector-emitter (C-E) junction due to reverse biased, offers high resistance.

Let

$$V_s = 20\text{mV} = 20 \times 10^{-3}\text{V}$$

$$R_i = 1k\Omega = 1 \times 10^3\Omega$$

$$I_B = \frac{V_s}{R_i} = \frac{20 \times 10^{-3}}{1 \times 10^3} = 20 \times 10^{-6} = 20\mu\text{A}$$

Assume, dc current gain (β) of the transistor is 100. So effective value of collector current $I_C = \beta I_B$.

$$\therefore I_C = 100 \times \frac{20 \times 10^{-6}}{1} = 2\text{mA}$$

$$V_o = I_{c} R_L$$

$$= 2 \text{ mA} \times 5 \text{ k}\Omega$$

$$= 2 \times 10^{-3} \times 5 \times 10^3$$

$$V_o = 10 \text{ V}$$

$$\text{Voltage gain } (A_v) = \frac{V_o}{V_s} = \frac{10 \text{ V}}{20 \text{ mV}} = \frac{10}{20 \times 10^{-3}}$$

$$= 0.5 \times 10^3$$



$$A_v = 500$$

Thus, transistor's amplifying action is basically due to capability of transferring its signal current from a low resistance to high resistance ckt.

Transfer + Resistor = Transistor

BJT as a switch:

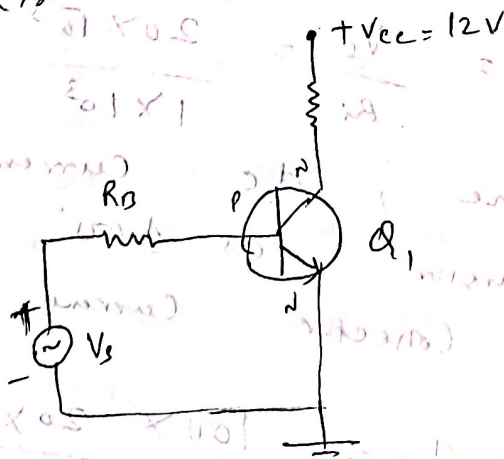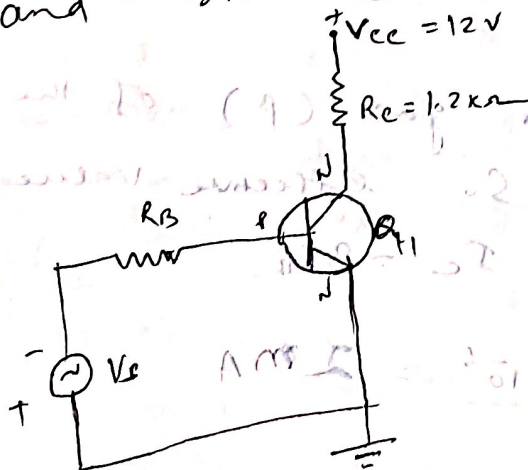- A BJT can be used as a switch.
- It is biased off (switch off) when $I_c = 0$
- and biased on (switch on) when $I_c = \text{maximum}$



- Fig (a) - 'off' biased transistor.
- (b) - 'on' biased transistor.

→ In fig (a), a -ve polarity of the base r/p voltage (V_{be}) biased the transistor (Q1) off. In this case only current flowing through the collector base leakage current (I_{CBO}) which is normally so small that it can be neglected.

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_B = 0 \Rightarrow I_C = 0 \quad (\because I_C = \beta I_B)$$

$$\therefore V_{CE} = V_{CC} \quad (1)$$

$$\frac{i/p}{0} \rightarrow \frac{o/p}{1}$$

→ In fig (b), a +ve polarity of base r/p voltage ensure transistor is in 'on' state and collector current I_C is max.

$$V_{CE} = V_{CC} - I_C R_C$$

Since $I_C = I_{C_{max}}$

$$V_{CC} \approx I_C R_C$$


$$\therefore V_{CE} = 0 \quad \frac{i/p}{1} \rightarrow \frac{o/p}{0}$$

Summary:

During Cutoff (Switch off)

$$i/p = 0 \text{ or } -ve, \quad I_C = 0, \quad V_{CE} \approx V_{CC} \text{ (say } 12V)$$
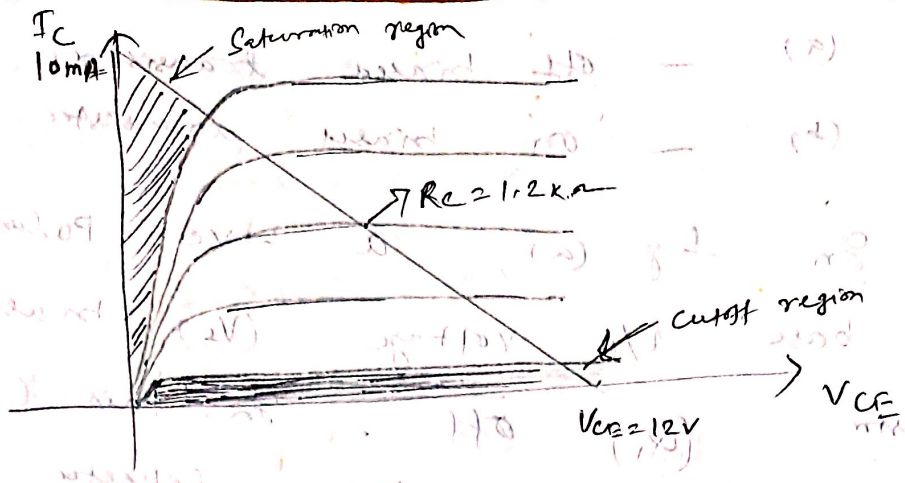
$$I_f \approx 0, \quad \therefore \frac{o/p}{1}$$



During Saturation (Switch on)

$i/p = 1 \approx I_C = I_{Cmax}, V_{CE} \approx 0$
 $I_C = 10mA (sat)$

Thus Transistor can act as a switch

Comparison

Parameters	CB	CE	C-C
1) I/P resistance	Very low ($\approx 10\Omega$)	low ($\approx 75\Omega$)	Very high ($750k\Omega$)
2) O/P resistance	Very high I. ($\approx 1M\Omega$)	High ($\approx 10k\Omega$)	low $\approx 50\Omega$
3) Current gain	Very less (≈ 0.98) ($\therefore \alpha < 1$)	High ($10-500$) ($\beta \gg 1$)	Very High (> 500) ($\gamma \gg 1$)
4) Voltage gain	Small (≈ 50)	Very high (≈ 500)	Very less (< 1)
uses	As high freq. amplification. As a Current Buffer ($\alpha \approx 1$)	As an amplifier & audio freq. application	Impedance matching. As a voltage buffer ($\gamma \gg 1$)

→ CC is never used as amplifier due to low voltage gain, high I/P impedance, it is preferred for impedance matching.

→ CE is used as amplifier, due to high voltage gain & current gain, \Rightarrow high power gain ($\therefore \text{Power gain} = \text{Voltage gain} \times \text{Current gain}$)