

Ch-4 - Microwave Filters [POZAR BOOK]

359

A microwave filter is a 2-port network used to control the freq. response at a certain point in a microwave system by providing transmission at frequencies within the passband of the filter and attenuation in the stopband of the filter. Typical freq responses include low-pass, highpass, bandpass and band-reject characteristics. Applications can be found in virtually any type of microwave communication, radar or test and measurement system.

Periodic Structures :-

An infinite transmission line or waveguide periodically loaded with reactive elements is referred to as periodic structure. As shown in fig 1, periodic structure can take various forms, depending on the transmission

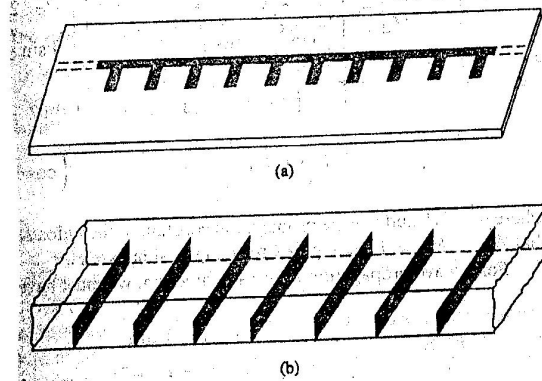


Fig 1:-
Examples of periodic structures. (a) Periodic stubs on a microstrip line. (b) Periodic diaphragms in a waveguide.

line means being used. Often the loading elements are formed as discontinuities on the line, but in any case they can be modeled as lumped reactances

across a transmission line as shown in figure 2.

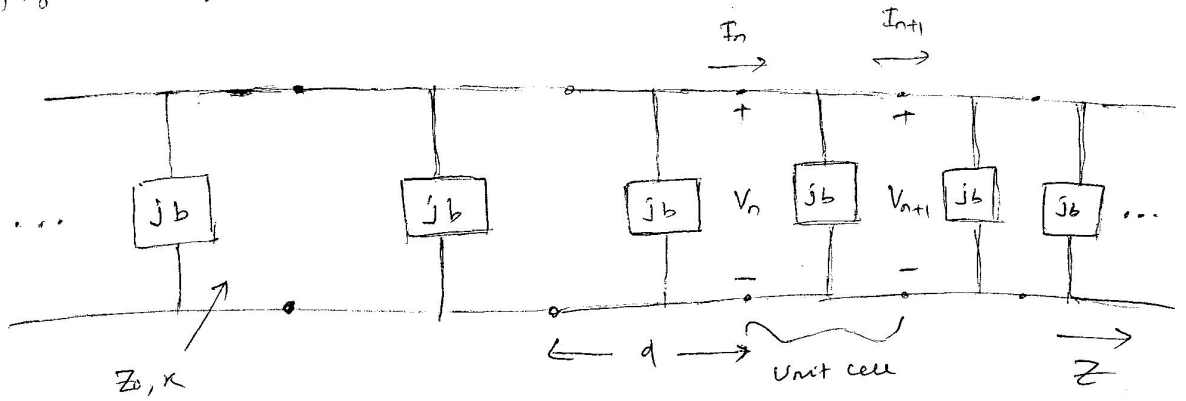


Fig 21 - Equivalent circuit of a periodically loaded transmission line. The unloaded line has characteristic impedance Z_0 and propagation constant k .

→ Periodic structures support slow-wave propagation (Slower than phase velocity of the unloaded line) and have passbands and stopbands characteristics similar to those filters; they find application in TWT, phase shifters and antennas (Traveling wave Tube)

→ Analysis of Infinite periodic structure: -

The analysis can be done using the propagation characteristic of the infinite loaded line shown in fig 2. Each unit cell of this line consists of length d of T.L with a shunt ~~susceptance~~ ^{susceptance} across the midpoint of the line; the susceptance 'b' is normalized to the characteristic impedance, Z_0 .

If we consider the infinite line as being

elements
any
stances

Composed of a cascade of identical two-port 356
 n/w's, we can relate the voltages and currents
 on either side of the nth unit cell
 using ABCD matrix:

$$\begin{bmatrix} V_n \\ I_n \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix} \quad \text{--- (1)} \Rightarrow$$

Where A, B, C, D are matrix parameters for a
 cascade of a transmission line section of length $\frac{d}{2}$
 and a shunt susceptance b and another T-L
 section of length $\frac{d}{2}$.

In normalized form,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j b & 1 \end{bmatrix} \begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix}$$

* Directly written in book

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \left(\cos \theta - \frac{1}{2} \sin \theta \right) & j \left(\sin \theta + \frac{1}{2} \cos \theta - \frac{1}{2} \right) \\ j \left(\sin \theta + \frac{1}{2} \cos \theta + \frac{1}{2} \right) & \left(\cos \theta - \frac{1}{2} \sin \theta \right) \end{bmatrix}$$

* Proof:

$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix} &= \begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j b & 1 \end{bmatrix} \begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \\ &= \begin{bmatrix} \cos \frac{\theta}{2} - b \sin \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} + j b \cos \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \end{aligned}$$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos^2 \frac{\alpha}{2} - b \sin^2 \frac{\alpha}{2} & \cos \frac{\alpha}{2} - \sin^2 \frac{\alpha}{2} \\ j \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} + j b \cos^2 \frac{\alpha}{2} & + j \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} \end{bmatrix}$$

$$\begin{bmatrix} j \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} \\ -j b \sin^2 \frac{\alpha}{2} + j \sin^2 \frac{\alpha}{2} \cos \frac{\alpha}{2} \\ -\sin^2 \frac{\alpha}{2} + b \sin^2 \frac{\alpha}{2} \cos \frac{\alpha}{2} \\ + \cos^2 \frac{\alpha}{2} \end{bmatrix}$$

(1)

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \alpha - \frac{b}{2} \sin \alpha & + 2j \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} - b \sin^2 \frac{\alpha}{2} \\ + 2j \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} + j b \cos^2 \frac{\alpha}{2} & \cos \alpha - \frac{b}{2} \sin \alpha \end{bmatrix}$$

$$\begin{bmatrix} \therefore \cos 2\alpha = \cos^2 \alpha - \sin^2 \alpha \\ \Rightarrow \cos \alpha = \cos^2 \frac{\alpha}{2} - \sin^2 \frac{\alpha}{2} \\ \sin 2\alpha = 2 \sin \alpha \cos \alpha \\ \Rightarrow \sin \alpha = 2 \sin \frac{\alpha}{2} \cos \frac{\alpha}{2} \end{bmatrix}$$

$$= \begin{bmatrix} \cos \alpha - \frac{b}{2} \sin \alpha & j \sin \alpha + j b \left(\frac{1 - \cos \alpha}{2} \right) \\ j \sin \alpha + j b \left(\frac{1 + \cos \alpha}{2} \right) & \cos \alpha - \frac{b}{2} \sin \alpha \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} (\cos \alpha - \frac{b}{2} \sin \alpha) & j (\sin \alpha + \frac{b}{2} \cos \alpha - \frac{b}{2}) \\ j (\sin \alpha + \frac{b}{2} \cos \alpha + \frac{b}{2}) & (\cos \alpha - \frac{b}{2} \sin \alpha) \end{bmatrix} \quad (2)$$

Where $\alpha = kd$ and k is propagation constant. (Proved)

and $AD - BC = 1$, as required for reciprocal

n/w.

→ For a wave propagating in +z direction, we must have

$$\begin{aligned} V(z) &= V(0) \cdot e^{-\gamma z}, & \text{--- 3(a)} \\ I(z) &= I(0) \cdot e^{-\gamma z}, & \text{--- 3(b)} \end{aligned}$$

for a phase reference at $z=0$. Since the structure is infinitely long, the voltage and current at the n th terminals can differ from the voltage and current at the $(n+1)$ terminals only by the propagation factor, $e^{-\gamma d}$. Thus

$$V_{n+1} = V_n e^{-\gamma d} \quad \text{--- (a)}$$

$$I_{n+1} = I_n e^{-\gamma d} \quad \text{--- (b)}$$

Using eqⁿ (a) and (b) result in eqⁿ (1),

$$\begin{bmatrix} V_n \\ -I_n \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{n+1} e^{-\gamma d} \\ I_{n+1} e^{-\gamma d} \end{bmatrix}$$

$$\therefore V_n = V_{n+1} e^{-\gamma d} \quad \text{--- (c)}$$

$$I_n = I_{n+1} e^{-\gamma d} \quad \text{--- (d)}$$

From eqⁿ (1),

$$\begin{bmatrix} V_n \\ I_n \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix} \quad \text{--- (e)}$$

But from eqⁿ (c) and (d),

$$\begin{bmatrix} V_n \\ I_n \end{bmatrix} = \begin{bmatrix} V_{n+1} e^{-\gamma d} \\ I_{n+1} e^{-\gamma d} \end{bmatrix} \quad \text{--- (f)}$$

Equating both the results, we have

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix} = \begin{pmatrix} V_{n+1} \cdot e^{\gamma d} \\ I_{n+1} \cdot e^{\gamma d} \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix} = \begin{pmatrix} e^{\gamma d} & 0 \\ 0 & e^{\gamma d} \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix} - \begin{pmatrix} e^{\gamma d} & 0 \\ 0 & e^{\gamma d} \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix} = 0$$

$$\Rightarrow \begin{pmatrix} A - e^{\gamma d} & B \\ C & D - e^{\gamma d} \end{pmatrix} \begin{pmatrix} V_{n+1} \\ I_{n+1} \end{pmatrix} = 0 \quad \text{--- (5)}$$

For non-trivial soln, the determinants of the above matrix must vanish.

$$(A - e^{\gamma d})(D - e^{\gamma d}) - BC = 0$$

$$\Rightarrow AD - A \cdot e^{\gamma d} - D \cdot e^{\gamma d} + e^{2\gamma d} - BC = 0$$

$$\Rightarrow AD + e^{2\gamma d} - (A+D) \cdot e^{\gamma d} - BC = 0 \quad \text{--- (6)}$$

Since for a reciprocal NW, $AD - BC = 1$,

$$\Rightarrow 1 + e^{2\gamma d} - (A+D) \cdot e^{\gamma d} = 0$$

$$\Rightarrow 1 + e^{2\gamma d} = (A+D) \cdot e^{\gamma d}$$

$$\Rightarrow A+D = \frac{e^{-\gamma d} + e^{\gamma d}}{e^{\gamma d}} = 2 \cosh \gamma d$$

$$\Rightarrow \cosh \gamma d = \frac{A+D}{2} \quad \text{--- (7)}$$

From eqn (2),

$$A = \cos \theta - \frac{j}{2} \sin \theta$$

$$D = \cos \theta - \frac{j}{2} \sin \theta$$

$$\Rightarrow \frac{A+D}{2} = \cos \theta - \frac{j}{2} \sin \theta \quad \text{--- (8)}$$

Using eqn (8) in eqn (7), we have

$$\Rightarrow \cosh \gamma d = \cos \theta - \frac{j}{2} \sin \theta \quad \text{--- (9)}$$

Now if $\gamma = \alpha + j\beta$, we have, $\cosh \gamma d$

$$\cosh (\alpha d + j\beta d) = \cosh \alpha d \cdot \cos \beta d + j \sinh \alpha d \cdot \sin \beta d \quad \text{--- (10)}$$

Using eqn (9), in eqn (10), we have

$$\cos \theta - \frac{j}{2} \sin \theta = \cosh \alpha d \cos \beta d + j \sinh \alpha d \sin \beta d \quad \text{--- (11)}$$

Since left hand side of eqn (11), is purely real we must have either $\alpha = 0$ or $\beta = 0$ [$\because \sinh 0 = 0$]

Case-1 :- $\alpha = 0, \beta \neq 0$ $\alpha =$ Attenuation constant
 $\beta =$ Propagation constant

This case corresponds to a nonattenuating, propagating wave on the periodic structure, and defines the passband of the structure. Then eqn (11) reduces to,

$$\cos \beta d = \cos \theta - \frac{j}{2} \sin \theta \quad \text{--- (12)}$$

$\because \sinh \alpha d = 0$
 $\cos \alpha d = \cos 0 = 1$

Since $|\cos \beta a| \leq 1$

$\Rightarrow |\cos \alpha - \frac{b}{2} \sin \alpha| \leq 1$

[Note there are an infinite number of values of β that can satisfy eqn (12)]

Case - 2 :- $\alpha \neq 0, \beta = 0, \pi$

In this case the wave does not propagate, but is attenuated along the line; this defines the stop band structure. Because the line is lossless, power is not dissipated, but is reflected back to the i/p of the line.

So eqn (11), reduces to

$\cos \alpha d = |\cos \alpha - \frac{b}{2} \sin \alpha| \geq 1$

(10)

which has only one solution ($d > 0$) for positively travelling waves; ($d < 0$) applies for -vely travelling waves.

(11)

Thus, depending on the free and normalized susceptance values, the periodically loaded line will exhibit either pass band or stop bands, and so can be considered as a type of filter.

by real
- 0 = 0

instant
constant

along

duces

• $\sin \alpha d = 0$
 $\alpha d = 0$
 $\cos 0 = 1$

Note :- The voltage and current waves defined on eqn (3) & (9), similar to the elastic waves (Block waves) that propagates through periodic crystal lattice.

We can define characteristic impedance at the unit cell terminal as

$$Z_B = Z_0 \cdot \frac{V_{n1}}{I_{n1}}, \quad \text{--- (13)}$$

Since V_{n1} and I_{n1} in the above derivation are normalized quantities. This impedance is also referred to as Bloch impedance.

From eq (8),

$$\begin{bmatrix} A - e^{j\theta} & B \\ C & D - e^{j\theta} \end{bmatrix} \begin{bmatrix} V_{n1} \\ I_{n1} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow (A - e^{j\theta}) V_{n1} + B I_{n1} = 0 \quad \text{--- (14)}$$

$$\Rightarrow (A - e^{j\theta}) V_{n1} = -B I_{n1}$$

$$\Rightarrow \frac{V_{n1}}{I_{n1}} = \frac{-B}{(A - e^{j\theta})} \quad \text{--- (15)}$$

Putting eq (15), in eq (13), we have

$$Z_B = Z_0 \cdot \left(\frac{-B}{A - e^{j\theta}} \right) = \frac{-B Z_0}{A - e^{j\theta}} \quad \text{--- (16)}$$

Eq (8) is a quadratic eqn
 $ax^2 + bx + c = 0$

$$(e^{j\theta})^2 - (A+D) e^{j\theta} + (AD-BC) = 0$$

at

$$\Rightarrow e^{\gamma d} = \frac{(A+D) \pm \sqrt{(A+D)^2 - 4(AD-BC)}}{2} \quad (17)$$

relation

is

$$\Rightarrow e^{\gamma d} = \frac{(A+D) \pm \sqrt{(A+D)^2 - 4}}{2} \quad (17)$$

($\because AD-BC=1$
for reciprocal
n/w as
discussed after
eqn (6))

Then Block Impedance, Z_B
will be given by, [putting eqn (17) in eqn (6)]

$$Z_B = \frac{-B \cdot Z_0}{A - \left[\frac{(A+D) \pm \sqrt{(A+D)^2 - 4}}{2} \right]}$$

$$= \frac{-2B Z_0}{2A - A - D \pm \sqrt{(A+D)^2 - 4}}$$

$$= \frac{-2B Z_0}{(A-D) \pm \sqrt{(A+D)^2 - 4}}$$

\therefore Block Impedance has 2 solⁿ, given by

$$Z_B^{\pm} = \frac{-2B Z_0}{(A-D) \mp \sqrt{(A+D)^2 - 4}} \quad (18)$$

(18)

For symmetrical cell [As shown in fig 2],
we will always have $A=D$. In this case,

$$Z_B^{\pm} = \frac{\pm 2B Z_0}{\sqrt{A^2 - 1}} \quad (19)$$

The \pm solutions corresponds to the characteristic

Impedance for travelling and travelling waves, 369
 respectively. For symmetrical n/ws these impedances
 are the same except for the sign;

The characteristic impedance for a travelling
 wave turns out to be ve because
 we have defined I_n in fig 2, as always being
 in the travelling direction.

From eqn (2), we see that 'B' is
purely imaginary.

If $\alpha = 0, \beta \neq 0$ [pass band] then

$$\cosh \gamma d = \cos \alpha - \frac{1}{2} \sin \alpha \quad [\text{from eqn 1}]$$

$$\cosh \gamma d = A \quad [\text{from eqn 2}]$$

$$\therefore A = \cos \alpha - \frac{1}{2} \sin \alpha \leq 1$$

$$\therefore Z_{03} = \frac{\pm B Z_0}{\sqrt{A^2 - 1}} \quad \left[\begin{array}{l} \text{Since } B \text{ is imaginary} \\ \text{and } A < 1 \end{array} \right]$$

Z_{03} is purely real.

If $\alpha \neq 0, \beta = 0$ [stop band].

$$\cosh \gamma d = \cosh \alpha = A \geq 1$$

and B is imaginary.

Z_{03} is imaginary.

Filter design by image parameter method :-

365

The image parameter method of filter design involves the specification of passband and stopband characteristics for a cascade two-port n/w. [Similar to periodic structure, as discussed]

Disadvantage:- Although the method is relatively simple but has the disadvantage that an arbitrary freq response can't be incorporated into the design.

Image Impedances and transfer f^n for 2-port n/w :-

Consider the arbitrary 2-port n/w shown in fig 3, where the n/w is specified by its ABCD parameters.

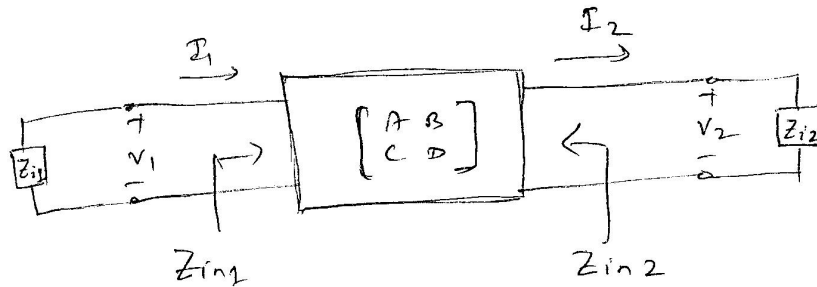


Fig 3:- A 2-port n/w terminated on its image impedances.

The image impedances, Z_{i1} and Z_{i2} are defined as,

Z_{i1} = i/p impedance at port 1 when port 2 is terminated with Z_{i2} .

Z_{i2} = i/p impedance at port 2 when port 1 is terminated with Z_{i1} .

Thus both ports are matched when terminated in their image impedances.

The port voltages and currents are related as

$$V_1 = AV_2 + BI_2, \quad \text{--- 2a(a)}$$

$$I_1 = CV_2 + DI_2, \quad \text{--- 2a(b)}$$

The input impedance at port 1, with port 2 terminated in Z_{i2} , is

$$Z_{in1} = \frac{V_1}{I_1} = \frac{AV_2 + BI_2}{CV_2 + DI_2} = \frac{A \cdot (Z_{i2} I_2) + BI_2}{C(Z_{i2} I_2) + DI_2}$$

$$\because Z_{i2} = \frac{V_2}{I_2} \Rightarrow V_2 = Z_{i2} I_2$$

$$\Rightarrow Z_{in1} = \frac{AZ_{i2} + B}{CZ_{i2} + D} \quad \text{--- (2)}$$

To find Z_{in} ,

$$\text{Inverse of } \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{\begin{bmatrix} D & -B \\ -C & A \end{bmatrix}}{AD - BC}$$

[To find inverse of 2×2 matrix short cut method is exchange the main diagonal elements, multiply \rightarrow in other 2 diagonal elements, Now divide the new matrix with determinant of original 2×2 matrix]

For a reciprocal n/w, $AD - BC = 1$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix}$$

$$\text{So } \begin{aligned} V_2 &= DV_1 - BI_1, & \text{--- 2a(c)} \\ I_2 &= -CV_1 + AI_1, & \text{--- 2a(d)} \end{aligned}$$

Then the impedance at port 2, with port 1 terminated with Z_{i1} , can be found as

$$Z_{in2} = \frac{-V_2}{I_2} = - \left[\frac{DV_1 - BI_1}{-CV_1 + AI_1} \right]$$

Since $Z_{i1} = -\frac{V_1}{I_1} \Rightarrow V_1 = -Z_{i1} I_1$

$$\therefore Z_{in2} = - \left[\frac{D(-Z_{i1} I_1) - BI_1}{-C(-Z_{i1} I_1) + AI_1} \right] = \frac{DZ_{i1} + B}{CZ_{i1} + A} \quad (23)$$

We desire that,
 $Z_{in1} = Z_{i1}$ and $Z_{in2} = Z_{i2}$

So Eqⁿ (21) & (23) becomes,

$$Z_{i1} = \frac{AZ_{i2} + B}{CZ_{i2} + D} \quad \text{and} \quad Z_{i2} = \frac{DZ_{i1} + B}{CZ_{i1} + A}$$

$$\Rightarrow Z_{i1} (CZ_{i2} + D) = AZ_{i2} + B \quad (24)$$

and $Z_{i2} (CZ_{i1} + A) = DZ_{i1} + B \quad (25)$

Solving eqⁿ (24) & (25),

$$Z_{i1} = \frac{AZ_{i2} + B}{CZ_{i2} + D} = \frac{A \cdot \left(\frac{DZ_{i1} + B}{CZ_{i1} + A} \right) + B}{C \cdot \left(\frac{DZ_{i1} + B}{CZ_{i1} + A} \right) + D}$$

$$\Rightarrow Z_{i1} = \frac{ADZ_{i1} + AB + BCZ_{i1} + AB}{CDZ_{i1} + BC + CDZ_{i1} + AD}$$

$$\Rightarrow CDZ_{i1}^2 + Z_{i1} \cancel{BC} + CDZ_{i1}^2 + ADZ_{i1} = ADZ_{i1} + AB + BCZ_{i1} + AB$$

$$\Rightarrow 2 CD Z_1^2 = 2 AB$$

$$\Rightarrow Z_1^2 = \frac{AB}{CD}$$

$$\Rightarrow \boxed{Z_{12} = \sqrt{\frac{AB}{CD}}} \quad \text{--- (26)}$$

$$\text{and } Z_{12} = \frac{D Z_{11} + B}{C Z_{11} + A}$$

$$= \frac{D \times \sqrt{\frac{AB}{CD}} + B}{C \times \sqrt{\frac{AB}{CD}} + A}$$

$$Z_{12} = \frac{D \sqrt{AB} + B \sqrt{CD}}{C \sqrt{AB} + A \sqrt{CD}}$$

$$= \frac{\sqrt{D} \sqrt{B} (\sqrt{D} \sqrt{A} + \sqrt{B} \sqrt{C})}{\sqrt{C} \sqrt{A} (\sqrt{C} \sqrt{B} + \sqrt{A} \sqrt{D})}$$

$$\Rightarrow \boxed{Z_{12} = \sqrt{\frac{BD}{AC}}} \quad \text{--- (27)}$$

$$\therefore \frac{Z_{11}}{Z_{12}} = \frac{\sqrt{AB}}{\sqrt{CD}} \times \frac{\sqrt{AC}}{\sqrt{BD}} = \frac{A \sqrt{BC}}{D \sqrt{BC}} = \frac{A}{D}$$

$$\Rightarrow Z_{11} = \frac{A}{D} Z_{12}$$

If the n/w is symmetric, A=D and

$$Z_{11} = Z_{12} \text{ as expected.}$$

Voltage Transfer function

Consider a 2-port n/w terminated on its image impedances, from eqn 22(a), we have (fig 4)

$$\begin{aligned}
 V_2 &= DV_1 - BI_1 = D(V_1 - I_1 Z_{i1}) \\
 &= \left(D - B \cdot \frac{I_1}{V_1}\right) V_1 \\
 V_2 &= \left(D - \frac{B}{Z_{i2}}\right) V_1 \quad \text{--- (28)} \\
 &\quad \left(\because Z_{i2} = \frac{V_1}{I_1}\right)
 \end{aligned}$$

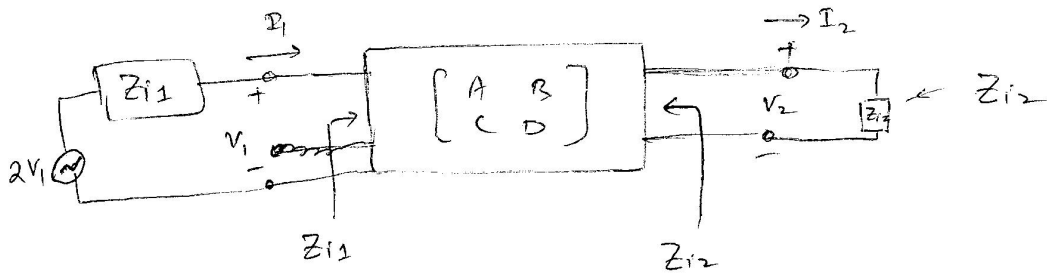


fig: - 4: - A 2-port n/w terminated on its image impedances and driven with a voltage generator

From eqn (28),

$$\frac{V_2}{V_1} = D - \frac{B}{Z_{i1}} = D - B \cdot \sqrt{\frac{CD}{AB}} \quad \text{[From eqn 26]}$$

$$\Rightarrow \frac{V_2}{V_1} = \sqrt{\frac{D}{A}} \left[\sqrt{AD} - \sqrt{BC} \right] \quad \text{--- (29)}$$

Similarly, from eqn 22 (b),

$$I_2 = I_1 \left(-C \frac{V_1}{I_1} + A \right) = I_1 (-C \cdot Z_{i1} + A)$$

$$\Rightarrow \frac{I_2}{I_1} = -C \cdot \sqrt{\frac{AB}{CD}} + A = \sqrt{\frac{A}{D}} \left[\sqrt{AD} - \sqrt{BC} \right] \quad \text{--- (30)}$$

The factor $\sqrt{\frac{D}{A}}$ occurs in reciprocal p.u. 370
 in (29) & (30) and so can be interpreted as transformer turns ratio.

The propagation factor for the n/w can be defined as,

$$e^{-\gamma} = \sqrt{AD} - \sqrt{BC}, \text{ where } \gamma = \alpha + j\beta \quad (31)$$


$$\text{Since, } e^{\gamma} = \frac{1}{\sqrt{AD} - \sqrt{BC}} = \frac{AD - BC}{\sqrt{AD} + \sqrt{BC}} \quad (32)$$

$$[\because AD - BC = (\sqrt{AD} + \sqrt{BC})(\sqrt{AD} - \sqrt{BC})]$$


$$\text{Cosh } \gamma = \frac{e^{\gamma} + e^{-\gamma}}{2} = \sqrt{AD} \quad (33)$$

Two important types of 2-port n/ws are T and π Circuits.

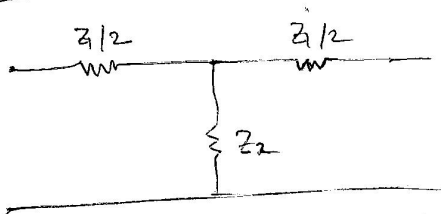Imp. parameters for T and π networks :- Table 1.1



T n/w fig 5:-

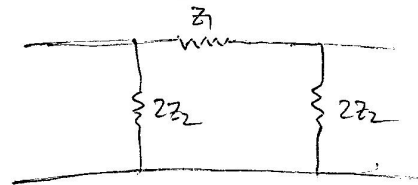

π n/w

ABCD Parameters

$$A = 1 + \frac{Z_1}{2Z_2}$$

$$B = Z_1 + \frac{Z_1^2}{4Z_2}$$

$$C = 1/Z_2$$

$$D = 1 + \frac{Z_1}{2Z_2}$$

Z-Parameters:

$$Z_{11} = Z_{22} = Z_2 + \frac{Z_1}{2}$$

ABCD Parameters

$$A = 1 + \frac{Z_1}{2Z_2}$$

$$B = Z_1$$

$$C = 1/Z_2 + \frac{Z_1}{4Z_2^2}$$

$$D = 1 + \frac{Z_1}{2Z_2}$$

Y-Parameters :-

$$Y_{11} = Y_{22} = \frac{1}{Z_1} + \frac{1}{2Z_2}$$

370

$$Z_{12} = Z_{21} = Z_2$$

$$Y_{12} = Y_{21} = \frac{1}{Z_1}$$

Image Impedance

Image Impedance

$$Z_{iT} = \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}}$$

$$Z_{i\pi} = \sqrt{Z_1 Z_2} / \sqrt{1 + \frac{Z_1}{4Z_2}} = \frac{Z_1 Z_2}{Z_{iT}}$$

Propagation Constant:-

Propagation Constant:-

$$e^{\gamma} = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} + \frac{Z_1^2}{4Z_2^2}}$$

$$e^{\gamma} = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} + \frac{Z_1^2}{4Z_2^2}}$$

defined as

(31)

√Bc (32)

Constant -k filter sections:-

Now we can develop low-pass and high-pass filter sections. Consider the 'T' n/w shown in figure 5.

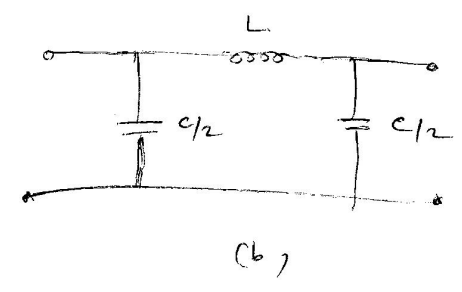
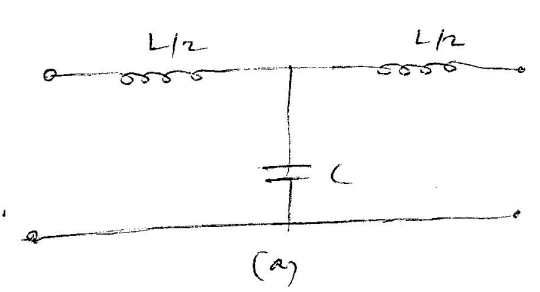


fig 6:- Low pass constant-k filter sections (a) T and (b) π

→ We can see that this is a low pass filter n/w because the series inductors and shunt capacitor tend to block high-freq signals while passing low-freq signals.

Compare fig 5 & 6

$$Z_1 = j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$

From Table 1:-

$$\text{and } Z_{iT} = \sqrt{Z_1 \cdot Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}} = \sqrt{j\omega L \cdot \frac{1}{j\omega C}} \sqrt{1 + \frac{j\omega L \times j\omega C}{4}}$$

$$Z_{iT} = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2 LC}{4}} \quad \text{--- (34)}$$

1/2Z2

To find cutoff freq

$$1 - \frac{\omega^2 LC}{4} = 0$$

$$\Rightarrow 1 = \frac{\omega_c^2 LC}{4}$$

$$\Rightarrow \omega_c^2 = \frac{4}{LC}$$

$$\Rightarrow \boxed{\omega_c = \frac{2}{\sqrt{LC}}} \quad \text{--- (35)}$$

a nominal
Defining Characteristic Impedance

$$R_0 = \sqrt{\frac{L}{C}} = k, \quad \text{where } k \text{ is a constant,}$$

then $Z_{IT} = R_0 \sqrt{1 - \frac{\omega^2}{\omega_c^2}} \quad \text{--- (36)} \quad \because \omega_c = \frac{2}{\sqrt{LC}}$

$$\therefore \boxed{Z_{IT} = R_0}, \quad \text{for } \omega = 0$$

$$\rightarrow \text{Propagation factor, } e^{\gamma} = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} + \frac{Z_1^2}{4Z_2^2}}$$

$$\therefore e^{\gamma} = 1 + \frac{j\omega L (j\omega C)}{2} + \sqrt{\frac{j\omega L (j\omega C)}{1} + \frac{j^2 \omega^2 LC}{4} (j^2 \omega^2 LC)}$$

$$\Rightarrow e^{\gamma} = 1 - \frac{\omega^2 LC}{2} + \sqrt{-\omega^2 LC + \frac{\omega^4 L^2 C^2}{4}}$$

$$= 1 - \frac{2\omega^2}{\left(\frac{4}{LC}\right)} + \sqrt{\omega^2 LC} \sqrt{\frac{\omega^2 LC}{4} - 1}$$

$$= 1 - \frac{2\omega^2}{\omega_c^2} + 2 \frac{\omega}{\left(\frac{2}{\sqrt{LC}}\right)} \sqrt{\frac{\omega^2}{\left(\frac{4}{LC}\right)} - 1}$$

$$\Rightarrow e^{\gamma} = 1 - \frac{2\omega^2}{\omega_c^2} + \frac{2\omega}{\omega_c} \sqrt{\frac{\omega^2}{\omega_c^2} - 1}$$

$$\therefore e^{\gamma} = 1 - \frac{2\omega^2}{\omega_c^2} + \frac{2\omega}{\omega_c} \sqrt{\frac{\omega^2}{\omega_c^2} - 1} \quad (37)$$

Now consider 2 freq regions:-

1) For $\omega < \omega_c$: This is the passband of the filter section. Eqⁿ (36) shows that Z_{IT} is real, and eqⁿ (37) shows that e^{γ} is imaginary. (since $\frac{\omega}{\omega_c} - 1$ is -ve)

$\frac{2}{\sqrt{LC}}$

2) For $\omega > \omega_c$:

This is the stopband of the filter. Eqⁿ (36) shows Z_{IT} is imaginary and eqⁿ (37) shows that e^{γ} is real.

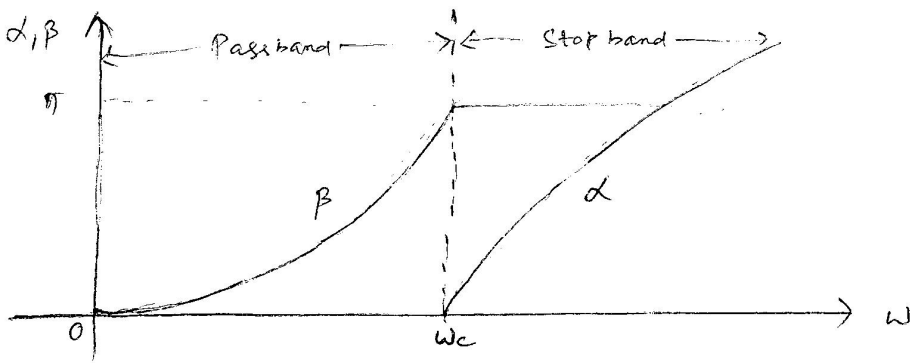


fig 7:- Typical Passband and Stopband Characteristics of low-pass Constant-K section

Typical phase and attenuation constants are sketched in fig 7. We observe that the attenuation, α , is zero or relatively small near the cutoff freq

and $L \rightarrow \infty$ as $\omega \rightarrow \infty$,

This type of filter is known as a constant-k low pass prototype. There are only two parameters to choose (L and C), which are determined by ω_c , the cutoff freq and R_0 , the image impedance at zero freq.

→ The above results are valid only when the filter section is terminated on its image impedance at both ports.

→ This is a major weakness of the design, because the image impedance is a function of freq, which is not likely to match a given source or load impedance.

→ This disadvantage can be eliminated with modified (m-derived) filter section.

→ For low pass π n/w $Z_1 = j\omega L, Z_2 = \frac{1}{j\omega C}$

So propagation factor is same as that of 'T' n/w.

Also the ω_c and R_0 are same as that of 'T' n/w.

→ At $\omega = 0, Z_{iT} = Z_{i\pi} = R_0$ where Z_{iT} is the image impedance of low-pass - π n/w, but Z_{iT} and $Z_{i\pi}$ are generally not equal at other frequencies.

→ High pass const-K section are shown in fig 8. The posⁿ of inductor and capacitor are reversed from that of low-pass prototype.

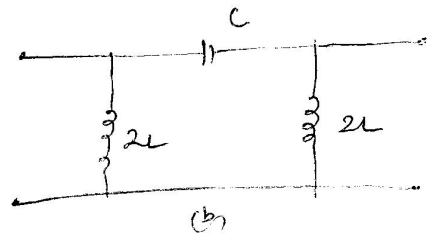
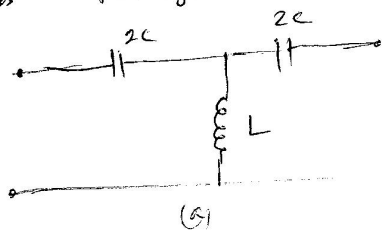


Fig 8 :- High Pass Const- x filter section in T and π form (a) T -section (b) π -section

The design eqⁿ can be shown to be

$$R_0 = \sqrt{\frac{L}{C}}, \quad \omega_c = \frac{1}{2\sqrt{LC}}$$

Note: R_0 is same as that Low-pass type

but $\omega_c = \frac{2}{\sqrt{LC}}$ in low pass type.

Filter Design by the Insertion loss method

→ The perfect (ideal) filter would have zero insertion loss in the passband, infinite attenuation in the stopband and a linear phase response (to avoid signal distortion) in the passband.

→ The image parameter method may yield a usable filter response, but there is no clear-cut way to improve the design, but the insertion loss method, allows a high degree of control over the passband and stopband amplitude and phase characteristics, with a systematic way to synthesize a desired response.

→ e.g

Minim insertion loss method - Binomial response ~~is~~ used.

Chebyshev response would satisfy a requirement for sharp cutoff.

Linear phase filter → for better phase response.

→ In all cases, insertion loss method allows filter performance to be improved in a straight forward manner, at the expense of higher order filter. [order of filter = Number of reactive components]

Characterization by Power loss ratio :-

370

In the insertion loss method a filter response is defined by its insertion loss, or power loss ratio, P_{LR} :

$$P_{LR} = \frac{\text{Power Available from source}}{\text{Power delivered to load}} = \frac{P_{inc}}{P_{refl}} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

$$P_{LR} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

(38)

 $\Gamma(\omega)$ = Reflection Coefficient

The insertion loss (IL) in dB,

$$IL = 10 \log P_{LR} \quad \text{--- (39)}$$

→ But we know that $|\Gamma(\omega)|^2$ is an even function of ω [Derivation given in Pozar Book sec-4.1], therefore it can be expressed as polynomial in ω^2 . Thus, we can write

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)} \quad \text{--- (40)}$$

where M & N are real polynomials in ω^2 .

∴ Using eqⁿ (40) in eqⁿ (38), we have

$$P_{LR} = \frac{1}{1 - \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}} = \frac{M(\omega^2) + N(\omega^2)}{M(\omega^2) + N(\omega^2) - M(\omega^2)}$$

$$\Rightarrow P_{LR} = 1 + \frac{N(\omega^2)}{M(\omega^2)} \quad \text{--- (41)}$$

Thus, for a filter to be physically realizable, its power

370 loss ratio must be of the form in eqn (41), 379

Some practical filter responses:

Maximally flat

The characteristic is also called binomial or Butterworth response, and is optimum in the sense that it provides the flattest possible passband response for a given filter complexity or order.

For a low pass filter, it is specified by

$$P_{LR} = 1 + K^2 \left(\frac{\omega}{\omega_c}\right)^{2N} \quad \text{--- (42)}$$

where N is the order of the filter and ω_c is the cutoff freq. The passband extends from $\omega=0$ to $\omega=\omega_c$. At the band edge the power loss ratio is $1+K^2$.

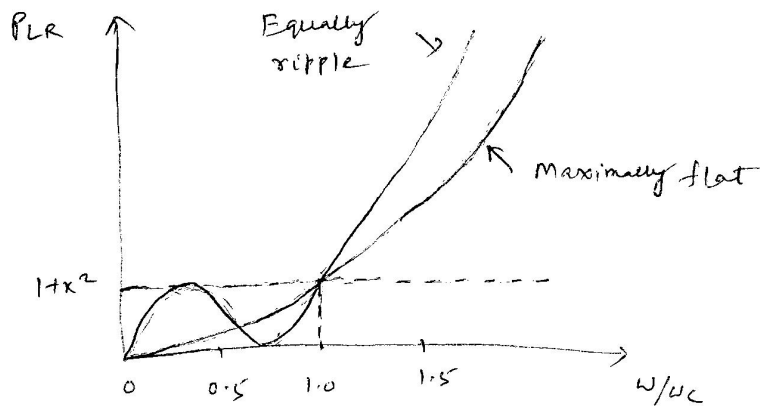


Fig: - 9:- Maximally flat and equal-ripple low-pass filter responses ($N=3$)

→ For -3dB point, $P_{LR} = 2$ (\because Power delivered to load = $\frac{1}{2}$ of power incident)

to power

$$\begin{aligned} \Rightarrow 1 + K^2 &= 2 \\ \Rightarrow K &= 1 \end{aligned}$$

For $\omega > \omega_c$, the attenuation increases monotonically with freq, [shown in fig 9].

For $\omega \gg \omega_c$, $PLR \approx K^2 \left(\frac{\omega}{\omega_c}\right)^{2N}$, which shows that insertion loss increases at the rate of $20N$ dB/decade. (42a)

Equal ripple:-

If a Chebyshev Polynomial is used to specify the insertion loss of an N-order low-pass filter as

$$PLR = 1 + K^2 T_N^2 \left(\frac{\omega}{\omega_c}\right) \quad (43)$$

then a sharper cutoff ^{with} result, although the passband response will have ripples of amplitude $(1+K^2)$, [fig 9],

Since $T_N(x)$ oscillates betⁿ ± 1 for $|x| \leq 1$. Thus, K^2 determines the passband ripple level. For larger x , $T_N(x) \approx \frac{1}{2} (2x)^N$, so for $\omega \gg \omega_c$

the insertion loss becomes,

$$PLR \approx \frac{K^2}{4} \left(\frac{2\omega}{\omega_c}\right)^{2N} \quad (44)$$

$\left. \begin{aligned} T_N(x) &= T_N\left(\frac{\omega}{\omega_c}\right) \\ x &= \frac{\omega}{\omega_c} \\ 2x &= \frac{2\omega}{\omega_c} \end{aligned} \right\}$

which also increases at the rate of $20N$ dB/decade. But the insertion loss for Chebyshev case is $\left(\frac{2^{2N}}{4}\right)$ greater than the binomial response, at any given freq $\omega \gg \omega_c$.
 [Comparing ^{Eq} 42(a) & (44)]

(a) The low-pass filter prototypes, we have studied, we've normalized designs having a source impedance of $R_s = 1 \Omega$ and a cutoff freq $\omega_c = 1$. Now we show how these designs can be scaled in terms of impedance and freq and converted to give high-pass, bandpass, or band-stop characteristics.

Impedance and freq scaling:-

Impedance Scaling:-

In prototype design, the source and load resistances are unity. A source resistance of R_0 can be obtained by multiplying the impedances of the prototype design by R_0 .

→ If we let primes (') denotes impedance scaled quantities, we have the new filter component values given by

$$L' = R_0 \cdot L \quad \text{--- (45)}$$

$$C' = \frac{C}{R_0} \quad \text{--- (46)}$$

$$R_s' = R_0 \quad \text{--- (47)}$$

$$R_L' = R_0 \cdot R_L \quad \text{--- (48)}$$

Where $L, C,$ and R_L are the component values for the original prototype

Frequency Scaling for low-pass filter:-

To change the cutoff freq of a low-pass prototype from unity

to ω_c requires that we scale the freq dependence 380 of filter by the factor $\frac{1}{\omega_c}$, which is accomplished by replacing ω by $\frac{\omega}{\omega_c}$:

$$\omega \leftarrow \frac{\omega}{\omega_c} \quad \text{--- (49)}$$

Then new power loss ratio will be

$$P'_{LR}(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right) \quad \text{--- (50)}$$

Where ω_c is the new cutoff freq; cutoff occurs when $\frac{\omega}{\omega_c} = 1$ or $\omega = \omega_c$. This transformation can be viewed as stretching or expansion of the original passband, as shown in fig 10 a, b.

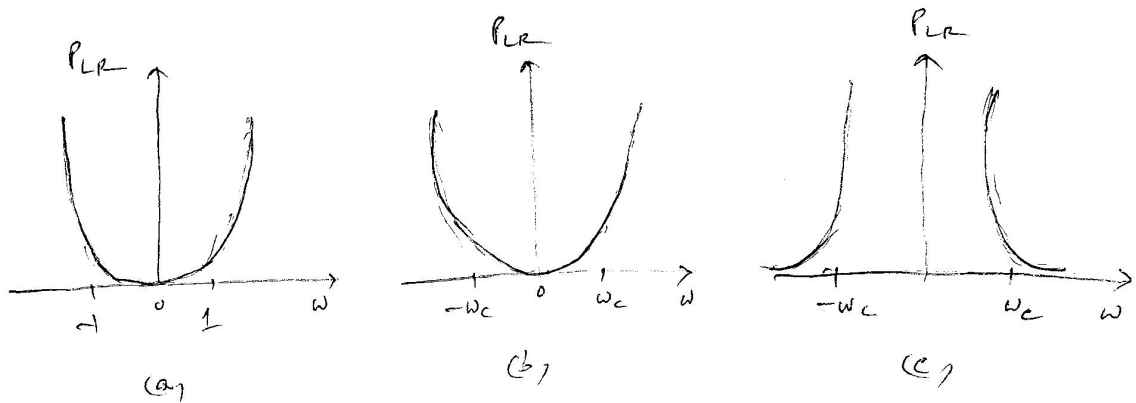


Fig 10:- Frequency scaling for low-pass filters and transformation to a high-pass response. (a) Low-pass filter prototype response for $\omega_c = 1$ (b) Frequency scaling for low-pass response (c) Transformation to high-pass response

→ The new element values are determined by applying the substitution of eq (49) to the series reactances, $j\omega L_k$ and shunt susceptance, $j\omega C_k$, of the prototype filter.

Thus,

$$jX_k = j \frac{\omega}{\omega_c} L_k = j \omega L'_k$$

$$jB_k = j \frac{\omega}{\omega_c} C_k = j \omega C'_k$$

which shows that the new element values are given by,

$$L'_k = \frac{L_k}{\omega_c} \quad \text{--- (51)}$$

$$C'_k = \frac{C_k}{\omega_c} \quad \text{--- (52)}$$

When both impedance & freq scaling are required, the results of (51) & (52) can be combined with (45) & (46), to give

$$L'_k = \frac{R_0 L_k}{\omega_c} \quad \text{--- (53)}$$

$$C'_k = \frac{C_k}{\omega_c R_0} \quad \text{--- (54)}$$

Low-pass to high-pass transformation:-

The freq substitution where

$$\omega \leftarrow -\frac{\omega_c}{\omega} \quad \text{--- (55)}$$

can be used to convert a low-pass response to a high pass response, shown in fig 10(c).

The substitution maps $\omega=0$ to $\omega=\pm\infty$ and vice versa;

Cut off occurs when $\omega = \pm \omega_c$.

The -ve sign is needed to convert inductors (and capacitor) to realizable capacitors (and inductors).

Applying eqⁿ (55) to series reactances, $j\omega L_k$ and shunt capacitances, $j\omega C_k$, of the prototype filter gives,

$$jX_k = j \left(-\frac{\omega_c}{\omega}\right) L_k = \frac{j}{j\omega C'_k} \quad \text{--- (56)}$$

$$jB_k = -j \frac{\omega_c}{\omega}, C_k = \frac{1}{j\omega L_k} \quad (57)$$

which shows that series inductors L_k must be replaced with capacitors C_k and shunt capacitor must be replaced by inductor L_k .

From eqⁿ (56) & (57), we have

$$C_k' = \frac{1}{\omega_c L_k} \quad (58)$$

$$L_k' = \frac{1}{\omega_c C_k} \quad (59)$$

Impedance scaling can be included by using,

$$C_k' = \frac{1}{R_0 \omega_c L_k} \quad (60)$$

$$L_k' = \frac{R_0}{\omega_c C_k} \quad (61)$$


Bandpass & Band Stop transformations:-

→ Low pass prototype filter designs can also be transformed to have the bandpass or bandstop response illustrated in fig 11. If ω_1 & ω_2 denote the edges of the passband, then a bandpass response can be obtained using the following


freq substitution:

$$\omega \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \quad (62)$$

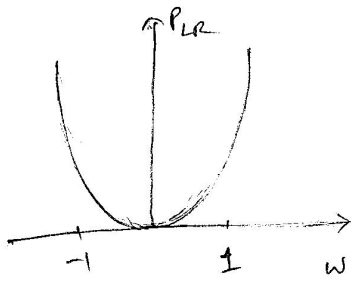
where $\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$ is the fractional BW of the passband. (63)



(a)

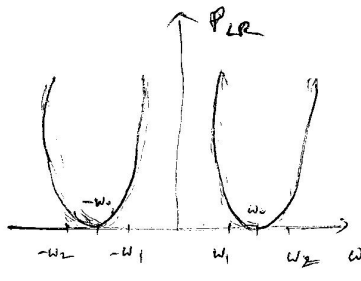

(b)

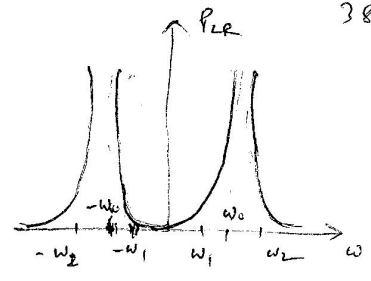

(c)

Fig 11:- Bandpass and band stop freq transformation (a)

Low-pass filter prototype response for $\omega_c = 1$

(b) Transformation to bandpass response (c) Transformation to band stop response.

→ The center freq, ω_0 , could be chosen as the arithmetic mean of ω_1 and ω_2 , but the eqⁿ are simpler if ω_0 is chosen as the geometric mean

$$\omega_0 = \sqrt{\omega_1 \omega_2} \quad \text{--- (64)}$$

Then the transformation of eqⁿ (62), maps the bandpass characteristics of figure 11 (b) to the low-pass response of fig 11 (a) as follows

$$\text{When } \omega = \omega_0, \quad \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = 0$$

$$\text{When } \omega = \omega_1, \quad \frac{1}{\Delta} \left(\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1} \right) = \frac{1}{\Delta} \left(\frac{\omega_1^2 - \omega_0^2}{\omega_0 \omega_1} \right) = -1;$$

$$\text{When } \omega = \omega_2, \quad \frac{1}{\Delta} \left(\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} \right) = \frac{1}{\Delta} \left(\frac{\omega_2^2 - \omega_0^2}{\omega_0 \omega_2} \right) = 1;$$

→ The new filter elements are determined by using eqⁿ (62), in the expression for series reactances and shunt capacitances. Thus

$\frac{\omega_0}{\omega}$ (62)

BW and

$$jX_k = j \cdot \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) L_k = \frac{j\omega L_k}{\Delta\omega_0} - \frac{j\omega_0 L_k}{\Delta\omega}$$

$$= j\omega L_k' - j \frac{1}{\omega C_k'}$$

which shows that series inductor, L_k , is transformed to a series LC cut with

element values, $L_k' = \frac{L_k}{\Delta\omega_0}$ — (65)

$$C_k' = \frac{\Delta}{\omega_0 L_k}$$
 — (66)

Similarly,

$$jB_k = j \cdot \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) C_k = \frac{j\omega C_k}{\Delta\omega_0} - \frac{j\omega_0 C_k}{\Delta\omega}$$

$$= j\omega C_k' - j \frac{1}{\omega L_k'}$$

which shows that a shunt capacitor, C_k , is transformed to a shunt LC cut with element values

$$L_k' = \frac{\Delta}{\omega_0 C_k}$$
 — (67)

$$C_k' = \frac{C_k}{\Delta \cdot \omega_0}$$
 — (68)

→ The low-pass filter elements are thus converted to series resonant cuts (low impedance at resonance) on series arms and to parallel resonant cuts (high impedance at resonance) on the shunt arms.

→ But both series & parallel resonator elements have a resonant freq of ω_0 .

→ Inverse transformation can be used to obtain

a band stop response, Thus,

$$\omega \leftarrow \Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1},$$

Δ & ω_0 are same as defined in (63) & (67)

Then series inductor of low-pass prototype are converted to parallel LC ckt's having element values given by

$$L'_k = \frac{\Delta L_k}{\omega_0} \quad \text{--- (69)}$$

$$C'_k = \frac{1}{\omega_0 \Delta L_k} \quad \text{--- (70)}$$


The shunt capacitor of the low-pass prototype is converted to series LC ckt having elements given by

$$L_k^1 = \frac{1}{\omega_0 \Delta C_k} \quad \text{--- (71)}$$



$$C_k^1 = \frac{\Delta C_k}{\omega_0} \quad \text{--- (72)}$$

Summary



Low-pass

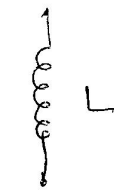



High pass

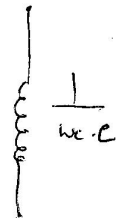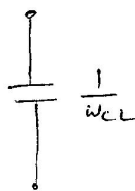

Band pass

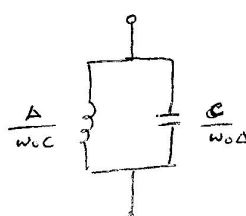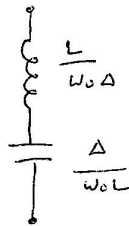

Band stop

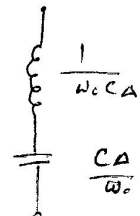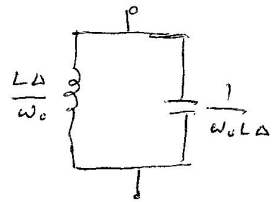

u
me)

Filter Implementation :-

[discussed earlier]

The lumped-element filter design, generally works well at low frequencies, but two problems arise at microwave frequencies.

First, lumped elements such as inductor and capacitors are generally available only for limited range of values and are difficult to implement at microwave frequencies, ~~in addition~~ but approximated with distributed components.

In addition, at microwave frequencies the distance betⁿ filter components is not negligible.

[But in circuit theory it is negligible].

→ Richard's transformation is used to convert lumped elements to Transmission line sections.

• While Kuroda's transformation identities can be used to separate filter elements by using transmission line sections. Because such additional T.L sections don't affect filter response, this type of design is called redundant filter synthesis.

Richard's Transformation :-

The transformation, $\Omega = \tan \beta z = \tan \left(\frac{\omega l}{v_p} \right)$ (Capitⁿ omega) $\left[\because \beta = \frac{\omega}{v_p} \right]$

maps the 'w' plane to the 'z' plane, which repeats with a period of $\omega l / v_p = 2\pi$.

This transformation was introduced by P. Richard to synthesize an LC network using open- and short circuited transmission lines. Thus, if we replace the freq variable 'w' with 'z', the reactance

of an inductor can be written as

$$jX_L = j\omega L = jL \tan \beta l \quad \text{--- (74)}$$

and the susceptance of a capacitor can be written as

$$jB_C = j\omega C = jC \tan \beta l \quad \text{--- (75)}$$

These results indicate that an inductor can be replaced with short-circuited stub of length ' βl ' and characteristic impedance L , while a capacitor can be replaced with an open-circuited stub of length ' βl ' and characteristic impedance $\frac{1}{C}$.

Note :- Recall in T.L, $Z_{in} = jZ_0 \tan \beta l$ for short-circuited line here it is $jL \tan \beta l$.
 $\therefore Z_0 = L$

→ Cutoff occurs at unity freq for low-pass filter prototype; to obtain the same cutoff freq for Richards-transformed filter, eqⁿ (73) shows that

$$\omega = 1 = \tan \beta l \quad \text{--- (76)}$$

which gives a stub length of $l = \frac{\lambda}{8}$, where λ

$$\left[\because \tan \beta l = 1 \Rightarrow \frac{2\pi}{\lambda} \cdot l = \frac{\pi}{4} \Rightarrow l = \frac{\lambda}{8} \right]$$

is the wavelength of the line at the cutoff freq, ω_c .

→ At ω freq $\omega = 2\omega_c$, the lines will be $\frac{\lambda}{4}$ long,

→ and an attenuation pole will occur

→ At freq away from ω_c the impedances of the stubs will no longer match the original lumped element impedances and the filter response will differ

from the desired prototype response. Also, the response will be periodic in freq; repeating every $4\omega_c$.

$$\left(\because 4\omega_c = 4\pi \frac{\lambda}{8\lambda} = \frac{\lambda}{2} \right)$$
 In each $\frac{\lambda}{2}$ (in Smith chart) repetition occurs. (repetition occurs) after $\frac{\lambda}{2}$.

→ In principle, then the inductor and capacitors of lumped-element filter design can be replaced with short-circuited and open-circuited stubs as shown in figure 12.

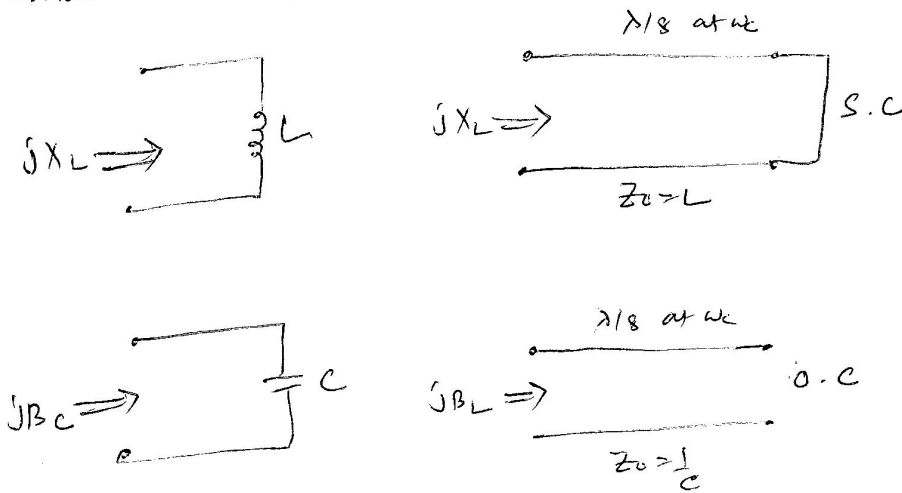


fig 12 - Richard's transformation (a) For an inductor to a short-circuited stub (b) For a capacitor to an open-circuited stub.

→ Since the lengths of all the stubs are same ($\frac{\lambda}{8}$ at ω_c), these lines are called commensurate lines.

Kuroda's Identities:-

The four Kuroda's identities are ~~use~~ redundant


transmission line section to achieve a more practical microwave filter implementation by performing any of the following operations.

- Physically separate transmission line stubs
- Transform series stubs into shunt stubs or vice versa.
- Change impractical characteristic impedances into more realizable ones.

The additional transmission line sections are called unit elements and are $\frac{\lambda}{8}$ long at ω_c ; the unit elements are thus commensurate with stubs used to implement the inductors and capacitors of the prototype design.



The four identities are illustrated in table 2,

Table 2:- The 4 Kuroda identities $[n^2 = 1 + \frac{Z_2}{Z_1}]$.

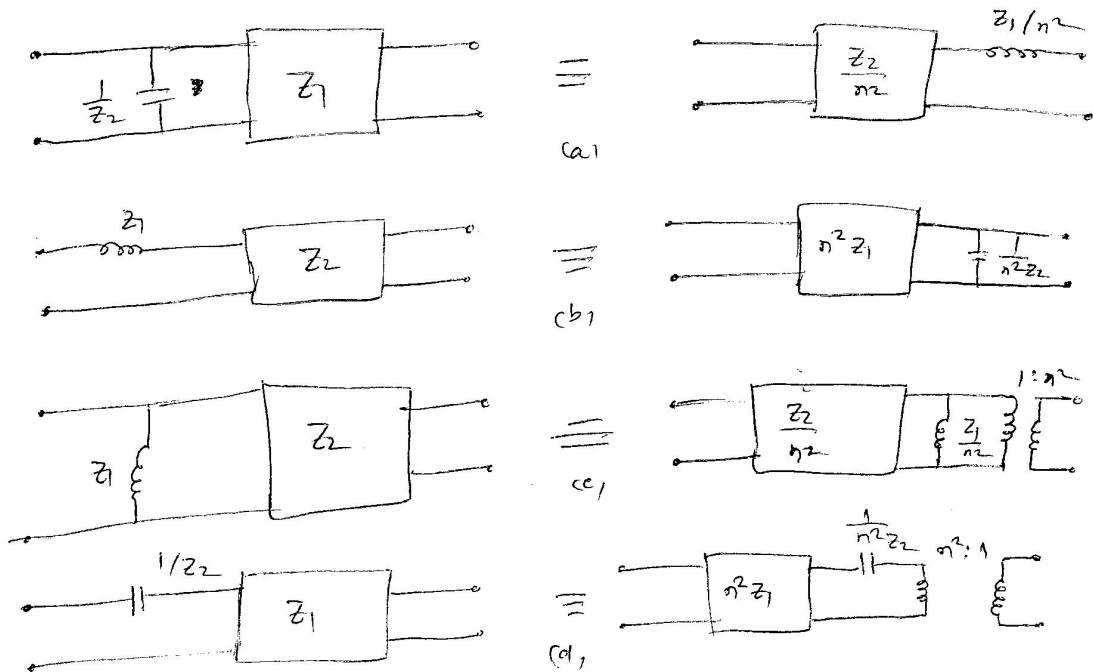

Here each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\frac{\lambda}{8}$ at ω_c). The inductor and capacitors represent short-circuit and open-circuit stubs, respectively.

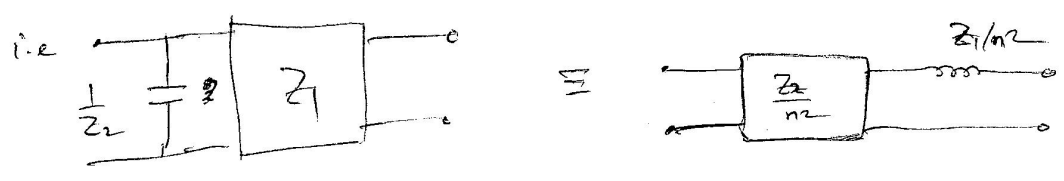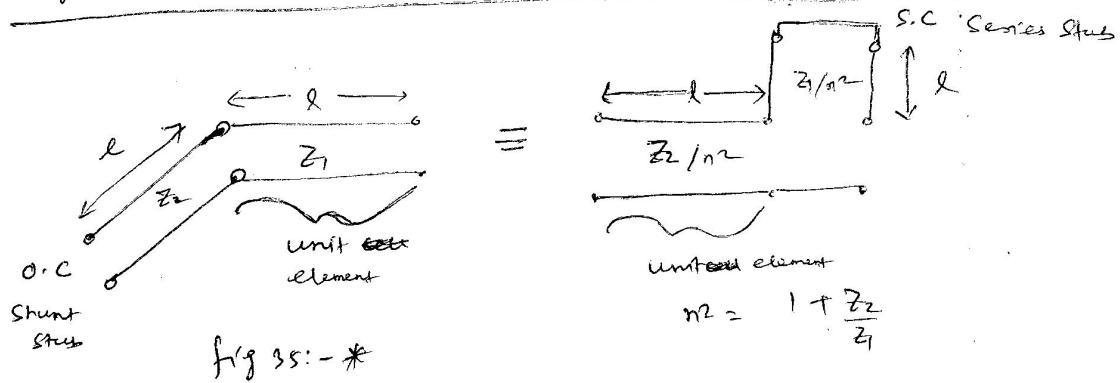* Equivalent Ckt of Kerndal's Identity (a)



Coupled line filters 2 -

→ The parallel coupled T.L can also be used to construct many types of filters. Fabrication of multisection band pass or band stop coupled line filters is particularly easy in microstrip or stripline form.

⇒ Filter Properties of a Coupled line Section :-

A parallel coupled line section is shown in fig 36 (a), with port voltage and current definitions. We will derive the open-circuit impedance matrix for this 4-port n/w by considering the superposⁿ of even and odd mode excitations which

390 are shown on fig 36(b) - Thus the current 391
 sources i_1 and i_3 drive the line in the even mode, while
 i_2 and i_4 drive the line in odd mode. By superposition,
 we see that the total port currents, I_1 , can be expressed
 in terms of the even and odd modes current as

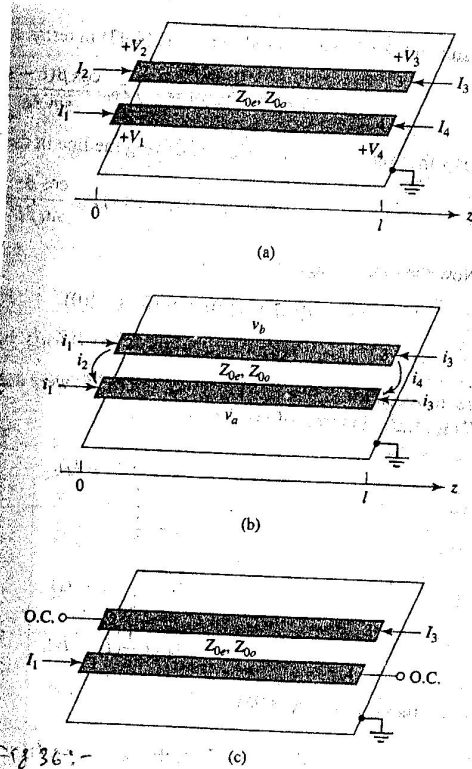


Fig 36: - (c)
 Definitions pertaining to a coupled line filter section. (a) A parallel coupled line section with port voltage and current definitions. (b) A parallel coupled line section with even- and odd-mode current sources. (c) A two-port coupled line section having a bandpass response.

$$I_1 = i_1 + i_2 \quad \text{--- 77(a)}$$

$$I_2 = i_1 - i_2 \quad \text{--- 77(b)}$$

$$I_3 = i_3 - i_4 \quad \text{--- 77(c)}$$

$$I_4 = i_3 + i_4 \quad \text{--- 77(d)}$$

(a),
 For Z_{0e} Consider the line as being driven on the even mode by the i_1 current sources. If the other ports are open circuited, the impedances seen at port 1 or 2 is

$$Z_{in}^e = -j Z_{0e} \cot \beta l \quad (78) \quad \left[\begin{array}{l} \text{Recall in} \\ \text{open circuit line } \end{array} \right] \quad 392$$

$$Z_{in} = -j Z_{0e} \cot \beta l$$

The voltage on either conductor can be expressed as

$$V_a^1(z) = V_b^1(z) = V_e^+ \left[\frac{-j\beta(z-l)}{e} + \frac{j\beta(z-l)}{e} \right]$$

$$= 2 V_e^+ \cos \beta (l-z) \quad (79)$$

So the voltage at port 1 or 2 is

$$V_a^1(0) = V_b^1(0) = 2 V_e^+ \cos \beta l = i_1 Z_{in}^e$$

This result and (78) can be used to rewrite (79)

in terms of i_1 as

$$V_a^1(z) = V_b^1(z) = -j Z_{0e} \frac{\cos \beta (l-z)}{\sin \beta l} i_1 \quad (80)$$

Similarly, the voltages due to current sources i_3 driving the line on the even mode are

$$V_a^3(z) = V_b^3(z) = -j Z_{0e} \frac{\cos \beta z}{\sin \beta l} i_3 \quad (81)$$

Now consider the line as being driven on the odd mode by current i_2 . If the other ports are open circuited, the impedance seen at port 1 or 2

$$Z_{in}^o = -j Z_{0o} \cot \beta l \quad (82) \quad \begin{array}{l} 0 \rightarrow \text{Zero} \\ 0 \rightarrow \text{odd} \end{array}$$

The voltage on either conductor can be expressed as

$$V_a^2(z) = -V_b^2(z) = V_o^+ \left[\frac{-j\beta(z-l)}{e} + \frac{j\beta(z-l)}{e} \right]$$

$$= 2 V_o^+ \cos \beta (l-z) \quad (83)$$

Then the voltage at port 1 or port 2 is

$$V_a^2(z) = -V_b^2(z) = 2V_0^+ \cos \beta z = i_2 Z_0 \quad (82)$$

The result and eqⁿ (82) can be used to rewrite eqⁿ (81)

in terms of i_2 as

$$V_a^2(z) = -V_b^2(z) = -j Z_0 \frac{\cos \beta (l-z)}{\sin \beta l} i_2 \quad (84)$$

Similarly, the voltages due to current i_4 driving the line in odd mode are

$$V_a^4(z) = -V_b^4(z) = -j Z_0 \frac{\cos \beta z}{\sin \beta l} i_4 \quad (85)$$

Now the total voltage at port 1 is

$$\begin{aligned} V_1 &= V_a^1(z) + V_b^2(z) + V_a^3(z) + V_a^4(z) \\ &= -j (Z_0 i_1 + Z_0 i_2) \cot \theta - j (Z_0 i_3 + Z_0 i_4) \csc \theta \end{aligned} \quad (86)$$

where the the result of (80), (81), (84), and (85) were used,

and $\theta = \beta l$. Next, we solve eqⁿ (77) for i_j

in terms of I_s :

$$I_1 = \frac{1}{2} (I_1 + I_2) \quad (87a)$$

$$I_2 = \frac{1}{2} (I_1 - I_2) \quad (87b)$$

$$I_3 = \frac{1}{2} (I_3 + I_4) \quad (87c)$$

$$I_4 = \frac{1}{2} (I_3 - I_4) \quad (87d)$$

and use these results in eqⁿ (86), we have

$$V_1 = -\frac{j}{2} (Z_{0e} I_1 + Z_{0e} I_2 + Z_{0o} I_1 - Z_{0o} I_2) \cot \theta$$

$$- \frac{j}{2} (Z_{0e} I_3 + Z_{0e} I_4 + Z_{0o} I_3 - Z_{0o} I_4) \operatorname{cosec} \theta \quad (88)$$

This result yields the top row of the open-circuit impedance matrix $[Z]$ that describes the coupled line section. From symmetry, all other matrix elements can be found once the first row is known.

The matrix elements are then

$$Z_{11} = Z_{22} = Z_{33} = Z_{44} = -\frac{j}{2} (Z_{0e} + Z_{0o}) \cot \theta \quad (89a)$$

$$Z_{12} = Z_{21} = Z_{34} = Z_{43} = -\frac{j}{2} (Z_{0e} - Z_{0o}) \cot \theta \quad (89b)$$

$$Z_{13} = Z_{31} = Z_{24} = Z_{42} = -\frac{j}{2} (Z_{0e} - Z_{0o}) \operatorname{cosec} \theta \quad (89c)$$

$$Z_{14} = Z_{41} = Z_{23} = Z_{32} = -\frac{j}{2} (Z_{0e} + Z_{0o}) \operatorname{cosec} \theta \quad (89d)$$

→ A 2-port n/w can be formed from the coupled line section by terminating 2 of the 4-ports in either open or short ckt's; there are 16 possible combinations as, illustrated in

table 3:

→ As indicated in this table, the various ckt's have different freq responses, including low-pass, bandpass, all pass and all stop. For bandpass filters, ~~the~~ fig 36(c) can be used, as open ckt are easier to fabricate than are short ckt's. In this case, $I_2 = I_4 = 0$, so the

TABLE 8.3 Ten Canonical Coupled Line Circuits

88

cut

- 89(a)

89(b)

89(c)

89(d)

Circuit	Image Impedance	Response
	$Z_{11} = \frac{2Z_{0c}Z_{0o} \cos \theta}{\sqrt{(Z_{0c} + Z_{0o})^2 \cos^2 \theta - (Z_{0c} - Z_{0o})^2}}$ $Z_{12} = \frac{Z_{0c}Z_{0o}}{Z_{11}}$	
	$Z_{11} = \frac{2Z_{0c}Z_{0o} \sin \theta}{\sqrt{(Z_{0c} - Z_{0o})^2 - (Z_{0c} + Z_{0o})^2 \cos^2 \theta}}$	
	$Z_{11} = \frac{\sqrt{(Z_{0c} - Z_{0o})^2 - (Z_{0c} + Z_{0o})^2 \cos^2 \theta}}{2 \sin \theta}$	
	$Z_{11} = \frac{\sqrt{Z_{0c}Z_{0o}} \sqrt{(Z_{0c} - Z_{0o})^2 - (Z_{0c} + Z_{0o})^2 \cos^2 \theta}}{(Z_{0c} + Z_{0o}) \sin \theta}$ $Z_{12} = \frac{Z_{0c}Z_{0o}}{Z_{11}}$	
	$Z_{11} = \frac{Z_{0c} + Z_{0o}}{2}$	All pass
	$Z_{11} = \frac{2Z_{0c}Z_{0o}}{Z_{0c} + Z_{0o}}$	All pass
	$Z_{11} = \sqrt{Z_{0c}Z_{0o}}$	All pass
	$Z_{11} = -j \frac{2Z_{0c}Z_{0o}}{Z_{0c} + Z_{0o}} \cot \theta$ $Z_{12} = \frac{Z_{0c}Z_{0o}}{Z_{11}}$	All stop
	$Z_{11} = j \sqrt{Z_{0c}Z_{0o}} \tan \theta$	All stop
	$Z_{11} = -j \sqrt{Z_{0c}Z_{0o}} \cot \theta$	All stop

Four port impedance matrix eqns reduces to

$$V_1 = Z_{11} I_1 + Z_{13} I_3, \quad \text{--- 90(a)}$$

$$V_3 = Z_{31} I_1 + Z_{33} I_3, \quad \text{--- 90(b)}$$

where Z_{ij} is given in eq (89).

We can analyze the filter characteristics of

this cut by calculating the image impedance (which is same at port 1 and port 3), and the propagation

1900,

2

2

the

constant. From Table 1 (Page 370), the image impedance in terms of Z-parameters is

$$Z_i = \frac{\sqrt{Z_{11}^2 - \frac{Z_{12} Z_{21} Z_{33}}{Z_{22}}}}{Z_{22}}$$

$$= \frac{1}{2} \sqrt{(Z_{oe} - Z_{oo})^2 \operatorname{cosec}^2 \theta - (Z_{oe} + Z_{oo})^2 \cot^2 \theta} \quad \text{--- (91)}$$

When the coupled line section is $\frac{\lambda}{4}$ long ($\theta = \frac{\pi}{2}$), the image impedance reduce to

$$Z_i = \frac{1}{2} (Z_{oe} - Z_{oo}) \operatorname{cosec}^2 \theta$$

$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$
 $\operatorname{cosec} \frac{\pi}{2} = 1$
 $\cot \frac{\pi}{2} = 0$

which is real and +ve, since $Z_{oe} > Z_{oo}$.

But when $\theta \rightarrow 0$ or π , $Z_i \rightarrow \pm j\infty$, indicating a stop band. The real part of image impedance is sketched in fig 37, where cutoff frequencies can be found

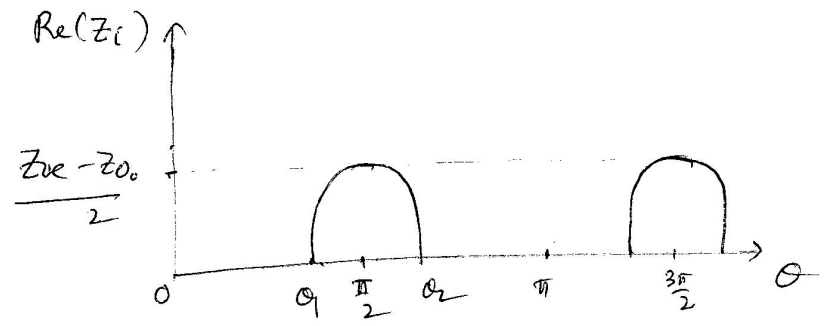



fig 37:- The real part of image impedance of bandpass w/d of fig 36 (c).

→ eqn (1), as $\cos \theta_1 = -\cos \theta_2 = \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}}$

The propagation constant can also be found from the result of table 1, as

$$\cos \beta = \sqrt{\frac{Z_{11} Z_{33}}{Z_{13}^2}} = \frac{Z_{11}}{Z_{13}}$$


$$\cos \beta = \frac{Z_{0e} + Z_{0o}}{Z_{0e} - Z_{0o}} \cos \alpha \quad \text{--- (93)}$$

(91) which shows β is real for $\alpha_1 < \alpha < \alpha_2 = \pi - \alpha_1$,

where

$$\cos \alpha_1 = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}}$$

Q) Why a 3-port n/w can't be matched at all ports? [E-plane Tee / H-plane Tee]

Proof :- Assume that all the 3-ports are matched,

$$S = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix} \quad \text{--- (1)}$$

From the symmetry property of S-matrix

$$S_{12} = S_{21}, \quad S_{13} = S_{31}, \quad S_{23} = S_{32} \quad \text{--- (2)}$$

From zero property of S matrix, the sum of products of each term of any column (or row) multiplied by complex conjugate of the corresponding terms of any other column (or row) is zero and it is

$$S_{11} S_{12}^* + S_{21} S_{22}^* + S_{31} S_{32}^* = 0 \quad \text{--- (3)}$$

Since $S_{11} = 0$ and $S_{22} = 0$, eqn (3) becomes

$$S_{31} S_{32}^* = 0$$

By symmetry, $S_{13} S_{23}^* = 0$ ——— (4)

This means that either S_{13} or S_{23}^* or both should be zero. However, from the unity property of S-matrix, the sum of the products of each term of any one row (or column) multiplied by its complex conjugate is unity; i.e.

$$S_{21} S_{21}^* + S_{31} S_{31}^* = 1 \quad \text{--- (5)}$$

$$S_{12} S_{12}^* + S_{32} S_{32}^* = 1 \quad \text{--- (6)}$$

$$S_{13} S_{13}^* + S_{23} S_{23}^* = 1 \quad \text{--- (7)}$$

Substitution of eqn (4) in eqn (5), we have

$$S_{12} S_{12}^* = 1 - S_{13} S_{13}^*$$

$$\Rightarrow |S_{12}|^2 = 1 - |S_{13}|^2$$

Similarly, from eqn (6), $|S_{12}|^2 = 1 - |S_{23}|^2$

$$\therefore |S_{12}|^2 = 1 - |S_{13}|^2 = 1 - |S_{23}|^2 \quad \text{--- (8)}$$

Eqn (7) and (8) are contradictory, for if $S_{13} = 0$, [eqn (8)] then S_{23} is also zero and thus eqn (7) becomes false

Similarly, if $S_{23} = 0$, S_{13} becomes zero, eqn (8) " " , [eqn (8)]

This inconsistency proves that our assumption is false.

The j^{th} [E/H] Plane Tee can not be matched to 3 arms. i.e. diagonal elements of S-matrix of Tee j^{th} are not all zeros.

* Best of Luck *