

Algorithm State Machine (ASM)

✓
 → The binary information stored in a digital system can be classified as either data or Control information.

→ Data are discrete elements of information that are manipulated to perform arithmetic, logic, shift and other similar data processing tasks. These operations are implemented with digital components such as adders, multiplexer, counters and shift registers.

→ Control information provides command signals that supervises the various operations in the data section in order to accomplish the desired data processing tasks.

→ Fig 1. shows the relationship between the control logic & data processing in a digital system.

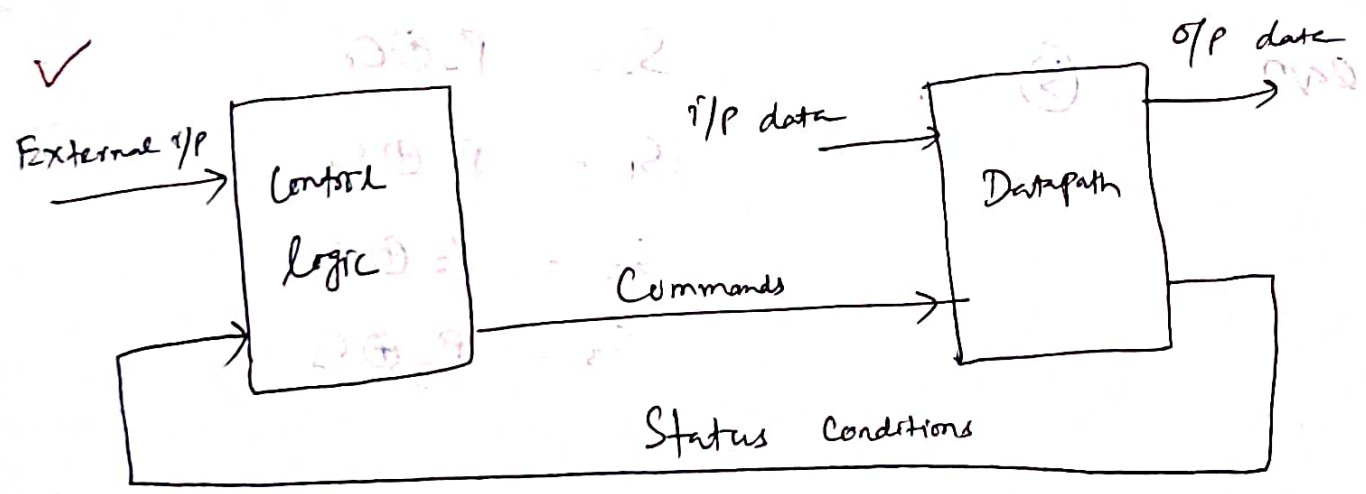


Fig 1:- Interaction between Control logic & datapath

The data processing path, commonly referred to as the datapath, manipulates data in registers according to the system's requirements.

The control logic initiates a sequence of commands to the datapath. The control logic uses status conditions from the datapath to serve as decision variables for determining the sequence of control signals.

So to design a digital system, we have to design 2 subsystem - datapath subsystem and control subsystem. A datapath subsystem consists of digital circuits which are required to perform specified operations on the data information.

A control subsystem is a sequential circuit which decides the control commands for the subsystem. The sequential circuit considers the status condition & other external i/p's to determine the next state to initiate other operations.

A state machine is another term for a sequential circuit which is the basic structure of a digital system.

Just as a flow chart serves as a useful aid in writing software programs, algorithm state machine (ASM) charts help in the hardware design of digital system.

A Conventional flow chart describes the sequence of procedural steps and decision paths for an algorithm without any concern for the time relationship.

The ASM Chart on the other hand describes the sequence of events as well as the timing relationship between the states of a sequence controller and the events that occur while going from one state to next state after each clock edge

Components of ASM Chart:-

There are 3 components of ASM Chart -

- 1) State Box
- 2) Decision Box
- 3) Conditional op Box

1) State Box

A state of a clocked sequential circuit is represented by a rectangle called State Box. It is equivalent to a node in the state diagram or a row in a state table


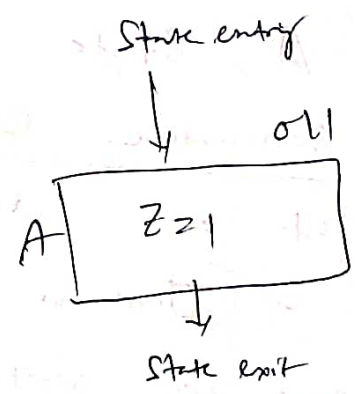
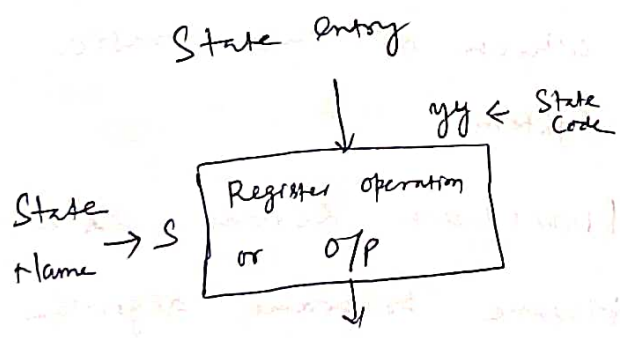


Fig 2: State Box (a) General description

(b) Specified example

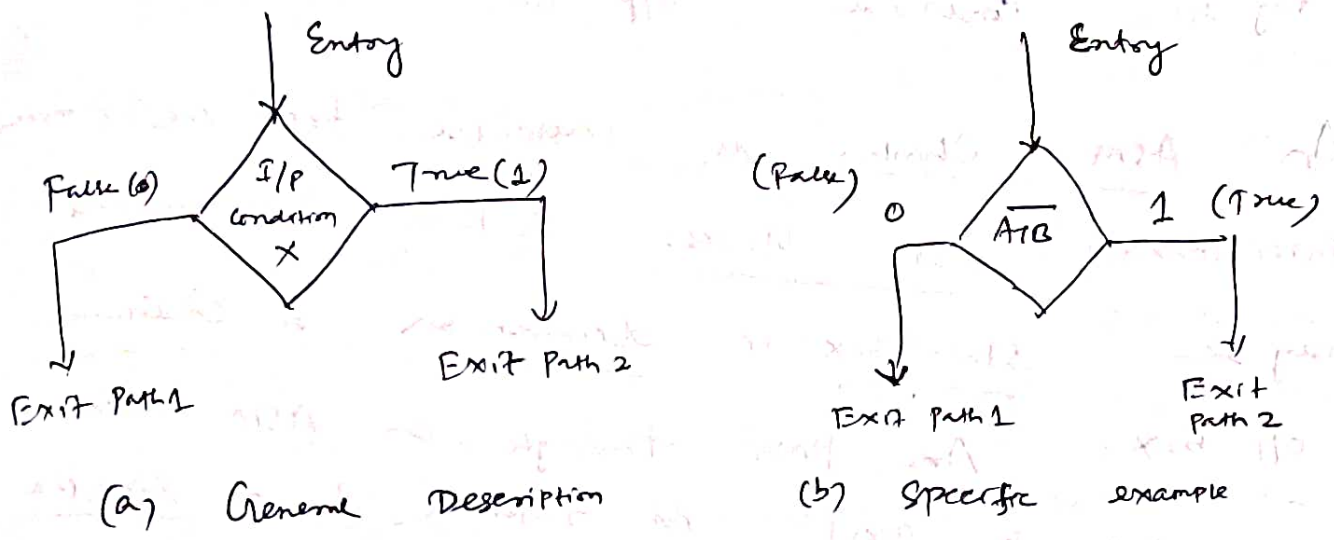2) Decision Box

The decision box or conditional box is represented by a diamond-shaped symbol with one i/p and two or more o/p paths.



(a) General Description

(b) Specific example

Fig 3:- Decision Box

For ex :- 'X' is written inside the box indicates that the decision is based on the values of X, where as $\overline{A/B}$ written inside the box indicates that the true path is chosen if $\overline{A/B}=1$ and the false path is chosen otherwise.

3) Conditional o/p Box

The conditional o/p box is represented by a rectangle with rounded corners or by an oval with one i/p line and one o/p line. The o/p's that depend on both the state of the system & i/p's are indicated inside the box. These are Mixed type o/p's.

 


Fig 4.1 - Conditional OP Box.

An ASM Chart is constructed from one or more interconnected ASM blocks. So these ASM blocks may be state box or decision box or conditional OP box. A path through an ASM block from entry to exit is referred to as loop path.

Salient Features of ASM Chart :-

- 1) An ASM Chart describes the sequence of events as well as the timing relationship between the states of a sequential controller and the events that occur while going from one state to the next.
- 2) An ASM Chart contains one or more interconnected ASM blocks.
- 3) Each ASM block contains exactly one state box together with the decision boxes and conditional OP boxes associated with that state.
- 4) Every block in an ASM Chart specifies the operations that are to be performed during one common clock pulse.

- 5) An ASM block has exactly one entrance and one or more exit paths represented by the structure of the decision boxes.
- 6) A path through an ASM block from entrance to exit is referred to as a link path.
- 7) The operations specified within the state and conditional o/p boxes in the block are performed on the datapath subsystem.
- 8) Internal feedback within an ASM block is not permitted. Even so, following a decision box or conditional o/p boxes, the machine may reenter the same state.
- 9) Each block in the ASM chart describes the state of the system during one clock pulse interval. When a digital system enters the state associated with a given ASM block, the o/p's indicated within the state box become true. The conditions associated with the decision boxes are evaluated to determine which path or paths to be followed to enter the next ASM block.

Some examples of ASM Charts: -

4) Mod-6 Counter

The state diagram of a Mod-6 counter is shown in Fig. 5.(a). ASM chart equivalent of Fig. 5.(a) is shown

In Fig 5(b). The states are now represented by state boxes instead of nodes.


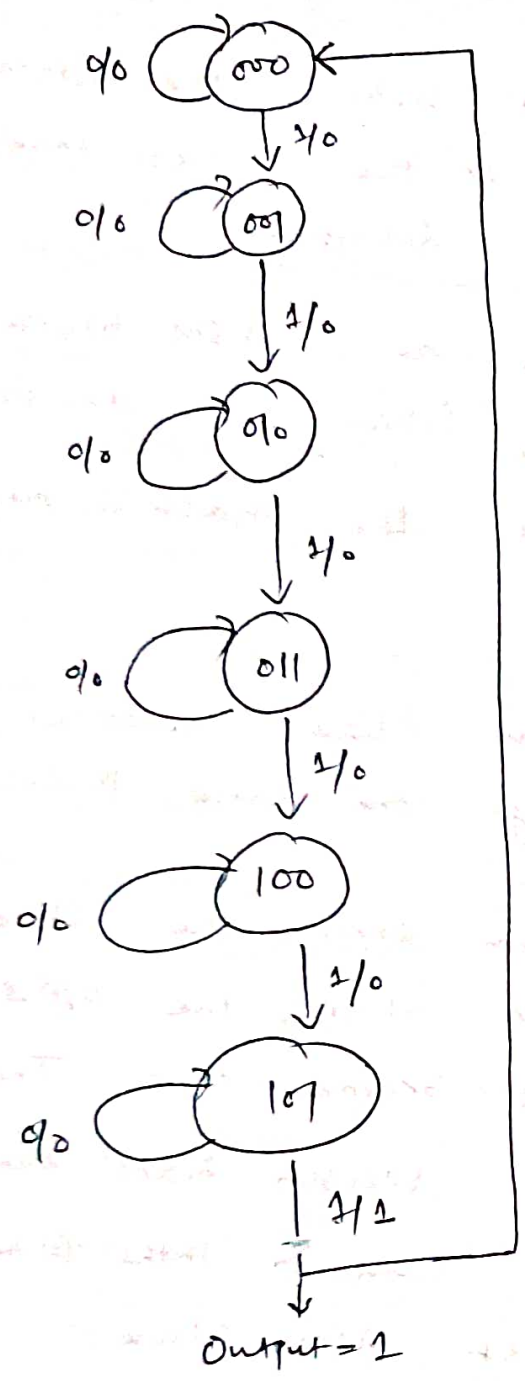


Fig 5 (a): State diagram

Fig 5:- State diagram & ASM chart for Mod-6 Counter

 

5: (b) ASM chart

The transitions are still represented by arrows but the I/Os indicated adjacent to arrows in the state diagram are replaced by decision boxes with true and false branches. In state diagram the O/Ps are indicated along with I/Os using a separator slash or comma. In ASM chart are now indicated in conditional O/P box.

The ASM chart has 6 state boxes named from S₀ to S₅. For every clock pulse, X is sensed. If X=1, the machine goes to next state; if X=0, then the machine remains in the same state as indicated by a return branch. All these happens in the same clock cycle.

When the machine is in state S₅, on the occurrence of the clock pulse, if X=1, the machine produces an O/P pulse indicated as Z' and goes to the initial state S₀. The states are assigned binary numbers (ex: 100) using three F/Fs.

Let's design it using D F/Fs. With D F/Fs, the excitation D_i has to be same as next state variable Y_i. [Note: - In 'D' F/F O/P is same as I/P to D]

Observing only state assignment indicated in ASM chart, we notice that the next value Y_0 has to become 1 for the present states $Y_2, Y_1, Y_0 = 000, 010, 100$ only.

Note - For present state

Present State	Next State
000 →	001
010 →	011
100 →	101

Here last bit is changing from 0 to 1. So Y_0 becomes 1.

Hence using decimal codes & remembering that states 6 (110) & 7 (111) never occur,

we get

$$D_0 = Y_0 = X \cdot \left[\sum m(0, 2, 4) + d(6, 7) \right]$$

Note: D_0 is multiplied or ANDed

$X=0$, D_0 & $Y_0 = 0$
 $X=1$, then $Y_0 = \left[\sum m(0, 2, 4) + d(6, 7) \right]$

Similarly

$$D_1 = Y_1 = X \cdot \left[\sum m(1, 2) + d(6, 7) \right]$$

Note

Present State	Next State
001 →	010
010 →	011

(Y_0 has to 1 & Y_1 should remain 1)

Similarly

✓ $D_2 = Y_2 = X \left[\sum m(3,4) + d(6,7) \right]$ 249

because

$\frac{P.S}{011}$	$\frac{N.S}{100}$
$\frac{100}{101}$	$\frac{101}{101}$

Similarly

✓ $Z = X \cdot \left[\sum m(5) + d(6,7) \right]$

because the state is 101 or 5 and

$X = 1$ the O/P = 1.
(Z)

Notice that the I/P X is ANDed with each of expressions for the excitations. If the I/P X is exclusively provided, then the circuit counts the number of clock pulses in the duration when X is at level 1. In other words X enables the counter.

Ex:-2 Sequence Detector

Consider the example we have done earlier :-
1010 sequence detector with overlapping permitted.

The state diagram of the sequence detector is shown in Fig 6-(a). The ASM chart of the sequence detector is shown in Fig. 6 (b).


 


Fig 6(a) State diagram

The machine has 4 states. So, 4 state boxes are required. While at each state, the machine has to decide to which next state it has to go when the i/p 0 or 1 is given. Four decision boxes with

 two branches each, are also required. It has to give a '1' once the sequence 1010 is detected. So it requires a conditional o/p box. The state assignment is arbitrary i.e., let it be



6(b) A sm Chart

$$S_0 = 00, \quad S_1 = 01, \quad S_2 = 10, \quad S_3 = 11, \quad 251$$

There are 4 states and $y_1 y_0$ are the binary values assigned to the states. If we decide to use two D FFs, the excitation table is identical to the transition table and

$$D_i = Y_i.$$

In this ASM chart, note that the next state variable Y_0 becomes 1 in states $S_1 (01)$ & $S_3 (11)$. The corresponding present states are $S_0 (y_1 y_0 = 00)$ & $S_2 (y_1 y_0 = 10)$ and transition occurs if $X = 1$.

Note:-
i.e.

	P. State		N. State
(S_0)	<u>00</u>	$\xrightarrow{1}$	01 (S_1)
S_2	<u>10</u>	$\xrightarrow{1}$	11 (S_3)

Thus, we may write the expression for excitation D_0 by inspection as follows.

$$D_0 = Y_0 = X \bar{y}_1 \bar{y}_0 + X y_1 \bar{y}_0 = X \bar{y}_0 (\bar{y}_1 + y_1)$$

$$\therefore D_0 = X \bar{y}_0 \quad \text{--- (1)}$$

From ASM chart we observe that Y_1 becomes 1 for S_2 on $X = 0$ from S_1 .

Similarly $Y_1 = 1$ for S_3 on $X = 1$ from S_2 .

Similarly $Y_1 = 1$ for S_3

(S_1)	01	$\xrightarrow{X=0}$	<u>10</u> (S_2)
(S_2)	10	$\xrightarrow{X=1}$	<u>11</u> (S_3)

$$\therefore D_1 = Y_1 = \bar{X} \bar{y}_1 y_0 + X y_1 \bar{y}_0$$

The OP $Z=1$ when if $X=0$ & Present state $y_1 y_0 = 11$. Therefore,

$$Z = \bar{X} y_1 y_0$$

A logic circuit can be drawn based on the above expressions.

ASM for Binary Multiplier:-

The binary multiplier is designed using the add shift algorithm. The manual working is given in Fig 7.

Fig 7:-

Manual multiplication algorithm

1 1 0 1	← multiplier (13) ₁₀
1 0 1 0	← multiplier (10) ₁₀
0 0 0 0	← partial product 1
0 0 0 0	← " " 2
1 1 0 1	← " " 3
0 0 0 0	← " " 4
1 0 0 0 0 0 1 0	← product (130) ₁₀

→ The product of two n digit numbers can be a number of '2n' digits atmost.

Digital implementation requires the following changes.

- 1) In manual working, we perform left shift on the subsequent partial product which is yet

to be formed, but this kind of anticipatory 253 job is not done by a physically realizable machine.

A real machine can operate only on the existing operands but not on future results. Hence, we shift the partial product already formed to the right by one bit and add the next partial product in its normal position. This would produce the correct result as the relative positions of the operands for additions are as they should be.

2) Instead of forming all the partial products and then adding, which would require a large number of registers to store them, each partial product is added to a register A (Accumulator) and shifted right. This job is repeated n times where n is the number of bits on the multiplier.

Data Subsystem for Binary Multiplier:-

Fig. '8' shows the datapath subsystem for the binary multiplier. It comprises the following

1. Register B to hold the multiplicand
2. Register Q to hold the multiplier.
3. Register A, called Accumulator, to hold the cumulative sum of the products.

- 4. A Parallel adder circuit
- 5. One RIF 'C' to hold the Carry, if any produced in addition
- 6. A Counter 'P' which is initialized to word length 'n' (i.e. no. of digits in the multiplier)
- 7. Provision to decrement P to check for zero.
- 8. Provision to concatenate the registers C, A, Q to form the combined register of length $1 + n + n = 2n + 1$ bits with facility to shift right.

→ Fig 9. illustrates how a digital computer performs multiplication using add-shift algorithm. Consider the

example (1101×1010) .

Initially the multiplicand is loaded into register B and multiplier is loaded into register Q. C & A are cleared i.e. 0 & 0. The word length 'n' is loaded into register P which acts as a counter.

The least significant bit Q₀ of the multiplier Q is sensed by the machine.

Case I If $Q_0 = 1$, then form the partial product

MULTIPLIER

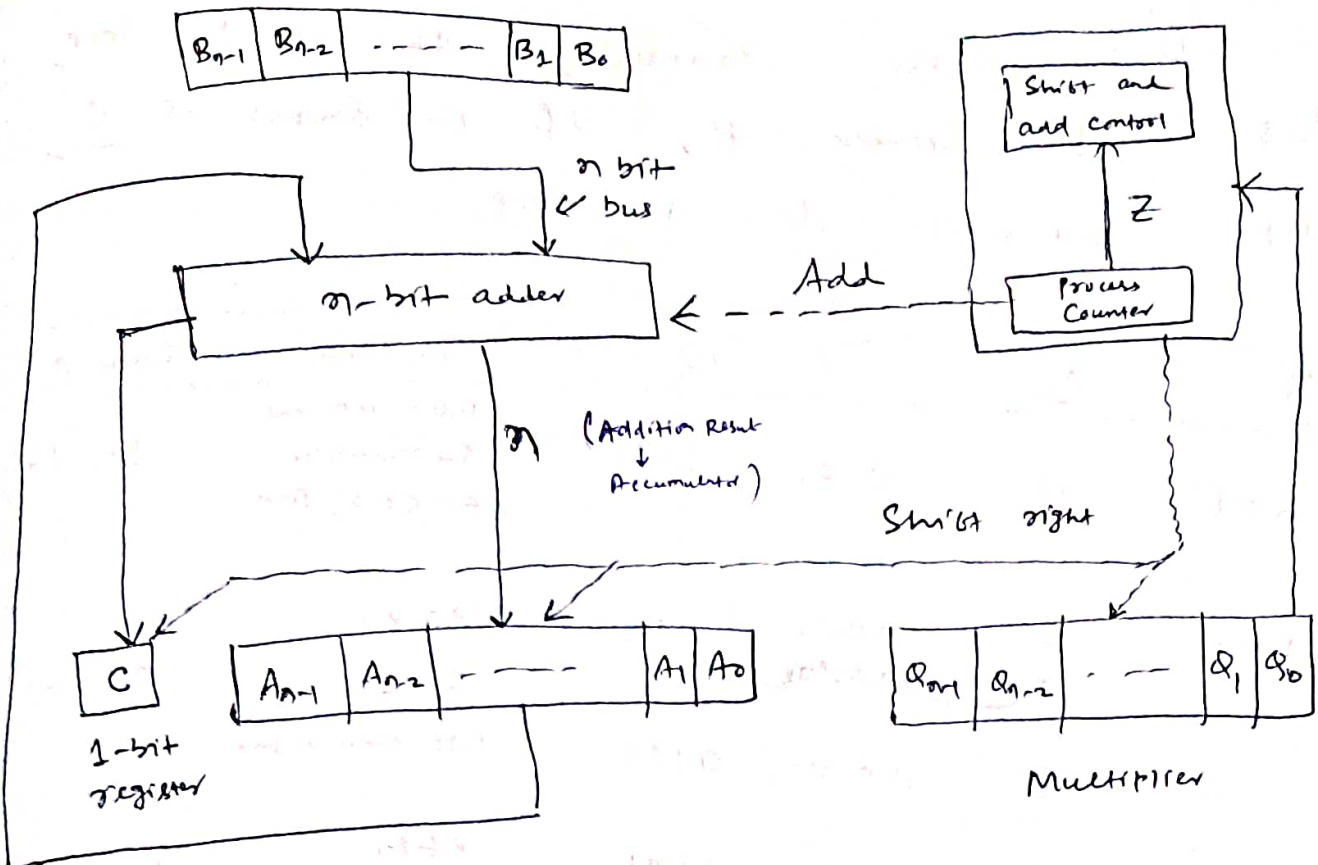


Fig 8:- Datapath subsystem for binary multiplier

{ by adding $\frac{B}{A}$ to A } that is $A \leftarrow A+B$.
 then store it in A

and then shift the combined register \underline{CAQ} to the right by 1 bit position so that 'C' goes to A_{n-1} & 'A' goes to Q_{n-1} & Q_0 goes out. In place of Q_0 , present Q_1 becomes Q_0 for the next iteration.

Case-II If Q_0 i.e. LSB of multiplier Q is '0', then the partial product is 0 and hence there is no need to add, so only shift \underline{CAQ} to the right. Repeat the process 'n' times

in a loop starting from (n-1) and proceed to 0. After traversing through the loop, test the counter P, if it shows as 0, stop and exit from the loop.

B	C	A	Q	Components	Count P
1101	0	0000	1010	B ← Multiplier Q ← Multiplier A ← 0, C ← 0, P ← n	100 (4)
1101	0	0000	1010	P ← P-1 Q ₀ = 0 CAQ shift right	011 (3)
1101	0	0000	0101	CAQ shift right	
1101	0	1101	0101	P ← P-1 Q ₀ = 1 A ← A+B CAQ shift right	010 (2)
1101	0	0110	1010	CAQ shift right	
1101	0	0110	1010	P ← P-1 Q ₀ = 0 CAQ shift right	001 (1)
1101	0	0011	0101	CAQ shift right	
1101	0	0000	0101	P ← P-1 Q ₀ = 1, A ← A+B CAQ shift right	000 (0)
1101	0	1000	0010		


 


Fig 9: Flow chart for multiplication of 1101 & 1010.

∴ Product is 01000010 = (130)₁₀

Flow Chart for Binary Multiplier

Fig 10, show the ASM chart for binary multiplier. The explanation is same as discussed just before.

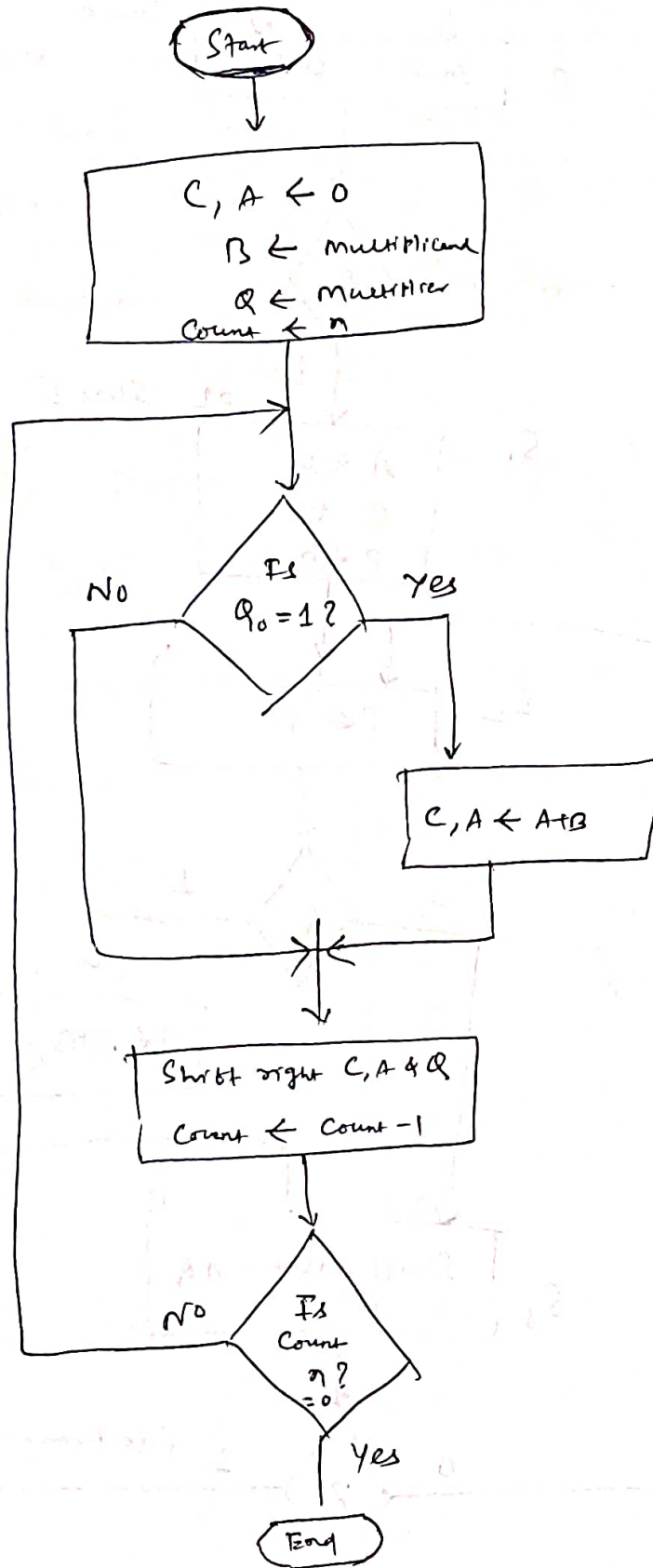

During
 A+B, add carry
 sum → A+B → A
 carry → C

Prog 202 - Flow Chart for multiplication operation

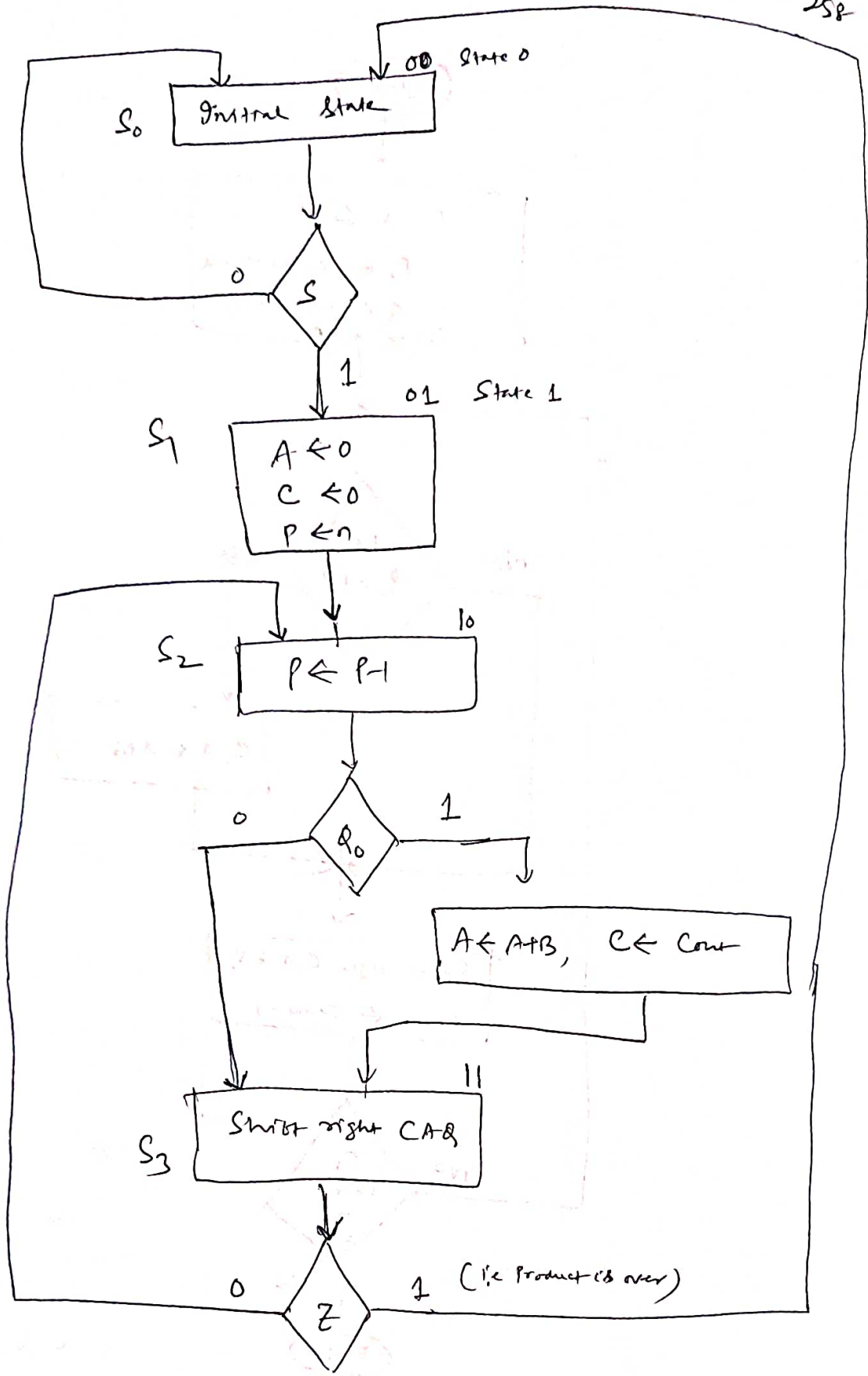


fig 11:- ASM Chart for binary multiplier

Control Subsystem Using logic gates :-

From the ASM Chart, shown in Figure 11, we notice that the binary multiplier has 4 states and three I/Ps. The state table for the control subsystem of a binary multiplier is shown in Table 1.

Look at, ~~the~~ present state PS ($Y_1 Y_0$) & next state NS ($Y_1 Y_0$) columns first. [Refer the ASM chart & design the table]

Table 1:- State Table for the control subsystem

<u>PS</u> $Y_1 Y_0$	<u>I/Ps</u> $S \quad Q_0 \quad Z$			<u>NS</u> $Y_1 \quad Y_0$		<u>O/Ps (Timing signals)</u> $T_0 \quad T_1 \quad T_2 \quad T_3 \quad Q_0 T_2$					
	00	0	-	-	0	0	1				
00	1	-	-	0	1	1					
01	-	-	-	1	0		1				
10	-	0	-	1	1			1			
10	-	1	0	1	1			1			1
11	-	-	0	1	0				1		
11	-	-	1	0	0				1		

Notice in the ASM Chart that there are two transitions from state 00. They are $00 \rightarrow 00$ & $00 \rightarrow 01$, when $S=0$ & $S=1$ respectively.

Other I/Ps for these transitions become don't care entries, shown by dashes.

For P.S '01', there is only one transition to state '10' in the ASM chart. Hence, only one row is provided. This transition has no I/P conditions and hence the columns of S, Q₀, Z become don't cares indicated by dashes.

For P.S '10', the transition to state '11' occurs in 2 paths depending on Q₀. If Q₀ = 0, then the machine goes straight to state '11'. If Q₀ = 1, then the machine has to add B to A and go to state 11.

For P.S of '11', there are two possible transitions. If Z = 0 (i.e. multiplication is not complete), goes to 10 state a decrement counter P. If Z = 1, (i.e. multiplication is over), it goes to initial state 00.

Now, for the I/P columns, T₀ is equal to 1 for P.S '00', Similarly T₁ is 1 for P.S '01', T₂ is 1 for P.S '10', T₃ is 1 for P.S '11'.

Finally, the I/P Q₀.T₂ is for the purpose of enabling addition in state 10.

All these ops eventually provide the control timing signals.

The control unit needs two FIRs. If we choose 2 FIRs, it is easy to get the following expressions for the excitations as functions of state variables y_1, y_0 and the i/p's s, q_0, z .

[Check the expression in table where $y_1 = 1$]

$$D_1 = Y_1 = \bar{y}_1 y_0 + y_1 \bar{y}_0 \bar{q}_0 + y_1 \bar{y}_0 q_0 + y_1 y_0 \bar{z}$$

$$D_1 = \bar{y}_1 y_0 + y_1 \bar{y}_0 + y_1 y_0 \bar{z}$$

Taking common
 $\therefore y_1 \bar{y}_0 (\bar{q}_0 + q_0)$
 $= y_1 \bar{y}_0$

$$D_0 = Y_0 = \bar{y}_1 \bar{y}_0 s + y_1 \bar{y}_0 \bar{q}_0 + y_1 \bar{y}_0 q_0$$

$$D_0 = \bar{y}_1 \bar{y}_0 s + y_1 \bar{y}_0$$

 


Fig: - 12 Control subsystem using logic gates.

Note: - The 17P Q_0 nearly enables 2br
the address on state 10 & hence it does not
participate in excitation functions. It has to produce
the control signal $Q_0 T_2$ to enable the address.

ASM for Weighing Machine

The weight of a binary number is defined as
the number of 1's present in its binary representation.

Here we want to design a sequential machine
which will calculate the weight of a given binary
number or in other words compute the number of
1s in a given binary number

Let the digital system (weighing
Machine) contain a register R to store the binary
number whose weight is to be determined, another
register W which acts as a counter to determine
the weight of the given binary number and
1 F/F.

Initially the number has to be loaded into
register 'R' and 'W' has to be initialized. Then shift
each bit of the register R into F/R 'F',
one at a time, sense the value of 'F'; whenever
it is '1', the register 'W' is incremented by
one. At the end 'W' contains the weight
of the word.

The ASM Chart for the weighing machine is shown in Figure 13.

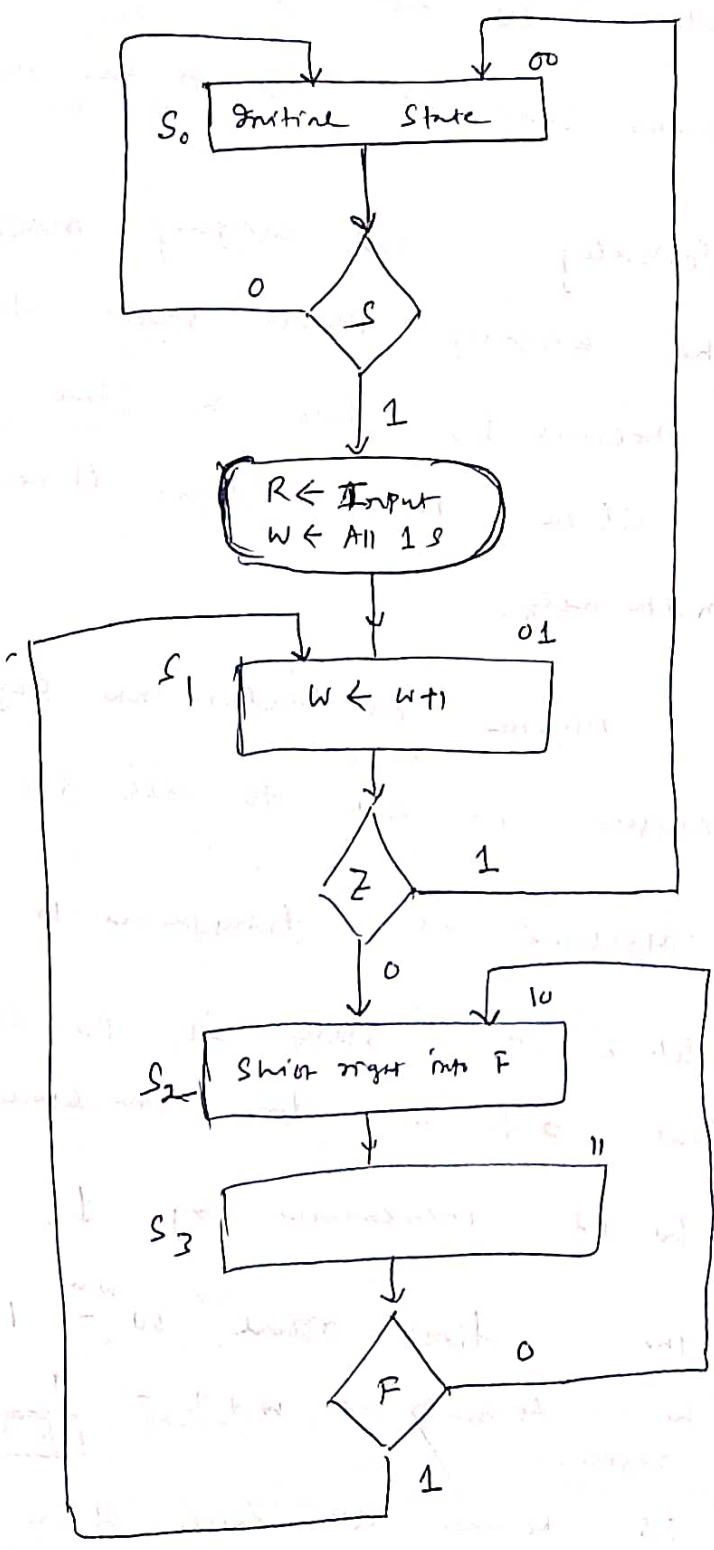


Fig 13:- ASM Chart for weighing machine

→ GA has 3 I/Ps S (Start), Z (Zero) and F (Flip Flop) and 4 States S0, S1, S2 and S3. S is the start I/P (S=1), starts the weight computation process, Z

is for sensing all zeros in R ($Z=1$ indicates all zero in R,) and the value of F decides whether W is to be incremented or not ($F=1$ indicates that W has to be incremented)

State S_0 :- Initially the weighing machine is in state S_0 . The weighing process starts when start signal becomes 1, where in state S_0 , if $S=1$, the clock pulse causes three jobs to be done simultaneously.

1. Binary number is loaded into Register R
2. W register is set to all 1s.
3. The machine is transferred to state S_1 .

State S_1 :- While in state S_1 , the clock pulse causes two jobs to be done simultaneously.

1. Counter W is incremented by 1.

Note:- From the first round, $W_n^{new} = 1111$ (lets say)
 (lets say W is 4 bit register.) and $W+1 = \begin{array}{r} + 1 \\ 1 \boxed{0000} \end{array}$

So all 1s becomes all zeros. W is reset to 0000.

2. If $Z=0$, the machine goes to the state S_2 ;
 if $Z=1$, the machine goes to state S_0 .
 (i.e. all shipping in R is completed & R becomes 0); weight of word indicated by W, and machine goes back to initial state

$Z=0$; means 'R' is not zero; ~~right~~ ^{right} shifting 2LS.
if not complete a shift some weights are there.
So it goes to next state 'S₂' to do the further shifting.

State S₂:

In this state, register R is shifted right by 1 bit so that LSB goes to R and MSB is loaded with 0.

State S₃ :-

In this state, the value of R is checked. If it is '0', machine is transferred to the state S₂. If it is '1', the machine is transferred to state 'S₁'. And W is incremented by 1.

System Design:-

The system (Machine) consists of 2 subsystems:-
data processor subsystem and control subsystem. The data processor subsystem performs the task prescribed for each state of the ASM block. The control subsystem ensures the proper sequence of states and transitions depending on the r/p and the present state of the machine.

Datapath Subsystem:-


Fig 14. Shows the datapath subsystem for the weighing machine. It shows the registers, F/Fs, Control Subsystem Ckt for Zero checking and connections of the control signals which controls the operation of these.

The Control Subsystem produces the signals T_0, T_1, T_2 and T_3 when the machine is on state S_0, S_1, S_2 & S_3 respectively. (Ex:- $T_0=1$ when the machine is on the state S_0 ; $T_1=1$ when the machine is in the state S_2 & S_0 on). These signals are used to activate desired operations on their respective states.

Initially, the machine will be on state S_0 , i.e. $T_0=1$. For starting the process, make the i/p S equal to 1. The clock pulse occurring while in S_0 loads the i/p word parallelly into register R and sets the register W to all 1s at the same time. The same pulse takes the machine to state S_1 and T_1 becomes 1.

While in the state S_1 , the clock pulse increments W and makes it 0 to begin with. The

same pulse senses Z . If $Z=1$, then it would mean that the word in R contains all 0s and so the same clock pulse takes

 

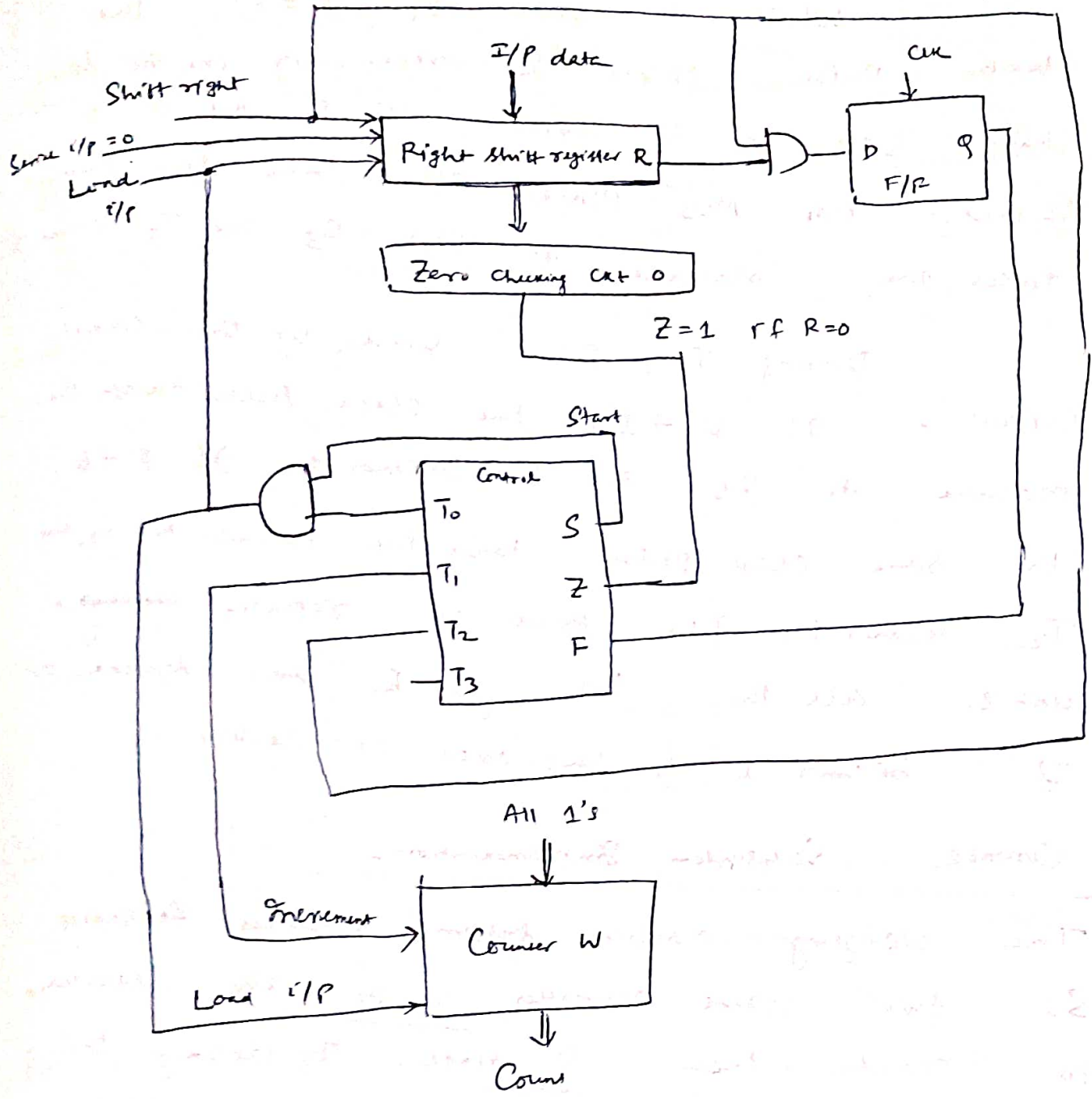


Fig 14:- Datapath subsystem for weighing machine

the machine to the initial state S_0 as the weight of the given word already indicated by W . and process ends.

If Z is sensed '0' during T_1 , then it means that binary word contains one or more 1's in it. So the process has to continue and the control ensures that the same clock pulse takes the machine to state S_2 and T_2 becomes 1.

268

While in state S_2 , ($T_2 = 1$), the clock pulse shifts 'R' right by one bit so that LSB of R appears in F and '0' is shifted into MSB place. The same clock pulse takes the machine to state S_3 and T_3 becomes 1.

During T_3 , R is sensed by the control circuit. If $F = 1$, the clock pulse takes the machine to S_1 and T_1 becomes 1. If $F = 0$, the same clock pulse takes the machine to S_2 and T_2 becomes 1. The process is repeated until all the bits of R are sensed or Z becomes 1, whichever is earlier.

Control Subsystem Implementation

The weighing machine system requires 4 states. So two state variables Y_1, Y_0 are required to provide these 4 states. By decoding the state variables, one can obtain the control timing signals T_0, T_1, T_2 & T_3 .

Let Y_1 & Y_0 be the next state variables which depends on the I/Ps S, Z, F and present state variables Y_1, Y_0 . Let us use D P/Rs, then the excitations D_1 & D_0 are $D_1 = Y_1$ and $D_0 = Y_0$. To design the control subsystem, we have to obtain minimal expression for D_1 & D_0 .

In terms of Y_1, Y_0, S, Z, F .

Table 2:- State Table for Working Machine

Present state $Y_1 \ Y_0$	I/Ps			N. state		F/R I/Ps	
	S	Z	F	Y_1	Y_0	$D_1 = Y_1$	$D_0 = Y_0$
0 0	0	-	-	0	0	0	S
0 0	1	-	-	0	1		
0 1	-	1	-	0	0	\bar{Z}	0
	-	0	-	1	0		
1 0	-	-	-	1	1	1	1
1 1	-	-	1	0	1	\bar{F}	F
			0	1	0		

Row 0: Row 0 shows that on the next state, the o/p of (F/R 1) is always 0, hence for any value of S. So we can put 0 on the column D_1 for row 0. Similarly, for (F/R 0) the next state Y_0 follows S i.e. when $S=0, Y_0=0$, when $S=1, Y_0=1$. that is why D_0 is written as 'S'.

Row 1: Row 1 shows that on the next state, the o/p of (F/R 1) follows the complement of Z. and (F/R 0) is always '0' independent of value of Z. so $D_0 = 0$.

Row 2 - Row 2 shows that, in the next state, ²⁷⁰
 the o/p of PPR1 & PPR2 are logic 1.
 Hence we can put 1 in the column of
 D_1 & D_0 .

Row 3 - Row 3 shows that, in the next state,
 the o/p of PPR1, $= \bar{F}$, & o/p of PPR0 = F.
 (follows the complement of F) (follows F)

Since the control signals T_0, T_1, T_2 & T_3
 corresponds to state S_0, S_1, S_2, S_3 i.e. row 0, row 1,
 row 2 & row 3, the expressions for the
 o/p of PPR1 & PPR0 are given by

$$D_1 = T_0 \cdot 0 + T_1 \cdot \bar{Z} + T_2 \cdot 1 + T_3 \cdot \bar{F}$$

$$D_1 = T_1 \cdot \bar{Z} + T_2 + T_3 \bar{F} \quad \text{--- (1)}$$

$$D_0 = T_0 \cdot S + T_1 \cdot 0 + T_2 \cdot 1 + T_3 \cdot F$$

$$D_0 = T_0 S + T_2 + T_3 F \quad \text{--- (2)}$$

Based on the above expressions for D_1 & D_0
 a logic diagram can be drawn as
 shown in figure 15.

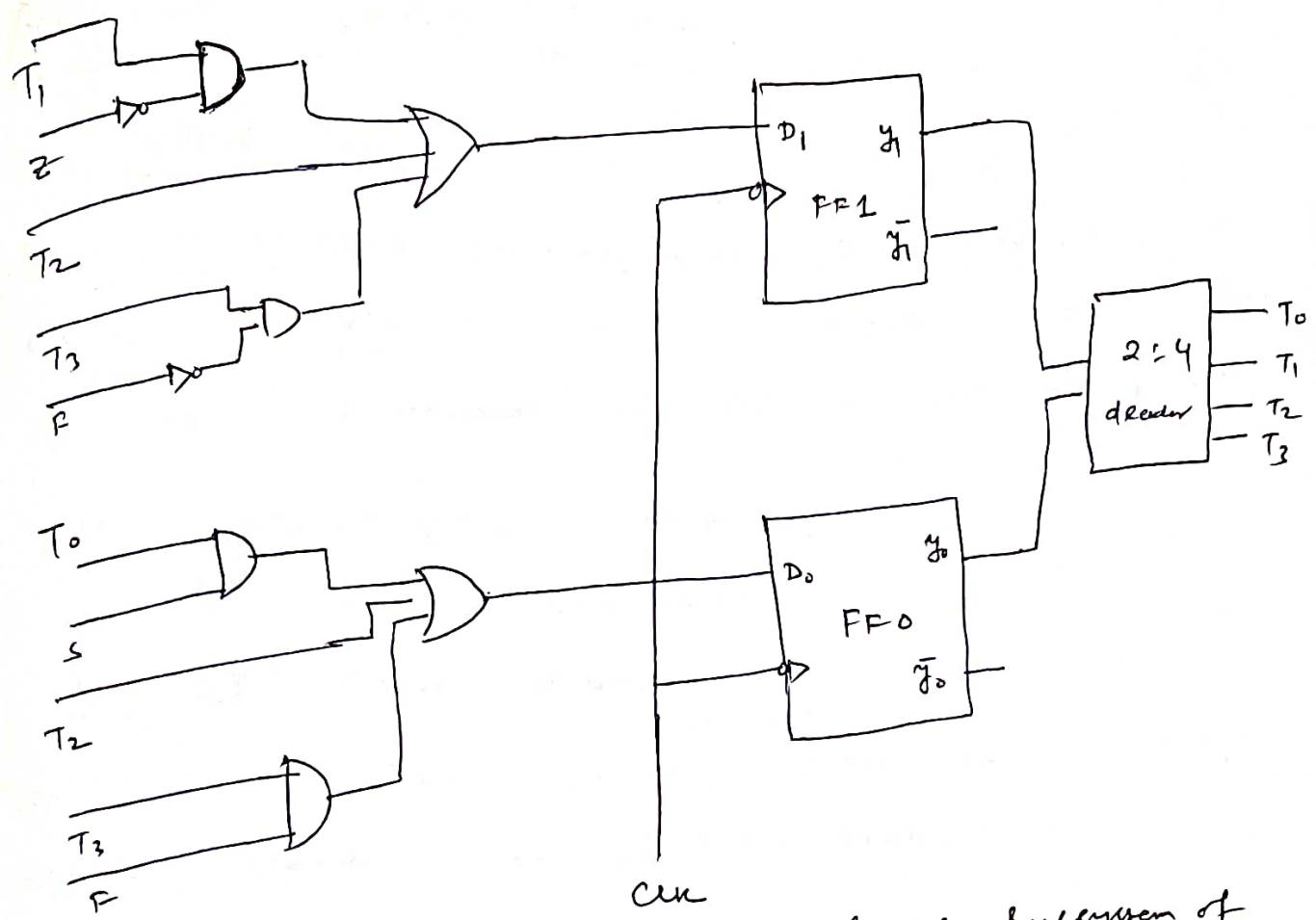


Fig. 15:- Logic ckt of control subsystem of weighing machine.

— 0 —