

25 marks  
4/10 to 7/10

# Digital Electronics Principle

## Number System

- Decimal number system
- Binary number system
- Octal number system.
- Hexadecimal number system.

→ All these number system are known as positional number system because each digit position is assigned with a particular weight.

→ The total number used in any number system is known as base or radix of that system and is denoted by  $r$ .

→ Decimal → 0, 1, 2, 3, 4, 5, 6, 7, 8, 9,  $\frac{r}{10}$

Binary → 0, 1, 2

Octal → 0, 1, 2, 3, 4, 5, 6, 7, 8

Hexadecimal → 0, 1, 2, ..., 8, 9, A, B, C, D, E, F, 16

Decimal number system:

← 2.9  
485.76 →

Suppose a number system having base  $y$  is

is written as  
( $a_n a_{n-1} \dots a_2 a_1 a_0 . b_1 b_2 b_3 \dots b_m$ )<sub>y</sub>

$a_n y^n$

$$= a_n y^n + a_{n-1} y^{n-1} + \dots + a_1 y^1 + a_0 y^0 + b_1 y^{-1} + b_2 y^{-2} + \dots + b_m y^{-m}$$

(5263.343)<sub>10</sub> is calculated as,

$$\begin{aligned}
 & 5 \times 10^3 + 2 \times 10^2 + 6 \times 10 + 3 + 3 \times 10^{-1} + 4 \times 10^{-2} + 3 \times 10^{-3} \\
 &= 5000 + 200 + 60 + 3 + \frac{3}{10} + \frac{4}{100} + \frac{3}{1000} \\
 &= 5263 + (.3 + .04 + .003) \\
 &= 5263 + 0.343 \\
 &= 5263.343
 \end{aligned}$$

$$\begin{array}{r}
 .3 \\
 .04 \\
 .003 \\
 \hline
 .343
 \end{array}$$

Number Base Conversion :-

(1) Decimal to binary

ex: 1      (19)<sub>10</sub> = ( )<sub>2</sub>

Ans:

$$\begin{array}{l}
 2 \overline{) 19} \\
 2 \overline{) 9} \rightarrow 1 \\
 2 \overline{) 4} \rightarrow 1 \\
 2 \overline{) 2} \rightarrow 0 \\
 2 \overline{) 1} \rightarrow 0 \\
 0 \rightarrow 1
 \end{array}
 \quad \uparrow
 \quad (19)_{10} = (10011)_2$$

(Ans)

ex-2 :-      (0.625)<sub>10</sub> = ( )<sub>2</sub>

$$\begin{array}{r}
 .625 \\
 \times 2 \\
 \hline
 1.250 \rightarrow 1 \\
 \hline
 .500 \rightarrow 0 \\
 \hline
 1.000 \rightarrow 1
 \end{array}$$

(.625)<sub>10</sub> = (0.101)<sub>2</sub>

∴ (0.625)<sub>10</sub> = (0.101)<sub>2</sub>

4 number system  
2 conversion at a time  
 $4_{P2} = \frac{4!}{2!} = 12 \text{ ways}$   
Decimal → binary  
          → octal  
          → hexadecimal  
binary → decimal  
          → octal  
          → hexadecimal  
Line that



$$(0.1875)_{10} = (\quad)_2$$

$$\times \begin{array}{r} 0.1875 \\ \hline 2 \end{array}$$

$$\begin{array}{r} 0.3750 \\ \hline 2 \end{array} \rightarrow 0$$

$$\begin{array}{r} 0.7500 \\ \hline 2 \end{array} \rightarrow 0$$

$$\begin{array}{r} 1.5000 \\ \hline 2 \end{array} \rightarrow 1$$

$$\begin{array}{r} 1.0000 \\ \hline 2 \end{array} \rightarrow 1$$

$$(0.1875)_{10} = (0.0011)_2$$

Ex-4 :

$$(26.375)_{10} = (\quad)_2$$

Consider integer part

$$\begin{array}{r} 2 \overline{) 26} \\ 2 \overline{) 13} \rightarrow 0 \\ 2 \overline{) 6} \rightarrow 1 \\ 2 \overline{) 3} \rightarrow 0 \\ 2 \overline{) 1} \rightarrow 1 \\ 2 \overline{) 0} \rightarrow 1 \end{array}$$

$$(26)_{10} = (11010)_2$$

$$\begin{array}{r} 0.375 \\ \hline 2 \end{array}$$

$$\begin{array}{r} 0.750 \\ \hline 2 \end{array} \rightarrow 0$$

$$\begin{array}{r} 1.500 \\ \hline 2 \end{array} \rightarrow 1$$

$$\begin{array}{r} 1.000 \\ \hline 2 \end{array} \rightarrow 1$$

$$(0.375)_{10} = (0.11)_2$$

$$(26.375)_{10} = (11010.011)_2$$

2) Decimal to Octal Conversion:-

ex-5

$$(8276)_{10} = (\quad)_{8}$$

$$8 \overline{) 8276}$$

$$8 \overline{) 1034} \rightarrow 4$$

$$8 \overline{) 129} \rightarrow 2$$

$$8 \overline{) 16} \rightarrow 1$$

$$8 \overline{) 2} \rightarrow 0$$

$$0 \rightarrow 2$$

$$(8276)_{10} = (20124)_8$$

ex-6

$$(5734)_{10} = (\quad)_{8}$$

$$8 \overline{) 5734}$$

$$8 \overline{) 716} \rightarrow 6$$

$$8 \overline{) 89} \rightarrow 4$$

$$8 \overline{) 11} \rightarrow 1$$

$$8 \overline{) 1} \rightarrow 3$$

$$0 \rightarrow 1$$

$$(5734)_{10} = (13146)_8$$

ex-7

$$(0.0078125)_{10} = (\quad)_{8}$$

.0078125

$$\textcircled{0} \begin{array}{r} 8 \\ \hline .0625000 \end{array} \rightarrow 0$$

$$\textcircled{0} \begin{array}{r} 8 \\ \hline .5000000 \end{array} \rightarrow 0$$

$$\textcircled{4} \begin{array}{r} 8 \\ \hline .0000 \end{array} \rightarrow 4$$

$$(0.0078125)_{10} = (0.004)_8$$



ex-8

(112.01)10 = ( )8

8 | 112
8 | 14 -> 0
8 | 1 -> 6
0 -> 1

(112)10 = (160)8

x . 01
8
0.08 -> 0
8
0.64 -> 0
8
0.12 -> 5
8
0.96 -> 0

(0.01)10 = (.0050)8

It will continue. Approximating to 4 digits.

(112.01)10 = (160.0050)8

3) Decimal to Hexadecimal Conversion

ex-9 (84)10 = ( )16

16 | 84
16 | 5 -> 4
0 -> 5

(84)10 = (54)16

ex-10

(0.02)10 = ( )16

$$\begin{array}{r}
 \times \quad .02 \\
 \hline
 \textcircled{0} \cdot 32 \rightarrow 0 \\
 \hline
 \textcircled{5} \cdot 12 \rightarrow 5 \\
 \hline
 \textcircled{1} \cdot 92 \rightarrow 1 \\
 \hline
 \textcircled{14} \cdot 72 \rightarrow E \\
 \vdots
 \end{array}$$

$$(.02)_{10} = (0.051E)_{16}$$

ex-1)

$$(89726.001953125)_{10} = (\quad)_{16}$$

$$\begin{array}{r}
 16 \overline{) 89726} \\
 \underline{5607} \rightarrow E \\
 \underline{350} \rightarrow 7 \\
 \underline{21} \rightarrow E \\
 \underline{1} \rightarrow 5 \\
 \underline{0} \rightarrow 1
 \end{array}$$

$$\begin{array}{l}
 (89726)_{10} \\
 \rightarrow \\
 (15E7E)_{16}
 \end{array}$$

$$\begin{array}{r}
 \underline{0.031250000} \rightarrow 0 \\
 \hline
 \underline{0.50000} \rightarrow 0 \\
 \hline
 \underline{0} \rightarrow 0
 \end{array}$$

$$\begin{array}{r}
 \textcircled{8} : 0 \rightarrow 8
 \end{array}$$

$$(.001953125)_{10} = (0.008)_{16}$$



$$\therefore (89726.001953125)_{10}$$

$$= (15E7E.008)_{16}$$

4) Binary to Decimal Conversion:-

$$(11010.101)_2 = ( )_{10}$$

$$1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3}$$

$$= 16 + 8 + 0 + 2 + 0 + \frac{1}{2} + 0 + \frac{1}{8}$$

$$= 26 + \left(\frac{1}{2} + \frac{1}{8}\right)$$

$$= 26 + \left(\frac{4+1}{8}\right)$$

$$= 26 + \frac{5}{8}$$

$$= 26 + 0.625$$

$$= 26.625$$

$$\therefore (11010.101)_2 = (26.625)_{10}$$

5) Octal to Decimal Conversion:-

$$(230.1)_8 = ( )_{10}$$

$$2 \times 8^2 + 3 \times 8^1 + 0 + 1 \times 8^{-1}$$

$$= 128 + 24 + \frac{1}{8}$$

$$= 152 + .125$$

$$(230.1)_8 = (152.125)_{10}$$

6) Hexadecimal to decimal conversion

$(A D 0 . C)_{16} = ( )_{10}$

$A \times 16^2 + D \times 16^1 + 0 + C \times 16^0$

$= 10 \times 256 + 13 \times 16 + \frac{12}{16}$

$= 2560 + 208 + \frac{3}{4}$

$= 2768 + .75$

$(A D 0 . C)_{16} = (2768.75)_{10}$

$(B A D)_{16} = ( )_{10}$

Ans:  $\rightarrow 2989$

7) Octal to Binary Conversion

Octal digit	Binary equivalent
0	000
1	001
2	010
3	011
4	100
5	101
6	110
7	111

$(765.234)_8 = ( )_2$



$(111 \quad 110 \quad 101 \quad . \quad 1010 \quad 011 \quad 100)_2$

$(765.234)_8 = (111110101.010011100)_2$



Binary to Octal Conversion:-

7.  $(011100111100101110001110)_2 = ( )_8$

$(011\ 001\ 111\ 010\ 110\ 001\ 110)_2 = ( )_8$

$(3\ 1\ 7\ 2\ 6\ 6)_8$

$(11011\ 1011)_2 = ( ? )_8$

$(011011\ 101100)_2 =$

$(3\ 3\ 5\ 4)_8$

Hexadecimal to Binary

Hex digit	Binary equivalent
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
A	1010
B	1011
C	1100
D	1101
E	1110
F	1111

①

$$(\text{ADFE}, 5CB)_{16} = (\quad)_2$$

$$(1010\ 1101\ 1111\ 1110\ 0101\ 1100\ 1011)_2$$

10) Binary to Hexadecimal

$$(1001\ 011\ 010\ 101, 1011\ 000\ 001)_2 = (\quad)_{16}$$

$$0001\ 0010\ 1101\ 0101, 1011\ 0000\ 0100 =$$

$$(1\ 2\ D\ 5, B\ 0\ 4)_{16}$$

11) Hex to Octal

- Step-1 → Hex - Binary  
 Step-2 → Binary - Octal.

Ex:  $(D03, F5)_{16} = (\quad)_8$

$$(D03, F5)_{16} = (1101\ 0000\ 0011, 1111\ 0101)$$

$$= (6403, 752)_8$$

12) Octal to Hex

- Step-1 → Octal - Binary  
 Step-2 → Binary to Hex.



$$\begin{aligned}
 & (1375.25)_8 \\
 &= (001\ 011\ 111\ 101\ 010\ 101)_2 \\
 &= (001\ 011\ 111\ 101\ 010\ 101)_2 \\
 &= (2FD.54)_{16}
 \end{aligned}$$

Some Important terms:-

- Bit → Abbreviation used for binary digit i.e. 0 or 1
- Byte → A group of 8 bits.
- Nibble → A group of 4 bits.
- 1 KB → 1 kilo Byte =  $2^{10}$  Bytes = 1024 bytes.
- 1 MB →  $2^{20}$  Bytes = 1024 × 1024 bytes
- 1 GB =  $2^{30}$  Bytes = 1024 × 1024 × 1024 bytes
- 4 G Bytes =  $4 \times 2^{30}$  =  $2^2 \times 2^{30}$  =  $2^{32}$  Bytes.

Ex :- Convert the following number with indicated base to decimal.

$$\begin{aligned}
 & (4310)_5 \\
 &= 4 \times 5^3 + 3 \times 5^2 + 1 \times 5 + 0 \\
 &= 500 + 75 + 5 \\
 &= (580)_{10}
 \end{aligned}$$

Q.10 :- What is the largest binary number that can be expressed with 12 bits? what is its decimal equivalent.

Ans :- (1111 1111 1111) = The largest binary no.

Its decimal equivalent =  $2^{12} - 1 = 4096 - 1 = 4095$ .

✓ (4 bit  $\rightarrow 2^4 - 1 = 16 - 1 = 15$ )

Binary Addition:

0+0  $\rightarrow$  0

0+1  $\rightarrow$  1

1+0  $\rightarrow$  1

1+1 = 10

↑ Carry

1+1+1 = 11

↑ Carry in binary (2 is 1 unit)

In decimal (10 is 1 unit)

ex :-

$$\begin{array}{r} 1011 \\ + 1111 \\ \hline 11010 \end{array}$$
 Compare with decimal add<sup>n</sup>

$$\begin{array}{r} 11 \\ + 15 \\ \hline 26 \end{array}$$

✓ Imp

$$\begin{array}{r} 1 \\ 11 \\ 111 \\ 1111 \\ \hline 11010 \end{array}$$

Verification :-

$$\begin{array}{l} \rightarrow 1 \\ \rightarrow 3 \\ \rightarrow 7 \\ \rightarrow 15 \\ \hline 26 \end{array}$$

$$\begin{array}{l} 2 \overline{) 26} \\ \underline{2} \phantom{0} \\ 13 \rightarrow 0 \\ \underline{12} \phantom{0} \\ 1 \phantom{0} \rightarrow 1 \\ \underline{2} \phantom{0} \\ 3 \rightarrow 0 \\ \underline{2} \phantom{0} \\ 1 \phantom{0} \rightarrow 1 \\ \underline{0} \phantom{0} \\ 0 \phantom{0} \rightarrow 1 \end{array}$$

$26 = (11010)_2$



## Additional Concepts / Problems :-

### A. Signed Binary Numbers

Positive integers (including zero) can be represented as unsigned numbers. However, to represent -ve integers, we need ~~additional~~ a notation for -ve values.

(i) Signed-Magnitude representation.

(ii)  $1^2$ s Complement representation.

(iii)  $2^2$ s Complement representation.

The user first fixes <sup>(assumes)</sup> whether he is using signed number or unsigned number.

If he is using signed number system

→ The leftmost bit represents the sign and rest of bits represent the number.

If the binary number is assumed to be unsigned, then the leftmost bit is the MSB of the number.

e.g 1) 01001 Considered as 9 (unsigned binary)  
or " " " " +9 (signed binary)

2) 11001 " " 25 (unsigned binary)  
11001 " " -9 (~~the~~ signed binary)

This is because the leftmost bit (1) designates a -ve and other 4 bits represent binary 9.



# 8 bit representation of (-9)

Signed Magnitude representation: 1 0 0 0 1 0 0 1  
 ↑  
 (For sign)

1's Complement representation :-

+9 → 0 0 0 0 1 0 0 1  
 -9 → 1 1 1 1 0 1 1 0 } → Making 1 to 0  
 & 0 to 1

2's Complement representation

[ 1's Complement representation + 1 ]

i.e. 1 1 1 1 0 1 1 0  
 + 1  
 -----  
 -9 → 1 1 1 1 0 1 1 1

The MSB '1' indicates it is -ve number in all the 3 way of representation.

in 2's Complement Method

Note:-

The +9 has same representation in signed-magnitude, 1's Complement & 2's Complement representation i.e. 00001001

Arithmetic addition of signed numbers. (2's Complement form)

1) +6 → 0 0 0 0 0 1 1 0  
 +13 → + 0 0 0 0 1 1 0 1  
 -----  
 +19 → 0 0 0 1 0 0 1 1

2) -6  
 +13  
 -----

To find -6 in 2's Complement form

+6 → 0 0 0 0 0 1 1 0  
 1's → 1 1 1 1 1 0 0 1  
 2's → + 1  
 -----  
 1 1 1 1 1 0 1 0

$$\begin{array}{r} -6 \\ +13 \\ \hline +7 \end{array}$$

$$\begin{array}{r} \rightarrow +11111010 \\ \rightarrow 00001101 \\ \hline \cancel{1}00000111 \end{array}$$

2's

(1 is discarded as 8 bit representation)

To find -13 in 2's Complement form

3) 
$$\begin{array}{r} +6 \\ -13 \\ \hline \end{array}$$

$$\begin{array}{r} +13 \rightarrow 00001101 \\ 1's \rightarrow 11110010 \\ 2's \rightarrow \begin{array}{r} +1 \\ \hline 11110011 \end{array} \end{array}$$

$$\begin{array}{r} +6 \\ -13 \\ \hline -7 \end{array}$$

$$\begin{array}{r} +00000110 \\ +11110011 \\ \hline 11111001 \end{array}$$

(Verification  $\rightarrow$ ) 
$$\begin{array}{r} +7 \rightarrow 00000111 \\ 1's \rightarrow 11110000 \\ 2's \rightarrow \begin{array}{r} +1 \\ \hline 11110001 \end{array} \end{array}$$

4) 
$$\begin{array}{r} -6 \\ -13 \\ \hline -19 \end{array}$$

$$\begin{array}{r} \rightarrow 11111010 \\ \rightarrow +11110011 \\ \hline \cancel{1}11001101 \end{array}$$

[As derived earlier]

(Verification  $\rightarrow$ ) 
$$\begin{array}{r} +19 \rightarrow 00010011 \\ 1's \rightarrow 11101100 \\ 2's \rightarrow \begin{array}{r} +1 \\ \hline 11101101 \end{array} \end{array}$$

$$\begin{array}{r} 2 \overline{) 19} \\ \underline{2 \times 9} \rightarrow 1 \\ 2 \overline{) 9} \rightarrow 1 \\ \underline{2 \times 4} \rightarrow 0 \\ 2 \overline{) 2} \rightarrow 0 \\ \underline{2 \times 1} \rightarrow 0 \\ 0 \quad 1 \end{array}$$



Q. No. → What is the largest binary number that can be expressed with 12 bits? what is its decimal equivalent?

Ans. → (1111 1111 1111) = The largest binary no.

Its decimal equivalent =  $2^{12} - 1 = 4096 - 1 = 4095$ .

✓ 4 bit →  $2^4 - 1 = 16 - 1 = 15$

Binary Addition:

0+0 → 0

0+1 → 1

1+0 → 1

1+1 = 10

↑ Carry

1+1+1 = 11

↑ Carry  
in binary (2 is 1 unit)

Ex :-

+	1011	→ 11	Compare with decimal add <sup>n</sup>
	1111	+ 15	
		26	
11010			

In decimal (10 is 1 unit)

1
879
240
1125

✓ imp

1
11
1111
11010

Verification :-

→ 1
→ 3
→ 7
→ 15
26

2		26	
2		13	→ 0
2		5	→ 1
2		3	→ 0
2		1	→ 1
2		0	→ 1

26 = (11010)<sub>2</sub>

Binary Subtraction

- (i) Direct Subtraction
- (ii) Complement Subtraction

Direct Subtraction :-

$0 - 0 = 0$   
 $0 - 1 = 1$  , with borrow 1  
 $1 - 0 = 1$   
 $1 - 1 = 0$

Ex -

11001	→ 25	3	→ 10
- 10010	→ 18	- 297	→ 5
00101	7	38	

It will come -ve.

So subtract from the bigger no, then attach a -ve sign.

10010	-	11001	=	-(101)
-------	---	-------	---	--------

( Generally not used. We use sign magnitude, 1's complement, 2's complement method to represent -ve numbers )



$$\begin{array}{r} 1010.11 \\ - 0110.01 \\ \hline 100.10 \end{array} \quad \left. \begin{array}{l} \rightarrow 10.75 \\ \rightarrow 6.25 \\ \hline 4.50 \end{array} \right\}$$

Negative number and their representation :-

Sign magnitude :-

In sign-magnitude representation the most significant bit (MSB) is used to represent the sign.

- If MSB is 0  $\rightarrow$  +ve ✓
- MSB is 1  $\rightarrow$  -ve ✓

- Ex :-
- 0101  $\rightarrow$  +5 ✓
  - 1101  $\rightarrow$  -5 ✓

In a n bit system,

Max +ve no. that can be represented  $\rightarrow +(2^{n-1} - 1)$   
 " -ve " " " "  $\rightarrow -(2^{n-1} - 1)$

Ex :- 4 bit system

0	000	Max +ve no	$\rightarrow 1 + (2^3 - 1) = +7$
0	001	"	"
0	010	"	"
0	011	"	"
0	100	"	"
0	101	"	"
0	110	"	"
0	111	"	"
1	000	-7	---
1	001	"	"
1	010	"	"
1	011	"	"
1	100	"	"
1	101	"	"
1	110	"	"
1	111	-7	---

Disadvantage :-

- +0  $\rightarrow$  0000
- 0  $\rightarrow$  1000

} to 0 -0 have different representation although  $+0 = -0 = 0$ .

One's Complement :-

→ If a binary number, if we replace 0 by 1 & each 1 by 0, we obtain another binary number which is 1's complement of the first binary number.

→ Both the numbers are complement to each other

→ If MSB, 0 → +ve no.

→ If MSB, 1 → -ve no.

→ But magnitude of -ve no is obtained by taking 1's complement of the number.

Ex:  $+7 \rightarrow 0111$   
 $-7 \rightarrow 1000$

OR  
 To find 1's complement the no. Subtract from 1111.  

$$\begin{array}{r} 1111 \\ - 0111 \leftarrow +7 \\ \hline 1000 \leftarrow (-7) \end{array}$$

Q → What is 1000 in 1's complement?

Step 1 → Since MSB 1 → -ve number.

To find its magnitude

Step-2 → Take 1's complement

$1000 \rightarrow 0111 \rightarrow 7$

∴ The no. is -7 (Ans)

→ Max +ve no →  $+(2^{n-1} - 1)$

" -ve no →  $-(2^{n-1} - 1)$

for 4 bit +7 to -7



Disadvantage :-

In 1's Complement representation,

Zero has 2 different representation.

Actually  $+0 = -0$ , but

in 1's Complement,

$+0 \rightarrow 0000$  ✓

$-0 \rightarrow 1111$  ✓

But in 2's Complement method, it has been corrected.

2's Complement representation :-

By adding 1 to one's complement of a binary number we get the 2's complement of that binary number.

$+5 \rightarrow 0101$  ✓

1's Complement  $\rightarrow 1010$

$+ 1$   

---

 $(2's \text{ " "}) \rightarrow 1011$

$(2's) -5 \rightarrow 1011$  ✓

Q) Why is the number which has 2's Complement representation 1011.

Ans :- MSB = 1

So  
 magnitude of Actual no.  $\rightarrow$  1010  
 Complement will be 0101

①  
 a -ve no. will be 1011  

$$\begin{array}{r} 1011 \\ - 0101 \\ \hline 1010 \end{array}$$
  
 $\rightarrow$  1010

$\rightarrow$  1010  
 to  $\rightarrow$  0000  
 -0  $\rightarrow$  0000

②  
 - (0101) i.e. -5  
 0000  
 0000  
 1111  
 + 1  
 $\hline$   
 ① 0000  
 2's complement

$\rightarrow$  1010  $\rightarrow$  0101  
 + 0  $\rightarrow$  0101  
 (sum have value 0000)

① 0000  
 2's complement  
 (sum have value 0000)

$\rightarrow$  Maxm +ve no  $\rightarrow$  0111  
 Min -ve no  $\rightarrow$  1000

$\rightarrow$  +  $(2^{n-1} - 1)$   
 $\rightarrow$  -  $(2^{n-1})$

4 bit  
 Single representation

$\rightarrow$  -8 to +7  
 = =

advantage to represent

for '0' gives the

Q - What is decimal equivalent of a number, whose 2's complement is 1011

Ans:- (-5)



	Sign, magnitude	1's Complement	2's Complement
1 →	0 0 0 1	0 0 0 1	0 0 0 1
2 →	0 0 1 0	0 0 1 0	0 0 1 0
3 →	0 0 1 1	0 0 1 1	0 0 1 1
4 →	0 1 0 0	0 1 0 0	0 1 0 0
5 →	0 1 0 1	0 1 0 1	0 1 0 1
6 →	0 1 1 0	0 1 1 0	0 1 1 0
7 →	0 1 1 1	0 1 1 1	0 1 1 1
+0 →	0 0 0 0	0 0 0 0	0 0 0 0
-0 →	1 0 0 0	1's Complement 1 1 1 1	0 0 0 0
-1 →	1 0 0 1	1 1 1 0	1's +1 1 1 1 1
-2 →	1 0 1 0	1 1 0 1	1 1 1 0
-3 →	1 0 1 1	1 1 0 0	1 1 0 1
-4 →	1 1 0 0	1 0 1 1	1 1 0 0
-5 →	1 1 0 1	1 0 1 0	1 0 1 1
-6 →	1 1 1 0	1 0 0 1	1 0 1 0
-7 →	1 1 1 1	1 0 0 0	1 0 0 1
-8 →	X	X	1 0 0 0

-8 with 2's Complement

+8 → 1 0 0 0

1's Complement → 0 1 1 1

2's  

$$\begin{array}{r} 0111 \\ + 1 \\ \hline 1000 \end{array}$$

-8 → 1 0 0 0


in 2's complement method.

Advantage of 2's Complement

- 1) +0 & -0 i.e. zero has ~~two~~ single representation
- 2) We can represent one extra number (e.g.  $\rightarrow -8$  in 4 bit representation)

Complement Subtraction:

(a) 1's Complement Subtraction

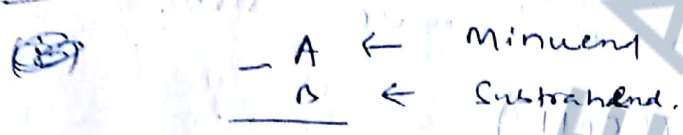

(i) Add 1's Complement of Subtrahend to the Minuend.

(ii) If there is End-Around-Carry (EAC), Remove EAC & add it to the result.

(iii) If there is no EAC, then attach a -ve sign.

Ex  $\rightarrow$

$$\begin{array}{r} 111 \\ - 100 \\ \hline \end{array}$$

Ans  $\rightarrow$  (i) 2's Complement of 100  $\rightarrow$  011

(ii)

$$\begin{array}{r} 111 \\ + 011 \\ \hline 1011 \\ \text{①} \rightarrow 1 \\ \hline 011 \text{ (Ans)} \end{array}$$



Ex:

$$\begin{array}{r} 1010 \\ - 1101 \\ \hline \end{array}$$

(i) 1's Complement of 1101  $\rightarrow$  0010

$$\begin{array}{r} 1010 \\ + 0010 \\ \hline 1100 \end{array}$$

(iii) Since no carry, re-complement it  $\underline{0011}$

and attach a -ve sign.

$$- (0011)$$

2's Complement Subtraction :-

(i) Add 2's Complement Subtrahend to the Minuend.

(ii) If there is End-Around Carry (EAC), then carry will be discarded and answer is +ve.

(iii) If no carry, then re-complement (2's) and attach a -ve sign.

$$\begin{array}{r} 110011 \\ - 100111 \\ \hline \end{array}$$

110  $\leftarrow$  001 ?

(i) 2's Complement of 100111

$$1's \rightarrow 011000$$

$$\begin{array}{r} 011000 \\ + 1 \\ \hline 011001 \end{array}$$

$$\begin{array}{r}
 (ii) \quad 110011 \\
 + 011001 \\
 \hline
 \end{array}$$

discard ←  $\textcircled{1}001100$

(iii) Ans is (001100)

ex :-

$$\begin{array}{r}
 1010 \\
 - 1101 \\
 \hline
 ?
 \end{array}$$

(i) 2's complement of 1101

$$\begin{array}{r}
 1101 \xrightarrow{1's} 0010 \\
 + 1 \\
 \hline
 0011 \xrightarrow{2's}
 \end{array}$$

(ii)

$$\begin{array}{r}
 1010 \\
 0011 \\
 \hline
 1101
 \end{array}$$

No carry

(iii) Again find 2's complement

$$\begin{array}{r}
 1101 \rightarrow \\
 1's \quad 0010 \\
 + 1 \\
 \hline
 2's \quad 0011
 \end{array}$$

Answer a -ve sign - (0011)

(Ans)



9's Complement:-

The 9's Complement of a decimal no. is obtained by subtracting each digit on the number from 9.

<u>Decimal digit</u>	<u>9's Complement</u>
0	$9 - 0 = 9$
1	$9 - 1 = 8$
2	$9 - 2 = 7$
3	$9 - 3 = 6$
4	$9 - 4 = 5$
5	$9 - 5 = 4$
6	$9 - 6 = 3$
7	$9 - 7 = 2$
8	$9 - 8 = 1$
9	$9 - 9 = 0$

ex :- Find 9's Complement of following decimal no.

- (i) 43      (ii) 122      and      (iii) 3267

(i)

$$\begin{array}{r} 99 \\ - 43 \\ \hline 56 \end{array} \quad (\text{Ans})$$

(ii)

$$\begin{array}{r} 999 \\ - 122 \\ \hline 877 \end{array} \quad (\text{Ans})$$

(iii)

$$\begin{array}{r} 9999 \\ - 3267 \\ \hline 6732 \end{array} \quad (\text{Ans})$$

23

①

9's Complement Subtraction method : - (Same as 1's Complement)

- (i) Add 9's Complement Subtrahend to the minuend.
- (ii) If there is EAC, then Carry will be added to the sum and answer is +ve.
- (iii) If there is no carry, then 9's Complement (9's) and attach a -ve sign.

ex :-

$$\begin{array}{r} 48 \\ - 24 \\ \hline ? \end{array}$$

(i) 9's Complement of 24  $\rightarrow$

$$\begin{array}{r} 99 \\ - 24 \\ \hline 75 \end{array}$$

(ii)

$$\begin{array}{r} + 48 \\ + 75 \\ \hline 123 \\ \text{①} \rightarrow 1 \\ \hline 24 \end{array} \text{ (Ans)}$$

ex :-

$$\begin{array}{r} 26 \\ - 38 \\ \hline ? \end{array}$$

(i) 38  $\rightarrow$

$$\begin{array}{r} 99 \\ - 38 \\ \hline 61 \end{array}$$

9's Complement

(ii)

$$\begin{array}{r} 26 \\ + 61 \\ \hline 87 \end{array}$$

(iii) Since no carry, 9's complement of



9's Complement

$$\begin{array}{r} 99 \\ - 87 \\ \hline 12 \end{array}$$

Attach -ve sign.  $-12$  (Ans)

10's Complement -

The 10's complement of a decimal number is obtained by adding 1 to the 9's complement of that no.

Ex:  $\underline{327} \rightarrow$  10's Complement ?

$$\begin{array}{r} 999 \\ - 327 \\ \hline 672 \\ + 1 \\ \hline 673 \end{array} \quad \text{(Ans)}$$

Subtraction Using 10's Complement : < Same as 2's Complement >

- (i) Add 10's Complement Subtrahend to the minuend.
- (ii) If there is a carry, then carry will be discarded and answer is +ve.
- (iii) If there is no carry, then recomplement (10's) and answer is -ve.

Ex:

$$\begin{array}{r} 277 \\ - 436 \\ \hline \end{array} ?$$

Step (1)

10's  
Complement

$$\begin{array}{r}
 999 \\
 - 436 \\
 \hline
 563 \\
 + 1 \\
 \hline
 564
 \end{array}$$

(ii) Add

$$\begin{array}{r}
 277 \\
 564 \\
 \hline
 841
 \end{array}$$

No carry

10's complement

$$\begin{array}{r}
 999 \\
 - 841 \\
 \hline
 158 \\
 + 1 \\
 \hline
 159
 \end{array}$$

(iii)

Attach

-ve

Sign

$$-159 \text{ (Ans.)}$$

ex:

$$\begin{array}{r}
 436 \\
 - 277 \\
 \hline
 \end{array}$$

(1)

10's Complement

of 277

$$\begin{array}{r}
 999 \\
 - 277 \\
 \hline
 722 \\
 + 1 \\
 \hline
 723
 \end{array}$$

(2)

Add

$$\begin{array}{r}
 436 \\
 723 \\
 \hline
 1159
 \end{array}$$

discard

$$\leftarrow \textcircled{1} 159$$

(3)

Ans. is

$$159$$



(1)

Binary Multiplication :-

(a)

$$\begin{array}{r}
 1101 \\
 \times 1010 \\
 \hline
 0000 \\
 1001 \\
 0000 \\
 1101 \\
 \hline
 0000010
 \end{array}$$

(Ans)

(b)

$$\begin{array}{r}
 11.01 \\
 \times 11.01 \\
 \hline
 1101 \\
 0000 \\
 1101 \\
 1101 \\
 \hline
 010.1001
 \end{array}$$

Binary Division -

$$\begin{array}{r}
 1011011 \div 111 \\
 111 \overline{) 1011011} \\
 \underline{0111} \phantom{000} \\
 1000 \\
 \underline{0111} \\
 0011 \\
 \underline{0} \\
 0011 \\
 \underline{0011} \\
 0
 \end{array}$$

$1011011 \div 111 = 1101$  (Ans)

Find x radix

(i) (431)<sub>x</sub> = (116)<sub>10</sub> → x = ?

Ans:

4x<sup>2</sup> + 3x + 1 = 116

⇒ 4x<sup>2</sup> + 3x + 1 = 116

⇒ 4x<sup>2</sup> + 3x - 115 = 0

x =  $\frac{-3 \pm \sqrt{9 - 4 \cdot (4) \cdot (-115)}}{2 \cdot 4}$

=  $\frac{-3 \pm 43}{8}$

x should be +ve,  $\frac{-3+43}{8} = \frac{40}{8} = 5$  (Ans)

Determine the base numbers

on each case for the following operations to be correct.

(i)  $\frac{17}{2} = 5$  (ii)  $\frac{54}{5} = 13$  (iii)  $24 + 17 = 40$

Ans:

i)  $\frac{(17)_x}{(2)_x} = (5)_x$

⇒  $\frac{1 \cdot x^1 + 7 \cdot x^0}{2 \cdot x^0} = 5 \cdot x^0 = 5$

⇒  $x + 7 = 2 \times 5 = 10$

⇒  $x = 10 - 7 = 3$  (Ans)



(ii)  $\frac{(54)_n}{(4)_n} = (13)_n$  ①

$\Rightarrow \frac{5 \cdot n^1 + 4 \cdot n^0}{4 \cdot n^0} = 1 \cdot n^1 + 3$

$\Rightarrow 5n + 4 = 4(n + 3) = 4n + 12$

$\Rightarrow n = 12 - 4 = 8$  (Ans)

(iii)  $(24)_n + (17)_n = (40)_n$

$\Rightarrow 2 \cdot n^1 + 4 + 1 \cdot n^1 + 7 = 4 \cdot n^1 + 0 \cdot n^0$

$\Rightarrow 2n + 4 + n + 7 = 4n$

$\Rightarrow 3n + 11 = 4n$

$\Rightarrow n = 11$  (Ans)

(iv)  $\sqrt{(14)_n} = (3)_n \Rightarrow n = ?$

Ans  $[\sqrt{(14)_n}]^2 = (3_n)^2$

$\Rightarrow (14)_n = (3_n) \cdot (3_n)$

$\Rightarrow 1 \cdot n^1 + 4 \cdot n^0 = (3 \cdot n^1) + (3 \cdot n^1)$

$\Rightarrow n + 4 = 3 \cdot 3 = 9$

$\Rightarrow \boxed{n = 5}$

verify  
 $(14)_5$   
 $= 1 \times 5^1 + 4 \cdot 5^0$   
 $= 5 + 4$   
 $= 9$   
 $\sqrt{9} = (3)_5$

# Logic Gates & Boolean Algebra

→ Logic gates perform logical operations. gates are the basic building blocks of a digital system. Basically there are 7 gates available in digital electronics, these are discussed in this section.

→ Boolean algebra, named after its pioneer George Boole, is the algebra of logic which has 2 states (0 & 1). Any digital circuit can be described using this algebra.


## Logic Gates:-

Logic gates are basic building blocks of any digital circuits. They can have one or more I/P and only one O/P. Each gate has a symbol.

- NOT, AND, OR } Basic gates
- NAND, NOR } Universal gates
- X-OR, X-NOR } Special gates

NOT gate:- IC (7404) or 74LS04

→ One I/P, one O/P.

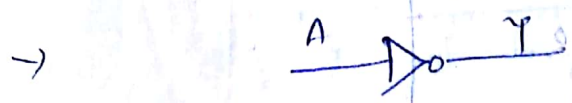


→  $Y = \bar{A}$

Truth Table

A	$Y = \bar{A}$
0	1
1	0

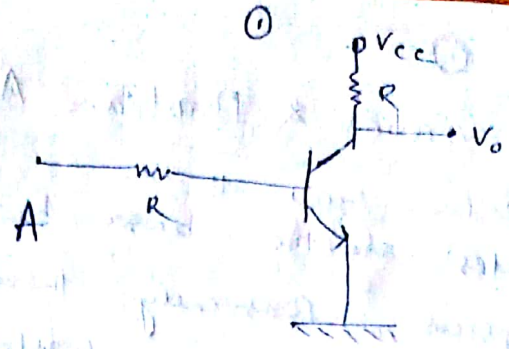→ If I/P is low O/P will be high. If I/P is high O/P is low.






If  $A=1$ , transistor conducts, o/p short circuited,

$V_0 =$  gnd. potential = 0.

If


$A=1, Y=0$

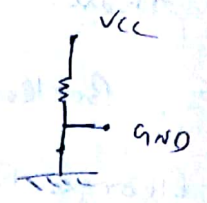

If  $A=0$ , transistor is off,

$V_0 = V_{cc} = 1$

$A=0, Y=1$

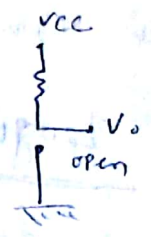

AND gate :- (74 LS 08)

→ Many i/p → one o/p.


→  $Y = A \cdot B$  ✓



→

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

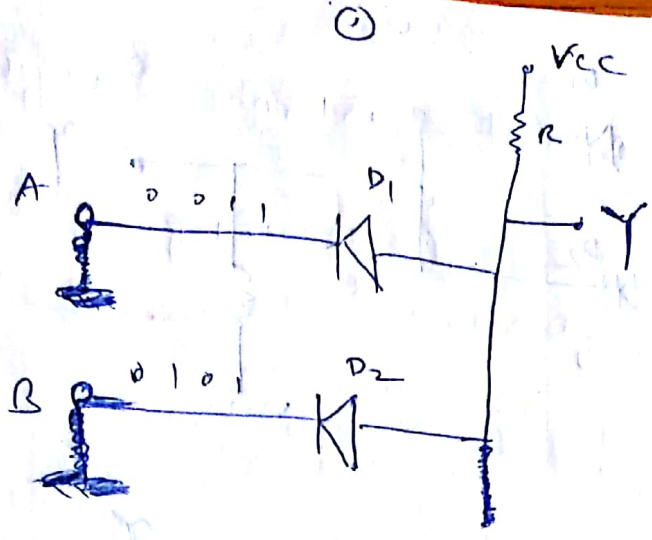→ The o/p of AND gate is high if all i/p's are high.



A	B	D <sub>1</sub>	D <sub>2</sub>	Y
0	0	on	on	0
0	1	on	off	0
1	0	off	on	0
1	1	off	off	1

OR Gate :- (74LS 32)


→ Many i/p → one o/p.

→  $Y = A + B$


→

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

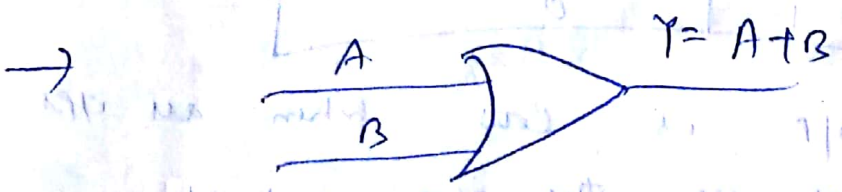→ The o/p of OR gate is high if any or all i/p's are high.





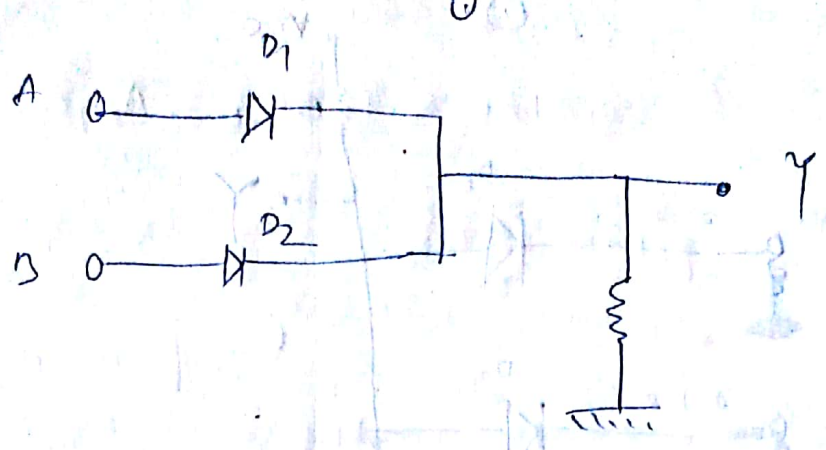


A	B	D <sub>1</sub>	D <sub>2</sub>	Y
0	0	off	off	0
0	1	off	on	1
1	0	on	off	1
1	1	on	on	0

NAND gate: (TTL500)


→ Many i/p one o/p.

→  $Y = \overline{AB}$

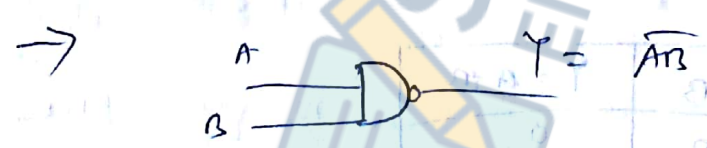

A	B	Y = $\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

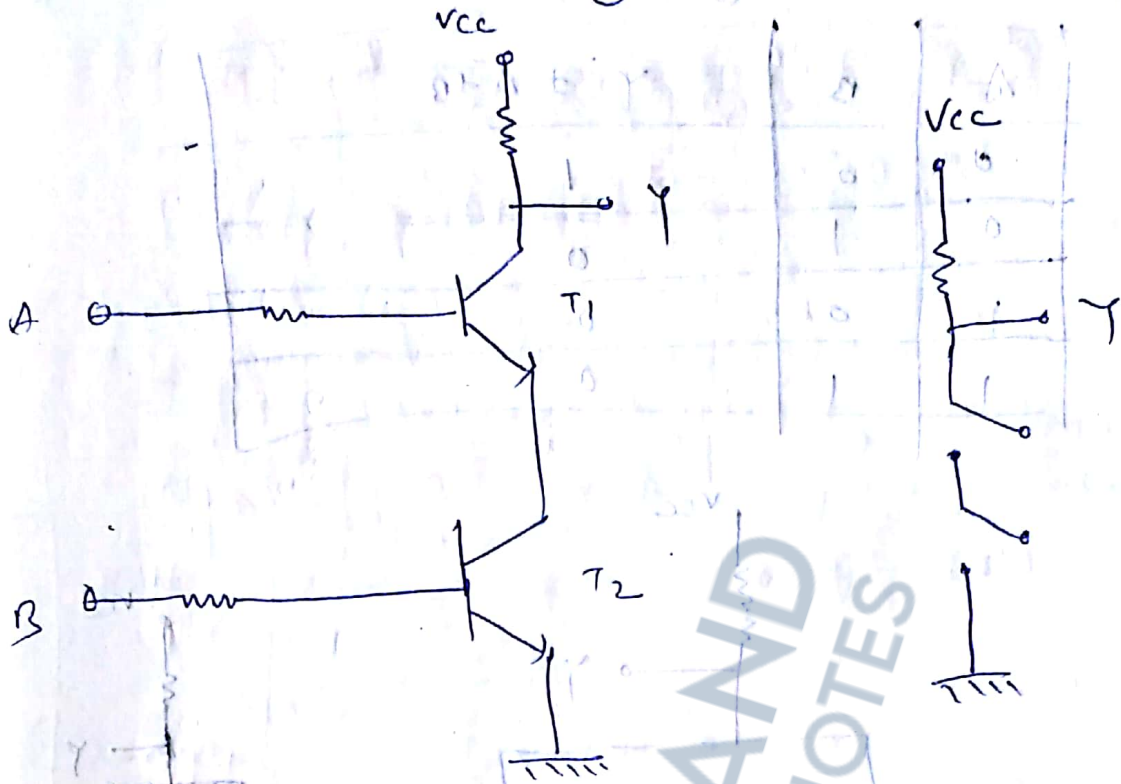→ The o/p is low when all i/p are high, otherwise the o/p is high.




A	B	T <sub>1</sub>	T <sub>2</sub>	Y
0	0	off	off	1
0	1	off	on	1
1	0	on	off	1
1	1	on	on	0

NOR Gate (74 LS 02)

→ Many I/P one O/P.


→  $Y = \overline{A+B}$

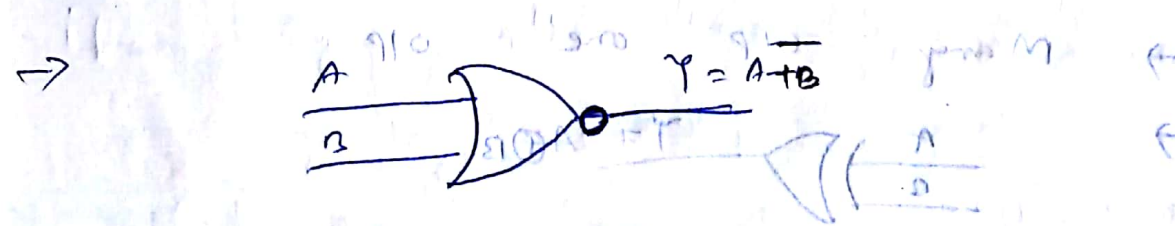

$\overline{A+B} = \overline{A} \cdot \overline{B}$



A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	0

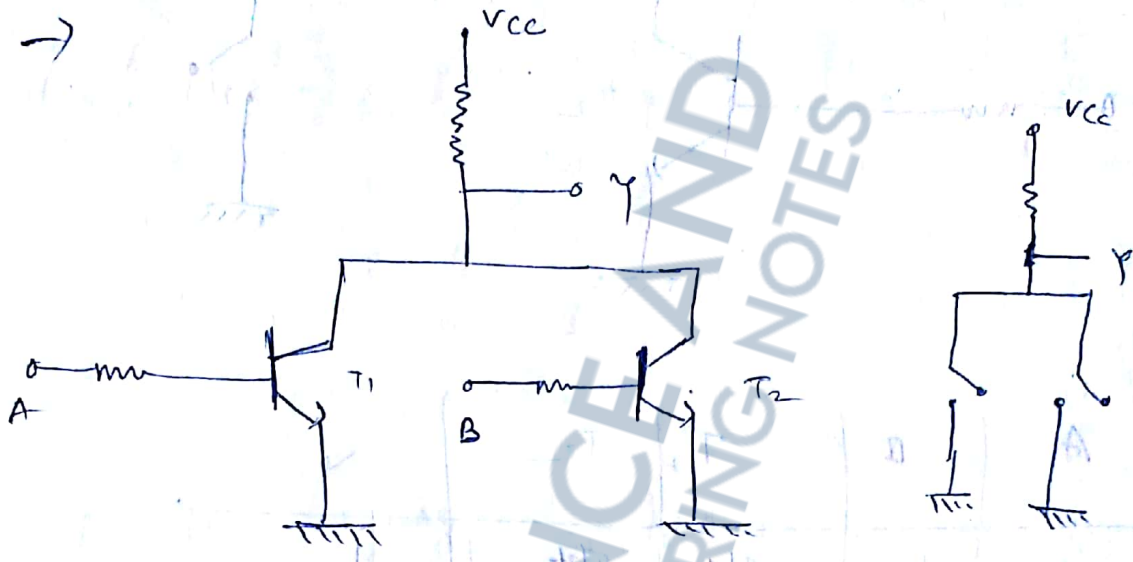

A	B	$T_1$	$T_2$	Y
0	0	off	off	1
0	1	off	on	0
1	0	on	off	0
1	1	on	on	0

EX-OR Gate :- (74LS86)

→ Many CIP one OIP




→  $Y = A \oplus B = A\bar{B} + \bar{A}B$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

→ The gate produces a high when inputs have odd no. of 1's.

EX-NOR (74LS266)

→ Many clip one of

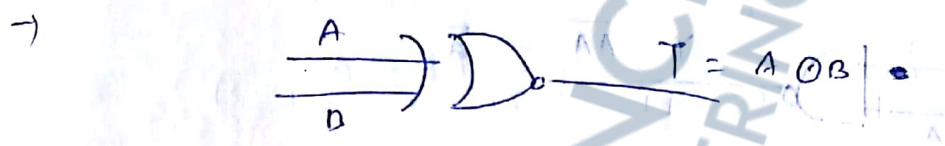

→  $A \oplus B = \overline{A}B + A\overline{B}$

A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

→ The output of X-NOR is high when inputs have even no. of 1's or even no. of 0's.

→ X-NOR gate is also known as Equivalence function.



# Universal Gates:-

→ NAND & NOR gates are called universal gates because both can be used to implement any logic gate or any logic expression.

## NAND as universal gate:-

### (1) NOT gate

$$Y = \bar{A}$$



A	B	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

Boolean Algebra should be taught before showing universal gates. Because the o/p of any gate can be simplified by boolean algebra.

## Boolean Algebra:- (Mathematics of digital system)

### ✓ Duality principle

It states that any boolean expression has a dual form which can be obtained as following 2 steps:-

- (a) Replace OR operation by AND operation.
- (b) Replace AND operation by OR operation.
- (c) Replace 1 by 0 & 0 by 1.

Q. Find dual of  $F = 1.A + \bar{B}.0 + C\bar{A}$

Ans =  $F = 1(0+A) + (\bar{B}+1) \cdot (C+\bar{A})$

Laws of Boolean Algebra

1) Commutative law

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

2) Associative law

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

3) Distributive law

Distributive law of addition

$$A \cdot (B + C) = AB + AC$$

Distributive law of multiplication

$$A + B \cdot C = (A + B) \cdot (A + C)$$

Theorems / Rules of Boolean Algebra :-

Then 1 (a)  $0 \cdot A = 0$  <sup>and</sup>

(b)  $1 + A = 1$  <sup>or</sup>

(b) is dual form of (a).

Note :-

- $\rightarrow$  Intersection
- +  $\rightarrow$  Union
- 0  $\rightarrow$   $\phi$  = Null set
- 1  $\rightarrow$  U = Universal set



Theorem

2 (a)

$1. A = A$

$1. 0 = 0$   
 $1. 1 = 1$   
 $1. A = A$

(A + B)

(b)

$0 + (A) = A$

Theorem

3 (a)

$A \cdot A = A$

$\rightarrow$  Intersecting  
 $\rightarrow$  Union

(b)

$A + A = A$

Theorem

4 (a)

$A \cdot \bar{A} = 0$

4 (b)

$A + \bar{A} = 1$

Theorem

5 (a)

$A + AB = A$

5 (b)

$A \cdot (A + B) = A$

Proof

5 (a)

$L.H.S = A + AB$

$= A(1 + B)$

$= A \cdot 1$

$= A \quad (R.H.S)$

(b)

$A \cdot (A + B)$

$= A \cdot A + A \cdot B$

$= A + AB$

$= A(1 + B)$

$= A \cdot 1$

$= A$

Theorem

6 (a)

$A + BC = (A + B)(A + C)$

$$\begin{aligned}
 & (A+B)(A+C) \\
 &= A \cdot A + A \cdot C + B \cdot A + B \cdot C \\
 &= A + A(C+B) + BC \\
 &= A[1 + (C+B)] + BC
 \end{aligned}$$

$$\begin{aligned}
 &= A \cdot 1 + BC \quad \because 1 + (C+B) = 1 \\
 &= A + BC
 \end{aligned}$$

(b)  $A \cdot (B+C) = AB + AC$  (Distributive law)

7.  $\overline{\overline{A}} = A$

DeMorgan's Theorem

(i)  $\overline{A+B} = \overline{A} \cdot \overline{B}$

(ii)  $\overline{AB} = \overline{A} + \overline{B}$

(i) The complement of sum of 2 or more variables is equal to the product of the complement of the variables.

(ii) The complement of the product of 2 or more variables is equal to the sum of the complement of the variables.

The above theorem can be proved by the help of truth table.

The above theorem can be proved by the help of truth table.



A	B	$\bar{A} \cdot B$	$A \cdot \bar{B}$	$A \cdot B$	$A + B$	$\overline{A \cdot B}$	$\overline{A + B}$	$\overline{A \cdot B}$	$\overline{A + B}$
0	0	1	1	0	0	1	1	1	1
0	1	1	0	0	1	1	1	0	0
1	0	0	1	0	1	1	1	0	0
1	1	0	0	1	1	0	0	0	0

From the above table, we proved that

(i)  $\overline{A + B} = \bar{A} \cdot \bar{B}$

(ii)  $\overline{A \cdot B} = \bar{A} + \bar{B}$

SL no	Thems.	Dual Rel <sup>n</sup>
1	$A + 0 = A$	$A \cdot 1 = A$
2	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
3	$A + A = A$	$A \cdot A = A$
4	$A + 1 = 1$	$A \cdot 0 = 0$
5	$\bar{\bar{A}} = A$	$\bar{\bar{A}} = A$
6	$A + B = B + A$	$A \cdot B = B \cdot A$
7	$A + (B \cdot C) = (A + B) \cdot C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
8	$A(B + C) = AB + AC$	$A + BC = (A + B)(A + C)$
9	$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{\bar{A} + \bar{B}} = A \cdot B$
10	$A + \bar{A} \cdot B = A + B$	$A \cdot (\bar{A} + B) = A \cdot B$

### Universal gates:

→ NAND & NOR gates are called

universal gates because both can be used

to implement any logic gates or any


logic expression.

NAND as universal gate



$$Y = \overline{AB}$$

(i) NOT Gate


$$Y = \overline{A}$$

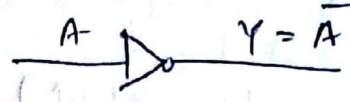

(ii) AND Gate

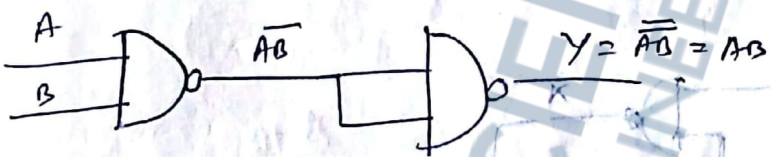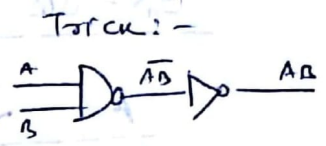

(iii) OR Gate


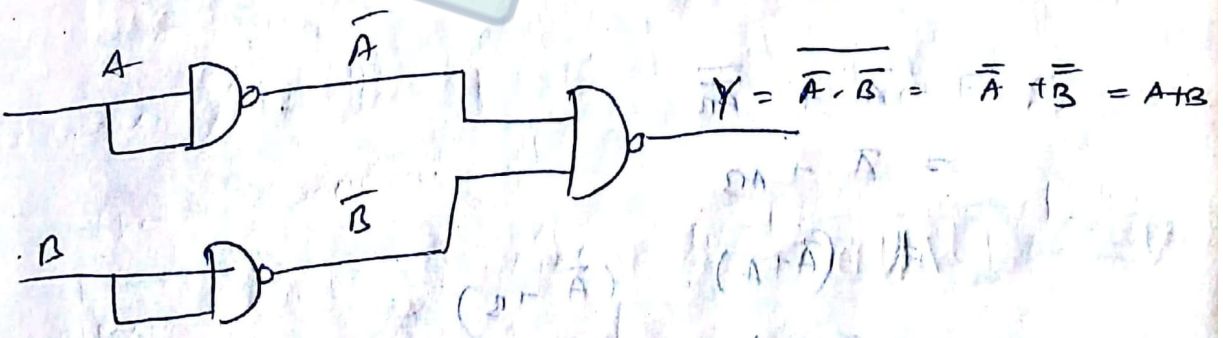


$$Y = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}} = A + B$$



$$A + \overline{A} = X$$



(iv) NOR gate

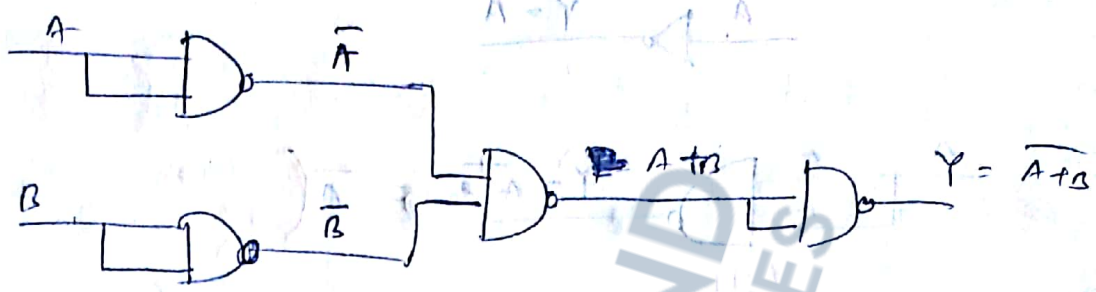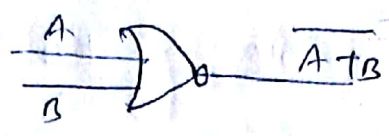

(v) EX-OR gate

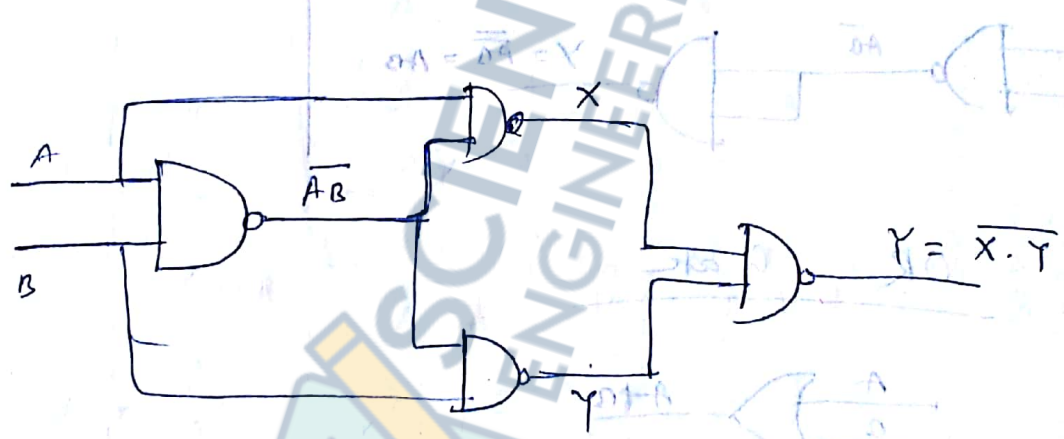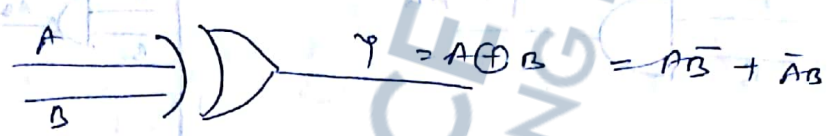

$$X = A \cdot \overline{B}$$

$$\overline{A+B} = \overline{A} + \overline{B}$$

$$= \overline{A} + \overline{B}$$

$$= (\overline{A} + A) \cdot (\overline{A} + B)$$

$$= 1 \cdot (\overline{A} + B)$$

$$X = \overline{A} + B$$

$Y = \overline{A \cdot B}$

$\overline{A \cdot B} \cdot B$

$= \overline{A \cdot B} + \overline{B}$

$= AB + \overline{B}$

$= \overline{B} + AB$

$= (\overline{B} + A) (\overline{B} + B)$

$= (\overline{B} + A) \cdot 1$

$= \overline{B} + A$

$Y = \overline{X \cdot Y}$

$= \overline{(\overline{A} + B) \cdot (\overline{B} + A)}$


$= \overline{\overline{A} \cdot \overline{B} + \overline{A} \cdot A + B \cdot \overline{B} + AB}$

$= \overline{\overline{A} \cdot \overline{B} + AB}$


$= \overline{A \oplus B}$

$Y = A \oplus B$  (Proved)

(vi) X-NOR gate

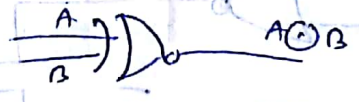


using NAND

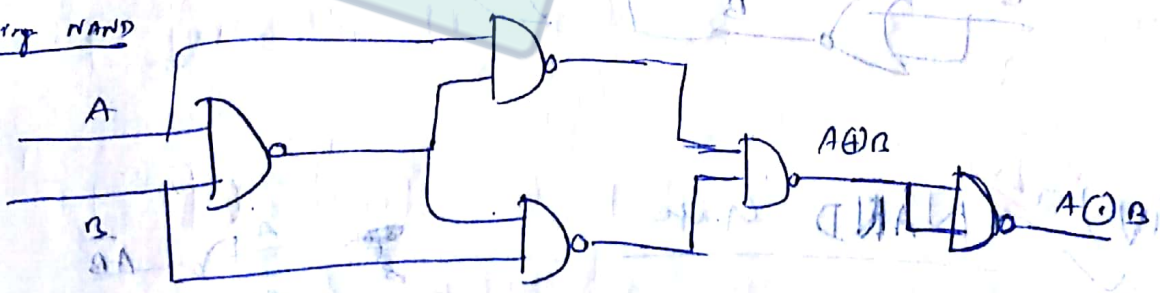




# NOR as universal gate:-


(i) NOT gate:-

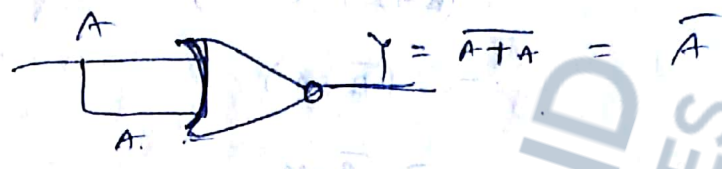


(ii) OR Gate:-

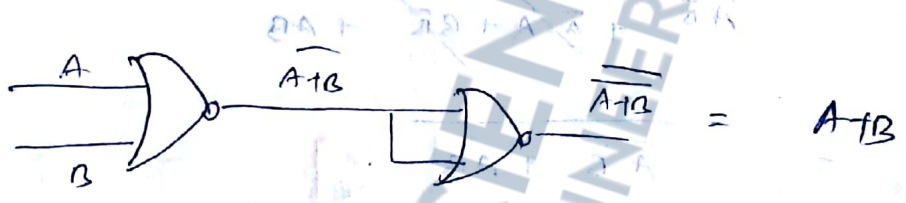

(iii) AND gate:-

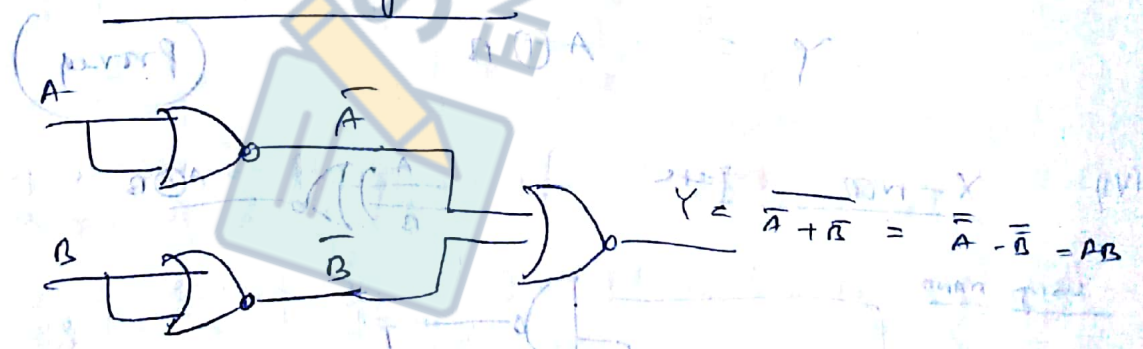


(iv) NAND gate

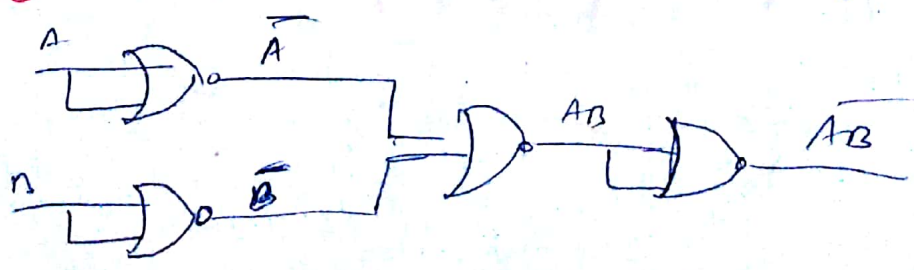

(N) EX-NOR gate

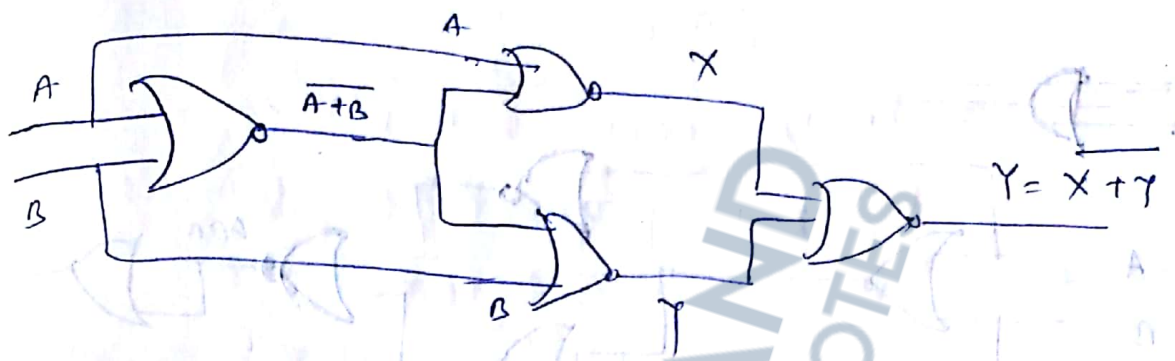$A \oplus B = \overline{A}B + A\overline{B}$



$X = \overline{A + \overline{A+B}}$  (Key)

$= \overline{A} \cdot \overline{\overline{A+B}}$

$= \overline{A} \cdot (A+B)$

$= \overline{A} \cdot A + \overline{A}B$

$= \overline{A}B$

$Y = \overline{B + \overline{A+B}}$

$= (\overline{B}) \cdot \overline{\overline{A+B}}$

$= (\overline{B}) \cdot (A+B)$

$= \overline{B}A + \overline{B}B$



$= \overline{B}A$

$Y = \overline{X + Y} = \overline{\overline{A}B + \overline{B}A} = \overline{\overline{A}B + \overline{B}A} = A \oplus B = A \odot B$

(Proved)




(vi) Ex-OR Gate

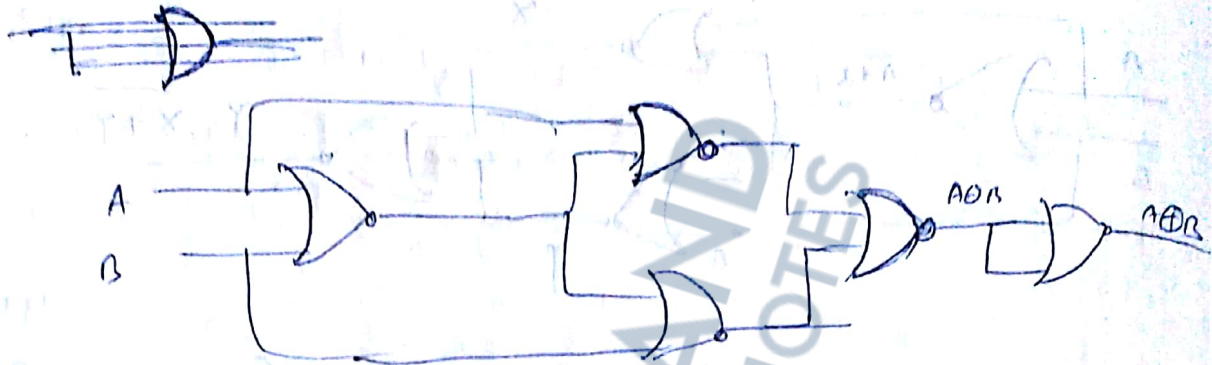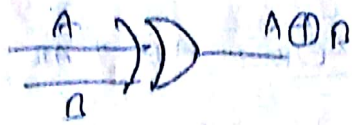

Draw X-or gate using basic gates

$$Y = A \oplus B = A\bar{B} + \bar{A}B$$

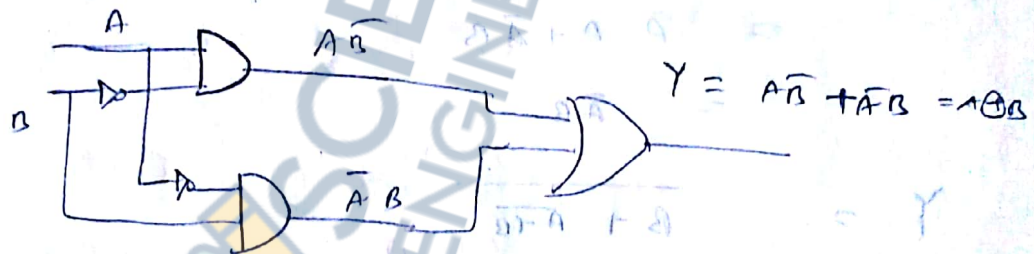

Standard Forms of Boolean Expression:-

There are 2 forms of Boolean expressions;

These 2 forms are

(i) SOP (Sum of the Product) form.

(ii) POS (Product of the Sum) form.

(2020/21)

## SOP form

This is an expression in which AND terms (product) are ORed (summed) together.

Ex:-  $F = \bar{A}BC + ABC + A\bar{B}C + ABC$

## POS form

This is an expression in which OR terms are ANDed (product) together.

Ex:-  $F = (A+B)(\bar{C}+D)(\bar{D}+A)$

## Conversion of a General expression to SOP form

Any logic expression can be changed to SOP form by applying Boolean Algebra technique

Ex-1,  $A(B+CD) = AB + ACD$

Ex-2  $A\bar{B} + B(CD + \bar{C}\bar{E}F)$   
 $= A\bar{B} + BCD + B\bar{C}\bar{E}F$

Ex-3:

$$\overline{(A+B)} + C$$

$$= \overline{(A+B)} \cdot \bar{C}$$

$$= \overline{(A+B)} \cdot \bar{C}$$

$$= \bar{A}\bar{B} + \bar{B}\bar{C} \quad (\bar{A}+\bar{B})(\bar{C})$$



The standard SOP form:- [Canonical form]

A standard SOP expression is one in which all the variables in the domain appear in the each product term.

Step-1: - Multiply each non standard product term by a term made up of sum of a missing variable and its complement. This results in 2 product terms.

Step 2: - Repeat step I, until all resulting product terms contain all variables in the domain in either complemented or uncomplemented form.

Ex:  $A\bar{B}C + \bar{A}B + AB\bar{C}D$

We know

$$A + \bar{A} = 1$$

$$B + \bar{B} = 1$$

$$(C + \bar{C}) = 1$$

$$D + \bar{D} = 1$$

$$\therefore A\bar{B}C(D + \bar{D}) + \bar{A}B(C + \bar{C})(D + \bar{D}) + AB\bar{C}D$$

~~$$= \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} +$$~~

Consider

$$(1) A\bar{B}C(D + \bar{D}) = A\bar{B}CD + A\bar{B}C\bar{D}$$

$$(2) \bar{A}B(C + \bar{C})(D + \bar{D})$$

$$= (\bar{A}B\bar{C} + \bar{A}B\bar{C}) (D + \bar{D})$$

$$= \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

(3)  $AB\bar{C}D$  ... contains 4 variables.

Finally

$$A\bar{B}C + \bar{A}B + AB\bar{C}D$$

$$= A\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D}$$

Binary representation of a standard SOP form -

Ex: If  $A\bar{B}.C.D = 1$ , what is  $\underline{ABCD}$ ?

Ans:  $A\bar{B}.C\bar{D} = 1$

Since their product is 1, individual terms must be 1. If any one would have zero, then their product would be zero.

$$\begin{aligned} A &= 1 \\ \bar{B} &= 1 \Rightarrow B = 0 \\ C &= 1 \\ \bar{D} &= 1 \Rightarrow D = 0 \end{aligned}$$

$ABCD = 1010$

Imp

A SOP expression is equal to 1 only if one or more of the product terms on the expression is equal to 1.

(Because  $A \cup 1 = 1$ ) (At least one expression = 1) (e.g.  $0 \cup 1 = 1, 0 \cup 1 \cup 1 = 1$ )



The Standard POS form (Canonical POS form)

A standard POS expression is one in which all the variables in the domain appear in each sum term in the expression.

Steps

1. Add to each nonstandard product term a term made up of the product of the missing variable and its complement. This results in 2 sum terms. (because we can add onto anything without changing its value).
2. Apply the rule  $A+BC = (A+B)(A+C)$
3. Repeat step 1 until all resulting sum terms contain all variables in the domain in either complemented or uncomplemented form.

Ex: <sup>Start</sup> Convert the following Boolean expression into standard POS form.

$$(A+B+C) (\bar{B}+C+\bar{D}) (A+\bar{B}+\bar{C}+D)$$

Ans:

$$A+B+C = \frac{A+B+C+DD}{A \quad B \quad C}$$

$$= (A+B+C+D) (A+B+C+\bar{D})$$

$DD=0$ , we can add.

$$A+B+C = (A+B)(A+C)$$

$$\bar{B}+C+\bar{D} = A\bar{A} + \bar{B} + C + \bar{D}$$

$$= \overline{B+C+D} + A\overline{A}$$

$$= (\overline{B+C+D} + A) (\overline{B+C+D} + \overline{A})$$

→  $(A+B+C+D)$  if contains all the variables.

∴ Prinally

$(A+B+C) (\overline{B+C+D}) (A+B+C+D)$  can be converted into standard POS form as

$$= (A+B+C+D) (A+\overline{B+C+D}) (\overline{B+C+D} + A) (\overline{B+C+D} + \overline{A})$$

$$= (A+B+C+D) (A+\overline{B+C+D}) (A+\overline{B+C+D}) (\overline{A+B+C+D})$$

Converting Standard SOP to Standard POS

Step 1: Evaluate each product term in the SOP expression. That is, determine the binary numbers that represent the product term.

Step 2: Determine all of the binary numbers not included in the evaluation of step 1.

Step 3: Write the equivalent sum term for each binary number from step 2 and expression in



Ex:-

$$\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C}$$

Ans:

SOP

$$000 + 010 + 011 + 101 + 111$$

$$0, 2, 3, 5, 7$$

So left 1, 4, 6

$$001, 100, 110$$

~~$$(\overline{A} + \overline{B} + \overline{C})$$~~

POS

$$(A + B + \overline{C}) (\overline{A} + B + C) (\overline{A} + \overline{B} + C)$$

In

POS

form

$$0 \rightarrow A$$

$$1 \rightarrow \overline{A}$$

In

SOP

form

$$0 \rightarrow \overline{A}$$

$$1 \rightarrow A$$

- Q) Convert POS to SOP  $(A+B+C)(\overline{A}+B+C)(\overline{A}+\overline{B}+C) \rightarrow ?$  SOP
- Q) Convert  $\overline{A}B + A\overline{B} = ?$  into POS.

→ A POS expression is equal to 0 only if one or more of sum terms in the expression are equal to 0

Ex Determine the binary value of the variables for which following POS

a) expression is equal to 0.

$$(A+B+C+D) (A+\bar{B}+C+D) (\bar{A}+B+C+\bar{D})$$

Ans: The total expression = 0, if any one of them is 0.

If  $A+B+C+D = 0 \Rightarrow A=0, B=0, C=0, D=0$

If  $A+\bar{B}+C+D = 0 \Rightarrow A=0, B=1, C=0, D=0$

If  $\bar{A}+B+C+\bar{D} = 0 \Rightarrow A=1, B=1, C=1, D=1$

Min term

~~Min~~ Minterm is a product term

which contains all the variables either in true form or complement form.

~~(2m)~~  $F(A, B, C) = ABC + \bar{A}BC + B\bar{C} + A\bar{C}$

00	(5) 1 1 1	1	0	0
01	(5) 1 1 0	1	0	0
10	(5) 1 0 1	0	1	0
11	(5) 1 0 0	1	1	0
21	(5) 0 1 1	0	0	1
20	(5) 0 1 0	1	0	1
31	(5) 0 0 1	0	0	1
30	(5) 0 0 0	0	0	0

2<sup>n</sup> min terms.   
 4 → 2<sup>2</sup> → 16 min terms.

Minimal SOP form - It is an SOP expression containing min product term which cannot be further simplified.



Max term:

Maxterm is sum term which contains all the variables given in the expression either in true form or in complement form.

Ex.  $F(A, B, C) = (A+B+C)(B+\bar{C})$

Minimal POS form is a POS expression containing min sum term which can't be further simplified.

Min term & Max term representation

For 3 variables binary variable function, we have  $2^3 = 8$  min terms as well as max terms.

$x$ $y$ $z$	min term ( $m_i$ )	Max term ( $M_j$ )
0 0 0	$\bar{x}\bar{y}\bar{z}$ ( $m_0$ )	$(x+y+z) M_0$
0 0 1	$\bar{x}\bar{y}z$ ( $m_1$ )	$(x+y+\bar{z}) M_1$
0 1 0	$\bar{x}y\bar{z}$ ( $m_2$ )	$(x+\bar{y}+z) M_2$
0 1 1	$\bar{x}yz$ ( $m_3$ )	$(x+\bar{y}+\bar{z}) M_3$
1 0 0	$x\bar{y}\bar{z}$ ( $m_4$ )	$(\bar{x}+y+z) M_4$
1 0 1	$x\bar{y}z$ ( $m_5$ )	$(\bar{x}+y+\bar{z}) M_5$
1 1 0	$xy\bar{z}$ ( $m_6$ )	$(\bar{x}+\bar{y}+z) M_6$
1 1 1	$xyz$ ( $m_7$ )	$(\bar{x}+\bar{y}+\bar{z}) M_7$

Q.2

→ For  $n$  input variables we have  $2^n$  mms as well as 2 max terms.

→ Min term is a product term whose value equal to 1 i.e denoted by

$\sum_{i=0}^{2^n-1} m_i = 1$ , i.e either of them 1.

e.g

$f(A, B, C) = \sum (0, 2, 4, 6)$

$= 000 + 010 + 100 + 110$

$= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + AB\overline{C}$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

→ Find the truth table?

→ Max term is a sum term whose value equal to 0, i.e denoted by

$\prod_{i=0}^{2^n-1} M_i = 0$ , i.e either of them is 0.

Find the truth table.

e.g

$F(A, B, C) = \prod (0, 2, 4, 7)$

$= (000) (010) (100) (111)$

~~$(\overline{A}\overline{B}\overline{C})$~~

$= (A+B+C) (A+B+\overline{C}) (\overline{A}+B+C) (\overline{A}+\overline{B}+\overline{C})$

→ Min term & max term are complement to each other.

$\sum (0, 2, 4, 6) = \prod (1, 3, 5, 7)$



Ex - 1  $\rightarrow$  minimization, (Simplify the following expression)

(i)  $ABC + A\bar{B}C + AB\bar{C}$

Ans:

$$\begin{aligned}
 & ABC + A\bar{B}C + AB\bar{C} \\
 &= AB(C + \bar{C}) + A\bar{B}C \\
 &= AB \cdot 1 + A\bar{B}C \\
 &= AB + A\bar{B}C \\
 &= A(B + \bar{B}C) \\
 &= A[(B + \bar{B}) \cdot (B + C)] \\
 &= A[1 \cdot (B + C)] \\
 &= A(B + C) \\
 &= AB + AC
 \end{aligned}$$

formula  
 $A + BC = (A + B)(A + C)$

(Ans)  $\rightarrow$  (Minimized expression)

(ii)  $(A + \bar{B} + C)(\bar{A}B\bar{C}D)$

$$\begin{aligned}
 &= A \cdot (\bar{A}B\bar{C}D) + \bar{B} \cdot \bar{A}B\bar{C}D + C \cdot \bar{A}B\bar{C}D \\
 &= 0 + 0 + 0 \\
 &= 0
 \end{aligned}$$

$A\bar{A} = 0$   
 $B\bar{B} = 0$   
 $C\bar{C} = 0$

(iii)  $\bar{x}\bar{y}z + yz + xz$

$$\begin{aligned}
 &= \bar{x}\bar{y}z + z(xy) \\
 &= z[\bar{x}\bar{y} + xy] \\
 &= z[(\bar{x}\bar{y}) + xy]
 \end{aligned}$$

$$\begin{aligned}
 &= Z \cdot [1] \\
 &= Z \quad (\text{Ans})
 \end{aligned}$$

$$1 + \bar{A} = 1$$

(iv)

$$AB + \bar{B}C + AC$$

~~$$A(B+C) + \bar{B}C$$~~

$$= AB + \bar{B}C + AC \cdot 1$$

$$= AB + \bar{B}C + AC(B + \bar{B})$$

$$= \overbrace{AB} + \overbrace{\bar{B}C} + \overbrace{ABC} + \overbrace{A\bar{B}C}$$


$$= AB(1+C) + \bar{B}C(1+A)$$

$$= AB + \bar{B}C + 0 + 0$$

See  $AB + \bar{B}C + AC = AB + \bar{B}C$   
 one term is eliminated (i.e.  $AC$ )

Trick:- See one term is complemented i.e.  $\bar{B}C$   
 for ans. keep the complemented term & its  
 corresponding uncomplemented term, eliminate the  
 other one.

$$AB + \bar{B}C + AC$$

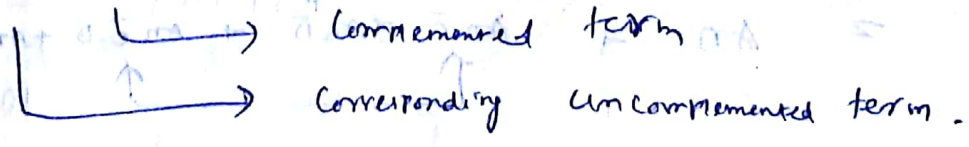

Keep these two.

$$\text{Ans} \rightarrow AB + \bar{B}C$$



$$= Z \cdot [1]$$

$$= Z$$

(Ans)

$$A + \bar{A} = 1$$

(iv)

$$AB + \bar{B}C + AC$$

$$= AB + \bar{B}C + AC \cdot 1$$

$$= AB + \bar{B}C + AC(B + \bar{B})$$


$$= AB + \bar{B}C + ABC + A\bar{B}C$$

$$= AB(1 + C) + \bar{B}C(1 + A)$$

$$= AB + \bar{B}C$$

See  $AB + \bar{B}C + AC = AB + \bar{B}C$   
 one term is eliminated (i.e. AC)

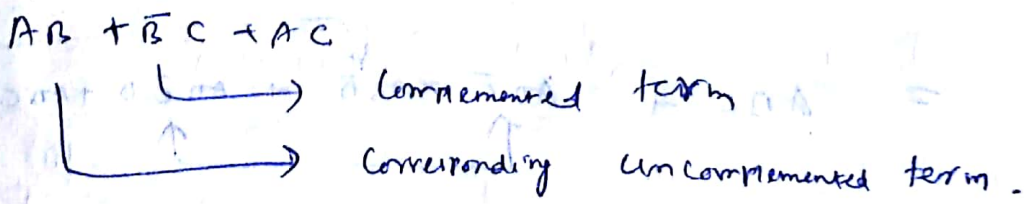Trick:- See one term is complemented i.e.  $\bar{B}C$   
 for ans. keep the complemented term & its  
 corresponding uncomplemented term, eliminate the  
 other one.



Keep these two.

Ans  $\rightarrow AB + \bar{B}C$

(v) Prove

$$AB + \bar{A}C + BC = AB + AC$$

Ans:

$$\begin{aligned} & AB + \bar{A}C + BC \cdot 1 \\ &= AB + \bar{A}C + BC(A + \bar{A}) \\ &= AB + \bar{A}C + ABC + \bar{A}BC \\ &= AB(1 + C) + \bar{A}C(1 + B) \\ &= AB + AC \end{aligned}$$

(vi) Prove

$$AB + B\bar{C} + AC = B\bar{C} + AC$$

(vii) Prove that

$$ABCD + AB\bar{C}D + ABC\bar{D} + ABCDE + AB\bar{C}DE + ABCDE$$

Ans:-

$$\begin{aligned} & ABCD + AB(\bar{C}D) + ABC\bar{D} + AB\bar{C}D \\ &+ ABCDE + AB\bar{C}DE \\ &= ABC(D + \bar{D}) + AB(\bar{C} + D) + AB\bar{C}D \\ &+ ABCDE + AB\bar{C}DE \\ &= ABC + AB\bar{C} + TAB\bar{D} + AB\bar{C}D + ABCDE + AB\bar{C}DE \\ &= ABC + AB\bar{C}(1 + D) + AB\bar{D}(1 + E) + ABCDE \\ &= ABC + AB\bar{C} + AB\bar{D} + ABCDE \end{aligned}$$



$$ABC(1+DE) + AB\bar{C} + A\bar{B}D$$

$$= ABC + AB\bar{C} + A\bar{B}D$$

$$= AB(C + \bar{C}) + A\bar{B}D$$

$$= AB + A\bar{B}D$$

$$= AB(1+D)$$

$$= AB$$

(Ans)

Prove that

(ii)

$$\overline{AB + BC + CA} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}$$

$$= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}$$

Proof:

$$\overline{AB + BC + CA}$$

$$= \bar{A}\bar{B} \cdot \bar{B}\bar{C} \cdot \bar{C}\bar{A}$$

Demorgan's theorem

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{C} + \bar{A})$$

multiply

Again Demorgan's theorem

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{B} + \bar{B}\bar{C}) (\bar{A} + \bar{C})$$

$$= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B} + \bar{B}\bar{C}) (\bar{A} + \bar{C})$$

~~$$= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}) (1 + \bar{C})$$~~

$$= [\bar{B} (1 + \bar{A} + \bar{C}) + \bar{A}\bar{C}] (\bar{A} + \bar{C})$$

$$= [\bar{B} + \bar{A}\bar{C}] (\bar{A} + \bar{C})$$

$$= \bar{B}\bar{A} + \bar{B}\bar{C} + \bar{A}\bar{C}\bar{A} + \bar{A}\bar{C}\bar{C}$$

$$= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}\bar{C}$$

$A \cdot A = A$   
 $A + 0 = A$

$$AB + BC + CA = (\overline{A} \overline{B} + \overline{B} \overline{C} + \overline{A} \overline{C}) \quad \left. \begin{array}{l} \therefore A + A = A \\ \text{(proved)} \end{array} \right\}$$

Alternative Method for Converting SOP  $\rightarrow$  POS

- 1) Take the complement of given SOP expression & expand using DeMorgan's theorem.
- 2) Simplify the above expression using the Boolean algebra.
- 3) Take once again complement of the simplified expression obtained in step 2, to get the POS form.

Ex:  $F = AB + \overline{A}B$

Step 1

$$\overline{F} = \overline{AB + \overline{A}B}$$

$$= \overline{AB} \cdot \overline{\overline{A}B}$$

$$= (\overline{A} + \overline{B}) (\overline{\overline{A}} + \overline{B})$$

$$= (\overline{A} + \overline{B}) (A + B)$$

Step 2

$$\overline{\overline{F}} = \overline{(\overline{A} + \overline{B})(A + B)}$$

$$= \overline{\overline{A} + \overline{B}} \cdot \overline{A + B}$$

$$= (A \cdot B) (\overline{A} \cdot \overline{B})$$

$$= AB + \overline{A} \overline{B}$$

Step 3

$$\overline{\overline{\overline{F}}} = \overline{AB + \overline{A} \overline{B}}$$

$$= \overline{AB} \cdot \overline{\overline{A} \overline{B}}$$

$$= (\overline{A} + \overline{B}) (\overline{\overline{A}} + \overline{\overline{B}})$$

$A = \overline{\overline{A}}$   
 $\overline{A} = \overline{A + A}$

$$F = (\overline{A} + \overline{B})(A + B) \quad \text{POS form}$$



# POS $\rightarrow$ SOP

Step 1: Expand the POS expression

Step 2: Simplify using the laws of Boolean algebra.

Ex:  $F = (\bar{A} + \bar{B})(A + B)$

Step 1:


$$F = \bar{A} \cdot A + \bar{A} \cdot B + \bar{B} \cdot A + \bar{B} \cdot B$$

$$= \bar{A}B + A\bar{B}$$

Step 2: (SOP form)

Q) Design  $A + BC$  using NAND/NOR

Digital waveform:-

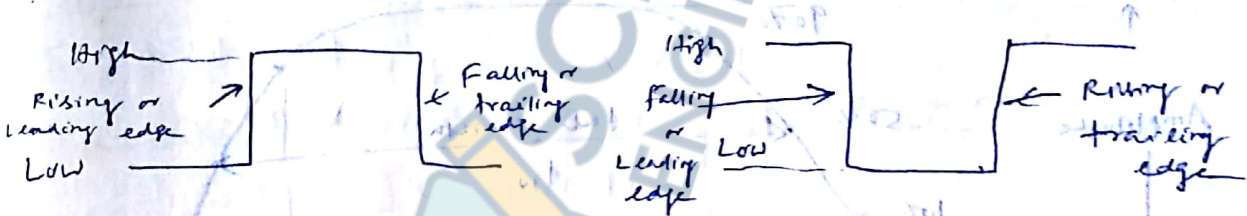

(a) +ve going pulse

(b) -ve going pulse

$\rightarrow$  A positive going pulse is generated when the voltage (current) goes from its normally low level to its high & then back to low level.


$\rightarrow$  A -ve going pulse is generated when the voltage goes from its normally high level to its low level & back to high level.

$t_r$  (Rise time)

The time required for the pulse to go from low level to high level is called rise time ( $t_r$ ). Practically, it is the measure of time from 10% of pulse amplitude to 90% of pulse amplitude.

$t_f$  (Fall time)

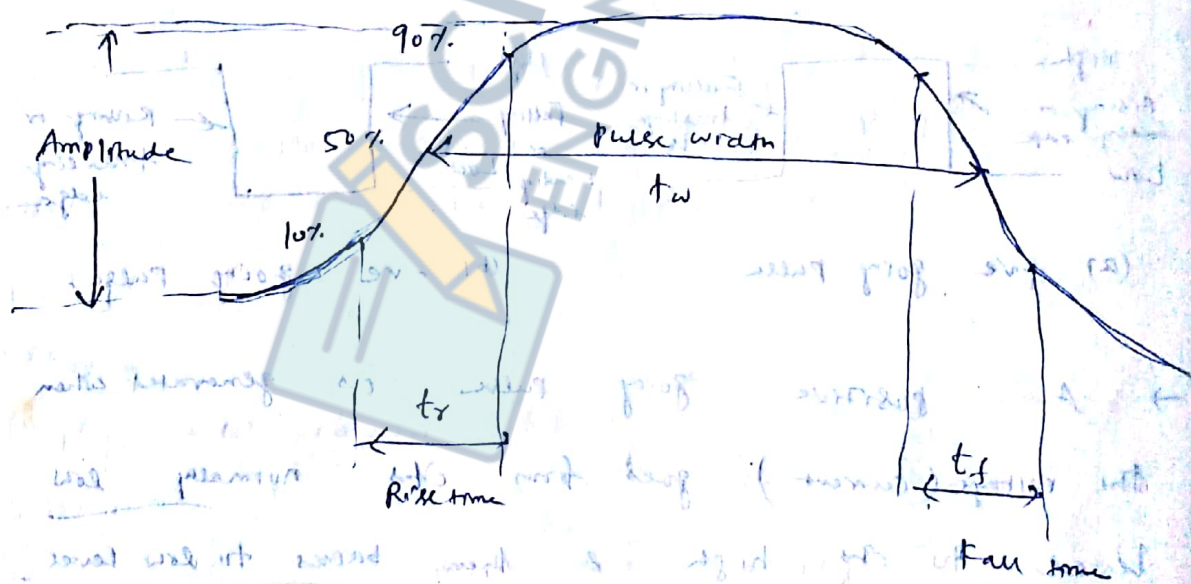The time required for the transition from high level to low level is called the fall time ( $t_f$ ). Practically it is the measure of time from 90% to 10% of pulse amplitude.



Duty cycle =  $\frac{t_w}{T} = \frac{\text{Pulse width}}{\text{Time Period}}$

$f = \frac{1}{T}$  i.e. frequency =  $\frac{1}{\text{Time period}}$



## pulse width:-

It is a measure of the duration of the pulse and is often defined as the time interval between 50% point on the rising & falling edge.


20  
1) (a)

Analog, digital, discrete time signal?

## Analog:-

The analog signal is that type of signal which varies continuously with certain interval of time.

e.g.  $y(t) = \sin t$

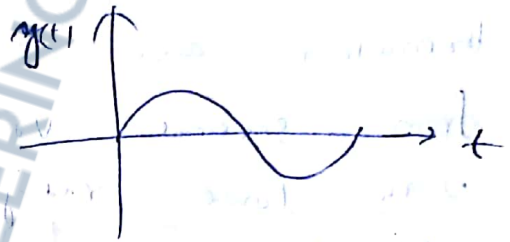

## Digital:-

Digital signal is that type of signal which is represented as a sequence of numbers (i.e. magnitude) at an constant of time.

e.g. = Pulse train shown.

High = +5V (logic 1)

Low = 0V (logic 0)




## Discrete-Time Signal:-

It is defined at certain specific values of time.

The time constant need not be equidistant in practice. They are usually taken at equally spaced intervals for computational convenience and mathematical help.

①
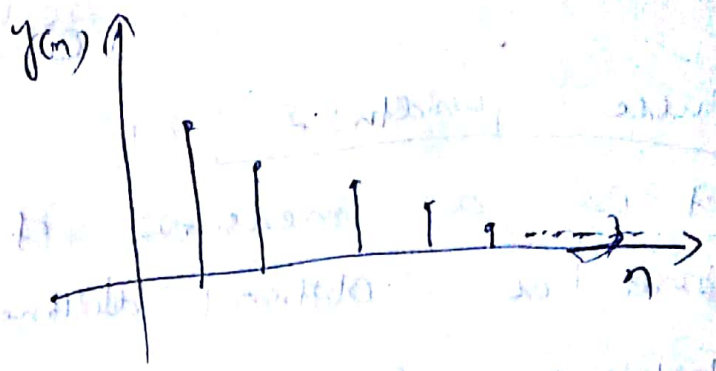
$$y(n) = \begin{cases} 0.2^n, & \text{for } n \geq 0 \\ 0, & \text{otherwise} \end{cases}$$



$n = \text{integer}$ .

b) P-N junction diode made up of which material (Si, Ge, GaAs) will have highest thermal stability? Why?

Ans :- P-N junction diode made up of Si material will have highest thermal stability, because Silicon diodes operated in Avalanche breakdown are available with maintaining voltages from several volts to several hundred volts with power rating up to 50 watts. They can operate in high temperature.

Internal - 4) An amplifier operating from  $\pm 5V$  supplies provides a 3.2 V peak sine wave across  $50\Omega$  load, when provided with 0.4 V peak e/p from which  $2.0 \text{ mA}$  peak is drawn. The avg current in each supply is measured to be 30 mA. Find voltage gain, current gain & power gain expressed in dB, as well as supply power, amplifier dissipation & amplifier efficiency.



# Logic Gates & Boolean Algebra

1) BPUT 2016

Prove that

$$\overline{AB+AC} + A\overline{B}C = \overline{A} + \overline{B}$$

Ans  $\Rightarrow$

$$\overline{AB+AC} + A\overline{B}C$$

$$= \overline{AB} \cdot \overline{AC} + A\overline{B}C$$

$$= (\overline{A+B})(\overline{A+C}) + A\overline{B}C$$

$$= \overline{A} \cdot \overline{A} + \overline{A} \cdot \overline{C} + \overline{A} \overline{B} + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} + \overline{A} \overline{C} + \overline{A} \overline{B} + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} (1 + \overline{C}) + \overline{A} \overline{B} + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} + \overline{A} \overline{C} + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} + (1 + \overline{B}) + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} + \overline{B} \overline{C} + A\overline{B}C$$

$$= \overline{A} + \overline{B} (\overline{C} + AC)$$

$$= \overline{A} + \overline{B} [(\overline{C}+A)(\overline{C}+C)]$$

$$= \overline{A} + \overline{B} (\overline{C}+A)$$

$$= \overline{A} + \overline{B} \overline{C} + A\overline{B}$$

$$= (\overline{A} + A) (\overline{A} + \overline{B}) + \overline{B} \overline{C}$$

$$= 1 \cdot (\overline{A} + \overline{B}) + \overline{B} \overline{C} = \overline{A} + \overline{B} + \overline{B} \overline{C}$$

~~$$= \overline{A} + (\overline{B} + \overline{B}) (\overline{B} + \overline{C})$$~~

$\therefore \overline{A+B} = \overline{A} \cdot \overline{B}$   
 $\therefore \overline{A-A} = \overline{A}$

$\therefore A+BC = (A+B)(A+C)$   
 $\overline{C}+C = 1$

$$\overline{AB+AC} = \overline{A} \overline{B} + \overline{A} \overline{C}$$

$$= \overline{A} + \overline{B} + \overline{B} \overline{C}$$

$$= \overline{A} + \overline{B} (1 + \overline{C})$$

$$= \overline{A} + \overline{B}$$


(Proved)

✓ (a) Draw the logic diagram for the boolean expression

$$Y = (A+B) \cdot (B+C) \cdot (C+A)$$

(b) Simplify the above equation & draw the logic diagram for simplified expression.

Ans -

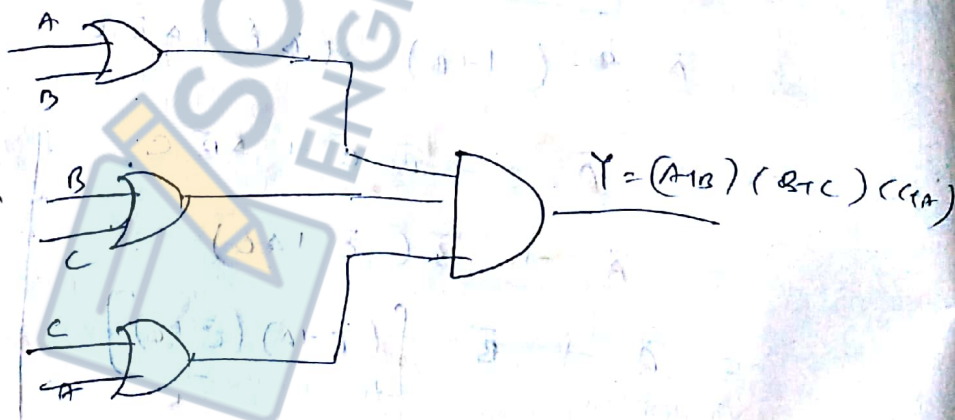

$$(ii) (A+B)(B+C)(C+A)$$

$$= (AB+AC+B\overline{B}+BC)(C+A)$$

$$= (AB+AC+B\overline{B}+BC)(C+A)$$


$$= (B(1+A+C)+AC)(C+A)$$



$$(A+B)(B+C)(C+A) = (B+AC)(C+A)$$

$$= BC + BA + A \cdot C + C \cdot C$$

$$= AB + BC + AC$$

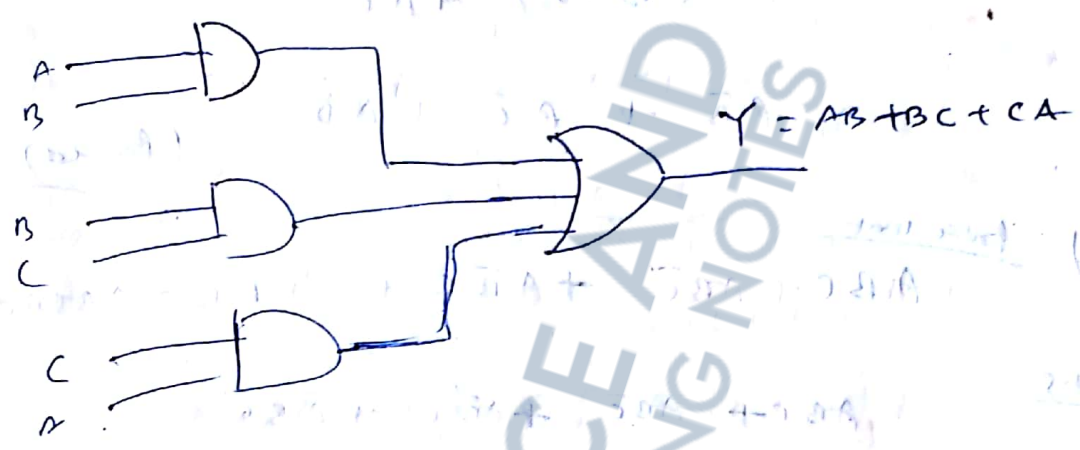

3) Prove that

$$A\bar{B} + AB\bar{D} + ABC\bar{D} = A\bar{B} + A\bar{C} + A\bar{D}$$

Proof

$$\begin{aligned} & A\bar{B} + AB\bar{D} + ABC\bar{D} \\ &= A\bar{B} + AB[\bar{D} + \bar{C}\bar{D}] \\ &= A\bar{B} + AB[(\bar{D} + \bar{C})(\bar{D} + \bar{D})] \\ &= A\bar{B} + AB[(\bar{C} + \bar{D})] \\ &= A\bar{B} + AB\bar{C} + AB\bar{D} \\ &= A(\bar{B} + B\bar{C}) + AB\bar{D} \\ &= A[(\bar{B} + B)(\bar{C} + \bar{D})] + AB\bar{D} \\ &= A[\bar{B} + \bar{C}] + AB\bar{D} \\ &= A\bar{B} + A\bar{C} + AB\bar{D} \\ &= A(\bar{B} + B\bar{D}) + A\bar{C} \end{aligned}$$

⇒

$$A\bar{B} + A\bar{B}\bar{D} + AB\bar{C}D$$

$$= A(\bar{B} + B\bar{D}) + A\bar{C}$$

$$= A[(\bar{B} + B)(\bar{B} + \bar{D})] + A\bar{C}$$

$$= A(\bar{B} + \bar{D}) + A\bar{C}$$

$$= A\bar{B} + A\bar{C} + A\bar{D} \quad (\text{Proved})$$

4) Prove that

$$ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC = AB + BC + CA$$

L.H.S

$$ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC$$

$$= AB(C + \bar{C}) + A\bar{B}C + \bar{A}BC$$

$$= AB + A\bar{B}C + \bar{A}BC$$

$$= A(B + \bar{B}C) + \bar{A}BC$$

$$= [A(\bar{B} + B)](B + C) + \bar{A}BC$$

$$= A(B + C) + \bar{A}BC$$

$$= AB + AC + \bar{A}BC$$

$$= AB + C(A + \bar{A}B)$$

$$= AB + C(A + \bar{A})(A + B) \quad \left| \begin{array}{l} \because \\ A + \bar{A} = 1 \end{array} \right.$$

$$= AB + C(A + B)$$

$$= AB + AC + BC$$

$$= R.H.S \quad (\text{Proved})$$



Find the complement of the function given below and implement using logic gates.

$$F = \bar{x} (\bar{y} + \bar{z}) (x + y + \bar{z})$$

$$\bar{F} = \overline{\bar{x} (\bar{y} + \bar{z}) (x + y + \bar{z})}$$

$$= \bar{\bar{x}} + \overline{(\bar{y} + \bar{z})} + \overline{(x + y + \bar{z})}$$

$$= x + (\bar{y} \cdot \bar{z}) + (\bar{x} \cdot \bar{y} \cdot \bar{z})$$

$$= x + (\bar{y} \cdot \bar{z}) + (\bar{x} \cdot \bar{y} \cdot \bar{z})$$

$$= x + yz + (\bar{x} \bar{y} \bar{z})$$

$$= x + z (y + \bar{x} \bar{y})$$

$$= x + z [(y + \bar{x}) (y + \bar{y})]$$


$$= x + yz + \bar{x}z$$

$$= (x + \bar{x}) (x + z) + yz$$

$$= (1 + z) + yz$$

$$= 1 + z(1 + y)$$

$$\bar{F} = x + z$$

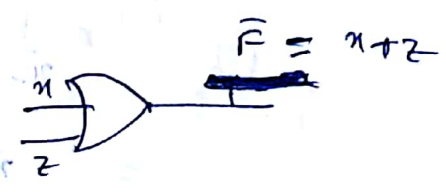

$\overline{ABC} = \bar{A} + \bar{B} + \bar{C}$   
 $\overline{A+B} = \bar{A} \cdot \bar{B}$

6) Simplify the following expression

$$F(x, y, z) = (x+y) \overline{x(y+z)} + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$(x+y) \overline{x(y+z)} + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x+y) \overline{x + (y+z)} + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x+y) (x + \overline{y+z}) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x+y) (x + yz) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x \cdot x + xyz + xy + yz) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x + xy + xyz + yz) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= \left( x(1+y+yz) + yz \right) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= (x + yz) + \overline{xy} + \overline{x} \cdot \overline{z}$$

$$= x + \overline{x} \cdot \overline{z} + yz + \overline{xy}$$

$$= (x + \overline{x} \cdot \overline{z}) + yz + \overline{xy}$$

$$= x + \overline{z} + yz + \overline{xy}$$

$$= x + \overline{y} + \overline{z} + yz$$

$$= x + \overline{y} + (\overline{z} + z) \cdot (\overline{z} + y)$$

$$= x + \overline{y} + \overline{z} + y$$

$$= 1 + \overline{x} + \overline{z} = 1 \quad (\text{Ans})$$



$$7) \text{ If } \bar{A}B + A\bar{B} = C$$

$$\text{Then prove } \bar{A}C + A\bar{C} = B$$

Proof :

$$\begin{aligned} & \bar{A}\bar{C} + \bar{A}C \\ &= A(\bar{A}B + A\bar{B}) + \bar{A}(\bar{A}B + A\bar{B}) \quad \left. \begin{array}{l} = \\ C = \bar{A}B + A\bar{B} \end{array} \right\} \\ &= A(\bar{A}B, A\bar{B}) + \bar{A} \cdot \bar{A} \cdot B + \bar{A} \cdot A \cdot B \\ &= A((\bar{A} + B)(\bar{A} + \bar{B})) + \bar{A}B \\ &= A((\bar{A} + B)(\bar{A} + \bar{B})) + \bar{A}B \\ &= A((\bar{A} + B)(\bar{A} + \bar{B})) + \bar{A}B \\ &= A(\bar{A}\bar{A} + \bar{A}B + B\bar{A} + B\bar{B}) + \bar{A}B \\ &= A(\bar{A}B + \bar{A}\bar{B}) + \bar{A}B \\ &= \underline{A\bar{A}B + A\bar{A}\bar{B}} + \bar{A}B \\ &= \underline{AB + \bar{A}B} \\ &= B(A + \bar{A}) \\ &= B \quad \text{(Proved)} \end{aligned}$$

8) Simplify the logic expression  
 & draw the logic diagram for the  
 simplified expression.

$$(\bar{x} + xy\bar{z}) + (\bar{x} + xy\bar{z})(x + \bar{y}z)$$

$$\begin{aligned}
 & (\bar{x} + xy\bar{z}) + (\bar{x} + x\bar{y}z) (x + \bar{x}\bar{y}z) \\
 &= (\bar{x} + xy\bar{z}) [1 + (x + \bar{x}\bar{y}z)]
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{\bar{x}}{A} + \frac{xy\bar{z}}{B \cdot C} \\
 &= (\bar{x} + x) (\bar{x} + y\bar{z}) \\
 &= \cancel{\bar{x} + x} \\
 &= \bar{x} + y\bar{z} \quad (\text{Ans})
 \end{aligned}$$

9) ✓

Given  $F = A(B + \bar{C}) + D$

Express it as

(a) Minimal SOP (or) minimal POS

Ans:

$$\begin{aligned}
 & A(B + \bar{C}) + D \\
 &= AB + A\bar{C} + D
 \end{aligned}$$

The above expression is itself minimal SOP, since further reduction is not possible.

∴ (i) Minimal SOP =  $AB + A\bar{C} + D$

(ii)

$$F = A(B + \bar{C}) + D$$

$$\begin{aligned}
 \bar{F} &= \overline{A(B + \bar{C}) + D} \\
 &= \overline{AB + A\bar{C}} \cdot \bar{D}
 \end{aligned}$$



$$\Rightarrow \bar{F} = \overline{AB} \cdot \overline{AC} \cdot \bar{D}$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{A} + \bar{C}) \cdot \bar{D}$$

$$= (\bar{A} + \bar{B}) (\bar{A} + \bar{C}) \cdot \bar{D}$$

$$= (\bar{A} \cdot \bar{A} + \bar{A} \bar{C} + \bar{A} \bar{B} + \bar{B} \bar{C}) \bar{D}$$

$$= (\bar{A} + \bar{A} \bar{C} + \bar{A} \bar{B} + \bar{B} \bar{C}) \bar{D}$$

$$= [\bar{A} (1 + \bar{C} + \bar{B}) + \bar{B} \bar{C}] \bar{D}$$

$$= [\bar{A} + \bar{B} \bar{C}] \bar{D}$$

$$= \bar{A} \bar{D} + \bar{B} \bar{C} \bar{D}$$

$$\bar{F} = \overline{\bar{A} \bar{D} + \bar{B} \bar{C} \bar{D}}$$

$$F = \overline{\bar{A} \bar{D}} \cdot \overline{\bar{B} \bar{C} \bar{D}} \quad \left| \begin{array}{l} \overline{A + D} \\ = \bar{A} \cdot \bar{D} \end{array} \right.$$

$$= (\bar{A} + \bar{D}) (\bar{B} + \bar{C} + \bar{D})$$

$$F = (A + D) (B + \bar{C} + D)$$

= Minimal POS form.

Q) Minimize the following expression

$$F = \Sigma (4, 5, 6, 7)$$

Ans:

①

71

$$F = \sum (4, 5, 6, 7)$$

~~$$= 0100 + 1000 + 1001 + 1100$$~~

$$= 100 + 101 + 110 + 111$$

$$= A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

$$= A\bar{B}(C + \bar{C}) + AB(C + \bar{C})$$

$$= A\bar{B} + AB$$

$$= A(B + \bar{B})$$

$$F = A$$

11) Convert following expression into pos form.

$$P = \sum (0, 1, 2, 6)$$

Ans:  $P = \prod (3, 4, 5, 7)$

$$F = m_0 + m_1 + m_2 + m_6$$

~~$$\bar{F} = \bar{m}_0 + \bar{m}_1 + \bar{m}_2 + \bar{m}_6$$~~
~~$$= \bar{m}_0 + \bar{m}_1 + \bar{m}_2 + \bar{m}_6$$~~

$$F = m_3 + m_4 + m_5 + m_7$$

$$= \overline{m_3 + m_4 + m_5 + m_7}$$

$$= \bar{m}_3 \cdot \bar{m}_4 \cdot \bar{m}_5 \cdot \bar{m}_7$$



$$F = M_3 \cdot M_4 \cdot M_5 \cdot M_7$$

$$F = 011 \cdot 100 \cdot 101 \cdot 111$$

$$F = (A + \bar{B} + \bar{C}) (\bar{A} + B + C) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C})$$

Q2) Simplify the following boolean expression

$$F = \sum(0, 2, 4, 6)$$

~~$$f = 000 + 001 + 010 + 011 + 100 + 101 + 110 + 111$$~~

$$F = 000 + 010 + 100 + 110$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C}$$

$$= \bar{A}\bar{C}(\bar{B} + B) + A\bar{C}(\bar{B} + B)$$

$$= \bar{A}\bar{C} + A\bar{C}$$

$$= \bar{C}(A + \bar{A})$$

$$= \bar{C} \quad (\text{Ans})$$

Q3) Realize the following expression using

- (a) Basic logic gates.
- (b) Universal logic gates.

~~$$F = ABC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$~~



$$F = \bar{A} + BC$$

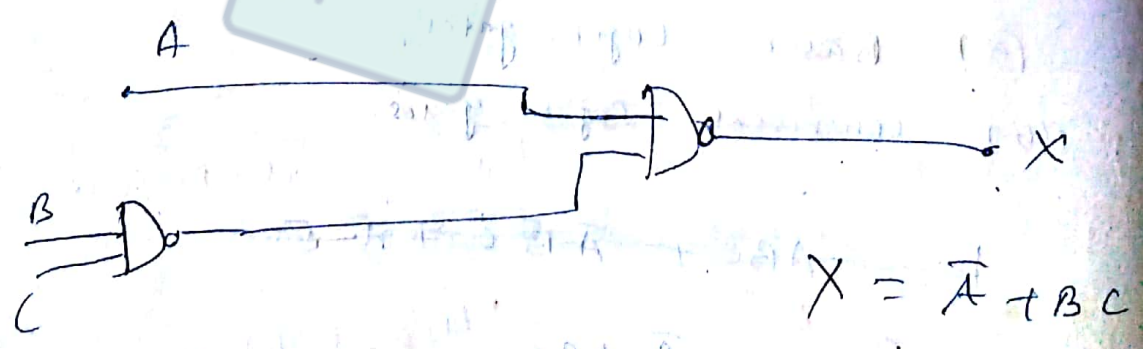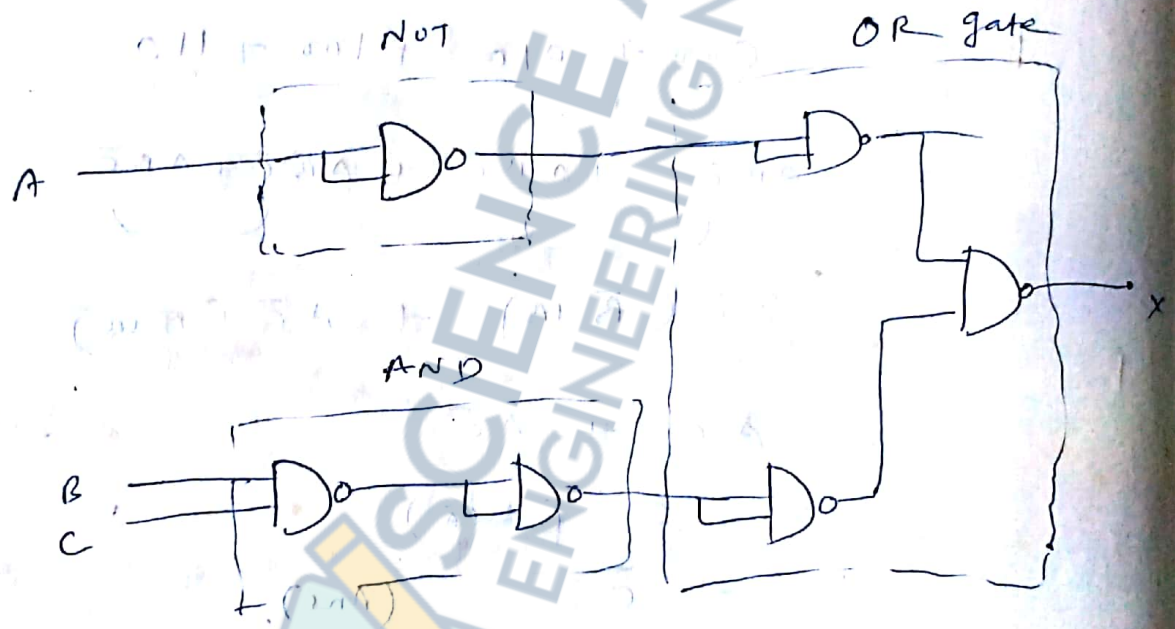(a) using Basic logic gates:-

$F = \bar{A} + BC$




Replacing each gate by corresponding NAND gate



$\therefore$  2 NOT gates cancel each other  $\bar{\bar{A}} = A$



Replacing each gate by NOR gate

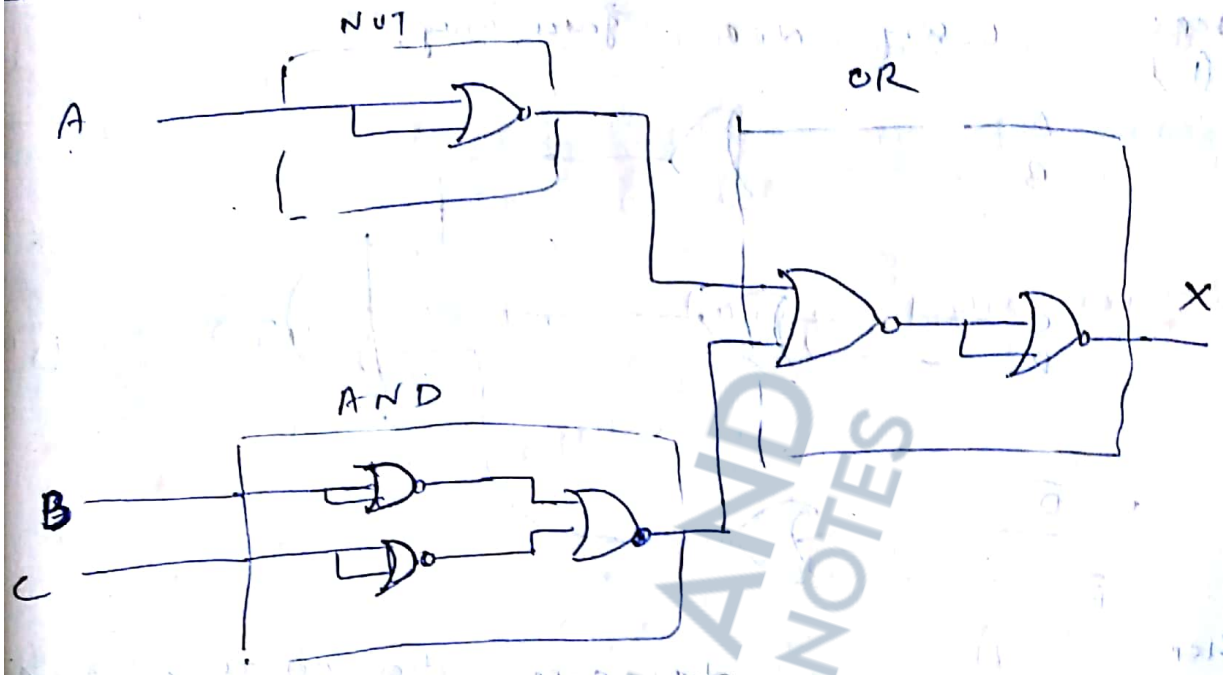


$$X = \bar{A} + BC$$

Note:-


- Bubbled AND = NOR
- Bubbled OR = NAND

Bubbled AND :-

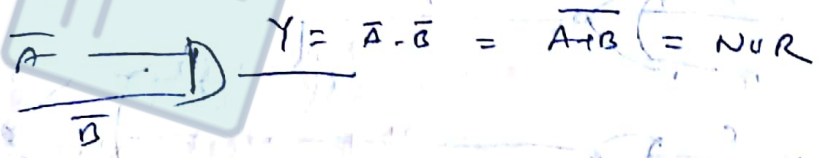

$$Y = \bar{A} \cdot \bar{B} = \overline{A+B} = \text{NOR}$$

Bubbled OR

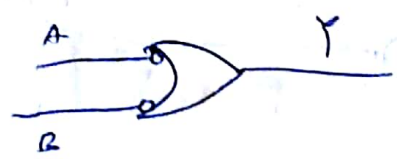

$$Y = \overline{A+B} = \overline{A \cdot B} = \text{NAND}$$


14)

Implement

$$F = (A+B) \cdot (C+D) \cdot (\bar{D}+E)$$


Step (1)

Using NOR gates only!

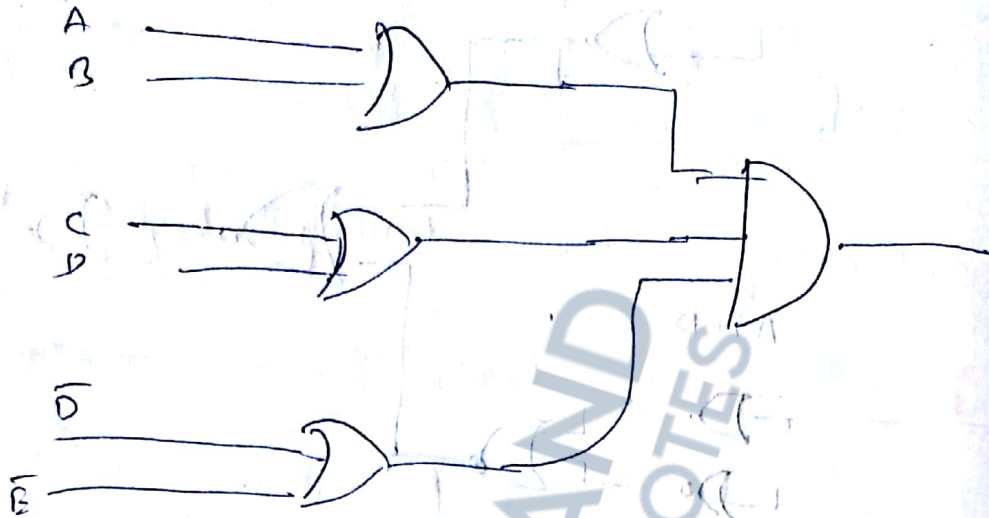


Step

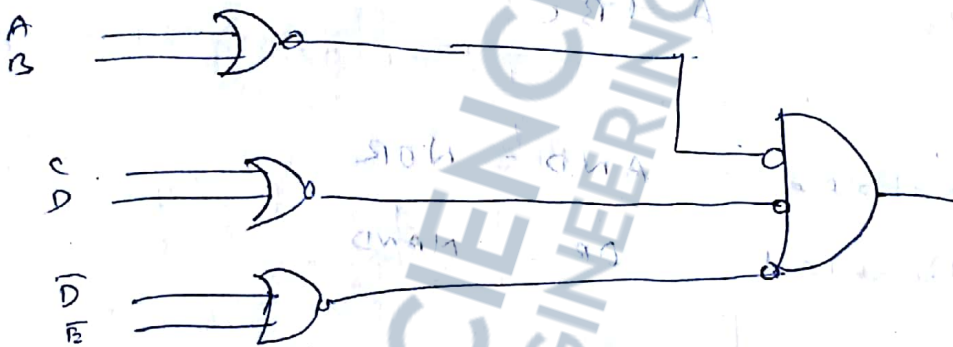(2) Adding 2 NOT gates does not change  $\bar{\bar{A}} = A$



(3)

Bubbled AND = NOR

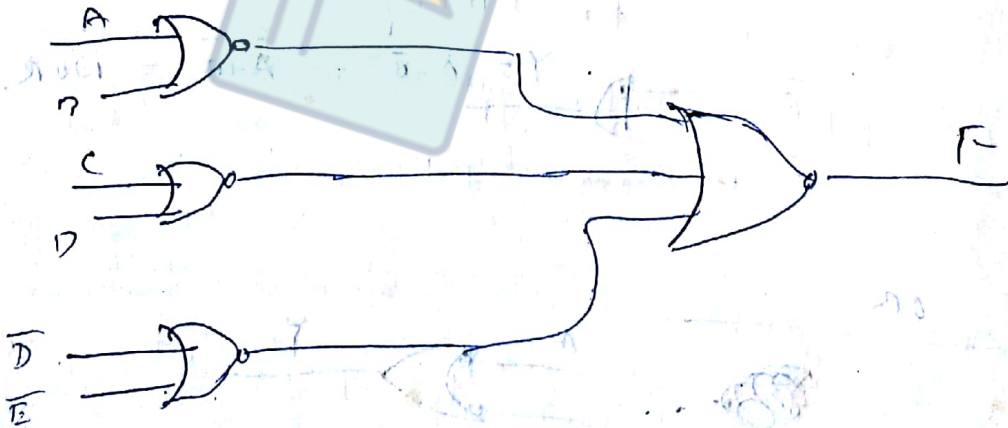



Another Method of Using NAND and NOR

Q) Implement  $A + B\bar{C}$  Using Minimum NAND gates & Minimum NOR gates.


Ans +

Minimum NAND gates  
 (Express in product term bar)

$$F = A + B\bar{C}$$

$$F = \bar{\bar{A + B\bar{C}}}$$
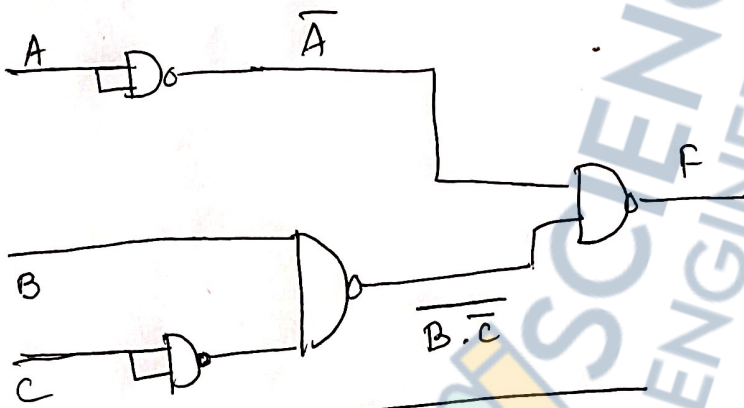
$$\Rightarrow F = \overline{\bar{A} \cdot \overline{B\bar{C}}}$$



$$F = \bar{A} \cdot \overline{B\bar{C}}$$


Minimum NOR gates  
 (Express in sum term bar)

$$F = A + B\bar{C}$$

$$F = \bar{\bar{A + B\bar{C}}}$$


$$\Rightarrow F = \overline{(A+B)(A+\bar{C})}$$
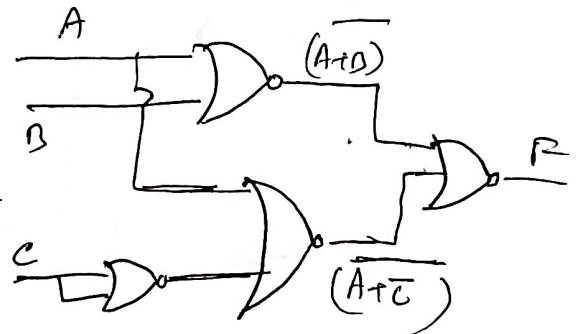
$$= \overline{(A+B)} + \overline{(A+\bar{C})}$$



$$F = \overline{(A+B)} + \overline{(A+\bar{C})}$$

# Digital Ckts. & Design

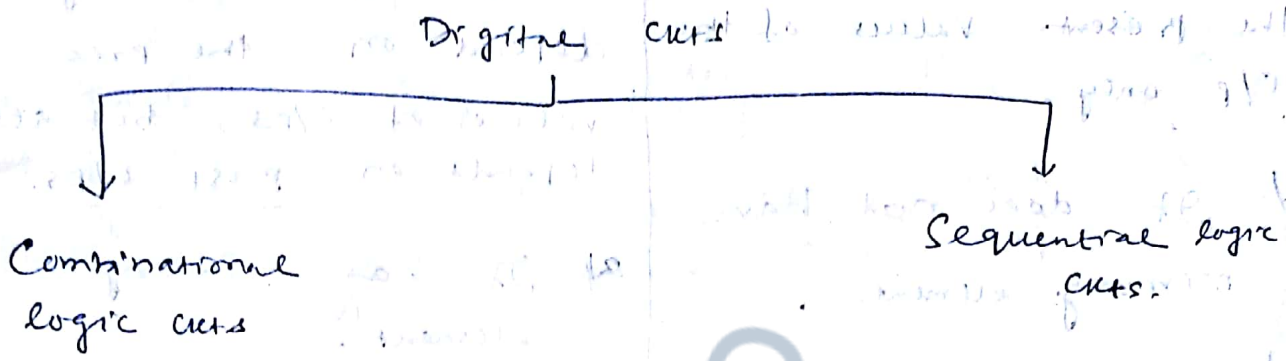

→ A Combinational Ckt consists of logic gates whose o/p at any time are determined from present combination of i/p's.

→ A Combinational Ckt's performs an operation that can be specified logically by a set of Boolean functions.

→ Sequential Ckts employ storage elements in addition to logic gates. Their o/p's are a function of previous i/p's. As a consequence, the o/p's of a sequential Ckt's depend not only on present values of i/p's, but also past i/p's and the Ckt. behavior must be specified by a time sequence of i/p's and internal states.

→ Comparison of Combinational & Sequential logic ckt's.



### Combinational Logic cut

- 1) Its o/p depend on the present values of the i/p only.
- 2) It does not have memory element.
- 3) It does not have feedback path from o/p to i/p.
- 4) It does not have a clock signal.
- 5) A combinational cut consists of logic gates.
- 6) Its action does not depend on clock transition.
- 7) Its cut is simpler than the ~~combinational~~ <sup>sequential</sup> logic cuts.
- 8) Ex → Adder, Subtractor, MUX, Demux, Decoder, Encoder etc.


### Sequential Logic cut

- 1) Its o/p not only depend on the present values of i/p's, but also depends on past i/p's.
- 2) It has memory element.
- 3) It has feedback path from o/p to i/p.
- 4) It has a clock signal.
- 5) A sequential logic gate consists of combinational logic cuts and memory elements.
- 6) Its action depend on clock transition.
- 7) Its cut is more complex than that of combinational logic cuts.
- 8) Ex: Flip-Flops, Counters, Shift-registers.
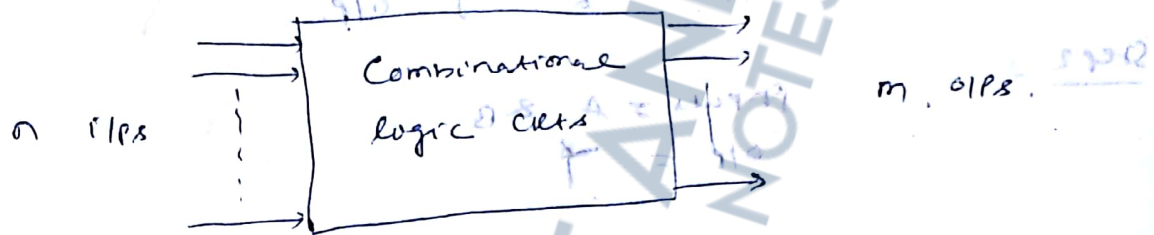
# Combinational Logic Ckt: -

A Combinational Ckt. Consists of I/P variables, logic gates and o/p variables.

The logic gates accept signal from the I/Ps and generate signal to the outputs.



The  $n$  I/P binary variables come from an external source. The  $m$  O/P variables go to external destination.

## Design procedure -

- 1) From the specification of the ckt, determine the required number of I/Ps and O/Ps.
- 2) Assign I/P & O/P variables.
- 3) Derive truth table that defines the relationship between I/Ps and O/Ps.
- 4) Obtain the simplified expression for O/P as function of I/P variables.
- 5) Draw the logic diagram & verify the correctness of the design.



Ex = 1) Design a 2 input digital circuit whose o/p is 1 if all inputs are same. The o/p is 0 otherwise. Design the digital circuits.

(a) Using Basic gates      b) Using NAND gates.

Ans :

Step 1 :      2 input      2      1 o/p.

Step 2 :      Inputs = A & B  
o/p = Y


Step-3

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


Step-4

$$Y = \bar{A}\bar{B} + AB \quad (\text{X-NOR})$$

Step-5 :-

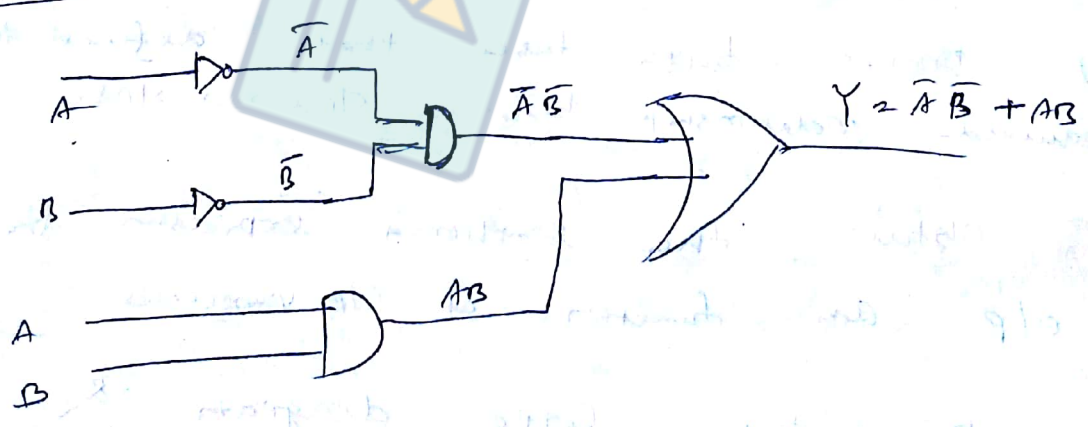

(a) using Basic gates.

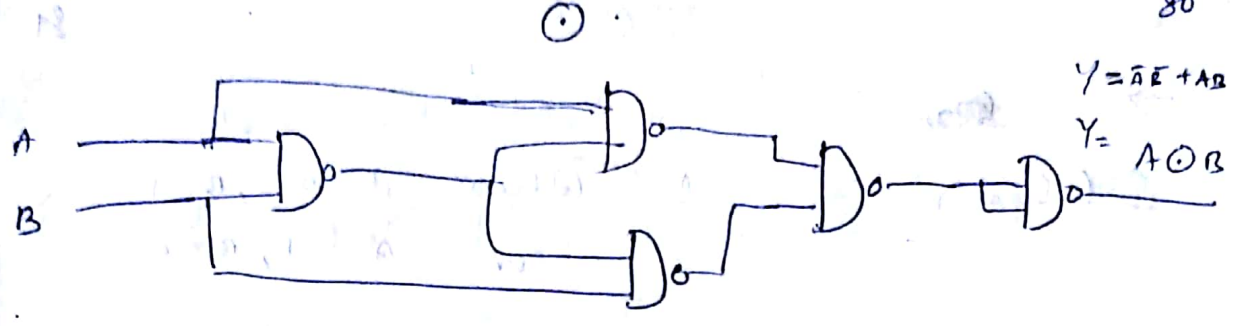

## Basic Adders: -

→ The most basic arithmetic operation is addition of 2 binary digits.

$0 + 0 = 0$	
$0 + 1 = 1$	
$1 + 0 = 1$	← carry
$1 + 1 = 10$	→ 1 0

→ The first three operation produces a sum of one digit and 4th one produces a carry.

→ A combinational ckt. that performs the addition of 2 bit is called half adder.

→ One that performs addition of 3 bit is called full adder.

### Half Adder: -

→ Half-adder is a combinational logic ckt, which perform 2 bits addition.

→ The result produces a sum as well as carry.

→ The simplified expression can be directly obtained from the truth table.

A	B	S	BC
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

← Truth table for half adder



→ ~~Sum~~  
 S (Sum) is 1 when  $A=0, B=1$   
 or  $A=1, B=0$

$$\therefore S = \bar{A}B + A\bar{B} \cong A \oplus B$$

C (Carry) is 1, when  $A=1, B=1$

$$\therefore C = AB$$

Block Diagram:-



fig (a)


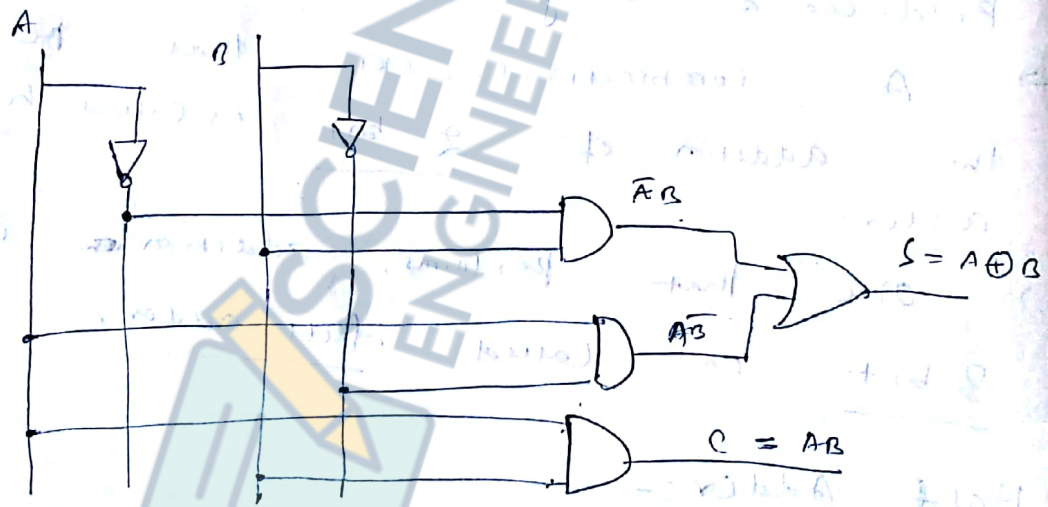


fig (b) using Basic logic gates.

Short

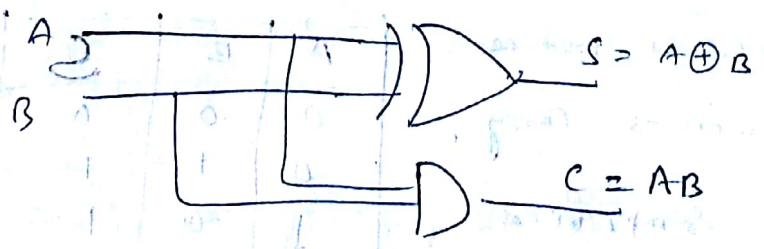

(c) using EX-OR and AND gate

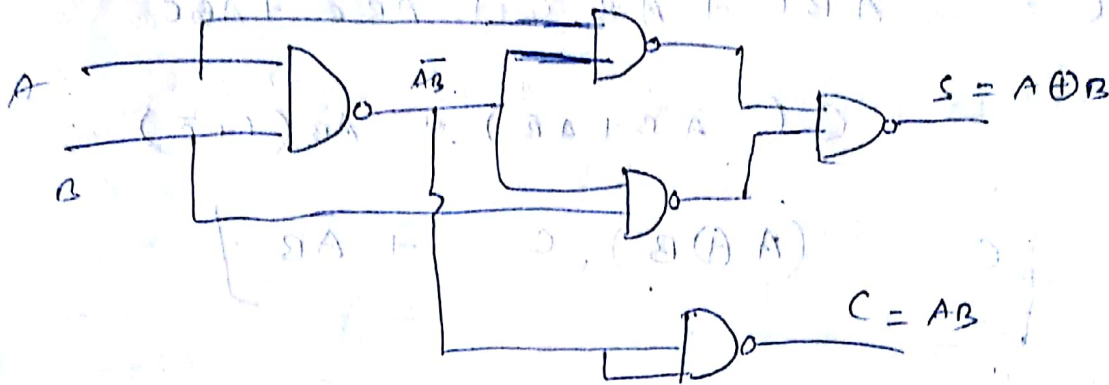


Fig (4) :- Using NAND gates only.

Full Adder :- *(Sum - Remains from 2 half adder)*

Full adder is a combinational logic circuit which performs 3 bit binary addition, which produces a sum as well as carry.

A	B	C	S (sum)	C (carry)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + ABC$$

$$= \bar{A} (\bar{B} C + B \bar{C}) + A (\bar{B} \bar{C} + BC)$$

$$= \bar{A} (B \oplus C) + A (B \odot C)$$

$$= \bar{A} Y + A \bar{Y}$$

$$= A \oplus Y$$

$$\left. \begin{aligned} B \oplus C &= Y \\ B \odot C &= \bar{Y} \end{aligned} \right\}$$

$$S = A \oplus B \oplus C$$



$$C = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= C(\bar{A}B + A\bar{B}) + AB(C + \bar{C})$$

$$C = (A \oplus B) \cdot C + AB$$

10

$$C = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + A\bar{B}C + AB(C + \bar{C})$$

$$= \bar{A}BC + A\bar{B}C + AB$$



$$= AB + \bar{A}BC + A\bar{B}C$$

$$= B(A + \bar{A}C) + A\bar{B}C$$

$$= B((A + \bar{A})(A + C)) + A\bar{B}C$$

$$= B(A + C) + A\bar{B}C$$

$$= AB + BC + A\bar{B}C$$

$$= AB + C(B + A\bar{B})$$


$$= AB + C(B + A)(B + \bar{B})$$

$$= AB + C(A + B)$$


$$C = AB + BC + AC$$

$$\therefore \begin{aligned} &A + BC \\ &= (A + B)(A + C) \end{aligned}$$

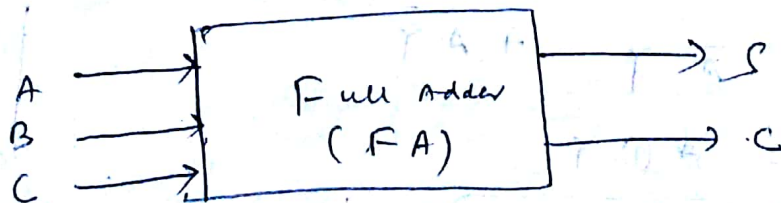
$$\therefore \begin{aligned} &A + BC \\ &= (A + B)(A + C) \end{aligned}$$



(a) Block diagram.

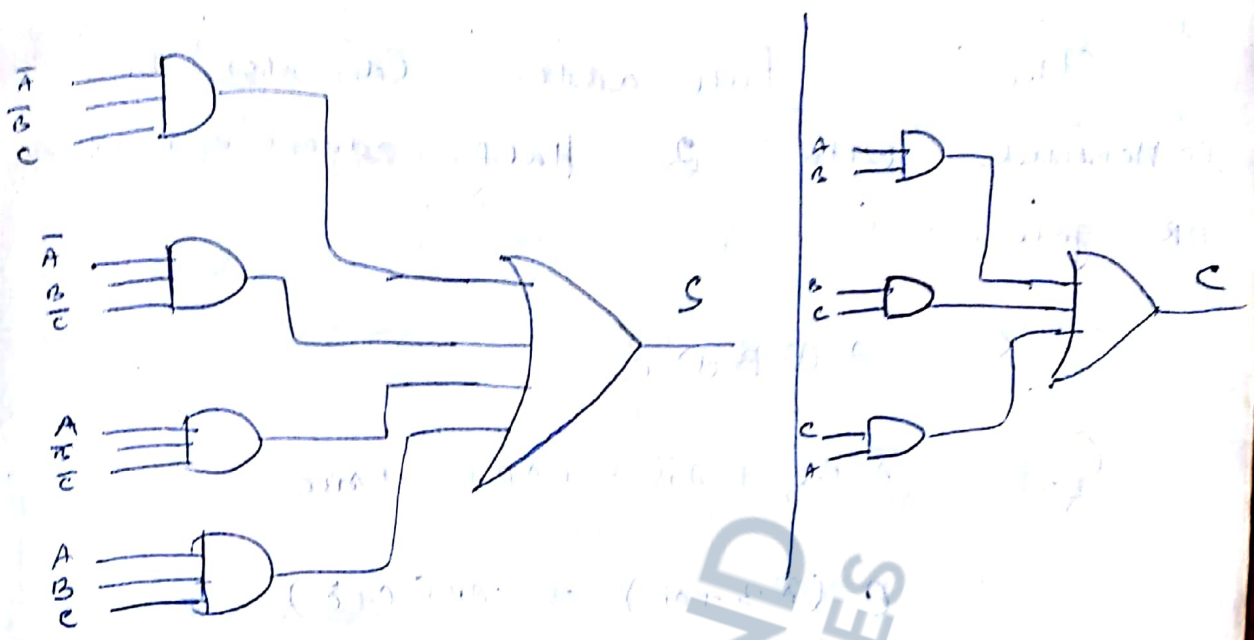

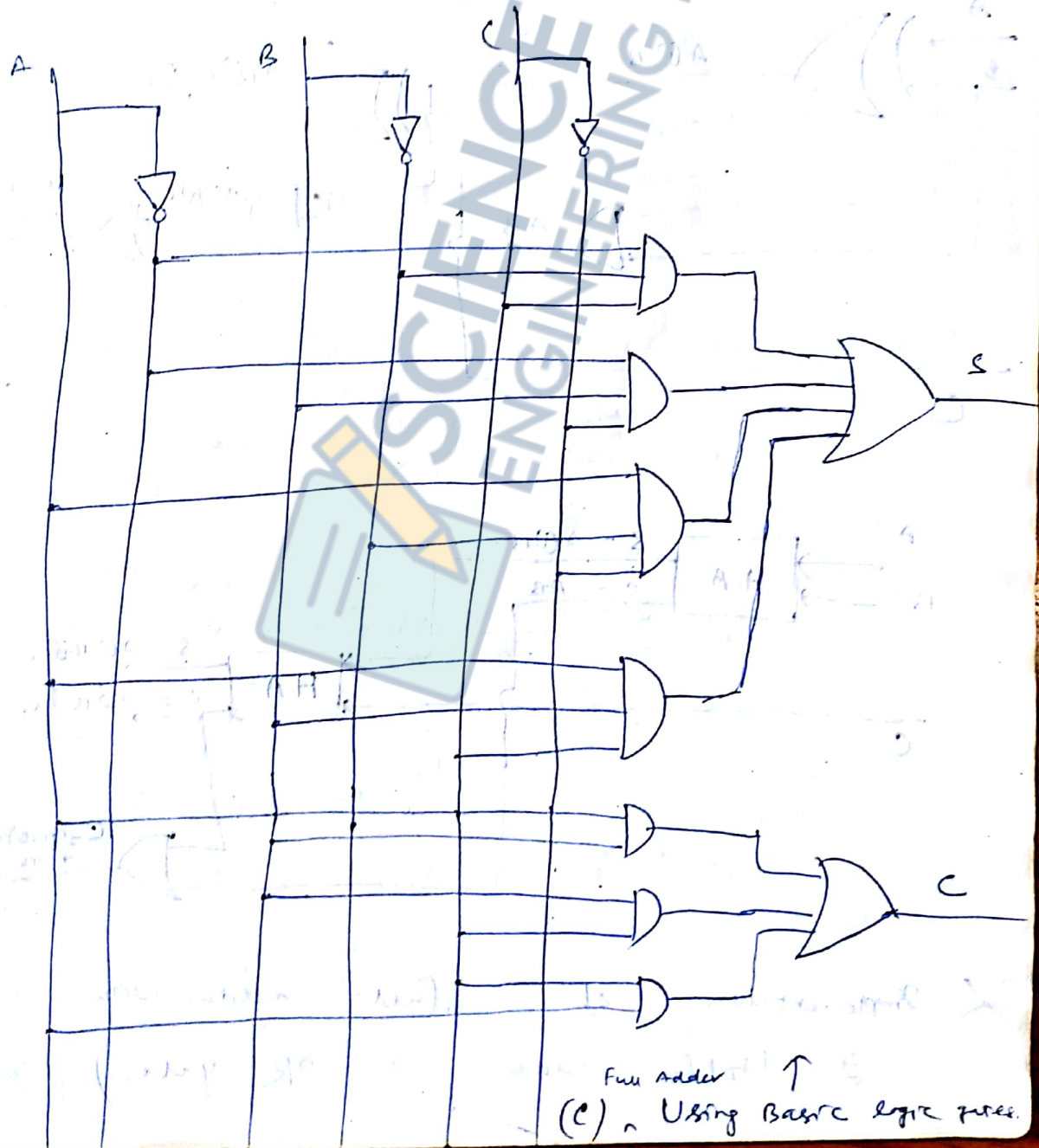(b) Implementation of full adder in sum of product (SOP)



(c) Full adder using basic logic gates





The full adder can also be implemented with 2 Half adders and one OR gate.

$$S = A \oplus B \oplus C$$

$$C = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= C(\bar{A}B + A\bar{B}) + AB(C + \bar{C})$$

$$= C(A \oplus B) + AB$$

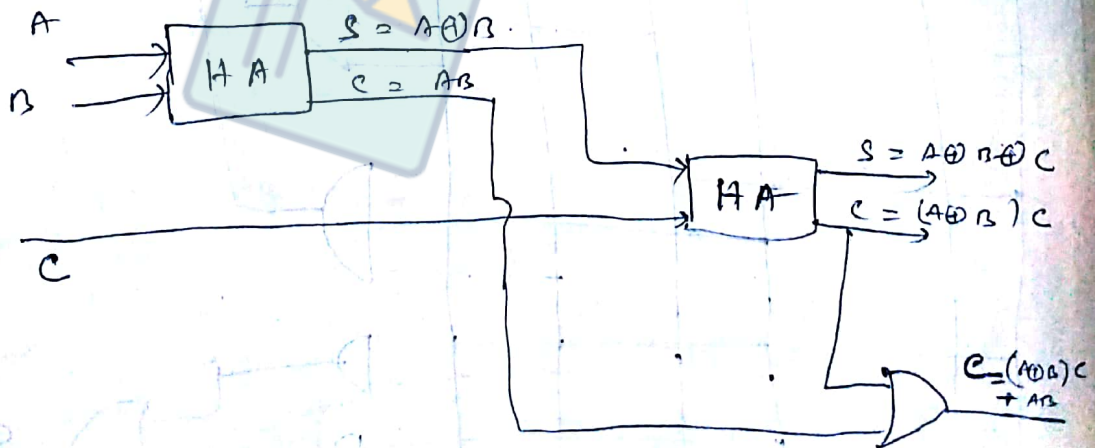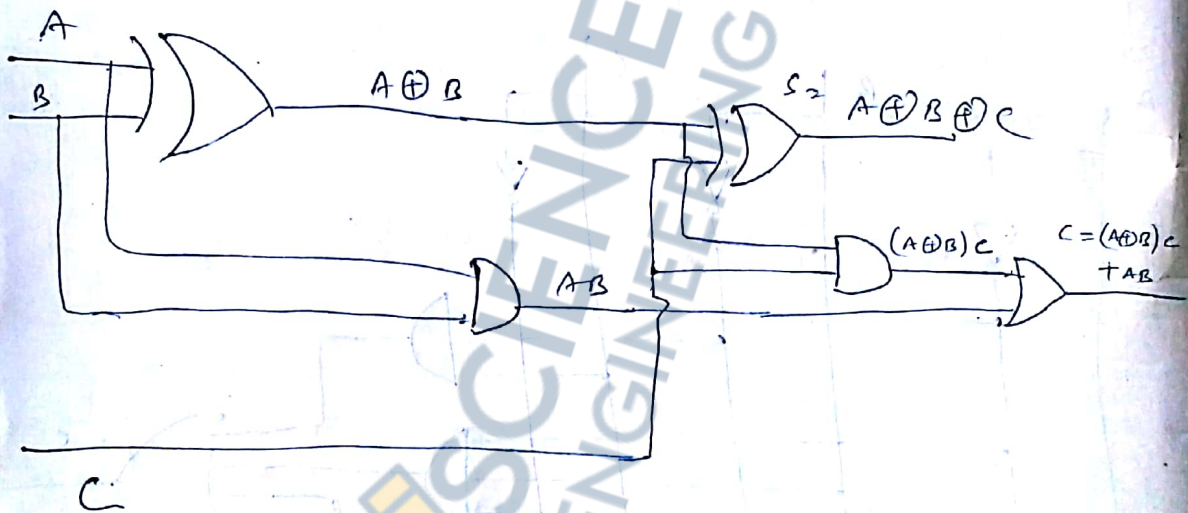

Implementation of full adder with 2 Half adder and OR gate

# Basic Subtractor :-

→ The simple subtraction consists of 4 possible elementary operations :-

$$0-0=0, \quad 0-1=11, \quad \text{Borrow 1.}$$

$$1-0=1, \quad 1-1=0$$

→ The Combinational ckt that performs ~~a difference of one digit and~~ the subtraction of 2 bit is called half subtractor.

→ one that performs the subtraction of 3 bits is called full subtractor.

→ 2 half subtractor can be used to complement a full subtractor.

## Half Subtractor :-

Half subtractor is a combinational ckt, which performs 2 bits subtraction, produces a difference as well as borrow.

Truth Table:-

A	B	D (Difference)	B (Borrow)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	1


$$\begin{array}{r} 100 \\ -011 \\ \hline \end{array}$$

$$\therefore D = \bar{A}B + A\bar{B} = A \oplus B$$


$$B = \bar{A}B$$

(Borrow)





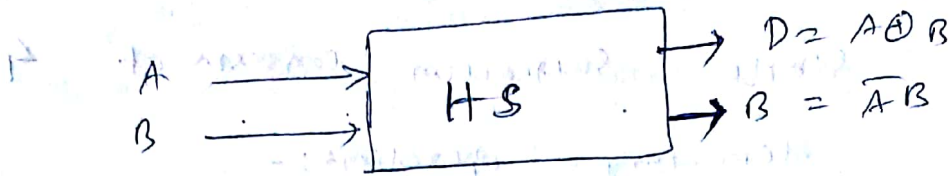


(a) Block diagram.

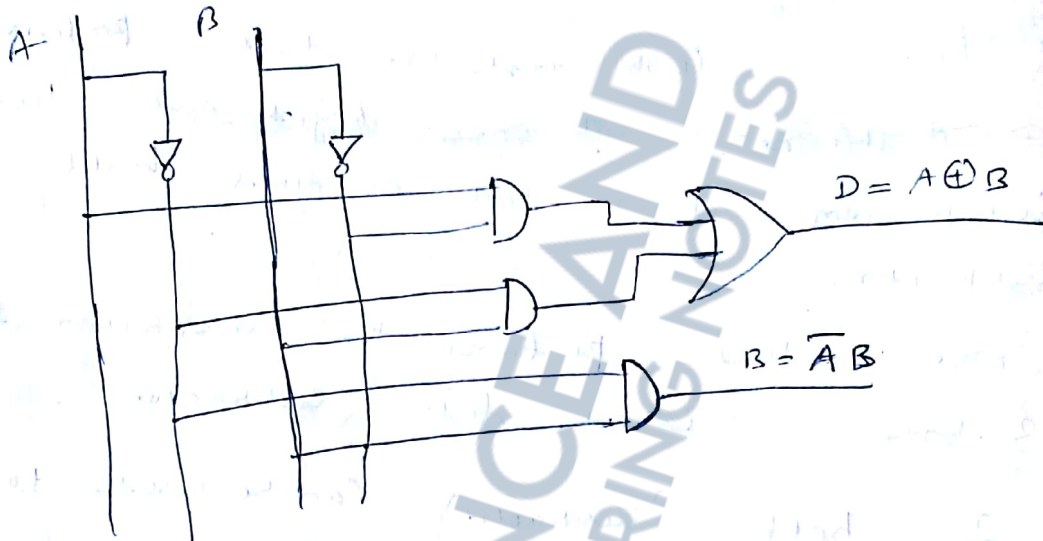

(b) using basic logic gates

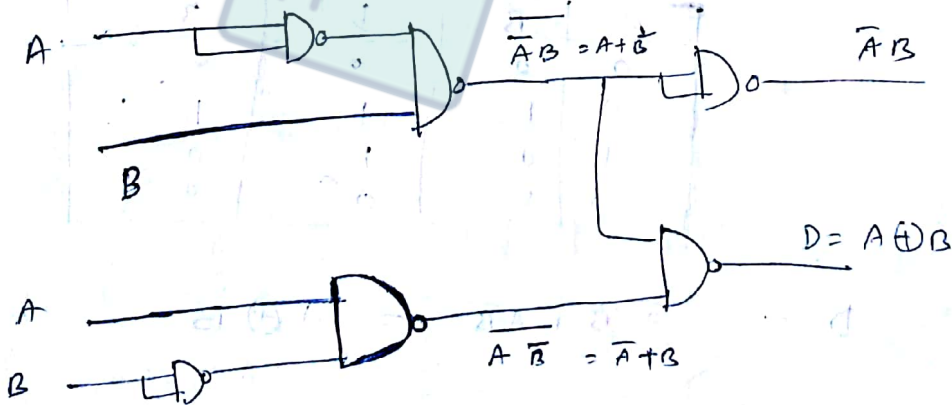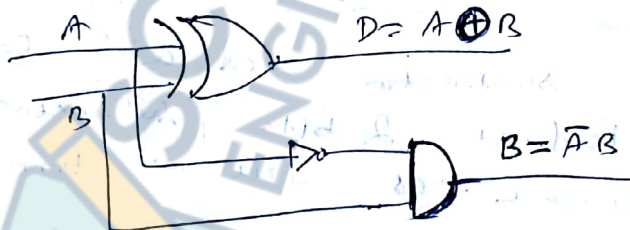

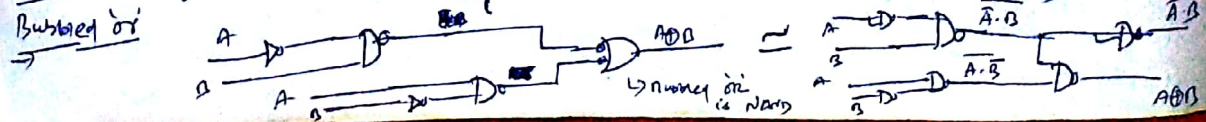Hints: - using ~~basic~~ (using NAND gate only)



Proof:-  $D = \overline{(A+B)} \cdot \overline{(A+B)}$

$$= \overline{(A+B)} + \overline{(A+B)}$$

$$= \overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{B}$$

$$= \overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{B}$$

$$= A \oplus B \quad (\text{Proved})$$

Full Subtractor :-

Full Subtractor is a combinational logic circuit which performs 3 bit binary subtraction, which produces a difference as well as a borrow.

Truth Table :-

A	B	C	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table :-

$$D = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} \overline{C} + ABC$$

$$= \overline{A} (\overline{B} C + B \overline{C}) + A (\overline{B} \overline{C} + BC)$$

$$= \overline{A} (B \oplus C) + A (B \odot C)$$

$$= \overline{A} Y + A \overline{Y}$$



$$= A \oplus Y = A \oplus B \oplus C$$

$B \oplus C = Y$   
 $B \odot C = \overline{Y}$




$$\begin{aligned}
 B \text{ (Borrow)} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC \\
 &= C(\bar{A}\bar{B} + \bar{A}B + \bar{A}C + AC) \\
 &= C(A \oplus B) + \bar{A}B
 \end{aligned}$$

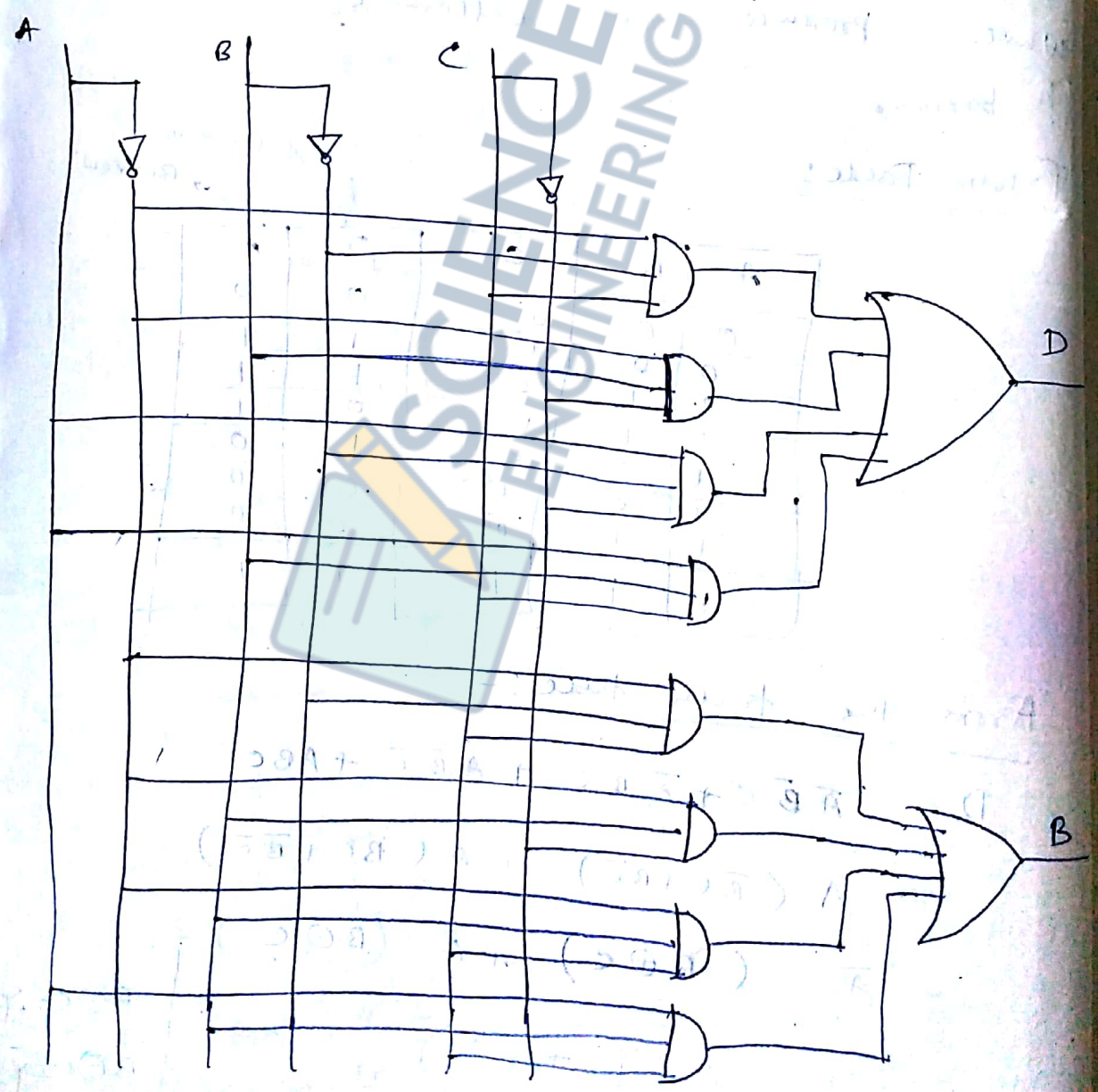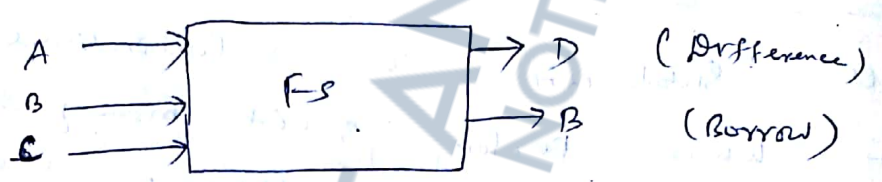The Block diagram for a full subtractor is shown




(Full Subtractor using Basic logic gates)

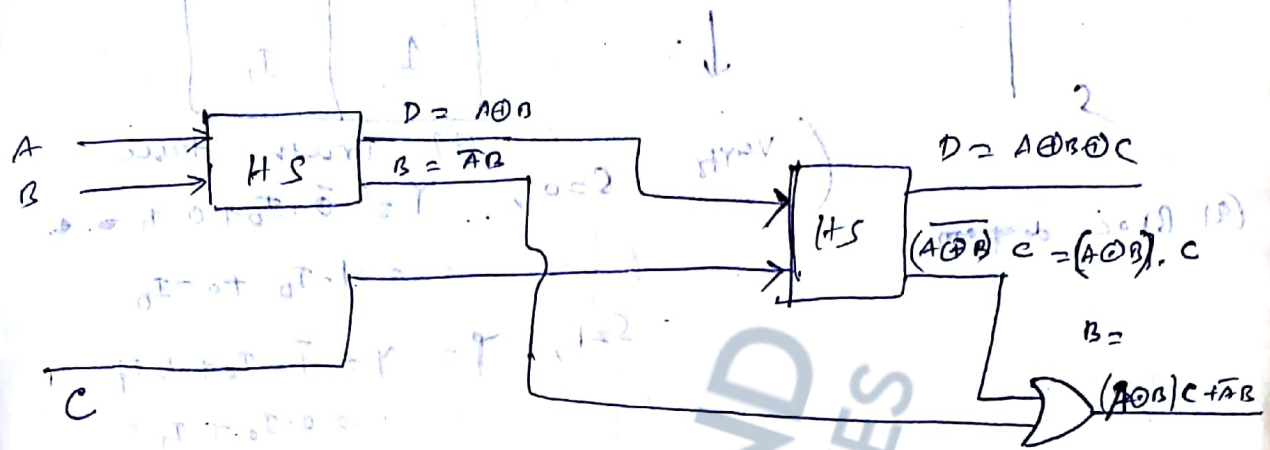Full Subtractor can also be realized with 2 half subtractor and one OR gate.



2mp  
Multiplexers :-

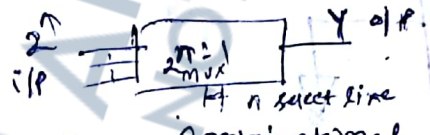

→ Multiplexer (MUX) is a combinational logic circuit that receives information from many I/Ps and directs this information to the O/P.

→ The I/P information that is selected is controlled by a selector lines.


→ A MUX with  $2^n$  I/Ps requires  $n$  selector lines.

→ Mux is also sometimes known as many to one or it is known as data selector.

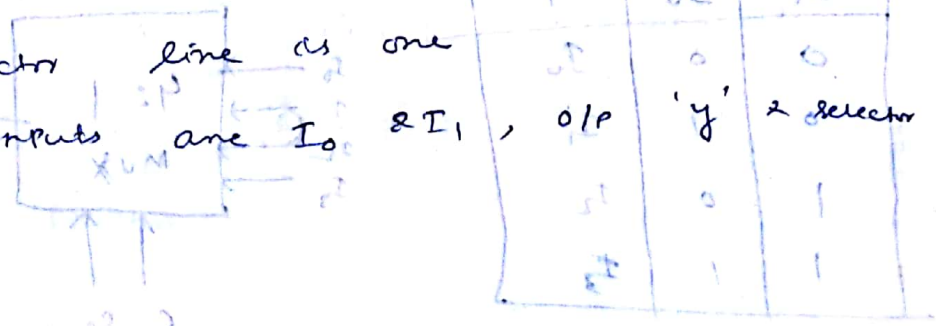
2:1 MUX

→ It has 2 I/Ps and one O/P, so no. of selector line is one.

→ Inputs are  $I_0$  &  $I_1$ , O/P 'y' & selector line 's'.





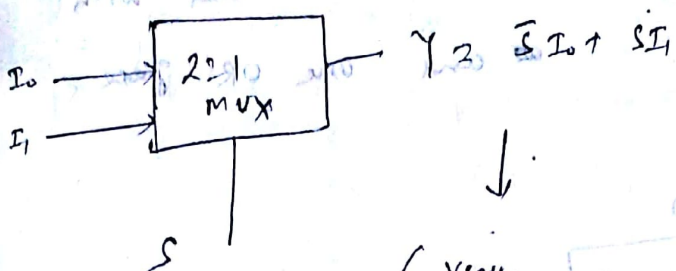

S	Y
0	I <sub>0</sub>
1	I <sub>1</sub>


(a) Block diagram

(b) Truth table

Verify

$$S=0, Y = 0 \cdot I_0 + 1 \cdot I_1 = I_1$$
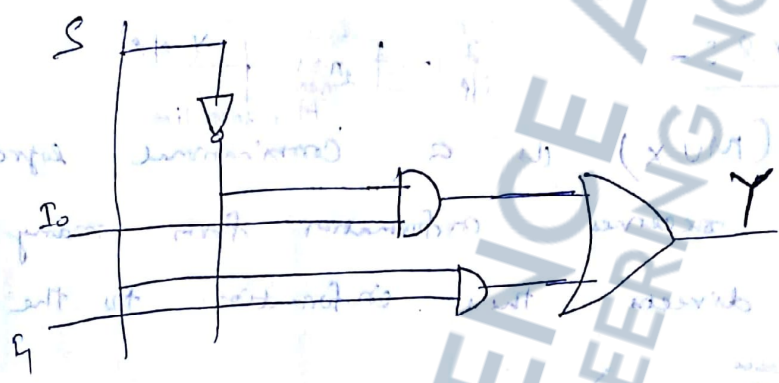
$$S=1, Y = 1 \cdot I_0 + 0 \cdot I_1 = I_0$$



(c) Logic circuit


4:1 MUX

→ It has 4 I/Ps and one O/P. So number of selector line is 2. ( $\because 4 = 2^2$ )

→ Inputs are I<sub>0</sub>, I<sub>1</sub>, I<sub>2</sub>, I<sub>3</sub> and selector lines S<sub>1</sub>, S<sub>0</sub>.

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>


(a) Truth table

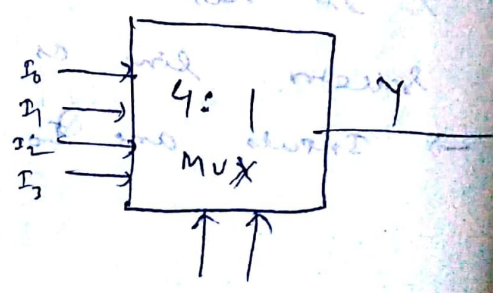

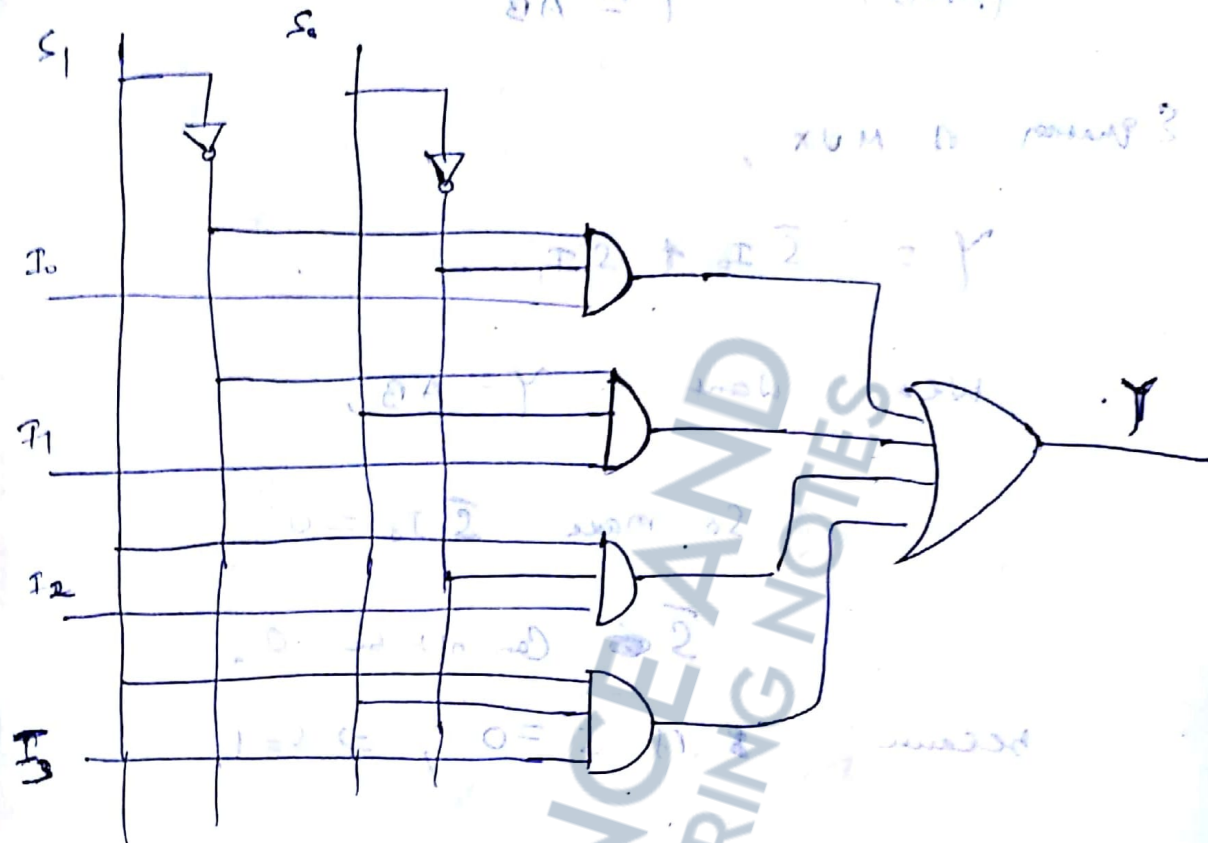(b) Block diagram

92

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$




Ex-1 :- Implement Inverter  $Y = \bar{A}$  using MUX

Ans :-  $Y = \bar{S} I_0 + S I_1$

If  $S = A, I_1 = 0, I_0 = 1$

$$Y = \bar{A} \cdot 1 + A \cdot 0$$

$$Y = \bar{A}$$

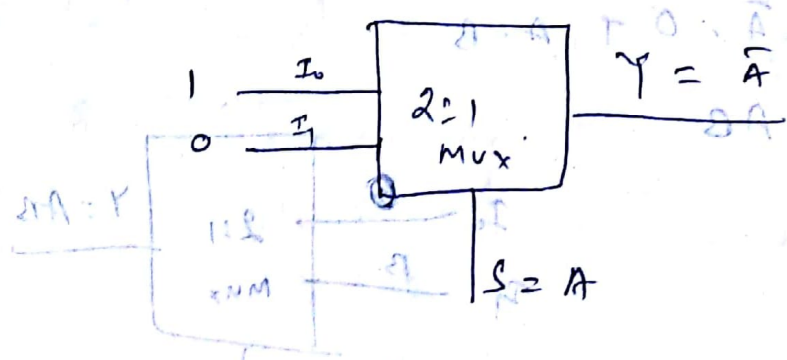

(A) 2



Ex-2

Implement 2 input AND gate using mux

Ans: (AND)  $Y = AB$

Equation of MUX,

$$Y = \bar{S} I_0 + S I_1$$

We want  $Y = AB$ ,  
 So make  $\bar{S} I_0 = 0$   
 $\bar{S}$  can not be 0,  
 because if  $\bar{S} = 0 \Rightarrow S = 1$

$$S I_1 = 1 \cdot I_1 = I_1$$

But we want  $S I_1 = AB$ .


$\therefore$  since  $\bar{S} \neq 0, I_0 = 0$  (because we want  $\bar{S} I_0 = 0$ )

Let's take  $S = A$   
 $I_1 = B$   
 $\bar{S} = \bar{A}$   
 $I_0 = 0$

$$Y = \bar{S} I_0 + S I_1$$

$$= \bar{A} \cdot 0 + A \cdot B$$

$$Y = AB$$

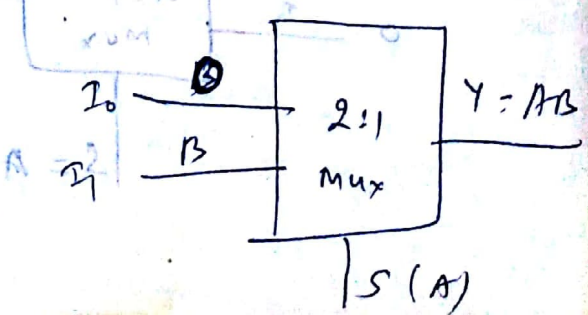

2

so x

$I_1 = A \cdot B$

$I_2 = A \cdot \bar{B}$

$\bar{I}_2 = \bar{A} \cdot B$


$I_0 = \bar{A} \cdot \bar{B}$

$Y = \bar{I}_2 \cdot I_0 + I_1 \cdot I_2$

$= \bar{A} \cdot B \cdot \bar{A} \cdot \bar{B} + A \cdot B \cdot A \cdot B$


$= \bar{A} \cdot B \cdot A \cdot B$

$= A \cdot B$

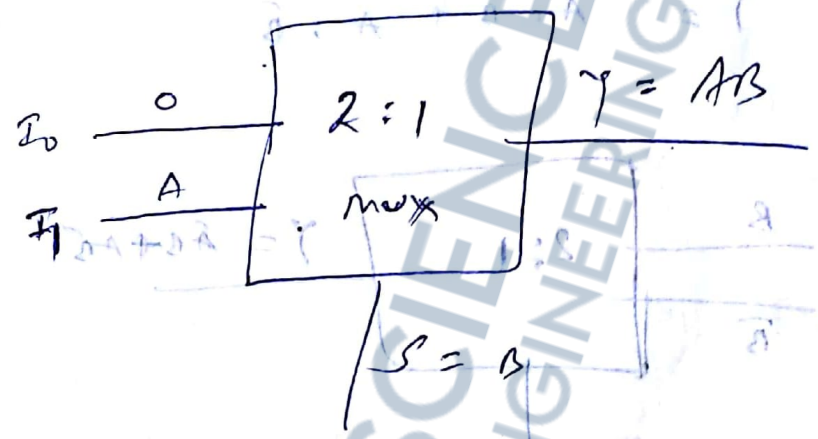

Ex 3

Using 4-to-1 mux

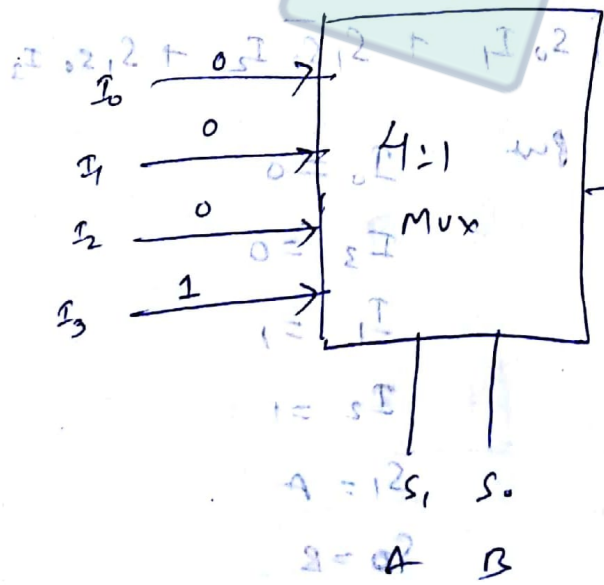

$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$

~~$Y = \bar{A} \cdot \bar{B} \cdot 0 + \bar{A} \cdot B \cdot 0 + A \cdot \bar{B} \cdot 0 + A \cdot B \cdot 1$~~

$Y = \bar{A} \cdot \bar{B} \cdot 0 + \bar{A} \cdot B \cdot 0 + A \cdot \bar{B} \cdot 0 + A \cdot B \cdot 1$

$= A \cdot B$  (AND gate)



Implement 2:1/2 X-OR gate using MUX.

Ans :


$$Y = \bar{A}B + A\bar{B}$$

But the eqn

$$Y = \bar{S}I_0 + SI_1$$


Let  $S = A, I_0 = B, I_1 = \bar{B}$

$$Y = \bar{A} \cdot B + A \cdot \bar{B}$$

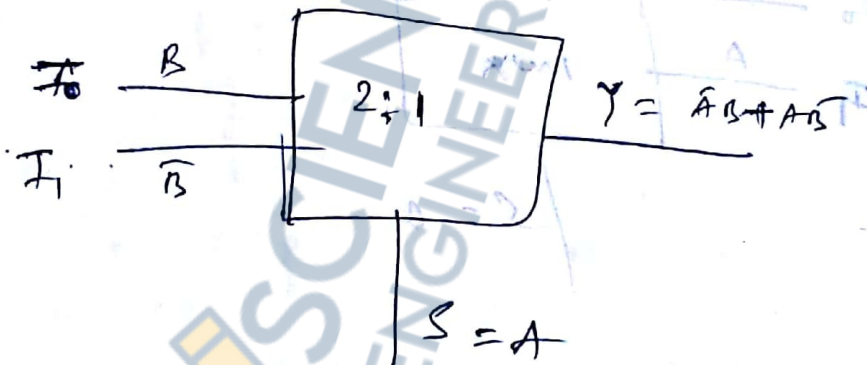


Using 4:1 MUX
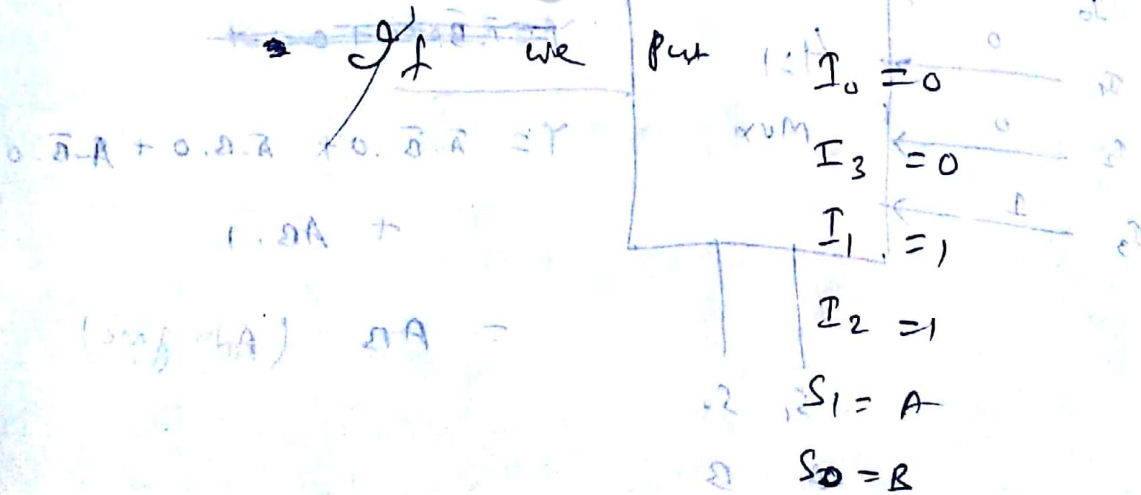
$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



$$Y = 0 + \bar{A}B \cdot 1 + A\bar{B} \cdot 1 + 0$$

$$= \bar{A}B + AB$$

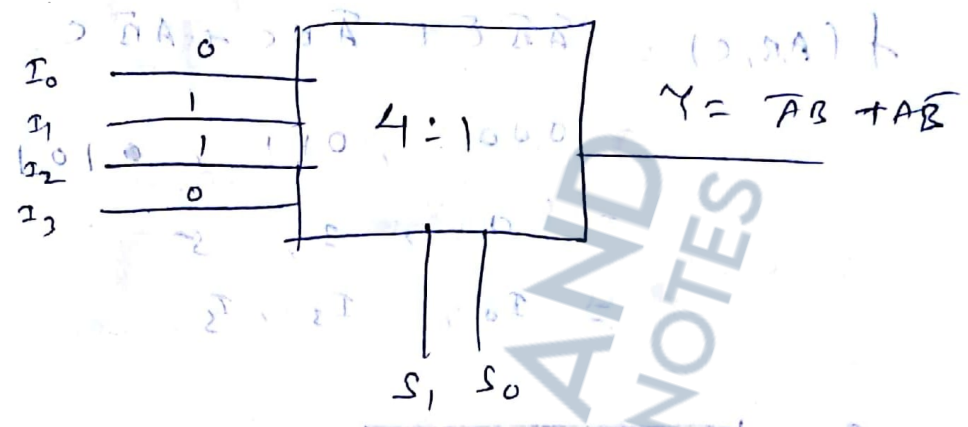


XNOR =  $\bar{A}B + AB$  Similar

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

- If we put,
- $I_0 = 0$
  - $I_1 = 0$
  - $I_2 = 1$
  - $I_3 = 1$
  - $S_1 = A$
  - $S_0 = B$
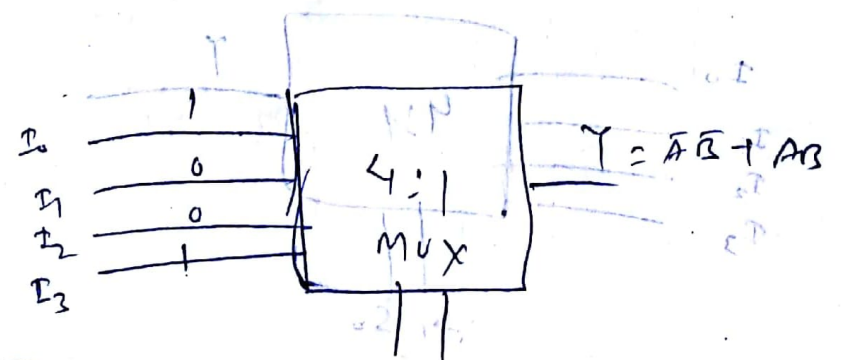
$$Y = \bar{A}\bar{B} \cdot 0 + 0 + AB \cdot 1 + AB \cdot 1$$





Ex: - 4

①

97

Implement

$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

using 8:1 MUX


Ans:

$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

$$= 000, 010, 100$$

$$= 0, 2, 4$$

$$= I_0, I_2, I_4$$

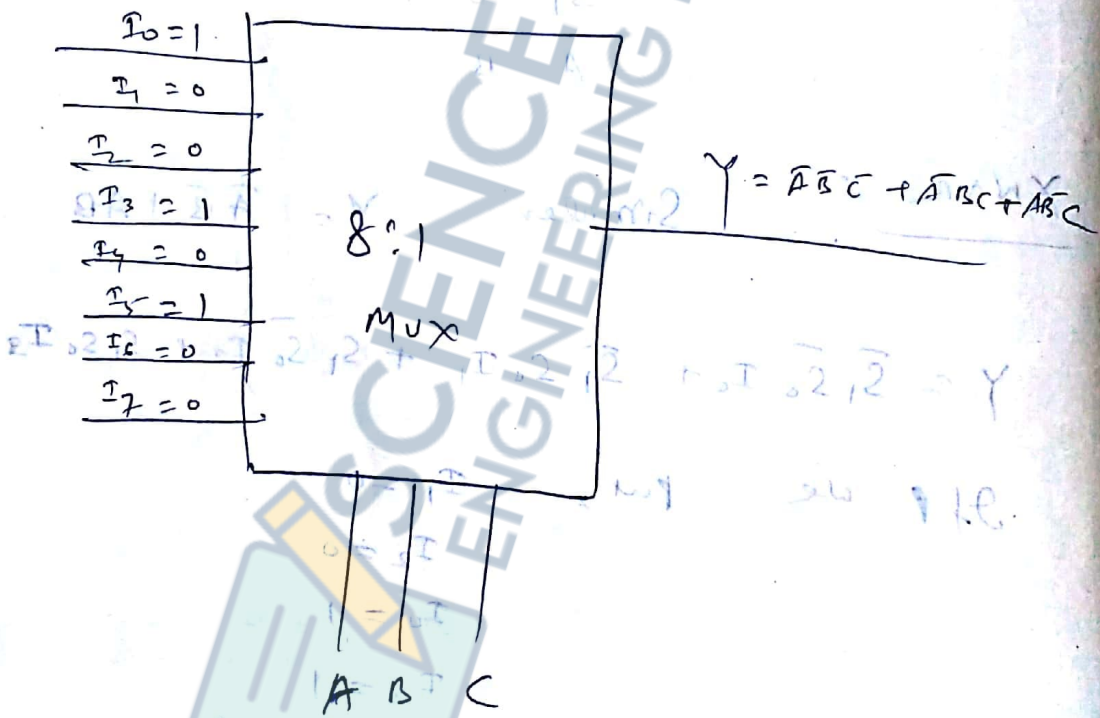


Ex: - 5

Realize


4:1 MUX

using

2:1 MUX

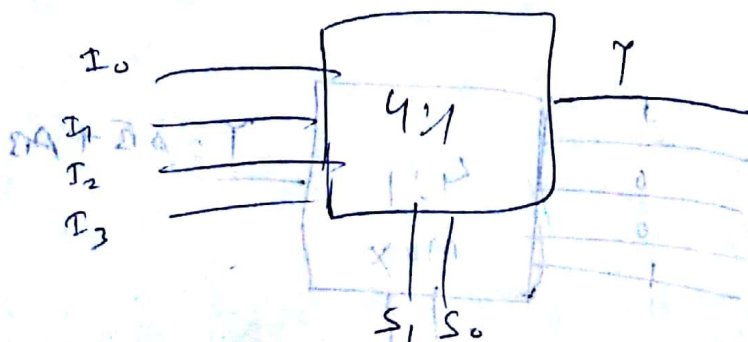

$S_1$	$S_0$	
0	0	} $Y_1$
0	1	
1	0	} $Y_2$
1	1	

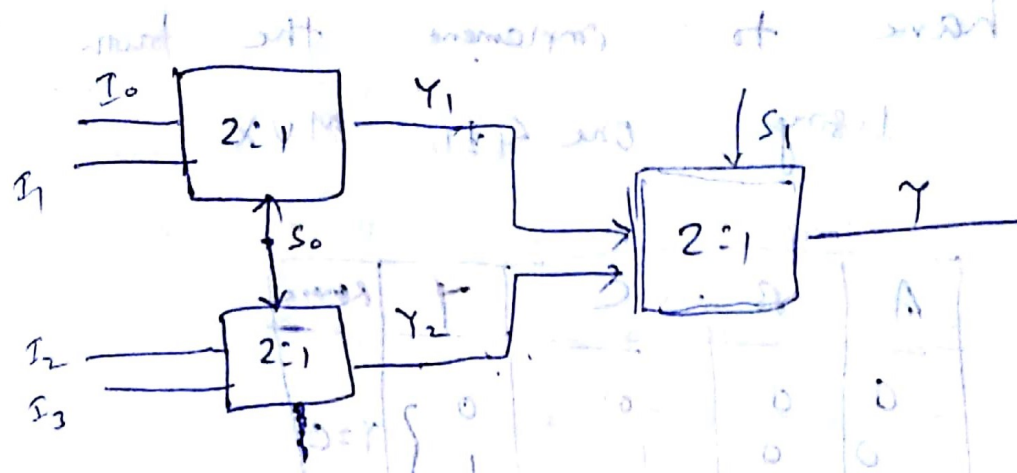

< we have 4 I/P pins & 2 select pin. Use ~~three~~ 2:1 MUX to construct the functionality of 4:1 MUX >

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

BIUT 2019  
Ex - 5

Hw) 1) 8:1 mux using 4:1 mux  
2) 8:1 mux using 2:1 mux

Implement the following boolean function with a 4:1 MUX.

$$f(x, y, z) = \sum (1, 2, 6, 7)$$


Ans: The truth table for the boolean function is given below

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1




We have to complement the truth table using one 4:1 MUX

A	B	C	Y	Remark
0	0	0	0	} $Y=C$
0	0	1	1	
0	1	0	1	} $Y=\bar{C}$
0	1	1	0	
1	0	0	0	} $Y=0$
1	0	1	0	
1	1	0	1	} $Y=1$
1	1	1	1	

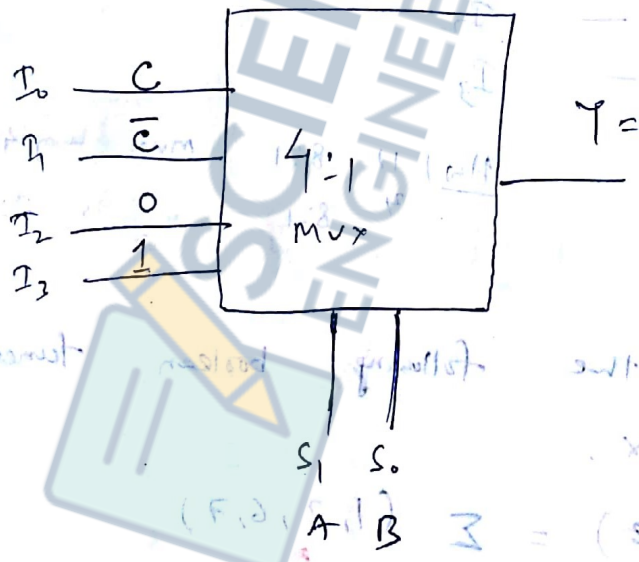

Using 8:1 mux

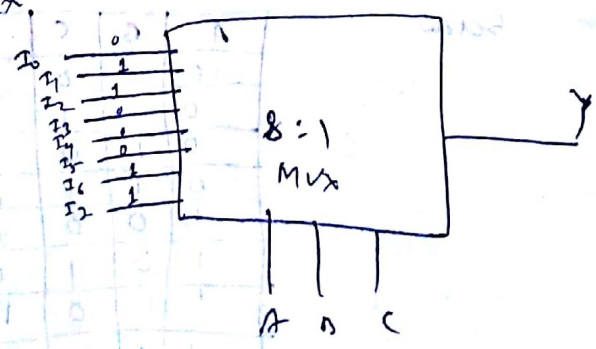o/p is 1,  
 at 1, 2, 6, 7  
 i.e.  
 $I_1, I_2, I_6, I_7$





# Demultiplexer

Demultiplexer (DE-MUX) is a <sup>logic</sup> combinational circuit that performs the reverse operation of MUX.

It has one i/p & many o/p's. The i/p information is transmitted to a particular o/p line depending on the data available at the selector line.

1:2 DE-MUX

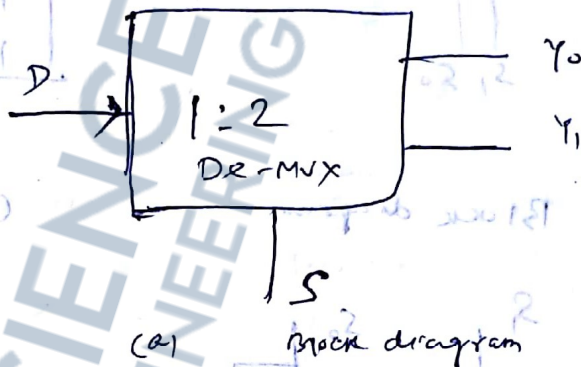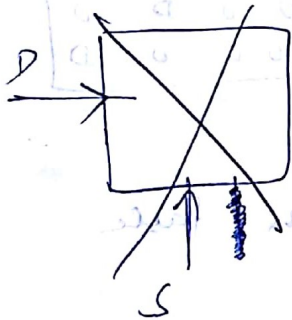


S	Y <sub>0</sub>	Y <sub>1</sub>
0	D	0
1	0	D

$$Y_0 = \bar{S}D$$

$$Y_1 = SD$$

(b) Truth table

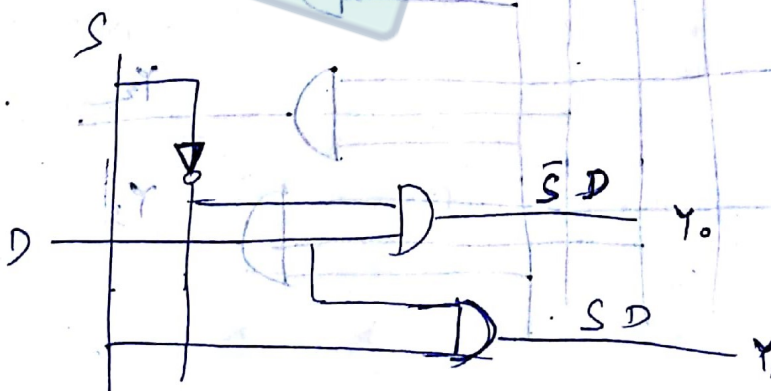

(c) Logic circuit



1:4

DE-MUX


Here 1 (input) & 4 (output), so it has

2 M select line

Input  $\rightarrow D$

Output  $\rightarrow Y_0, Y_1, Y_2, Y_3$


Select line -  $S_1, S_0$

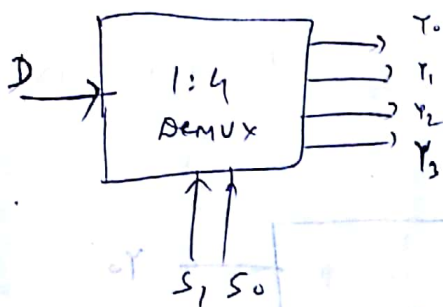

$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

(a) Block diagram

(b) Truth table

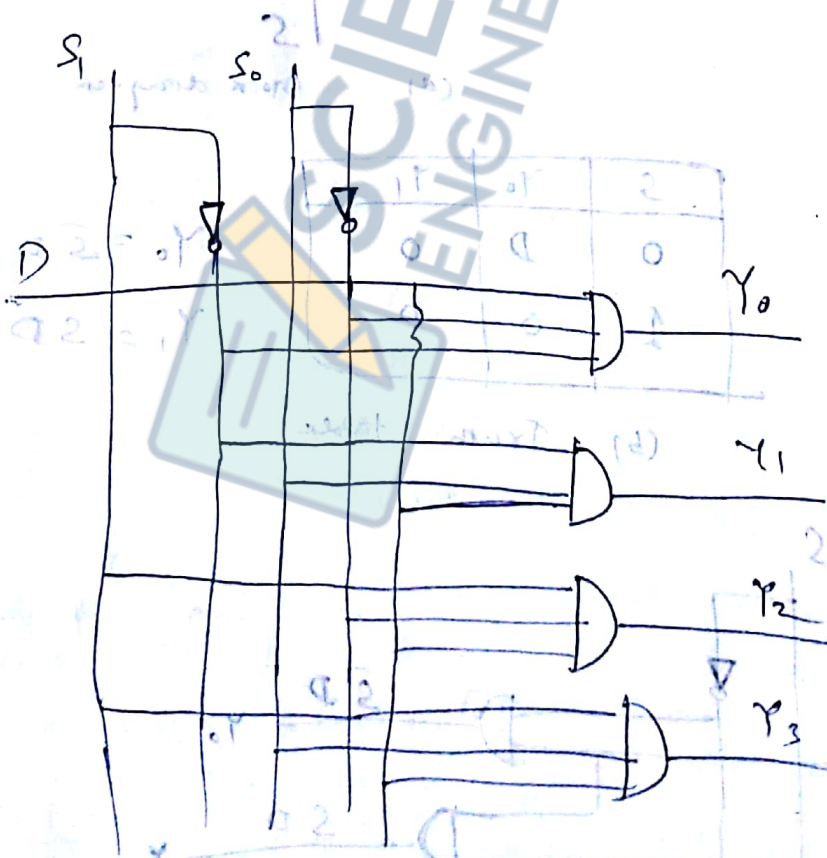

(c) Logic circuit.

$Y_0 = \bar{S}_1 \bar{S}_0 D$

$Y_1 = \bar{S}_1 S_0 D$

$Y_2 = S_1 \bar{S}_0 D$

$Y_3 = S_1 S_0 D$

Ex:-

Multiplexes



Demultiplexer

- 1) It is a data selector.
- 2) It has many I/P and single O/P.
- 3) Parallel to Serial Converter.
- 4) It has  $2^n$  no of I/P,  $n$  select line and 1 O/P.

- 1) It is a data distributor.
- 2) It has single I/P and many O/P.
- 3) Serial to Parallel Converter.
- 4) It has 1 I/P,  $n$  select line and  $2^n$  O/P.

5) Ex:-

5) Ex:-

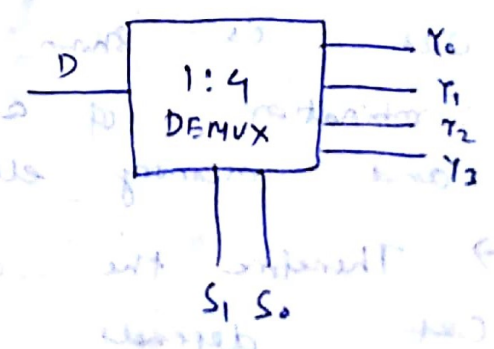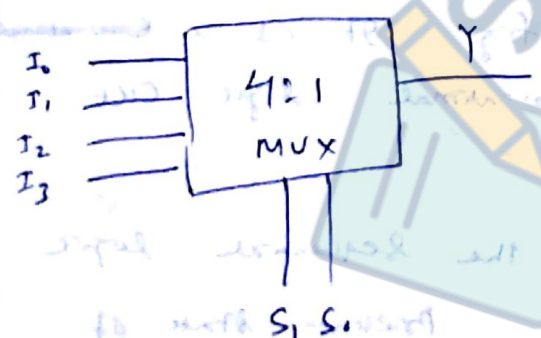




# MUX as Universal gate

1) NOT gate using 2:1 MUX

A	Y
0	1
1	0

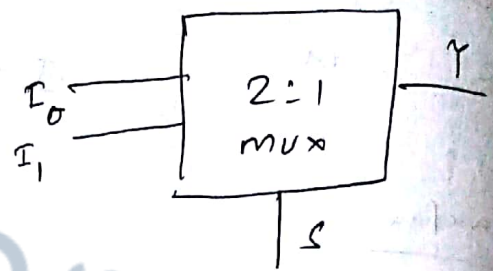

Step 1:- We have one select line. A select line can take 2 values '0' or '1'. So let's take 'A' as select line because it has value 0 & 1.


Step 2:- when

$$A = 0, Y = I_0$$

$$A = 1, Y = I_1$$

A	Y
0	$I_0$
1	$I_1$

— (1)

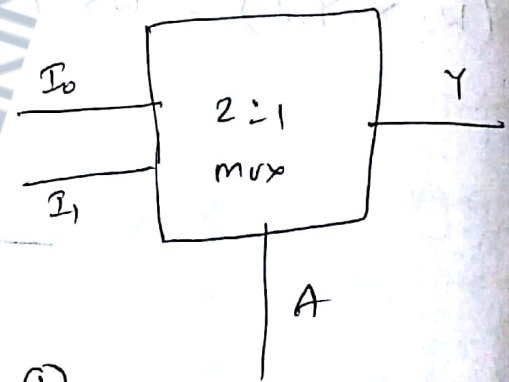

Step 3:- Relation of Y with A

$$Y = \bar{A}$$

( when  $A = 0, Y = 1$   
when  $A = 1, Y = 0$  )


A	Y	$\bar{A}$
0	1	$\bar{A}$
1	0	$\bar{A}$

— (2)

Equating ① & ②


$$I_0 = \bar{A}$$

$$I_1 = A$$


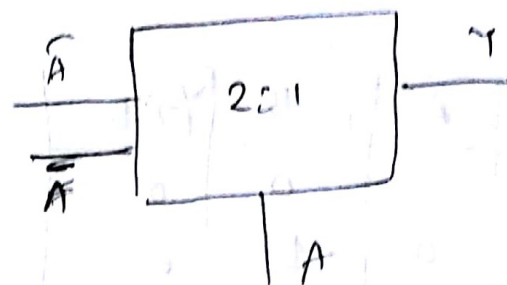


ex:-

When  $A=0$

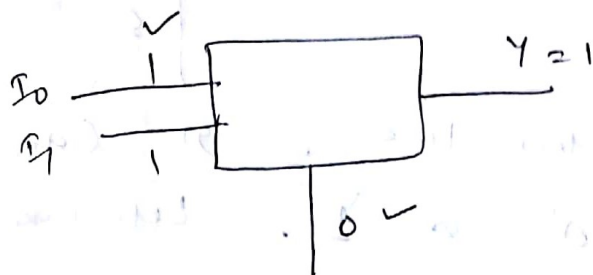

When  $A=1$

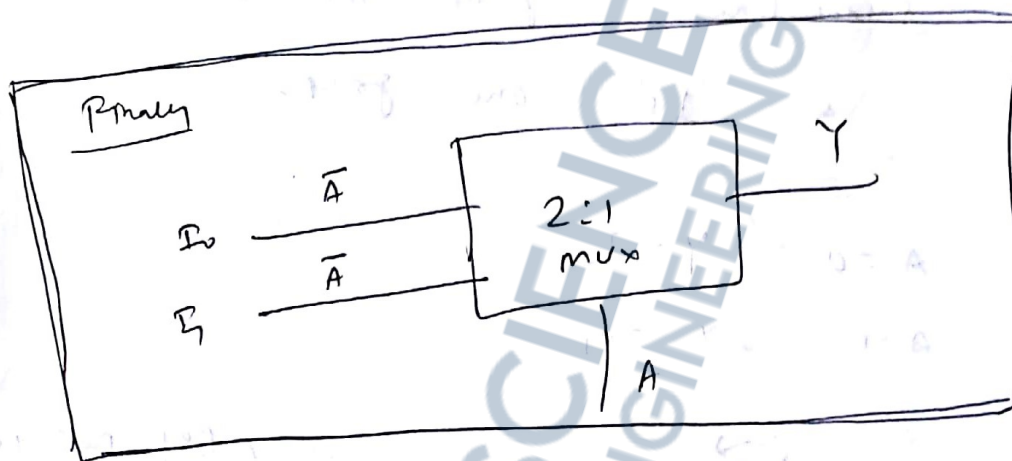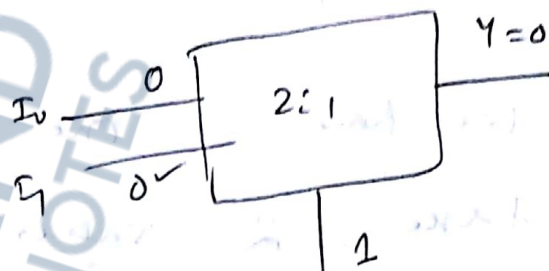

Answer 1

~~AND gate~~


(52)

Equating ① & ②

$$I_0 = 1$$

$$I_1 = 0$$

Answer 2

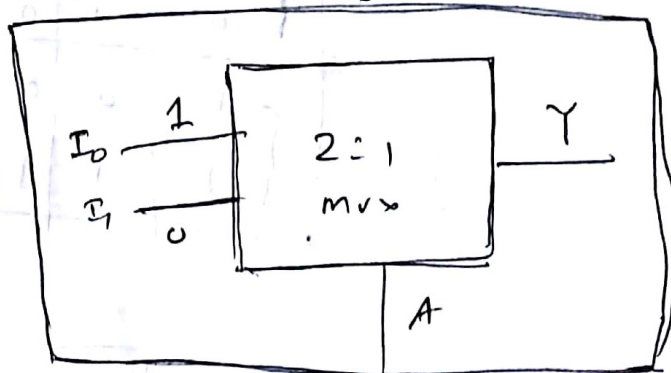

Verify

When  $A=0$ ,  $I_0$  is selected  $\Rightarrow Y=1$ .  
 When  $A=1$ ,  $I_1$  is selected  $\Rightarrow Y=0$ .  
 } Act as NOT gate


$$\text{Verify; } Y = \bar{A} \cdot I_0 + A \cdot I_1 = \bar{A} \cdot 1 + A \cdot 0 = \bar{A}$$



2)

AND gate

A	B	$Y=AB$
0	0	0
0	1	0
1	0	0
1	1	1

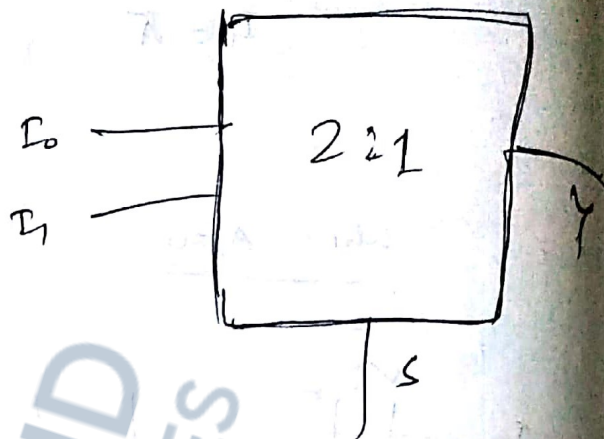

We have one select line. It can take 2 values '0' or '1'. Let's take 'A' as select line group the '0's' as one group a '1's' one group.


For  $A=0, Y=I_0$   
 $A=1, Y=I_1$

A	B	Y	Y	Remark (Ref <sup>n</sup> Best Y and B)
0	0	0	$I_0$	<del>0</del> 0
	1	0		
1	0	0	$I_1$	<del>B</del> B
	1	1		

is always  $Y=0$ , independent of B.  
 $Y=B$

$\therefore I_0 = 0$

$\therefore I_1 = B$

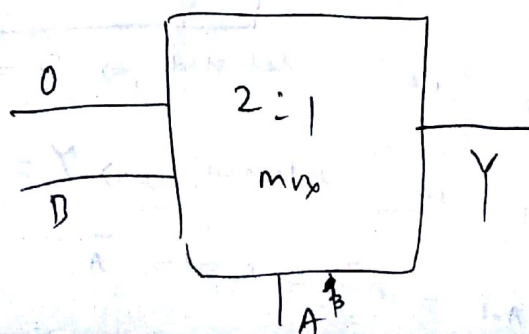

Verify

$$Y = \bar{S} I_0 + S I_1$$


$$= \bar{A} \cdot 0 + A \cdot B$$

3)

OR gate = AB

A	B	Y	Y	Y
0	0	0	$I_0$	B
0	1	1	$I_1$	1
1	0	0		
1	1	1		

A2 Select line

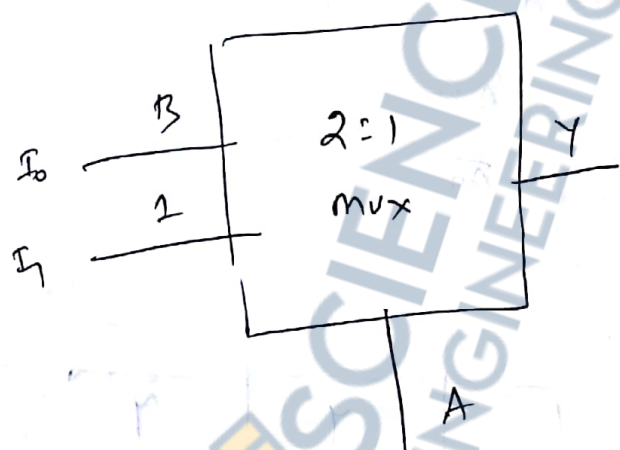

Verify ( $Y = \bar{S} I_0 + S I_1$ )

$$Y = \bar{A} \cdot B + A \cdot 1$$

$$= A + \bar{A} B$$

$$= (A + \bar{A})(A + B)$$


$$Y = A + B$$

4)

NAND gate:

A	B	Y	Y	Y
0	0	1	$I_0$	1
0	1	1	$I_1$	$\bar{B}$
1	0	0		
1	1	0		



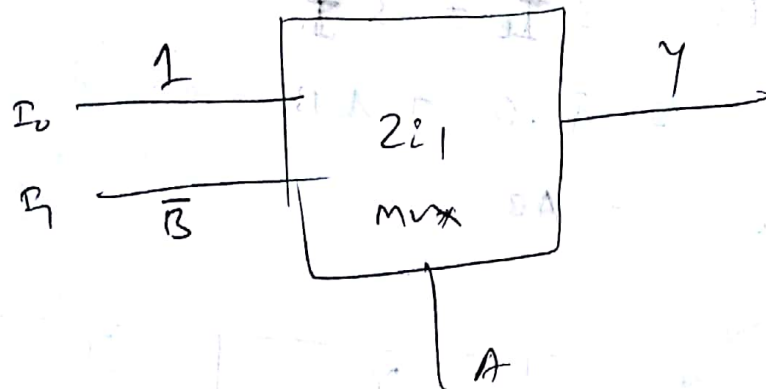


Verify :

$$\begin{aligned}
 Y &= \bar{1}I_0 + 1I_1 \\
 &= \bar{A} \cdot 1 + A \cdot \bar{B} \\
 &= \bar{A} + A\bar{B} \\
 &= (\bar{A} + A)(\bar{A} + \bar{B}) \\
 &= \bar{A} + \bar{B} \\
 Y &= \overline{AB}
 \end{aligned}$$

5) MUX


A	B	Y	Y	Y
0	0	1	I <sub>0</sub>	$\bar{B}$
0	1	0	I <sub>1</sub>	0
1	0	0		
1	1	0		

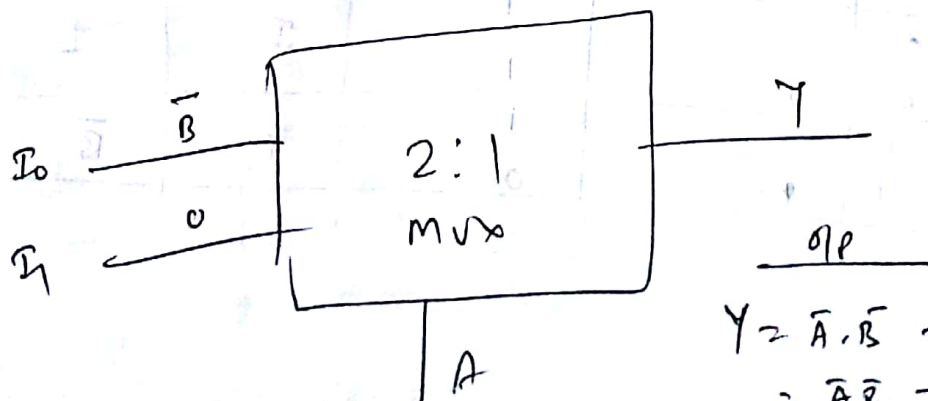

$$\begin{aligned}
 Y &= \bar{A} \cdot \bar{B} + A \cdot 0 \\
 &= \bar{A}\bar{B} = \overline{AB}
 \end{aligned}$$

6) Ex-OR


A	B	Y	Y	Y
0	0	0	$\bar{A} \cdot \bar{B}$	$\bar{B}$
0	1	1	$\bar{A} \cdot B$	$\bar{A}$
1	0	1	$A \cdot \bar{B}$	$A$
1	1	0	$A \cdot B$	$B$

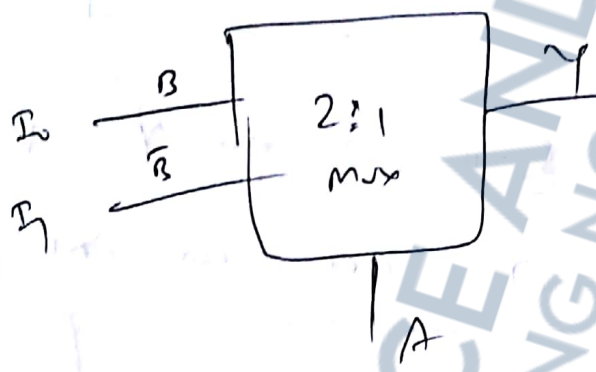

Verth:  $Y = \bar{A} \cdot B + A \cdot \bar{B} = A \oplus B$

7) Ex-NOR

A	B	Y	Y	Y
0	0	1	$\bar{A} \cdot \bar{B}$	$\bar{B}$
0	1	0	$\bar{A} \cdot B$	$\bar{A}$
1	0	0	$A \cdot \bar{B}$	$A$
1	1	1	$A \cdot B$	$B$

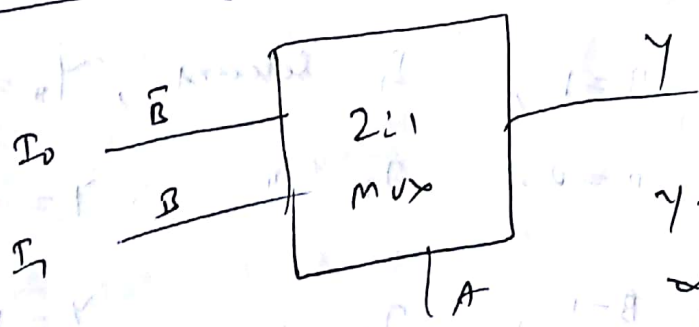

$Y = \bar{A} \cdot \bar{B} + A \cdot B$   
 $Y = A \odot B$

(verified)




8)

Implementation

$Y = AB$


Using

4:1 MUX

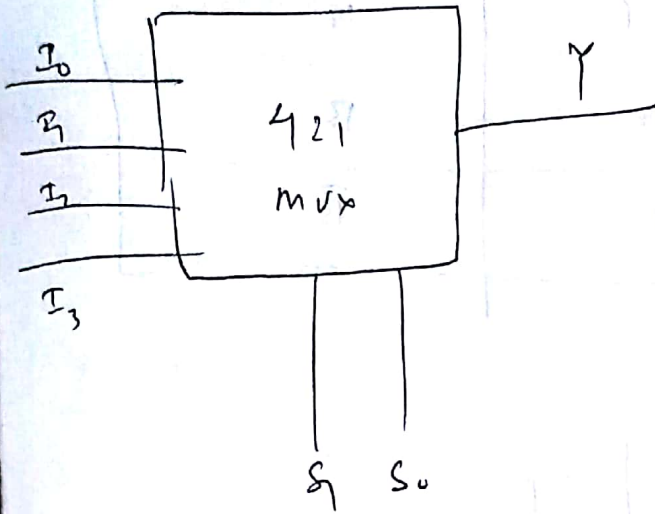

A	B	Y	$Y$
0	0	0	$I_0$
0	1	0	$I_1$
1	0	0	$I_2$
1	1	1	$I_3$

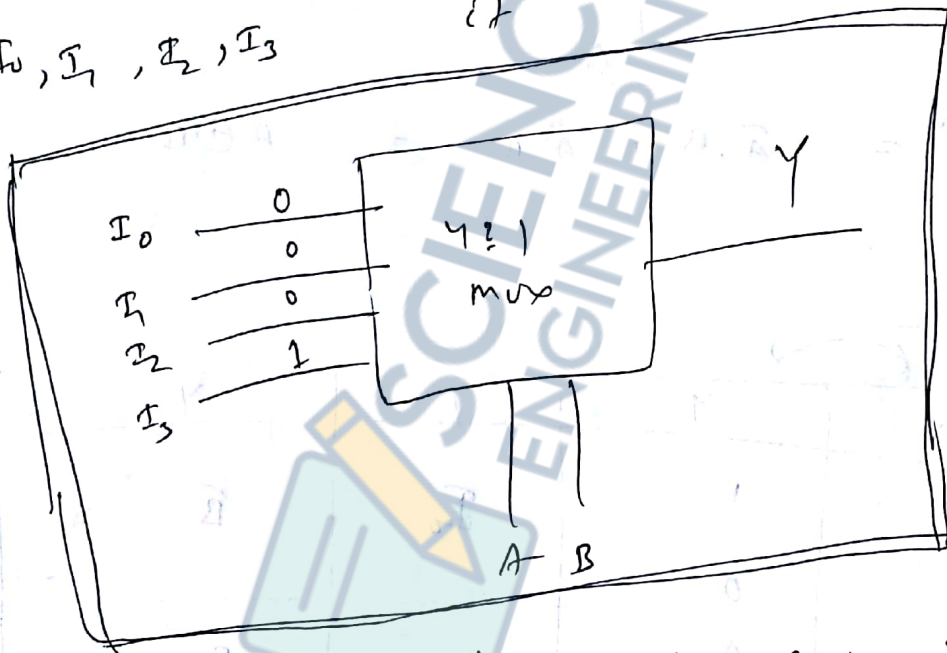If  $S_1 = A$  &  $S_0 = B$  are  $Y$  values to  $I_0, I_1, I_2, I_3$  act as AND gate



Ex. When  $A=0, B=0, I_0$  is selected value is '0'.

When  $A=0, B=1, I_1$  selected,  $Y=0$

$A=1, B=0, I_2$  " " ,  $Y=0$


$A=1, B=1, I_3$  " " ,  $Y=1$

∴ It behaves as AND gate.

1) Similarly other gates can be implemented using 4:1 MUX. With A, B select line &  $I_0, I_1, I_2, I_3$  one four table values.  $\therefore$  that gate-

Ex:

A + B

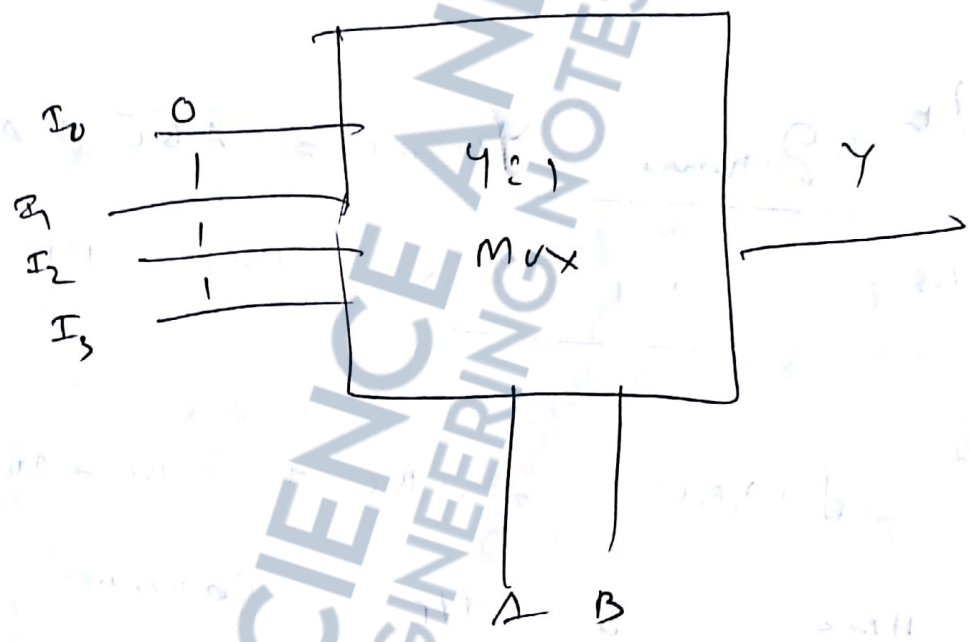

Implementation of any function using MUX

- First check what are the ~~inputs~~ combinations required.
- ~~if~~ (Ex:- AND gate: 4 combinations)
- Then check what are the i/p line available.
- if 2:1 MUX → 2 i/p line →  $I_0, I_1$
- if 4:1 MUX → 4 " " →  $I_0, I_1, I_2, I_3$
- if 2 i/p line then we have to make a group -



$$A_2 \begin{cases} 0 \\ 0 \end{cases} \rightarrow 1 \text{ group} \rightarrow I_0$$

$$A_2 \begin{cases} 1 \\ 1 \end{cases} \rightarrow 1 \text{ group} \rightarrow I_1$$

If 4 lines for 4 possible combinations, no need of grouping fourth case. Just assign the corresponding values to  $I_0, I_1, I_2, I_3$ .

Ex 10)

Implement  $f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C$

using 8:1 mux, using 4:1 mux, 2:1 mux

Ans 2

$$f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C$$

Here 8 combinations, if we use a 8:1 mux, just we have to assign the fourth case values.


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = 000, 011, 101$$

$$= 0, 3, 5$$

$$= I_0, I_3, I_5$$

$\therefore I_0, I_3, I_5$  will be 1 and rest will be zero. A, B, C are the select lines.

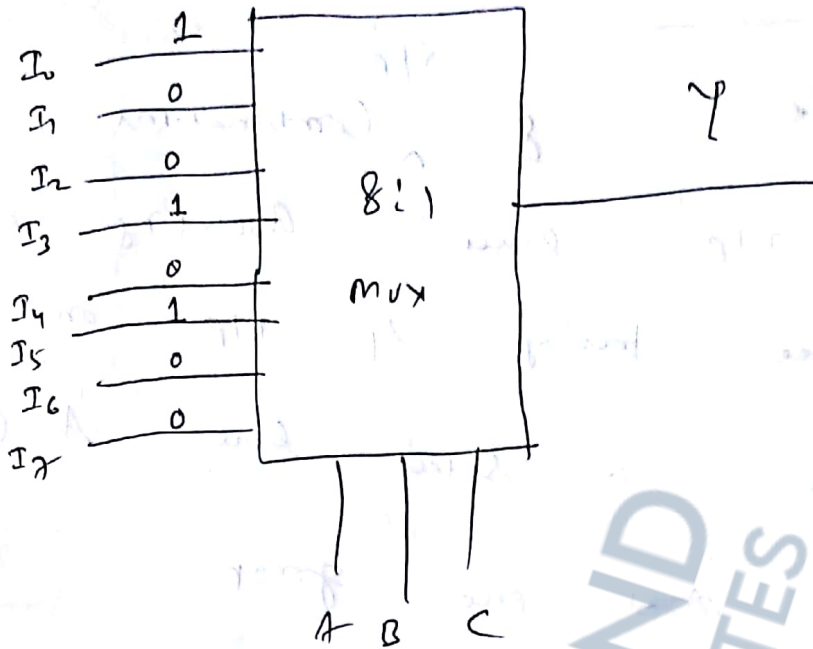

Using 4:1 MUX

A	B	C	Y	Y	Y
0	0	0	1	$I_0$	$\bar{C}$
0	0	1	0		
0	1	0	0	$I_1$	C
0	1	1	1		
1	0	0	0	$I_2$	C
1	0	1	1		
1	1	0	0	$I_3$	0
1	1	1	0		

8 r/r combination

We have 4

output line.

So we have to

make grouping.


Let's say

'A' as the

select line.

00, 01, 10, 11

4 groups.

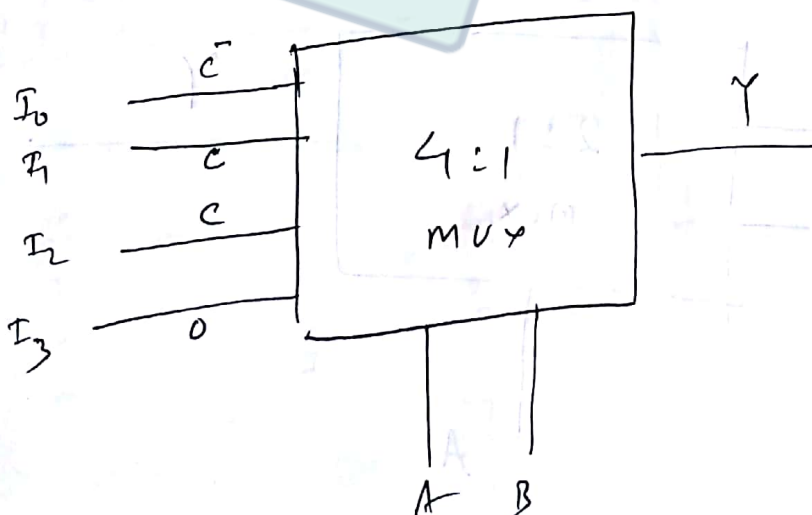



We have 8 combinations, but we have 2 1/1P lines, grouping is made taking 4 1/1P one group.


→ We have a select line 'A' (lets say)

→ A = 0, ~~A = 0~~ one group

A = 1, another group.

A	B	C	Y	Y	Y
0	0	0	1	I <sub>0</sub>	$\bar{B}\bar{C} + BC$
0	0	1	0		
0	1	0	0		
0	1	1	1		
1	0	0	0	I <sub>1</sub>	$\bar{B}C$
1	0	1	1		
1	1	0	0		
1	1	1	0		


Rel<sup>n</sup> of B and C with Y

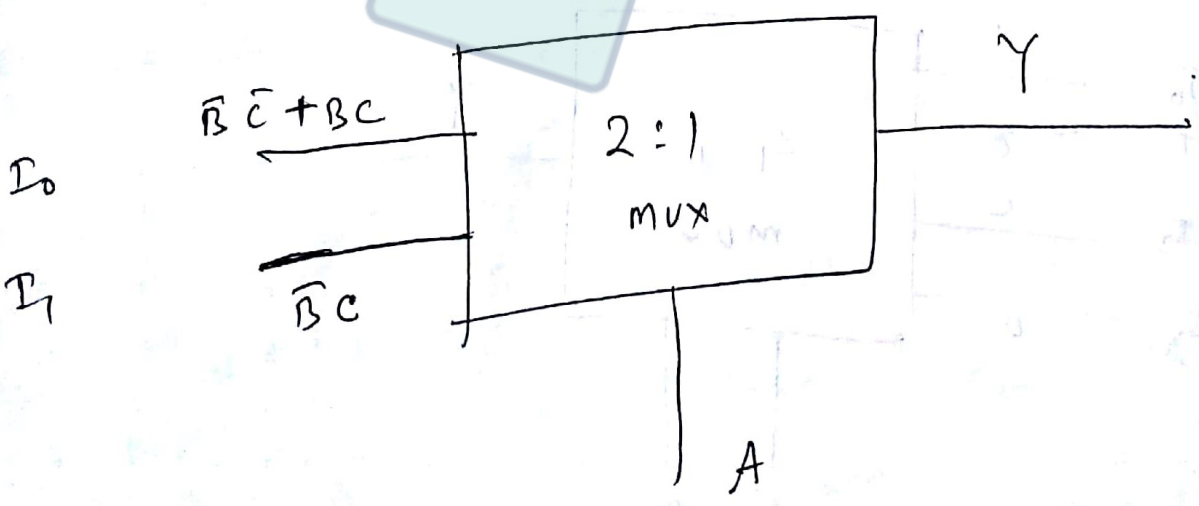


10/11/2009  
BPUT-2009

$f(A, B, C) = \sum(1, 2, 6, 7)$  Using 4:1 MUX.

A	B	C	$\gamma$	$\gamma$	$\gamma$
0	0	0	0	$I_0$	$\gamma = C$
0	1	0	1	$I_1$	$\gamma = \bar{C}$
1	0	0	0	$I_2$	$\gamma = 0$
1	1	0	1	$I_3$	$\gamma = 1$
1	1	1	1		

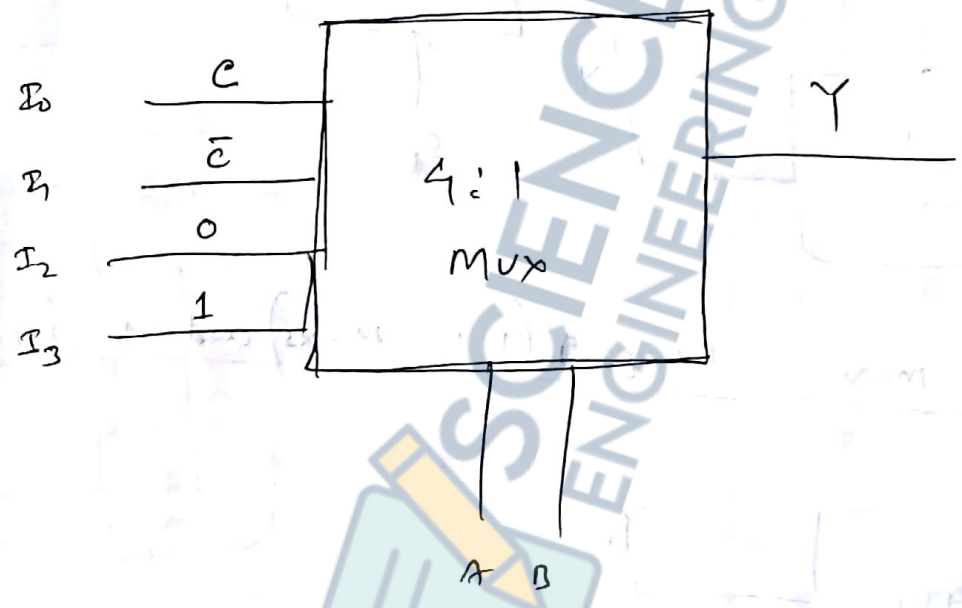


11) Realize 4:1 MUX using 2:1 MUX

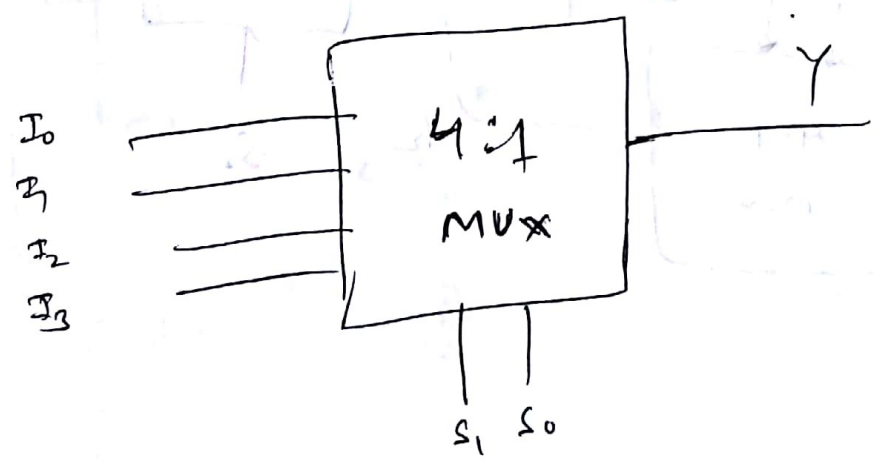




$S_1$	$S_0$	$Y$	$Y$
0	0	$I_0$	$Y_1$
0	1	$I_1$	
1	0	$I_2$	$Y_2$
1	1	$I_3$	

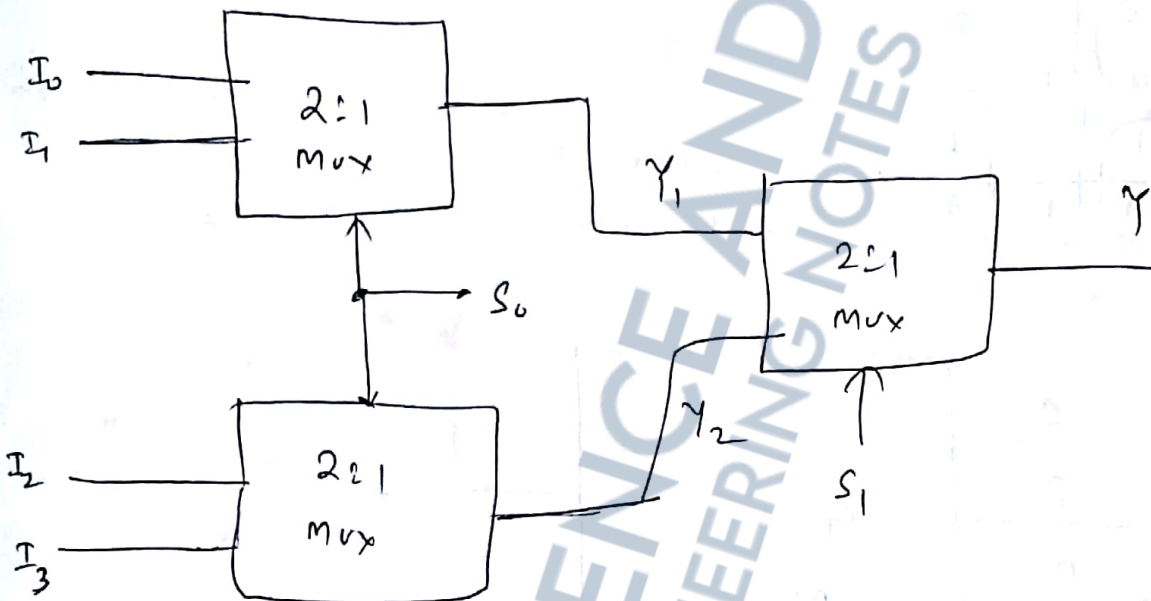

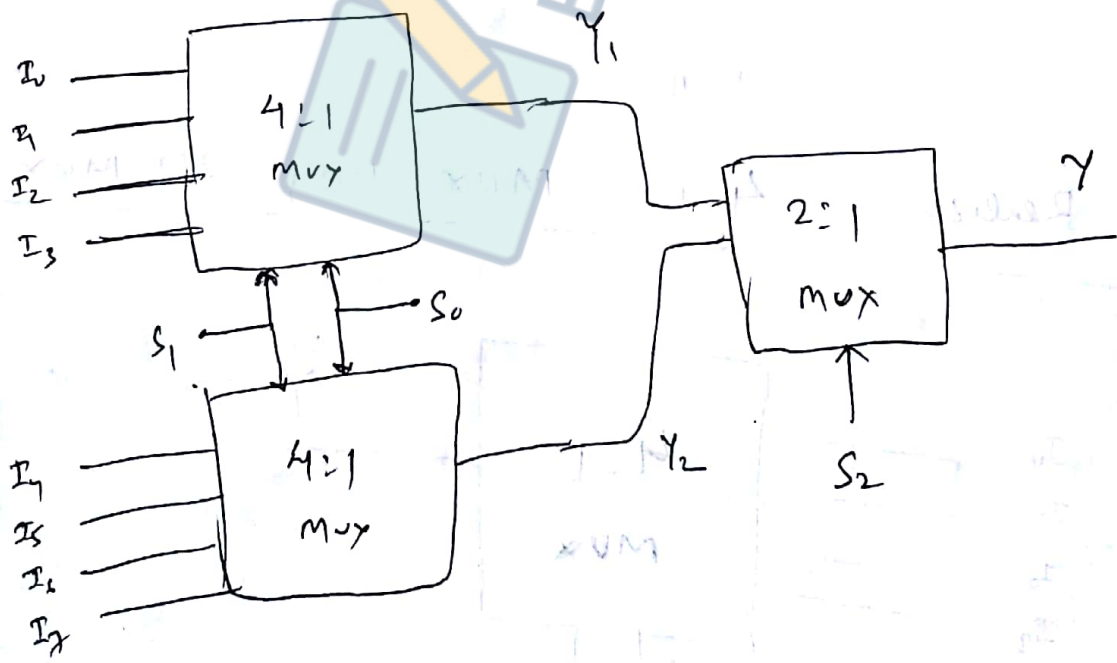12) 8:1 mux using 2 (4:1 muxs) and 1 (2:1 mux)



$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

Pr

$S_2 = 0$ ,  $Y_1$  is selected.

$Y_1$  depends on  $S_1, S_0$ .

Let's check

$S_2 = 0, S_1 = 0, S_0 = 0$ .


$S_1 = 0, S_0 = 0, Y_1 = I_0$

$Y_2 = I_4$

Again since  $S_2 = 0$ ,

$Y_1$  is selected i.e.  $I_0$ .

8:1 Mux Using 2:1 Mux

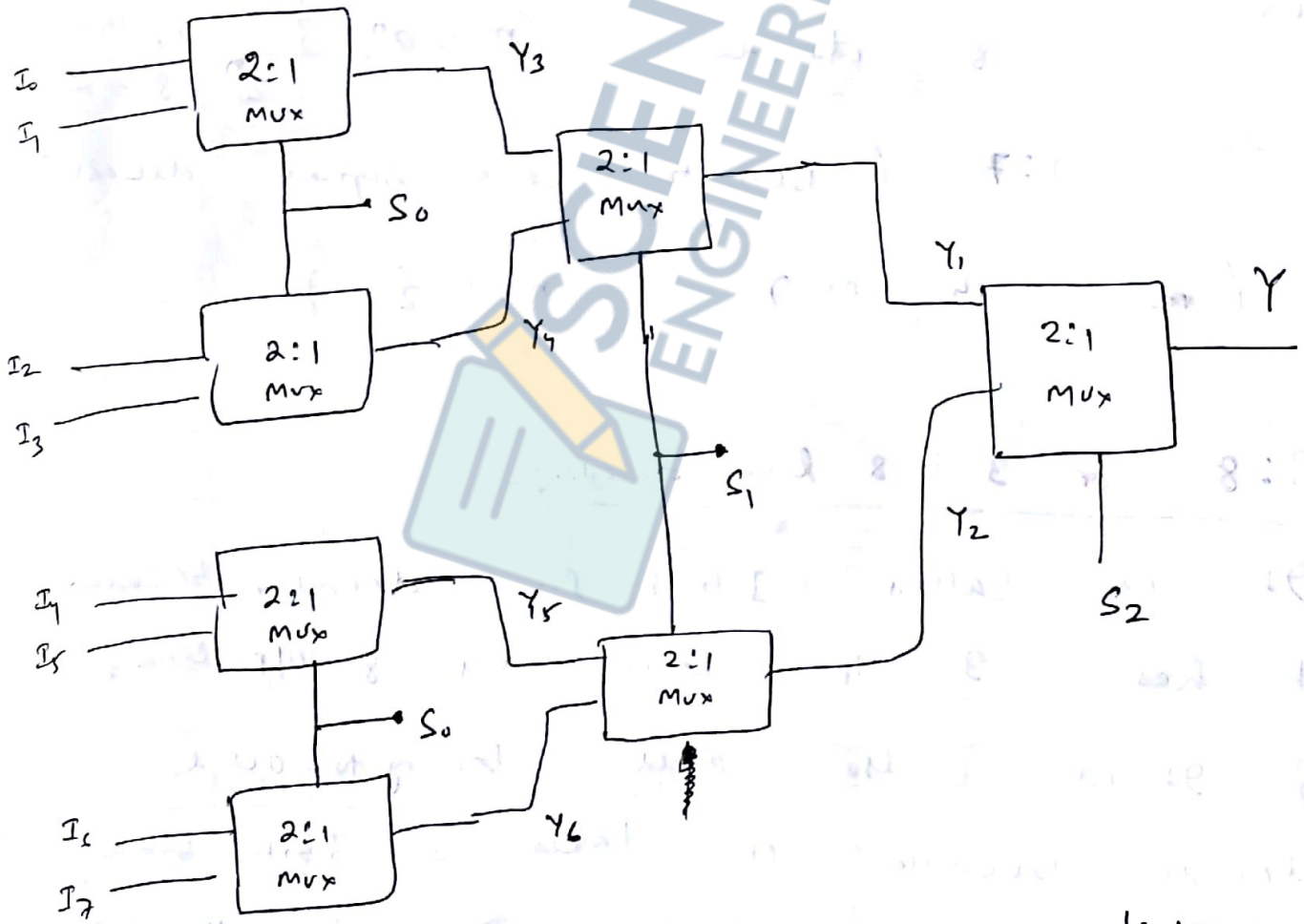

Total

2:1 Mux

required =  $4 + 2 + 1$


= 7


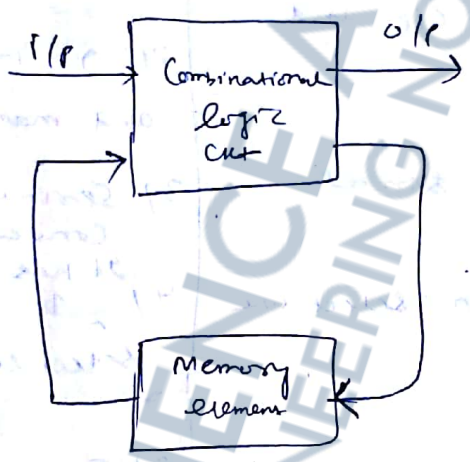
# Sequential Logic cut :-

→ In sequential logic cut, the o/p not only depends upon the present i/p but also depends on the past i/p.

→ Although every digital system is likely to have combinational cuts, most systems encountered in practice also include storage elements.



→ ~~is~~ A block diagram of sequential cut is shown in fig. It is a ~~combination~~ combination of a combinational logic cut and memory element.

→ Therefore the o/p of the sequential logic cut depends on the present state of i/p and state of the memory element.

→ The state of memory element in term depends on the previous state o/p, which in term depends on the previous state i/p.

→ The Basic sequential logic cuts are Latch and flip-flops.

Latches :-


→ A latch is a type of temporary storage device that has 2 stable states (bistable)

→ Two stable states are **SET (1)** and **RESET (0)**. they can retain either of these states indefinitely, making them useful as storage devices.

→ For storing 1 bit data, latch is used.  
SR Latch :-

→ The SR Latch is a circuit with 2 cross-coupled NOR gates or two cross-coupled NAND gates.

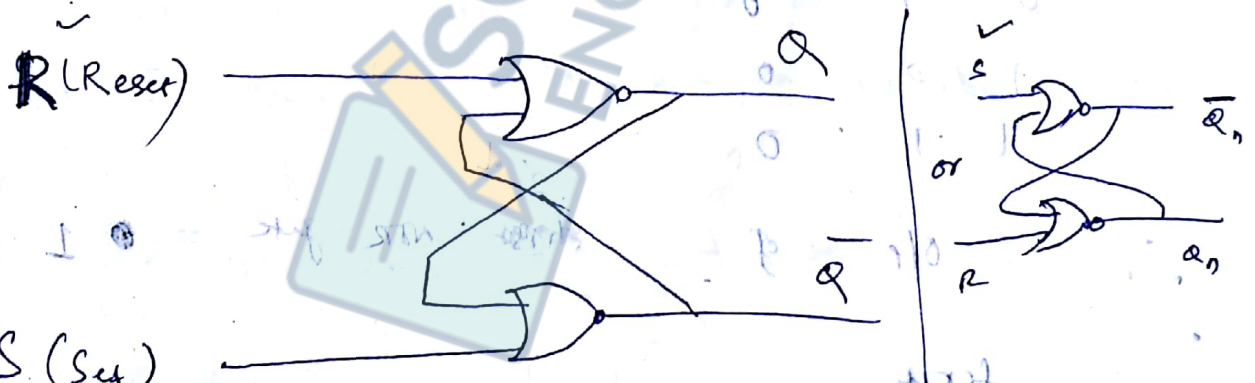→ It has 2 inputs labeled S for Set and R for Reset



S (Set)

Jump

S	R	Q <sub>n+1</sub>	Q̄ <sub>n+1</sub>	Remarks
0	0	Q <sub>n</sub>	Q̄ <sub>n</sub>	No change
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Invalid

→ In this case, it acts as storage element


NOT used





Case - II

$S = 0$  ,  $R = 1$  ,  $Q = 1$

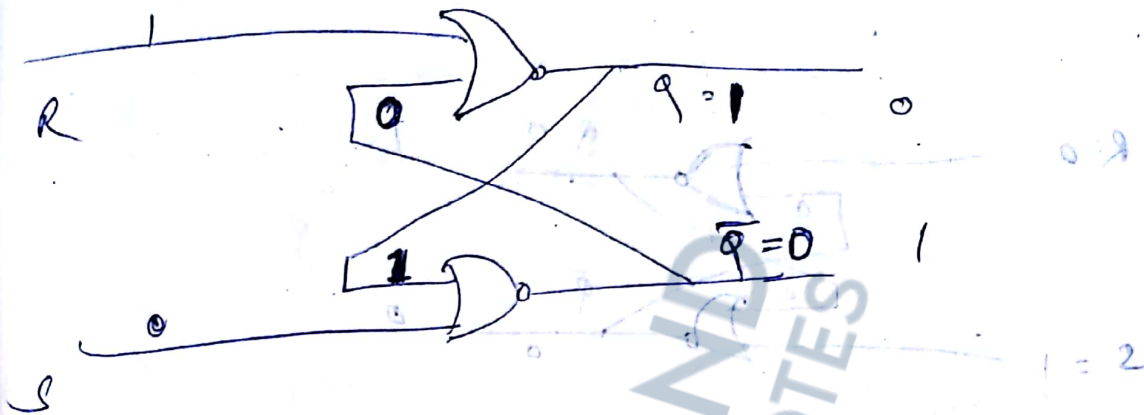

Let  $Q = 1$

i/p for 2nd NOR gate is  $1, 0$   
o/p is 0.

Now i/p for first NOR gate is  $1, 0$   
(because o/p of 2nd NOR gate connected to first NOR gate)

o/p of first NOR gate is 0.  
Now the 0 will be connected to 2nd NOR gate i.e.  $0, 0$  i/p.  
o/p of 2nd NOR gate will be 1.

$Q = 0$  ,  $\bar{Q} = 1$


∴  $Q$  is reset to 0.

S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remark
0	1	0	1	Reset.



Qn - III

$S = 1, R = 0, Q = 0, \bar{Q} = 1$

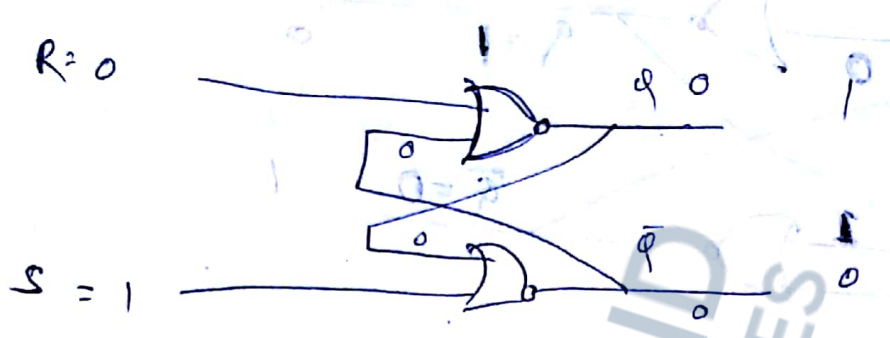

$Q = 0$   
 off for 2nd gate is 0, 1  
 off of 2nd NOR gate is 0

Now, off for first gate is 0, 0  
 off of 1st NOR gate is 1,  $\bar{Q}$


Now off for 2nd gate is 1, 1  
 off of 2nd gate is 0,  $\bar{Q}$

$\therefore Q$  is now set to 1.

$S$	$R$	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remarks
1	0	1	0	Set

1	0	1	0	2
---	---	---	---	---


$S = 1, R = 1, Q = 0$

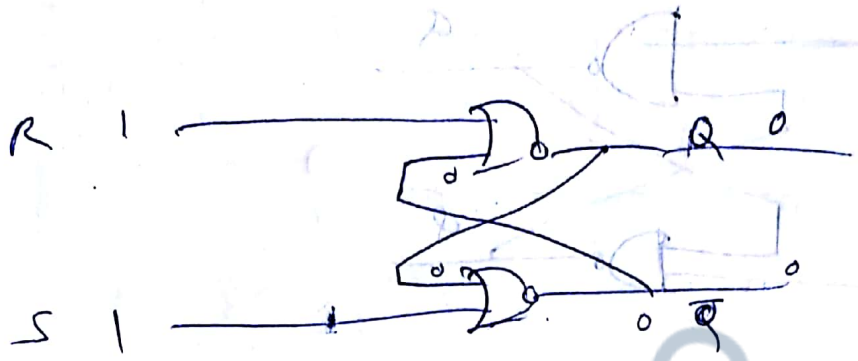

$Q = 0$	flip for 2nd NOR gate	is	$0, 1$
	of 1	" "	$0$
Now	flip for first NOR gate	is	$1, 0$
	of first NOR gate	is	$0$

From now onwards the flip & of both will remain at  $0, 0$ .  
Invalid.

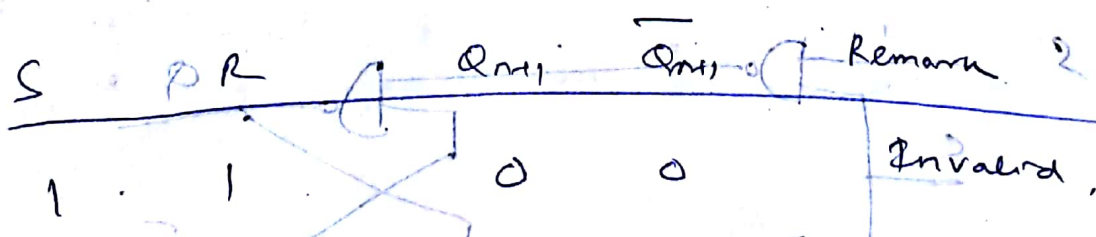Because  $\bar{Q}$  should be complemented of  $Q$ , but both remain at  $0, 0$ .




Another explanation when both ops are  $0, 0$ , and we give  $R=0, S=0$

then it should retain the value  $0, 0$ , as  $R=0, S=0$  is the requirement for a latch behaving as memory device. But the op is  $0, 1$ , which is not expected, so  $S=1, R=1$  is never used. It is a useless or invalid flip.




SR Latch with NAND gates: -

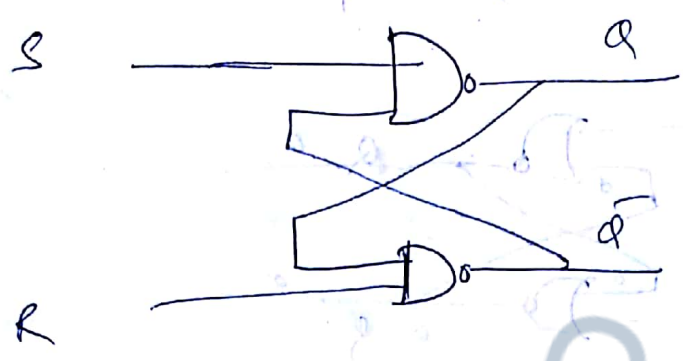

S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remark
0	0	1	1	Invalid
0	1	1	0	<del>Reset</del>
1	0	0	1	Set
1	1	$Q_n$	$\bar{Q}_n$	No change

S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remark
0	0	1	1	Invalid / unused
0	1	1	0	Set
1	0	0	1	Reset
1	1	$Q_n$	$\bar{Q}_n$	No change → Used memory element.


SR Latch with Control CP

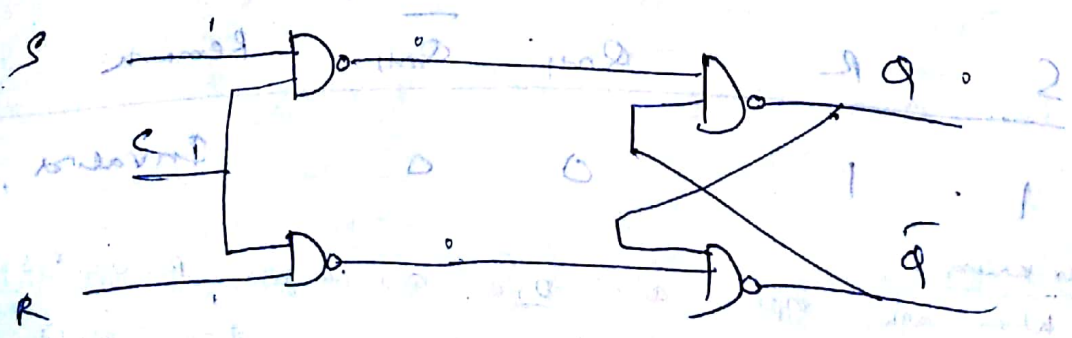

C	S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remark
0	X	X	$Q_n$	$\bar{Q}_n$	No change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	1	1	Invalid

If  $C=0$ , what ever be the value of S & R ( $X, X$ ),  $X \rightarrow$  Don't care, the O/P remains unchanged.

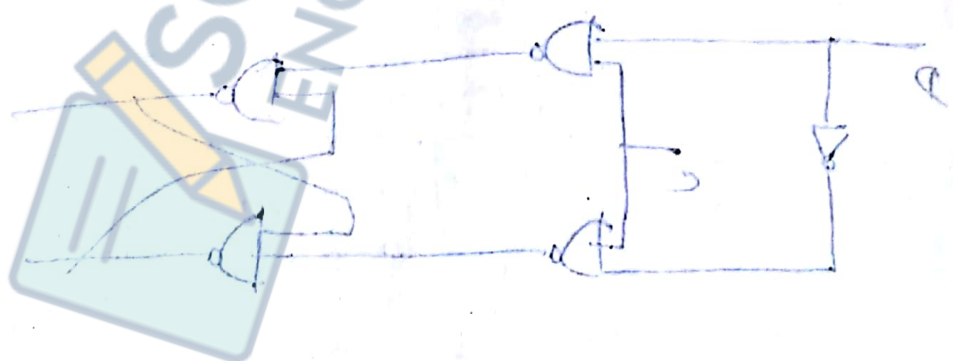( $C=0$ , O/P of 2 NAND gates is 1, 2)   
 this is ~~not~~ ~~is~~ ~~not~~ for the   
 second, 2 NAND gates)   
 total



Remark	$Q_{n+1}$	$\bar{Q}_{n+1}$	Q	C
No change	$Q_n$	$\bar{Q}_n$	X	0
Reset	0	1	0	1
Set	1	0	1	1
Invalid	1	1	1	1

Control is not needed if the output is 1 or 0



## D Latch:-


→ One way to eliminate the undesirable condition of indeterminate / invalid comp<sup>n</sup> in SR Latch is to ensure that  $S \neq R$  should never be equal.

→ This is done by D latch.

→ It has 2 I/Ps: D (Data)  
C (Control)

2 O/P →  $Q$  &  $\bar{Q}$

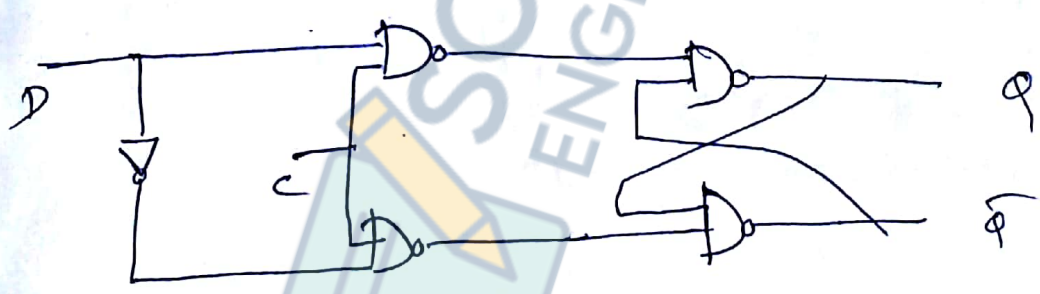
→ We have connected a not gate in between SR Latch to convert into D latch.




C	D	$Q_{n+1}$	$\bar{Q}_{n+1}$	Remark
0	X	$Q_n$	$\bar{Q}_n$	No change
1	0	0	1	'0' is latched
1	1	1	0	'1' is latched.

If control is not enabled, it will remain as it is.

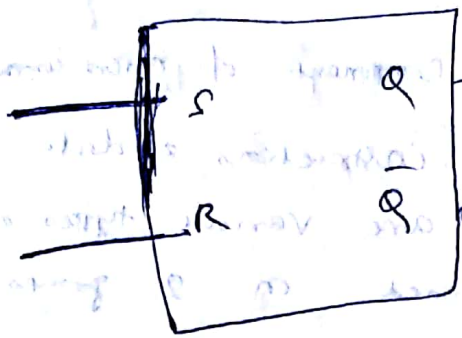If control is 1,  $\begin{cases} D = 0, & Q = 0 \\ D = 1, & Q = 1 \end{cases}$




(SR Latch)

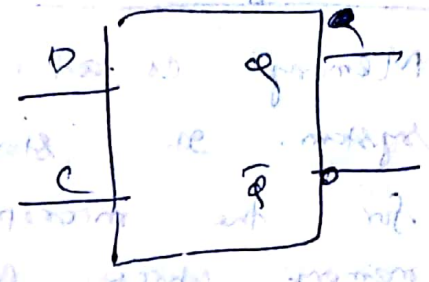

(D Latch)

Ques: - SR F/R

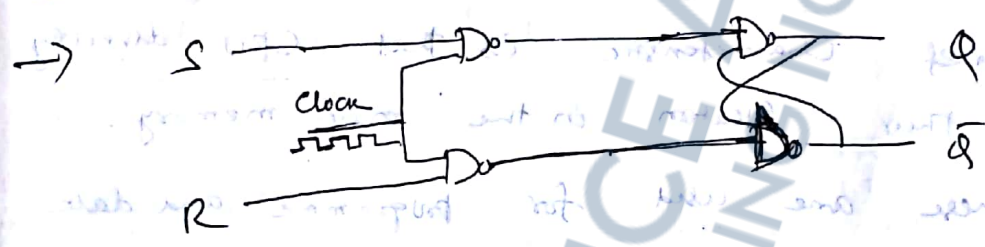

Clock	S	R	$Q_n$	$\bar{Q}_n$	Remark
0	X	X	$Q_n$	$\bar{Q}_n$	No change
↑	0	0	$Q_n$	$\bar{Q}_n$	No change
↑	0	1	0	1	Reset
↑	1	0	1	0	Set
↑	1	1	1	1	Invalid

2-mark - 2013  
SP1

Difference between Latch & F/R


- The difference between latch and F/R is that latch does not have a clock signal, whereas F/R always have a clock signal.
- Latch is level triggered whereas F/R is edge triggered.



## Memory Classification:-

Memory is an essential component of micro computer system. It stores binary instructions & data for the microprocessor. There are various types of memory which can be classified in 2 groups such as

1. Primary Memory.
2. Secondary Memory.

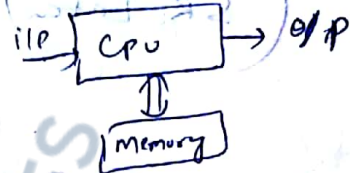

(writing a c-program)

### Primary Memory:-

The chief characteristic is that CPU directly accesses their location in the main memory.

These are used for programme and data storage, during computer operations. Total capacity of a primary memory varies from a few KB for small computing system to several MB/GB for large systems.

→ If a memory has  $n$  address lines then the memory capacity is  $2^n$  bytes.

→ Basically the primary memory are divided into 2 groups

1. Read/Write memory (RAM)
2. Read only memory (ROM)

### Read/Write Memory (RAM)

The microprocessor can write into & read from this memory. It is popularly known as RAM (Random Access Memory).

It is used primarily for information that is likely to be altered, such as writing programs or receiving data.

→ This memory is volatile, meaning that when power is turned off, all the contents are destroyed.

→ Two types of R/W memories - Static and dynamic (SRAM / DRAM)

### SRAM (Static RAM)

→ This memory is made up of flip-flop and it stores the bit as a voltage.

→ Each memory cell requires six transistors.

→ Therefore the memory chip has low density ~~and~~ but high speed.

→ This memory is more expensive and consumes more power than dynamic memory.

→ In high speed processor, SRAM known (as cache memory), ~~is~~ included on the processor chip.

→ In addition, high speed cache memory is also included external to the processor to improve the performance of a system.

### DRAM (Dynamic RAM)

→ This memory is made up of MOS transistor and it stores the bit as a charge.

→ The advantages of dynamic memory are that it has high density and low power consumption.



And is cheaper than static memory.

→ The disadvantage is that the charge (bit information) leaks, therefore stored information needs to be read and written again every few milliseconds.

→ This is called refreshing the memory, and it requires extra circuitry, adding to the cost of the system.

V. diff

Static RAM

Dynamic RAM

- 1) It uses registers & latches / Flip flops for data storage
- 2) The stored information are retained in it as long as power supply is on.
- 3) It does not require refreshing ckt.
- 4) It is used for small amount of data storage
- 5) It consumes more power and are more expensive
- 6) Faster

- 1) It uses capacitors for data storage.
- 2) It loses its content in a very short time even though the power supply is on.
- 3) It requires refreshing ckt
- 4) It is used for large amount of data storage
- 5) It consumes less power & less expensive
- 6) Slower

7) It stores the bit as a voltage

7) It stores the bit as a charge

Both SRAM & DRAM are volatile.

## ROM (Read-only - Memory)

- The ROM is a non-volatile memory.
- It retains information even if the power is turned off.

→ The ROM, like the RAM is random-access memory, but the term RAM traditionally means a random-access read/write memory.

→ This memory is used for programs and data that need not to be altered.

→ As the name suggests, the information can be read only, which means once a bit pattern is stored, it is permanent.

ROM are classified into 5 types, such as

- (a) Masked ROM
- (b) PROM
- (c) EPROM
- (d) EEPROM
- (e) Flash Memory

a) Masked ROM :-

In this ROM, a bit pattern is permanently recorded by the masking and metallization process.

Memory manufacturers are generally required to do this process. It is expensive and specialized process. But economical for large production quantities.



111 (1) 117  
PROM (Programmable Read only Memory) :-

→ This memory has nichrome and poly silicon wires arranged on a matrix

→ These wires can be functionally viewed as diodes or fuses. This memory can be programmed by the user with a special PROM programmer that selectively burns the fuses according to the bit patterns to be stored. This process is known as burning the PROM and the information is stored permanently.

< like Burning a Read only CD >

EPROM (Erasable Programmable Read only memory)

The information can be erased by exposing the chip to ultra violet light and the chip can be reprogrammed. Because the chip can be used many times, this memory is ideally suited for product development, experimental projects and college laboratories.

EE - PROM (Electrically Erasable PROM)

This memory is functionally similar to EPROM, ~~but~~ except that information can be altered by using electrical signals at of the register level rather than erasing all the information. This has an advantage of on field and remote control application.

## Flash Memory:

This is a variation of EE-PROM that is becoming popular. The major difference between the flash memory and EE PROM is the erase procedure. The EE-PROM can be erased at a register level, but the flash memory must be erased either entirely or at the sector (block) level. Faster than EE-PROM.

## Secondary Memory:

If it is necessary to store more data than the maximum capacity of primary memory then secondary memory is employed.

→ The CPU can't directly access a secondary memory device. The secondary memories can be accessed only through I/O ports or in a serial format using proper software and hardware.

→ Magnetic tapes, floppy disks, CD-ROM, Hard-disk, Pen drive etc are common examples of secondary memory.