

Unit-II

Electro-dynamics

Formulae

1. $I = \frac{Q}{t} \Rightarrow 1 \text{ Amp} = \frac{1 \text{ Coulomb}}{1 \text{ sec}}$

2. Ohm's law is $V = RI$

Where R = Resistance of the conductor through which a current of I amperes is flowing

V = Potential difference between the two ends of the conductor

3. Resistances when connected in series the equivalent resistance is given by

$$R_s = R_1 + R_2 + R_3 + \dots$$

4. Resistances when connected in parallel the equivalent resistance (R_p) is given by

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

5. Relation between e.m.f and p.d (G)

$$E = V + I\gamma$$

where γ = Internal resistance of

a battery or cell

$$E = \text{e.m.f}$$

$V = \text{P.D}$ across the external resistance.

$$= RI$$

⑥ Resistance is related to length of the conductor (l) and area of cross section (A) by the formula

$$R_m = \rho \frac{l}{A}$$

where ρ = specific resistance which is a constant characteristic of the material of the conductor and temperature.

Problems

- Calculate the number of electrons passing through a lamp in a day for which a current of 1.6 Amp is passing. (Ans $\rightarrow 1.8.64 \times 10^{23}$)

- 3 resistances 1Ω , 2Ω , 3Ω are connected to form a triangle ABC. Find the equivalent resistance between A and B, B and C and C and A.

$$(\text{Ans: } \frac{5}{6}, \frac{4}{3}, \frac{3}{2})$$

3. A battery is connected to a rheostat gives some current. When a lamp of resistance $150\ \Omega$ is inserted in series, the current is reduced

- (a) $\frac{1}{3}$ of the former value. What is the resistance of the rheostat

$$(\text{Ans: } 75\ \Omega)$$

4. A uniform wire 2 meter long having resistance $0.8\ \Omega$ is connected in series with

a battery having a terminal voltage

6 volts, and a rheostat that has a resistance of 1 ohm. What is the reading

of a voltmeter placed across

60 cm of the wire.

$$(\text{Ans: } 1.65\text{ v})$$

5. A wire of resistance $40\ \Omega$ is

melted and another wire of radius

half of the radius of the previous wire

is prepared out of it. Find

the new resistance.

$$(\text{Ans: } 640\ \Omega)$$

6. 1 kg of Cu is drawn into a wire.

(a) 1 mm in diameter

(b) 3 mm in diameter.

Compare their resistances at the same temperature.

(Ans: 81 : 1)

7. Two Cu wires whose lengths are

in the ratio 1 : 2 are of the same resistance. Compare the diameter of the wires. (Ans: 1 : $\sqrt{2}$)

8. Two coils when connected in series

have an equivalent resistance of $18\ \Omega$.

And when connected in parallel the equivalent resistance becomes $4\ \Omega$. Find the resistances. (Ans: $6\ \Omega, 12\ \Omega$)

9. Three resistances of which 2 are equal, when joined in series have

an equivalent resistance of $250\ \Omega$.

When they are joined in II, the equivalent resistance becomes $25\ \Omega$. Find the resistances. (Ans: $100\ \Omega, 100\ \Omega, 50\ \Omega$) or $(625, 625, 125)$

10. The terminal voltage of a battery is 9V when supplying a current of 4 Amp and 8.5 Volt when supplying 6 Amp. Find the internal resistance and e.m.f of the battery

$$(\text{Ans: } 0.25 \Omega, 10V)$$

Answers

10. Relation between E.m.f and P-V

$$E_p = V_i + I_1 r$$

Terminal voltage of battery is $= 9V$ connected to load, current supplied = 4 Amp

$$\Rightarrow E = 9 + 4r \quad \text{(i)}$$

Terminal voltage connected to battery = 8.5 V, current supplied = 6 Amp

$$E = 8.5 + 6r \quad \text{(ii)}$$

Subtracting eqn (ii) from eqn (i)

$$0 = 8.5 - 2r$$

$$\Rightarrow 2r = 8.5$$

$$\Rightarrow r = 4.25 \Omega$$

Internal resistance $= 0.25 \Omega$

Putting this value in eqn (1)

$$E = 9 + 4 \cdot (25)$$

$$\Rightarrow E = 9 + 1$$

$$\therefore E = 10 \text{ volt}$$

Q. Let the three resistances be R, R, R_1

When connected in series

$$R_s = R + R + R_1 = 2R + R_1$$

$$\Rightarrow 250 = 2R + R_1 \quad \text{--- (i)}$$

$$\Rightarrow R_1 = 250 - 2R$$

When they are connected in II

$$\frac{1}{R_s} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R_1}$$

$$\Rightarrow \frac{1}{25} = \frac{R_1 + R_1 + R}{RR_1}$$

~~$$\Rightarrow RR_1 = 2R_1 + R$$~~

~~$$\Rightarrow 25R(250 - 2R) = 2(250 - 2R) + R$$~~

~~$$\Rightarrow 625R^2 - 50R^2 = 500 - 4R + R$$~~

$$\Rightarrow 50R^2 - 6250R + 12500 = 0$$

~~$$\Rightarrow 50R^2 - (625)R + 12500 = 0$$~~

$$\Rightarrow RR_1 = 250R_1 \text{ or } 125R$$

$$\Rightarrow R(250 - 2R) = 50(250 - 2R) - 125R$$

$$\Rightarrow 250R - 2R^2 = 12500 - 100R + 25R$$

$$\Rightarrow 2R^2 - 75R + 12500 = 0$$

$$\Rightarrow 2R^2 - 325R + 12500 = 0$$

$$\Rightarrow R = \frac{325 \pm \sqrt{(325)^2 - 4 \cdot (2) \cdot (12500)}}{2 \cdot 2}$$

$$= \frac{325 \pm \sqrt{105625 - 100000}}{4}$$

$$= \frac{325 \pm \sqrt{5625}}{4}$$

$$= \frac{325 \pm 75}{4}$$

$$= \frac{325 + 75}{4} \text{ or } \frac{325 - 75}{4}$$

$$R = \frac{400}{4} \text{ or } \frac{-250}{4}$$

$$= 100 \Omega \text{ or } 62.5 \Omega$$

when $R = 100 \Omega$

$$R_1 = 250 - 2 \cdot (100) = 50 \Omega$$

∴ Three resistances are $(600\ \Omega, 1W, 50\ \Omega)$

$$\text{Qr } R = 62.5\ \Omega$$

$$R_1 = 250 - 25(62.5) = 198\ \Omega$$

$$= 250 - 125 = 125\ \Omega$$

$$= 125\ \Omega$$

∴ Three resistances are $(62.5, 62.5, 125\ \Omega)$

8. When resistance coils are connected in series $R_s = 18\ \Omega$

$$\text{Connected in series } R_s = 18\ \Omega$$

$$\Rightarrow R_1 + R_2 = 18\ \Omega$$

$$\Rightarrow R_1 = 18 - R_2$$

When connected in \parallel

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_p} \quad \frac{1}{R_2}$$

$$\Rightarrow \frac{R_1 + R_2}{R_1 R_2} = \frac{1}{R_p}$$

$$\Rightarrow \frac{R_1 R_2}{R_1 + R_2} = 4$$

$$\Rightarrow \frac{(18 - R_2) R_2}{(18 - R_2) + R_2} = 4$$

$$\Rightarrow 18R_2 - R_2^2 = 72$$

$$\Rightarrow R_2^2 - 18R_2 + 72 = 0$$

$$\Rightarrow R_2 = \frac{18 \pm \sqrt{324 - 4 \cdot (1) \cdot (7^2)}}{2 \cdot (1)}$$

$$= \frac{18 \pm \sqrt{324 - 288}}{2}$$

$$= \frac{18 \pm \sqrt{36}}{2}$$

$$= \frac{18 \pm 6}{2}$$

$$\therefore R_2 = \frac{24}{2} \text{ or } \frac{12}{2}$$

$$= 12 \text{ or } 6$$

~~Q~~ or $R_2 = 12 \Omega$, $R_1 = 18 - 12 = 6 \Omega$

~~Q~~ $R_2 = 6 \Omega$, $R_1 = 18 - 6 = 12 \Omega$.

R_1 and R_2 are 6 and 12
or 12 and 6

7.

$$\frac{l_1}{l_2} \Rightarrow \frac{1}{2}$$

They have same resistance $\epsilon = R$.

$$R = \rho \frac{A_1}{A_1}$$

$$R = \rho \frac{l_2}{l_2}$$

Dividing $\Rightarrow 1 = \frac{A_1 \cdot A_2}{A_1 \cdot l_2} = \frac{l_1}{l_2} \cdot \frac{A_1}{A_2} = \frac{1}{2} \cdot \frac{A_2}{A_1}$

$$\Rightarrow A_2 = 2 A_1$$

$$\Rightarrow \frac{\sigma_2^2}{\sigma_1^2} = 2 \cdot (\frac{\sigma_1^2}{\sigma_2^2})$$

$$\Rightarrow \frac{\sigma_2^2}{\sigma_1^2} = 2$$

$$\Rightarrow \frac{\sigma_1^2}{\sigma_2^2} = \frac{1}{2}$$

$$\Rightarrow \frac{\sigma_1}{\sigma_2} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \frac{\frac{d_1}{\sqrt{2}}}{\frac{d_2}{\sqrt{2}}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow d_1 : d_2 = 1 : \sqrt{2}$$

(Ans)

6. We know that

$$R_1 = f \frac{l_1}{A_1} = f \frac{d_1}{\frac{4}{3}\pi r^2}$$

$$R_2 = f \frac{l_2}{A_2}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{l_1}{A_1} \times \frac{A_2}{l_2} = \frac{l_1}{l_2} \times \frac{\frac{4}{3}\pi r_1^2}{\frac{4}{3}\pi r_2^2}$$

$$= \frac{l_1}{l_2} \times \frac{d_1^2}{d_2^2} = \frac{l_1}{l_2} \times \frac{1}{9}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{l_1}{9A_2}$$

But Volume are same

$$\pi r_1^2 l_1 = \pi r_2^2 l_2$$

$$\Rightarrow \frac{l_1}{l_2} = \frac{r_2^2}{r_1^2} = \frac{d_2^2}{d_1^2} = \frac{9}{1}$$


$$\Rightarrow \frac{l_1}{l_2} = 9$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{a_1^2} = \frac{1}{9} \times 9 = \frac{81}{1}$$

∴ resistances are in the ratio 81:1

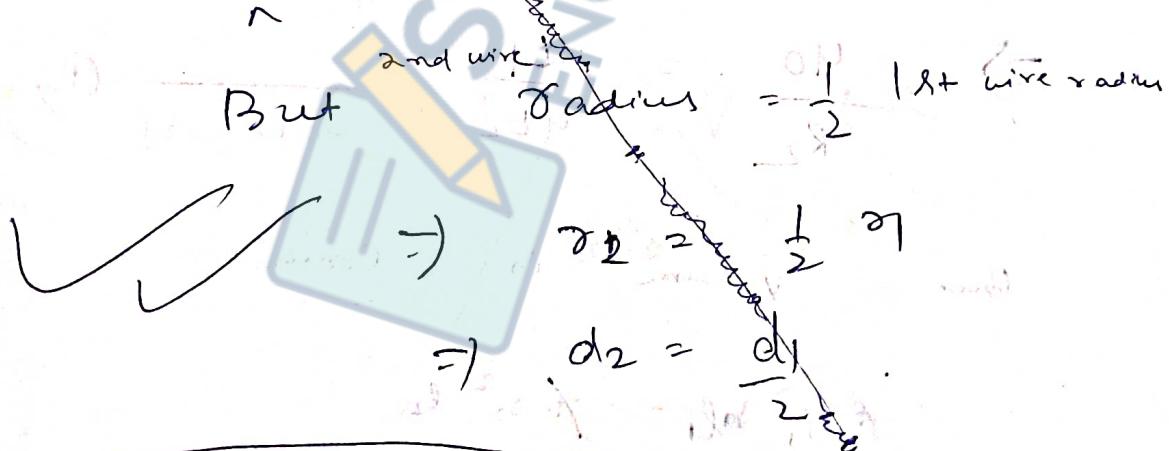5. A wire has resistance $R_1 = 4\Omega$.

If it is melted to another wire having resistance R_2 .



$$\text{But } R_1 = \frac{L}{A_1} = \frac{L}{\pi d_1^2} = \frac{L}{\pi d_1^2} \cdot \frac{4}{4} = \frac{L}{\pi d_1^2}$$

$$R_2 = \frac{L}{A_2} = \frac{L}{\pi d_2^2} = \frac{L}{\pi d_2^2} \cdot \frac{4}{4} = \frac{L}{\pi d_2^2}$$

$$\frac{R_1}{R_2} = \frac{\frac{L}{\pi d_1^2}}{\frac{L}{\pi d_2^2}} = \frac{(d_1)^2}{(d_2)^2} = \frac{1}{9} \cdot \frac{1}{9} = \frac{1}{81}$$

$$\frac{R_1}{R_2} = \frac{1}{16}$$

$$\Rightarrow \frac{q_0}{R_2} = \frac{1}{16}$$

$$\Rightarrow R_2 = 16 q_0$$

5.

$$R_1 = \frac{\pi L}{A_1}, R_2 = \frac{\pi L_2}{A_2}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{\frac{\pi L_1}{A_1}}{\frac{\pi L_2}{A_2}} = \frac{L_1}{L_2} \cdot \frac{\pi \left(\frac{d_2}{2}\right)^2}{\pi \left(\frac{d_1}{2}\right)^2}$$

$$= \frac{L_1}{L_2} \times \frac{d_2^2}{d_1^2} = \frac{L_1}{L_2} \times \frac{\left(\frac{d_1}{2}\right)^2}{\left(\frac{d_1}{2}\right)^2}$$

$$\Rightarrow \frac{q_0}{R_2} = \frac{L_1}{4L_2} \quad \text{--- (1)}$$

But Volume $\propto d^3$ Constant

$$\pi r_1^2 l_1 = \pi r_2^2 l_2$$

$$\Rightarrow \frac{r_1^2}{r_2^2} = \frac{l_2}{l_1}$$

$$\Rightarrow \frac{d_1^2}{d_2^2} = \frac{l_2}{4}$$

$$\Rightarrow \frac{dI^2}{dx} = -\frac{l_2}{l_1}$$

$$(\frac{dI}{dx})^2$$

$$\Rightarrow \frac{d^2x}{dx^2} = \frac{l_2}{l_1}$$

$$\Rightarrow \frac{l_1}{l_2} = 4 \cdot V \Rightarrow \frac{l_1}{l_2} = l_1$$

$$\Rightarrow \frac{l_1}{l_2} = \frac{1}{4}$$

\therefore From eqn (1) $\frac{V_0}{R_2} = \frac{1}{4} \times \frac{64}{7} = \frac{1}{16}$

$$\Rightarrow R_2 = 64 \Omega \text{ Ans}$$

(3) A battery is connected to a rheostat.

Lamp 1 has resistance 150Ω .

We know $V = I R$

$$\Rightarrow V_1 = I_1 R_1$$

In second can $V_2 = I_2 R_2$

$$\Rightarrow V_2 = \frac{I_1}{3} \cdot 150$$

Division $= \frac{I_1 R_1 \times 3}{I_1 \times 150}$

3. A battery connected to a resistor.

∴ There $V = IR$ — (1)

When it is connected 15Ω , then I

becomes $\frac{I}{3}$

$$\therefore V = \frac{I}{3}(R + 15\Omega)$$

$$I = \frac{VR \times 3}{2(R + 15\Omega)}$$

$$\Rightarrow R + 15\Omega = 3R$$

$$\Rightarrow 2R = 15\Omega$$

$$\Rightarrow R = 7.5\Omega$$

2. $R = ?$


Equivalent resistance

A cross

AB

BC

CA

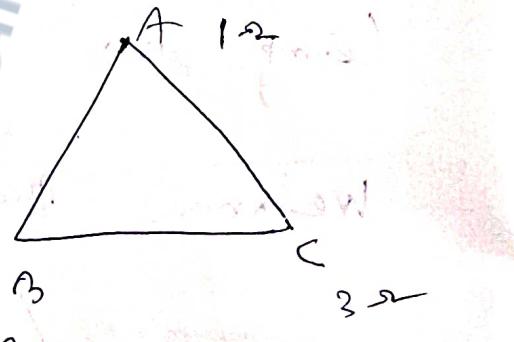

In this case A and B are connected

in series and C is in " "

∴ The equivalent resistance

$$= R_2 = 3\Omega$$

C has resistance $= 3\Omega$

$$\frac{1}{R_p} = \frac{1}{3} + \frac{1}{3} = \frac{2}{3}$$

$$\Rightarrow R_p = \frac{1}{\frac{2}{3}} = \frac{3}{2} \Omega$$

$$\Rightarrow R_p = \frac{3}{2} \Omega$$

\therefore Across A, B resistance $\frac{3}{2} \Omega$

When A, C are connected in series

$$\text{B then resistance} = (1+3) \Omega = 4 \Omega$$

$$B \text{ has resistance} = 2 \Omega$$

They are connected in parallel connected

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{2} = \frac{1+2}{4} = \frac{3}{4}$$

$$\Rightarrow R_p = \frac{4}{3} \Omega$$

\therefore A and C has resistance $\frac{4}{3} \Omega$

B and C are connected in series

$$R_s = 2 + 3 = 5 \Omega$$

But B has resistance 1Ω .
Connected in parallel.

R_s and A

$$\therefore \frac{1}{R_p} = \frac{1}{5} + \frac{1}{1} = \frac{1+5}{5} = \frac{6}{5}$$

$$\therefore R_p = \frac{5}{6} \Omega$$

\therefore Across B and C resistance $\frac{5}{6} \Omega$

$$I = 1.6 \text{ Amp}$$

t_2 Time = 24 hours $\Rightarrow (24 + 3600) \text{ sec}$

$$Q = I \cdot t = 1.6 \times 24 \times 3600$$

$$= 138240 \text{ Coulomb}$$

each electron has charge $= 1.6 \times 10^{-19}$

each electron has charge $= 1.6 \times 10^{-19}$

so $1.6 \times 10^{-19} \text{ C}$ the electron remain ≈ 1

$$\frac{1.6 \times 10^{-19}}{1.6 \times 10^{-19}} = 1 \text{ electron}$$

$$(138240) \div 1 = 138240$$


$$\frac{138240}{1.6 \times 10^{-19}}$$

$$= 864 \times 10^{19}$$

$$= 8.64 \times 10^{23} \text{ electrons}$$

∴ Number of electrons $= 8.6 \times 10^{23}$ electrons

4.

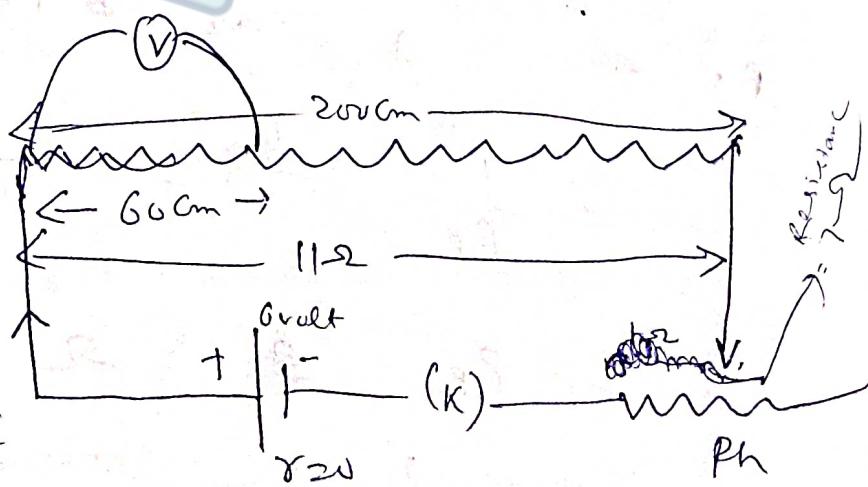

The resistors or resistances
11Ω and 12Ω are connected in series.

$$\therefore R_s = 11 + 12 = 23 \Omega$$

When connected in battery.

$$V = IR$$

$$6 \text{ volt} = 23I \cdot 12 \Omega$$

$$\therefore I = \frac{1}{2} \text{ Amp}$$

Given 2 cm width
resistance = 11Ω

$$11 = \frac{11}{2} \Omega$$

$$11 = \frac{11}{2} \times \frac{6^3}{10}$$

$$= \frac{33}{10} \Omega$$

$$R = \frac{33}{10} \Omega$$

$$I = \frac{1}{2} \text{ Amp}$$

$$V = IR = \frac{1}{2} \times \frac{33}{10} = 1.65 \text{ Volt}$$

(Ans)

$$\frac{1}{2} \times 11 = V$$

$$R = \frac{V}{I} = \frac{5.5}{\frac{1}{2}} = 11 \Omega$$

10.

We know that

$$= \frac{105}{2200}$$

$$V = I R$$



A dry cell has emf 1.55 V.

And current passes through

22 Amp.

$$\text{Internal resistance } R = \frac{V}{I} = \frac{1.55}{22} = 0.0704 \text{ Ohm}$$


14.

$$Q = It$$

$$\Rightarrow 600 C = I \times (120 s)$$

$$\Rightarrow I = \frac{600}{120} = 5 \text{ Amp}$$

15.

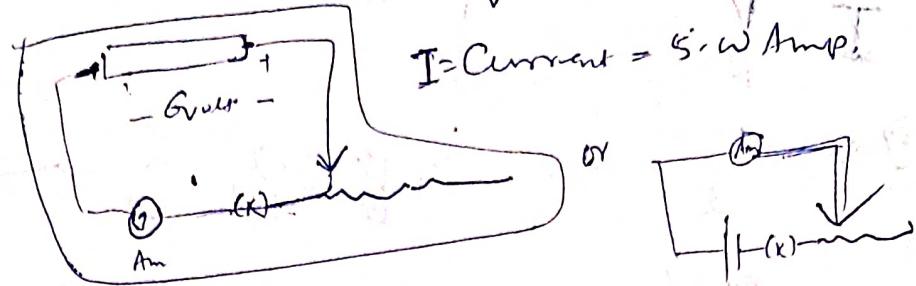

$$\rho = \frac{V}{I} = \frac{6}{5} = 1.2 \Omega$$

17. Given a theoretical $I = .45 \text{ A}$

Potential between the terminals = 6 V .

$$\rho = \frac{V}{I} = \frac{6}{.45} = \frac{6000}{45}$$

$$= 133.33 \Omega$$

Theoretical $I = .45 \text{ A}$

Wire has resistance $\rho = 1.75 \Omega/\text{ft}$

i.e. R for length of 1 ft / resistance = 1.75Ω

Toaster has $V = 115 \text{ V}$

$$I = \frac{V}{R} = \frac{115}{8.25}$$

$$\rho = \frac{V}{I} = \frac{115}{8.25} = 13.93 \Omega$$

for 1.75Ω , wire length $= 1 \text{ ft}$

$$11.1 \Omega \quad " \quad " = \frac{1}{1.75} \text{ ft}$$

$$13.93 \Omega \quad " \quad " = \frac{1}{1.75} \times 13.93 = 7.96 \text{ ft}$$


21 Ammeter reads $5 \text{ A} = I$

R_h has resistance R

AC Cording question

$$I = \frac{V}{R} \Rightarrow 5 = \frac{V}{R}$$

~~$$\frac{5}{R} = L_{(i)}$$~~

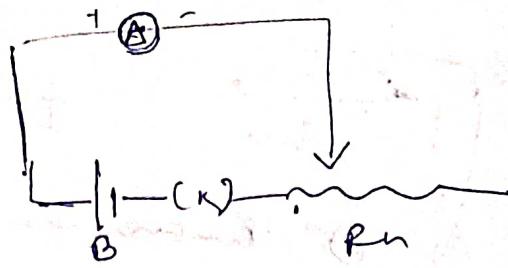

$$I = \frac{V}{R+R_L} \text{ (fig) } \Rightarrow V = \frac{V}{R+R_L} - (ii)$$

$$\begin{aligned} \Rightarrow VR = 5, \quad VR_1 = 2V &\geq 4 \\ \Rightarrow VR = 4 - 2V & \\ 5 = 4 - 2V & \\ \Rightarrow 2V = & \\ & \end{aligned} \quad \therefore V = 5R - (iii)$$

~~Equating~~

$$\begin{aligned} V &= VR + 8 \\ 5R &= VR + 8 \\ R &= 8 \Omega \end{aligned}$$

$$V = 5 - R = 5 - 8 = 40 \text{ volt}$$

\therefore Resistance or $R_L = 8 \Omega$.

Q3.

Fan motor
in Operated

at $I = 3.50 \text{ Amp}$

$$V = 115 \text{ V}$$

$$R = \frac{V}{I} = \frac{115}{3.50} = 32.8 \Omega$$

When it is connected in ~~series~~ ^{parallel},

$$V = 125 \text{ V},$$


Rating Current = 3.50Ω ,

$$R = \frac{V}{I} = \frac{125}{3.5} = 35.71 \Omega$$

Extra d resistor will be connected

$$\text{of resistance} = 35.712 - 32.852$$

$$= 2.86 \Omega$$

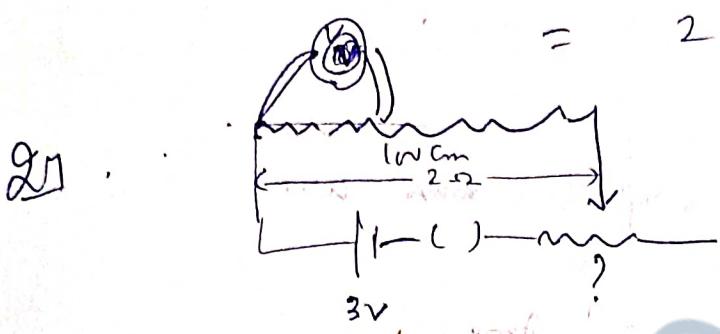

For the

$$R = \frac{V}{I}$$

Length 1mm

$$11 \quad 1000 \text{ mm}$$

Voltage = 1mV

$$11 = 1000 \text{ mV} \\ = 1 \text{ Volt}$$

$$(i) \text{ Current } I = \frac{V}{R + r} = \frac{1}{2.52 + r} \quad (\text{where } r \text{ is resistance of rheostat})$$

$$\Rightarrow I = \frac{1}{2.52}$$

of paper through

battery 3V -

$$R = \frac{V}{I}$$

$$V = \frac{3}{I} = 6 \Omega$$

Current in the

$$\text{curve } I = \frac{V}{R} = \frac{1 \text{ volt}}{2 \Omega} = \frac{1}{2} \text{ amp.}$$

Total Potential

$$\text{difference} = 3V + 1V = 4V$$

Total

$$\text{resistance} = R + r \\ = 2.52 + r$$

$$V = IR$$

$$VI = \frac{V}{R+r}$$

$$\Rightarrow 4 = \left(\frac{1}{2} + \frac{r}{2}\right) \cdot (2 + r)$$


$$\Rightarrow \frac{1}{2} + \frac{V_{\text{battery}}}{R+r} = \frac{V}{R+r} = \frac{4}{2+r}$$

$$\Rightarrow 4 = \left(\frac{1}{2} + \frac{3}{2}\right) (2+r)$$

$$= \left(\frac{7}{2}\right) (2+r)$$

$$\Rightarrow 8r = 28 - 7r^2 - 14 - 6r$$
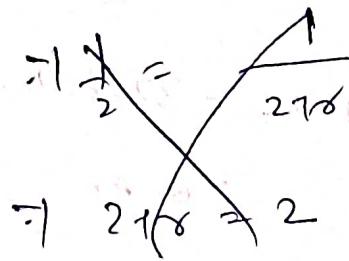
$$\Rightarrow \frac{1}{2} + \frac{3}{2+r} = \frac{4}{2+r}$$



Current through the wire

$$I = \frac{V}{R} = \frac{1}{\frac{1}{2}} = 2 \text{ Amp}$$

i.e. Actual Current flowing through battery is 2 Amp.

battery has $V = 3V$

~~$I = \frac{1}{2} \text{ volt}$~~

$$R = \frac{V}{I} = \frac{3V}{\frac{1}{2} V} = 6 \text{ volt}$$

This $R = R_h + \text{resistance of wire}$

$$\Rightarrow 6 = \gamma + 2$$

~~$\Rightarrow \gamma = 4 \Omega$~~

therefore resistance of $R_h = 4 \Omega$


$$25. Q = IT$$

$$\Rightarrow Q = 1.2 \times (24 \times 3600)$$

$$= 108 \times 10^3 = 10.8 \times 10^4$$

$$\text{Number of electrons} = \frac{10.8 \times 10^4}{1.6 \times 10^{-19}} = 6.2 \times 10^{23}$$

4.

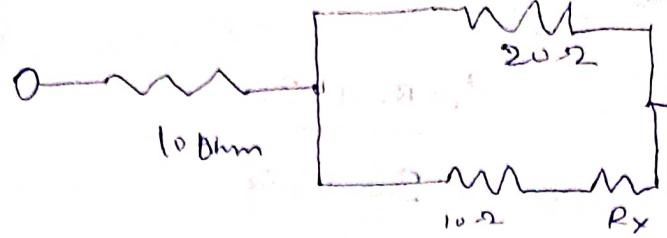

When 20Ω , 10Ω and R_x are connected in ~~series~~ parallel

$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{10} + \frac{1}{R_x}$$

$$\frac{1}{R_p} = \frac{R_x + 2R_x + 20}{20R_x}$$

$$\Rightarrow R_p = \frac{20R_x}{3R_x + 20}$$

But

 R_p and

10 ohm are in series

Connected in series

$$\text{then } R_s = \left(\frac{2R_x + 20R_x + 20}{20R_x + 3R_x} + 10 \right)$$

$$\left(\frac{20R_x + 200 + 3R_x}{20R_x + 3R_x} \right)$$

Net resistance =

But

According

to question

$$20R_x^2 - 203R_x - 20 = 0$$

$$\Rightarrow R_m = \frac{203 + \sqrt{(203)^2 - 4(80)(-20)}}{2 \cdot (20)}$$

= 203

$$R_x = \frac{50R_x + 2w}{20 + 3R_x}$$

$$\Rightarrow 20R_x + 3R_x^2 = 50R_x + 2w$$


$$\Rightarrow 3R_x^2 - 30R_x - 2w = 0$$

$$\Rightarrow R_x = 30 \pm \frac{\sqrt{900 - 4 \cdot (3) \cdot (-2w)}}{2 \cdot (3)}$$

$$= 30 \pm \sqrt{900 + 24w}$$

$$= 30 \pm \sqrt{33w}$$

Again

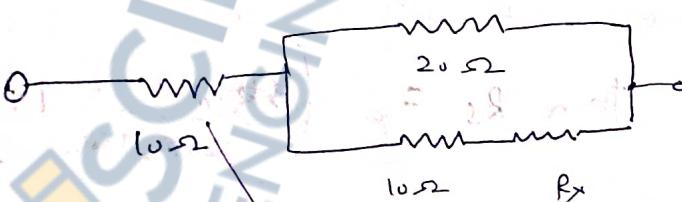

When $20, 10, R_x$

are connected in Parallel

$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{10} + \frac{1}{R_x} = \frac{R_x + 2R_x + 20}{20R_x} = \frac{3R_x + 20}{20R_x}$$

$$\Rightarrow R_p = \frac{20R_x}{20 + 3R_x}$$

Then R_p and 10Ω are connected in Series.

$$\therefore \text{Net resistance} = \frac{10 + 20R_x}{20 + 30R_x}$$

$$= \frac{200 + 300R_x + 20R_x}{20 + 30R_x}$$

$$= \frac{200 + 320R_x}{20 + 30R_x}$$

$$= \frac{200 + 50R_x}{20 + 30R_x}$$

According

to question

$$R_x = \frac{200 + 50R_x}{20 + 30R_x}$$

$$\Rightarrow 20R_x + 30R_x^2 = 200 + 50R_x$$

$$\Rightarrow 3R_x^2 - 30R_x + 200 = 0$$


$$\Rightarrow R_x = \frac{30 \pm \sqrt{900 - 4 \cdot (-3) \cdot (-200)}}{6}$$

$$= 30 \pm \sqrt{900 + 2400}$$

$$= 30 \pm \sqrt{3300}$$

$R_x = \text{Net resist}$
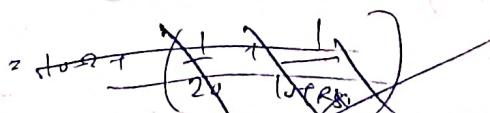
$$R_x = \frac{10 \Omega + R_p}{30 + 2R_x} = \frac{10\Omega + 2 \cdot (10 + R_p)}{30 + 2R_x}$$



$$R_p = \frac{1}{2} (10 + R_p)$$

Solve it

$$\frac{10 + R_p + 20}{20(10 + R_p)} = \frac{30 + R_p}{20(10 + R_p)}$$

$$R_p = 20 \Omega$$

$$R_p = \frac{2(10 + R_p)}{30 + R_p}$$

10/19/23

Q. Two lamps with ~~current~~

$$\text{have potential difference } = (5V + 5V) V \\ = 10V.$$

They are connected in series $\Rightarrow 120V_{\text{vol}}$

Potential difference remain = 2 volt

$$\text{Current} = 2 \text{ Amp.}$$

$$\text{Resistance of } R_h \text{ will be } \Rightarrow \frac{V}{I} = \frac{20}{2} = 10 \Omega$$

Q.

$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{30} + \frac{1}{70}$$

$$\Rightarrow \frac{1}{R_p} = \frac{614 + 3}{120} = \frac{13}{120}$$

$$\Rightarrow R_p = \frac{120}{13} = 9.23 \Omega$$

23. 5Ω and 7Ω are connect in ||.

$$\frac{1}{R_p} = \frac{1}{5} + \frac{1}{7} = \frac{7+5}{35} = \frac{12}{35}$$

$$\Rightarrow R_p = \frac{35}{12}$$

Y_{12} and $3\ \Omega$ are connected
in parallel.

$$R_{P_1} = \frac{4 \times 3}{4+3} = \frac{12}{7}\ \Omega$$

Then R_{P_1} and R_{P_2} are connected in series.

$\therefore R_S = \frac{\text{Total resistance}}{\text{Resistance}}$

$$= \frac{12}{7} + \frac{35}{12}$$

$$= \frac{144 + 245}{12 \times 7}$$

$$\therefore R_S = \frac{389}{84} \Omega = \frac{389}{84} \Omega$$

$Y_{12} 63\ \Omega$

Electrodynamics

It is a branch of physics that deals with Change in motion.

When charges flow through a conductor, electric current is produced.

Rate of flow of charge is called Current.

$$\therefore I = \frac{Q}{t}$$

In S.I system, Q is in coulomb, t in sec and I is in ampere.

$$\therefore 1 \text{ Ampere} = \frac{1 \text{ Coulomb}}{1 \text{ sec}}$$

Defn of Ampere

When 1 Coulomb of charge is made to flow through a conductor in 1 sec, a current of 1 Ampere is developed in it.

Ohm's law :-


Statement :-

Temp remaining constant, the potential difference between the two ends of a conductor is directly proportional to the current flowing through it.

If the two ends of the conductor be denoted by A and B, then

$$(V_A - V_B) \propto I$$

$$\text{or } V_A - V_B = RI$$

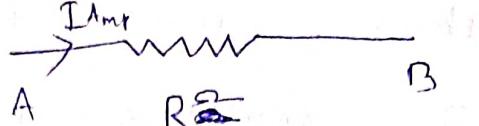

where R is a constant called Resistance which depends on temperature and nature of the material.

If we write $V_A - V_B = V$, then

Ohm's law will be given by

$$V = RI$$

In practical system of units, V is Ohms and I is expressed in volts, R in Ampere.

Def'n of volt

It is that amount of potential difference developed between the two ends of a conductor of resistance 1 ohm through which a current of 1 amp. is flowing.

Def'n of Ohm

It is that amount of resistance of a conductor through which the flow of a current of 1 amp. can develop a potential difference of 1 volt between the two ends.

Def'n of amp


It is that amount of current which when flows through a conductor of resistance 1 Ohm can develop a potential difference of 1 volt between its two ends.

Experimental Verification of Ohm's law in the laboratory


A closed series circuit is prepared with a D.C battery, a key (to start or stop current), a rheostat (by which resistance of the circuit can be changed), a resistance wire AB of fixed resistance R ohm, an ammeter (by which current can be measured).

A voltmeter is connected in parallel to the resistance wire AB as shown in the circuit diagram. By this instrument the potential difference between the two ends of the conductor can be found out.

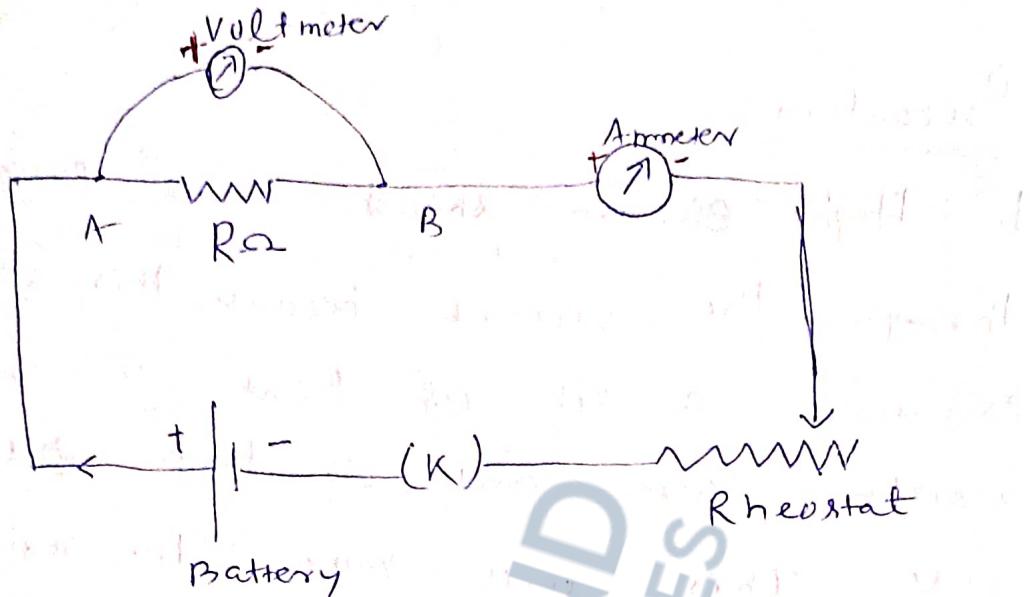By changing the resistance of the rheostat, different currents are produced in the circuit which are



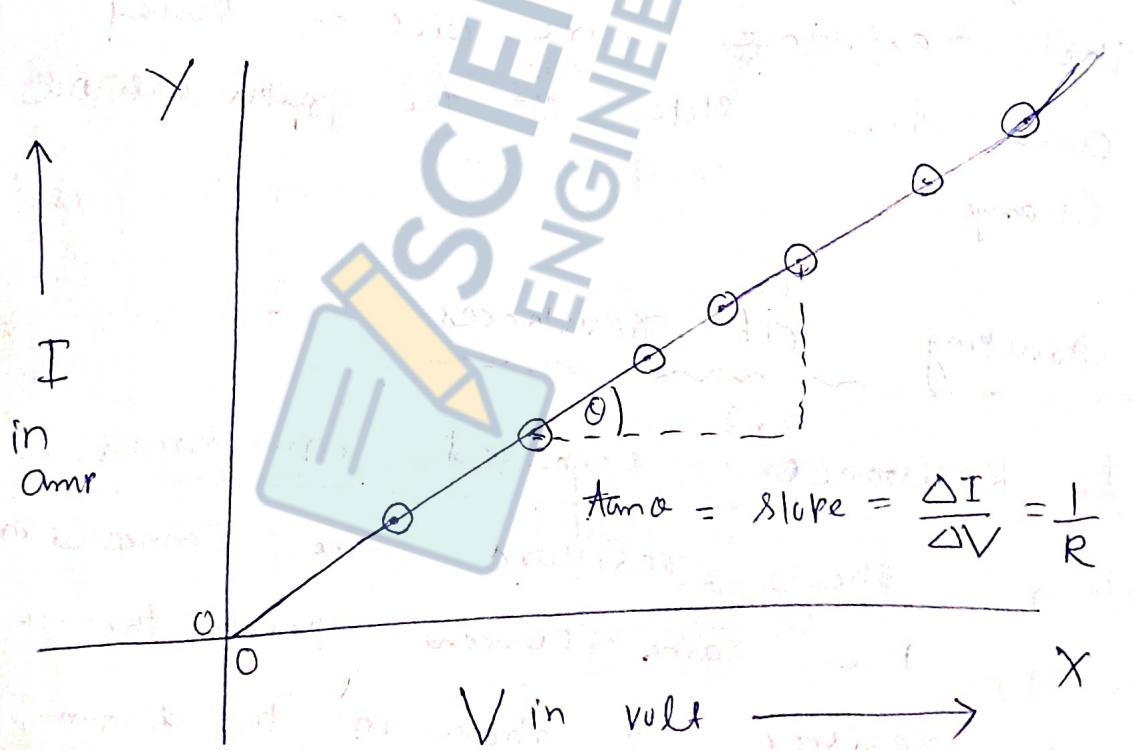directly measured by the Ammeter. Each time, the potential difference between A and B can also be measured - by the Voltmeter.



A graph can be plotted between P.d. and Current, which comes out to be a straight line passing through the origin.

This verifies Ohm's law. Because $V \propto I$

Precautions

1. High current should not be passed through the circuit because this will produce a lot of heat in the resistance wire and its temp will rise. This will make the resistance to increase, then we will not get a straight line graph.

2. In between two observations, the key should be taken out so that the resistance wire will be cooled and the slope of the graph will not change.


Grouping of resistances

1. Resistances connected in series:

When the resistors are connected in series, the same current passes through each resistor as shown in the diagram.

Therefore the p.d across each resistor will be different. Applying Ohm's law to each conductor, we have
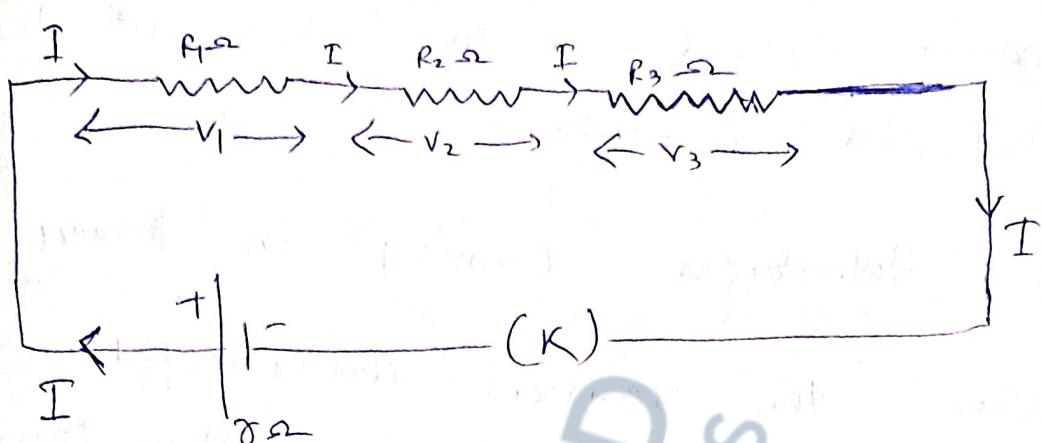
$$V_1 = R_1 I, \quad V_2 = R_2 I, \quad V_3 = R_3 I \quad \text{--- (1)}$$



\$V\$ = Terminal P.D

If the P.D. across the three resistors be '\$V\$' volt, then


$$V = V_1 + V_2 + V_3 \quad \text{--- (2)}$$

If the equivalent resistance be \$R_s\$,

then Ohm's law gives.

$$R_s I = V \quad \text{--- (3)}$$

Equivalent Circuit

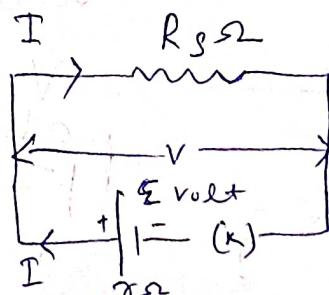

Using eqn (1) in eqn (3), we get

$$R_s I = R_1 I + R_2 I + R_3 I$$

$$\Rightarrow R_s = R_1 + R_2 + R_3$$


Thus the equivalent resistance when the resistors are connected in series is equal to the sum of the individual resistances.

Resistances Connected in parallel

When the resistors are connected in parallel, different currents flow through different resistor.

Applying Ohm's law to each resistor, we get
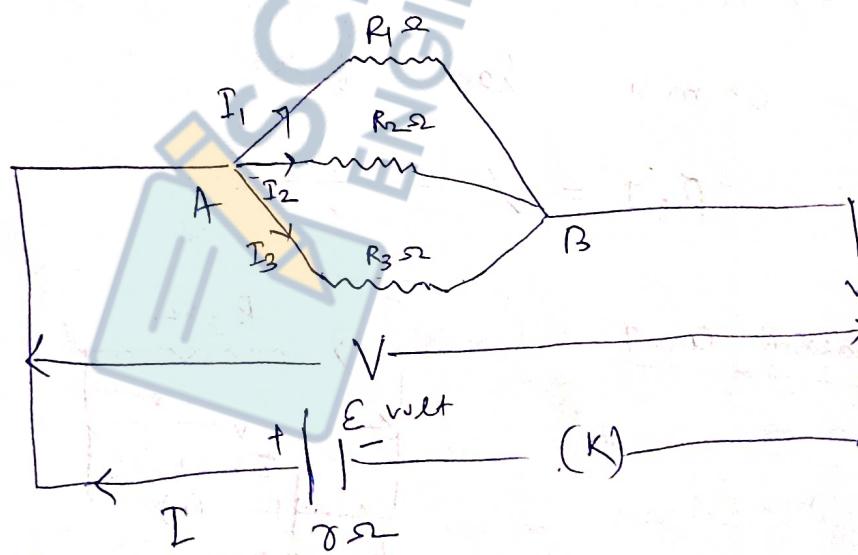
$$V = I_1 R_1, V = I_2 R_2, V = I_3 R_3 \dots$$




$$\therefore I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \dots$$

$$\text{But } I = I_1 + I_2 + I_3 \quad \text{--- (2)}$$

Given the equivalent resistance be R_p ,

then Ohm's law gives
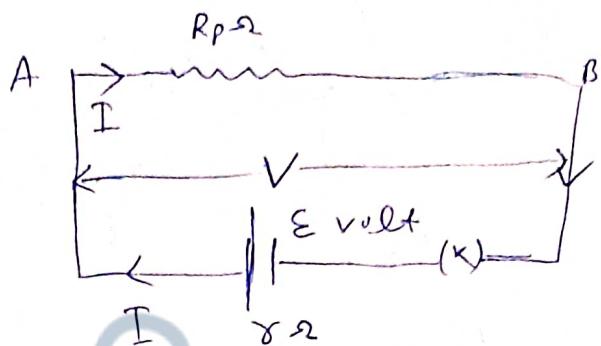
$$IR_p = V \quad (3)$$
$$\Rightarrow I = \frac{V}{R_p} \quad (4)$$



Using eqn (2) and (4) Equivalent circuit


In eqn (3), we get

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$
$$\Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

∴ Thus the reciprocal of the equivalent resistance when the resistors are connected in parallel is equal to the sum of the reciprocals of the individual resistances.



Problem : find the equivalent resistances

between A and B

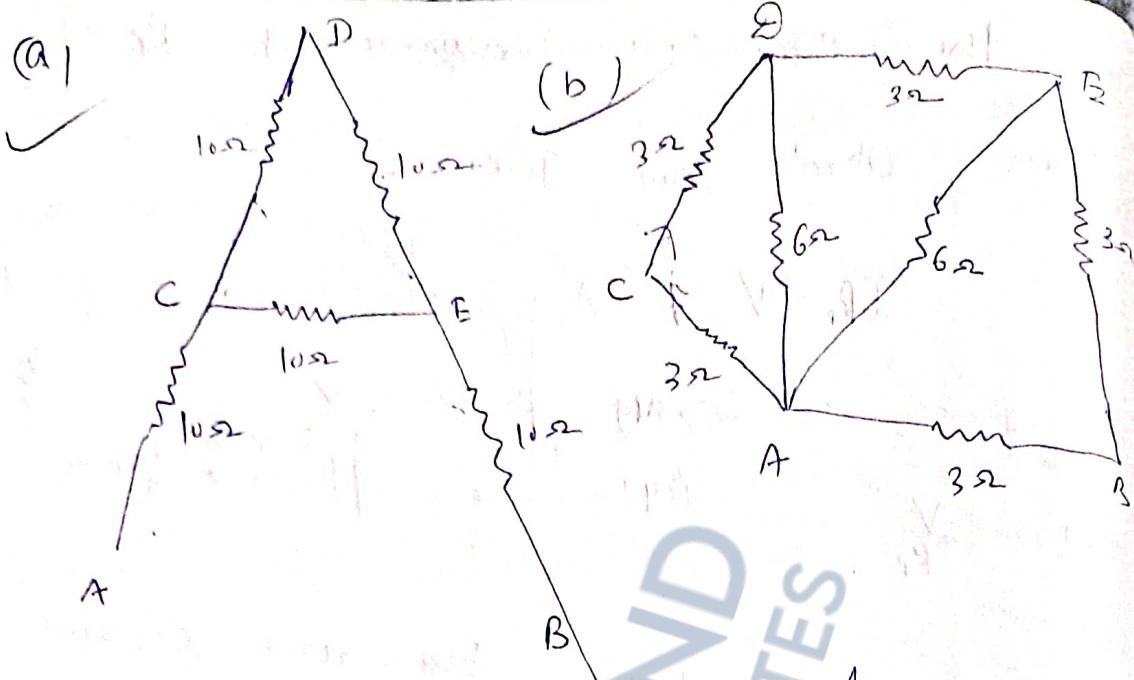


$$\text{Ans} \equiv \frac{80}{3} \text{ rad}$$


$$\text{Ans} \equiv 2 \text{ rad}$$

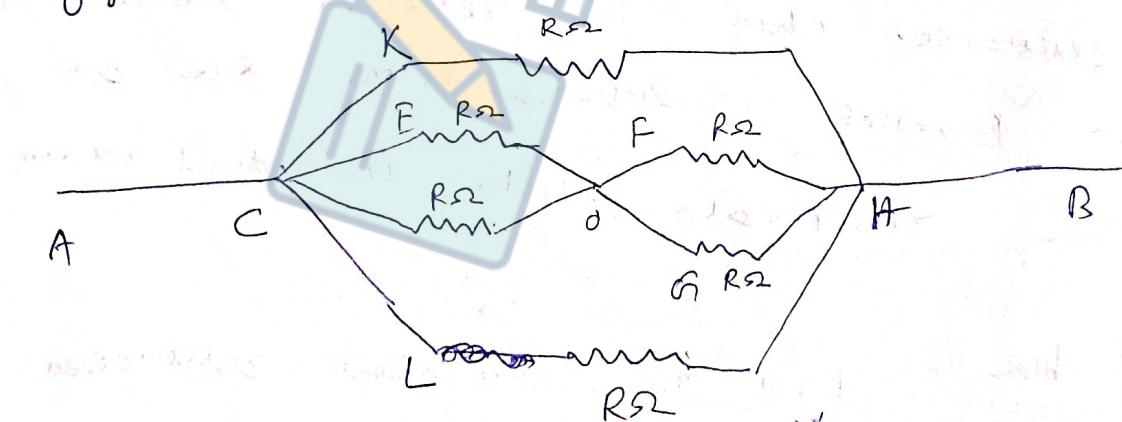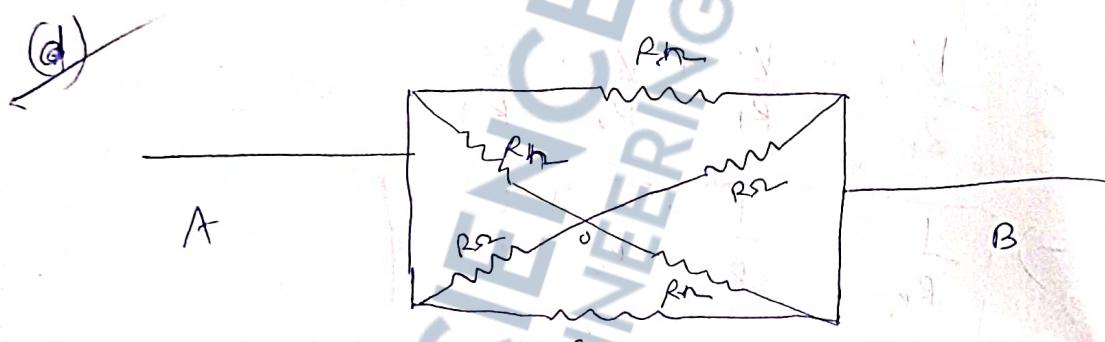


$$\text{Ans} \equiv \frac{R}{3}$$

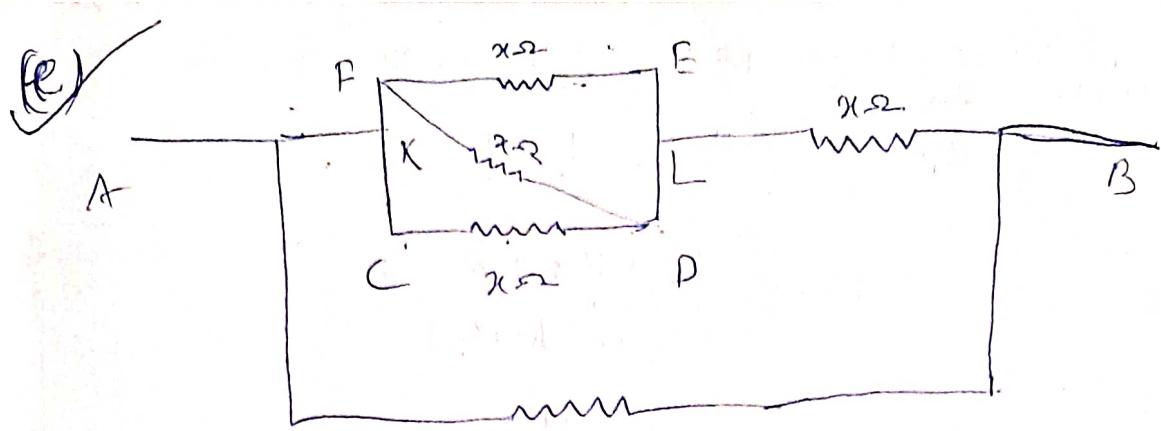

$$Ans = \frac{4k}{7}$$

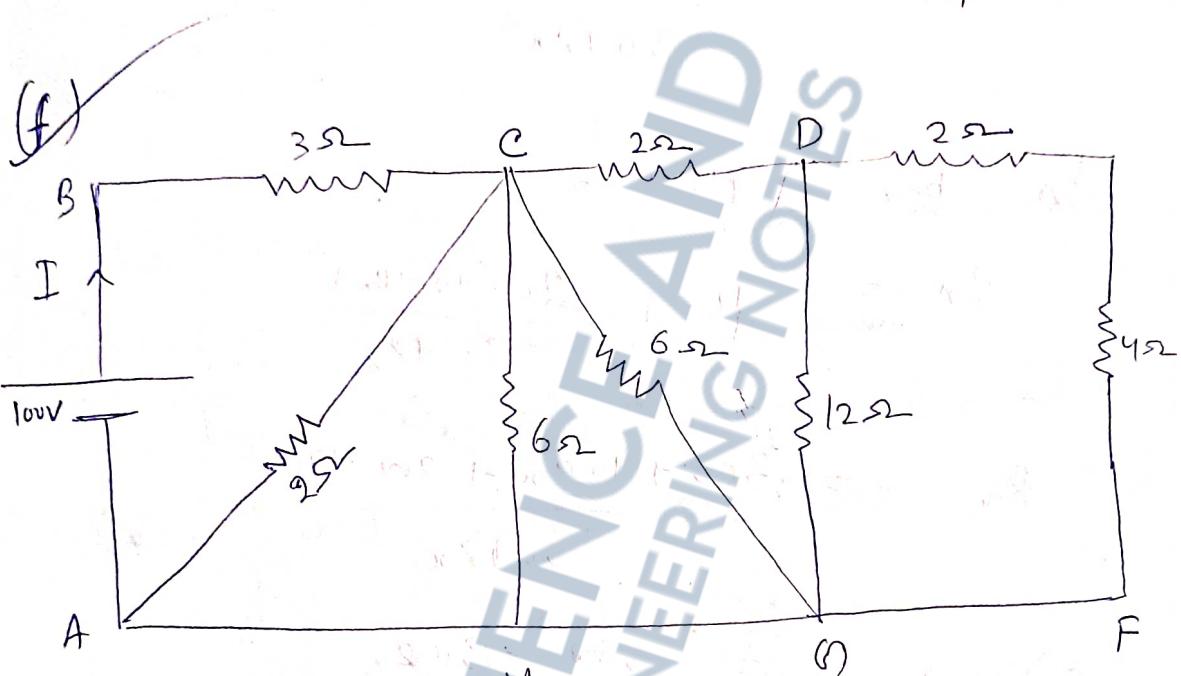

$$Ans = 25 \text{ Amp}$$

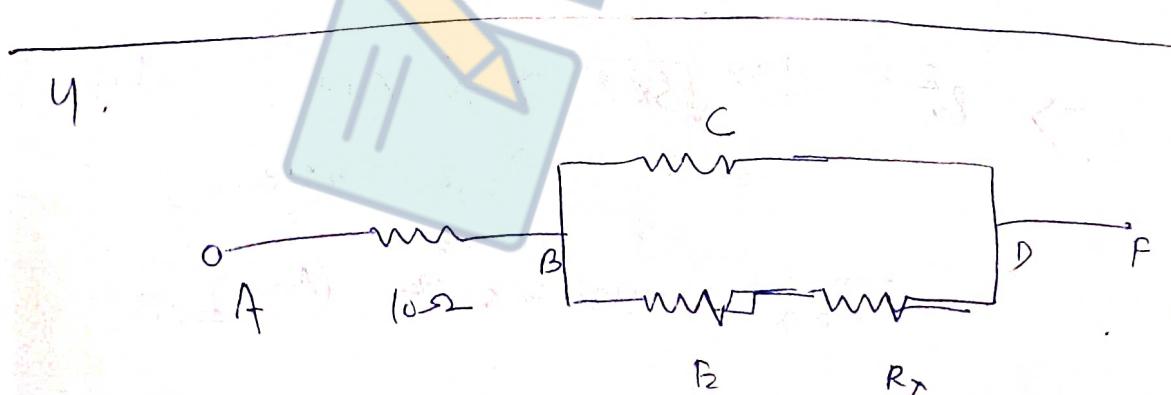

$$\text{Circuit} \quad R_{AF} = R_x$$

$$\begin{aligned} \text{Now} \quad R_{AF} &= R_{AB} + R_{BD} + R_{DF} \\ &= 10 + R_p + 0 \end{aligned}$$

$$\text{Now } \frac{1}{R_p} = \frac{1}{20} + \frac{1}{10+R_x}$$

$$= \frac{10+R_x+20}{20(10+R_x)}$$

$$\Rightarrow R_p = \frac{20(10+R_x)}{30+R_x}$$

An per question

$$R_m = 10 + \frac{20(10+R_x)}{30+R_x}$$

$$R_m = \frac{300 + 10R_x + 200 + 20R_x}{30+R_x}$$

$$\Rightarrow R_x = \frac{500 + 30R_x}{30+R_x}$$


$$\Rightarrow 30R_x + R_m^2 = 500 + 30R_x$$

$$\Rightarrow R_x^2 = \sqrt{500} = \sqrt{5} \times 10$$

$$= 2.236 \times 10$$

$$\therefore R_x = 22.36 \Omega \text{ (Ans)}$$

Answer to the Problems

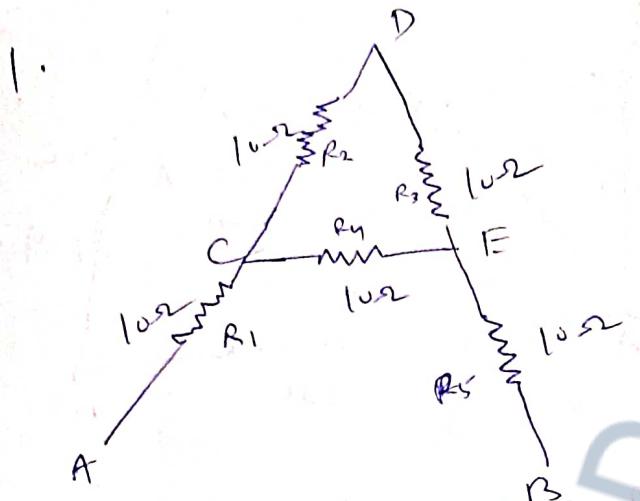

R_2 and R_3 are connected in series

Then the equivalent resistance

$$R_{S1} = \frac{1}{2} (10\Omega + 10\Omega) = 20\Omega$$

R_{S1} and R_4 are connected in parallel.

$$\frac{1}{R_{P1}} = \frac{1}{10} + \frac{1}{20} = \frac{2+1}{20} = \frac{3}{20}$$

$$\Rightarrow R_P = \frac{20}{3}\Omega$$

Also R_1 and R_P are connected in series.


Then equivalent resistance

$$R_{S2} = 10 + \frac{20}{3} + 10$$

$$= \frac{30 + 20 + 30}{3} = \frac{80}{3}\Omega$$

∴ Equivalent resistance between A and B $\frac{80}{3}\Omega$

(b)

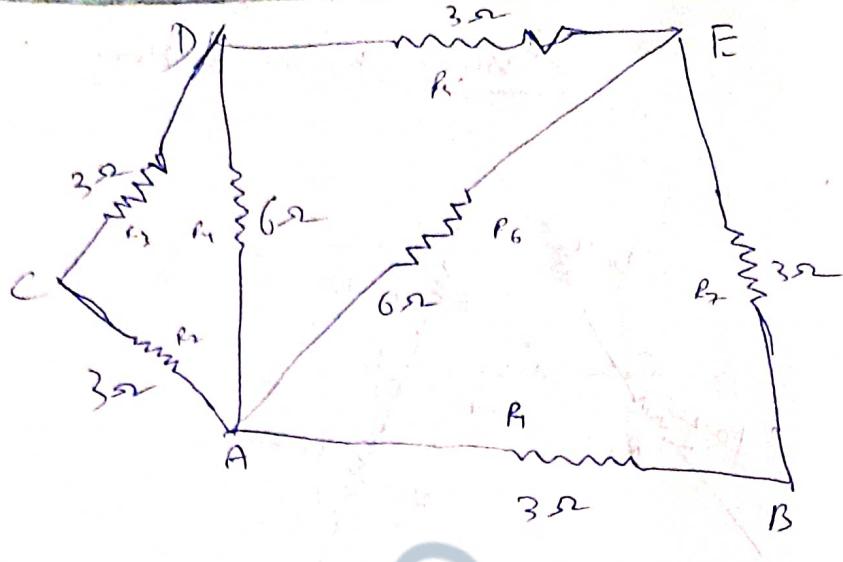

R_2 and R_3 are connected in series.

Equivalent resistance $R_{S1} = 6 \Omega$

R_4 is connected in parallel then

Equivalent resistance

$$\frac{1}{R_{P1}} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6} = \frac{1}{3}$$

$$\Rightarrow R_{P1} = 3 \Omega$$

R_{P1} and R_5 are connected in series

$$R_{S2} = 3 + 3 = 6 \Omega$$

R_{S2} and R_6 are connected in parallel

$$\frac{1}{R_{P2}} = \frac{1}{6} + \frac{1}{2} = \frac{2}{6} = \frac{1}{3}$$

$$\therefore R_{P2} = 3 \Omega$$

R_{P_2} and R_7 are connected in series


$$\therefore R_{S_3} = 3 + 3 = 6 \Omega$$

R_{S_3} and R_1 are connected in parallel

$$\therefore \frac{1}{R_{P_2}} = \frac{1}{6} + \frac{1}{R_3} = \frac{1+2=3}{6} = \frac{3}{6} = \frac{1}{2}$$


$$\therefore R_{P_3} = 2 \Omega$$

(d)

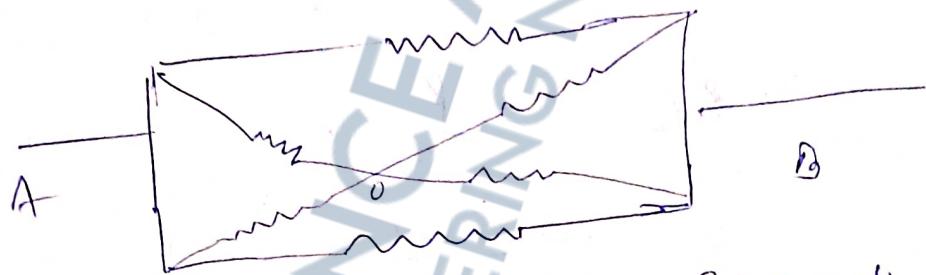

This figure can be

changed to

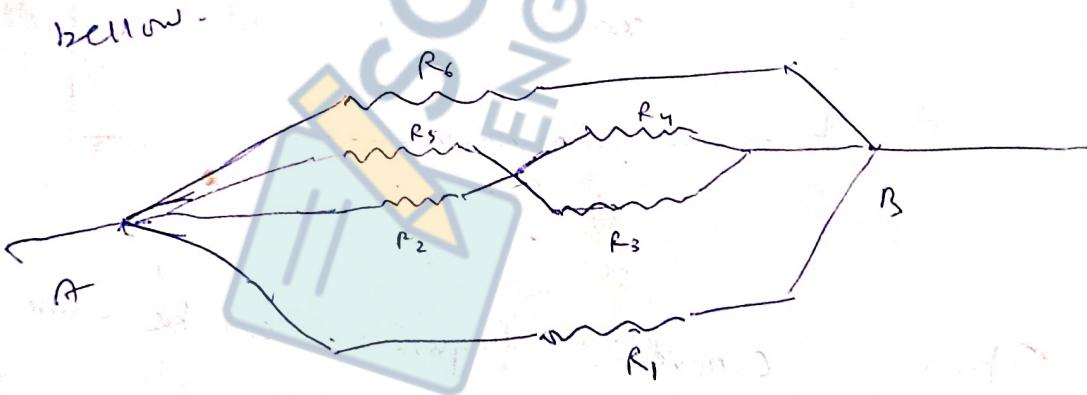

$$\text{But } R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R$$

R_2 and R_5 are connected in parallel $\therefore R_{P_1} = \frac{R_2 R_5}{R_2 + R_5} = \frac{R \cdot R}{2R} = \frac{R}{2}$

R_1 and R_3 are connected in parallel $= \frac{R}{2}$

$$\text{Equiv. resistance} = \frac{R}{2}$$

But R_2 and R_5 are shorted.

∴ Net resistance $R_{S_1} = \frac{R}{2} - \frac{R}{\sum} = R$



∴ R_1 , R_{S_1} and R_S are parallel

$$\therefore \frac{1}{R_{P_2}} = \frac{1}{R_1} + \frac{1}{R_{S_1}} + \frac{1}{R_S}$$

$$= \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$

$$\Rightarrow R_{P_2} = \frac{R}{3}$$

(e)

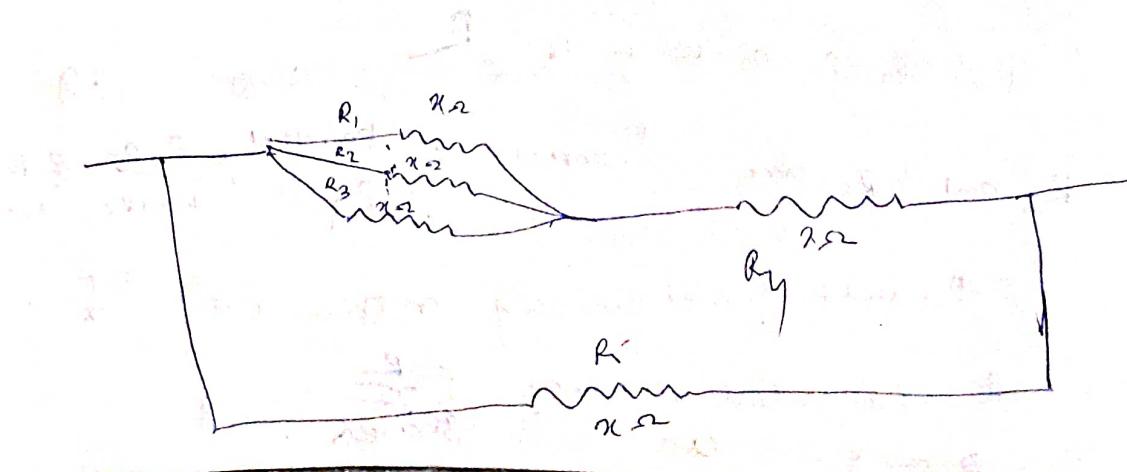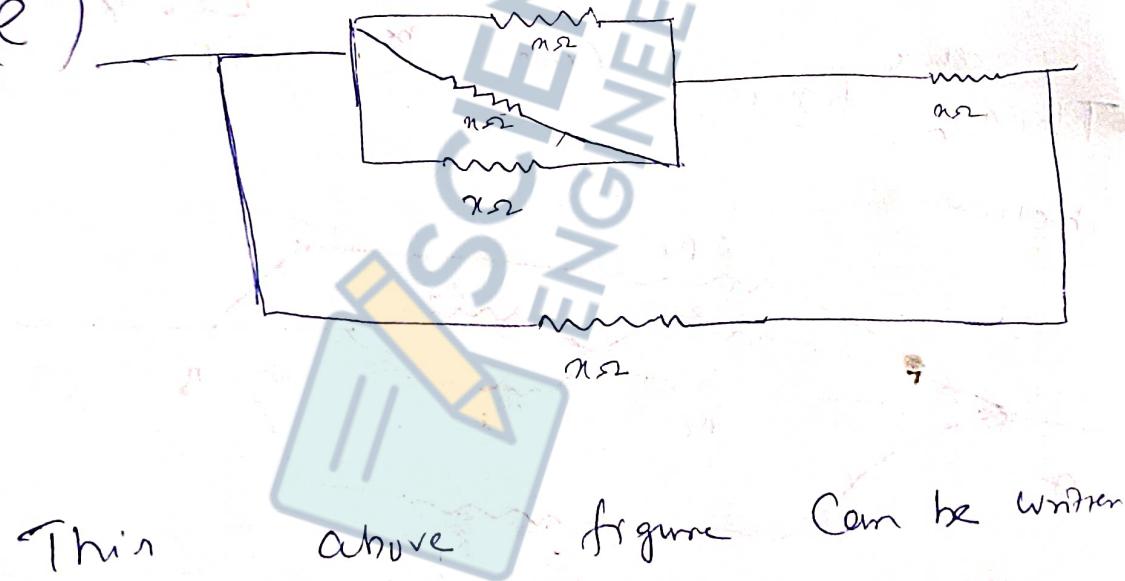

From the figure R_1 and R_2 and R_3

are connected in series.

The equivalent resistance R_{P1}

$$\therefore \frac{1}{R_{P1}} = \frac{1}{n} + \frac{1}{n} + \frac{1}{n} = \frac{3}{n}$$

$$\Rightarrow R_{P1} = \frac{n}{3} \Omega$$

then R_{P1} and R_1 are connected in series.

$$\therefore R_{C1} = \frac{2}{3} n - \frac{n+3n}{3} = \frac{4n}{3}$$

Then R_{S1} is connected in parallel


with R_{C1}

$$\therefore \frac{1}{R_{P2}} = \frac{1}{n} + \frac{3}{4n}$$

$$\Rightarrow \frac{1}{R_{P2}} = \frac{4n}{4n} = \frac{7}{7n} \Omega$$

$$\Rightarrow R_{P2} = \frac{7n}{7} \Omega$$

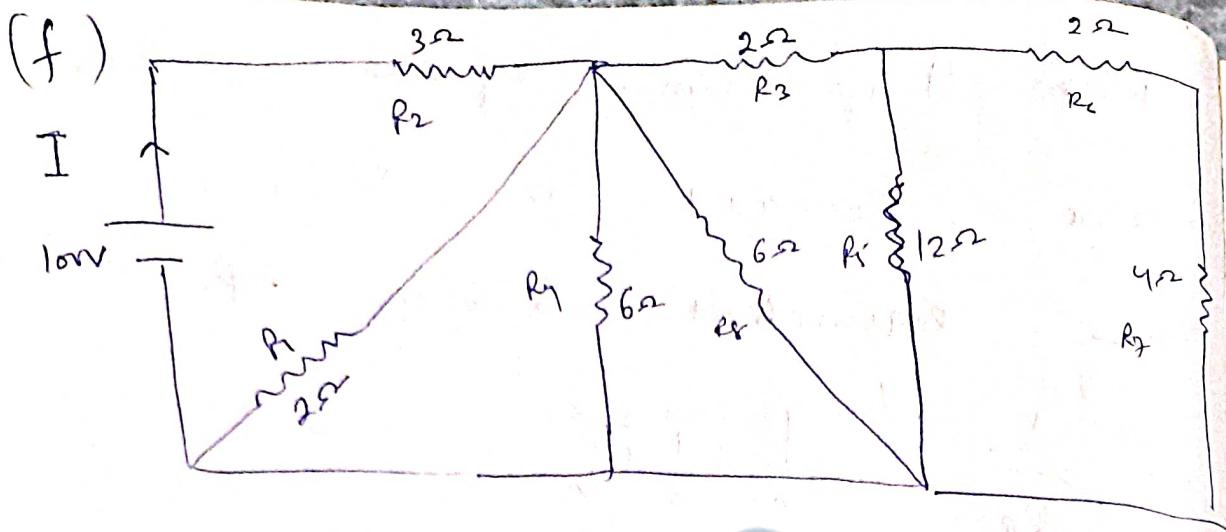∴ Equivalent resistance between A and B is $\frac{7n}{7}$



R_6 and R_7 are connected in series.

$$R_{S4} = 2 + 4 = 6\Omega$$

R_{S1} and R_{S2} are connected in parallel

$$\frac{1}{R_{P1}} = \frac{1}{6} + \frac{1}{12} = \frac{2+1}{12} = \frac{3}{12}\Omega$$

$$\Rightarrow R_{P1} = \frac{12}{3} = 4\Omega$$

R_{P1} and R_3 are connected in series

$$R_{S2} = 4\Omega + 2\Omega = 6\Omega$$

R_{S2} and R_4 are connected in parallel

$$\frac{1}{R_{P2}} = \frac{1}{6} + \frac{1}{2} = \frac{2+6}{12} = \frac{8}{12} = \frac{2}{3}\Omega$$

$$\Rightarrow R_{P2} = 3\Omega$$

R_4 and R_3 are connected in series.

$$R_{S3} = 6 + 3 = 9\Omega$$

R_P , R_{P_2} and R_Y are connected in parallel.

$$\therefore \frac{1}{R_P} = \frac{1}{3} + \frac{1}{6} = \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$\therefore R_P = 2\Omega$

R_P and R_Y are connected in parallel.

$$\therefore \frac{1}{R_{P_Y}} = \frac{1}{2} + \frac{1}{2} = 1$$

$R_{P_Y} = 1\Omega$

R_Y is connected in parallel.

$$R_P, R_{P_Y}$$
 and R_Y are connected in series.

$$\therefore R_{S3} = 1\Omega + 3\Omega = 4\Omega$$

$$R = 4\Omega$$

\therefore Net resistance $= 4\Omega$

Voltages $100V$ -

25 Amp.

$$I = \frac{V}{R} = \frac{100V}{4\Omega} = 25 \text{ Amp.}$$

Variation of resistance with temperature

When a temperature of a wire is increased the atoms or molecules start to vibrate more and more. As a result the free electrons will experience greater number of collisions and the resistance increases. The formula connecting the resistance at a higher temperature with a resistance at $0^\circ C$ is given by

$$R_\theta = R_0(1 + \alpha\theta)$$

where, α is a constant for a particular material is called co-efficient of resistance.

R_0 R_0 = Resistance at $0^\circ C$

R_θ = Resistance at $\theta^\circ C$

$$\alpha = \frac{R_\theta - R_0}{R_0 \cdot \theta} = \frac{\Delta R}{R_0 \cdot \Delta \theta}$$

Because
 $\Delta \theta = \theta - 0$

= Rate of
temp.

Thus, a co-efficient of resistance can

be defined as the ratio of change in resistance to the original resistance at $0^\circ C$ per degree rise of temp.

Unit of α


$$/^\circ\text{C} = \text{C}^{-1} \text{ or } \text{F}^{-1}$$

If a graph be plotted with Ω along X-axis and R_0 along Y-axis, it comes out to be a straight line having Intercept = R_0 and Slope = $R_0 \alpha$.

(My answer
no. 20)

$$R_0 = R_0 + R_0 \alpha \theta$$

$$y = C + m \alpha$$

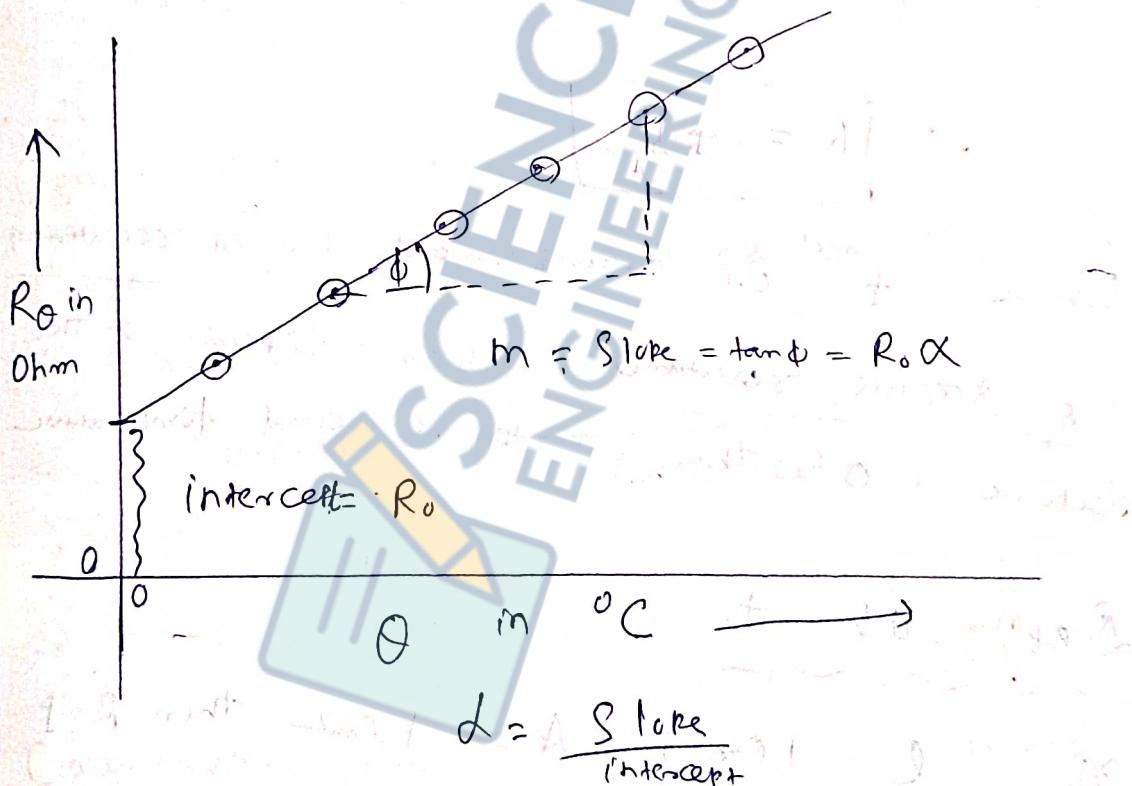

Resistivity or Specific Resistance

Experimentally it is found that resistance of a conductor vary directly on the length of it when area or cross-section is kept constant.

$\therefore R \propto l$, when A is Kept Constant.

Resistance of conductor is found to be inversely proportional to the Area or Cross-Sectional Area of conductor when length of conductor is kept constant.

$\therefore R \propto \frac{1}{A}$, when l is kept constant.

Combining these two variations, we have

$R \propto \frac{l}{A}$, when l and A vary, but


$$\therefore R = \rho \frac{l}{A}$$

where ρ is a constant called resistivity

or specific resistance which depends on the nature of the material and temperature.

Defn of ρ

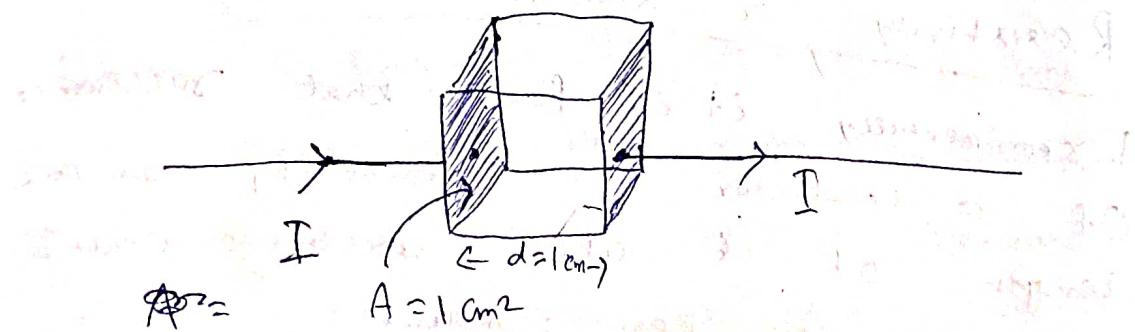if $l = 1 \text{ cm}$, $A = 1 \text{ cm}^2$ then $R = \rho$



Thus, specific resistance or resistivity of a material can be defined as numerically equal to the resistance between the opposite faces of a unit cube made out of the material.

Unit of ρ

$$\rho = \frac{RA}{l}$$

$$1. \text{ C.G.S. Unit} = \frac{\text{Ohm} \cdot \text{cm}^2}{\text{cm}} = \text{Ohm} \cdot \text{cm}$$

$$2. \text{ M.K.S. Unit} = \frac{\text{Ohm} \cdot \text{m}^2}{\text{m}} = \text{Ohm} \cdot \text{metre}$$

Conductivity and Conductance

Conductance is defined as the reciprocal of resistance.

$$1. e \quad \text{Conductance} = \frac{1}{\text{Resistance}} = \frac{1}{\text{Ohm}} = (\text{Ohm})^{-1}$$

or mho

(V)

Conductivity is defined as reciprocal of resistivity.

$$\text{Conductivity} (\sigma) = \frac{1}{\text{Resistivity} (\rho)}$$


$$(1) \text{ C.G.S. unit of } \sigma = \frac{1}{\text{Ohm} \cdot \text{cm}} = \frac{1}{\text{Ohm}} \cdot \frac{1}{\text{cm}}$$

$$= \text{mho} \cdot \text{cm}^{-1}$$

$$\textcircled{2} \text{ M.K.S unit of } (\rightarrow) \text{ is } \frac{1}{\Omega \cdot \text{metre}} = \frac{1}{\Omega} \cdot \frac{1}{\text{metre}} = \text{mho} \cdot \text{m}^{-1}$$

* Shunt

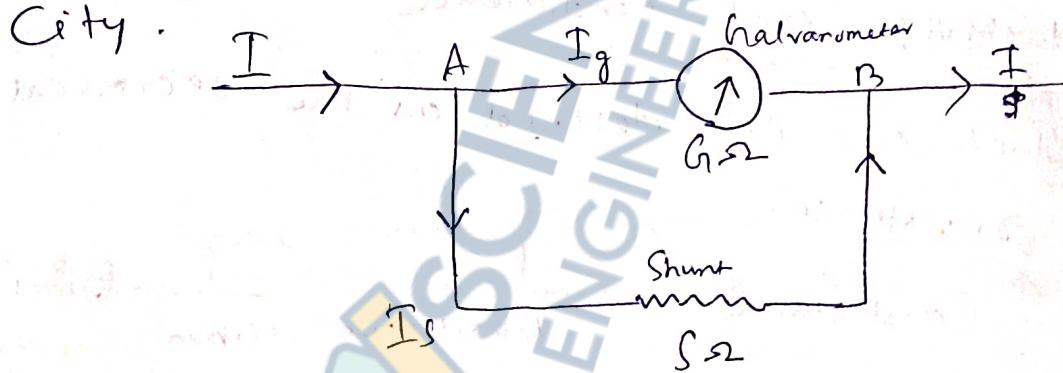It is a ~~for~~ low resistance connected in parallel to ~~costly~~ electrical instrument like galvanometers to save them from damage caused by the passage of high current. In this regard shunt acts like a bypass road of a city.



To express the galvanometer current (I_g) and the shunt current I_s in terms of the main current I , we

see that

$$V_A - V_B = I_g \cdot G = I_s \cdot S$$

$$\text{or } \frac{I_s}{I_g} = \frac{G}{S}$$

Applying Adding 1 to both the sides,

we have

$$\frac{I_s}{I_g} + 1 = \frac{G}{S} + 1$$

$$\Rightarrow \cancel{\frac{I_s + I_g}{I_g}} -$$

$$\Rightarrow \frac{I_s + I_g}{I_g} = \frac{G + S}{S}$$

or $\frac{I}{I_g} = \frac{G + S}{S}$

or $\frac{I_g}{I} = \frac{S}{G + S}$

$\therefore I_g = I \left(\frac{S}{G + S} \right)$

$$\therefore I_s = \frac{I_g \cdot G}{S} = \frac{\left(\frac{S}{G + S} \right) \times I \times G}{S}$$


$$= \frac{S \times G \times I}{S(G + S)}$$

$$= \left(\frac{G}{G + S} \right) I$$

So most of the current flows through shunt so the current it carries

To prove that $I = nAve$

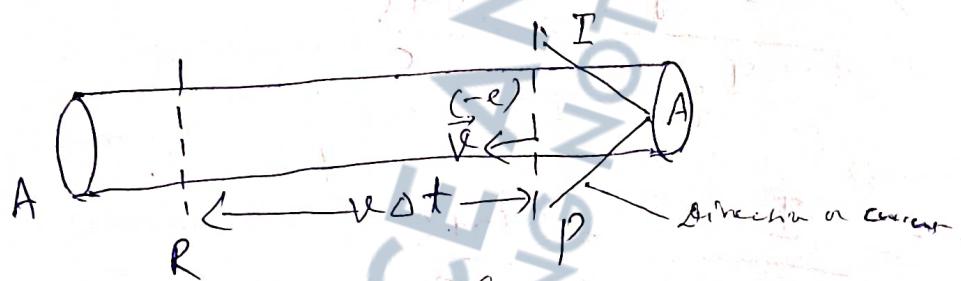Let there be a conductor of area of cross section A in which a current of I ampere is flowing. Let's try to calculate the number of electrons crossing a particular reference line P.



In a time Δt , all the electrons crossing the reference line P will be within the cylinder between P and R. The volume of the cylinder between P and R is $\pi r^2 \Delta t$.

A next Av Δt

If n be the number of electrons per unit volume, then total number of electrons present within this cylinder equal to $n \pi r^2 \Delta t$. Magnitude

of flux charge contained by each electron equal to e .

Total Charge present in the cylinder

$$= n \cdot A \cdot V \cdot e$$

$$= \Delta Q \text{ (say)}$$

= Charge that has crossed the reference line at P during Δt sec.

$$\therefore I = \frac{\Delta Q}{\Delta t} = \frac{n A V e \Delta t \cdot e}{\Delta t} = n A V e$$

Where n = number of electrons per unit volume (Bouyed)

A = Area of cross section of conductor

v = velocity of electron, e = charge of electron.

Origin of resistance

It has been calculated that number of electrons present per meter³ or a good conductor is 10^{28} . This is a large number.

In external electric field, these electrons move at random and the vector sum of the velocities becomes zero.

$$\vec{V}_{avg} = \vec{U}_1 + \vec{U}_2 + \dots + \vec{U}_n$$

$$= 0$$

If t_1 be the time taken by the first electron to collide with another

electron, due to the application of an external electric field intensity, then the velocity at the time of collision is given by $\vec{V}_1 = \vec{U}_1 + \vec{a} t_1$

$$\text{and it is given by}$$

Where $\vec{a} = \text{accn of the electron}$,

$$= \frac{\text{Force}}{\text{Mass}} = \frac{q \cdot \vec{E}}{m} = \frac{-e \vec{E}}{m}$$

Where $\vec{E} = \text{net external field intensity along in the direction of motion of first electron, acting on the first electron.}$

Similarly, the second electron will have a velocity $\vec{V}_2 = \vec{U}_2 + \vec{a} t_2$, given by

$$\vec{V}_2 = \vec{U}_2 + \vec{a} t_2$$

and for the last electron

$$\vec{V}_N = \vec{U}_N + \vec{a} t_N$$

Average velocity of all these electrons colliding with other electron is given by

$$\vec{V}_{avg} = \frac{\vec{V}_1 + \vec{V}_2 + \vec{V}_3 + \dots + \vec{V}_N}{N}$$

$$\vec{V}_{AV} = \frac{(\vec{U}_1 + \vec{a}t_1) + (\vec{U}_2 + \vec{a}t_2) + \dots + (\vec{U}_N + \vec{a}t_N)}{N}$$

$$= \frac{(\vec{U}_1 + \vec{U}_2 + \dots + \vec{U}_N)}{N} + \frac{\vec{a}(t_1 + t_2 + \dots + t_N)}{N}$$

$$= 0 + \vec{a}\gamma$$

Initial velocity

Caused by

Relaxation time

where γ is called average relaxation time
 which is defined as the average time taken by the electrons to collide with another electron.

The average speed of an electron inside the conductor is due to many collisions this average velocity or electron is called drift velocity given by the expression.

$$\vec{V}_d = \vec{a} \cdot \gamma = \left(-\frac{e \cdot \vec{E}}{m} \right) \cdot \gamma$$

We know that current is relate to the drift velocity by the formula

$$I = n \cdot A \cdot V_d \cdot e$$

$$= n \cdot A \cdot \left(-\frac{e \cdot \vec{E}}{m} \right) \cdot \gamma \cdot e$$

$$\text{or } \frac{I}{R} = n \cdot A \cdot \left(-\frac{e \cdot \vec{E}}{m} \right) \cdot \gamma \cdot e \cdot R$$

$$\text{Or } \frac{V}{R} = -n A \cdot (-e \cdot \frac{\Delta V}{\Delta \phi}) \propto \frac{e}{m}$$

$$\Rightarrow \frac{V}{R} = n A e \frac{V}{l} \cdot \frac{n \cdot e}{m}$$

Because

$$V = \text{P.d. across the Conductor}$$

over length l

$$= \Delta V$$

$$\Rightarrow \frac{1}{R} = \frac{n \cdot A \cdot e^2 \cdot l}{m \cdot l} = \text{Conductance} \quad (i)$$

$$R = \frac{m \cdot l}{n \cdot A \cdot e^2 \cdot l} = \text{Resistance} \quad (ii)$$

But resistivity (ρ) is related to the resistance by the formula

$$R = \rho \cdot \frac{l}{A} \quad (3)$$

Comparing the eqns (2) and (3) we get

$$\rho = \frac{m}{n e^2 \cdot l} \quad (4)$$

ρ = Resistivity

$$\text{Conductivity} = \sigma = \frac{1}{\rho} = \frac{n e^2 \cdot l}{m} \quad (5)$$


When the temp or conductor is increased
the electrons will cause thermal
energy $(\frac{1}{2}kT)$ per degree of freedom]

and they will collide more often
hence γ will be decrease from the
expression (i) and (iv) we see that
resistance and resistivity will increase

on the other hand from the expression (5)
and (ii) we see that conductivity and conductance
decreases.

Page \rightarrow 654

3v.

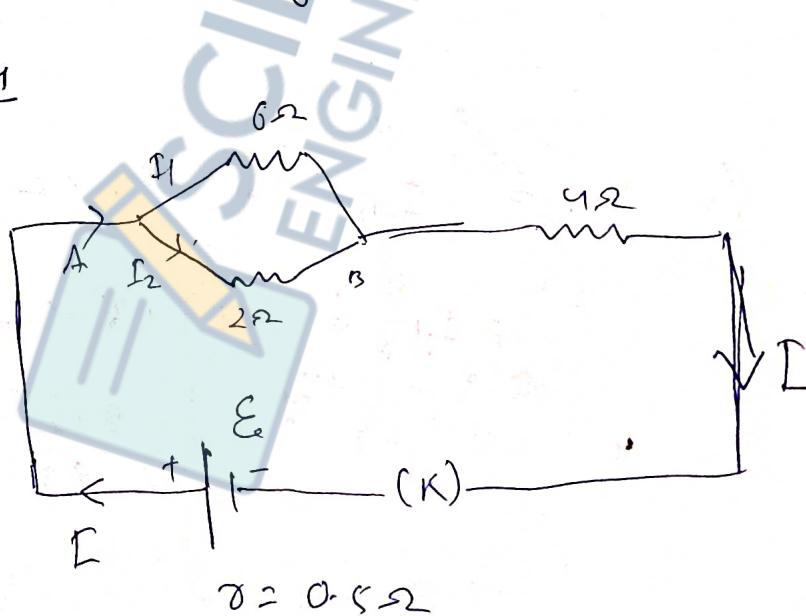

6 Ω resistance and 2 Ω resistance are
connected in parallel

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{2} = \frac{2+6}{12} = \frac{8}{12} \Rightarrow$$

$$R_p = \frac{12}{8} = \frac{6}{4} = \frac{3}{2}$$

R_p and g_2 are connected in series.

$$R_s = R_p + g_2 = \frac{3}{2} + 4 = \frac{3+8}{2} = \frac{11}{2}$$

Total resistance = $R_{s1} + g_2$

$$= \frac{11}{2} + 0.8$$

$$= \frac{11+1.6}{2} = \frac{12.6}{2}$$

Current = $\frac{\text{Voltage}}{\text{total resistance}}$

$$V_A - V_B = I_1 \cdot 6 = I_2 \times 2$$


$$-I_2 \cdot 6 = 18 \times 2$$

$$\Rightarrow I_1 = \frac{8 \times 2}{6} = \frac{16}{6} = \frac{8}{3}$$

$$\text{Total current} = I_1 + I_2$$

$$= \frac{8}{3} + 0.8$$

$$= \frac{8+2.4}{3} = \frac{10.4}{3}$$

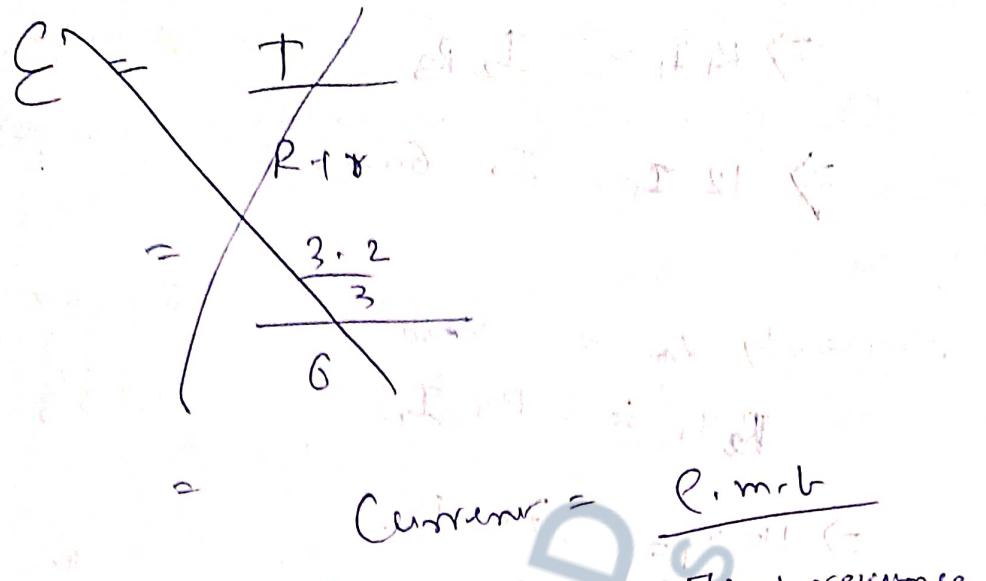

~~Total~~ \Rightarrow $\text{emf } V = \text{Current} \times \text{Total resistance}$
 $\frac{3 \cdot 2}{3} \times \frac{2}{6} \Omega$
 $= 6.4 \text{ volt}$

21. 22

20.


Given that

$$R_1 = 12\Omega, R_2 = 15\Omega$$

$$R_3 = 6\Omega, R_4 = 7.5\Omega$$

$$R_n = 10\Omega$$

$$V = 2.48 \text{ V}$$

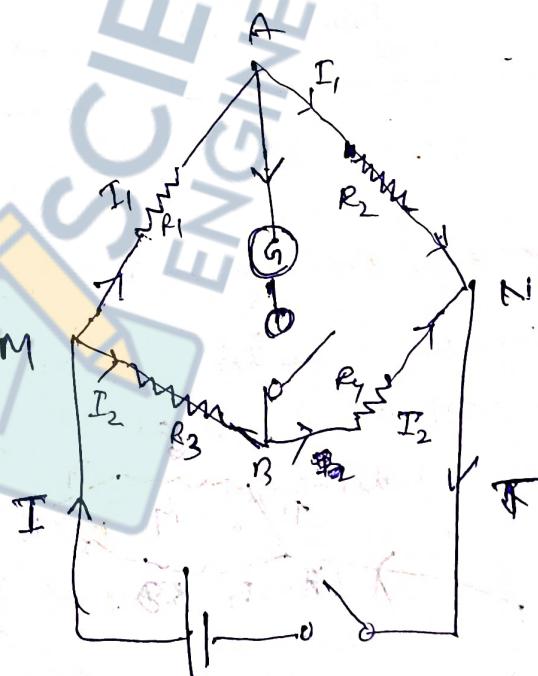

The nodes A and B should be at same potential.

When A and B are at same potential.

$$I_1 \cdot R_1 = V_{AB} = V_{MB}$$

$$\Rightarrow R_1 I_1 = I_2 R_3$$

$$\Rightarrow 12 \cdot I_1 = I_2 \cdot 60 \Omega$$

Similarly $V_{AB} = V_{BDA}$


$$R_2 I_1 = R_4 \cdot I_2$$

$$\Rightarrow 15 I_1 = 75 \cdot I_2$$

But Galvanometer has $R = 125 \Omega$.

Polarized
Magnet
Chemical effect
or electric current

Q2 :-

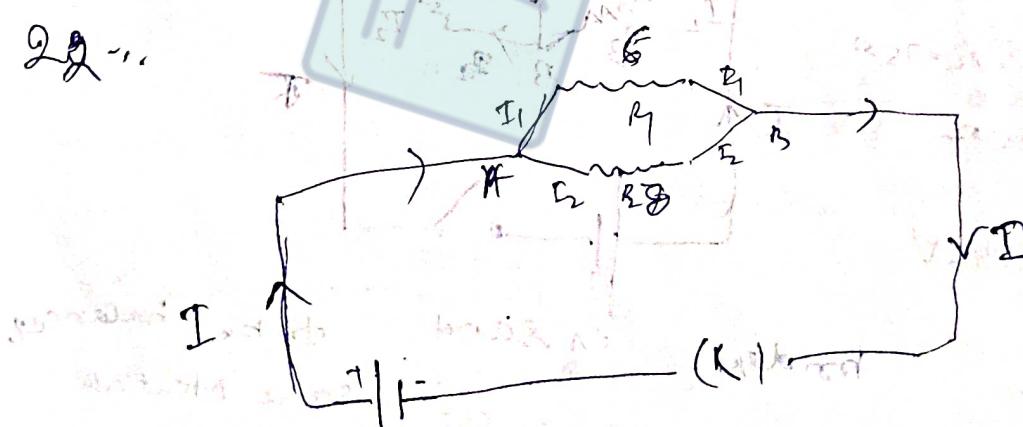

$$\gamma = 0.2 \Omega$$

R_1 and R_2 are connected in series

$$R_{P1} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 8}{6+8} = \frac{48}{14} = \frac{24}{7} \Omega$$

R_{P1} and σ are connected in series.

$$(R_{10}) = R_{S1} = \frac{24}{7} + \frac{2}{70} = \frac{240 + 14}{70} = \frac{254}{70} \Omega$$

$$V_A - V_B = I_1 6 = I_2 8$$

$$\Rightarrow I_1 \times 6 = 0.2 \times 8$$

$$\therefore I_1 = \frac{8 \times 1}{10} = \frac{8}{30}$$


$$E = I (R + \sigma)$$

$$= (I_1 + I_2) (R + \sigma)$$

$$= \left(\frac{8}{30} + \frac{2}{10} \right) \times \frac{254}{70} = \frac{8+16}{30} \times \frac{254}{70} = \frac{144}{30} \times \frac{254}{70} = 1.69 \text{ Volt}$$

1. Problems

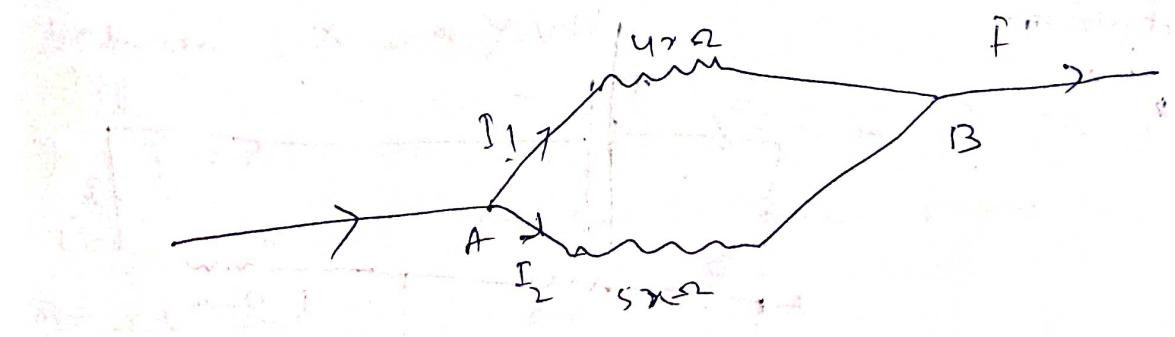1. A conductor carrying a current divider into two branches where resistances are in the ratio 4:5. Compare the amounts of heat generated in the branches (Ans: 5:4)



$$V_A - V_B = I_1 \text{ units } I_2 5\pi$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{5}{4}$$

$$\frac{I_1^2 R_1 t}{I_2^2 R_2 t} = \left(\frac{I_1}{I_2} \right)^2 = \left(\frac{5}{4} \right)^2 = \left(\frac{25}{16} \right)$$

$$\frac{I_2^2 R_2 t}{I_1^2 R_1 t} = \frac{16}{25} \times \frac{4}{3}$$

$$= 5 \cdot 4 \cdot \frac{4}{3} = 3$$

- (2) The resistance of a Copper wire $\frac{1}{12}$ inch in diameter stands $8\Omega/\text{mile}$. What will be the resistance of the


Copper wire $\frac{1}{20}$ inch in diameter and stands long.

$$(\text{Ans: } 22.22\Omega)$$

$$R = \rho \cdot \frac{L}{A}$$

$$\rho = \text{constant}$$

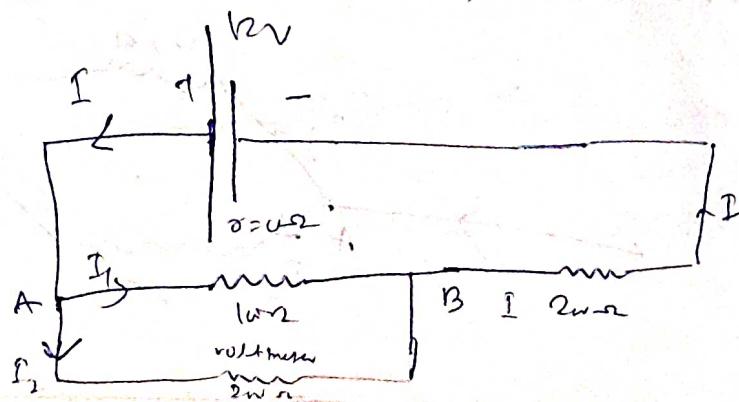- (3) Find Voltmeter reading in the following circuit. (Ans: 3V)



$$V_A - V_B = I W X I_1 = 2 W X I_2 = I \cdot R_p$$


Q. A $6\text{W} \times 1\Omega$ resistor and $4\text{W} \times 2\Omega$ resistor are connected in series across a 90V line. A voltmeter across the $6\text{W} \times 2\Omega$ resistor reads 45V .

(a) Find the voltmeter resistance.

(b) Find the reading of the same

Voltmeter if connected across the $4\text{W} \times 2\Omega$ resistor.

(Ans: $12\text{W} \times 2\Omega$, 30V)

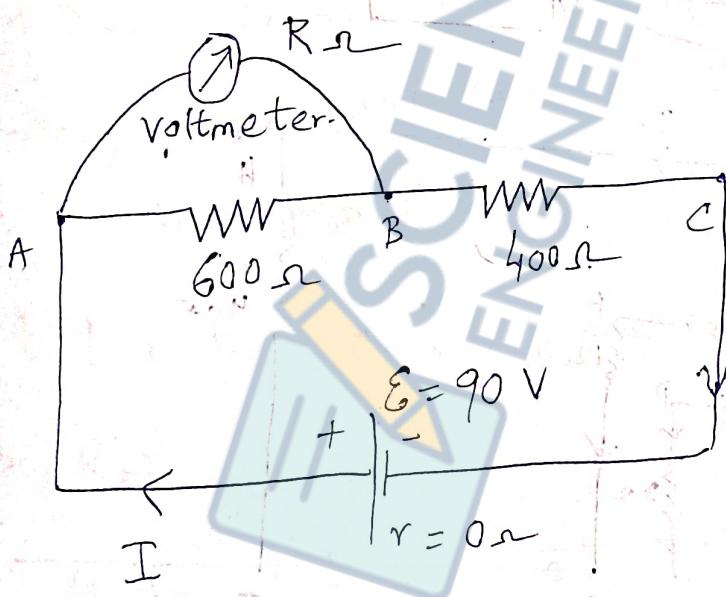


Q.(a) Calculate the equivalent resistance between X and Y.

(b) Find the P.D. between X and a current in the $8\text{W} \times 2\Omega$ resistor

is 0.5Amp .

Ans: $8\text{W} \times 2\Omega$, 12V

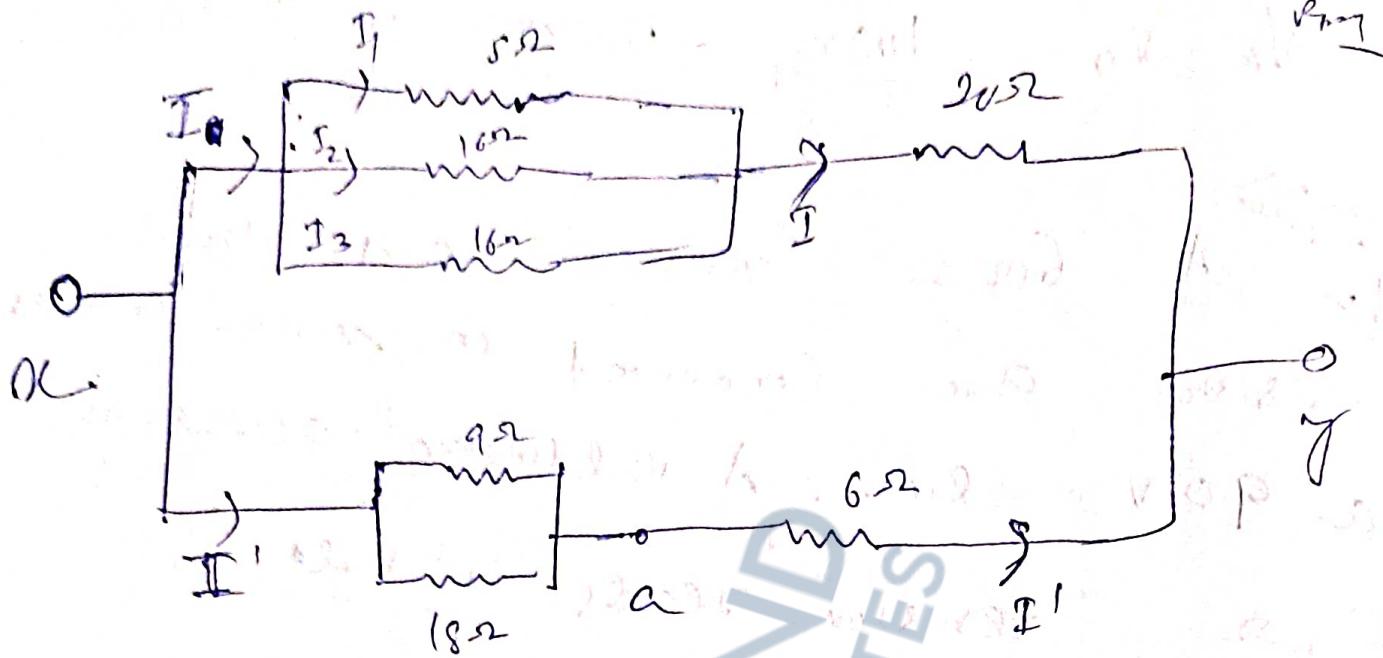


~~6. ^{comes from} what is the Rauvalan resistance between x and y~~

(h) For P-D between Xandy at 320 Volt,

Then find P-D between B and C

Ans. 322, 120 volt

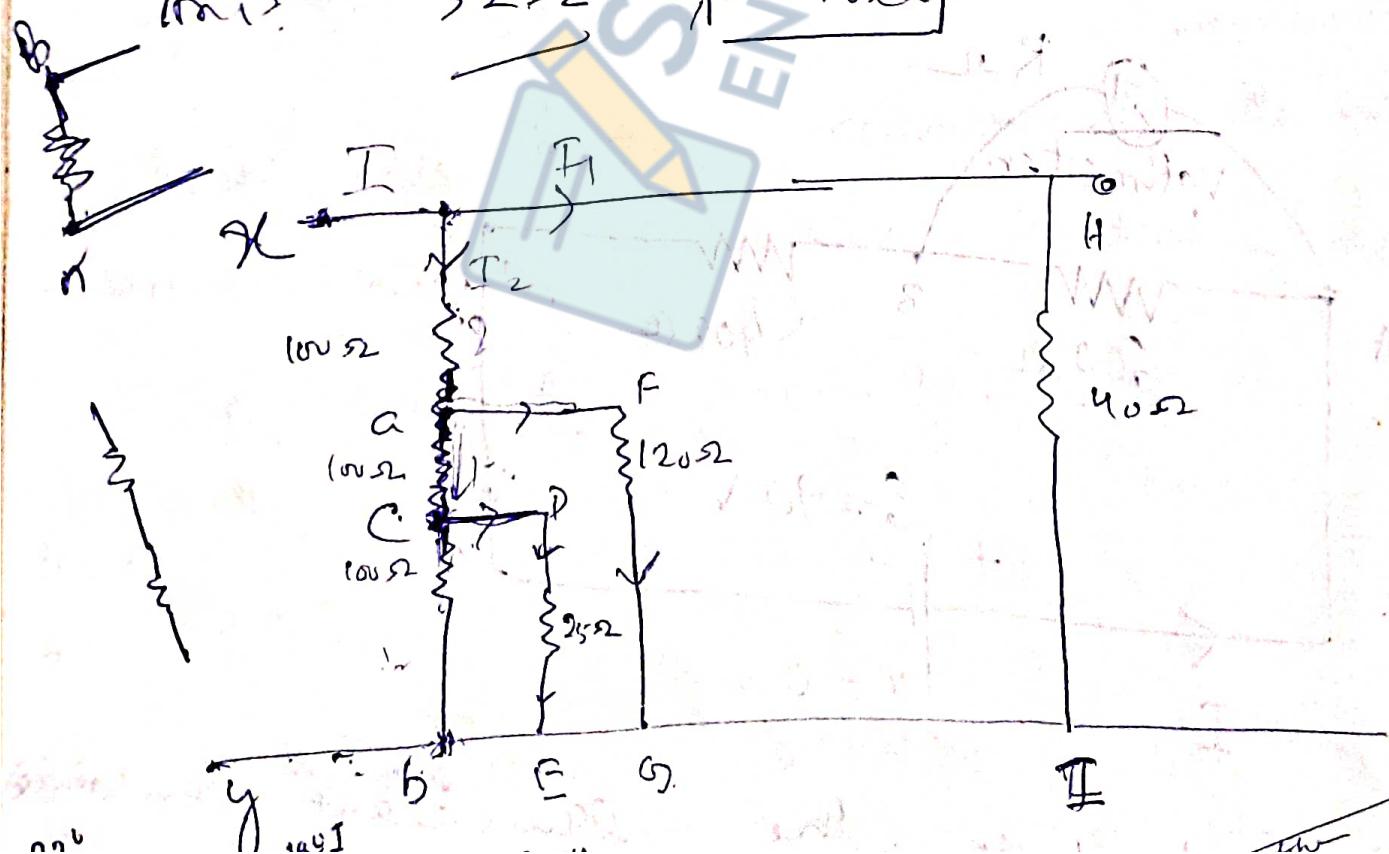

17. Due to symmetry we can think that the current I entering at A will divide into 3 equal parts i.e. $\frac{I}{3}$ along AB,

AD, AF. Each such current will again divide into two equal parts

i.e. along BC and BF it's

$\frac{I}{6}$, along DC and DH it's

along EF and EH it's

Now the currents along BC

and DC combine to become $\frac{I}{3}$ along CB

Similarly there are currents $\frac{I}{3}$ along

FG and HG

Let the equivalent resistance between F and G

be R'_{Ω}

$$\therefore V_A - V_B = R'_{\Omega} I \quad (i)$$

But

$$V_A - V_B = (V_A - V_B) + (V_B - V_C) + (V_C - V_G)$$

$$= \frac{R + R}{3} + \frac{RI}{6} + \frac{RI}{3}$$

$$= \frac{5RI}{6} \quad (ii)$$

Comparing (i) and (ii)

$$R' I^2 = \frac{5SR}{6}$$


$$R' I^2 = \frac{5SR}{6} =$$

$$R' = \frac{5S}{6C}$$

Now our problem $R = 1\Omega$

$$\therefore R' = \frac{5}{6} \Omega$$

I' ?

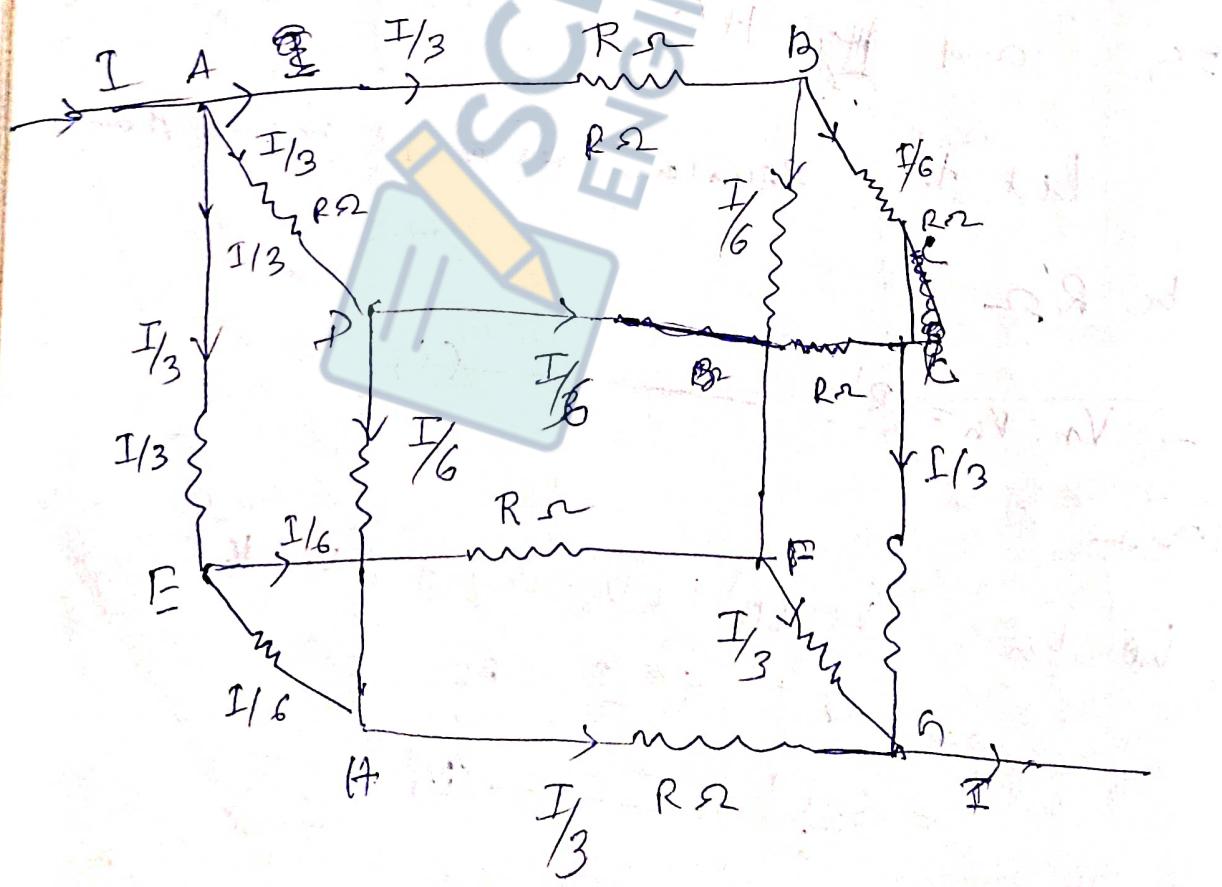

Index →

Answers to problems

2. Copper wire has diameter $\frac{1}{12}$ in ch.

$d_1 = \frac{1}{12}$ inch.

$R_1 = 100 \text{ m} \Omega$

$$l_1 = 8 \Omega / \text{mile}$$

$$d_2 = \frac{1}{20}$$
 inch.

$$l_2 = 1 \text{ mile}$$

$$\gamma_1 = \frac{\pi}{4} \frac{l_1}{A_1}$$

$$\gamma_1 = 1 \frac{\Omega}{\text{m}}$$

$$\therefore \gamma_2 = \frac{\pi}{4} \frac{l_2}{A_2} \text{ and } l_2 = 1$$

$$\frac{\gamma_1}{\gamma_2} = \frac{\frac{\pi}{4} \times A_1}{\frac{\pi}{4} \times A_2} = \frac{L_1 \times \pi d_1^2 \times 4}{L_2 \times \pi d_2^2}$$

$$= \frac{L_1 \times 1 \times \pi \times 400}{L_2 \times 1 \times \pi \times 400} = \frac{L_1 \times 400}{L_2 \times 400}$$

$$= \frac{1}{1} = 1$$

$$\therefore \gamma_2 = \frac{L_1 \times 400}{144} = \frac{L_1 \times 400}{144} \Omega/m$$

$$144 =$$

Again →

$$R = \frac{\gamma \cdot L_1}{\pi d_1^2} = \frac{\gamma \cdot L_1 \times 4 \times 144}{\pi \times 1}$$

$$\therefore \frac{8 \Omega}{\text{mile}} = \frac{\gamma \cdot L_1 \times 576}{\pi}$$

$$\therefore 1 \Omega/mile = \frac{8 \Omega \times \pi}{576 \times \text{miles}}$$

For 2nd case

$$R_{22} = \frac{R \cdot A}{\frac{1}{4}}$$

$$\Rightarrow I = \frac{R \times \pi d^2}{4 \times \pi} = \frac{R \times \pi d^2}{4 \times \pi}$$

$$\Rightarrow I_{\text{min}} = \frac{R \times \pi d^2}{4 \times \pi} = \frac{R \times \pi d^2}{4 \times \pi}$$

$$I = \frac{8 \times \pi d^2}{4 \times \pi} \times \frac{50}{R \times \pi} = \frac{8 \times 50}{R \times \pi}$$

$$I = 50 \times \frac{8}{R \times \pi}$$

$$I = 50 \times \frac{8}{72 \times \pi} = 50 \times \frac{8}{22 \times 22}$$

$$I = 50 \times \frac{8}{22 \times 22} = 50 \times \frac{8}{484} = 50 \times 0.0165 = 0.825 \Omega$$

②

$$R_1 = \frac{\pi L_1}{A_1} = \frac{\pi \cdot L_1}{\pi d_1^2} = \frac{\pi \cdot L_1 \times 4}{\pi d_1^2}$$


$$R_2 = \frac{\pi L_2 \times 4}{\pi d_2^2}$$

$$\frac{R_1}{R_2} = \frac{\frac{\pi L_1 \times 4}{\pi d_1^2} \times \frac{\pi d_2^2}{\pi d_2^2}}{\frac{\pi L_2 \times 4}{\pi d_2^2}} = \frac{(L_1)}{(L_2)} \cdot \left(\frac{d_2^2}{d_1^2} \right)$$

$$\Rightarrow \frac{8 \times \pi}{R_2} = \left(\frac{1}{1} \right) \cdot \left(\frac{1}{400} \times \frac{144}{1} \right) = \frac{72}{200}$$

$$\therefore R_2 = \frac{1600}{72} = \frac{800}{36} = \frac{400}{18} = \frac{200}{9} = 22.22 \Omega$$

The second resistance is 22.22 Ω.

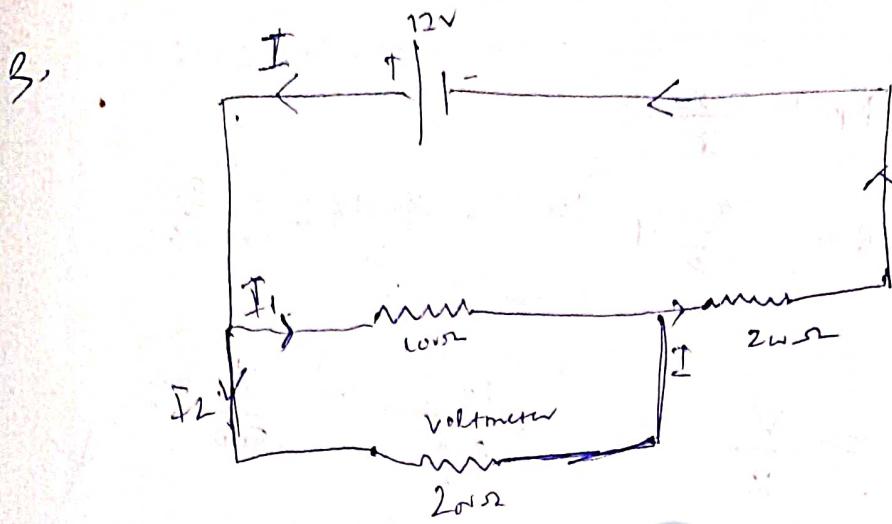

100Ω and

200Ω

are connected in

parallel.

$$\text{i. } R_p = \frac{100 \times 200}{300} = \frac{200}{3} = 66.66\Omega$$

R_p and 200Ω

parallel

connected in

$$R_s = 66.66 + 200 = 266.66\Omega$$

Total performance at $R = 266.66\Omega$.

Voltage = 12V.

$$I = \frac{V}{R} = \frac{12}{266.66\Omega}$$

$$V_A - V_B = I \times R_p = \frac{12^3}{266.66} \times 66.66$$

$$\Rightarrow 12 = \frac{12}{266} \times 66.66$$

Op

$$R_p = \frac{200}{3}$$


$$\text{Total } R = \frac{200}{3} + 200 = \frac{200+600}{3} = \frac{800}{3}$$

$$I = \frac{V}{R} = \frac{12}{\frac{800}{3}} = \frac{36}{800}$$

$$\text{Volmeter reading} = V_A - V_B = R_p \times I$$

$$= \frac{200 \times 36}{800} / 12$$

$$= 3 \text{ volt}$$

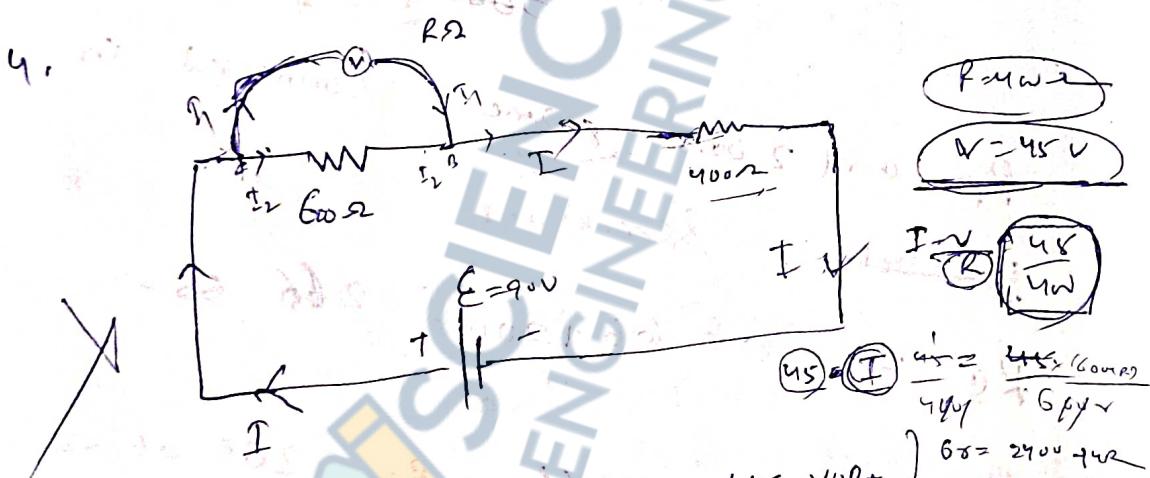

The voltmeter
in the house
total p.d. must = 45 volt
total p.d. = 90V

$$R = 400\Omega, V = 45 \text{ volt}$$

$$I = \frac{V}{R} = \frac{45}{400}$$

600Ω and the internal resistance
of voltmeter are connected in
parallel

$$\text{Net resistance} = \frac{\gamma \times 600}{\gamma + 600}$$

$$\text{Voltage} = 45$$

$$I = \frac{V}{R} = \frac{45}{600}$$

V - IR

~~$$V_A - V_B = I_1 \times R_V = 45 \times 600 \Omega$$~~

~~$$= I_1 \times R_V = I_2 \times 600 \Omega = I \times R_{eq}$$~~

$$\Rightarrow R_V = \frac{I_2 \times 600 \Omega}{I_1}$$

$$45 = I = I_1 + I_2 = \frac{V_1 + V_2}{R_1 + R_2}$$

$$\Rightarrow \frac{I}{R} = \frac{45}{R} + \frac{45}{600} = \frac{45 \times 600 + R}{R(600)}$$

$$\Rightarrow \frac{I}{R} = R(600)$$

∴ $\frac{I}{R} = R(600)$

$$I = \frac{V}{R}$$

Let the resistance of Voltmeter be γ ohm.

∴ R_{out} and γ are connected in II.

$$\therefore \text{Equivalent resistance } R_p = \frac{\gamma \times 600}{\gamma + 600}$$

Net resistance in the circuit. $400 + \frac{600 \times \gamma}{\gamma + 600}$

$$\frac{400}{400 + \frac{600 \times \gamma}{\gamma + 600}} = I \quad (i)$$

$$V_A - V_B = I \times R_p = I \times \frac{600 \times \gamma}{\gamma + 600}$$

$$\Rightarrow 45 \times \frac{600 \times \gamma}{\gamma + 600} = I \quad (ii)$$

Equating both sides or eqn (i) and (ii) ,

We get

$$\frac{90}{4000 \times \frac{600}{600+\alpha}} = 45 \times \frac{600+\alpha}{600} \times \frac{120}{90}$$

$$\Rightarrow \frac{9000 \times (600+\alpha)}{2400000 + 9000\alpha} = 3 \times \frac{(600+\alpha)}{400}$$

$$\Rightarrow 360000 = 720000 + 3000\alpha$$

$$\Rightarrow \cancel{60000} = \cancel{360000} + 3000\alpha$$

$$\Rightarrow \alpha = \frac{360000 - 720000}{3000} = \frac{-360000}{3000} = \underline{\underline{1200}}$$

Again Let the voltmeter resistance be R ohm.

600Ω resistor and R are connected in series.

$$\therefore \text{Equivalent resistance} = \frac{600R}{600+R} = R_p$$

α is connected to 400Ω resistor

$$\text{Net resistance} = 400 + \frac{600R}{600+R} = \frac{240000 + 400R + 600R}{600+R} = \frac{240000 + 1000R}{600+R}$$

$$I = \frac{V}{R} = \frac{90V \times (600+R)}{240000 + 1000R}$$

$$\text{But } V_A - V_B = R_p \times I$$

$$\therefore 45 = R_p \times I$$

$$\Rightarrow I = \frac{45}{R_p} \quad \text{--- (ii)}$$

Equating (i) and (ii), we get

$$\frac{90V^2(600+R)}{240000+1000R} = \frac{45^2(600+R)}{600R}$$

$$\Rightarrow 1200R = 240000 + 1000R$$

$$\Rightarrow 200R = 240000$$

$$\Rightarrow R = \frac{240000}{200} = 1200\Omega$$


(Ans)

Another process

Potential difference

$$= 45 \text{ volt}$$

Potential difference

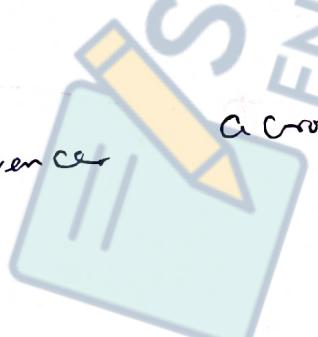

600Ω resistor across 45V cell.


$$45V =$$

$$I \times 600\Omega$$

$$I = \frac{45}{600}$$

$$I = 0.075A$$

$$I = 75mA$$

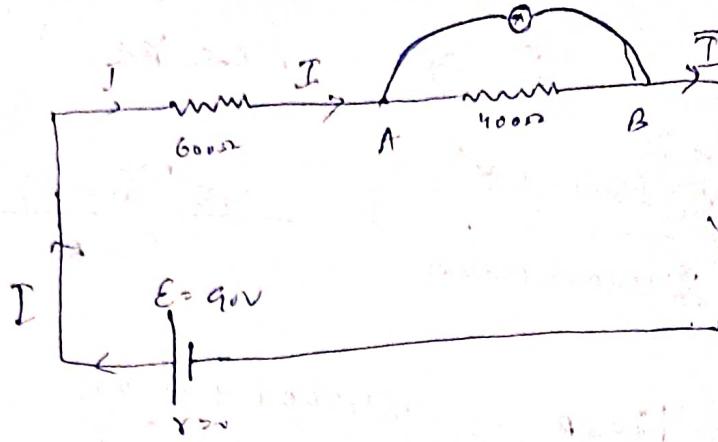

Net resistance = $600 + R_P \rightarrow 600 + \frac{400 \times \gamma}{400 + \gamma}$

* Total Current = $I = \frac{V}{R} = \frac{90 \times (400 + \gamma)}{2400 + 1000\gamma} \quad \text{(i)}$

Also $V_A - V_B = I \times R_P$

$$\Rightarrow \frac{V}{R_P} = I$$

$$\Rightarrow \frac{V (400 + \gamma)}{(400\gamma)} = I$$

Equating (i) and (ii)

$$\frac{V (400 + \gamma)}{400\gamma} = \frac{90 \times (400 + \gamma)}{(240000 + 1000\gamma)}$$


$$\Rightarrow \frac{V}{400 \times 1200} = \frac{90}{(240000 + 1000 \cdot 1200)} \quad \left\{ \begin{array}{l} \text{+ The} \\ \text{same volt} \\ \text{meter is} \\ \text{connected} \\ \text{whole} \\ \gamma = 1200 \Omega \end{array} \right\}$$

$$\Rightarrow V = \frac{400 \times 1200 \times 90}{24,00000 + 1200000}$$

$$= 400 \times 1200 \times 90$$

$$1440000000$$

$$= 30 \text{ volt}$$

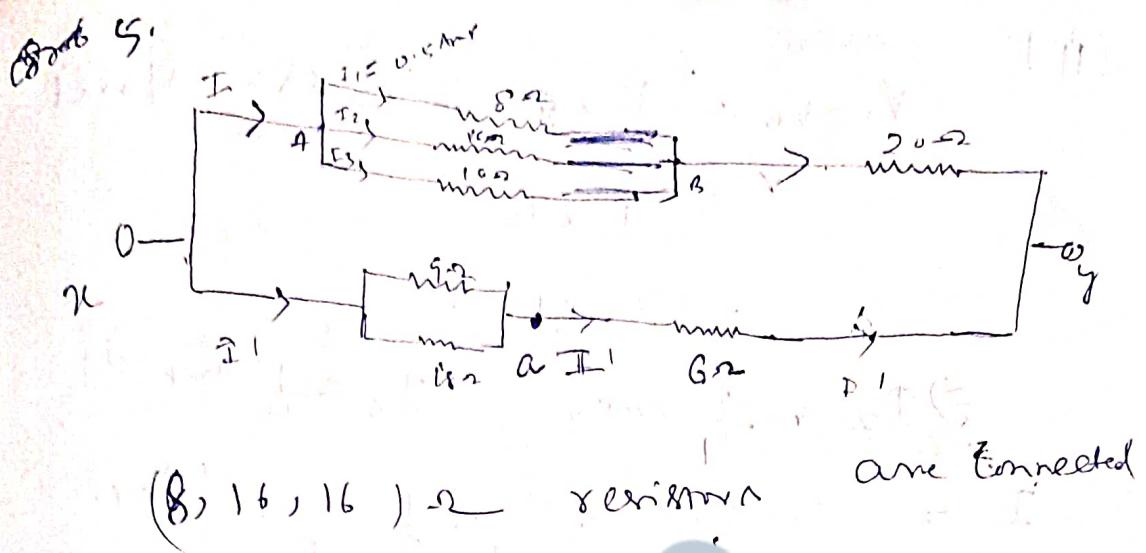

in Parallel.

$$\frac{1}{R_p} = \frac{1}{8} + \frac{1}{16} + \frac{1}{16} = \frac{8+3+3}{48} = \frac{14}{48}$$

$$\therefore R_p = \frac{48}{14}$$

$$\frac{1}{R_p} = \frac{1}{8} + \frac{1}{16} + \frac{1}{16} = \frac{2+1+1}{16} = \frac{4}{16} = \frac{1}{4}$$


$$R_p = 4$$

4Ω and 2Ω are connected in series.

4Ω and 2Ω

$$R_{S1} = 2\Omega$$

9Ω and 18Ω are connected in II.

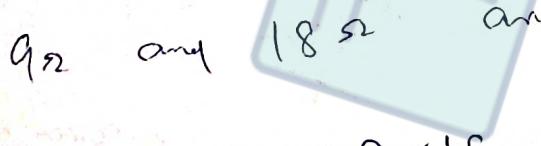

$$\therefore R_{P2} = \frac{9 \times 18}{9+18} = \frac{9 \times 18}{27} = 6\Omega$$

$$R_{S2} = 6\Omega \text{ and } 6\Omega = 12\Omega$$

6Ω and 6Ω are connected in II.

$$R_{S3} = \frac{24 \times 12}{24+12} = \frac{24 \times 12}{36} = 8\Omega$$

$$(11) \quad V_A - V_B = I_1 \times 8 = 1.5 \times 8 = 12 \text{ volt.}$$

$$= I_2 \times 16$$

$$= I_3 \times 16$$

$$\Rightarrow I_2 = \frac{1}{4} \text{ Amp}, \quad I_3 = \frac{1}{4} \text{ Amp.}$$

$$I = I_1 + I_2 + I_3 = \frac{1}{4} + \frac{1}{2} + \frac{1}{4} = 1 \text{ Amp.}$$

Potential drop across 20Ω resistor $\Rightarrow I \times R = 1 \times 20 = 20 \text{ volt.}$

$$V_{xy} = V_A - V_B + 20 \text{ volt} = 4 - 20 = 24 \text{ volt}$$

$$R_{xy} = 8 \Omega$$

$$I_{\text{Total}} = \frac{V_{xy}}{R_{xy}} = \frac{24}{8} = 3 \text{ Amp.}$$

$$I^1 = I_{\text{Total}} - I = 3 - 1 = 2 \text{ Amp.}$$

9Ω resistor and 18Ω resistor are in parallel connect

$$R_P = 6 \Omega$$

$$V_{xa} = R_P \times I^1 = 6 \times 2 = 12 \text{ volt} \quad (\text{Ans})$$

Q. Form the circuit diagram

and R_{ce}

the circuit

are connected in parallel.

$$R_P = \frac{100 \times 25}{100+25} = \frac{100 \times 25}{35} = 20 \Omega$$

20Ω and R_{ce} are connected in series

$$\therefore R_{eq} = 120 \Omega$$

120Ω and 120Ω are connected in parallel.

$$\therefore R_{P2} = \frac{120 \times 120}{240} = 60 \Omega$$

6Ω and 10Ω are connected in series.

$$R_{S2} = 10\Omega + 6\Omega = 16\Omega$$

16Ω and 4Ω are connected in parallel.

$$\therefore R_{xy} = \frac{16\Omega \times 4\Omega}{20\Omega} = 3.2\Omega$$

P.D between X and Y = 320 Volt

Resistance

$$= 3.2\Omega$$

$$\text{Current } I = \frac{V}{R} = \frac{320}{3.2} = 10 \text{ Amp.}$$

Due to symmetry $I_1 - I_2 = 5 \text{ Amp.}$

$$V_{xy} = 16\Omega \times I_2 = I_2 \times 4\Omega$$

$$\Rightarrow 320 = 16\Omega I_2 = 4\Omega I_1$$

$$\therefore I_1 = 8 \text{ Amp.} \quad I_2 = 2 \text{ Amp.}$$

I_2 again is 2 Amp. again divided into 1 amp and 2 amp.


Through a & b $= I^{\prime} \text{ Amp.}$ through $c = 1 \text{ Amp.}$ (I)

$$R_{P1} = 20\Omega$$

$$V_{bc} = I_{ac} R_P = 1 \times 20 = 20 \text{ Volt}$$

Current In Ares

Q. 31.

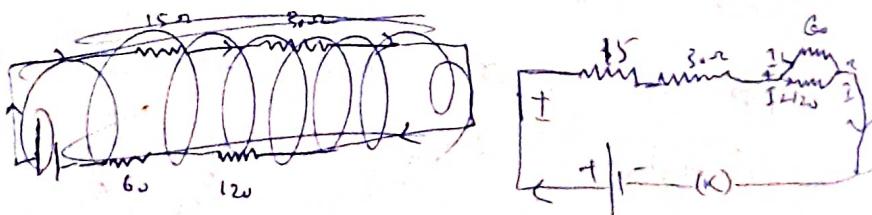

$$V_A - V_B = I_1 \times 60 : I_2 \times 120^2$$

$$\Rightarrow I_1 = 2I_2$$

AC from 15 and 30 Ω resistor at heat developed.

$$\frac{I^2 R_1 t}{T}, \quad \frac{I^2 R_2 t}{T}$$

The ratio = $\frac{R_1}{R_2} = \frac{15}{30} = \frac{1}{2}$

After heat developed
The ratio across 60 and 120 Ω resistor.


$$\frac{\frac{I^2 R_1}{T}}{\frac{I^2 R_2}{T}} = \frac{I^2 120 \times K}{I^2 60 \times K} = \frac{(2I)^2 \times 60}{I^2 \times 120} = \frac{24 I^2}{120 I^2} = 2 : 1$$

$$V = 3.00 \text{ volt}$$

$$\gamma = 1\Omega$$

$$l = 10 \text{ cm}$$

$$R = 5 \text{ ohm}$$

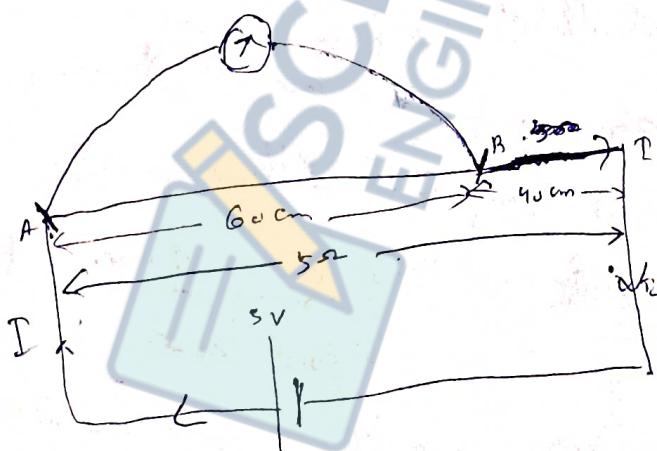

$$\gamma = 1\Omega$$

$$\text{Total resistance} = 5\Omega + \gamma = 5\Omega + 1\Omega = 6\Omega$$

$$\text{Potential of the battery} = 3 \text{ V}$$

$$\text{Current flowing} = \frac{V}{R} = \frac{3 \text{ V}}{6\Omega} = \frac{1}{2} \text{ Amp.}$$

$$200 \text{ cm wire has resistance } 5 \Omega$$

$$1 \text{ " " " " } \frac{5}{200} \Omega$$

$$60 \text{ cm " " " " } = \frac{5}{200} \times 60 = 0.75 \Omega$$

Voltmeter reading $V_A - V_B = I \times 1.5$

$$= \frac{1}{2} \times 0.75 \times 3 \Omega$$

$$= 1.5 \text{ volt}$$

~~9V Voltmeter has resistance 150 Ω.~~

then 150Ω and 3Ω are connected in ~~parallel~~ series

$$R_S = \frac{150 + 3}{153} = \frac{153}{153} = 1 \Omega$$

The resistance of wire 5Ω is continued as 3Ω in parallel, 2Ω in series.

$$R_S = 1 \Omega \quad \frac{450 + 1 + 2}{153} = \frac{453}{153} = 3 \Omega$$

$$I = \frac{V}{R} = \frac{9.09}{153} = \frac{9.09}{153} = 0.06 \text{ A}$$

$$= 0.06 \times 153 = 9.18 \text{ A}$$

$$V_A - V_B = I \times R_p$$

$$= \frac{51}{101} \times \frac{150 \times 3}{153} = 1.485 \text{ volt}$$

Current density (\vec{J})

It is a vector quantity whose magnitude is equal to the current per unit area or cross-section.

$$\therefore |\vec{J}| = \frac{I}{A}$$

The direction of \vec{J} is along the outward drawn normal.

$$\therefore J = \frac{n A e^2 \tau E}{m} = \frac{n e^2 \tau E}{m}$$

or
$$\boxed{\vec{J} = \sigma \vec{E}}$$

Derivation of Ohm's law from the relation

$$J = \sigma E$$

From the defn of J , we know that

$$J = \frac{I}{A} \quad \text{and} \quad E = \frac{V}{l}$$

$$\therefore J = \sigma E \quad \text{becomes} \quad \frac{I}{A} = \frac{1}{\rho l} \cdot \frac{V}{l}$$

$$\text{or} \quad V = \frac{\rho l}{A} I = RI$$

This is Ohm's law.

Heating effect of electric current

It is experimentally found that heat is generated in the conductors when an electric current is made to flow for sometime. Joule has established three laws regarding the quantity of heat produced.

① First law

Statement : The amount of heat generated in a conductor is directly proportional to the square of the current when resistance of the wire and time of passing current are kept constant.

$$\therefore H \propto I^2, \text{ when } R \text{ and } t \text{ are kept constant.}$$

Explanation

Suppose 1 amp or current be passed for 20 minutes through a resistance wire which is dipped in a liquid taken in a Calorimeter. The amount of heat generated be H_1 cal.

$$\therefore H_1 \propto (I)^2$$

Now the resistance of the rheostat be decreased so that the current will be increased to 2 amp. Let this current be allowed to flow for 20 minutes and heat generated by be H_2 cal.

$$\text{Then } H_2 \propto (I)^2$$

$$\text{Hence } \frac{H_1}{H_2} = \frac{1}{4} = 0.25 \text{ (expected)}$$

In actual experiments, there may be loss of heat due to radiation. If $\frac{H_1}{H_2} \approx 0.25$

be obtained then the first law will be verified.

(2)

Second Law

Statement : The amount of heat generated in a conductor is directly proportional to the resistance of the wire when the

amount or heat produced depends upon current and time or passing. Current are kept constants.

$\therefore H \propto R$, when I and t are kept constants.

Explanation:

Suppose 1 amp of current be produced in a circuit having a battery, key, rheostat, Ammeter and a resistance wire of length l (say). By calorimeter device the amount of heat produced is found to be H_1 cal in 20 minute.

$\therefore H_1 \propto R$. To maintain the heat produced in the wire be made of the same material and diameter.

Now, the length of the wire be made with no change in the and material. The resistance of the rheostat be decreased to maintain the current at 1 amp. The amount of heat produced in 20 min be H_2 cal found by calorimeter device.

$$\therefore H_2 \propto I^2 R$$

$$\text{Thus } \frac{H_1}{H_2} = \frac{1}{2} = 0.5 \text{ (expected)}$$

In practice, if $\frac{H_1}{H_2} \approx 0.5$ be obtained,

Then the second law will be verified.

③ → Third law

Statement: The amount of heat generated in a conductor is directly proportional to the time or passing current when the amount of current and resistance of the wires are kept constant.

Explanation: Hold it, when I and R are kept constant.

Explanation: Suppose 1 Amp of current be produced in a circuit for 20 minutes having a battery, key, & resistor, Ammeter and a resistance wire which is dipped in a liquid taken in a Calorimeter. By Calorimeter device, the

Amount of heat produced is H_1 Cal in 20 min.

∴ $H_1 \propto t$

Now, the time taken is t_0 minutes.

The amount of heat produced in t_0 min be H_2 Cal found by Calorimetric device.

$$H_2 \propto 2t$$

Thus $\frac{H_1}{H_2} = \frac{t_1}{t_2} = \frac{1}{2}$ (Lecture)

In practice, if $\frac{H_1}{H_2} \approx 0.5$ be obtained then the third law will be verified.

Combining these variations we have

$$H \propto I^2 R t \quad \text{when all the quantities vary.}$$

$\Rightarrow H = K I^2 R t$ where K is a constant found to be equal to the reciprocal of the mechanical equivalent of heat.


$$= \frac{1}{J} = \frac{1}{4.2 \text{ Joule/cal}}$$

$$\therefore H = \frac{I^2 R t}{J} \text{ Cal}$$

Experimental determination of 'J' in the laboratory by Joule's Calorimeter

A simple series circuit is prepared with a battery, key, Ammeter, & heater and a resistance wire. By changing the

Resistance of the rheostat, a desired current can be produced. A Voltmeter can be placed across the resistance wire. From the voltmeter and ammeter reading resistance of the wire can be found out ($V = RI$). The wire is dipped in a Kerosene or water taken in a Calorimeter. Stirring is done to have uniform mixing. Initial and final temperatures are found out after a specified time for which the current is passed.

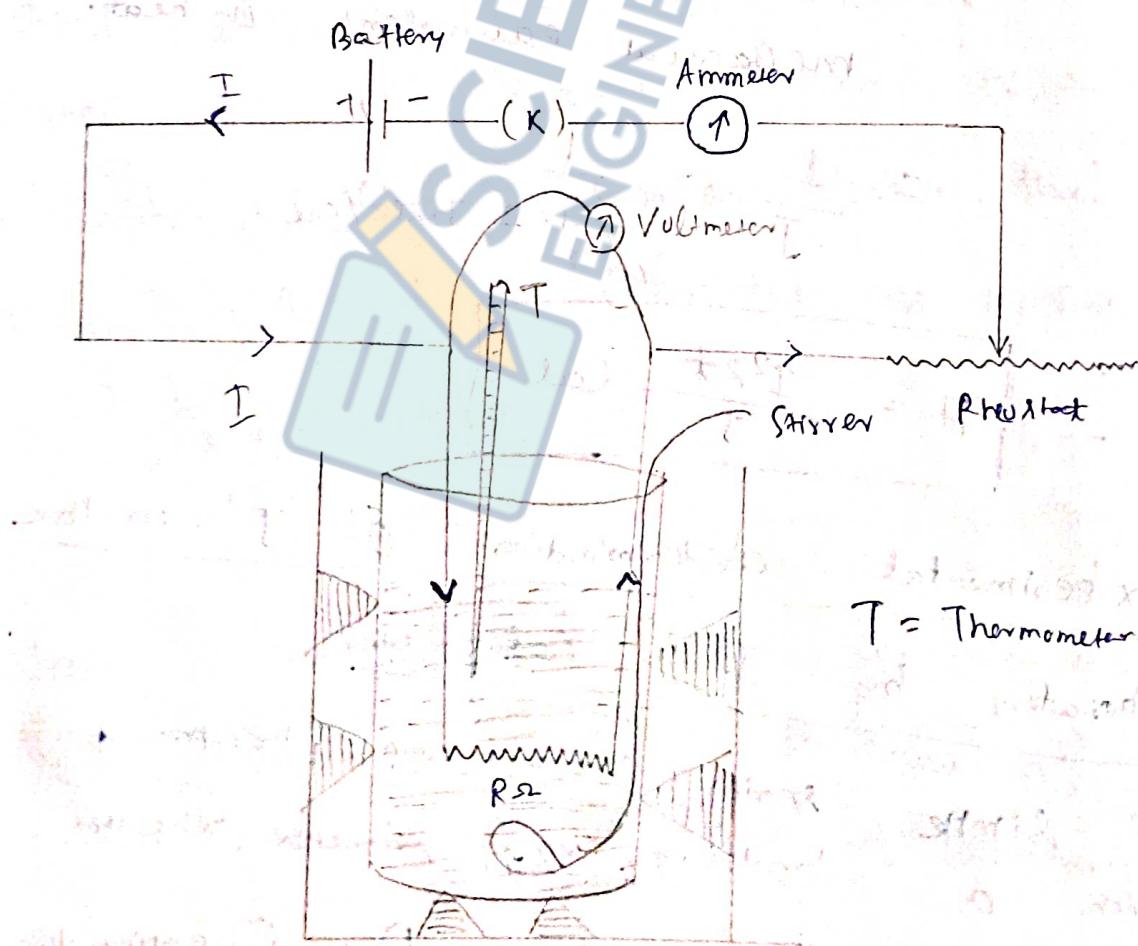

Calculation

Heat lost by electric wire

= Heat gained by the Calorimeter, stirrer
and the liquid

$$\frac{I^2 R t}{J} = m_1 s_1 \Delta \theta + (m_2 - m_1) s_2 \Delta \theta$$

Where m_1 = Mass of the empty Calorimeter
and stirrer in gms.

m_2 = Mass of the Calorimeter + stirrer
+ liquid in gms.

$\therefore m_2 - m_1$ = Mass of the liquid taken
in gms.

s_1 = Specific heat of the Calorimetric
substance (Copper)

s_2 = Specific heat of the liquid

$\Delta \theta$ = Rise of temp in $^{\circ}\text{C}$ or K

$$\frac{I^2 R t}{J} = [m_1 s_1 + (m_2 - m_1) s_2] \Delta \theta$$

$$\Rightarrow J = \frac{I^2 R t}{[m_1 s_1 + (m_2 - m_1) s_2] \Delta \theta} \text{ Joule / Cal.}$$


Precautions:

1. High Current. Should not be passed because this will make large quantity of heat loss in the process of radiation.
2. The current should be passed for that amount of time till the temp rises by 10°C to 20°C .
3. Radiation Correction procedure should be followed to have correct temp of mixing.
4. Stirring must be constant continuously done to have uniform temp throughout.

Electrical work energy and power

Let's have a conductor of resistance

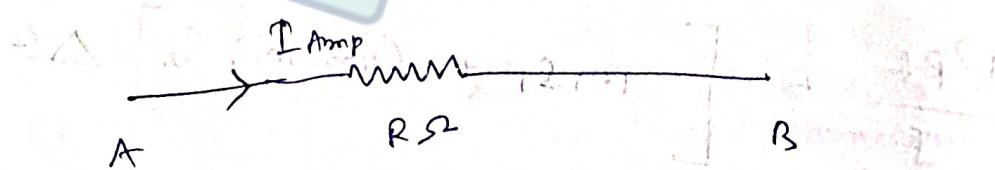R ohm, through which a current I Amp flowing for t sec.



The amount of charge flowing through it is given by $q = I t$.

The amount of workdone to blow a unit of charge through the wire

$$W = q \cdot \Delta V = I t \cdot R I = I^2 R t \text{ Joule}$$

Thus, Electrical Workdone = $I^2 R t$ Joule.

Electrical Power = $\frac{\text{Electrical Workdone}}{\text{Time taken}}$

$$= \frac{I^2 R t}{t}$$

$$= I^2 R \text{ Watt} = IR, I = V/I \text{ Watt}$$

$$= V \cdot \frac{V}{R} = \frac{V^2}{R} \text{ Watt.}$$

The practical unit by which electrical work or energy is measured is called

KWh (Kilo watt hour)

$$1 \text{ KWh} = \frac{10^3 \text{ Joule}}{3600 \text{ sec}}$$

$$= 36 \times 10^5 \text{ Joule.}$$

Bigger units like mega watt hour

are also used.

$$1 \text{ MWh} = 10^6 \frac{\text{Joule}}{\text{sec}} \times 3600 \text{ sec}$$

$$= 36 \times 10^9 \text{ Joule.}$$

Smaller units like watt-hour are also used.

$$1 \text{ Wh} = \frac{1 \text{ Joule}}{3600 \text{ sec}} \times 3600 \text{ sec} = 360 \text{ Joules.}$$

4. An electric kettle has two thermal coils - with current in one coil, water boils in 6 minutes and with current in the other coil it boils in 8 minutes.

When both coils are joined in

(a) Series (b) Parallel,

How long will it take to boil?

(Ans: 3.428 minute, 14 minute)

(Thinks: $I + \frac{1}{R_1} = I + \frac{1}{R_2} = H_s = I + P = \text{Constant}$, $I = \text{constant}$)

Ans: Let R_1 and R_2 be the resistances of the two coils.

Amount of heat required to boil a given amount of water remains the same

$$H_1 = H_2$$

$$\frac{\cancel{J}^2 R_1 t_1}{\cancel{J}} = \cancel{J}^2 R_2 t_2$$

$$\Rightarrow R_1 \times 6 \text{ min} = R_2 \times 8 \text{ min}$$

$$\Rightarrow 3R_1 = 4R_2 \quad \text{(i)}$$

When the two wires are joined in the series let the time taken to boil the water in the kettle be t_s minute

$$H_1 = H_s \text{ gives } \mathbb{P}$$

$$\frac{\cancel{J}^2 R_1 t_1}{\cancel{J}} = \cancel{J}^2 R_s \cdot t_s$$

$$\Rightarrow R_1 \times 6 \text{ min} = (R_1 + R_2) t_s \text{ min}$$

$$\Rightarrow 6R_1 = (R_1 + 3R_1) t_s$$

$$= \frac{8R_1}{4} t_s$$

$$\Rightarrow 8t_s = \frac{6R_1 + 4}{7} = \frac{2y}{7} = 3.428 \text{ minute}$$

When the wires are joined in parallel let the time taken to boil the water in the kettle be t_p minute

$$H_1 = H_p \text{ gives } \mathbb{P}$$

$$\frac{R_1 \cdot 6 \text{ min}}{J} = \frac{R_p + R_{mix}}{J}$$

$$\Rightarrow R_1 \cdot 6 \text{ min} = \left(\frac{R_1 R_2}{R_1 + R_2} \right) t_p$$

$$\Rightarrow R_1 \cdot 6 \text{ min} = \left(\frac{R_1 \cdot 3R_1}{R_1 + 3R_1} \right) t_p$$

$$= \frac{3R_1^2}{4} \times \frac{4}{771} t_p$$

$$\Rightarrow t_p = \frac{2}{3} \times 7 = 14 \text{ minutes}$$

~~Solve Error not
written correctly
Power $\propto \frac{1}{V^2}$~~

Q. Two lamps marked "60W, 120V"

and "40W, 120V" are joined in series across a 120 volt line.

What power is consumed in each lamp?

Ans: (240Ω, 360Ω, 9.6 watt, 14.4 watt)

6. If equal P.D resistors are connected in series, when a certain P.D is applied across the combination, the total power consumed is 10W. What power would be consumed if the three resistors were connected in parallel across the same P.D (Ans: 9W)

Problems on Chemical Effect of Current

✓ Prove that $\frac{Z_1}{Z_2} = \frac{E_1}{E_2}$

where $Z = E \cdot C \cdot E$

$$E = C \cdot E$$

Ans: Let's have two electrolytes placed in series in a circuit having d.c voltage.

If the masses of the ions deposited at the cathode be m_1 and m_2 respectively,

then of Faraday's first law gives

$$\frac{m_1}{m_2} = \frac{Z_1 I t}{Z_2 I t} = \frac{Z_1}{Z_2} \quad \text{(i)}$$

From Faraday's second law, we know that

$$t \times Z_1 \times \frac{m_1}{m_2} = \frac{E_1}{E_2} \quad \text{(ii)}$$

From Eqs (i) and (ii), we get

$$\frac{Z_1}{Z_2} = \frac{E_1}{E_2} \quad \text{(proved)}$$

Q. A spoon having an area 20 square mm. is to be both coated with Ag to a thickness of 0.01 mm.

Q2 A current of 0.15 Amp is used, calculate the time for which it must flow? (Ans. 12.52 sec)

$$\text{Eqn} \quad E = C E \quad \text{or} \quad \text{silver} = 0.00111 \frac{\text{gm}}{\text{cm}^2 \text{sec}}$$

~~SCIENCE AND NOTES~~

$$\text{or} \quad \text{silver} = 10.5 \text{ cm/sec.}$$

Ans:

$$\text{Area} = 20 \text{ mm}^2 = 20 \times 10^{-2} \text{ cm}^2$$

$$\Rightarrow \text{Thickness} = 0.01 \times 10^{-1} = 0.001 \text{ cm.}$$

$$\text{Volume} = 20 \times 10^{-2} \times 10^{-3} = 20 \times 10^{-5} \text{ cm}^3$$

$$\text{mass} = \text{Volume} \times t = 20 \times 10^{-5} \times 10.5 = 21 \times 10^{-4} \text{ gm}$$

we know from Faraday's Law

$$m = Z I t$$

$$\Rightarrow 21 \times 10^{-4} = 0.001118 \times 0.15 \times t$$

$$\Rightarrow t = \frac{21 \times 10^{-4}}{0.15 \times 0.001118}$$

$$= \frac{21 \times 10^{-4} \times 10^2 \times 10^3}{15 \times 1118}$$

$$= \frac{210000}{15 \times 1118}$$


$$= 12.52$$

3) Three voltmeters in parallel are connected to the ends of a battery with resistance. After 30 minutes the depolarites are 0.763, 0.742 and 0.785 gm. Find the strength of the current drawn from the battery.

(Ans: 3.867 Amperes)

$$E \cdot C \text{ or } C = 0.000329 \text{ gm Coulombs}$$

Ans:

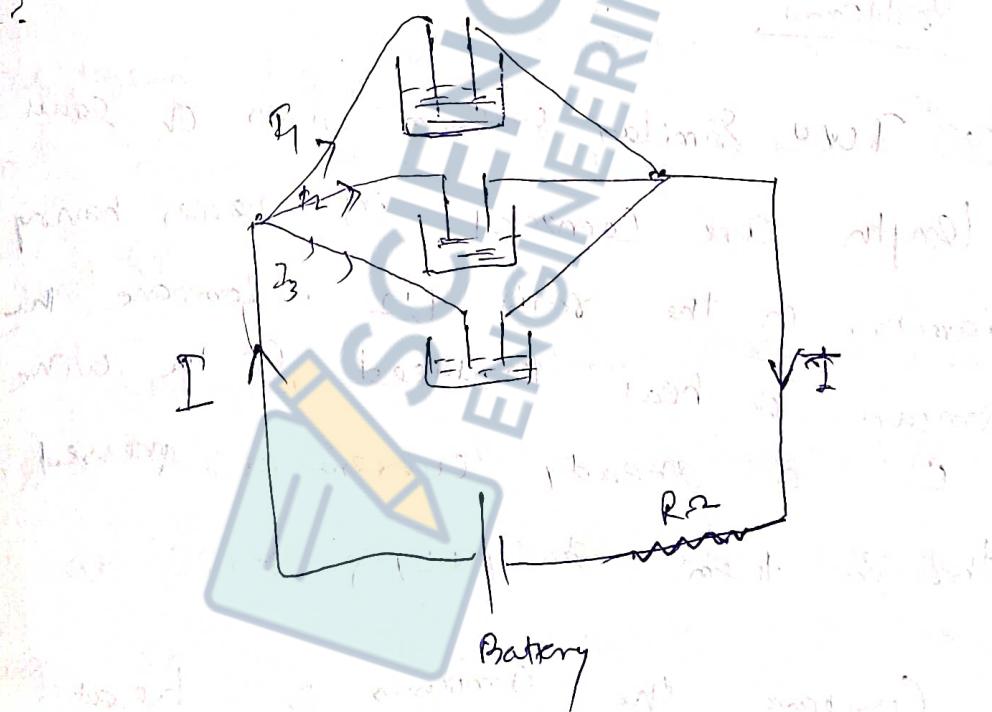

From Faraday's law

$$m_1 = Z I_1 t$$

$$m_2 = Z I_2 t$$

$$m_3 = Z I_3 t$$

$$m_1 + m_2 + m_3 = Z t (I_1 + I_2 + I_3) = Z I t$$

$$0.763 + 0.742 + 0.785 = 0.000329 \times \frac{30}{60} \times I$$

$$2) \frac{2.290}{1000329 \times 30 \times 10^6} = I$$

$$I = \frac{2.290 \times 10^{-6}}{329 \times 30 \times 3760^6}$$

$$= \frac{2290 \times 10^{-12}}{9.87 \times 10^6}$$

$$= \underline{\underline{22.900^9}}$$

$$= 3.8269 \text{ A.U.}$$

Problems

1. Two similar uniform wires of equal length are connected in series having diameters in the ratio 1:2. Compare the amount of heat produced in the wire if a steady current is passed through them. Ans (4:1)

2. Compare the amounts of heat developed in the four arms of a balanced Wheatstone bridge when the resistances of the arms are 1Ω , 6Ω , 3Ω , 3Ω .
Ans (30 : 3 : 10 : 1)

3/ A current of 5 amp flows through a wires or resistance 1Ω for 2 min. If the heat produced is exclusively supplied to 100 gms of water, through how many degrees will the temp be raised. Ans: (71.4°C)

4/ An electric copper kettle weighing 1000 gms holds 1800 gms of water.

If a current of 5 amp at 200 Volts passes through a kettle. Calculate the time taken by water to reach boiling point from 20°C ? (Ans: 10 min 38.4 sec)
 $\text{Sp. gr. of water} = 0.1$

5. Calculate the time required to boil the ϕ a litre of water which is at 25.4°C , the available energy being at the rate of 1 H.P (75000 cal/min).

6. Calculate the amount of heat produced in 5 min in 20 watt lamp.

Ans: 1428.57 cal.

✓ 7. A lamp with a carbon filament works at 2.5 watt under a voltage of 200 volts. What is the resistance of the lamp? [Ans: 160 ohms]

✓ 8. An electrode is red when hot. It has a rated resistance of 80 ohms and it is used on a 200-volt circuit. What will be the current or current for 2 hours on energy consumption per kWh.

✓ 9. Two points at a given difference of potential are joined by n wires of equal resistances. Prove that the heat produced when both the wires are joined in parallel = n^2 times the heat generated when they are arranged in series.

Ans. $K \rightarrow 654 \text{ kg}^{-1} \text{ J}^{-1}$

✓ 10. An electric bulb is marked 220 volt and 60W. What does it mean?

If such a bulb be made to work

for 5 hrs a day during the whole month of September, what should be the bill if the charge is 16 units per unit
(Ans: 3 rupees)

A university hotel has 360 lamps installed. The lamps consume 50 watts each and they are lighted for 6 hrs daily for 9 months. The voltage parallel or supply is 220 and the current cost is $\frac{3}{4} = (318 \text{ pps per Kwh})$

Find the Cost of the current as well as the max current may.

(Ans: 10935 RS, 81.81 Ams)

Q. An electric kettle when water equivalent in 100 gms contains 1000 gms of water at 15°C . If the kettle takes 4 Amps at 230 Volts.


Find

(i) The time required to boil water

assuming that heat of hear generated is 10^6 J

(b) Rate of generation of heat in ohm
 $(A = 7 \text{ mm}^2, \rho = 54 \text{ sec}, 21 \text{a. Caffee})$

Ans:

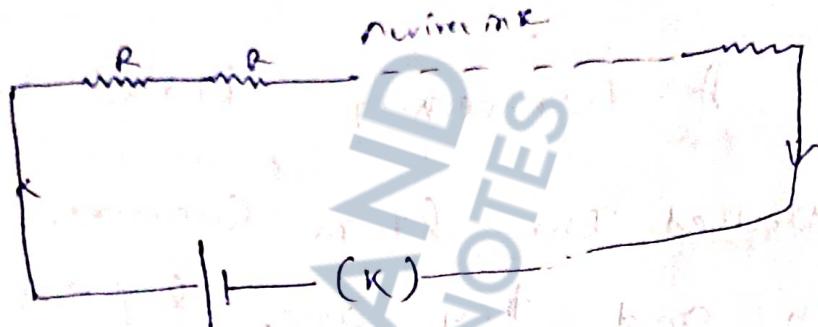

Since n wires are connected in series,


$$R_s = R + R + \dots + R + R_n$$

$$\text{Here } I = \frac{V}{R_s} = \frac{V}{nR}$$

$$\text{Heat produced in 1 wire } \frac{I^2 R t}{J}$$

$$\text{Heat produced in } n \text{ wires } H_s = \frac{(V)^2}{n \frac{\rho A \pi R}{J}} \cdot R \cdot t$$

$$= \frac{V^2 +}{n J \cdot R}$$

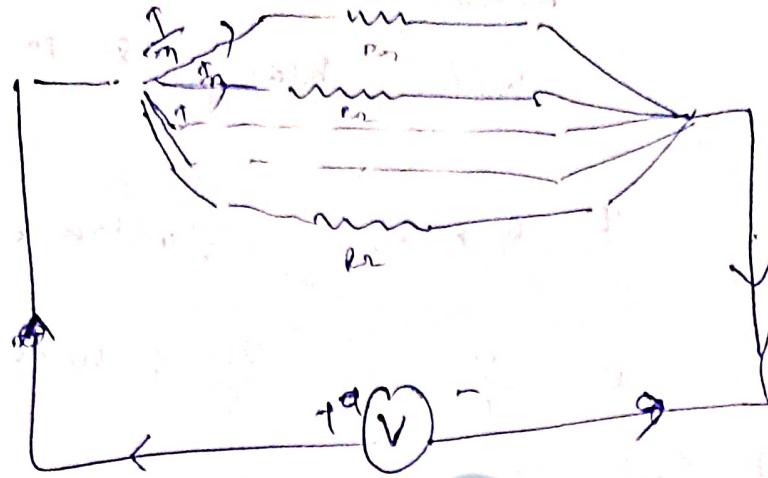

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{R_3}$$

$$= \frac{n}{R}$$

$$\Rightarrow R_p = \frac{R}{n}, \text{ and } I_m = \frac{V}{\frac{R}{n}} = \frac{Vn}{R}$$

Heat produced in 1 mm

$$= \frac{(I_m)^2 R}{n} = \frac{V^2 n^2 \cdot R}{R^2 n} = \frac{V^2 n^2}{R} J$$

Heat produced in n wires

$$(H_p) = \frac{V^2 n^2}{R J} \times n$$

$$= n V^2 \frac{J}{R J}$$

$$\frac{H_p}{I_s} = \frac{n V^2 J}{R J} \times \frac{n J R}{J^2 K}$$

$$\Rightarrow H_p = n^2 I_s^2 = n^2 I_s^2 C_p (\text{Power})$$

4. Kettle has mass = 1000 gm.
Water holder = 1800 gm.

$$I = 5 \text{ Amper}, \quad \text{Voltage} = 200 \text{ volt}$$

$$R = \frac{V}{I} = \frac{200}{5} = 40 \Omega$$

$$\text{Heat produced, } \frac{I^2 R t}{J} = \frac{25 \times 40 \times t}{4 \cdot 2} \rightarrow (1)$$

(Heat lost by kettle + water)

$$\begin{aligned} Q &= m_1 s_1 \Delta \theta_1 + m_2 s_2 \Delta \theta \\ &= 1000 \times 1 \times (100 - 20) + 1800 \times 1 \times (100 - 20) \\ &= 100 \times 80 + 1800 \times 80 \\ &= 800 (1900) \\ &= 152000 \end{aligned}$$

$$\therefore \frac{25 \times 40 \times t}{4 \cdot 2} = 152,000$$


$$\therefore t = \frac{152,000 \times 4 \cdot 2}{25 \times 40}$$

$$= 638.4 \text{ sec}$$

$$= 10.64 \text{ min}$$

$$= 10 \text{ min} \cdot 64 \times 60$$
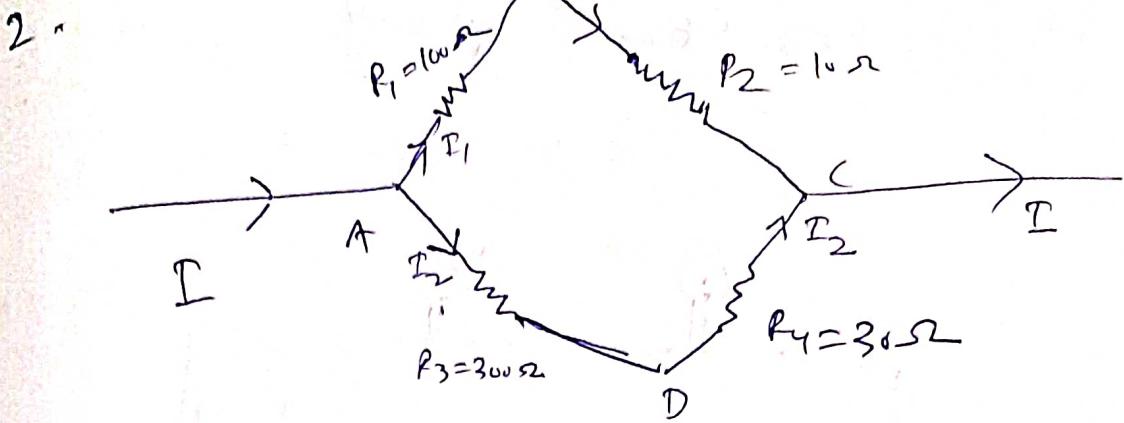
$$= 10 \text{ min} \cdot 38.4 \text{ sec}$$



$$\text{Now } V_A - V_C = .I_1 \times (10 + 10) = I_2 (300 + 30)$$

$$\Rightarrow 110 I_1 = 330 I_2$$

$$\Rightarrow I_1 = 3 I_2$$

$$I_1 : I_2 : I_3 : I_4$$

$$= I_1^2 \cdot \frac{10\pi}{J} : I_1^2 \frac{10\pi}{J} : I_2^2 \frac{300\pi}{J} : I_2^2 \frac{30\pi}{J}$$

$$= (3I_2)^2 \cdot 10\pi : (3I_2)^2 10 : I_2^2 300 : I_2^2 30$$

$$= 9I_2^2 \cdot 10\pi : 9I_2^2 10 : 300 : 30$$

$$= 90\pi : 30 : 30$$

$$= 30 : 30 : 1$$

Point to exercise 5


Two lamps marked '60w', '120v'
'40w', '120v'

$$P_1 = 60w, V = V_1 + V_2 = 120V \text{ or } 60V$$

$$P_2 = 40w$$

Ans.

We know that $P = \frac{V^2}{R}$

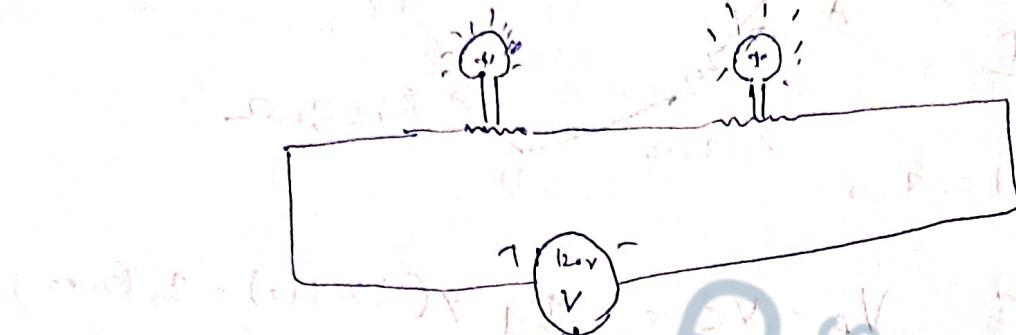

For first lamp $60W = \frac{(120)^2}{R}$

$$\Rightarrow R = \frac{120^2 \times 120}{60} = 240\Omega$$

For the second lamp $90W = \frac{(120)^2}{R}$

$$\Rightarrow R = \frac{(120)^2 \times 90}{90} = 360\Omega$$

Total

Total

Voltage = 120V \therefore Total resistance $= (360 + 240) = 600\Omega$

$$I = \frac{V}{R}$$

$$\frac{120}{600} = \frac{1}{5} \text{ Amps}$$

(i) Power consumed by first lamp


$$= P = \frac{V \cdot I}{R}$$

$$= I^2 R$$

$$= \frac{1}{25} \times 240 = 9.6 \text{ Watts.}$$

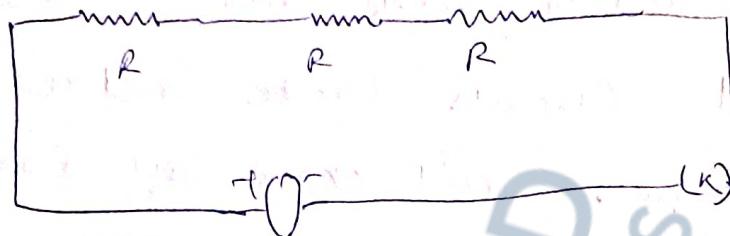(ii) Power Consumed by second lamp = ?

$$P = \frac{V^2 R}{R} = \frac{1}{25} \times 360 = 14.4 \text{ watt}$$



The resistors are connected in series.

$$R_s = \underline{\underline{3R}}$$

Power consumed = 10W.

$$P = \frac{V^2}{R_s} = \frac{V^2}{3R}$$

$$\Rightarrow \frac{V^2}{3R} = 10 \text{ W}$$

$$\Rightarrow V^2 = \underline{\underline{30R}} \text{ volt}$$

When

Connected in parallel

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{3}{R}$$

$$\therefore R_p = \frac{R}{3}$$

$$\text{Power-consumed} = \frac{V^2}{R_p} = \frac{3UR}{R/3} = \frac{3U^2 R}{R} = 90 \text{ Watt.}$$


Analysis of Multiloop Circuits

We have seen that Ohm's law is applicable to single conductors and it can be extended to simple loop circuits. Even complicated circuits can be reduced to simple circuits, and Ohm's law can be applied. But, if there are many loops in a circuit which can not be reduced to simple loop circuits, then then Ohm's law fails to give the values of currents in such circuits. Kirchhoff's 2 laws are very helpful in solving such multiloop circuits.

1. Kirchhoff's 1st Law

The algebraic sum of currents meeting at a point is zero.

$$\sum I = \text{Zero}$$

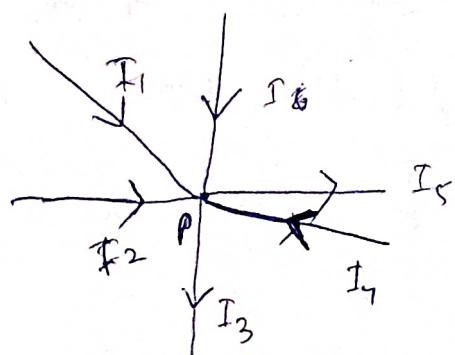

(4th)

By Convention Currents coming towards the junction point are taken as +ve and currents going away from the junction point are taken as negative.

~~Expt.~~

$$\therefore I_1 + I_2 + I_6 - I_5 - I_3 + I_4 = 0$$

$$\Rightarrow I_1 + I_2 + I_6 - I_5 = I_4 + I_3$$

\Rightarrow Sum of currents coming towards the junction point

= Sum of current going away from the junction point.

\Rightarrow Charges can not be stored at any junction point.

Kirchhoff's Second law

The algebraic sum of product of current and resistance of a closed circuit is equal to the algebraic sum of electromotive forces present in that circuit.


$$\boxed{\sum RI = \sum E}$$

Illustration

By taking clockwise sense as +ve for currents and -ve otherwise. The

EMFs are also taken as +ve if they try to send Current in the clockwise direction and -ve otherwise. 3 currents I_1, I_2, I_3 have been assumed for the three branches.

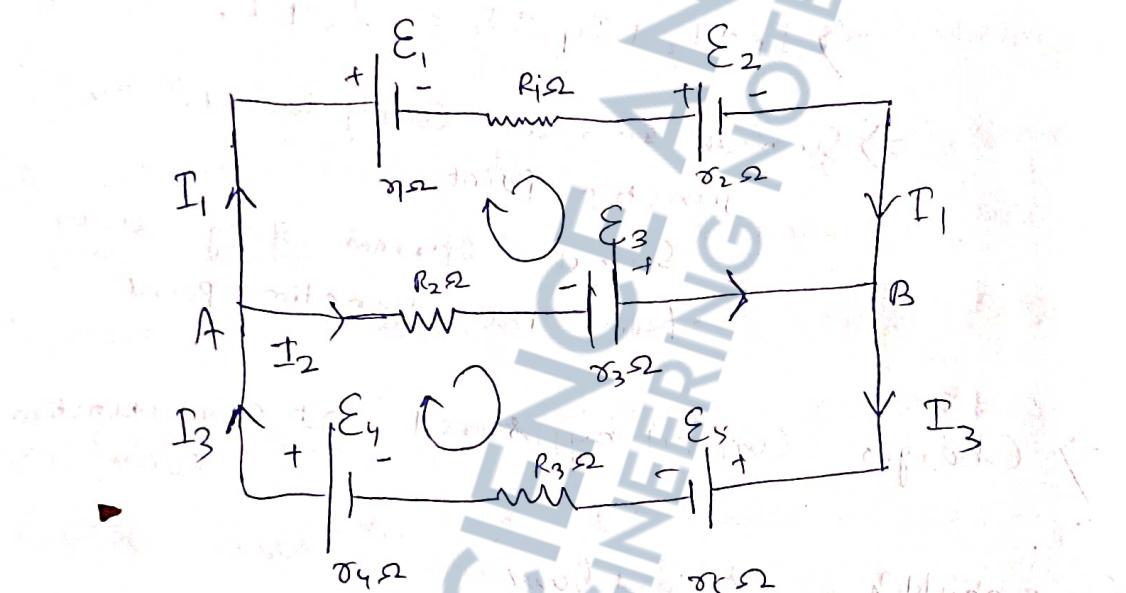Applying Kirchhoff's second law to the upper loop, we get



$$\gamma_1 I_1 + R_1 I_1 + \gamma_2 I_1 - \gamma_3 I_2 - R_2 I_2 = -E_1 - E_2 - E_3 \quad (i)$$

Applying Kirchhoff's second law to the lower loop, we get

$$R_2 I_2 + \gamma_3 I_2 + \gamma_5 I_3 + R_3 I_3 + \gamma_4 I_3 = E_3 - E_5 + E_4 \quad (ii)$$

Applying Kirchhoff's first law to the junction

point A, we get

$$I_3 - I_1 - I_2 = 0 \quad (\text{iii})$$

Solving these three eq's, we can get the values of I_1 , I_2 and I_3 .

Problem
1. Two cells of emf 1.5 and 2
volt with internal resistances 1 Ω
and 2 Ω respectively are connected in
parallel to an external resistance of
5 Ω . Calculate the current in each
branch of the net work.


(Ans: 0.029, 0.265, 0.294 Amperes)

2. Two cells of emf 1.5 and 2
volt with internal resistances 2 Ω and 1 Ω
respectively have their -ve terminals
joined by a wire of 6 Ω and +ve
terminals by a wire of 4 Ω resistance.
A third resistance of 8 Ω connects the
midpoints of these two wires. Find
the p.d. at the ends of the third wire.
(Ans \rightarrow 1.26 volt)

3. Two cells of emf E_1 and E_2 have internal resistances γ_1 and γ_2 respectively. If these cells are connected in parallel with an external resistance R so as to send a current in the same direction. Show that the current through R is given by $\frac{E_1 \gamma_2 + E_2 \gamma_1}{\gamma_1 \gamma_2 + R(\gamma_1 \gamma_2)}$

Ans

1.

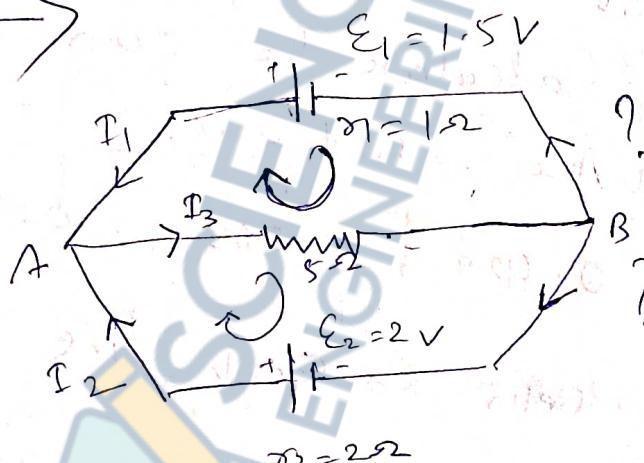

Applying

At junction A

Kirchhoff's first law

$$I_1 + I_2 - I_3 = 0 \quad (i)$$

Applying Kirchhoff's 2nd law for upper loop,

$$-I_1 \frac{1}{\gamma_1} - I_3 5 = -E_1 \quad (ii)$$

For lower loop $\Rightarrow I_1 + 5I_3 = 1.5$

$$I_3 5 + I_2 2 = E_2 \quad (iii)$$

$$5I_3 + 2I_2 = 2$$

From eqn (iii)

$$I_3 = \frac{2 - 2I_2}{5}$$

Putting this value in eqn (ii)

$$I_1 + 8 \cdot \left(\frac{2 - 2I_2}{5} \right) = 1.5$$

$$\Rightarrow I_1 + 2 - 2I_2 = 1.5$$

$$\Rightarrow I_1 - 2I_2 = -0.5$$

$$\Rightarrow I_1 = 2I_2 - 0.5$$

But $I_3 = I_1 + I_2$

~~Eqn 3~~

$$= 2I_2 - 0.5 + I_2$$

$$= 3I_2 - 0.5$$

Putting the values in eqn (i)

$$I_1 + I_2 - I_3 = 0$$

$$\Rightarrow (2I_2 - 0.5) + I_2 - (3I_2 - 0.5) = 0$$

$$\Rightarrow 2I_2 + I_2$$

OR

$$I_3 = I_1 + I_2$$

Putting this value in eqn (i)

$$I_1 + 5(I_1 + I_2) = 1.5$$

$$\Rightarrow 6I_1 + 5I_2 = 1.5 \quad \text{(iv)}$$

$$S(I_1 + I_2) - 2I_2 = 2$$

$$\Rightarrow \text{OP } 5I_1 + 7I_2 = 2 \quad \rightarrow (V)$$

$$30I_1 + 125I_2 = 74.5$$

$$\begin{array}{r} 30I_1 + 142I_2 = 12 \\ (-) \quad (-) \end{array}$$

$$-17I_2 = 74.5$$

$$\Rightarrow I_2 = \frac{74.5}{17} = \frac{45}{170} = \frac{9}{34}$$

$$= 0.2647 \text{ Amper}$$

$$6I_1 + 5\left(\frac{9}{34}\right) = 1.5$$

$$\Rightarrow 6I_1 = 1.5 - \frac{45}{34}$$

$$= \frac{51 - 45}{34} = \frac{6}{34}$$

$$= \frac{6}{34} \times \frac{1}{6} = \frac{1}{34}$$

$$\Rightarrow I_1 = \frac{1}{34} = 0.029 \text{ Amper}$$

~~$$5I_3 + 2I_2 = 2$$~~


$$\Rightarrow 5I_3 + 2\left(\frac{9}{34}\right) = 2$$

$$21 \times I_3 = 12 - \frac{9}{17} = \frac{25}{17}$$

$$21 I_3 = \frac{5}{17} = + 0.294$$

$$I_3 = 0.294, I_2 = 0.294, I_1 = 0.294$$

2.

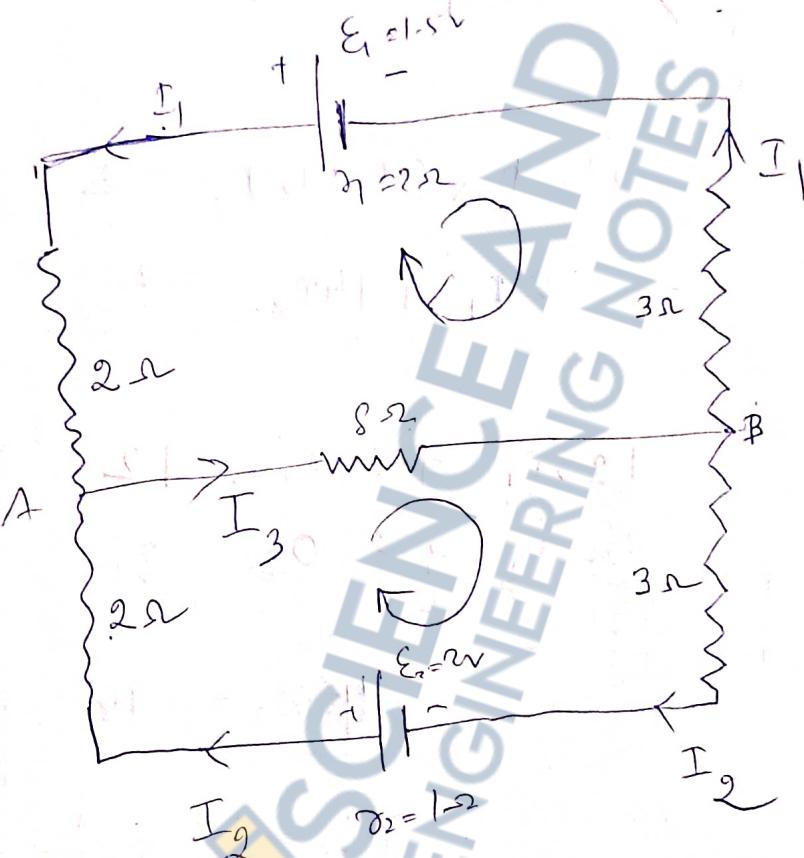

Applying

Kirchhoff's

first law at A

$$I_1 + I_2 - I_3 = 0 \quad (i)$$

Applying Kirchhoff's 2nd law for upper loop.

~~$$-2I_1 - 2I_1 - 3I_1 - 8I_3 = 12 - 1.5 \quad (ii)$$~~

~~$$-7I_1 + 8I_3 = 1.5 \quad (iii)$$~~

for lower loop

$$I_3 8 + I_3 3 + I_2 1 + I_2 2 = 8.2$$

$$\Rightarrow 6I_2 + 8I_3 = 2 \quad (iv)$$

$$I_1 + I_2 = I_3 \quad \text{from eqn (i)}$$

Putting this value in eqn (1)

$$7I_1 + 8(I_1 + I_2) = 1.5$$

$$\Rightarrow 15I_1 + 8I_2 = 1.5 \quad \text{--- (a)}$$

$$6I_2 + 8(I_1 + I_2) = 2$$

$$\Rightarrow 8I_1 + 14I_2 = 2 \quad \text{--- (b)}$$

$$120I_1 + 64I_2 = 12$$

$$120I_1 + 210I_2 = 30$$

$\frac{210}{64} I_2$

$$\underline{\underline{146I_2 = 18}}$$

$$\therefore I_2 = \frac{18}{146} = \frac{9}{73}$$

$$\Rightarrow I_1$$

$$6I_2 + 8I_3 = 2$$

$$\Rightarrow 6 \cdot \frac{9}{73} + 8I_3 = 2$$

$$\Rightarrow 8I_3 = 2 - \frac{54}{73} = \frac{146 - 54}{73}$$

$$= \frac{92}{73}$$

$$\Rightarrow I_3 = \frac{\frac{23}{46}}{\frac{92}{73}} \times \frac{1}{\frac{8-9}{2-9}} = \frac{23}{146}$$

Chemical effect of electric current

Electrolysis : The process of breaking a compound in soln into its constituents by passing a direct current through the soln is called electrolysis.

Electrolyte :

The compound in soln through which the current is passed is called electrolyte.

Electrode : The two conducting metals placed in the soln at a separation by which current is passed from an external circuit are called electrodes. That electrode which is connected to the +ve terminal or the battery is called anode. And the other electrode which is connected to the -ve terminal of the battery is called cathode.

Voltmeter : If it includes the electrolyte and the electrodes.

Ex:-

- (1) In a silver voltameter, there are two silver electrodes dipped in a soln of AgNO_3 . When a battery is connected to these two electrodes, AgNO_3 breaks up into

Ag^+ and NO_3^- . The silver ions (Ag^+) moves towards the Cathode and gets deposited there as the NO_3^- ion moves towards the anode and brings out a silver atom and again AgNO_3 is formed with a -ve charge given to the anode. As a result, the anode becomes lighter and the cathode becomes heavier with the passage of time.

Ex: ②

In a Copper Voltameter there are

two Copper electrodes dipped in a soln of CuSO_4 .



The Cu^{2+} ion moves towards the Cathode

and SO_4^{2-} moves towards the anode. The conc of CuSO_4 soln remains unchanged.

Although the Cathode becomes heavier and the anode becomes lighter.

Faraday's laws on Electrolysis

Faraday has given two laws regarding the mass of ions deposited at the cathode due to passage of current through the electrolyte.

$$m \propto Q$$

or

$$m = ZQ$$

Where Z is called constant for a particular element or electrolyte.

Called electro chemical equivalent (E.C.E)

~~defn~~

$$\text{But } I = \frac{Q}{t}$$

$$\therefore Q = It$$

$$\text{Thus } m = ZIt$$

$$\text{At } 1 \text{ sec. } Z = m \text{ when } I = \text{Amp}$$

Defn of Z

The electro chemical equivalent may numerical defined as the amount of substance depurated when 1 amp current passed for 1 sec through the electrolyte.

Two laws can be stated

(a) $m \propto I$, when time is kept constant.

Statement: The mass of ions deposited at an electrode is directly proportional to the amount of current passing through the electrolyte when time of passing current is kept constant.

Explanation

By adjusting the resistance of the rheostat, let us have a current of 1 amp in the circuit which is passed for 30 min through some electrolyte. The mass of man at the cathode gives the mass of ions deposited. (m_1 gm, say)

The current be changed to 2 amp and again it should be passed for 3 min. The mass of ions deposited = m_2 gm (say)

$$\text{Thus } \frac{m_1}{m_2} = \frac{1}{2} \text{ (expected)}$$

(b) m_2 & when Current (I) is kept constant.

Statement

The mass of ions deposited at an electrode is directly proportional to the time or passing current when current is kept constant.

Explanation


Let us pass 1 amp of current for 30 min. through an electrolyte and the mass of

ions deposited at the electrode be m_1 gm. Keeping current constant at 1 amp let us pass it through the electrolyte for 60 min and the mass deposited at the cathode be m_3 gm.

$$\therefore \frac{m_1}{m_3} = \frac{1}{2} \text{ (expected)}$$

The value of Z at Ag = 0.001118 gm/Coulomb.

Z for Cu = 0.000329 gm/Coulomb.

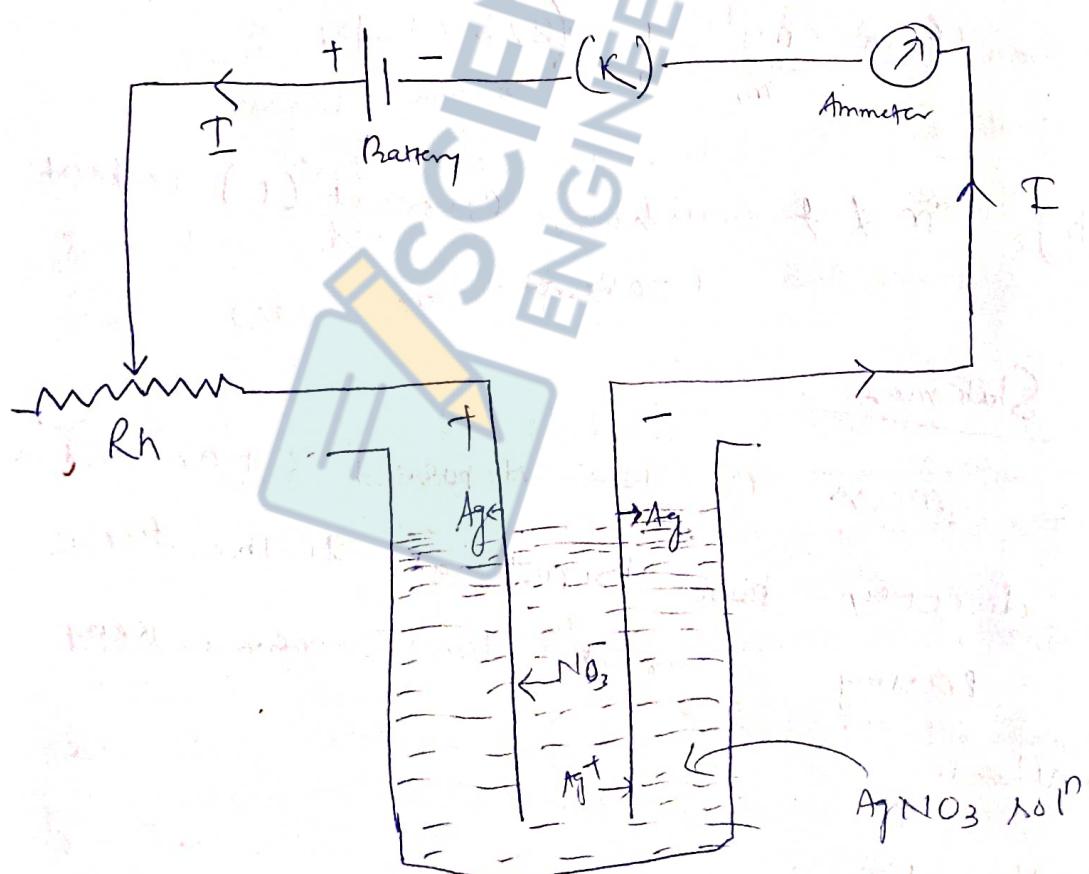

The above circuit can be used to verify Faraday's first law of electrolysis.

② Second law

Statement : If the same amount of current be passed through two different electrolytes placed in series, then the mass of ions deposited at different electrodes are proportional to their respective chemical equivalents.

$$\text{Chemical equivalent} = E(\text{say}) = \frac{\text{Atomic weight}}{\text{Valency}}$$

E = Equivalent weight.

$\therefore m_1 \propto E_1$ between m_1 and E_1 .

and $m_2 \propto E_2$


$$\frac{m_1}{m_2} = \frac{E_1}{E_2}$$

Where m_1 = Mass of the ions deposited at the Cathode of the 1st electrolyte.

m_2 = Mass of the ions deposited at the Cathode of 2nd electrolyte.

Experimental Verification of the 2nd Law

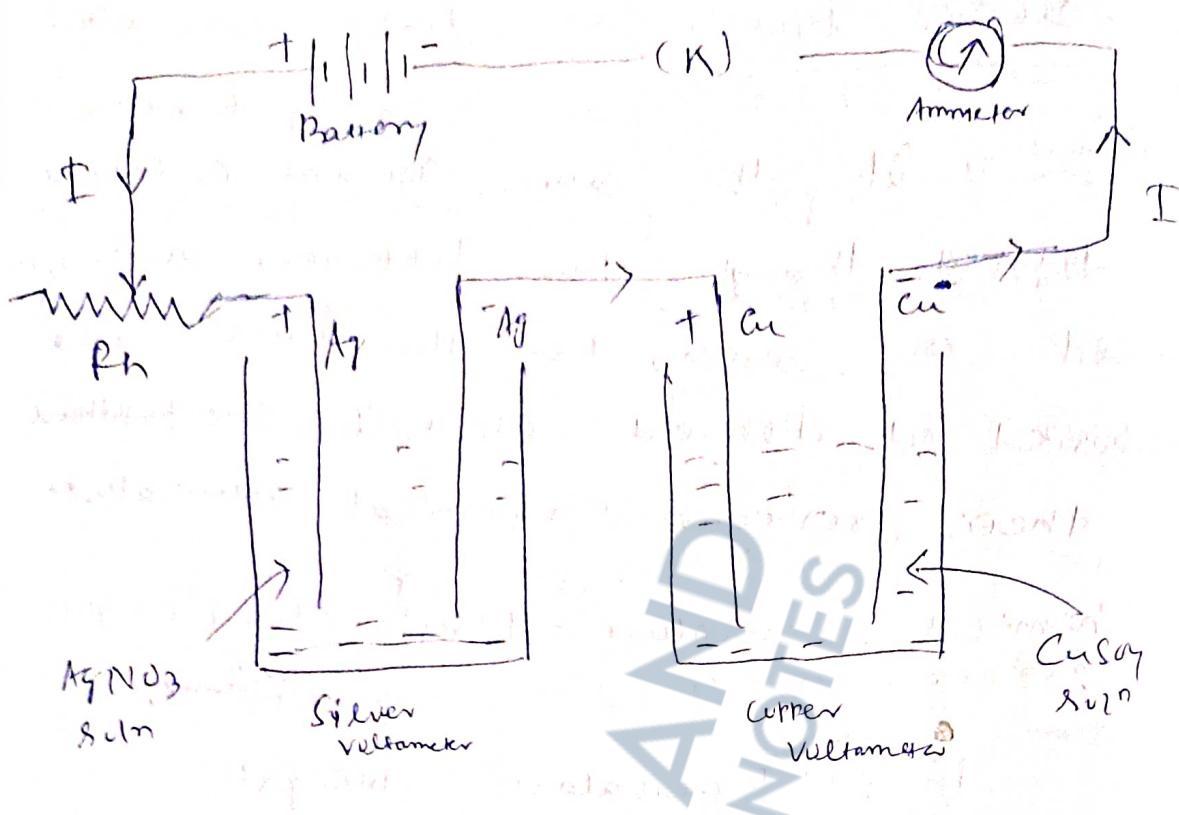Suppose 1 Amp of current be passed for 1 hour and the masses deposited at the Cathodes of the two Voltmeter be m_1 and m_2 .



$$E_1 \text{ for silver} = \frac{108}{1} = 108$$

$$E_2 \text{ for Cu} = \frac{63.5}{2} = 31.75$$

Thus $\frac{m_1}{m_2} = \frac{108}{31.75}$ (Expected)

If the deposited silver at the cathode be 3.4 times at the man or Cather deposited at its Cathode, then the 2nd law of Faraday is Verified.

Faraday Unit or Charge

It is that amount or charge which can deposit 1 gm equivalent of any substance.

at the Cathode. The value of 1 Faraday is 96,500 Coulomb, which is calculated from Faraday's 1st law.

Ex: 1: Applying Faraday's 1st law

$m = ZQ$ for AgNO_3 soln, we have

$$107.87 \text{ gm} = 0.001118 \text{ gm/Coulomb} \times Q$$

$$\Rightarrow Q = \frac{107.87}{0.001118} = \underline{96484.79428} \text{ Coul.}$$

Ex: 2: Applying Faraday's 1st law

$m = ZQ$ for CuSO_4 soln, we have

$$31.77 = 0.000329 \text{ gm/Coul} \times Q$$

$$\Rightarrow Q = \frac{31.77}{0.000329} = \underline{96565.34954} \text{ Coul}$$


Application of electrolysm

1. Electroplating

The process of depositing a layer of some ^{superior} metals such as gold, silver, nickel etc on an object by electrolysm is called electro plating.

Answers to problems

Q1.

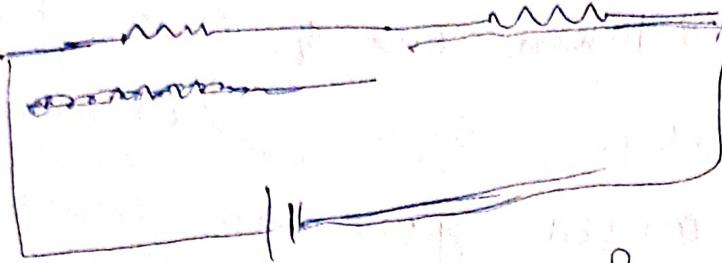

$$H_1 = \frac{I}{2\pi} \cdot \frac{J^2 \cdot R_1 \cdot t}{J}, \quad H_2 = \frac{I^2 R_2 t}{J}$$

$$\frac{H_1}{H_2} = \frac{\frac{I}{2\pi} \cdot \frac{J^2 R_1 t}{J}}{\frac{I^2 R_2 t}{J}} = \frac{R_1}{2\pi R_2} = \frac{4\pi d_2}{4\pi d_1} = \frac{d_2}{d_1} = 4 : 1 \quad \checkmark$$

Q53 part

Since the wind will blow through the balance Wheatstone bridge

Therefore no current through galvanometer. So resistance omitted.

Can

R_1 and R_2

are in series, $R_{S1} = 27 \Omega$

R_3 and R_4

are in series $R_{S2} = 135 \Omega$

Net resistance $= \frac{27 \times 135}{27 + 135} = 22.5 \Omega$

$$V = 2.48$$

$$I = \frac{V}{R} = \frac{2.48}{22.5} = 0.1102222 \text{ A.m}$$

$$\text{But } V_{MA} = V_{MB}$$

$$\Rightarrow I_1 R_1 = I_2 R_3$$

$$\Rightarrow I_1 \times 12 = I_2 \times 60$$

$$\Rightarrow I_1 = 5 I_2$$

$$\text{But } I_1 + I_2 =$$

$$\Rightarrow 5I_2 + I_2 = 1102222 \text{ Amperes}$$

$$\Rightarrow I_2 = \frac{1102222}{6} = 1837037 \text{ Amperes}$$

$$I_1 = 5 \times 1837037 = 091851857 \text{ Amperes}$$

$$V_{MA} = V_{MB} = I_2 \times R_3 = 1.10 \text{ Volts}$$

$$V_{AB} = V_{BN} = I_2 \times R_{BZ} \Rightarrow I_2 \times 75$$

$$= 1.3727 \text{ volts}$$

Since Galvanometer is balanced

$$\text{Volt } V_{AB} = 0 \text{ (Ans)}$$

3.

$$I = 5 \text{ Amp}$$

$$R = 10 \Omega$$

$$t = (2 \times 60) \text{ sec}$$

$$\frac{I^2 R t}{J} = m s \cdot \Delta \theta$$

$$\Rightarrow \frac{25 \times 10 \times 2 \times 60^2}{2 \cdot 7} = 100 \times 1 \times \Delta \theta$$

$$\Rightarrow \frac{50 \times 10 \times 11}{7} = \Delta \theta$$

$$\Rightarrow \frac{500}{7} = \Delta \theta$$

$$7) 50 \cdot (71.472)$$

$$②) \text{Temp } \text{measured} = 71.4^\circ \text{C} \checkmark$$

$$\frac{50}{10}$$

$$\frac{7}{30}$$

$$\frac{24}{20}$$

$$\frac{14}{6}$$

5.

$$\text{Heat measured } \text{in } s \Delta \theta \quad 1. (100 - 25.4)$$

$$= 1000 \times 74.6$$

$$74600 \text{ Cal}$$

~~Q.C.2~~

$$\frac{I^2 R t}{J} = 74600 \text{ Cal}$$

$$\Rightarrow \frac{746 \text{ watt} \times t}{4.2} = 74,600 \text{ Cal}$$

$$\Rightarrow t = \frac{74600 \times 4.2}{746} = 420 \text{ sec}$$

$$= 7 \text{ min}$$

$$6. \quad I^2 R = 20$$

$$H = \frac{I^2 R}{J} = \frac{2^2 \times 5 \times 60}{2 \times 2} = \frac{1000}{2} = 1428.57 \text{ Joules}$$

$$7) \frac{15000}{7} (1428.57)$$

$$\frac{30}{28}$$

$$\frac{20}{2}$$

$$\frac{24}{60}$$

$$\frac{56}{48}$$

$$\frac{32}{24}$$

$$\frac{16}{12}$$

$$\frac{4}{3}$$

$$\frac{1}{1}$$

$$7. \quad P = 2.5 = \frac{V^2}{R} = \frac{(20)^2}{R}$$

$$= 1.25 = \frac{400}{R} \quad \frac{400}{2.5} = \frac{160}{25} = 16 \Omega$$

$$8. \quad \gamma = 80 \Omega$$

$\frac{200}{25} \times \frac{16}{25} = \frac{3200}{625} = \frac{6.4}{125} = \frac{6.4}{500} = 0.0128$

$\frac{200}{25} = \frac{8}{1} = 8$

$\frac{16}{25} = \frac{4}{5} = 0.8$

$\frac{6.4}{500} = \frac{0.0128}{125} = 0.0001024$

$$\frac{V^2}{R} = \frac{200^2}{80} = \frac{40000}{80} = 500 \Omega$$

$$I = \frac{V}{R} = \frac{200}{80} = 2.5 \text{ Amperes}$$

$$\text{Power Consumed} = I^2 R = (2.5)^2 \times 80 = 500 \text{ Watts}$$

If it is working for $\frac{2}{1000}$ hours ie $\frac{2}{1000}$ hours

$$P = 500 \text{ Watts} \times 2 = 1000 \text{ Watts} \cdot \text{hr}$$

$$= 10^3 \text{ Kwh}$$

\therefore The money has to spend is 1 rupee.

7. ✓ 1. ✓

$$V = 220 \text{ V} \cdot \text{A},$$

It means that when potential difference of 220 volts then it will supplies 60 watt at power.

$$g_m \text{ one day.} = 60 \times 5 = 300 \text{ Watt hr.}$$

$$Q_m \text{ one day} = Q_m 30 \text{ day} = 300 \times 30 = 9 \times 10^3 \text{ watt hr} \\ = 9 \text{ KWh hour} \\ = 9 \text{ unit.}$$

$$\begin{array}{lll} 3 \text{ units} & \text{Cent} = & 1 \text{ rupee}, \\ 9 \text{ units} & \text{Cent} = & 3 \text{ rupees}. \end{array}$$

$$12. \quad \text{Total Lamps} = 360$$

1 flame Continuum = 50 watt.

360 " 1/2 360, 3,

$$11 = (360 \times 50) \text{ wat.}$$

One fighter = 6 hrs.

Each row lights

Each lamp lights $360 \times 50\pi$

Power Consumption = $300 \times 50 \text{ W}$

$$\text{Total Power Consumed} = \frac{(9 \times 30)}{4} \text{ kW hr}$$

$$(9 \times 3^0) = \frac{360 \times 50 \times 6 \times 9 \times 3}{4} \\ = 29,160 \times 10^3$$

$$= 29,160 \text{ Kwh}$$
$$= 29,160 \text{ kWh}$$

91 Cents | Unit = $\frac{3}{8}$ Rupee

29, 160 count = 10,935
82 rpm

$V = 220 \text{ V}_{\text{AC}}$, ~~Reel 1 Ppppppppppp~~

Power - Each lamp will consume = 5瓦特 + $360 \text{瓦特} \times 50 \text{盏}$.

$$P = \frac{360 \text{瓦特} + 360 \times 50 \text{瓦特}}{220 \text{伏特.}} = 18000 \text{瓦特.}$$

$$I = \frac{P}{V} = \frac{18,000}{220} = 81.81 \text{ 安培.}$$

B. Water equivalent = $MS = 100 \text{ 公斤.}$
 $Q_i = 15^\circ \text{C}$.
 $Q_f = 10^\circ \text{C}$.
 Water has mass = 100 公斤.
Required to boil water

Heat = Heat gain by kettle to boil water produced by kettle
 \Rightarrow Heat gain by water + Heat gain by kettle
 $= Heat$
 $= 1000 \times 1 \times (100-15) + 100 \times (10-0)$.
 $= 85,000 \text{ 焦耳} \rightarrow 85,000 \text{ 卡路里}$

$\Rightarrow \frac{P_{ht}}{J} = 1 \text{ KW}$

10-7. heat = 93,500 卡路里
 Since heat input is more than required = 9,350卡路里
So heated needed = 93,500
Total heat consumed = $\frac{93,500}{9,350} = 102,850 \text{ 卡路里}$

$$\therefore \frac{I^2 R t}{J} = 102,850$$

$$\Rightarrow \frac{V \cdot I \cdot t}{J} = 102,850$$

$$\Rightarrow \frac{230 \times 4 \times t}{4.2} = 102,850$$

$$\Rightarrow t = \frac{102,850 \times 4.2}{230 \times 4}$$

$$= 469.53 \text{ sec}$$

$$= 7.82 \text{ min}$$

Total time = 7 min, 49 sec.


Total heat = 102,850 Cal.

Total time = 469.53 sec.

$$\text{Heat per sec} = \frac{102,850}{469.53}$$

= 219 Cal/sec.

Problems on Kirchhoff's Law

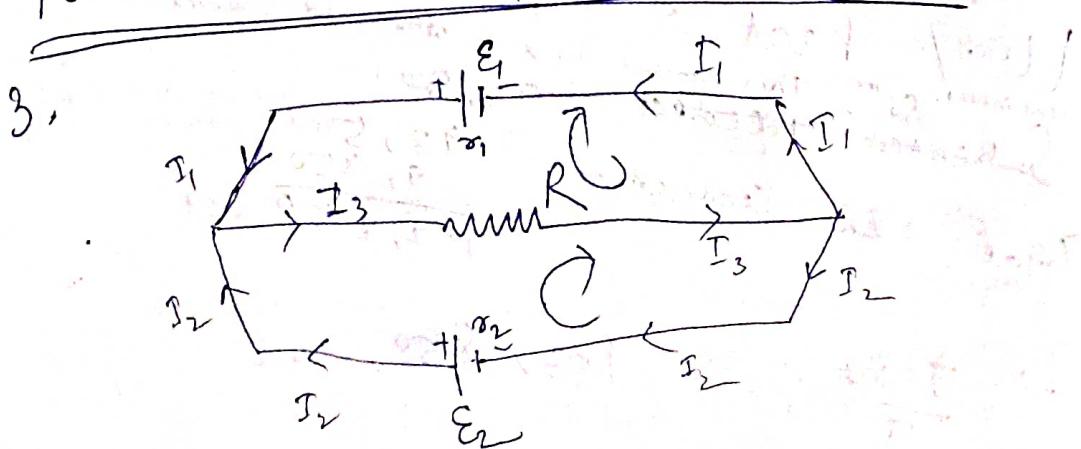

Applying Kirchhoff's law for the point A,

$$I_1 + I_2 - I_3 = 0 \quad (i)$$

Applying Kirchhoff's law to the upper loop,

$$-I_1 \cdot \sigma_1 - I_3 R = -\varepsilon_1 \quad (ii)$$

$$\Rightarrow I_1 \sigma_1 + I_3 R = \varepsilon_1 \quad (ii)$$

Applying Kirchhoff's 2nd law for the lower

loop, $I_3 R + I_2 \sigma_2 = \varepsilon_2 \quad (iii)$

from eqn (ii) and (iii), $I_3 = I_1 + I_2$, Putting

thus value in (ii) and (iii)

$$I_3 = I_1 \sigma_1 + (I_1 + I_2) R = \varepsilon_1 \quad (iv)$$

$$I_1 \sigma_1 + I_1 R + I_2 R = \varepsilon_1$$

$$(I_1 + I_2) R + I_2 \sigma_2 = \varepsilon_2 \quad (v)$$

Subtract v from (iv)

$$I_1 \sigma_1 - I_2 \sigma_2 = \varepsilon_1 - \varepsilon_2$$

$$\Rightarrow I_1 = \frac{\varepsilon_1 - \varepsilon_2 + I_2 \sigma_2}{\sigma_1} \quad (vi)$$

Putting this value in eqn (iv), we get

$$\left(\frac{\varepsilon_1 - \varepsilon_2 + I_2 \gamma_2}{\gamma_1} \right) \gamma_1 + \left(\frac{\varepsilon_1 - \varepsilon_2 (\gamma_2 R)}{\gamma_1} \right) R$$

$$+ I_2 R = \varepsilon_1$$

$$\Rightarrow \frac{\varepsilon_1 \gamma_1 - \varepsilon_2 \gamma_1 + I_2 \gamma_2 \gamma_1 + \varepsilon_1 R \varepsilon_2 R + I_2 \gamma_2 R + I_2 R \gamma_1 - \varepsilon_1}{\gamma_1} = \varepsilon_1$$

$$\Rightarrow I_2 (\gamma_2 \gamma_1 + \gamma_2 R + R \gamma_1) + \left(\frac{\varepsilon_1 \gamma_1 - \varepsilon_2 \gamma_1 + \varepsilon_1 R}{-\varepsilon_2 R} \right) = \varepsilon_1$$

$$\Rightarrow I_2 = \frac{-\varepsilon_1 R + \varepsilon_2 \gamma_1 + \varepsilon_2 R}{\gamma_1 \gamma_2 + \gamma_2 R + \gamma_1 R}$$

Putting this value in eqn (V)

$$I_3 R + \left(\frac{\varepsilon_1 R - \varepsilon_2 \gamma_1 - \varepsilon_2 R}{\gamma_1 \gamma_2 + \gamma_2 R + \gamma_1 R} \right) \gamma_2 = \varepsilon_2$$

$$\Rightarrow I_3 R = \varepsilon_2 - \frac{\varepsilon_1 R \gamma_2 - \varepsilon_2 \gamma_1 \gamma_2 - \varepsilon_2 R \gamma_2}{\gamma_1 \gamma_2 + \gamma_2 R + \gamma_1 R}$$

$$\Rightarrow I_3 R = \frac{\varepsilon_2 \gamma_1 \gamma_2 + \varepsilon_2 \gamma_2 R + \varepsilon_2 \gamma_1 R - \varepsilon_1 R \gamma_2 + \varepsilon_2 \gamma_1 \gamma_2 + \varepsilon_2 R \gamma_1}{\gamma_1 \gamma_2 + \gamma_2 R + \gamma_1 R}$$

$$\Rightarrow I_3 = \frac{1}{R} \left(\frac{\varepsilon_2 \gamma_1 \gamma_2 + \varepsilon_2 \gamma_2 R + \varepsilon_2 \gamma_1 R - \varepsilon_1 R \gamma_2 + \varepsilon_2 \gamma_1 \gamma_2 + \varepsilon_2 R \gamma_1}{\gamma_1 \gamma_2 + R(\gamma_1 + \gamma_2)} \right)$$

Problems on Kirchhoff's law

1.

4Ω and 12Ω are connected in parallel

$$R_P = \frac{12 \times 4}{16} = 3\Omega$$

3Ω and 1Ω are connected in series

$$R_{S1} = 4\Omega \quad V = 4 \text{ volt}$$

$$I_1 = \frac{V}{R} = \frac{4}{4} = 1 \text{ Amp}$$

Let current be I_1 , I_2 and I_3 through 3Ω , 4Ω , 12Ω resistors

Let current

be I_1 , I_2 and I_3

Applying Kirchhoff's first law

$$I_1 - I_2 - I_3 = 0$$

$$\Rightarrow I_1 = I_2 + I_3$$

$$\Rightarrow I = I_2 + I_3 \quad \text{for loop considering}$$

Applying second law

4Ω and 12Ω

$$4I_2 - 12I_3 = 0 \quad (ii)$$

$$\Rightarrow 4(1 - I_3) - 12I_3 = 0$$

$$\Rightarrow 4 - 16I_3 = 0$$

$$\Rightarrow I_3 = \frac{4}{16} = \frac{1}{4} \text{ Amp.}$$


$$I_2 = 1 - I_3 = 1 - \frac{1}{4} = \frac{3}{4} \text{ Amp.}$$

Ans

Voltage across 4Ω resistor

$$= I_2 \times R = \frac{3}{4} \times 4 = 3 \text{ volt}$$

Ans

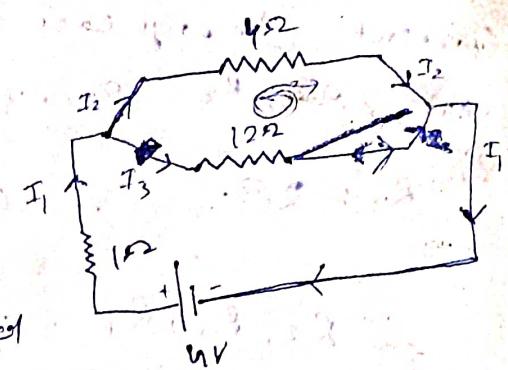


2. Calculate the

current through each resistor.

$$R_1 = 2\Omega, R_2 = 3\Omega, R_3 = 6\Omega$$

$$R_4 = 2\Omega, V = 6 \text{ volt}$$

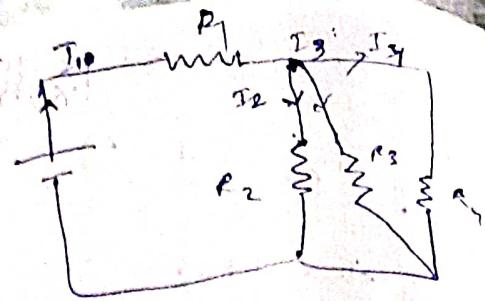

R_2, R_3, R_4 are in parallel across

R_1 is in series.

$$\therefore R = R_1 + \left(\frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} \right)$$

$$= 2 + \left(\frac{3 \cdot 6 \cdot 2}{12 + 6 + 18} \right)$$

$$= 2 + \left(\frac{36}{36} \right)$$

$$= 2 + 1$$

$$= 3 \Omega$$

$$V = 6 \text{ volt}$$

$$I_1 = \frac{V}{R} = \frac{6}{3} = 2 \text{ A}$$

Applying Kirchhoff's 2nd law in

$$I_2 R_4 - I_3 R_3 = 0$$

$$\Rightarrow I_2 \cdot 2 - I_3 \cdot 6 = 0$$

$$\therefore 2 I_2 = 6 I_3$$

$$I_3 R_3 - I_2 R_2 = 0$$

$$\Rightarrow I_3 \cdot 6 = I_2 \cdot 3$$

$$\therefore I_2 = 2 I_3$$

$$\text{Ans} \Rightarrow A_1 = 2, A_2 = \frac{2}{3}, A_3 = \frac{1}{3}, A_4 = \frac{1}{3}$$

Q1, Q2

Applying KCL at node,

$$\text{But } I_2 + I_3 + I_4 = 2 \text{ Amp}$$

$$\Rightarrow 2I_3 + I_3 + 3I_3 = 2$$

$$\therefore 6I_3 = 2$$

$$\therefore I_3 = \frac{2}{6} = \frac{1}{3}$$

$$I_2 = 2 \cdot \frac{1}{3} = \frac{2}{3}$$

$$I_4 = 3 \cdot \frac{1}{3} = 1$$

$$I_2 = \frac{2}{3}, I_3 = \frac{1}{3}, I_4 = 1 \text{ Amp}$$

$$\therefore I_1 = 2 \text{ Amp}$$

(5.) A uniform wire 4 metre long

and 6Ω per meter resistance

in bent form of a square

name ABCD. The adjacent

Corners A and B are connected to a


battery or e.m.f 3 Volt. and

internal resistance 4Ω . Find the

current along AB.

$$(\text{Ans} = \frac{9}{34} \text{ Amp})$$

Sol?

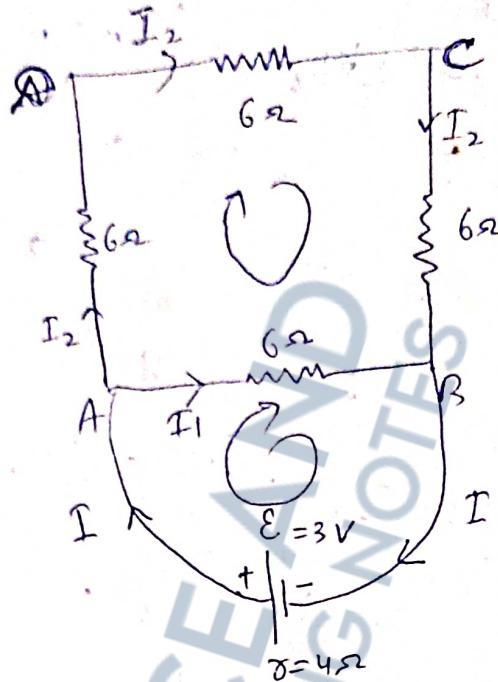

Method - 1

AD, CD only CB resistors
each is equal to 6Ω are
connected in series.

Equivalent resistance

$$R_s = 18 \Omega$$

R_s and AB are connected
in parallel.

$$R_p = \frac{18 \times 8}{2 + 8} = \frac{18}{3} \Omega$$

Total resistance of the circuit

$$\begin{aligned}
 &= \frac{1}{4} (18 + 4 \cdot 2) \\
 &= \frac{18 + 16}{4} \\
 &= \frac{34}{4} \Omega \\
 &= \frac{17}{2} \Omega
 \end{aligned}$$

$E = 3 \text{ V}$ mult

$$\text{Current}(I) = \frac{V}{R} = \frac{3}{\frac{17}{2}} = \frac{6}{17} \text{ Amp.} \quad \checkmark$$

$$V_A - V_B = I_1 \times R_P = I_2 \times 18 = I_1 \times 6$$

$$\Rightarrow \cancel{I_1 \times 6} = I_1 \times 6$$

$$\Rightarrow \frac{6}{17} \times \frac{18}{2} = I_1 \times 6$$

$$\Rightarrow I_1 = \frac{6}{17} \times \frac{18}{2} \times \frac{1}{6} = \frac{9}{34} \text{ Amp.}$$

$$I_2 = \frac{3 \times 6}{17} \times \frac{18}{2} \times \frac{1}{18} = \frac{3}{34} \text{ Amp.}$$

Method-2

Applying Kirchhoff's law for the upper loop,

$$I_2 \cdot 6 + I_2 \cdot 6 + I_2 \cdot 6 - I_1 \cdot 6 = 0$$

$$\Rightarrow 18I_2 - I_1 \cdot 6 = 0$$

$$\Rightarrow 3I_2 - I_1 = 0$$

$$\Rightarrow I_1 = 3I_2$$

For the lower loop,

$$I_{1,6} + I_4 = 3 \quad \text{--- (i)}$$

(i)

For the function point A,

$$T - I_1 - I_2 = 0$$

$$\Rightarrow I = I_1 + I_2$$

Putting this in eqn (i),

$$I_{1,6} + (I_1 + I_2) 4 = 3$$

$$\Rightarrow I_{1,6} + 4I_1 + 4I_2 = 3$$

$$\Rightarrow 10I_1 + 4I_2 = 3 \quad \text{--- (ii)}$$

$$\Rightarrow 10(3I_2) + 4I_2 = 3$$

$$\Rightarrow 34I_2 = 3$$

$$\Rightarrow I_2 = \frac{3}{34} \text{ Amperes}$$

$$I = 3I_2 = 3 \cdot \frac{3}{34} = \frac{9}{34} \text{ Amperes}$$

Current @ cross


$$A_B = \frac{9}{34} \text{ Amperes}$$

Parameter Change δR_{AB}

Current change δI_A ,

✓ Wheat-Stone's bridge. (Unbalanced)

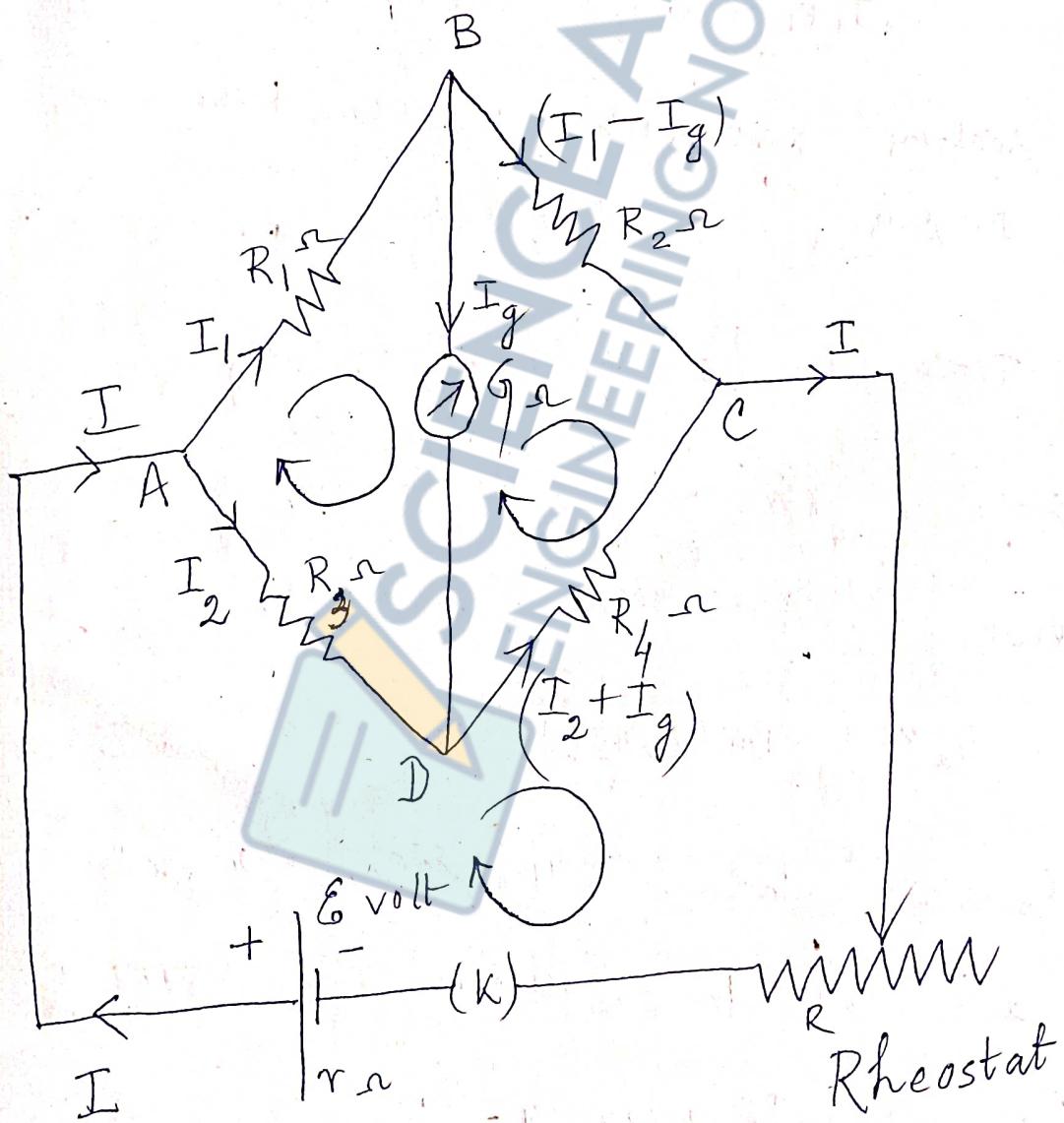This is a typical arrangement of 4 resistances forming the four sides of a quadrilateral such that the galvanometer is connected to the opposite corners while the battery is connected to the other two opposite corners.



In general, there will be some current flowing through the galvanometer and we call such a bridge as unbalanced.

Wheatstone's bridge

Applying Kirchhoff's first law to the junction Point A, we get

$$I_{\text{in}} - I_1 - I_2 = 0 \quad \text{(i)}$$

Applying Kirchhoff's second law to the loop ABCDA, we get

$$I_1 R_1 + I_g G - I_2 R_3 = 0 \quad \text{(ii)}$$

Applying Kirchhoff's second law to the loop

BCDAB, we get

$$(I_1 - I_g) R_2 - R_4 (I_2 + I_g) - G I_g = 0 \quad \text{(iii)}$$

Applying Kirchhoff's second law to the

loop ADCKA, we get

$$I_2 R_3 + R_4 (I_2 + I_g) + R I + \gamma D = \Sigma \quad \text{(iv)}$$

Solving these 4 eqns, one

can get the values of currents

like I , I_1 , I_2 , I_g .

Balanced Wheatstone's Bridge

This is a typical arrangement of 4 resistances forming the four sides of a quadrilateral. A galvanometer is connected to any two opposite corners where as other two opposite corners are connected to the galvanometer. By adjusting it through the resistances, it is possible to have no current i.e. $I_g = 0$.

Only when the 4 resistances satisfy a condition, it is possible to have no deflection in the galvanometer.


Let's try to derive the balanced Kirchhoff's laws for the bridge using levels ABD A and BCD B

Applying Kirchhoff's second law

to the loop ABDA, $\sum RI = \sum E$

$$I_1 R_1 + G.O - I_2 R_3 = 0$$
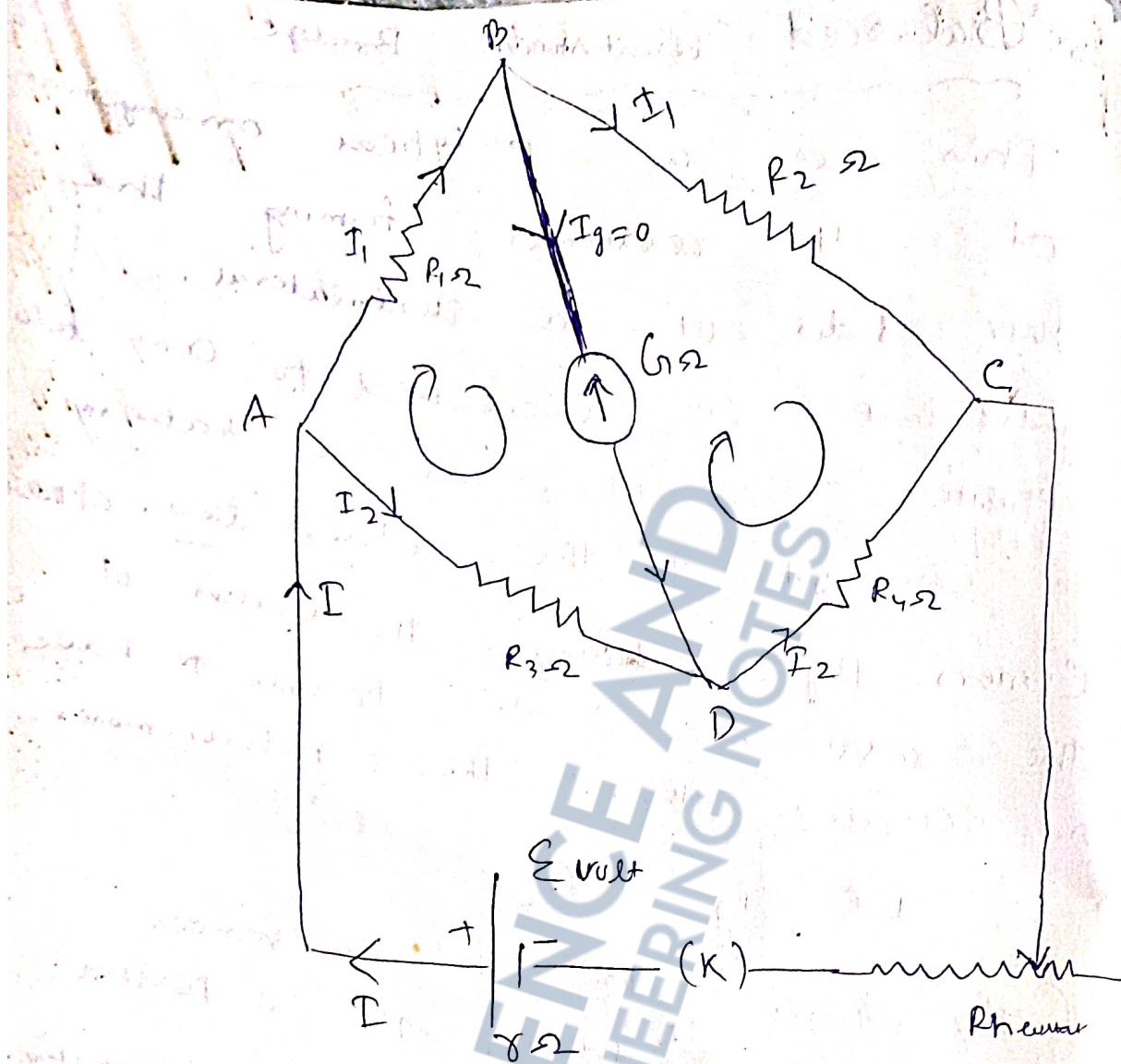
$$\Rightarrow I_1 R_1 = I_2 R_3 \quad \text{---(1)}$$



Applying Kirchhoff's law to the loop B C D B

$$\sum IR = \sum E$$

$$R_2 I_1 - R_4 I_2 - E_{volt} = 0$$

$$\Rightarrow I_1 R_2 = I_2 R_4 \quad \text{--- (ii)}$$

Dividing eqn (i) by eqn (ii)

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

or

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$


$$\Rightarrow \frac{I_2}{I_1} = \frac{R_2}{R_1}$$

This is the condition of balance of a wheatstone bridge.

This principle is applied to instruments like meter bridge and post office box to find the unknown resistance of a wire.

Application = (Meter bridge)

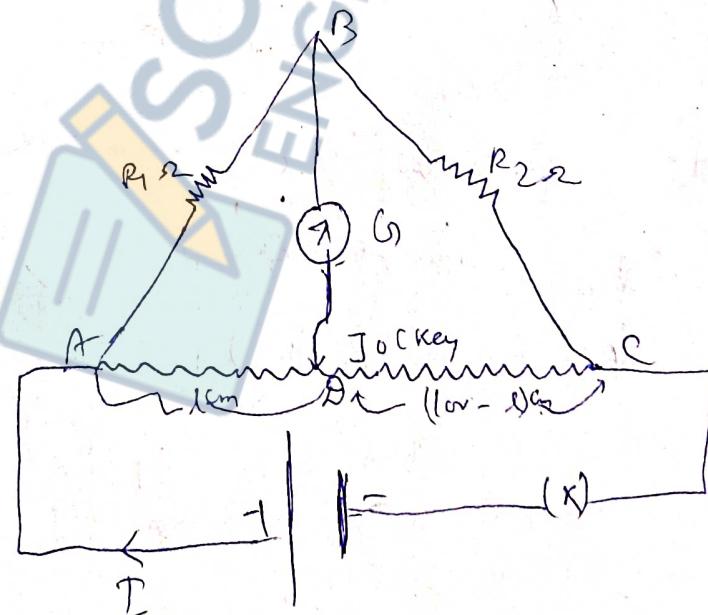
It is a modification of wheatstone bridge by which resistance of a wire can be determined. Here the two resistances R_3 and R_4 have been replaced by a uniform wire of length 100 cm. There is a contact maker called jockey which slides divides the wire into two parts.



$$R_3 = lf$$

$$R_4 = (100-l)f$$

where f = resistance per unit length.

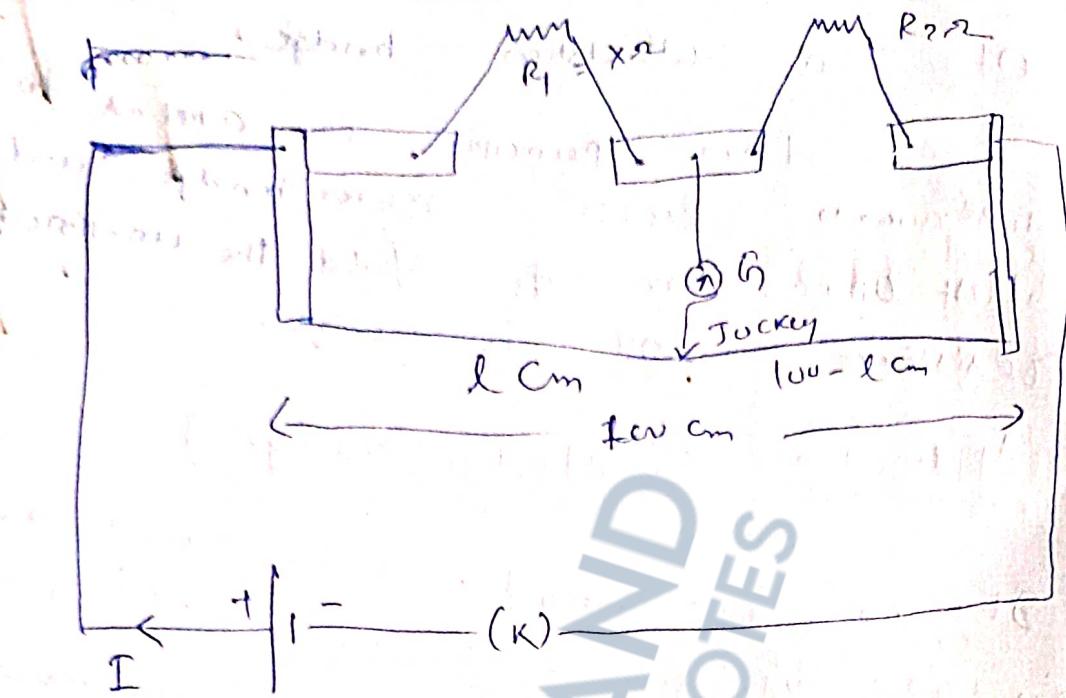

For no current through the galvanometer

$$\frac{X}{R_2} = \frac{R_3}{R_4} = \frac{l}{(100-l)}$$

$$\text{or } X = R_2 \cdot \frac{l}{100-l}$$

If the unknown resistance be interchanged

With R_2 , then R_3 be R_2 and

$$R_4 = (100-l) \Omega$$

$$\frac{R_2}{X} = \frac{l}{(100-l)} = \frac{l}{100-l}$$

$$\frac{X}{R_2} = \frac{(100-l)}{l}$$

$$\therefore X = \frac{R_2 (100-l)}{l}$$

Mean of these two values of X be taken


(6) ABCD is in a quadrilateral of which the arms have resistances $AB = 1\Omega$, $BC = 2\Omega$, $CD = 3\Omega$, $DA = 4\Omega$.

A galvanometer or resistance 5Ω is placed across BD. If a current of 1 Amp is passed through A and leaves

at C, calculate the current in the galvanometer. (Ans: $\frac{1}{15}$ Amp)

(7) A current of 0.1 Amp enters a Wheatstone bridge consisting of 3 arms and one of 11Ω each. Find the current through the galvanometer whose resistance is 100Ω . (Ans: $\frac{1}{4520}$ Amp)

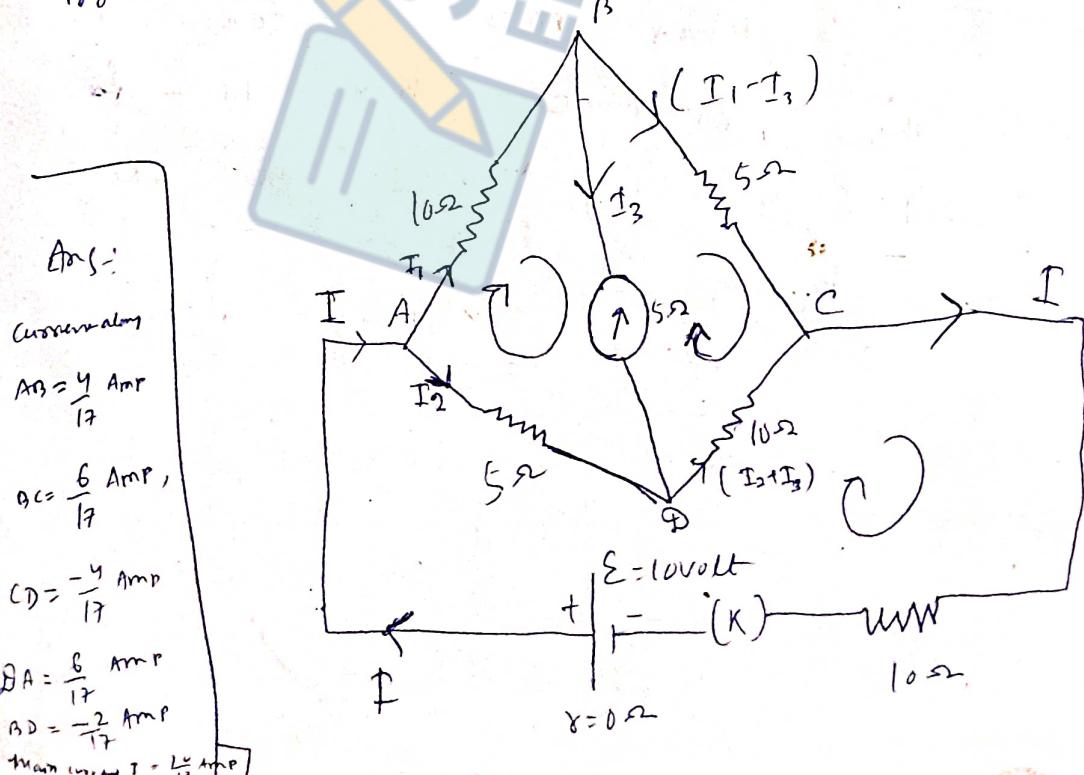(8) Determine the current in each branch of the following network.



Problem on Chemical effect of current

4. A series circuit is completed with a battery of negligible resistance, a 14 voltameter and a resistance box with $5\ \Omega$ from the box, the mass of Cu deposited is 0.36 gm in 10 minute. With $10\ \Omega$ from the box, the mass of Cu deposited is 0.48 gm. In 20 min. Find the internal resistance of the voltmeter. ($A_n = 5\ \Omega$)

Ans: If the internal resistance of the voltmeter is $x\ \Omega$, when $5\ \Omega$ is included in

$$\text{From } R \rightarrow Q \quad \text{when } 5\ \Omega \text{ is included in the circuit, current will be given by } I_1 = \frac{E}{5+x}$$

When $10\ \Omega$ is taken out from the resistance box, $10\ \Omega$ is included in the circuit and the current becomes $I_2 = \frac{E}{10+x}$

$$\therefore \frac{I_1}{I_2} = \frac{10+x}{5+x}$$

From Faraday's first law

$$m_1 = Z I_1 t_1$$

$$\text{and } m_2 = \frac{I_1}{I_2} t_2$$

$$\therefore \frac{m_1}{m_2} = \frac{I_1 t_1}{I_2 t_2}$$

$$\Rightarrow \frac{36 \text{ gm}}{48 \text{ gm}} = \frac{10 + 8}{5 + 8} \cdot \frac{18 \text{ min}}{24 \text{ min}}$$

$$\Rightarrow \frac{3}{4} = \frac{10 + 8}{10 + 8}$$

$$\Rightarrow 30 + 6x = 40 + 4x$$

$$\Rightarrow 2x = 10$$

$$\Rightarrow x = 5 \text{ sec}$$

(5.) In the electrolysis of water, 83.7 C.C or hydrogen were collected at a pressure or 68 cm of mercury at 25°C . When a current was passed through Cu. Calculate the E.C.F. (Ans: 0.0003216 gm/Coul)

$$\text{Given } \frac{1}{t} \text{ At wt of Cu} = 63.57$$

$$\text{At wt of H} = 1.008$$

$$\text{Density of hydrogen at } 0^\circ\text{C} = 0.0898 \text{ gm/lit}$$

Thus \rightarrow Using combined gas law volume of hydrogen at N.T.P be found out.

$$m = \text{Volume} \times \rho = I_1 I_2 t_1 \times \frac{m_1}{F_1} \times \frac{F_2}{m_2}$$

6. ~~A~~ A tangent galvanometer has a
 current of 1A when the
 deflection is 45°. The same
 current passes through a copper voltmeter
 where it develops 0.3 gm of Cu in
 30 minutes. If the P.C.E of Cu
 is 0.00033 gm/Coul, find the
 value of the current. (Ans: 0.505 Amp)

Hint: For a tangent galvanometer,

$$I = 10K \tan \theta$$

7. ~~An~~ An electric circuit contains
 a T.G. which gives deflection
 of 45° when an additional resistance
 of 4Ω is put in the circuit. The
 deflection is reduced to 30°. Calculate
 the total resistance in the first case.

$$\text{Ans: } \frac{5}{2} (\sqrt{3} + 1) \Omega$$

$$I_1 = \frac{\epsilon}{R}$$

$$I_2 = \frac{\epsilon}{R+4}$$

Q. A battery of internal resistance γ is connected with a T.G in series and resistance R . The deflection being α when R is replaced by R' , the deflection in β . Now that the internal resistance or galvanometer is

$$\left(\frac{R' \tan \beta - R \tan \alpha}{\tan \alpha - \tan \beta} \right) - \beta$$

Ans: $I_1 =$ Current in the first can

$$= \frac{E}{R + \gamma + \beta}$$

$I_2 =$ Current in the second can

$$= \frac{E}{R' + \gamma + \beta}$$

$$\frac{I_1}{I_2} = \frac{R' + \gamma + \beta}{R + \gamma + \beta} \quad (i)$$

For a T.G we know that

$$I_1 = 10 K \tan \alpha$$

$$I_2 = 10 K \tan \beta$$

$$\therefore \frac{I_1}{I_2} = \frac{\tan \alpha}{\tan \beta} \quad (ii)$$

B quantity the P.H.S of (i) and (ii)

$$\frac{R^1 \tan \gamma + B}{R \tan \alpha + B} = \frac{\tan \alpha}{\tan \beta}$$

$$\Rightarrow R^1 \tan \beta + \gamma \tan \beta + B \tan \beta = R \tan \alpha + \gamma \tan \alpha + B \tan \alpha$$

$$\begin{aligned} \Rightarrow & \gamma (\tan \beta - \tan \alpha) = R \tan \alpha - B \tan \alpha - R^1 \tan \beta \\ & \quad - B \tan \beta \\ \Rightarrow & \gamma = \frac{-B (\tan \alpha - \tan \beta) - R^1 \tan \beta}{(\tan \beta - \tan \alpha)} \\ & = \frac{R^1 \tan \beta - R \tan \alpha + B \tan \alpha + B \tan \beta}{(\tan \beta - \tan \alpha)} \end{aligned}$$

$$\Rightarrow R^1 \tan \beta + B \tan \beta - R \tan \alpha - B \tan \alpha$$


$$= \gamma (\tan \alpha - \tan \beta)$$

$$\Rightarrow \frac{R^1 \tan \beta - B (\tan \alpha - \tan \beta) - R \tan \alpha}{(\tan \alpha - \tan \beta)} = \gamma$$

$$\Rightarrow \frac{R^1 \tan \beta - R \tan \alpha}{(\tan \alpha - \tan \beta)} - B = \gamma$$

Q(4) Find the equivalent resistance between A and F.

$$A_m = \frac{7R}{5} \Omega$$

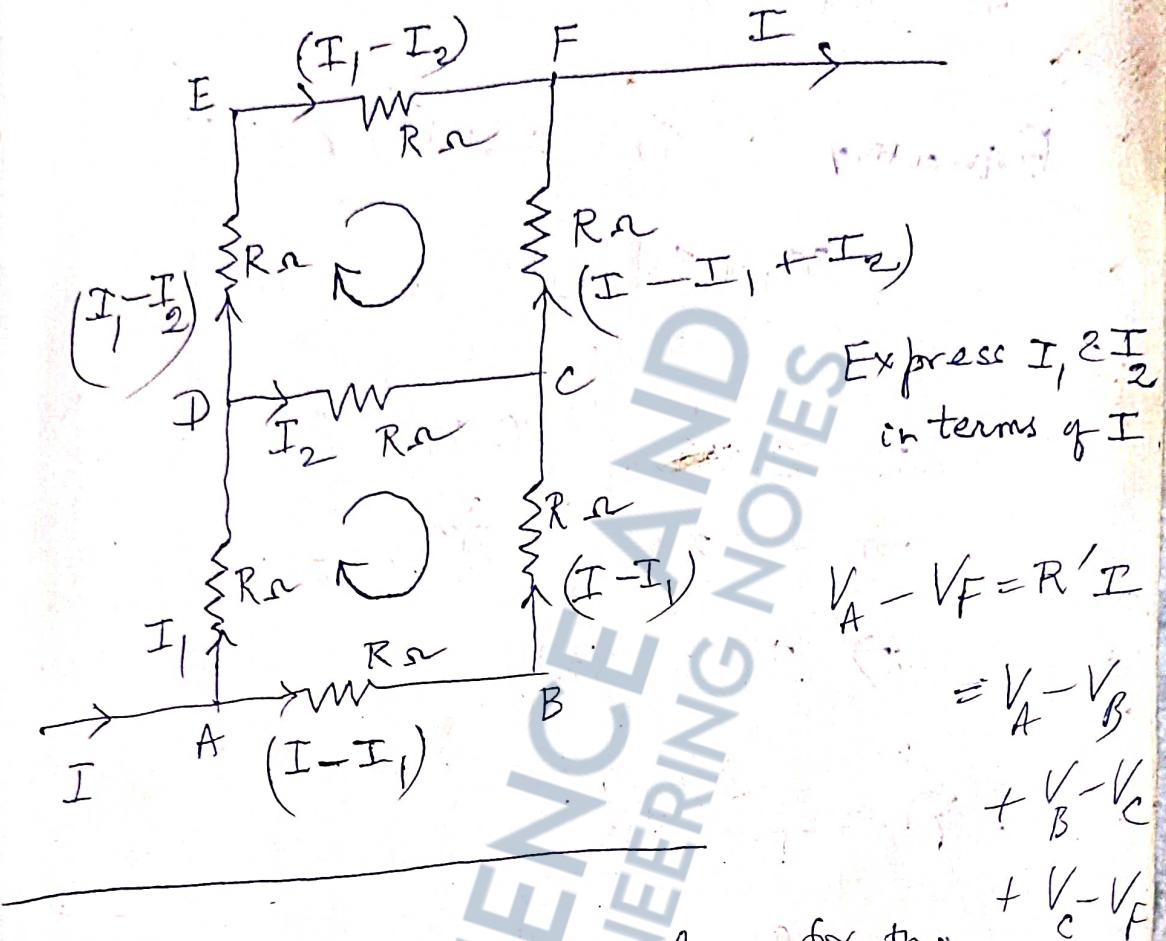

Express I_1 & I_2
in terms of I .

$$V_A - V_F = R' I$$

$$= V_A - V_B$$

$$+ V_B - V_C$$

$$+ V_C - V_F$$

Applying Kirchhoff's 2nd law for the loop AD CBA, we get:

$$I_1 R + I_2 R - (I - I_1) R - (I - I_1) R = 0$$

$$\Rightarrow I_1 R + I_2 R - I R + I_1 R - I R + I_1 R = 0$$

$$\Rightarrow 3I_1 R + I_2 R - 2I R = 0$$

$$\Rightarrow 3I_1 + I_2 = 2I \Rightarrow I = \frac{3I_1 + I_2}{2} \quad (i)$$

Applying Kirchhoff's 2nd law for the loop AFCA, we get

$$(I_1 - I_2) R + (I_1 - I_2) R - (I - I_1 + I_2) R - I_2 R = 0$$

$$\Rightarrow I_1 R - I_2 R + I_1 R - I_2 R - 2R + I_1 R - I_2 R - I_2 R = 0$$

$$\begin{aligned} \Rightarrow 3I_1R - 4I_2R &= IR_2 \\ \Rightarrow 3I_1 - 4I_2 &= I \quad \text{---(i)} \end{aligned}$$

Equating (i) and (ii), we get

$$\frac{3I_1 + I_2}{2} = 3I_1 - 4I_2$$

$$\Rightarrow 3I_1 + I_2 = 6I_1 - 8I_2$$

$$\Rightarrow 3I_1 = 9I_2$$

$$\Rightarrow I_1 = 3I_2$$

~~$$- 2I_1 - 8I_2$$~~

From (i)

$$3 \cdot (3I_2) - 4I_2 = I$$

$$\Rightarrow 9I_2 - 4I_2 = I$$

$$\Rightarrow 5I_2 = I$$

$$\Rightarrow I_2 = \frac{I}{5}$$

$$I_1 = 3 \times \frac{I}{5} = \frac{3I}{5}$$

$$V_A - V_f = RI = V_A - V_B + V_B - V_C + V_C - V_f$$

$$\Rightarrow R' = \frac{R(I - I_1) + R(D - I_1) + R(I - I_1 + I_2)}{I}$$

$$= R \left(\frac{3I - 3I_1 + I_2}{I} \right) = R \left(\frac{3I - 3 \cdot \frac{3I}{5} + \frac{I}{5}}{I} \right) = \frac{R \times 7I}{5 \cdot I} = \frac{7R}{5}$$

Equivalent resistance $\frac{I}{5}$.

(Ans)

Grouping of cells


30.07.2K1

Suppose we are provided with N number of cells, each of e.m.f E volt and internal resistance r ohm.

(1) Cells in series

Cells are said to be connected in series when the -ve terminal of one cell is connected to the +ve terminal of the other cell and the free ends are connected to an external resistance R_2 .

R_2

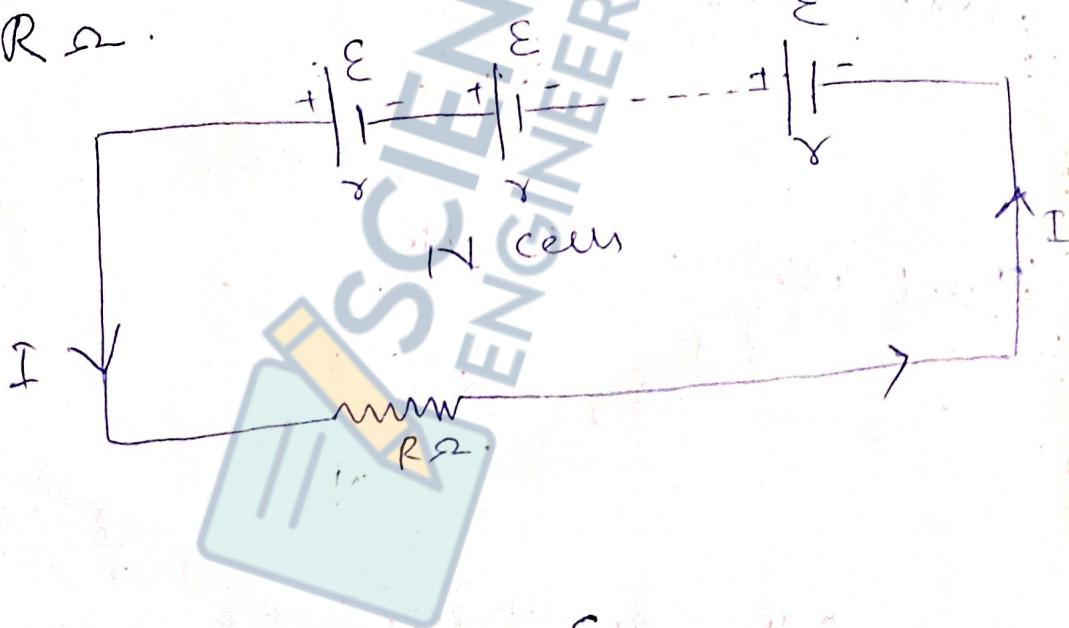

$$\text{Net e.m.f} = N \cdot E$$

because all the cells try to push the charges in the same direction.

$$\text{Total resistance} = R + N \cdot r$$

$$\text{Current} = \frac{\text{Net e.m.f}}{\text{Total resistance}}$$

R should
be high


$$I = \frac{N\epsilon}{R + N\gamma}$$

(Ans) If $R < N\gamma$, then $I = \frac{N\epsilon}{N\gamma} = \frac{\epsilon}{\gamma}$
 Current is independent. There is no increase in current providing more and more cells. So their connection is not useful.

Current increases with $R > N\gamma$.
 External resistance in very very higher than internal resistance of cell.
Ans or $R \gg N\gamma$, $I = \frac{N\epsilon}{R}$.

(2) Cells in series with one of the

Cells being wrongly connected

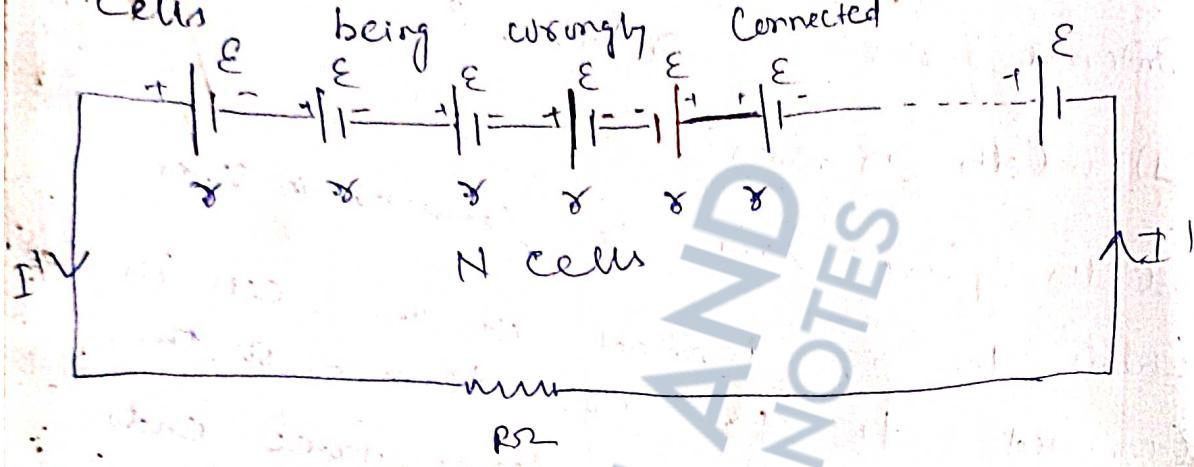

$$\begin{aligned}\text{Net emf} &= (N-1)\epsilon - \epsilon \\ &= (N-2)\epsilon\end{aligned}$$

$$\text{Total resistance} = R + N\gamma$$


$$\text{Current} = I^1 = \frac{(N-2)\epsilon}{R + N\gamma}$$

(3) Cells in parallel

Cells are said to be connected in parallel when all the +ve terminal

are connected to one point and all the -ve terminals are connected to another point.

These two points can be connected to an

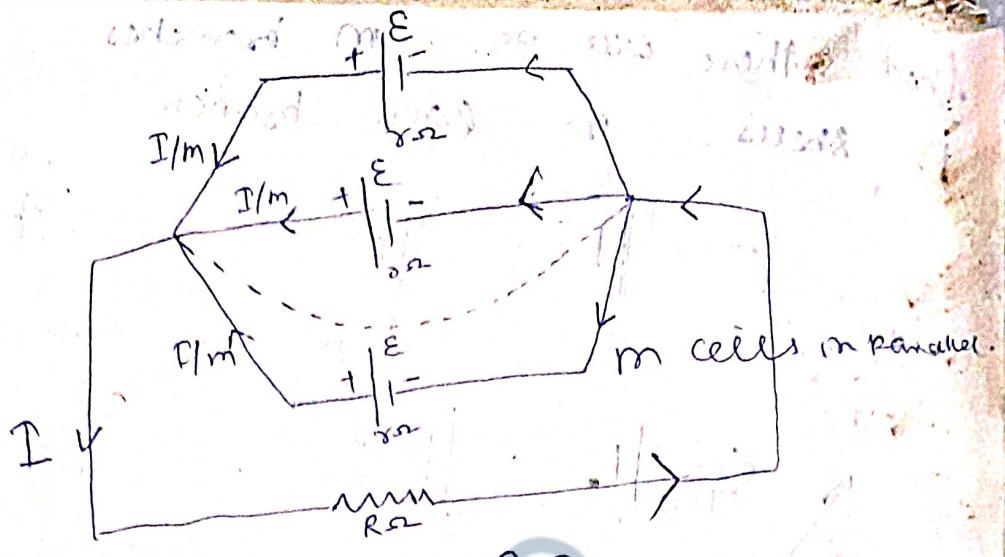

External resistance R_{S2} .

$$\text{Net e.m.f} = \sum E$$

$$\text{Total resistance} = R + \gamma_p$$

where γ_p equivalent resistance of all the cells which are connected in parallel.

$$\therefore \frac{1}{\gamma_p} = \frac{1}{\gamma} + \frac{1}{\gamma} + \frac{1}{\gamma} \dots \text{upto } m \text{ terms.}$$

$$\Rightarrow \gamma_p = \frac{\gamma}{m}$$

$$\text{Current} = \frac{\text{Net emf}}{\text{Total resistance}}$$

(Main)

$$\Rightarrow I = \frac{\sum E}{R + \frac{\gamma}{m}}$$


Case-1 $R \gg \frac{\gamma}{m}$ $I = \frac{\sum E}{R}$, so net emf in increasing No of cells.	Case-2 $R \leq \frac{\gamma}{m}$, $I = m \times \frac{\sum E}{\gamma}$, so it is univeral. So external resistance should be very low.
---	---

$$= \frac{m \cdot \sum E}{mR + \gamma}$$

④ Mixed grouping of Cells

Let's make a combination of cells such

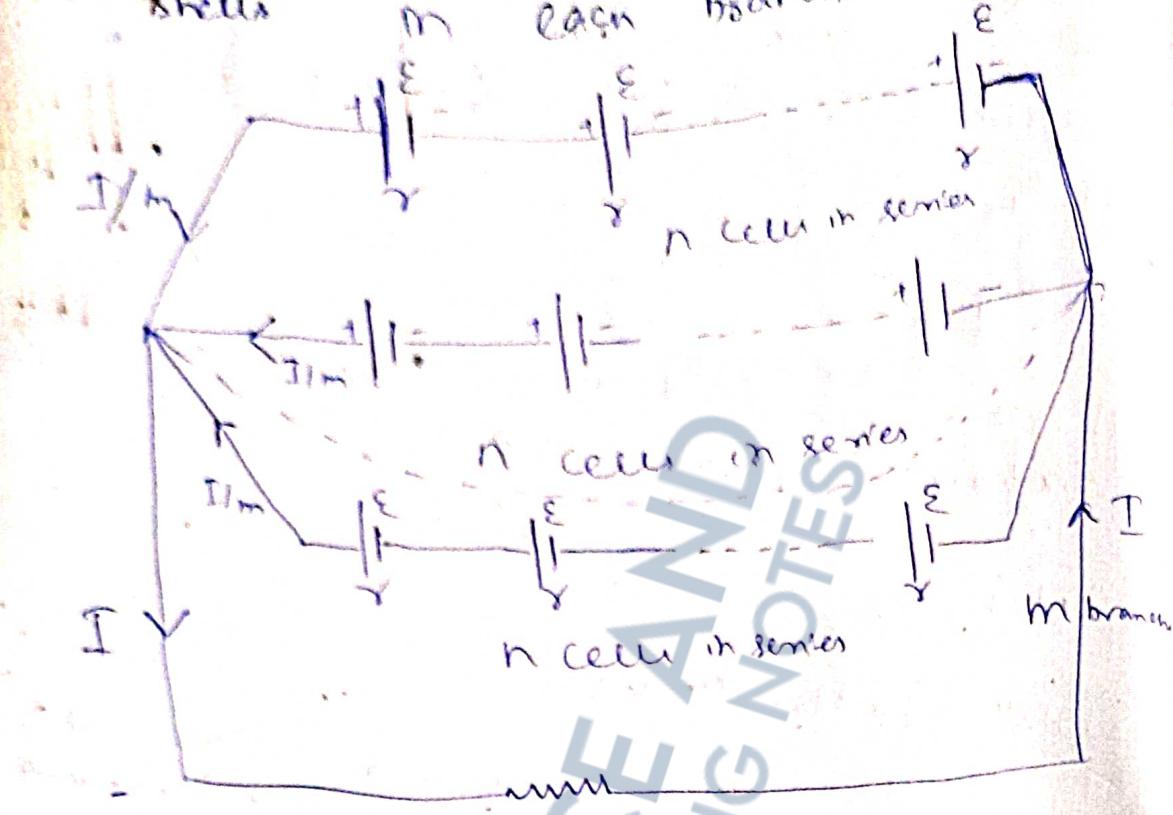that there will be m branches with n cells in each branch.



$$\text{Net e.m.f} = \text{e.m.f of each branch} \\ = nE$$

$$\text{Total resistance of the circuit} = R + \gamma_p$$

where γ_p = Equivalent resistance of all the cells

$$\therefore \frac{1}{\gamma_p} = \frac{1}{n\gamma} + \frac{1}{n\gamma} + \dots \text{upto } m \text{ terms}$$

$$\frac{1}{\gamma_p} = \frac{m}{n\gamma}$$

$$\therefore \gamma_p = \frac{n\gamma}{m}$$

$$\therefore \text{Current through the external} \\ \text{resistance} = \frac{\text{Net e.m.f}}{\text{Total resistance}}$$

$$I = \frac{n \sum_{R=1}^m m n \varepsilon}{m p_1 n \gamma} = \frac{N \varepsilon}{m p_1 n \gamma}$$

(5) Condition to have max^m current
Out of a given number of cells

Suppose $N = 24 = mn$

Possible Combinations

$$m = 2, n = 12$$

$$m = 12, n = 2$$

$$m = 3, n = 8$$

$$m = 8, n = 3$$

$$m = 4, n = 6$$

$$m = 6, n = 4$$

To know the right combination to have max current, we see from the expression

$$I = \frac{N \varepsilon}{m p_1 n \gamma} \text{ i.e. that the}$$

numerator is a constant and the denominator can be changed if the d.r be made a min^m then I will be max^m.

$$\begin{aligned} m p_1 n \gamma &= (\sqrt{m \gamma})^2 + (\sqrt{n \gamma})^2 \\ &= (\sqrt{m \gamma} - \sqrt{n \gamma})^2 + 2\sqrt{m \gamma} \cdot \sqrt{n \gamma} \end{aligned}$$

$$= (\sqrt{M} - \sqrt{n})^2 + 2\sqrt{NMR}$$

The second term is a constant quantity and can be made zero only when the squared quantity becomes $0 \cdot (N\gamma)$.

$$\therefore \sqrt{M} = \sqrt{n}$$

$$\Rightarrow M = n$$

$$\Rightarrow R = \frac{n\gamma}{m} = \gamma_p$$

Thus the current will be maximum when the external resistance will be equal to the effective internal resistance of all the small cells put together.

Problem :-

1. 24 cells, each of r.m.v 1.4 volt and internal resistance 2Ω are to be connected so as to produce maximum current through a wire of resistance 12Ω .

(i) How you will connect them?

(ii) Find the strength of the current through each cell.

~~(c) Find the P.d across the external resistance.~~

Ans:

Let there be m branches with n cells in each branch.

$$\therefore mn = 24 \quad (i)$$

The condition is for max current out of a given number of cells,

$$R = \frac{n\gamma}{m}$$

$$\Rightarrow 12 = \frac{n^2}{m} \quad (ii)$$

$$\Rightarrow \frac{n}{m} = 6$$

Multiplying (i) and (ii),

$$n^2 = 144$$

$$\Rightarrow n = 12$$

$$m = \frac{24}{12} = 2$$

i.e. there will be two branches with 12 cells in each branch

$$(ii) I = \frac{NE}{m\gamma + ns} = \frac{24 \cdot (1.4)}{2 \cdot 12 + 2 \cdot 2} = \frac{24 \times 1.4}{28} = 0.7 \text{ Amps.}$$

Current flowing from each branch

$$= \frac{0.2}{2} = 0.35 \text{ Amp.}$$

= Current through

cell

(ii)

(i)

$$V = RI = 12 \times 0.3 = 8.4 \text{ vule}$$

657,


Cell - 38

$\rightarrow 1.18v, 2.066 \text{ relt}$

$$\textcircled{7} \rightarrow 19.12 - 114.3 \text{ vult.}$$

Answers to Problems

6.

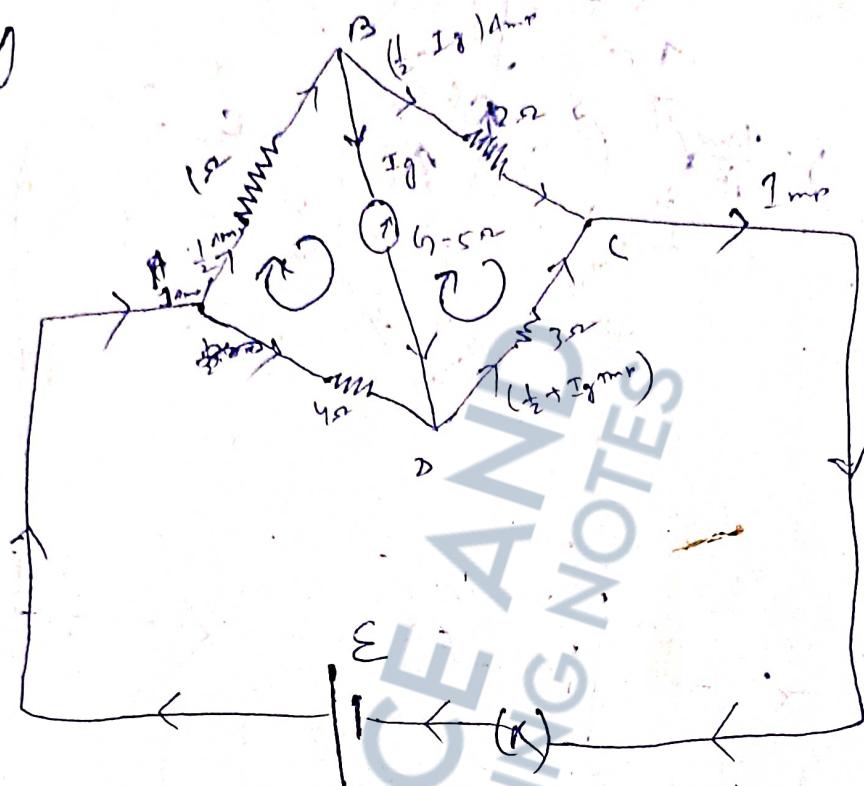

At A, I_Amp current divides into $\frac{1}{2}Amp$ and $\frac{1}{2}Amp$.

Applying Kirchhoff's law, for the loop ABDA,

we get

$$\frac{1}{2} \cdot 1 + I_g \cdot 5 - \frac{1}{2} \cdot 4 = 0$$

6. Applying Kirchhoff's first law at the junction point A, we get

$$I_1 + I_2 = 1 \text{ Amp} \quad (\text{i})$$


Applying Kirchhoff's second law for the loop ABDA, we get

$$I_1 + I_g \cdot 5 - I_2 \cdot 4 = 0 \quad (\text{ii})$$

For the loop BCDA,

$$(I_1 - I_g) \cdot 2 + (I_2 + I_g) \cdot 3 - I_g \cdot 5 = 0 \quad (\text{iii})$$

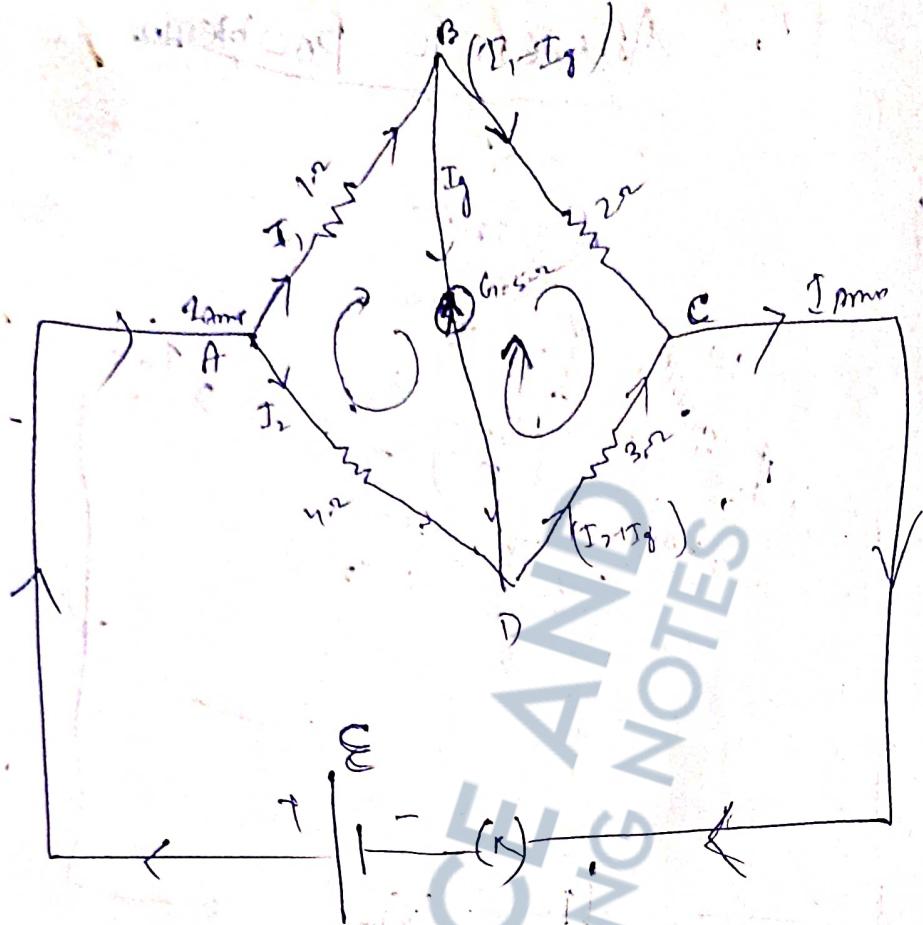Now applying KVL, $I_2 \cdot 4 + (I_2 + I_g)^2 + \varepsilon = I$ — (iv)



From

Eqn (ii)

$$I_1 - 4I_2 = -I_g$$

$$2) I_g = \frac{4I_2 - I_1}{5}$$

From Eqn (III)

$$2I_1 - 2I_g - 3I_2 - 3I_g - 5I_g = 0$$

$$2) 2I_1 - 3I_2 - 10I_g = 0$$

$$\Rightarrow 2I_1 - 3I_2 - 10 \cdot \left(\frac{4I_2 - I_1}{5} \right) = 0$$

$$2) 2I_1 - 3I_2 - 8I_2 + 2I_1 = 0$$

$$\Rightarrow 4I_1 - 11I_2 = 0 \quad \text{---(i)}$$

$$\Rightarrow 4(1-I_2) - 11I_2 = 0$$

$$\Rightarrow 4 - 4I_2 - 11I_2 = 0$$


$$\Rightarrow 4 = 15I_2$$

$$\Rightarrow I_2 = \frac{4}{15}$$

$$I_1 = 1 - \frac{4}{15} = \frac{11}{15}$$

$$I_g = \frac{4I_2 - I_1}{15} = \frac{4\left(\frac{4}{15}\right) - \frac{11}{15}}{15}$$
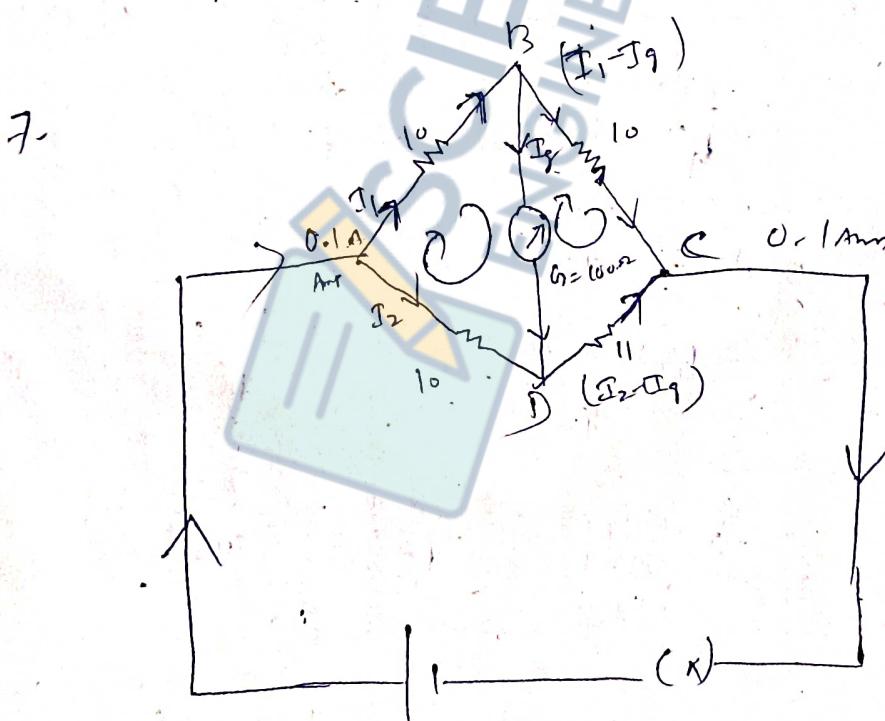
$$= \frac{(16 - 11)}{15 \times 15} = \frac{5}{15 \times 15} = \frac{1}{15} \text{ Amp.}$$



$$I_1 + I_2 = 0.1 \quad \text{---(i)}$$

$$I_1(10) + I_g \cdot 10 - 10I_2 = 0 \quad \text{---(ii)}$$

$$(I_1 - I_2)10 + (I_2 + I_1)10 - I_g \cdot 10 = 0 \quad \text{---(iii)}$$

$$I_g = \frac{10I_2 - 10I_1}{100} = \frac{I_2 - I_1}{10}$$

From eqn (iv)

$$10I_1 - 10I_g - 11I_2 - 11I_g = -10I_g \text{ or } 20$$

$$\Rightarrow 10I_1 - 11I_2 - 12I_g = 0$$

$$\Rightarrow 10I_1 - 11I_2 - 12\left(\frac{I_2 - I_1}{10}\right) = 0$$

$$\Rightarrow 10I_1 - 11I_2 - 12I_2 + 12I_1 = 0$$

$$\Rightarrow 22I_1 - 23I_2 = 0$$

$$\Rightarrow 22(0.1 - I_2) - 23I_2 = 0$$

$$\Rightarrow 2.2 - 22I_2 - 23I_2 = 0$$

$$\Rightarrow I_2 = \frac{2.2}{45.2}$$


$$\begin{aligned} I_1 &= 0.1 - \frac{2.2}{45.2} \\ &= \frac{45.2 - 2.2}{45.2} = \frac{43}{45.2} \end{aligned}$$

$$I_g = \frac{I_2 - I_1}{10} = \frac{\frac{2.2}{45.2} - \frac{43}{45.2}}{10}$$

$$= \frac{43 - 2.2}{45.2 \times 10} \text{ Amm.}$$

We have assumed that current

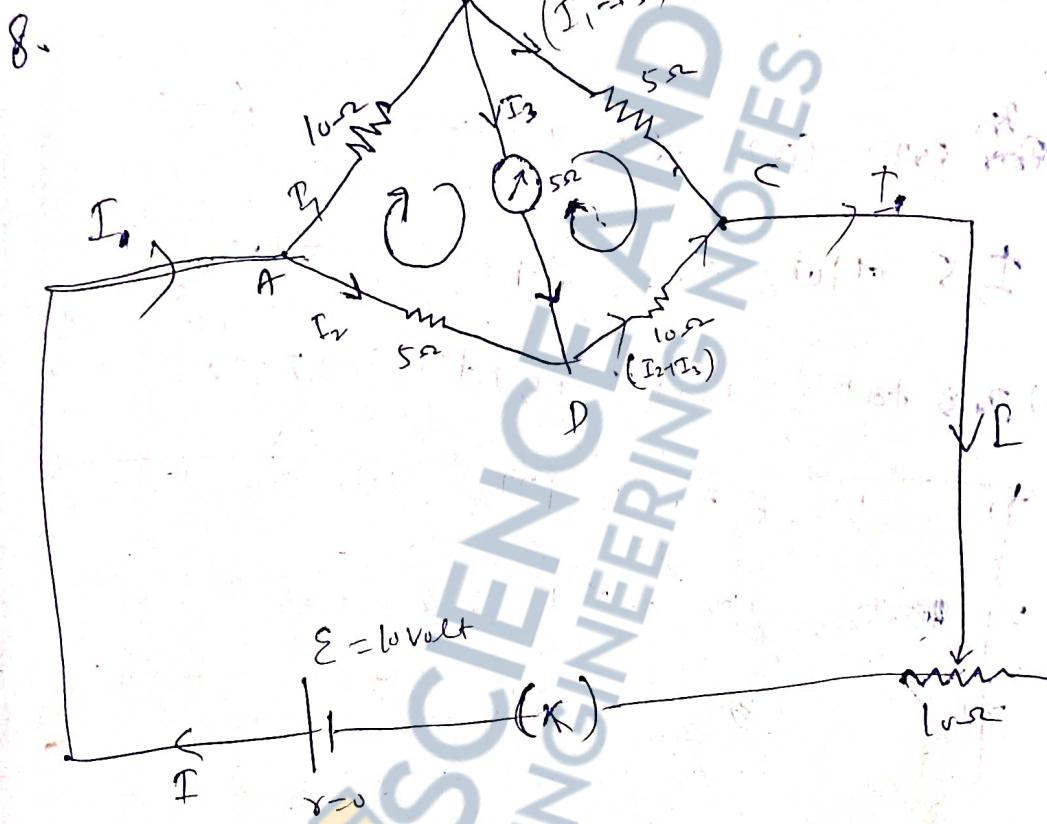down from B to D, but the
 -ve sign shows that current flows
 from D to B, i.e. the galvanometer
 current is $\frac{1}{4520}$ Amp



$$I = I_1 + I_2 \quad (i)$$

$$10I_1 + I_3 5 - I_2 5 = 0 \quad (ii)$$

$$(I_1 - I_3) 5 - (I_2 + I_3) 10 - I_3 5 = 0 \quad (iii)$$

$$I_2 5 + (I_2 + I_3) 10 + I_0 10 = 10 \quad (iv)$$

$$\text{From (ii), } 10I_1 - 5I_2 = -I_3 \Rightarrow I_3 = -2I_1 + I_2$$

$$\text{From (iii) } 5I_1 - 5I_3 - 10I_2 - 10I_3 - I_3 5 = 0$$

$$\Rightarrow 5I_1 - 10I_2 - 20I_3 = 0 \Rightarrow I_1 - 2I_2 - 4I_3 = 0$$

$$7I_1 - 2I_2 - 8I(-2I_1 + I_2) = 0$$

$$7I_1 - 2I_2 + 8I_1 - 8I_2 = 0$$

$$\Rightarrow 9I_1 - 6I_2 = 0$$

$$\Rightarrow 3I_1 - 2I_2 = 0$$

$$3I_1 = 2I_2$$

$$\Rightarrow I_2 - 5I_1 = 0 \quad (\text{V})$$

From eqn. (IV), putting the value in R form. eqn (V)

$$15I_2 - 10I_2 + 10I_3 + 10I = 10$$

$$\Rightarrow 15I_2 + 10(-2I_1 + I_2) + 10(I_1 + I_2) = 10$$

$$\Rightarrow 15I_2 - 20I_1 + 10I_2 - 10I_1 - 10I_2 = 10$$

$$\Rightarrow 10I_2 - 5I_2 + 10I_1 = 10$$

$$\Rightarrow -2I_2 + 2I_1 = 2 \quad (\text{VI}')$$

$$\Rightarrow -5I_1 + 2I_1 = 2$$

$$\Rightarrow -3I_1 = 2$$

$$\Rightarrow I_1 = -\frac{2}{3}$$

$$\Rightarrow 15I_2 - 20I_1 + 10I_2 + 10I_1 + 10I_2 = 10$$

$$\Rightarrow 35I_2 - 10I_1 = 10$$

$$\Rightarrow 35\left(\frac{2}{3}I_1\right) - 10I_1 = 10$$

$$\Rightarrow \frac{105I_1 - 20I_1}{2} = 10$$

$$\Rightarrow I_1 = \frac{20}{85} = \frac{4}{17} \text{ Amper}$$

$$I_2 = \frac{3}{2} I_1 = \frac{3}{2} \times \frac{4}{17} = \frac{6}{17}$$

$$I_3 = I_2 - 2 I_1 \\ = \frac{6}{17} - \frac{2}{17} = \frac{-2}{17} \text{ Amper}$$

$$I = I_1 + I_2 = \frac{10}{17} \text{ Amper}$$

$$\text{Along AB} = I_1 = \frac{4}{17}$$

$$\text{Along BC} = I_1 - I_3 = \frac{4}{17} + \frac{2}{17} = \frac{6}{17}$$

$$\text{Along CD} = I_2 + I_3 = \frac{6}{17} + \frac{2}{17} = \frac{8}{17}$$

$$\text{Along AD} = I_2 = \frac{6}{17}$$

$$\text{Along RD} = I_3 = \frac{-2}{17}$$

$$\text{Max current } I = \frac{10}{17} \text{ Amper}$$

Chemical effect

If we know form combined gas law

$$\frac{P_1 V_1}{T_1} = \frac{P_2 V_2}{T_2}$$

$$\Rightarrow \frac{76 \times V_1}{273} = \frac{68 \times 83.7}{298}$$

$$\Rightarrow V_1 = \frac{39^{17} \times 273 \times 68 \times 83.7}{76 \times 29.8} \times 10^{-5}$$

$$= \cancel{273} \times 68 \times 83.7 \times 10^{-5} \rightarrow 68.606 \text{ ml}$$

$$I = 0.5 \text{ Amper}$$

$$t = 20 \times 60 = 1200 \text{ sec.}$$

$$\text{Mass or wt.} = 68.606 \text{ ml} \times \text{density}$$

$$\text{density} = \frac{0.898 \text{ kg/m}}{\text{lt}} = \frac{0.898 \text{ m}}{1000 \text{ ml}}$$

$$= 0.000898$$

$$= 68.606 \times 0.000898$$

$$= 6.1608188 \times 10^{-3}$$

$$\Rightarrow Z \cdot (0.5) \cdot (1200 \times 0) = " "$$

$$\left. \begin{aligned} \frac{Z_{Cu}}{Z_2} &= \frac{E_1}{E_2} \\ &: \end{aligned} \right\} \Rightarrow Z = \frac{6.1608188 \times 10^{-3}}{600} = 6.102 \times 10^{-5}$$

$$\Rightarrow \frac{Z_{Cu}}{1.02 \times 10^{-5}} = \frac{31.78}{1.008}$$

$$\Rightarrow Z_{Cu} = \frac{1.02 \times 31.78 \times 10^{-5}}{1.008}$$

$$= 32.1583 \times 10^{-5}$$

$$= 0.00321583 \approx 0.00321 \text{ g/cm}^3$$

6. 31.77 gpm circ is deposited by $96,500 \text{ cu. ft.}$

\times " " " $\frac{96,500}{31.77} \text{ cu. ft.}$

" " " " " $\frac{96,500}{31.77} (0-3) \text{ cu. ft.}$

$$Q = Z I +$$

$$\Rightarrow \frac{96500 \times 3}{317.7} = 0.00033 \cdot I \times (30 \times 60)$$

$$\Rightarrow I =$$

$$= \frac{96500 \times 3}{317.7 \times 1800} \times 1$$

~~$$= \frac{96500 \times 3}{317.7 \times 1800} \times 1$$

$$= \frac{96500 \times 3}{317.7 \times 1800} \times 1$$

$$= \frac{15300 \times 10^3}{317.7 \times 3600} \times 1$$

$$= 0.0506 \text{ Amperes}$$~~

✓ $m_2 = Z \cdot I +$

$$\Rightarrow 0.3 = 0.00033 \cdot I \times (30 \times 60)$$

$$\Rightarrow I = \frac{0.3 \times 10^3 \times 10^2}{33 + 18 \times 10^2}$$

$$= \frac{300}{519}$$

$$= 0.585 \text{ Amperes}$$

7. Let R be the resistance of the circuit

$$T_1 = \frac{\epsilon}{R} = 10 \text{ K tan } 45^\circ$$

when 5Ω is connected

$$T_2 = \frac{\epsilon}{5+R} = 10 \text{ K tan } 30^\circ$$

$$\frac{I_1}{I_2} = \frac{R + r}{R} = \frac{R + R}{R} = \frac{2R}{R} = 2$$

$$\Rightarrow \frac{R + r}{R} = \frac{1}{\frac{1}{\sqrt{3}}} = \sqrt{3}$$

$$\Rightarrow R + r = \sqrt{3}R$$

$$\Rightarrow R(\sqrt{3}-1) = r$$

$$\Rightarrow R = \frac{r}{\sqrt{3}-1}$$

$$\Rightarrow R = \frac{5}{\sqrt{3}-1} = \frac{5(\sqrt{3}+1)}{3-1} = \frac{5(\sqrt{3}+1)}{2}$$

Gmank

Q8



Let the current flow in the Circuit I.


They are in helping series means the end in connected to -ve and -ve end is connected to the end of battery.

$$\text{Current } I = \frac{E}{R + (R_1 + R_2)} = \frac{2 + 4}{2 + 2 + 2} = \frac{6}{6} = 1 \text{ Amp}$$

$$= \frac{6}{2 + 2 + 2} = \frac{6}{6} = 1 \text{ Amp}$$

When they are connected in helping series potential drop across 2V battery I_s
 $= 2 \times 1 = 2$.

Terminal Potential $- 2 - 1^2 = 1$ volt

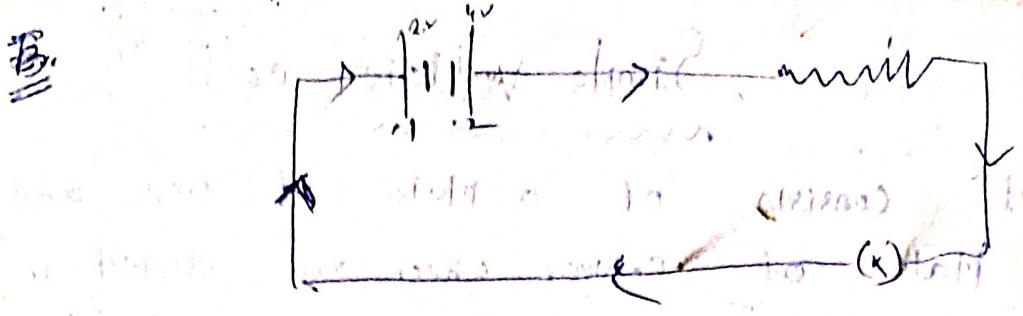

In the opposing series, the current flow by 2V battery.

by the 4V battery is opposed by 2V battery.

$$\text{Net E.m.f} = (4 - 2) = 2 \text{ Volts}$$

$$I = \frac{\Sigma}{R_{\text{tot}}} = \frac{2}{2 + 1 + 3} = \frac{2}{6} = 0.6666 \text{ Amp}$$

$$\text{Potential drop} = I \times r = (0.6666) \times (1) = 0.6666$$

$$\begin{aligned} \text{Terminal Potential across 2V battery} &= \Sigma + I \times r \\ &= 2 + 0.6666 \\ &= 2.6666 \text{ Volts} \end{aligned}$$

$$7. \quad r = 0.5 \Omega$$

$$I = 5 \text{ Ams.}$$

$$\Sigma = 12$$

$$\Sigma = I(r_{\text{tot}}) = 5(R + 0.5) \quad \text{Helping Series}$$

$$\Rightarrow \frac{98}{12} = 5R + 2.5$$

$$\Rightarrow 5R = 98 - 2.5 = 95.5$$

$$\Rightarrow R = \frac{95.5}{5} = 19.1 \Omega$$

$$V = \frac{\Sigma}{2} - Ir_2$$

$$= 2 - 2 \times 0.1$$

$$= 1.8 \text{ Volt}$$

Opposing Series

$$\begin{aligned} \text{Terminal potential} &= V + Ir \\ &= 12 + (5 \times 0.5) \\ &= 14.5 \text{ Volt} \end{aligned}$$

I' is -ve
for smaller battery

$$\begin{aligned} V &= \frac{\Sigma}{2} + Ir_2 \\ &= 12 + 5 \times 0.5 \\ &= 14.5 = 2 + \frac{2}{3} \times 0.1 \\ &= 2.066 \text{ Volt} \end{aligned}$$


Simple Voltaic cell

It

consists of a plate of Zinc and a plate of Copper which are dipped in a dilute H_2SO_4 such that $\frac{3}{4}$ (nearly) of the plates are immersed.

At the beginning, H_2SO_4 molecule breaks up into $2H^+$ ion and SO_4^{2-} ion.

The ionic reaction is

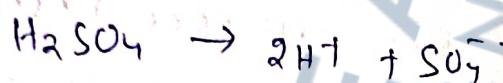

Copper has the affinity towards positive ions and Zinc has the affinity towards negative ions.

Hence the +ve ions move towards the Copper plate and become H_2 gas.



This process continues till the Copper plate acquires a voltage of 0.46 Volts.

Any further movement of $2H^+$ ion towards it is not possible because of strong repulsion.

The -ve ions move towards the Zinc plate and combine with Zinc atoms forming $ZnSO_4$ and the Zinc plate gradually becomes -vely charged. This process will continue till the Zinc plate acquires a potential of -0.62 Volts.


Thus, the potential difference between Cu and Zn plates

$$= 0.46 - (-0.62)$$

$$= 1.08 \text{ volts}$$

If the terminals of the Cu and Zn plate be connected by means of a conducting wire, then some of the -ve charges from the Zn plate will flow towards the Cu plate and get neutralized. Then the Zn plate and the Cu plate receive more ions.

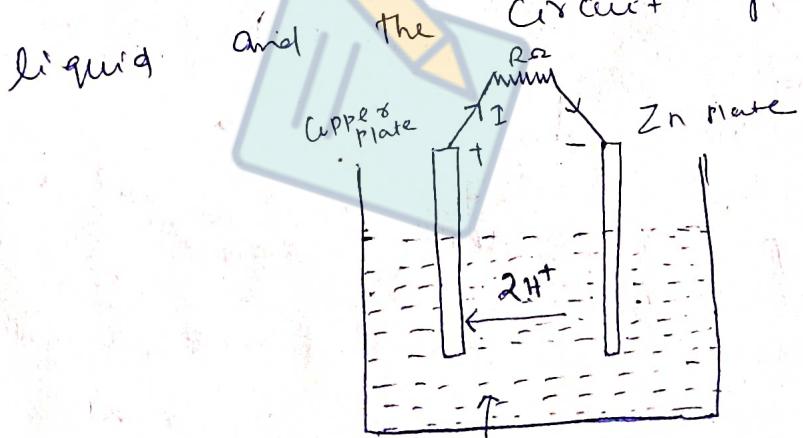The electrons will flow from the Cu plate through the current direction Zn plate towards the outer connecting wire. Hence plate towards the in from the cell. This current also proceeds inside the liquid and the circuit gets completed.



Dilute H_2SO_4 Soln


Defects of a simple voltaic cell:

A voltaic cell has two common defects

1. Local action, 2. Polarisation

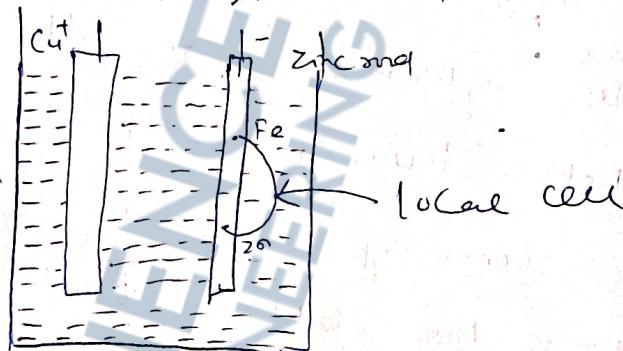1. Local action

The commercial Zinc contains many impurities like Carbon, Arsenic, lead and iron. These impurities are electroactive with respect to Zinc. As a result, small cells are formed between Zinc and impurity atoms via the solution as shown in the diagram.



Then smaller currents are produced and the Zinc rod gets heated. Thus current can't be utilised for any useful purpose.

Remedy (Simple)

The Zinc plate should be amalgamated. When Zinc plate is amalgamated with mercury, the impurity atoms remains inside and the pure atoms of Zinc comes outside. Hence the acid cannot come

In contact with impurity atoms.



Thus, the reaction is possible only between Cu and Zn through the soln.

2. Polarisation :

Due to formation of a layer of hydrogen bubbles, the current through the cells falls and finally it may stop altogether. This is called Polarisation.

Remedy

1. Mechanical method :

The positive plate (Cu), may be made rough and constantly shaken or brushed to remove hydrogen bubbles. But this method is inefficient.

2. Chemical method :

Here the hydrogen is oxidised into water by oxidising agents like MnO_2 , as in the Leclanche cell and $K_2Cr_2O_7$ as in the bichromate cell.




3. Electro-Chemical method :

In this method, hydrogen is electrochemically

Substituted by some less trouble some element.

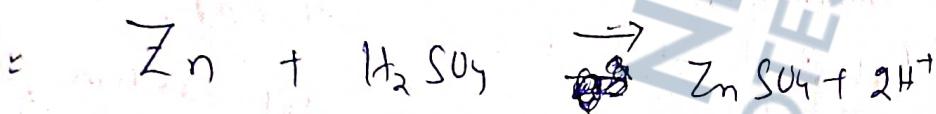For example, in a Daniell Cell, we use CuSO_4 solution as electrolyte and hydrogen is substituted by Copper which does not produce any back emf.



Relation between emf and potential difference

Electromotive force (emf) is not a force and is defined as the amount of work done to move 1 coul of charge throughout the circuit including the cell.

$$E = \Delta w \text{ in the outer circuit} + \Delta w \text{ in the inner circuit}$$

$$= q \cdot \Delta V \text{ in the outer circuit} + q \cdot \Delta V \text{ in the inner circuit}$$

$$= 1 \text{ coul. RI volt} + 1 \text{ coul. RI volt}$$

where γ = internal resistance
of the cell which depends
on

1. Separation of plates in the cell.
2. ~~connection~~ concentration of the salt.
3. Temperature
4. Nature of liquid.

Thus $E = RI + \gamma I$

$$E = V + \gamma I$$

where V is called terminal potential difference (T.P.D)

γI is called lost volt. Because
this much of voltage is not available
for useful work.

Thus $E = I(\gamma + R)$




$$\text{or } I = \frac{E}{\gamma + R}$$

ie Current = Net emf
Total resistance

The Dry Cell:

These cells are the modified form of Leclanche's cell made portable by dispensing with liquids. The -ve plate (Zn) is a hollow cylinder of Zn which forms the wall and bottom of the cell. The +ve plate is a carbon rod (C) placed in the centre of the cylinder. The carbon rod is fitted with a brass cap (B), which forms the terminal of the +ve pole. A paste of NH_4Cl , MnO_2 , C (Coke or graphite) and a little water is used in between the carbon rod and Zinc cylinder. A paper lining ($P.L$) separates the paste from the wall of the cylinder and NH_4Cl acts through this. The carbon rod is insulated from the bottom of the cylinder by means of a far paper washer ($T.P.W$). The top of the cell is filled up.

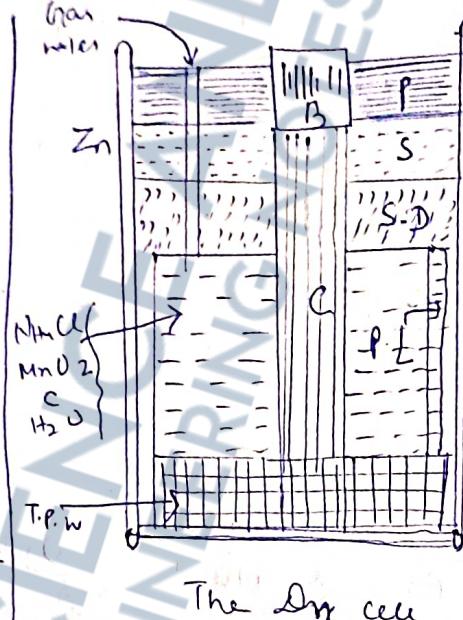

The Dry cell

with a layer of sawdust (S.O), followed by a layer of sand (S), then by a layer of pitch or wax (P) to prevent loss of water by evaporation and short-circuiting of the poles. There is a pinhole in the pitch, through which the gases escape. The ZnCl₄ formed by the action of Zn on NH₄Cl absorbs the NH₃ gas. The coke or graphite reduces the internal resistance. The e.m.f.

of the cell is about 1.5 volts. On continued use it may polarise, but recovers its e.m.f. if allowed to remain on open circuit for a while.


The dry cell is indispensable for electric touch, portable testing sets and for high tension duty of radio sets.

The Leclanché's Cell:


This cell consists of an amalgamated Zinc rod (Z) immersed in a strong soln of NH₄Cl contained in an outer glass vessel. In this vessel a porous pot is placed with a granular carbon rod C.

Out of the centre surrounded by a mixture of broken carbon and powdered powdered manganese dioxide (MnO_2)

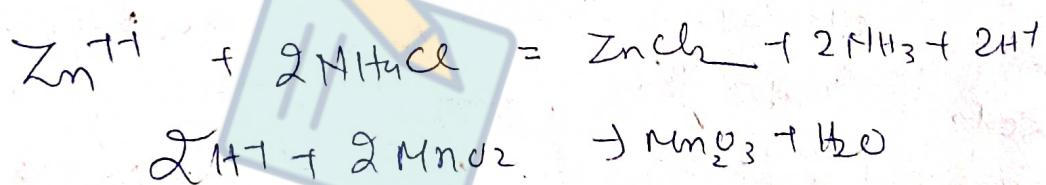This Zinc rod acts as the -ve plate, Carbon rod as the +ve plate, Hence as exciting liquid any MnO_2 as depolariser. The Charcoal powder is mixed up to make the depolariser an electrical conductor. By the action of Zinc on HgCl_2 , NH_3 is liberated which escapes through the mixture while the hydrogen ion liberated is oxidised by the MnO_2 into H_2O according to the following chemical reaction.



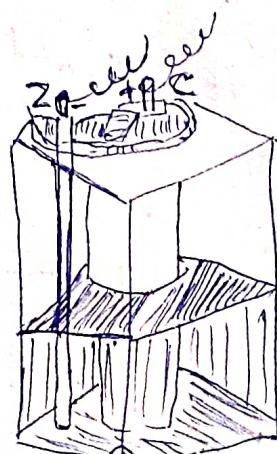Here MnO_2 is the oxidising agent, but as it is solid, its action is slow, so the cell acts for some time.



Leclanche cell

time. A polarization sets in, and the current falls off. This is an obvious disadvantage with thick cell but if

the cell is given rest for some time, it regains its strength. So the cell is suitable for intermittent work.

Q. E.M.F. is about 1.5 volt.
ball etc. Cell last for a very long time.

This cell

1) Find the resistance of the following

~~ladder made out of 1Ω resistances~~

If a 12 Volt battery be connected between A and B ; Find the current of the

internal resistance

battery is 0.5Ω .

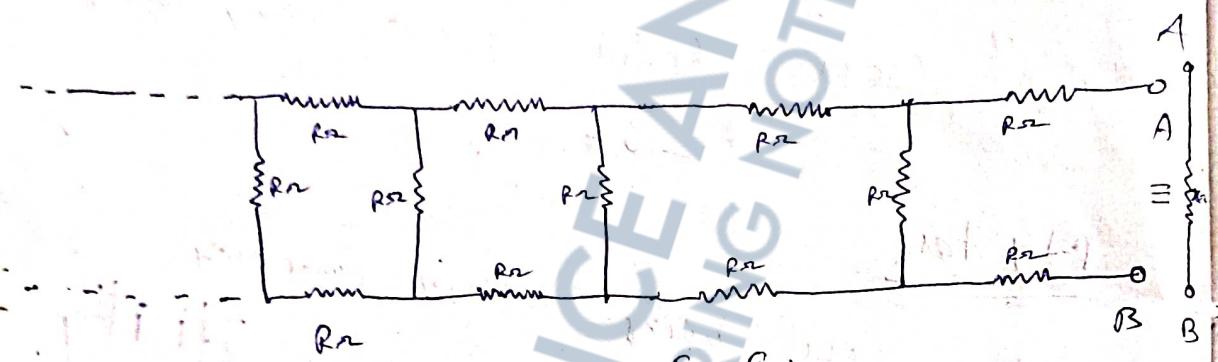


Fig (I)

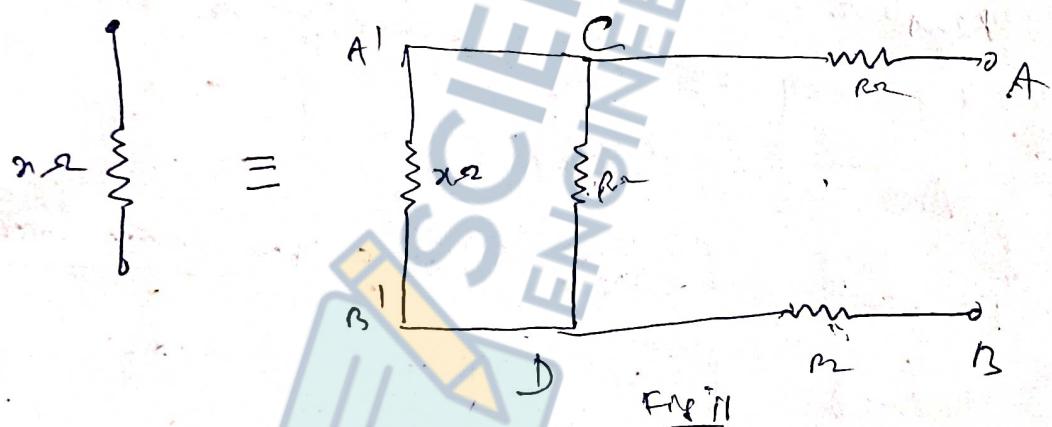


Fig (II)

Let R_p be the equivalent resistance between the points C and D.

Or fig (i)

$$\frac{1}{R_p} = \frac{1}{x} + \frac{1}{R} = \frac{R+x}{xR} = \frac{R}{xR}$$

$$\Rightarrow R_p = \frac{xR}{R+x}$$

$$\therefore R_{AB} = R_{BD} + R_{PA} + R_{CA}$$

$$= R + \frac{\alpha R}{R+x} + R$$

From fig (ii), we see that

$$R_{AB} = x$$

$$\Rightarrow R + \frac{\alpha R}{R+x} + R = x$$

$$\Rightarrow 2R + \frac{\alpha R}{R+x} = x$$

$$\Rightarrow \frac{2R^2 + 2Rx + Rx}{R+x} = x$$

$$\Rightarrow 2R^2 + 3Rx = xR + x^2$$

$$\Rightarrow x^2 - 2Rx - 2R^2 = 0$$

$$\Rightarrow x = \frac{2R \pm \sqrt{4R^2 - 4 \cdot 1 \cdot (-2R^2)}}{2 \cdot 1}$$

$$= \frac{2R \pm 2\sqrt{3}R}{2}$$

$$= (1 \pm \sqrt{3})R$$

Since resistance is always +ve, we
use +ve value of resistance can not accepted.

$$\therefore x = (1 + \sqrt{3})R = 2.732R$$

~~Ans~~ Here $R = 1\Omega$

$$X_r = 2.372 \Omega$$


$$\Sigma = V_1 I_x$$

$$\text{Hence } = E_R + I_x R = I (R + r)$$

$$12 = I \left(\frac{2.372}{2.372 + 1.5} \right)$$

$$\therefore I = \frac{12}{3.232} = 3.7128 \text{ Amp.}$$

33.

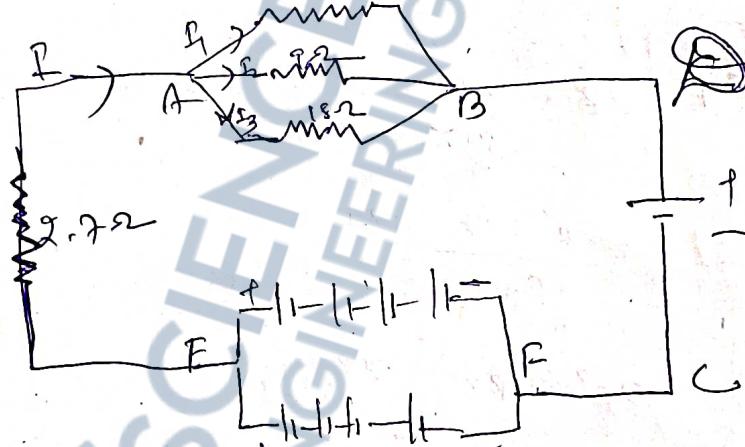

Solⁿ: Let the equivalent resistance

between A and B be $\delta_P \Omega$.

$$\therefore \frac{1}{\delta_P} = \frac{1}{6} + \frac{1}{9} + \frac{1}{18}$$

$$= \frac{3+2+1}{18}$$

$$= \frac{6}{18}$$

$$\delta_P = 3 \Omega$$

Let the equivalent resistance between
the points B and F be $X_P \Omega$

$$\therefore \frac{1}{R_P} = \frac{1}{4\Omega} + \frac{1}{4\Omega} = \frac{1}{2\Omega} = \frac{1}{2\Omega} = \frac{1}{2\Omega}$$

$$\therefore R_P = 2\Omega$$

$$= 2 \times (0.1) = 0.2\Omega$$

out of the circuit

\therefore Total resistance

$$= \cancel{R_P} + R_{CO}$$

$$= R_P + R_{CO} + R_{EF} + 2\Omega - 2\Omega$$

$$= 3 + 0.2 + (0.1) + (2) + 2\Omega$$

$$= 6\Omega$$

$$\rightarrow V_E - V_F = 4\varepsilon$$

$$\text{Net Emf} = 4\varepsilon - \varepsilon$$

$$= 3\varepsilon$$

$$= 3 \times 1.5$$

$$= 4.5$$

(r: C)

Cell

as connected in opposite sense)

$$\text{a), } I = \frac{\text{Net Emf}}{\text{Total resistance}} = \frac{4.5}{6\Omega} = \frac{4.5}{6}$$

$$= \frac{4.5}{6\Omega} = \frac{3}{4} = 0.75 \text{ Amp}$$

(Ans)

(b) To find the current along the q_2 resistor.

We can write

$$V_A - V_B = R_1 I_1 + R_2 I = R_3 I_3 = I \cdot R_P$$

$$7) R_2 I_2 = I P_P$$

$$7) (9 \times I_2) = \frac{3 \times 9}{4}$$

$$7) I_2 = \frac{1}{4} = .25 \text{ Amp.}$$

Heat produced in 15 minutes along the resistor

$$= \frac{I_2^2 \cdot R_2 \cdot t}{J} \quad \text{Cal}$$

$$= \frac{(1/4)^2 \cdot (9) \cdot (15 \times 60)}{4 \times 2} \quad \text{Cal}$$

$$= \frac{9 \times 15 \times 60 \times 15}{16 \times 4 \times 2} \quad \text{Cal}$$

$$= 120.53 \quad \text{Cal.}$$

(e) From fig we see that the current in -ve for the cell

$$V = \Sigma + IR$$

$$= 1.5 + \frac{0.75}{3} \cdot (0-1)$$

$$= 1.5 - 0.25$$

$$= 1.575 \text{ Volt}$$

(1) Electrical energy converted into
chemical energy in hour.

$$W_B = \epsilon B I t \quad 900$$

$$= (1.5) \times (\frac{3}{4}) \times \frac{(900)}{3600} \text{ Joule}$$

$$= \frac{1.5 \times 3 \times 900}{3600} \text{ watt hour}$$

$$= 1.125 \text{ watt hour}$$

Q8. The relation between e.m.f and T.P.D.

$$\epsilon = V + I \delta$$

For a point

X - W - coordinate

$$\therefore I = 0$$

$$\text{Hence } \epsilon = V = 1.1 \text{ volt}$$

For a point on the X - axis the
Y - coordinate in zero.

$$\therefore V = 0$$

$$\therefore \epsilon = 0 + I_{\max}$$

where I_{\max} = Max. value of current obtained

When there is no short circuit current.

From the graph we find

$$I_{\max} = 0.265 \text{ Amper}$$

$$\therefore 1.1 \text{ Volts} = \gamma \times (0.265 \text{ Amper})$$

$$\Rightarrow \gamma = \frac{1.1}{0.265} = 4.15 \Omega$$

Magnetic effect of electric current

Oersted was the first scientist to show that a conductor produces a magnetic field around it. Laplace gave a formula for the magnetic induction developed around the conductor.

He did not give the direction of magnetic field intensity. Thus, Laplace's formula is only quantitative.

Biot and Savart gave an expression

for the magnetic induction in vector form. Thus, magnitude and direction